

Assignment 5

Copyright reserved

Electricity and Electronics EBN 122

14 October 2021

Test Information

Maximum marks:	23	Full marks:	23
Due Date:	21 October 23:59	Open/Closed book:	Open
Total number of pages (this page included)		12	

Lecturers: Prof P. de Villiers, Prof P. Jacobs, Dr S. Smith**Assistant Lecturers:** L. Kokot, N.-J. Lord, M. Maritz, J. Thiselton, M. Trivedi**Important**

1. The examination regulations of the University of Pretoria apply.
2. Write your answers on the Excel spreadsheet found on the AMS system. The spreadsheet contains unique parameter values for each student. Therefore, you must download the Excel spreadsheet from your own AMS account. Follow the instructions on the AMS spreadsheet carefully.
3. Final answers must be written as real numbers and not as fractions. Use at least 5 significant figures to write numbers, including complex numbers. Use decimal points and NOT decimal commas.
4. Answers must include units where applicable. (Refer to the EECE Rules for Electronic Assessments of tests and examinations for guidelines on how to enter units. Also refer to the example list of units on the Excel spreadsheet.)
5. **By uploading your assessment, you declare the following:**

The University of Pretoria commits itself to produce academic work of integrity. I affirm that I am aware of and have read the Rules and Policies of the University, more specifically the Disciplinary Procedure and the Tests and Examinations Rules, which prohibit any unethical, dishonest or improper conduct during tests, examinations and/or any other forms of assessment.


I hereby declare that the work herewith is completely my own and that no parts have been copied in any way from current or previous students or other sources.

Online assessment submission rules and time-line

The following rules and time-line apply for all tests for EBN111/122 as illustrated by the figure below:

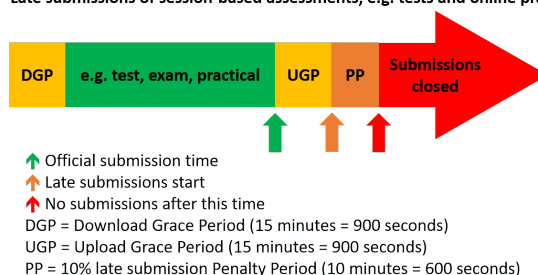1. The Download Grace Period (DGP) is a 15 minute period before the official start of the test for students to download all documents related to the test and read all the necessary instructions.
2. The start of the green section after the DGP indicates the official start of the test.
3. The upward green arrow at the end of the green section indicates the official submission deadline for the test.
4. Students must aim to submit their Excel spreadsheet with their answers on the AMS before the official submission deadline.
5. Students can request assistance via **e-mail** ebn2021.ams@gmail.com if they experience any technical issues with respect to uploading their Excel spreadsheets on the AMS.
6. An Upload Grace Period (UGP) of 15 minutes follows the official submission deadline. Students may submit their Excel spreadsheets with answers on the AMS during this period without incurring any penalties.
7. A Penalty Period (PP) of 10 minutes follows the UGP. If a student submits an Excel spreadsheet during this period, the student incurs a 10% penalty to their final test mark.
8. No late submissions are accepted after the PP.


Late submissions of session-based assessments, e.g. tests and online practicals






Additional guide for Complex numbers


The following examples illustrate how to appropriately enter complex numbers on the Excel Spreadsheet:


- **Correct:** $1-j2$ or $-3+j4$
 - This is the rectangular form of a complex number. This format is acceptable as a single number entry in the numeric field.
 - Capital J is however incorrect, and $1-2j$ is also not acceptable.
 - If a complex number has no real part, for example $0+j2$, write $0+j2$ as the final answer.
- **Correct:**
 - With angle in degrees: $12\angle 34\deg$;
 - With angle in radians: $12\angle 0.5934$
 - A complex number in its polar form is regarded as a single number entry with the angle in degrees or radians.
- **Incorrect:**
 - $1-i2$ (Use j instead of i)
 - $1 - j2$ (no spaces between characters)
 - $12 \angle 34$; $34 \deg$; (no spaces between characters)
 - $j10+1$ (Real part before the imaginary part for rectangular form.)
 - $-3+4j$ (should be $j4$ instead of $4j$)

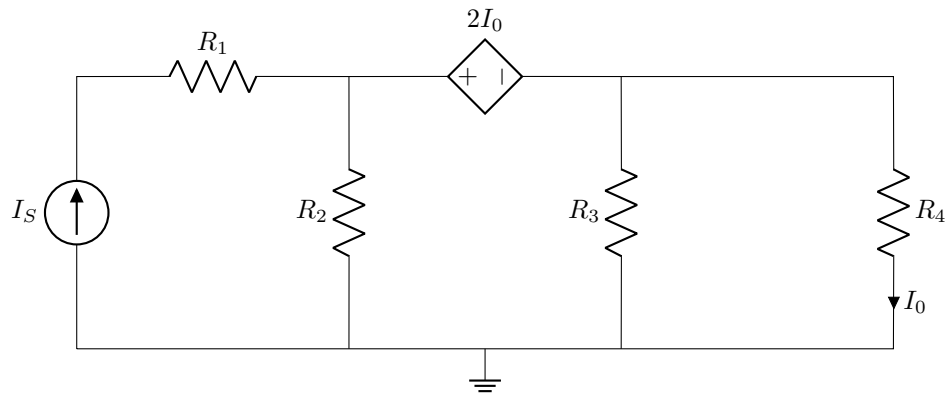
Section 1**Question 1 [2]**Given: R_1 , R_2 , R_3 , R_4 .**01** Use the principle of linearity to determine I_0/I_S . [2]

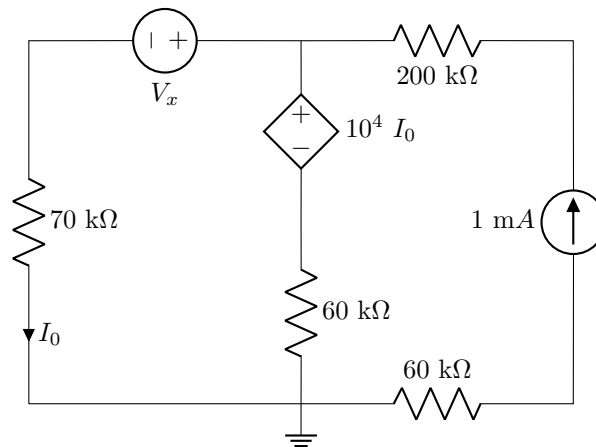
Question 2 [2]Given: V_x .**02**Find $I_0(V_x)$, the independent contribution of V_x to I_o [2]

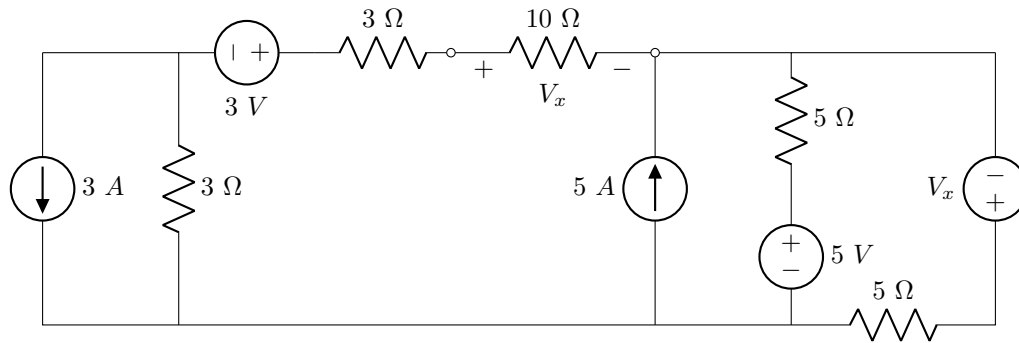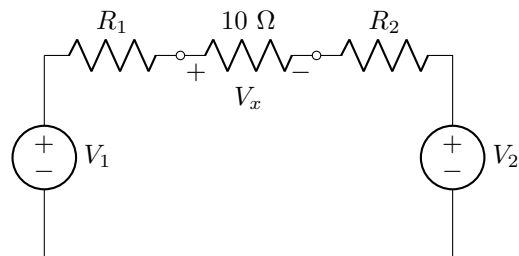
Question 3 [2]Given: V_x , V_1 , R_1 , R_2 .Use source transformation to obtain Circuit B so that it is equivalent to Circuit A. Determine V_2 in Circuit B.**Circuit A:****Circuit B:****03** | V_2 [2]

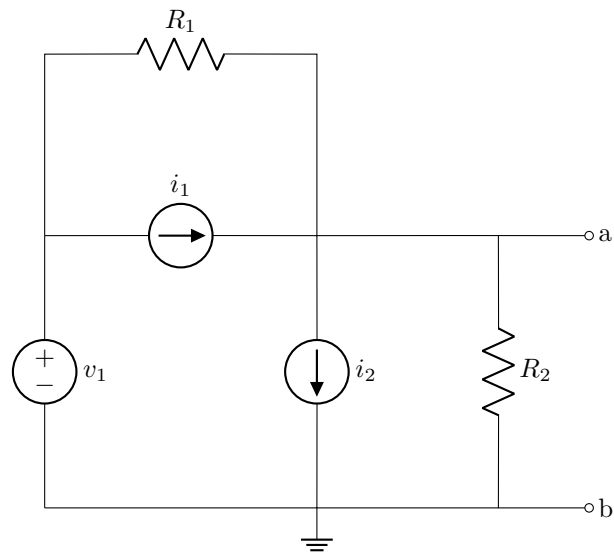Question 4 [2]Given: R_1 , R_2 , v_1 , i_1 , i_2 .**04** Find the Thevenin equivalent voltage V_{Th} with regards to terminals a - b . [2]

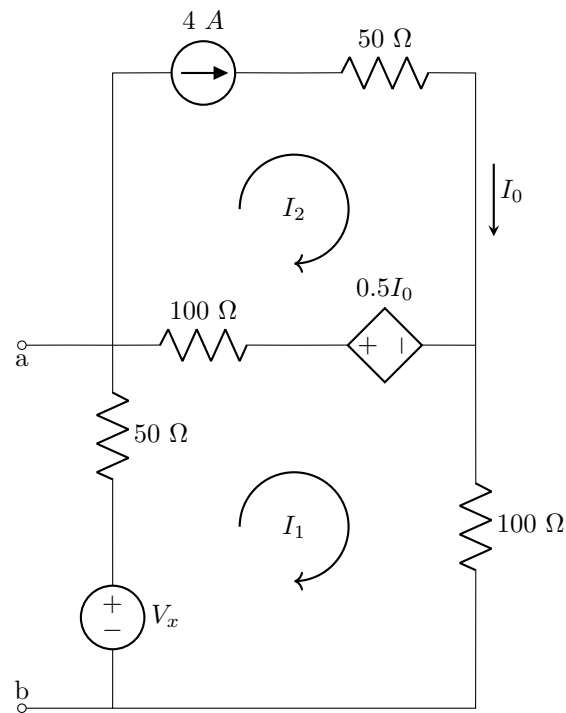
Question 5 [2]Given: V_x .**05** Find the Thevenin equivalent voltage V_{Th} between terminals a - b . [2]

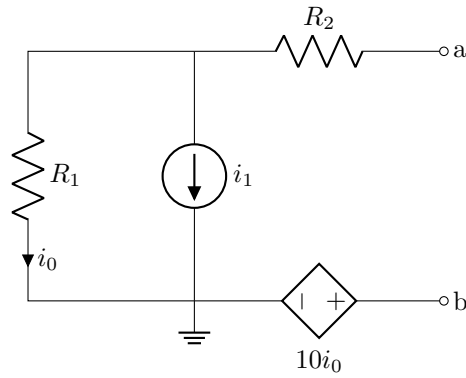
Questions 6 to 7 [4]Given: R_1 , R_2 , i_1 .**06** Determine the Norton equivalent current I_N . [2]**07** Determine the Norton equivalent resistance R_N . [2]

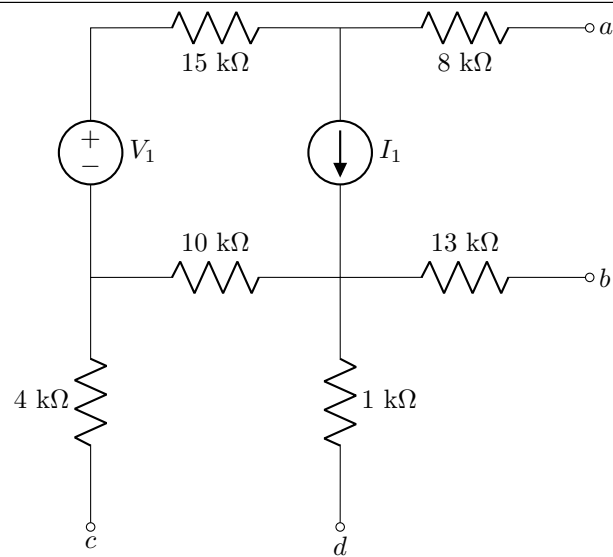Question 8 [2]Given: V_1 , I_1 .**08** Determine the Norton equivalent current I_N between terminals c - d . [2]

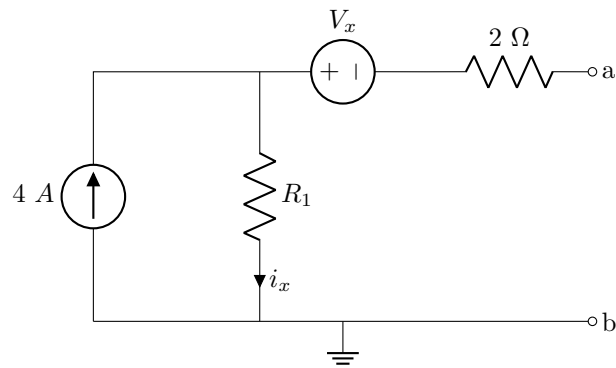Questions 9 to 11 [4]Given: R_1 , V_x .

09	Find the Thevenin equivalent voltage V_{Th} across terminals a - b . [2]
10	Find the Thevenin equivalent resistance R_{Th} across terminals a - b . [1]
11	Calculate the maximum power that can be transferred to a load resistor R_L that can be connected between terminals a - b . [1]

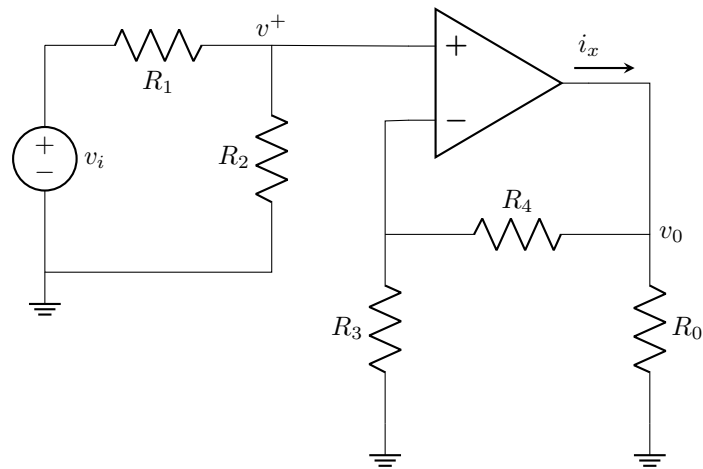Questions 12 to 13 [2]Given: R_3, R_4 .Given: R_0, v^+ **12** Find the current i_x . [1]Given: $R_1 = R_2$ **13** Calculate the closed-loop gain (v_0/v_i) of the circuit. [1]

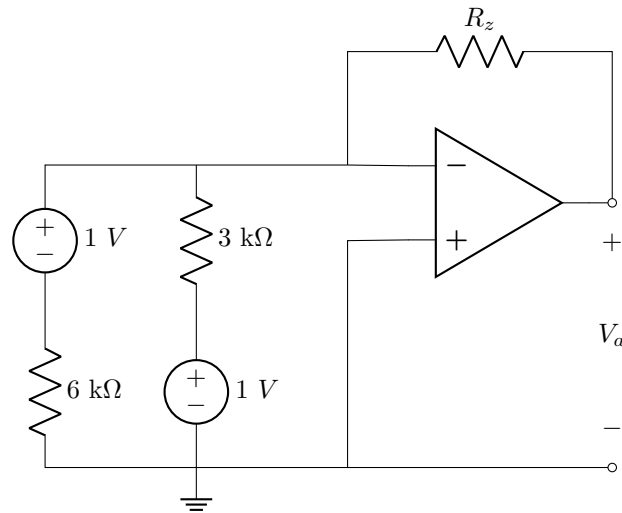Question 14 [1]Given: R_z .**14** Determine V_a . [1]**Total Section 1: [23]****Grand Total : [23]**