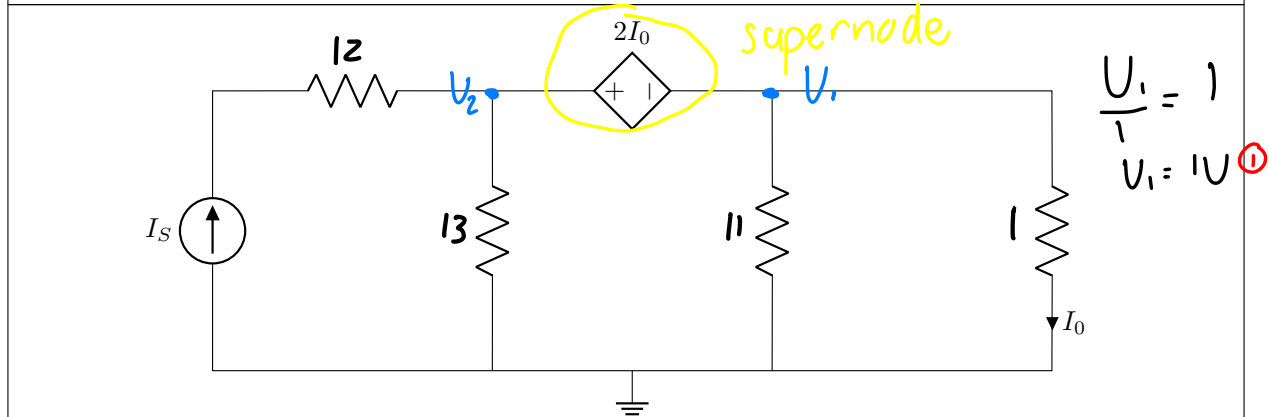


Section 1

Question 1 [2]

Given: R_1, R_2, R_3, R_4 .01 Use the principle of linearity to determine I_0/I_S . [2]Assume $I_0 = 1\text{A}$ Supernode: $V_2 - V_1 = 2I_0$

$$V_2 - V_1 = 2$$

$$\textcircled{1}: V_2 - 1 = 2$$

$$V_2 = 3\text{V}$$

$$\text{Nodal: } -I_S + \frac{V_2}{13} + \frac{V_1}{11} + \frac{V_1}{1} = 0$$


$$I_S = \frac{189}{143}\text{ A}$$

$$I_0/I_S = \frac{1}{\frac{189}{143}}$$

$$= \frac{143}{189}$$


$$= 0.75661$$

Question 2 [2]

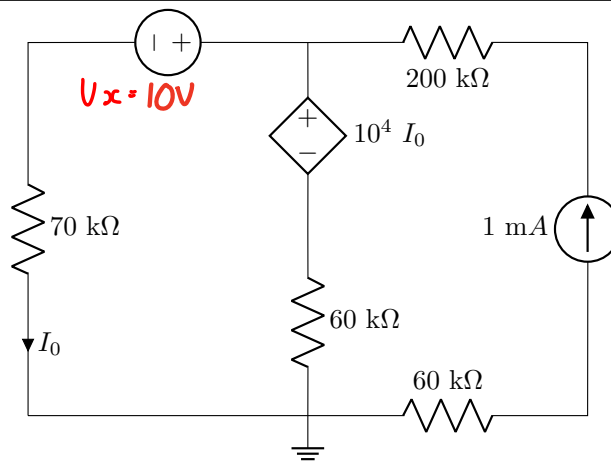Given: V_x .

Voltage: close
Current: remove

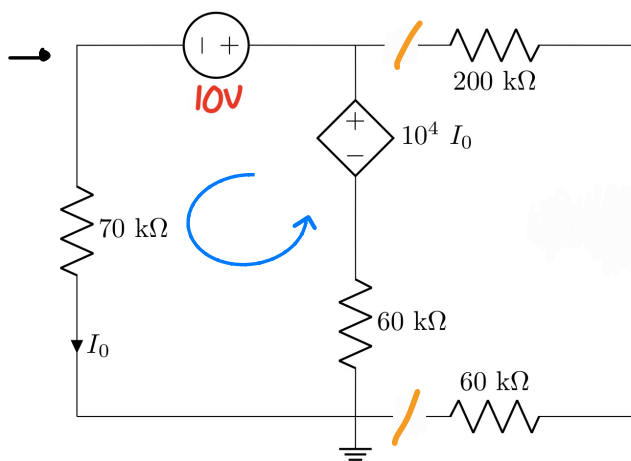02 Find $I_0(V_x)$, the independent contribution of V_x to I_o [2]




KVL: $-10^4 I_0 + 10 + 70 \times 10^3 I_0 + 60 \times 10^3 I_0 = 0$
 $120 \times 10^3 I_0 = -10$
 $I_0(V_x) = -83.33 \mu A$



Question 3 [2]

Given: V_x , V_1 , R_1 , R_2 .Use source transformation to obtain Circuit B so that it is equivalent to Circuit A. Determine V_2 in Circuit B.



Circuit A:

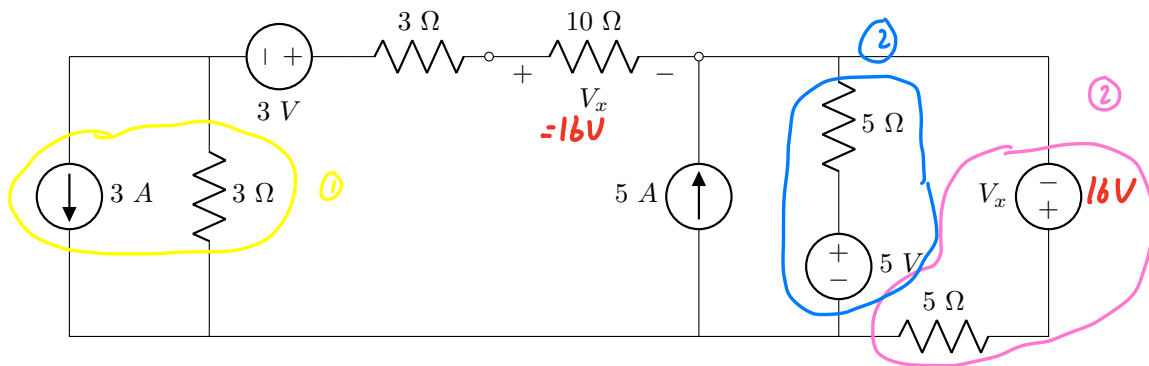

Circuit B:

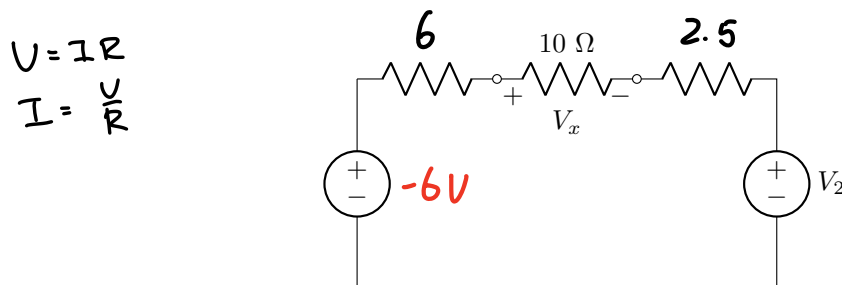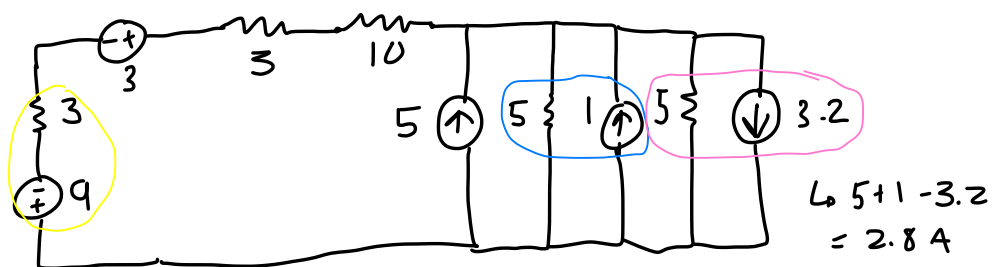03 V_2 [2]


$$I = 5 + 1 - 3.2 = 2.8 \text{ A}$$

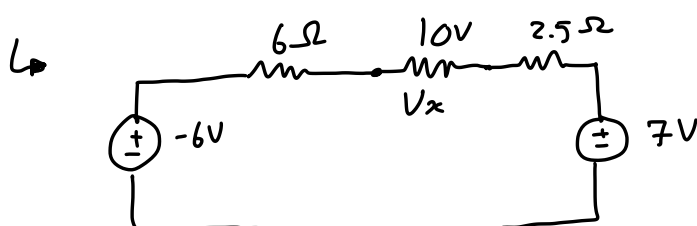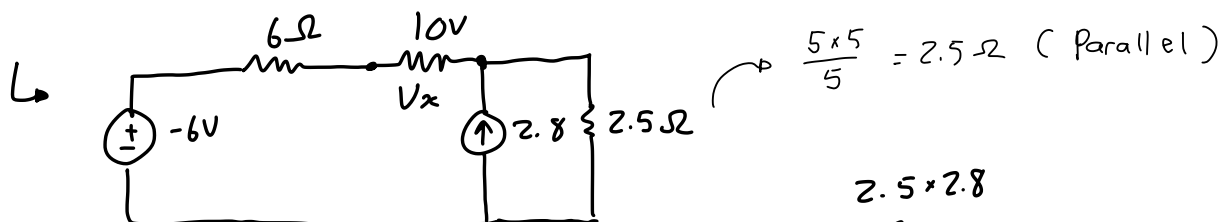

$$2.5 \times 2.8 = 7$$

$$\therefore V_2 = 7 \text{ V}$$

Question 4 [2]

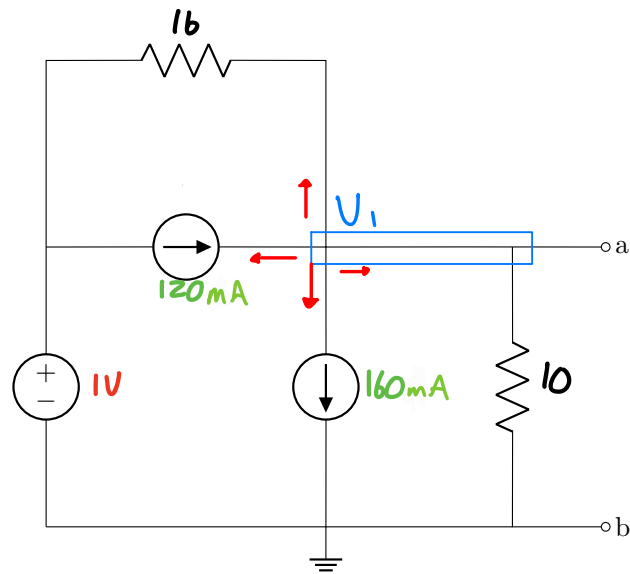Given: R_1 , R_2 , v_1 , i_1 , i_2 .04 Find the Thevenin equivalent voltage V_{Th} with regards to terminals $a-b$. [2]

Nodal: $\frac{V_1 - 1}{16} + \frac{V_1}{10} - 120 \times 10^{-3} + 160 \times 10^{-3} = 0$


$$V_1 \left(\frac{1}{16} + \frac{1}{10} \right) = -40 \times 10^{-3} + \frac{1}{16}$$

$$\frac{13}{80} V_1 = 22.5 \times 10^{-3}$$

$$V_1 = V_{ab} = V_{Th}$$

$$\underline{V_{Th} = 138.462 \text{ mV}}$$

Question 5 [2]

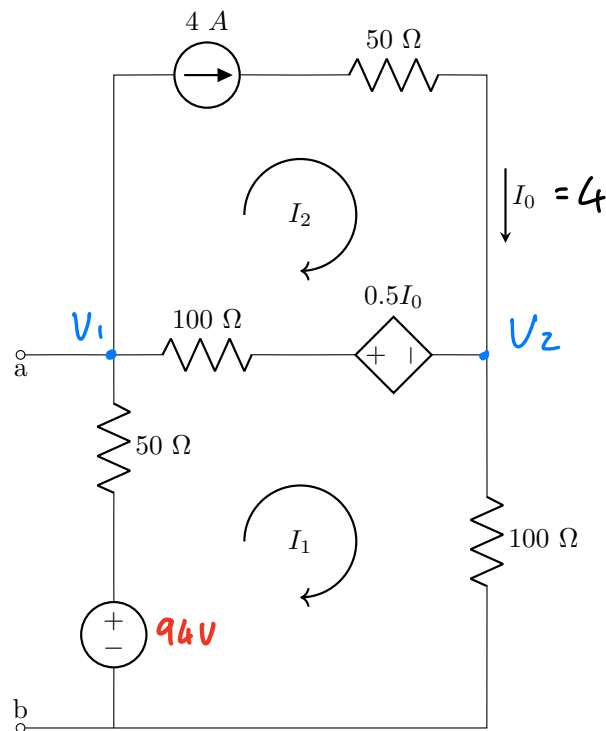Given: V_x .05 Find the Thevenin equivalent voltage V_{Th} between terminals $a-b$. [2]

Nodal @ V_1 :
$$\frac{V_1 - 0.5(4) - V_2}{100} + \frac{V_1 - 94}{50} + 4 = 0$$

$$\frac{3}{100} V_1 - \frac{1}{100} V_2 = -2.1 \quad (1)$$

@ V_2 :
$$\frac{V_2 + 0.5(2) - V_1}{100} + \frac{V_2}{100} - 4 = 0$$

$$-\frac{1}{100} V_1 + \frac{1}{50} V_2 = 3.98 \quad (2)$$


① & ② in calculator

↳ $V_1 = -6.4 \text{ V}, V_2 = 196.8 \text{ V}$

$V_{th} = V_{ab} = V_1$
 $= -6.4 \text{ V}$

$V = IR$

Questions 6 to 7 [4]

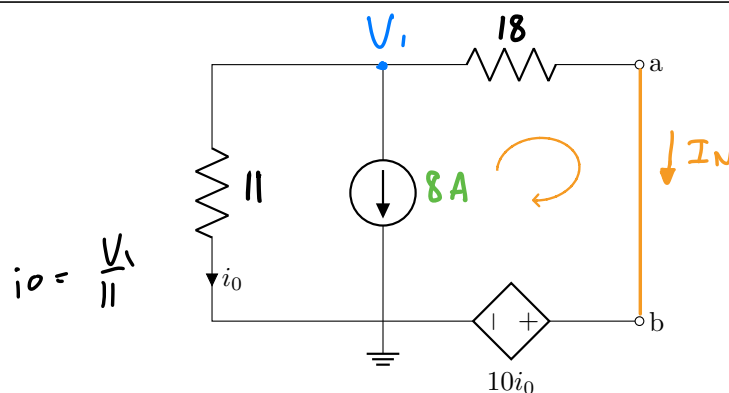Given: R_1 , R_2 , i_1 .

06	Determine the Norton equivalent current I_N . [2] ; if 1A, $I_N = -227.27mA$
07	Determine the Norton equivalent resistance R_N . [2]

⑥ @ V_1 : $\frac{V_1}{11} + 8 + \frac{V_1 - 10i_0}{18} I_N = 0$


$$\frac{29}{198} V_1 - \frac{5}{9} i_0 = -8$$

$$\frac{29}{198} V_1 - \frac{5}{99} V_1 = -8$$


$$V_1 = -83.37V$$

$$I_N = \frac{-83.37 - \left(-\frac{10}{11} 83.37\right)}{18}$$

$$= -421.06mA$$

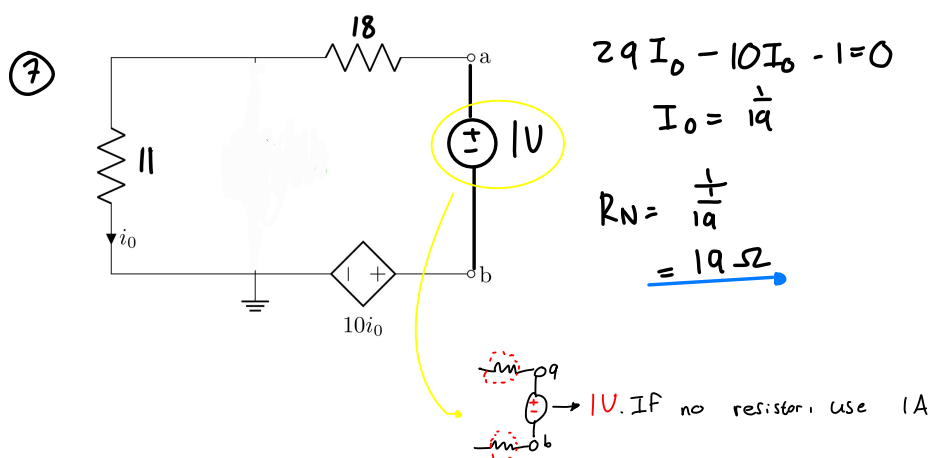


Question 8 [2]

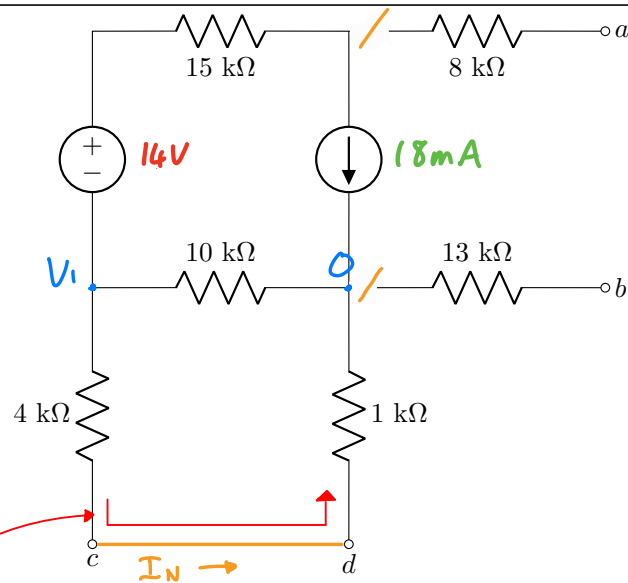Given: V_1 , I_1 .08 Determine the Norton equivalent current I_N between terminals c - d . [2]

@ V_1 : $\frac{V_1}{5000} + \frac{V_1}{1000} + 18 \times 10^{-3} = 0$
 $V_1 = -108V$

$I_N = \frac{V_1}{5000}$
 $= \frac{-108}{5000}$
 $= -21.6 \times 10^{-3} \text{ mA}$

Questions 9 to 11 [4]

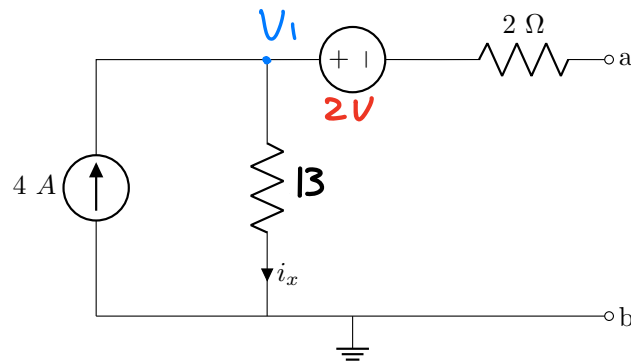Given: R_1 , V_x .

- | | |
|----|--|
| 09 | Find the Thevenin equivalent voltage V_{Th} across terminals $a-b$. [2] |
| 10 | Find the Thevenin equivalent resistance R_{Th} across terminals $a-b$. [1] |
| 11 | Calculate the maximum power that can be transferred to a load resistor R_L that can be connected between terminals $a-b$. [1] |


⑨ @ V_1 : $\frac{V_1}{13} - 4 = 0$
 $V_1 = 52 \text{ V}$

$V_1 - V_{ab} = 2$
 $52 - V_{ab} = 2$
 $V_{ab} = V_{th} = 50 \text{ V}$

⑩ $\frac{2}{13} = 15 \Omega$

⑪ $P_{max} = \frac{V_{th}^2}{4R_{th}}$
 $= \frac{50^2}{60}$
 $= 41.667 \text{ W}$

Questions 12 to 13 [2]

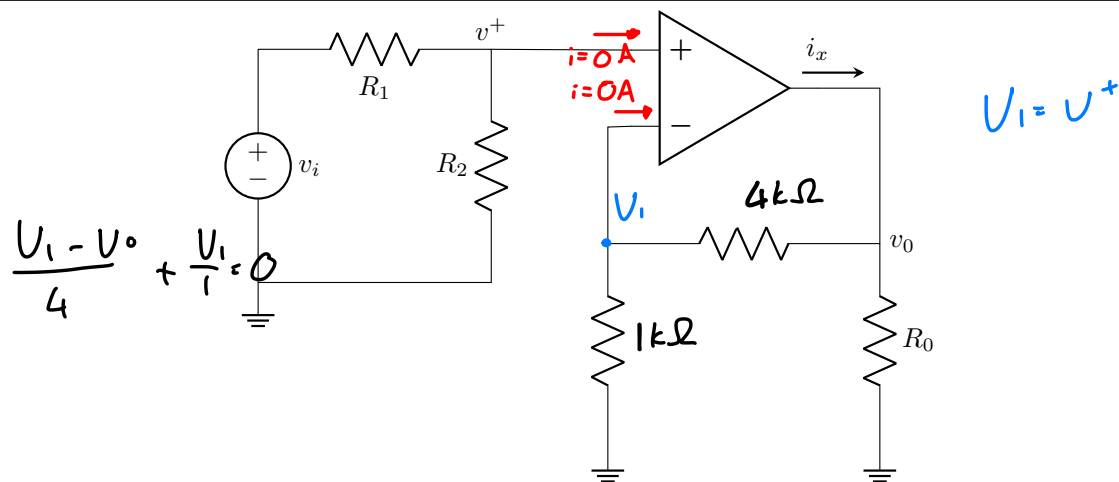Given: R_3, R_4 .Given: R_0, v^+ $R_0 = 41\Omega, v^+ = 3V$ 12 Find the current i_x . [1]

X

Given: $R_1 = R_2$ 13 Calculate the closed-loop gain (v_0/v_i) of the circuit. [1]

⑫ $U_1 = U^+ = 3V$

@ U_1 : $\frac{U_1}{1000} + \frac{U_1 - U_0}{4000} = 0$

$$5U_1 = U_0$$

$$U_0 = 15V$$

@ U_0 : $\frac{U_0 - U_1}{4000} + \frac{U_0}{41} - i_x = 0$

$$i_x = \frac{15 - 3}{4000} + \frac{15}{41}$$

$$= 368.85mA$$

⑬ @ U^+ : $\frac{U^+ - U_i}{R_1} + \frac{U^+}{R_2} = 0$


$$2U^+ = U_i$$

$$U_i = 6V$$

$$\frac{U_0}{U_i} = \frac{15}{6}$$

$$= 2.5$$

Question 14 [1]

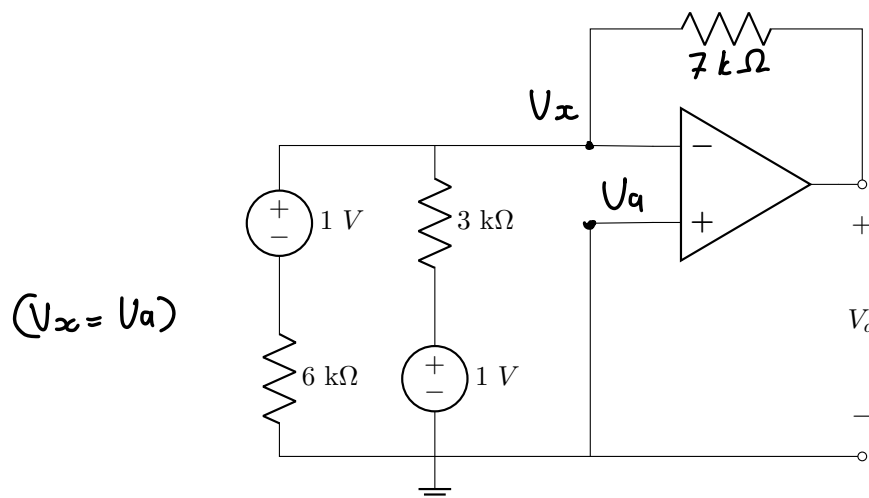Given: R_z .14 Determine V_a . [1]

✗

@ V_x : $\frac{V_x - 1}{6 \times 10^3} + \frac{V_x - 1}{3 \times 10^3} + \frac{V_x - V_a}{7 \times 10^3} = 0$

$$V_x = V_a$$

$$V_a \left(\frac{1}{6k} + \frac{1}{3k} \right) = \frac{1}{6k} + \frac{1}{3k}$$

$$\underline{V_a = 1V}$$

$$7V_x - 7 + 14V_x - 14 + 6V_x - 6V_a = 0$$

$$27V_x - 6V_a = 21$$

$$V_a = 1V$$

Total Section 1: [23]

Grand Total : [23]