

EBN111 Class Test / Klastoets 1 (3 Mar 2017)

15 Marks / Punte

30 Minutes / Minute


Question 1 [4]

- a) The lamp beside your bed uses an old 100 W tungsten globe. You replace the old globe with a 5 W LED globe. How much money do you save over one year (365 days) if the light is on for 90 minutes per day and electricity costs R1.6 per kWh?
- b) The energy associated with a certain element in a circuit decreases linearly from 20 mJ to 10 mJ between 0 ms and 4 ms. If a constant voltage of 10V is applied over the element, what is the current through the element after 2 ms? (Assume current flows from the positive to the negative voltage terminal through the element.)

Vraag 1 [4]

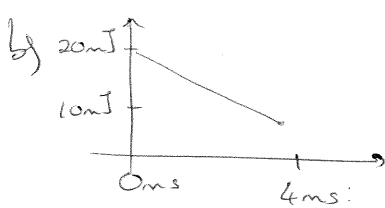- a) Die lamp langs jou bed gebruik 'n ou 100 W tungsten gloeilamp. Jy vervang die ou gloeilamp met 'n 5 W LED gloeilamp. Hoeveel geld bespaar jy oor een jaar (365 dae) indien die gloeilamp aan is vir 90 minute per dag en elektrisiteit kos R1.6 per kWh?
- b) Die energie geassosieer met 'n sekere element in 'n kringbaan val lineêr van 20 mJ tot 10 mJ tussen 0 ms en 4 ms. Indien daar 'n konstante spanning van 10 V oor die element is, wat is die stroom wat deur die element vloei na 2 ms? (Aanvaar die stroom vloei vanaf die positiewe na die negatiewe spanningsterminaal deur die element.)

$$a) R = 1.6 \text{ R/kWh} \times 1.5 \text{ h/day} \times 365 \text{ days} \times (0.1 - 0.005) \text{ kWh} \\ \approx \underline{\underline{R 83.22}} \quad \checkmark$$



$$p = \frac{dw}{dt} = v \cdot i$$

$$\text{At } t = 2 \text{ ms:}$$


$$\frac{-10 \text{ mJ}}{4 \text{ ms}} = 10 \cdot i \Rightarrow i = \underline{\underline{-250 \text{ mA}}} \quad \checkmark$$

Question 2 [4]

- If $V_0 = 140 \text{ V}$, calculate the power associated with the
a) 50 V voltage source (P_V), and
b) the dependant current source (P_A).

Vraag 2 [4]

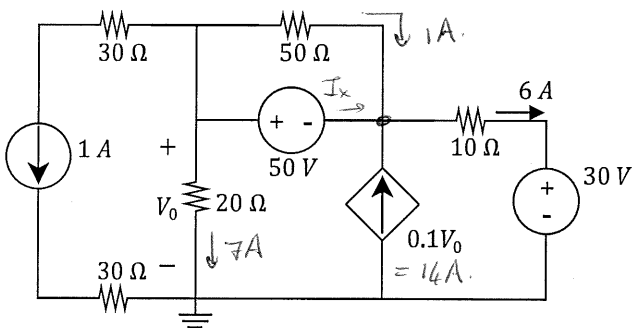
- Indien $V_0 = 140 \text{ V}$, bepaal die drywing geassosieer met
a) die 50 V stroombron (P_V), en
b) die afhanklike stroombron (P_A).



$$\begin{aligned} * I_x &= 6 - 1 - 14 \\ &= -9 \text{ A} \end{aligned}$$

$$P_V = +50 \cdot I_x$$
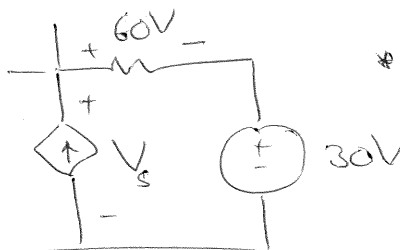
$$= \underline{\underline{-450 \text{ W}}} \quad \checkmark$$



$$* -V_s + 60 + 30 = 0$$

$$V_s = 90 \text{ V}$$



$$* P_A = - (0.1 V_0) (90)$$

$$= \underline{\underline{-1.26 \text{ kW}}} \quad \checkmark$$

Question 3 [2]

 Determine R_{ab} .

Vraag 3 [2]

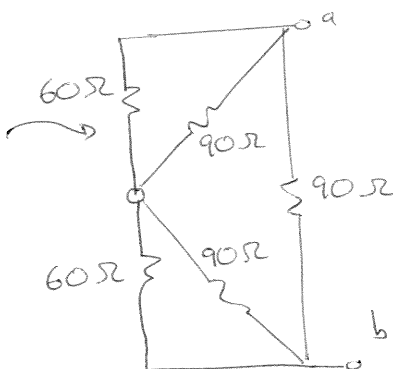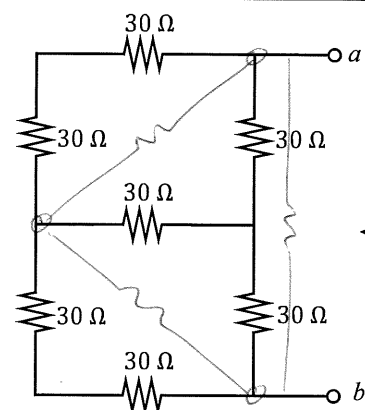 Bepaal R_{ab} .


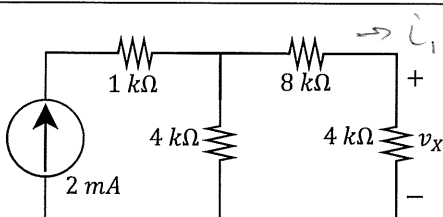
$$R_{\Delta} = 3R_Y$$

$$\begin{aligned} R_{ab} &= (90 \parallel 60 + 90 \parallel 60) \parallel 90 \\ &= (36 + 36) \parallel 90 \\ &= 72 \parallel 90 \\ &= \frac{72 \times 90}{72 + 90} \\ &= 40 \Omega \end{aligned}$$

Question 4 [2]

 Determine v_x .

Vraag 4 [2]

 Bepaal v_x .


$$\begin{aligned} * i_1 &= \frac{2 \text{ mA} \times 4 \text{ k}}{4 \text{ k} + 8 \text{ k} + 4 \text{ k}} \quad (\text{I-division}) \\ &= 0.5 \text{ mA} \end{aligned}$$

$$\begin{aligned} * v_x &= +0.5 \text{ mA} \times 4 \text{ k} \\ &= 2 \text{ V} \end{aligned}$$

Question 5 [4]


Use nodal analysis to set up two equations of the following form:

$$\begin{aligned} aV_1 + bV_2 &= 12 \\ cV_1 + dV_2 &= 21 \end{aligned}$$

Vraag 5 [4]

Gebruik nodeanalyse om twee vergelykings van die volgende vorm op te stel:
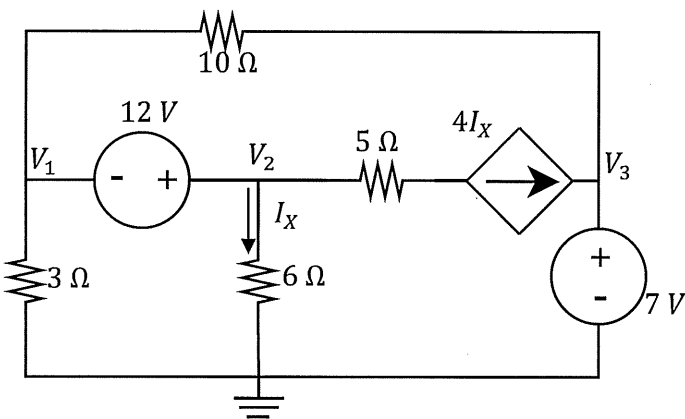
$$\begin{aligned} aV_1 + bV_2 &= 12 \\ cV_1 + dV_2 &= 21 \end{aligned}$$



$$* V_2 - V_1 = 12 \text{ V}$$

$$\therefore -V_1 + V_2 = 12 \text{ V}$$

$$* I_x = \frac{V_2}{6}$$

$$* \frac{V_1}{3} + \frac{V_1 - 7}{10} + 5I_x = 0$$

$$\therefore \frac{V_1}{3} + \frac{V_1}{10} + 5 \cdot \frac{V_2}{6} - \frac{7}{10} = 0$$

$$(\times 30) \quad 10V_1 + 3V_1 + 25V_2 - 21 = 0$$

$$13V_1 + 25V_2 = 21$$