

Class Test 1

Copyright reserved

Electricity and Electronics EBN 111

16 March 2022

Test Information

Maximum marks:	16	Full marks:	15
Duration of test:	35 min	Open/Closed book:	Open
Total number of pages (this page included)		9	

Lecturers: Prof X. Ye, Prof J.D. le Roux, Mr V. Dube**Assistant Lecturers:** N. Matic, K. Mphaga, J. Thiselton, D.A. Wepener**ECSA outcome assessment**

The following ECSA graduate outcomes are assessed at entry level in this question paper: GA1 and GA2

Important

1. The examination regulations of the University of Pretoria apply.
2. The departmental rules relevant to electronically graded assessments apply.
3. Write your answers on the Excel spreadsheet found on the AMS system. The spreadsheet contains unique parameter values for each student. Therefore, you must download the Excel spreadsheet from your own AMS account. Follow the instructions on the AMS spreadsheet carefully.
4. Final answers must be written as real numbers and not as fractions. Use at least 5 significant figures to write numbers, including complex numbers. Use decimal points and NOT decimal commas.
5. Answers must include units where applicable. (Refer to the EECE Rules for Electronic Assessments of tests and examinations for guidelines on how to enter units. Also refer to the example list of units on the Excel spreadsheet.)
6. **By uploading your assessment, you declare the following:**

The University of Pretoria commits itself to produce academic work of integrity. I affirm that I am aware of and have read the Rules and Policies of the University, more specifically the Disciplinary Procedure and the Tests and Examinations Rules, which prohibit any unethical, dishonest or improper conduct during tests, examinations and/or any other forms of assessment.


I hereby declare that the work herewith is completely my own and that no parts have been copied in any way from current or previous students or other sources.

Online assessment submission rules and time-line

The following rules and time-line apply for all tests for EBN111/122 as illustrated by the figure below:

1. The Download Grace Period (DGP) is a 15 minute period before the official start of the test for students to download all documents related to the test and read all the necessary instructions.
2. The start of the green section after the DGP indicates the official start of the test.
3. The upward green arrow at the end of the green section indicates the official submission deadline for the test.
4. Students must aim to submit their Excel spreadsheet with their answers on the AMS before the official submission deadline.
5. Students can request assistance via **e-mail** ebn2022.ams@gmail.com if they experience any technical issues with respect to uploading their Excel spreadsheets on the AMS during the official test time.
6. An Upload Grace Period (UGP) of 15 minutes follows the official submission deadline. Students may submit their Excel spreadsheets with answers on the AMS during this period without incurring any penalties. Submission problems must be reported within the first 10 minutes of the UGP.
7. A Penalty Period (PP) of 10 minutes follows the UGP. If a student submits an Excel spreadsheet during this period, the student incurs a 10% penalty to their final test mark.
8. No late submissions are accepted after the PP.

Late submissions of session-based assessments, e.g. tests and online practicals

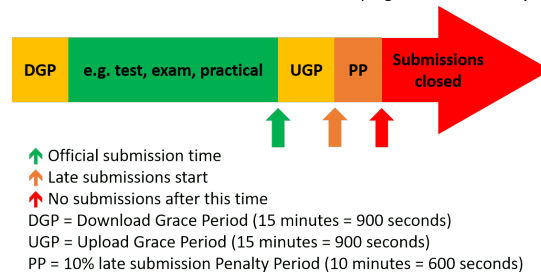


Section 1

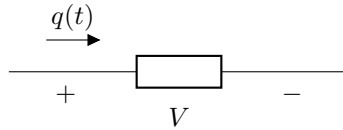
Question 1 [2]


Given: a , b , T , V .


The charge $q(t)$ flowing through the device below changes linearly from $q(0) = a$ mC to $q(T) = b$ mC. There is a constant voltage, V , over the device for the entire time period $t = 0$ s to $t = T$ s.




01	What is the power associated with the device? [2]
-----------	---

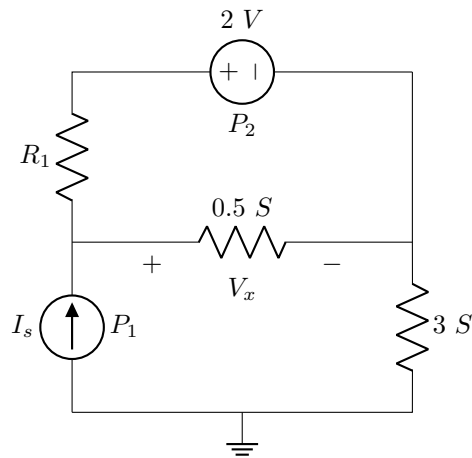
Questions 2 to 3 [4]Given: I_s , V_x .The value of R_1 is unknown. Calculate the power associated with:**02** P_1 [2]**03** P_2 [2]

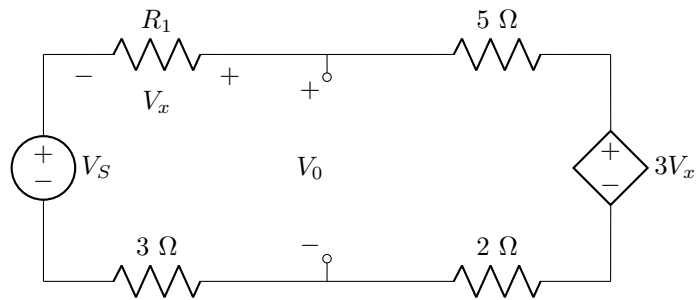Question 4 [2]Given V_S and R_1 .**04** Determine V_0 . [2]

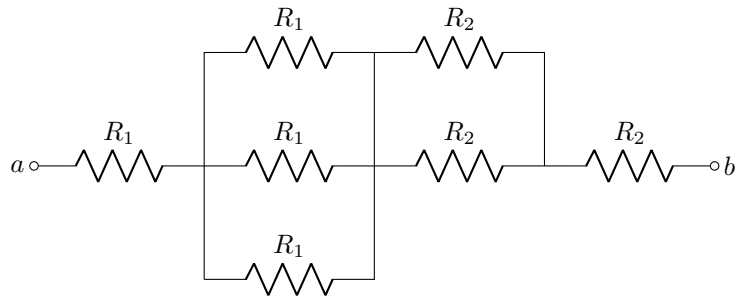Question 5 [2]Given: R_1 , R_2 .**05** Determine R_{ab} . [2]

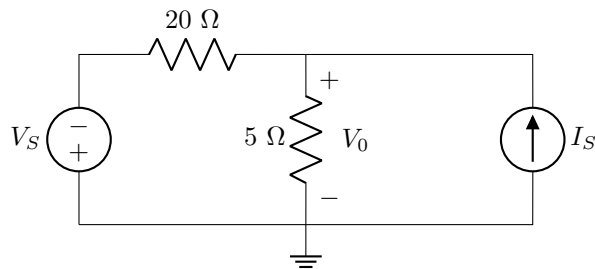Question 6 [2]Given: I_S and V_S .**06** Use nodal or mesh analysis to solve for V_0 . [2]

m Direction same as
current direction

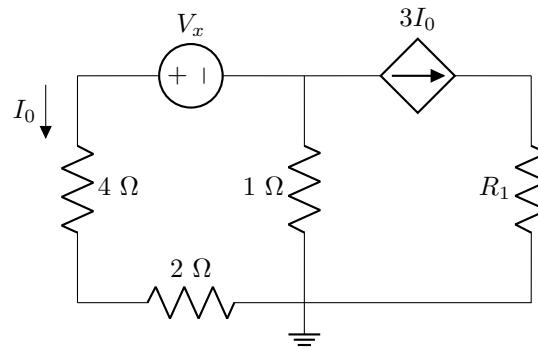Question 7 [2]Given: V_x and R_1 .**07** Use nodal or mesh analysis to solve for I_0 [2]

Question 8 [2]	
Given: a, b, c .	
$\begin{bmatrix} a & -2 \\ 1 & b \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} c \\ 0 \end{bmatrix}$	
08	Determine V_1 . [2]

Total Section 1: [16]

Grand Total : [16]
