

EBN III Class Test 1 (15 March 2024)

Memo

Question 1 to 3

$$\begin{aligned} 01) Q_b &= \int_0^{t_0} i(t) dt = \text{Area under } i(t) \text{ from } 0h \text{ to } 8h \\ &= 1.8.60.60 \\ &= 28800 \text{ C} \end{aligned}$$

$$02) P(t) = v(t) \cdot i(t) = v(t) \cdot 1 = v(t)$$

$$\begin{aligned} W_b &= \int_0^{t_0} P(t) dt = \int_0^{t_0} v(t) dt = \text{Area under } v(t) \\ &\quad \text{from } 0h \text{ to } 8h \end{aligned}$$

$$= 10 \cdot 8 + \frac{1}{2} \cdot 80 \cdot 8$$

$$= 80 + 320$$

$$= 400 \text{ Wh}$$

$$03) \text{ Cost} = W_b \times \text{Price}$$

$$= 0,4 \text{ kWh} \times R2,50 \text{ per kWh}$$

$$= R1,00$$

Question 4 to 5

$$\text{KVL: } -12 + 10 I_0 - 0,5 V_0 + 5 - V_0 = 0$$

$$-7 + 10 I_0 - 1,5 V_0 = 0$$

— ①

$$\text{Ohm @ } 5 \Omega : V_0 = -5 I_0$$

— ②

$$\textcircled{2} \text{ in } \textcircled{1} : -7 + 10 I_0 + 7,5 I_0 = 0$$

$$17,5 I_0 = 7$$

04)

$$I_0 = \frac{7}{17,5} = 0,4 \text{ A}$$


05)

$$V_0 = -5 I_0$$


$$= -5 \cdot 0,4$$

$$= -2 \text{ V}$$




Question 6

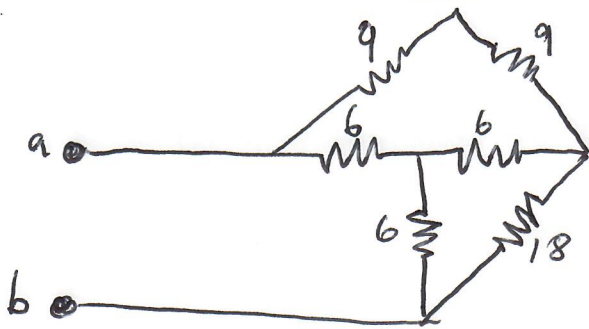

Wye to delta :

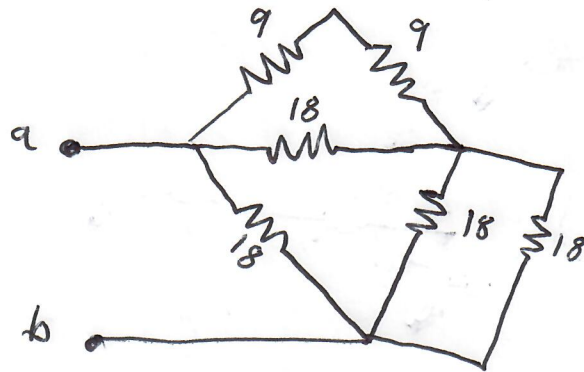

$18 \parallel 18$ and $9+9$:

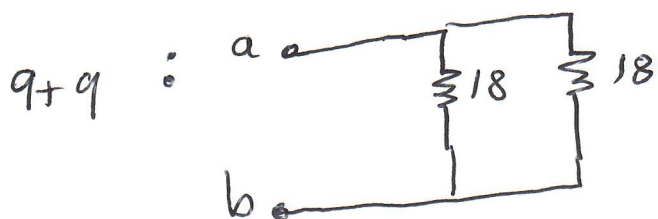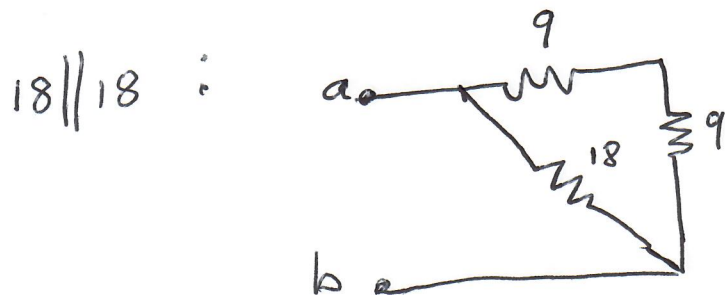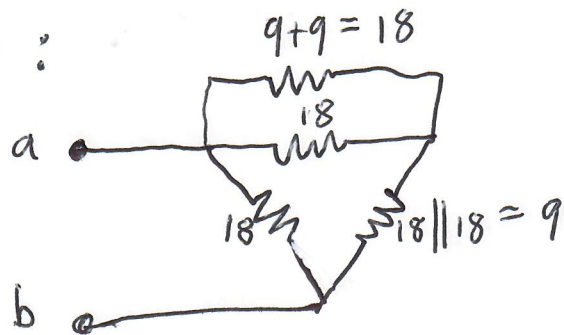

06) $R_{ab} = 9$

Question 7

Nett current flowing into top node:

$$\begin{aligned} I_1 &= 14 - 7 \\ &= 7A \end{aligned}$$

Current through 2Ω (use current divider)

$$\begin{aligned} I_o &= I_1 \cdot \frac{5}{2+5} \\ &= 7 \cdot \frac{5}{7} \\ &= 5A \end{aligned}$$

Questions 8 to 11

$$\text{KCL @ node 1: } \frac{V_1 - 10}{10} + \frac{V_1 - 0}{20} + \frac{V_1 - V_2}{5} + 3 = 0 \quad \text{--- (1)}$$

① $\times 20$:

$$2V_1 - 20 + V_1 + 4V_1 - 4V_2 + 60 = 0$$

$$7V_1 - 4V_2 = -40 \quad \text{--- (2)}$$

$$\text{Ohm @ } 10\Omega : \quad 10 - V_1 = V_0 \quad \text{--- (3)}$$

$$\text{KCL @ node 2: } V_2 = 5V_0 \quad \text{--- (4)}$$

③ in ④ :

$$V_2 = 50 - 5V_1$$

$$\therefore 5V_1 + V_2 = 50 \quad \text{--- (5)}$$

Thus :

$$7V_1 - 4V_2 = -40$$

$$5V_1 + V_2 = 50$$

08) $a = 7$

09) $b = -40$

10) $c = 5$

11) $d = 1$