

EBN111 Klastoets/Class Test#1: 2 Maart/March 2012

Naam/Name:	MEMORANDUM
Studente/Student nr:	
Graad/Degree:	B. Ing/Eng()

Q1	Q2	Q3	Q4
t = 3 sec. ✓	t = 6.7 uur ✓✓	P _{10A} = -800 W ✓ P _{2Ω} = 2888 W ✓	V _{ab} = 3 V ✓✓
Q5	Q6	Q7	Q8
I ₁ = -2.5 A ✓✓	V ₂ = 5.71 V ✓✓	a = 19 ✓✓ b = -4 ✓✓ c = -6 ✓ d = 11 ✓	V ₁ = 0.2 V ✓✓

Finale Punt/Final Mark:

/15

- (1) Indien die stroom in 'n geleier 2mA is, hoe lank sal dit neem voordat 6mC deur die geleier beweeg het/If the current in a conductor is 2mA, how much time is required for 6mC to pass through the conductor? [1]


$$i = \frac{\Delta Q}{\Delta t} \Rightarrow \Delta t = \frac{\Delta Q}{i} = \frac{6 \text{ mC}}{2 \text{ mA}} = 3 \text{ sec.} \rightarrow$$

- (2) Teen 60 sent per kWh, hoeveel ure kan jy 'n 250W TV-stel gebruik vir 'n totale koste van een rand/At 60 cent per kWh, how many hours can you watch a 250W TV for one rand? [2]

$$\frac{1}{0.6} = 1.67 \text{ kWh kan gehoop word met een rand}$$

$$\frac{1.67}{0.25} = 6.7 \text{ uur} \rightarrow$$

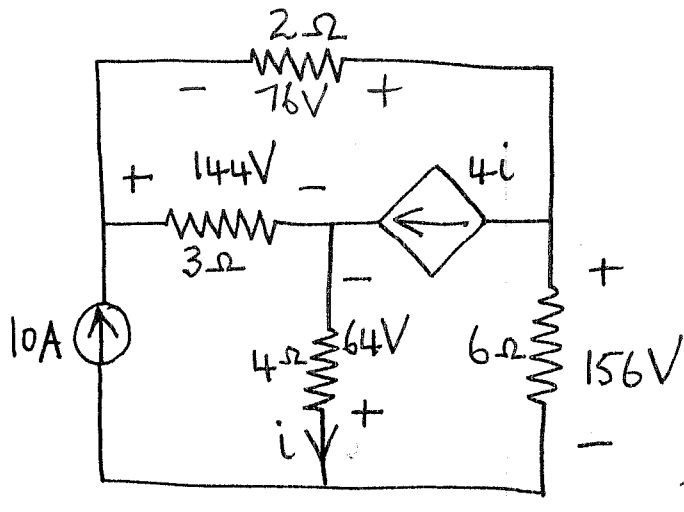- (3) Bereken die drywings ge-assosieer met die 10A bron en die 2Ω weerstand/Calculate the power associated with the 10A source and the 2Ω resistor. [2]



$$10A \uparrow \quad V_{10A} = 144 - 64 = 80V$$



$$P_{10A} = -10 \times 80 = -800W \rightarrow$$

$$I_{2\Omega} \rightarrow$$

$$3i + 10 = I_{2\Omega}$$

$$I_{2\Omega} = 3\left(-\frac{64}{4}\right) + 10 = -38A \quad P_{2\Omega} = (+76) \times (-38) = 2888W \rightarrow$$


- (4) Bereken/Calculate V_{ab} . [2]

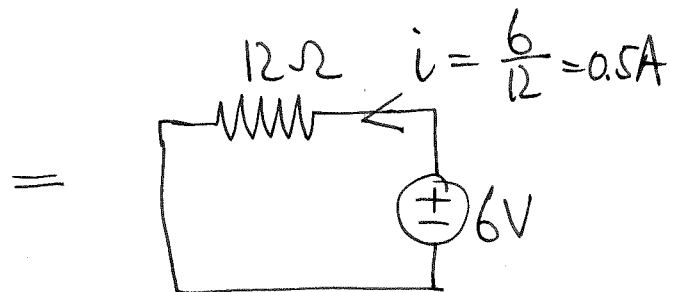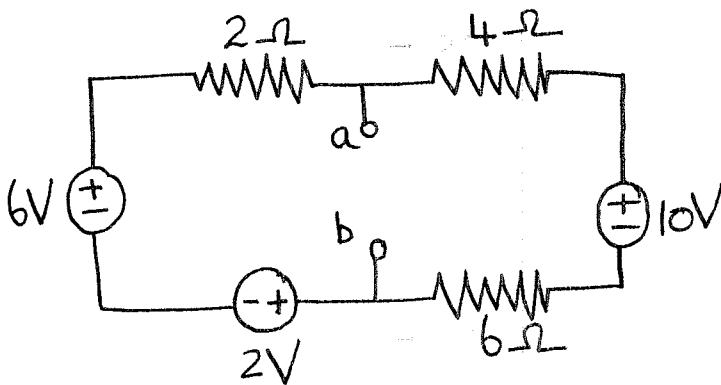

$$-V_{ab} - (4+6) \times 0.5 + 10 = 0$$

$$V_{ab} = -5 + 10 = 5V \rightarrow$$


(5) Bereken/Calculate I_1 . [2]

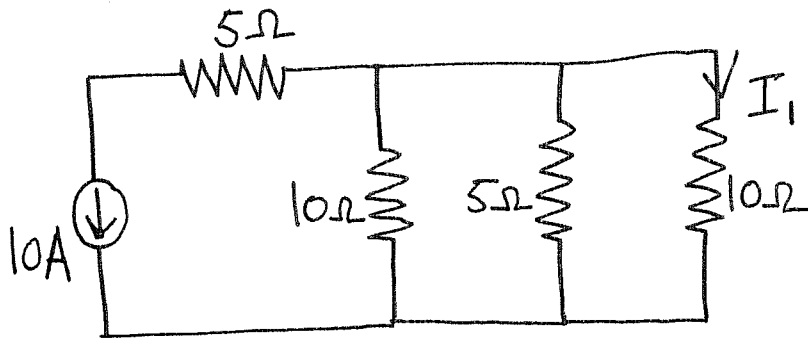

$$10 \parallel 5 = \frac{50}{15} = 3.33 \Omega$$

$$I_1 = -10 \times \frac{3.33}{10 + 3.33} = -2.5 A \rightarrow$$

(6) Bereken/Calculate V_2 . [2]

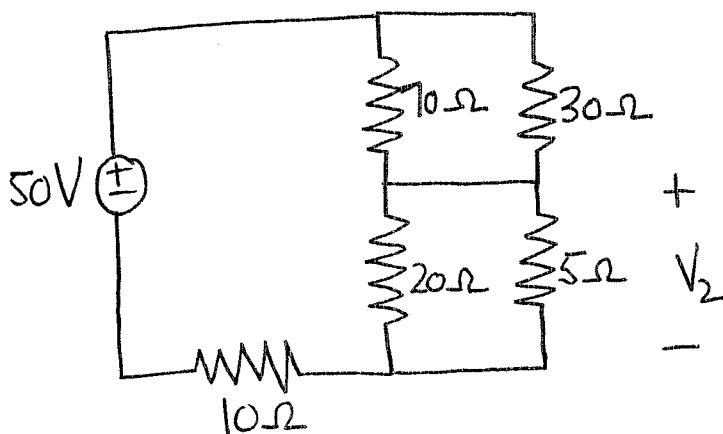


$$30 \parallel 70 = 21 \Omega$$

$$20 \parallel 5 = 4 \Omega$$

$$V_2 = \frac{4}{21 + 4 + 10} \times 50 = 5.71 V \rightarrow$$

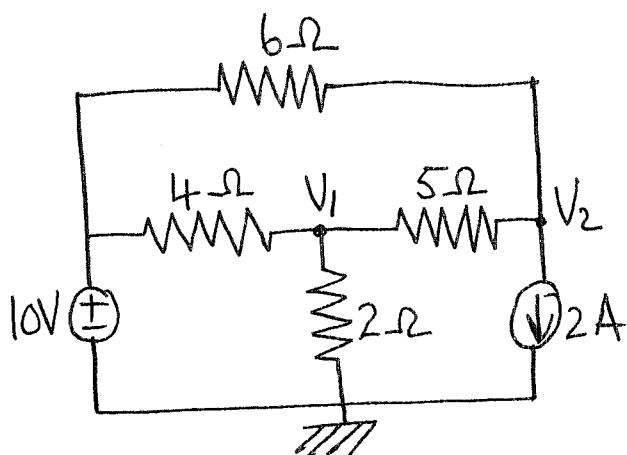(7) Gebruik-node-analise om twee vergelykings van die volgende vorm op te stel/Use nodal analysis to set up two

equations of the following form: $aV_1 + bV_2 = 50$
 $cV_1 + dV_2 = -10$ [2]



KCL at node 1:

$$\frac{V_1 - 10}{4} + \frac{V_1}{2} + \frac{V_1 - V_2}{5} = 0$$

$$\times 20: 5V_1 - 50 + 10V_1 + 4V_1 - 4V_2 = 0$$

$$\underline{19V_1 - 4V_2 = 50}$$

KCL at node 2:

$$2 + \frac{V_2 - V_1}{5} + \frac{V_2 - 10}{6} = 0$$

$$\times 30: 60 + 6V_2 - 6V_1 + 5V_2 - 50 = 0$$

$$\underline{-6V_1 + 11V_2 = -10}$$

(8) Bepaal/Determine V_1 : $\begin{bmatrix} 4 & -3 \\ 4 & 2 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 2 \\ 0 \end{bmatrix}$ [2]

$$V_1 = \frac{\begin{vmatrix} 2 & -3 \\ 0 & 2 \end{vmatrix}}{\begin{vmatrix} 4 & -3 \\ 4 & 2 \end{vmatrix}} = \frac{4 - 0}{8 - (-12)} = \frac{4}{20} = \underline{0.2V}$$