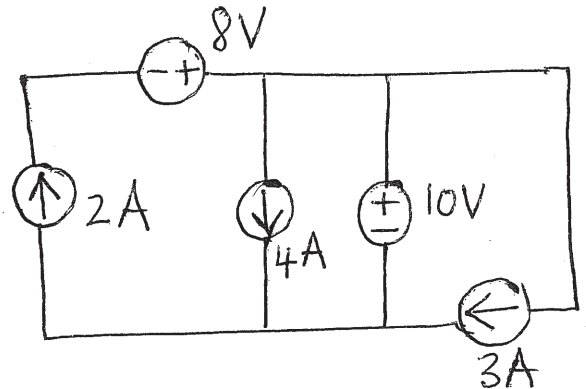



EBN111 Klastoets/Class Test#1: 1 Maart/March 2013

- Q1 'n Nuwe soort battery lewer $10W$ drywing vir 8 ure sonder enige variasie in spanning of stroom. Na 8 ure val die drywingsuitset lineêr van $10W$ na 0 binne 30 minute. Bepaal die energie stoorkapasiteit van die battery. [2]
A new type of battery delivers $10W$ of power for 8 hours without voltage or current fluctuation. After 8 hours the power output drops linearly from $10W$ to 0 in 30 minutes. Determine the energy storage capacity of the battery.


- Q2 Bereken die drywing ge-assosieer met die $8V$ spanningsbron en die $3A$ stroombron. [2]
Calculate the power associated with the $8V$ voltage source and the $3A$ current source.



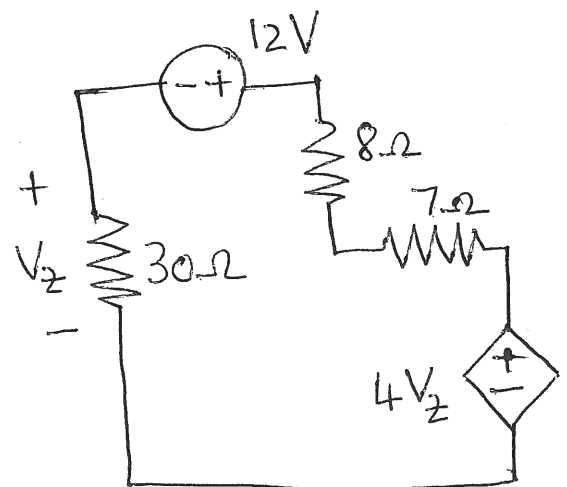
- Q3 Bepaal v_z in die stroombaan. [2]
Determine v_z in the circuit.



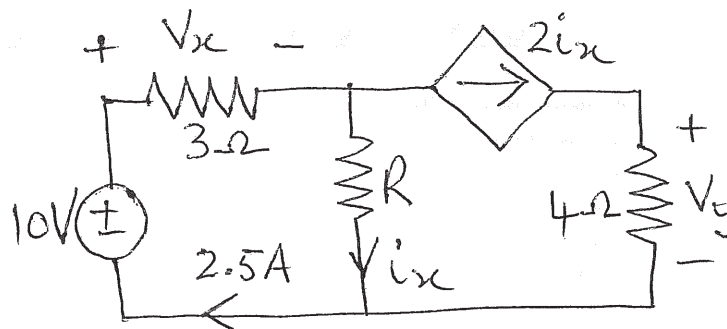- Q4 Bereken v_x , v_y en i_x in die stroombaan. [3]
 Calculate v_x , v_y and i_x in the circuit.



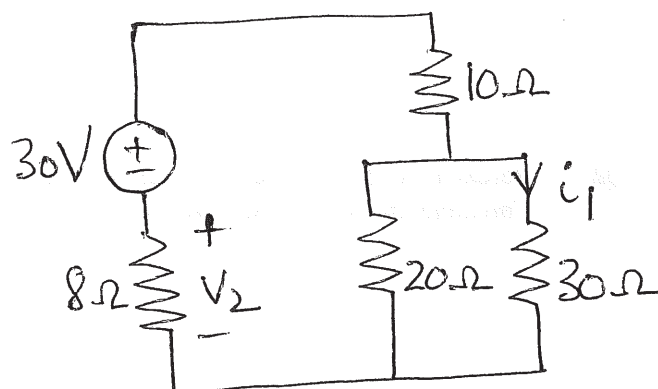- Q5 Bereken/Calculate
 (a) i_1 [2]
 (b) v_2 [2]



- Q6 Bereken R_{eq} . [2]
 Calculate R_{eq} .

