

Memo

EBN111 CLASS TEST 2 / KLASTOETS 2

8 April 2016


[30 min / 15 marks]

Question 1 [3]

Determine the mesh-current equations by means of inspection.


Vraag 1 [3]

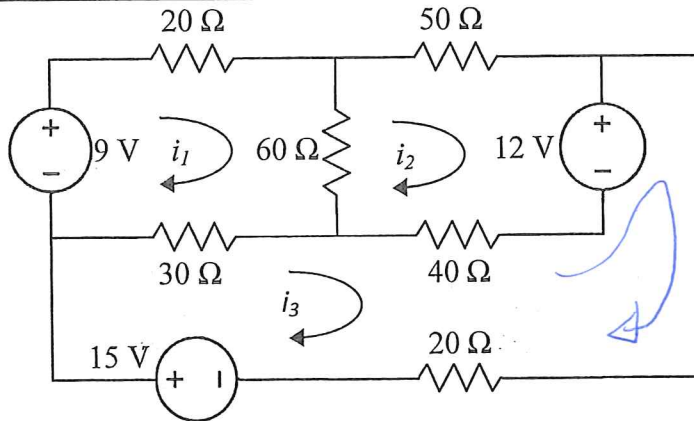Bepaal die lus-stroom vergelykings deur inspeksie.



$$\begin{bmatrix} 110 & -60 & -30 \\ -60 & 150 & -40 \\ -30 & -40 & 90 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} 9 \\ -12 \\ 27 \end{bmatrix} \begin{matrix} \checkmark \\ \checkmark \\ \checkmark \end{matrix}$$

* 1 mark per correct row

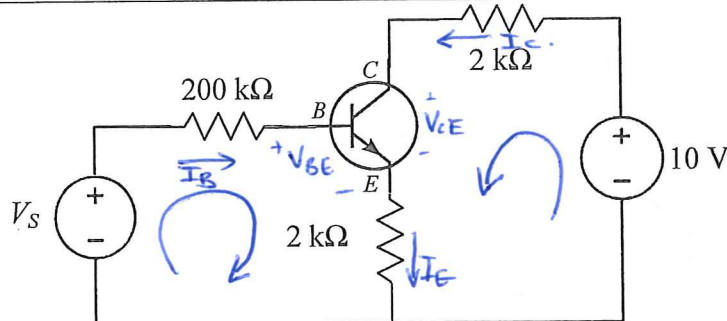Question 2 [4]Given: $\beta = 99$ and $V_{BE} = 0.7$ V.a) If $I_C = 0.5$ mA, determine V_S . [2]b) If $I_B = 10$ μ A, determine V_{CE} . [2]**Vraag 2 [4]**Gegee: $\beta = 99$ en $V_{BE} = 0.7$ V.a) Indien $I_C = 0.5$ mA, bepaal V_S . [2]b) Indien $I_B = 10$ μ A, bepaal V_{CE} . [2]

a) $I_C = 0.5 \text{ mA}$

$$\therefore I_B = \frac{I_C}{\beta} = 5.0505 \mu\text{A}$$

$$I_E = I_C + I_B = (1 + \beta)I_B = 5.051 \times 10^{-4} \text{ A}$$

$$\therefore -V_S + 200\text{k} I_B + V_{BE} + 2\text{k} I_E = 0$$

$$\begin{aligned} V_S &= 200\text{k}(5.0505 \mu) + 0.7 + 2\text{k}(5.051 \times 10^{-4}) \\ &= +2.72 \text{ V} \end{aligned}$$

b) $I_B = 10 \mu\text{A}$

$$\therefore -10 + 2\text{k}(\beta I_B) + V_{CE} + 2\text{k}(1 + \beta)I_B = 0$$





$$V_{CE} = +6.02 \text{ V}$$

Question 3 [2]

Use source transformation and determine V_x .

Vraag 3 [2]

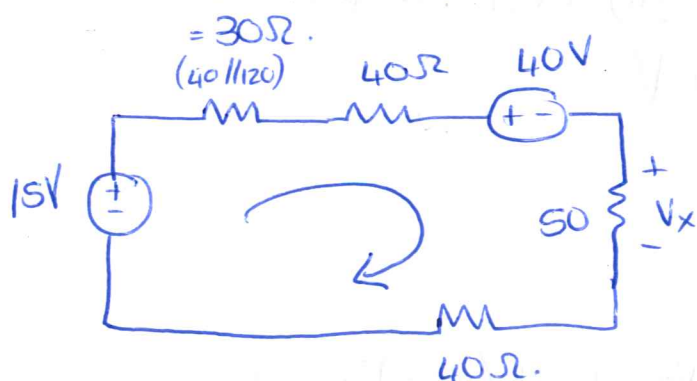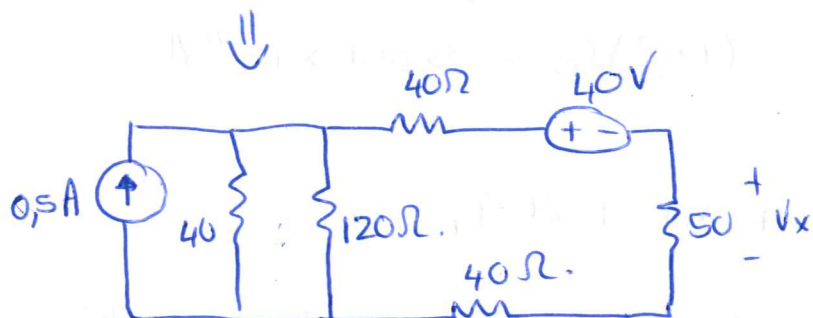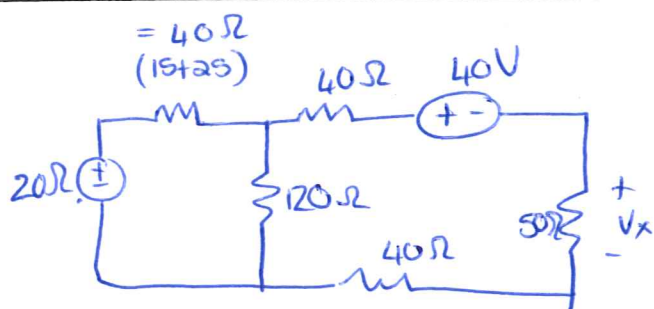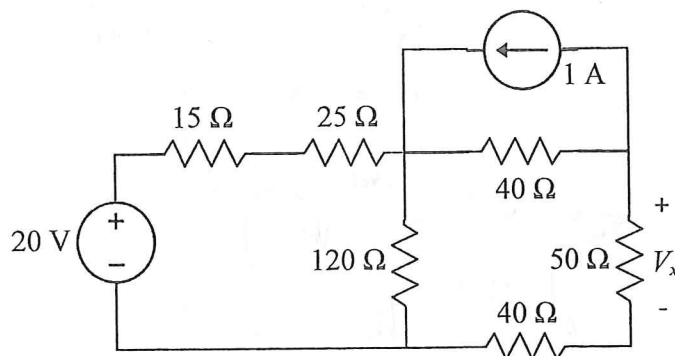Gebruik brontransformatie en bepaal V_x .



$$-15 + (30 + 40 + 50 + 40)I + 40 = 0$$

$$\therefore I = -0,15625 \text{ A}$$


$$\begin{aligned} \therefore V_x &= I(50) \\ &= -7,81 \text{ V} \end{aligned}$$

Question 4 [2]



Use superposition and determine I_x due to the current source.

Vraag 4 [2]

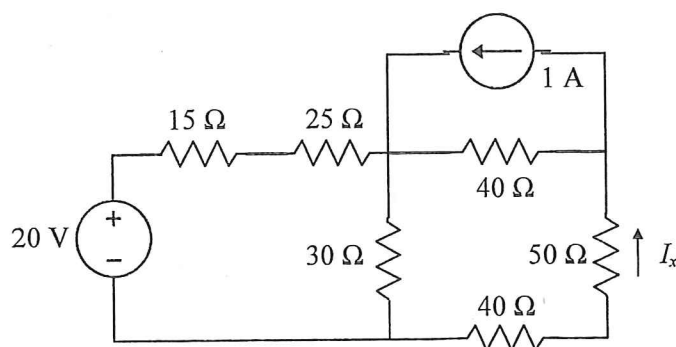Gebruik superposisie en bereken I_x agv die stroombron.



$\therefore I_x$ due to current source:

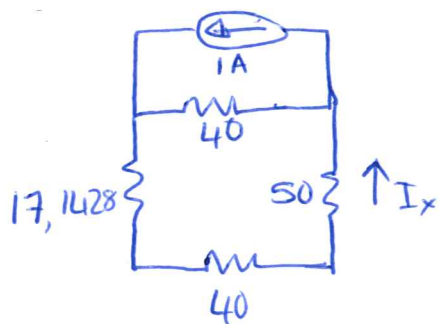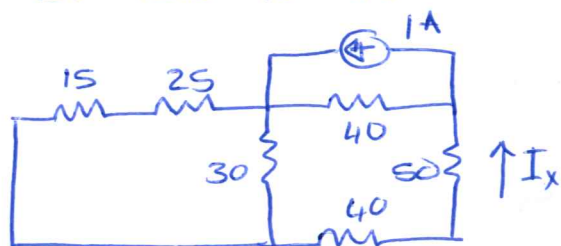

$$\therefore I_x = 1 \left(\frac{40}{40 + (17,143 + 40 + 50)} \right)$$

$$= 0,271 \text{ A}$$

✓

Question 5 [4]

Gebruik superlus-analyse om twee vergelykings van die volgende vorm op te stel:

$$ai_1 + bi_2 = 15$$


$$ci_1 + di_2 = 0$$

Vraag 5 [4]

Use supermesh analysis to set up two equations of the following form:

$$ai_1 + bi_2 = 15$$

$$ci_1 + di_2 = 0$$

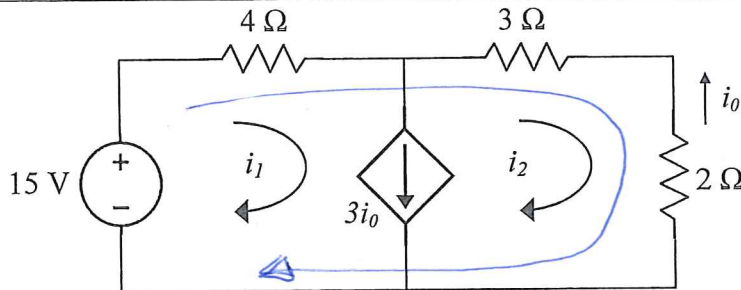

$$\textcircled{1} \quad -15 + 4i_1 + 3i_2 + 2i_2 = 0$$

$$\textcircled{4}i_1 + \textcircled{5}i_2 = 15$$

$$\textcircled{2} \quad i_0 = -i_2$$

$$i_1 - i_2 = 3i_0$$

$$i_1 - i_2 = 3(-i_2)$$

$$\therefore \textcircled{1}i_1 + \textcircled{2}i_2 = 0$$

$$a = 4 \checkmark \quad b = 5 \checkmark$$

$$* \quad c = 1 \checkmark \quad d = 2 \checkmark$$

we also accepted

$$\boxed{c = -1 \quad d = -2}$$

ONLY if both coefficients were negative.

Memo

EBN111 CLASS TEST 2 / KLASTOETS 2 (8 APR 2012) ANSWER SHEET / ANTWOORDBLAD

Surname: Van:		Student number: Studentenommer:						
Initials: Voorletters:		Group: Groep:	ENG	ENG (Mech)		AFR		

Tot:	/15
-------------	------------

1	$\begin{bmatrix} 110 & -60 & -30 \\ -60 & 150 & -40 \\ -30 & -40 & 90 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} 9 \\ -12 \\ 27 \end{bmatrix}$ ✓✓✓	
2	a) $V_S = 2,72V$ ✓✓ b) $V_{CE} = 6,02V$ ✓✓	
3	$V_x = -7,81V$ ✓✓	
4	$I_x = 0,271 A$ ✓✓	
5	a = 4 ✓	b = 5 ✓
	c = 1 ✓	d = 2 ✓

0/0/0/0

20

107

p

w

f

UNIVERSITY

OF

THE

STATE

2

4

1

1