
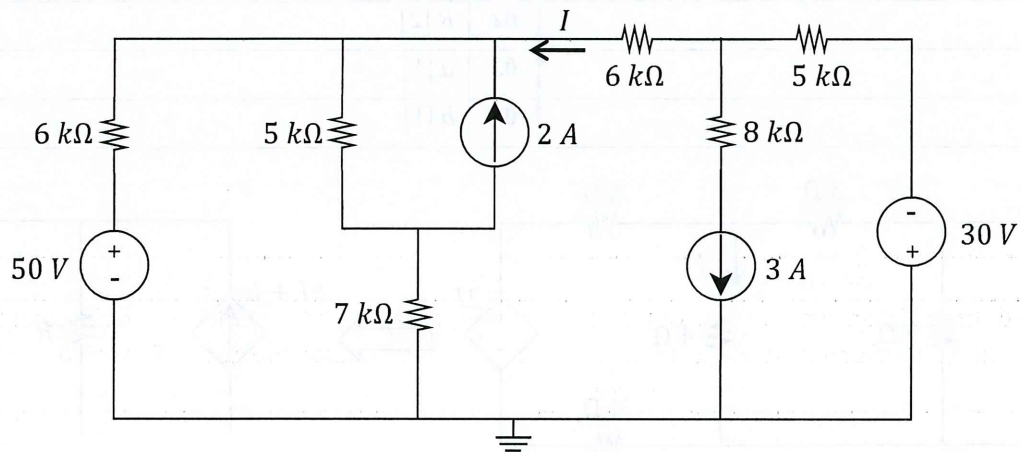



Question 1 [2]		Vraag 1 [2]	
01	Use superposition to find the exclusive contribution of the 3A current source to the current I .	01	Maak gebruik van superposisie en bepaal die bydra van die 3 A stroombron tot die stroom I alleenlik.

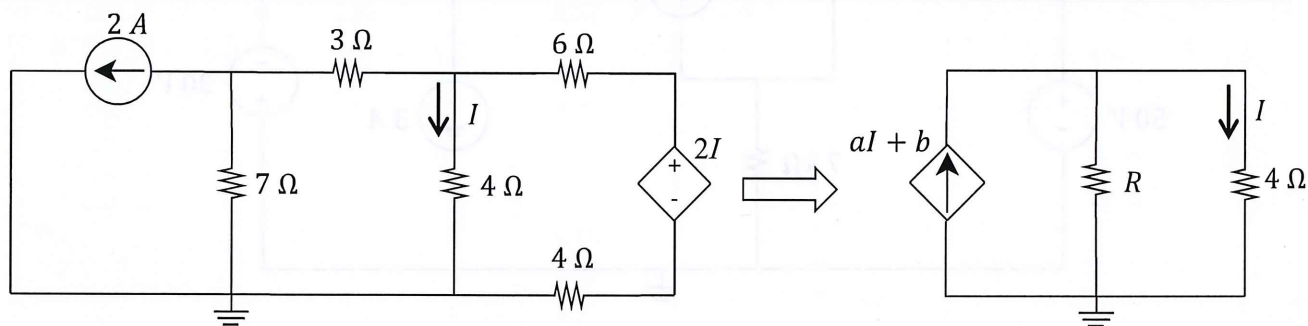


Question 2 - 4 [4]		Vraag 2 - 4 [4]	
Simplify the circuit on the left by means of source transformation so that it looks like the one on the right. Determine:		Vereenvoudig die stroombaan aan die linkerkant met behulp van brontransformasie sodat dit lyk soos die kringbaan aan die regterkant. Bepaal:	
02	R [2]	02	R [2]
03	a [1]	03	a [1]
04	b [1]	04	b [1]




Question 5 & 6 [4]		Vraag 5 & 6 [4]	
Determine the Thevenin equivalent voltage V_{TH} and resistance R_{TH} w.r.t. terminals a - b .		Bepaal die Thevenin ekwivalente spanning V_{TH} en weerstand R_{TH} met verwysing tot terminale a en b .	
05	V_{th}	05	V_{th}
06	R_{th}	06	R_{th}

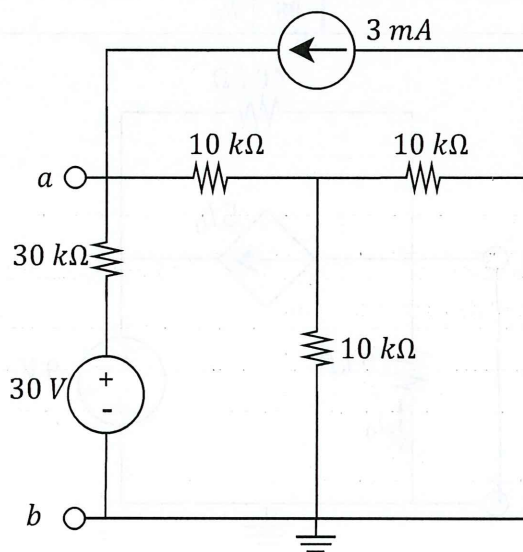

Question 7 & 8 [4]		Vraag 7 & 8 [4]	
Determine the Norton equivalent current I_N and resistance R_N w.r.t. terminals a - b .		Bepaal die Norton ekwivalente stroom I_N en weerstand R_N met verwysing tot terminale a en b .	
07	I_N	07	I_N
08	R_N	08	R_N

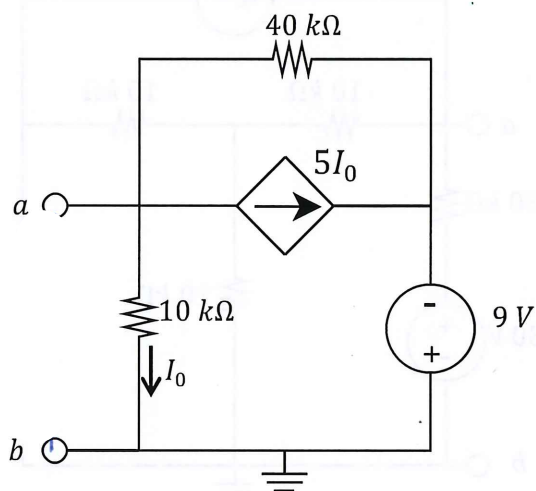

Question 9 [2]		Vraag 9 [2]	
09	Find V_o for the circuit below.	09	Bepaal V_o in onderstaande kringbaan.

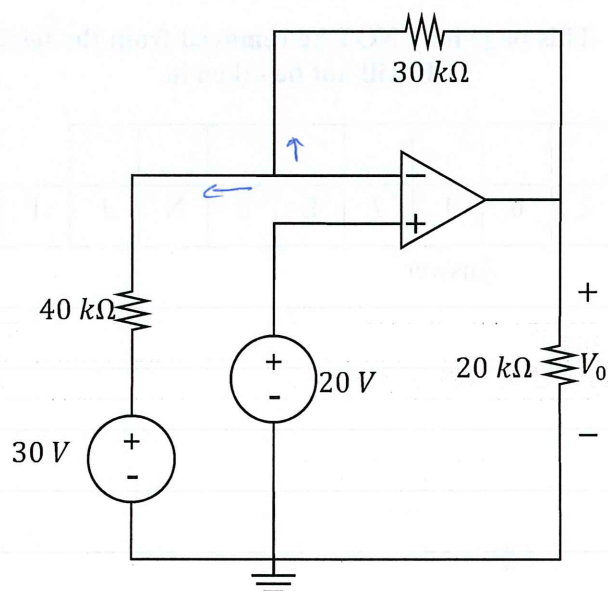

PRACTICE ANSWER SHEET / OEFEN ANTWOORDBLAD

This page may NOT be removed from the test!
It will not be taken in.

Student number

Assessment ID

2	0	1	7	E	B	N	1	1	1	C	2		

Answer

Unit

01	$I =$												
02	$R =$												
03	$a =$												
04	$b =$												
05	$V_{th} =$												
06	$R_{th} =$												
07	$I_N =$												
08	$R_N =$												
09	$V_0 =$												