

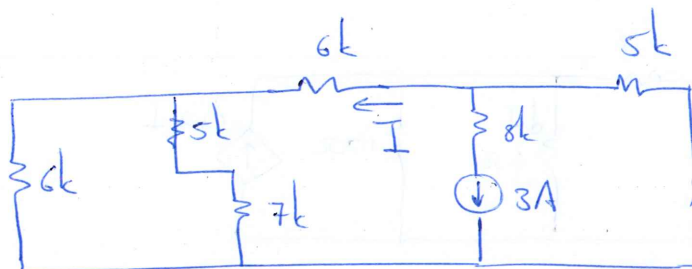


Question 1 [2]	Vraag 1 [2]
01 Use superposition to find the exclusive contribution of the 3A current source to the current I .	01 Maak gebruik van superposisie en bepaal die bydra van die 3 A stroombron tot die stroom I alleenlik.




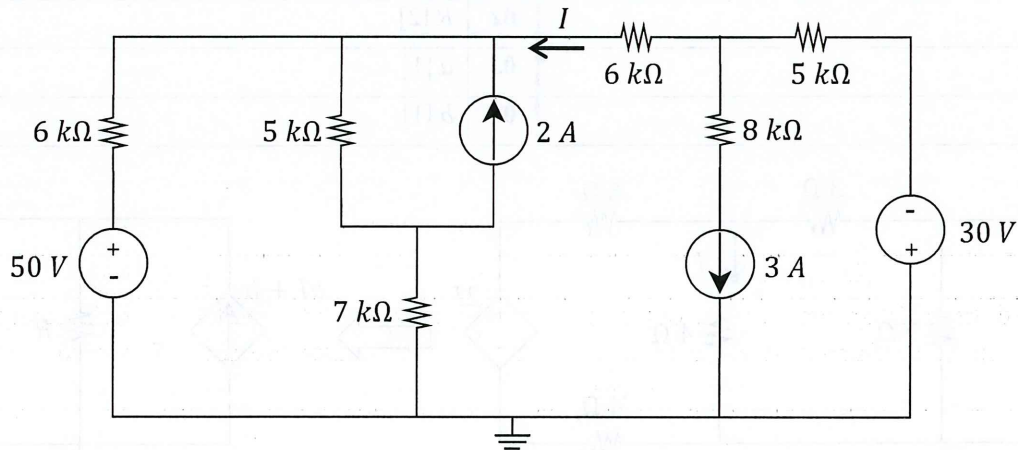

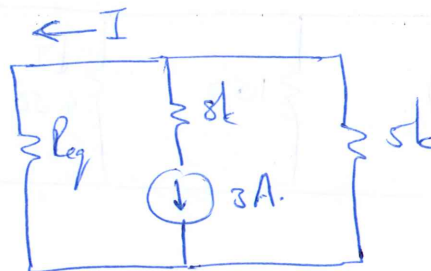
$$\begin{aligned}
 R_{eq} &= 6k + 6k \parallel (5+7)k \\
 &= 6k + \left(\frac{6 \times 12}{6+12} \right) k \\
 &= 10k \Omega
 \end{aligned}$$



$$\begin{aligned}
 \therefore I &= \frac{-3 \times 5k}{10k + 5k} \\
 &= \underline{-1 A}
 \end{aligned}$$

Question 2 - 4 [4]		Vraag 2 - 4 [4]	
Simplify the circuit on the left by means of source transformation so that it looks like the one on the right. Determine:		Vereenvoudig die stroombaan aan die linkerkant met behulp van brontransformasie sodat dit lyk soos die kringbaan aan die regterkant. Bepaal:	
02	R [2]	02	R [2]
03	a [1]	03	a [1]
04	b [1]	04	b [1]

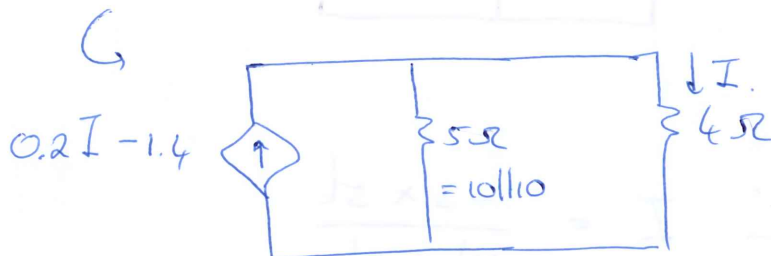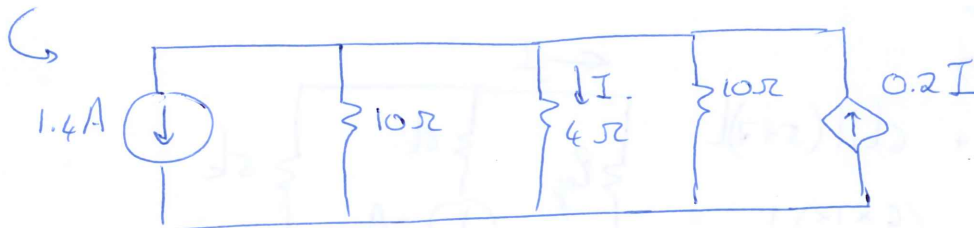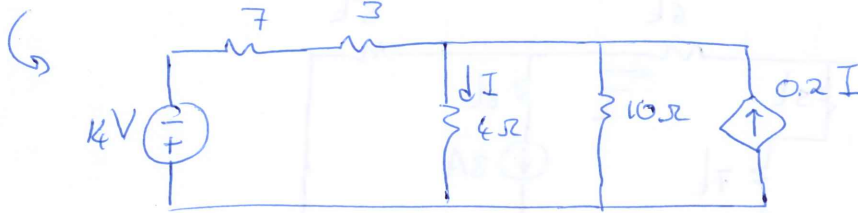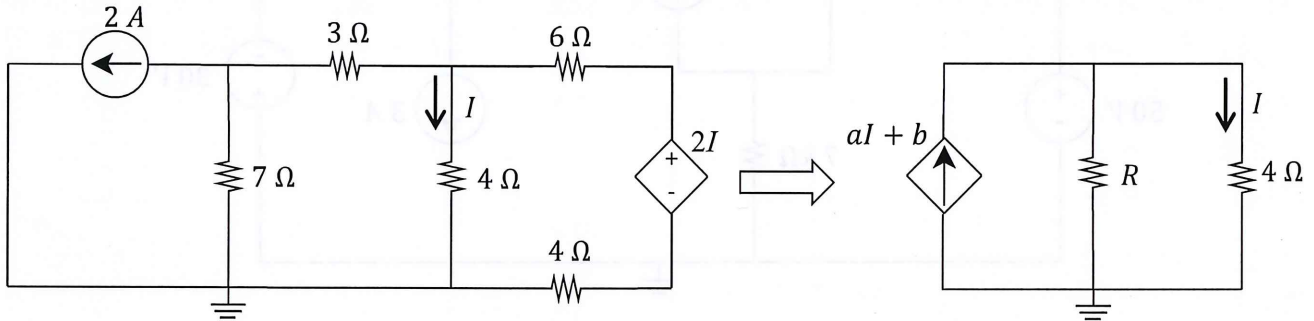


$$R = 5\Omega \quad \checkmark$$


$$a = 0.2 \quad \checkmark$$

$$b = -1.4 \quad \checkmark$$

Question 5 & 6 [4]		Vraag 5 & 6 [4]	
Determine the Thevenin equivalent voltage V_{TH} and resistance R_{TH} w.r.t. terminals $a-b$.		Bepaal die Thevenin ekwivalente spanning V_{TH} en weerstand R_{TH} met verwysing tot terminale a en b .	
05	V_{th}	05	V_{th}
06	R_{th}	06	R_{th}

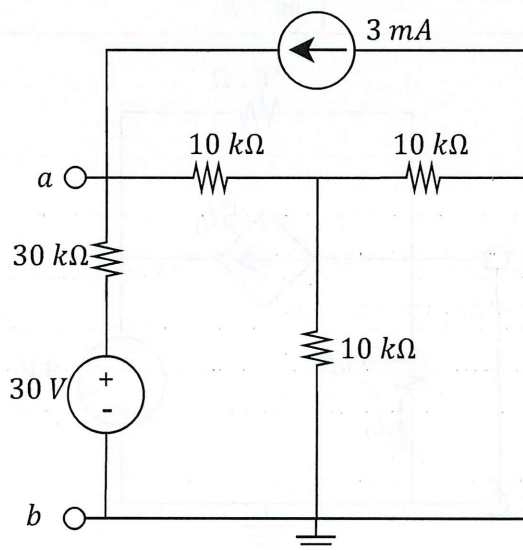

R_{TH}


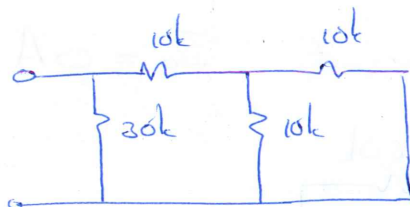


$$R_{eq} = (10 + 10 || 10) || 30$$

$$= (10 + 5) || 30$$

$$= \frac{15 \times 30}{15 + 30} = 10k\Omega$$

V_{TH}

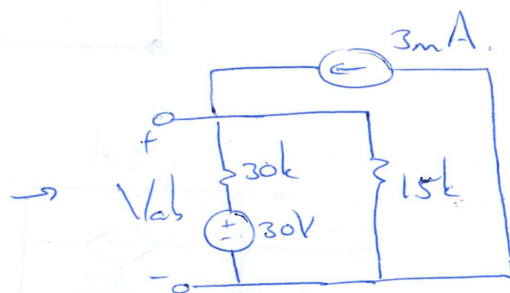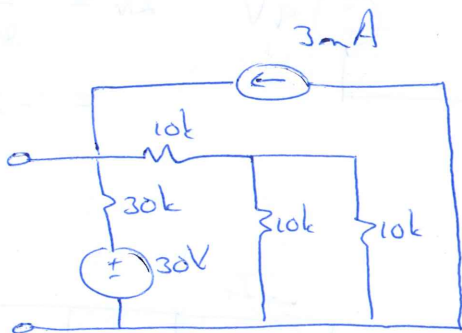

$$\frac{V_{ab} - 30}{30k} + \frac{V_{ab}}{15k} = 3mA$$


($\times 30$)

$$V_{ab} - 30 + 2V_{ab} = 90$$

$$3V_{ab} = 120$$

$$V_{ab} = 40V$$


Question 7 & 8 [4]		Vraag 7 & 8 [4]	
Determine the Norton equivalent current I_N and resistance R_N w.r.t. terminals a - b .		Bepaal die Norton ekwivalente stroom I_N en weerstand R_N met verwysing tot terminale a en b .	
07	I_N	07	I_N
08	R_N	08	R_N

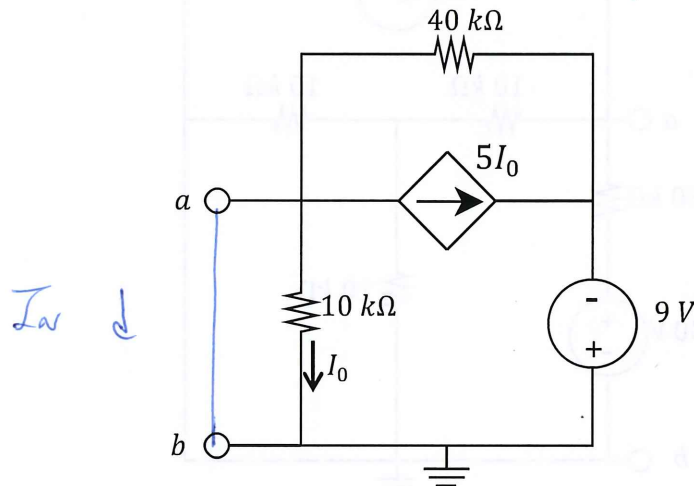


I_N

* Because of short circuit: $I_0 = 0 \text{ A}$.

* Therefore:

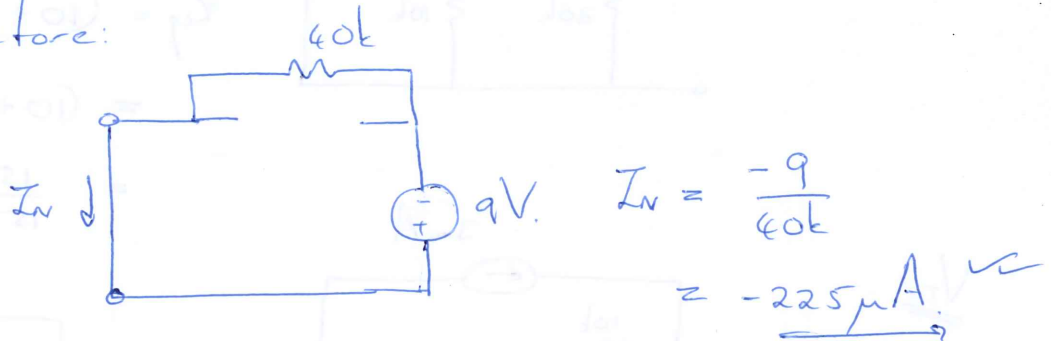

R_N

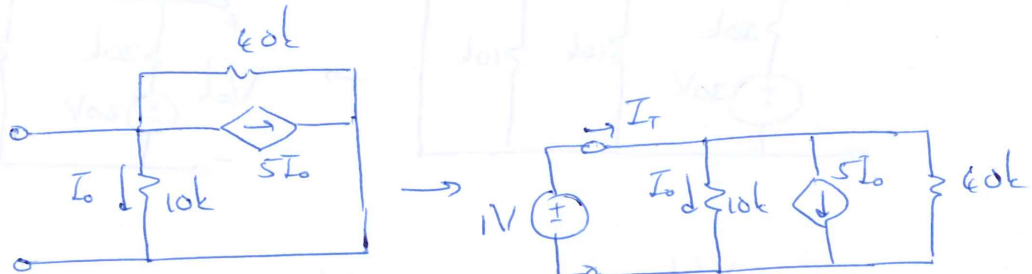


$$I_T = \frac{1}{10k} + \frac{1}{40k} + 5\left(\frac{1}{10k}\right)$$

$$= \frac{6}{10k} + \frac{1}{40k} = \frac{24 + 1}{40k} = \frac{25}{40k}$$

$$R_T = \frac{1}{I_T} = \frac{40k}{25} = 1.6k\Omega \quad \checkmark$$

Question 9 [2]		Vraag 9 [2]	
09	Find V_o for the circuit below.	09	Bepaal V_o in onderstaande kringbaan.

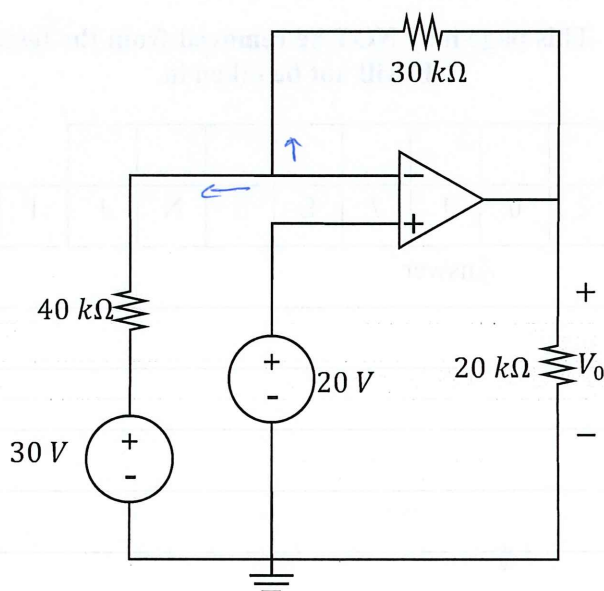

$$\star V_+ = 20V \quad \therefore V_- = 20V$$

$\star$ KCL at V_-

$$\frac{20 - 30}{40k} + \frac{20 - V_o}{30k} = 0$$

$$30k \left(\frac{-10}{40k} \right) = V_o - 20$$

$$V_o = 20 - \frac{30}{4}$$

$$= 20 - 7.5$$

$$= \underline{12.5V} \quad \checkmark \checkmark$$

Memo

PRACTICE ANSWER SHEET /
OEFEN ANTWOORDBLAD

This page may NOT be removed from the test!
It will not be taken in.

Student number

Assessment ID

2	0	1	7	E	B	N	1	1	1	C	2		

Answer

Unit

01	$I = -1$	A
02	$R = 5$	Ω
03	$a = 0.2$	
04	$b = -1.4$	
05	$V_{th} = 40$	V
06	$R_{th} = 10$	$k\Omega$
07	$I_N = -225$	μA
08	$R_N = 1.6$	$k\Omega$
09	$V_0 = 12.5$	V