



EXAM MEMO


June 2020

Exam, Page 1 of 11

2020EBN111E01

Section 1

Questions 1 to 2 [4]

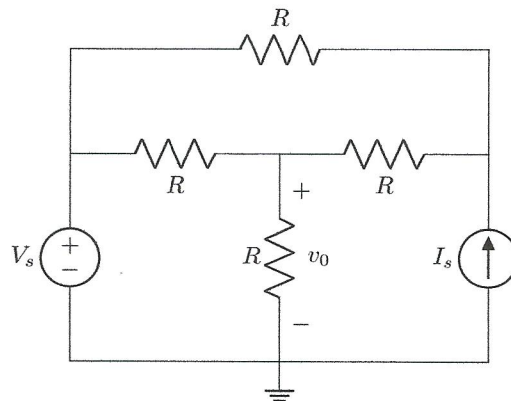

- 01** Determine the contribution to v_0 of the voltage source V_s alone if $I_s = 1 \text{ mA}$ and $R = 6 \text{ k}\Omega$. [2]
(The value of V_s is given in ClickUP.)
- 02** Determine the contribution to v_0 of the current source I_s alone if $V_s = 10 \text{ V}$. [2]
(The values of I_s and R are given in ClickUP.)

01

$V_s = 10 \text{ V}$

$(6+6) \parallel 6 = 4 \text{ k}\Omega$

$V_s = 10 \text{ V}$

$V_0 = V_s \left(\frac{6 \text{ k}}{6 \text{ k} + 4 \text{ k}} \right) = \frac{3}{5} V_s [\text{V}] (*)$

$= \frac{3}{5} (10) = 6 \text{ V}$

02

$R = 6 \text{ k}\Omega$

$I_s = 1 \text{ mA}$


$R = 6 \text{ k}\Omega$

$R \parallel R$



$i_0 = I_s \left(\frac{R}{R + \left(\frac{R}{2} + R \right)} \right) = \frac{I_s R}{\frac{5}{2} R} = \frac{2}{5} I_s$

$V_0 = \frac{2}{5} I_s \times \frac{R}{2} = \frac{I_s R}{5} [\text{V}] (*) = \frac{(1 \text{ mA})(6 \text{ k}\Omega)}{5}$

Question 3 [2]

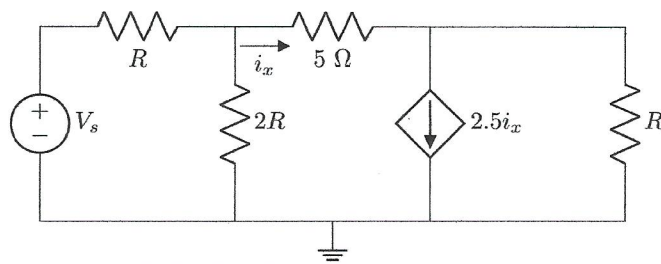

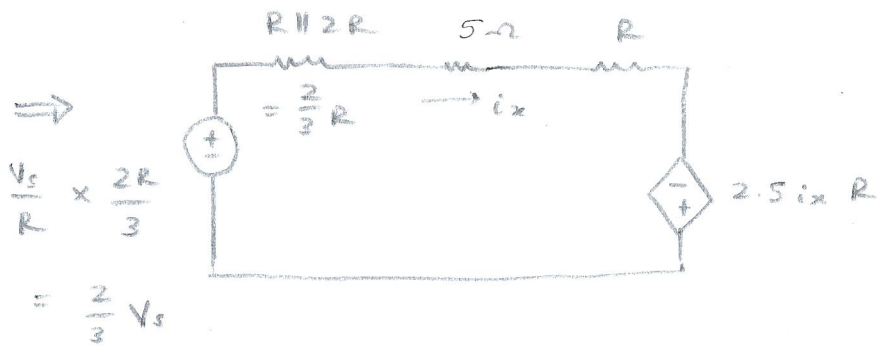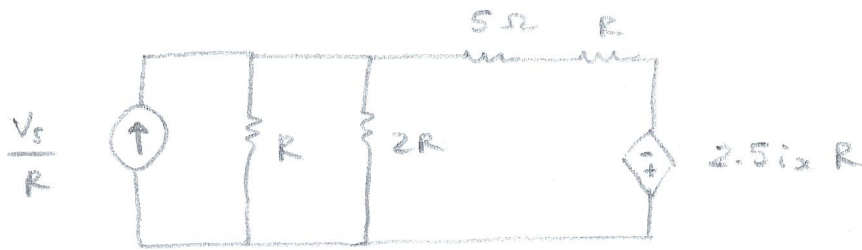- 03 Use source transformation to determine i_x . [2]
(The values of V_s and R are given in ClickUP.)




$$i_x = \frac{\frac{2}{3}V_s + 2.5i_x R}{\frac{2}{3}R + 5 + R}$$

$$i_x = \frac{\frac{2}{3}V_s}{(5 - \frac{5}{6}R)} \quad [A] \quad *$$

$$V_s = 18V, \quad R = 12\Omega:$$

$$I = \frac{18}{12} = 1.5A$$

$$12 \parallel 24 = 8\Omega$$

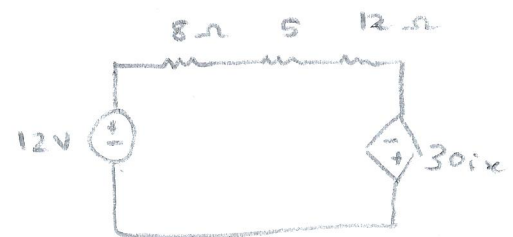

$$i_x = \frac{12 + 30i_x}{25}$$

$$25i_x = 12 + 30i_x$$


$$i_x = -\frac{12}{5}$$

$$\therefore i_x = -2.4A$$

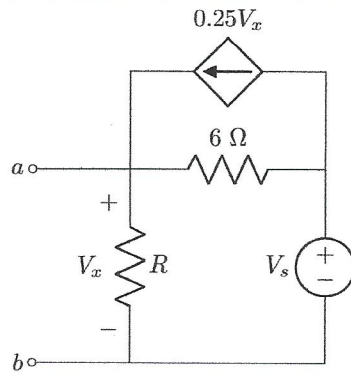Questions 4 to 5 [4]

Find the Thevenin equivalent voltage V_{TH} and Thevenin equivalent resistance R_{TH} , with reference to terminals $a-b$.

(The values of V_s and R are given in ClickUP.)



04 Determine V_{TH} . [2]

05 Determine R_{TH} . [2]

04

$$V_{TH} = V_x$$

$$V_s = 45 \text{ V}$$

$$R = 4 \Omega$$

$$\frac{V_x}{R} + \frac{V_x - V_s}{6} = 0.25 V_x$$

$$\frac{V_x}{4} + \frac{V_x - 45}{6} = 0.25 V_x$$


$$V_{TH} = \frac{V_s R}{6 - 0.5 R} \text{ [V]} (*)$$

$$(x12): 3V_x + 2V_x - 90 = 3V_x$$

$$2V_x = 90$$

$$V_x = 45 \text{ V}$$

05

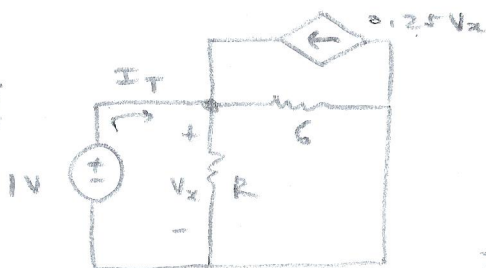

$$V_x = 1 \text{ V}$$

$$I_T = \frac{1}{R} + \frac{1}{6} - 0.25(1)$$

$$R = 3 \Omega$$

$$R_{TH} = \frac{1 \text{ V}}{I_T} = \frac{1}{\left(\frac{1}{R} + \frac{1}{6} - 0.25\right)}$$

$$R_{TH} = \frac{1}{\frac{1}{3} + \frac{1}{6} - 0.25}$$


$$x6R: = \frac{6R}{6 - 0.5R} \text{ [\Omega]} (*)$$

$$R_{TH} = 4 \Omega$$

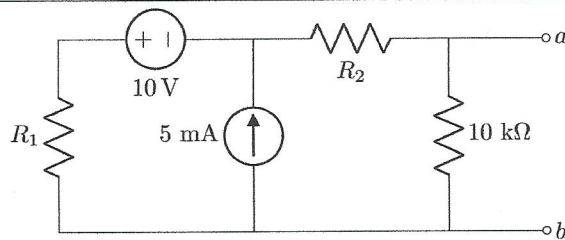Questions 6 to 7 [4]

Find the Norton equivalent current I_N and Norton equivalent resistance R_N , with reference to terminals $a - b$.

(The values of R_1 and R_2 are given in ClickUP.)




06 Determine I_N . [2]

07 Determine R_N . [2]


06

I_N :

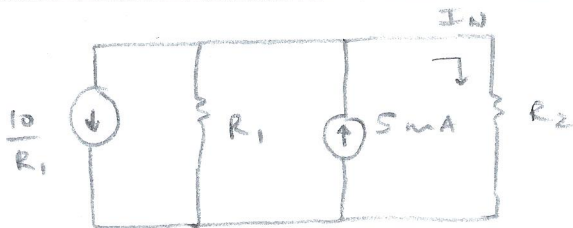

$$R_1 = 7k\Omega$$

$$R_2 = 3k\Omega$$

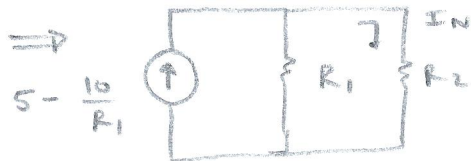


$$I_N = \left(5 - \frac{10}{R_1} \right) \left(\frac{R_1}{R_1 + R_2} \right)$$

$$I_N = \frac{5R_1 - 10}{R_1 + R_2} \text{ [mA]} \quad (*)$$

$$I_N = 3.572 \left(\frac{7k}{10k} \right) = 2.5 \text{ mA}$$

07:

R_N :

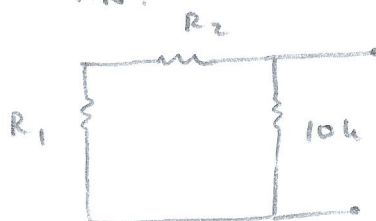

$$R_1 = 7k$$


$$R_2 = 3k$$

$$R_N = (R_1 + R_2) \parallel 10k$$

$$R_N = \frac{10(R_1 + R_2)}{(10 + R_1 + R_2)} \text{ [k}\Omega\text{]} \quad (*)$$

$$R_N = \frac{10(10)}{20} = 5 \text{ k}\Omega$$

Questions 8 to 9 [4]

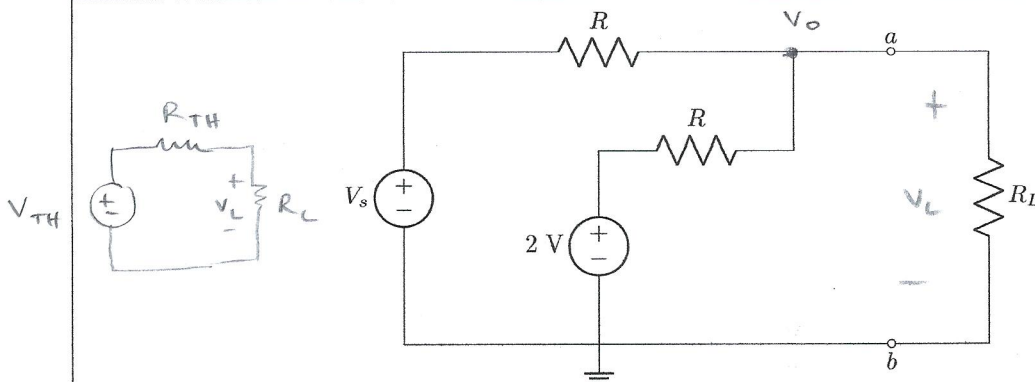

- 08 Determine the voltage V_L across the load R_L for maximum power transfer if $R = 250 \Omega$. [2]
(The value of V_s is given in ClickUP.)
- 09 Determine the value of R such that the maximum power P_{max} is delivered to the load, given that $V_s = V_L = 2 \text{ V}$. [2]
(The value of P_{max} is given in ClickUP.)

08:
$$\frac{V_o - V_s}{R} + \frac{V_o - 2}{R} = 0$$

$$2V_o = V_s + 2$$

$$V_o = \frac{V_s + 2}{2} = V_{TH}$$

$$V_L = \frac{V_{TH}}{2} \therefore V_L = \frac{V_s + 2}{4} \text{ [V]}$$

(max power $R_{TH} = R_L$)

$V_s = 4 \text{ V}$

$V_L = 1.5 \text{ V}$

09:
$$P_{max} = \frac{V_{TH}^2}{4R_{TH}} = \frac{(2V_L)^2}{4\left(\frac{R}{2}\right)} = 1 \text{ (} V_L = 1 \text{ V)}$$

$$P_{max} = 10 \text{ mW}$$


$$R_{TH} = \frac{R}{2}$$

$$P_{max} = \frac{4}{4\left(\frac{R}{2}\right)} = \frac{2}{R}$$

$$R = \frac{2}{P_{max}}$$

$$R = \frac{2}{10 \text{ mW}} = 200 \Omega$$

Question 10 [2]

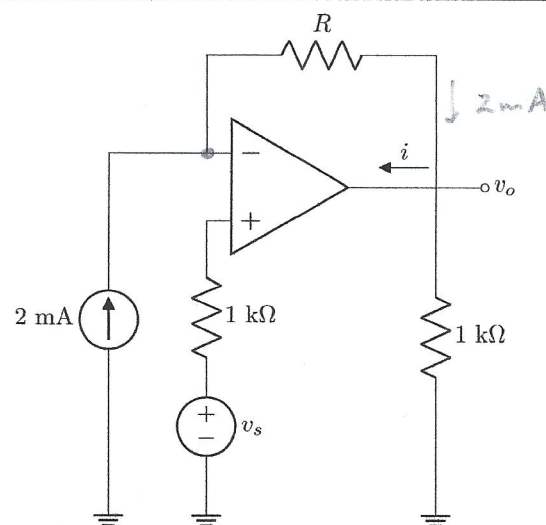

- 10 Find i . [2]
(The values of v_s and R are given in ClickUP.)

$$V_s = 6V$$

$$R = 10k\Omega$$

$$-2mA + \frac{V_s - V_o}{R} = 0$$

$$V_o = V_s - 2mA(R)$$

$$i = 2mA - \frac{V_o}{1k\Omega}$$

$$i = 2mA - \frac{V_s - 2mA(R)}{1k\Omega}$$

$$i = 2 - \frac{V_s + 2R}{1k} [mA] (*)$$


$$-2 + \frac{6 - V_o}{10} = 0$$

$$-20 + 6 = V_o$$


$$V_o = -14$$

$$i = 2 - \left(\frac{-14}{1k} \right)$$


$$i = 16mA$$

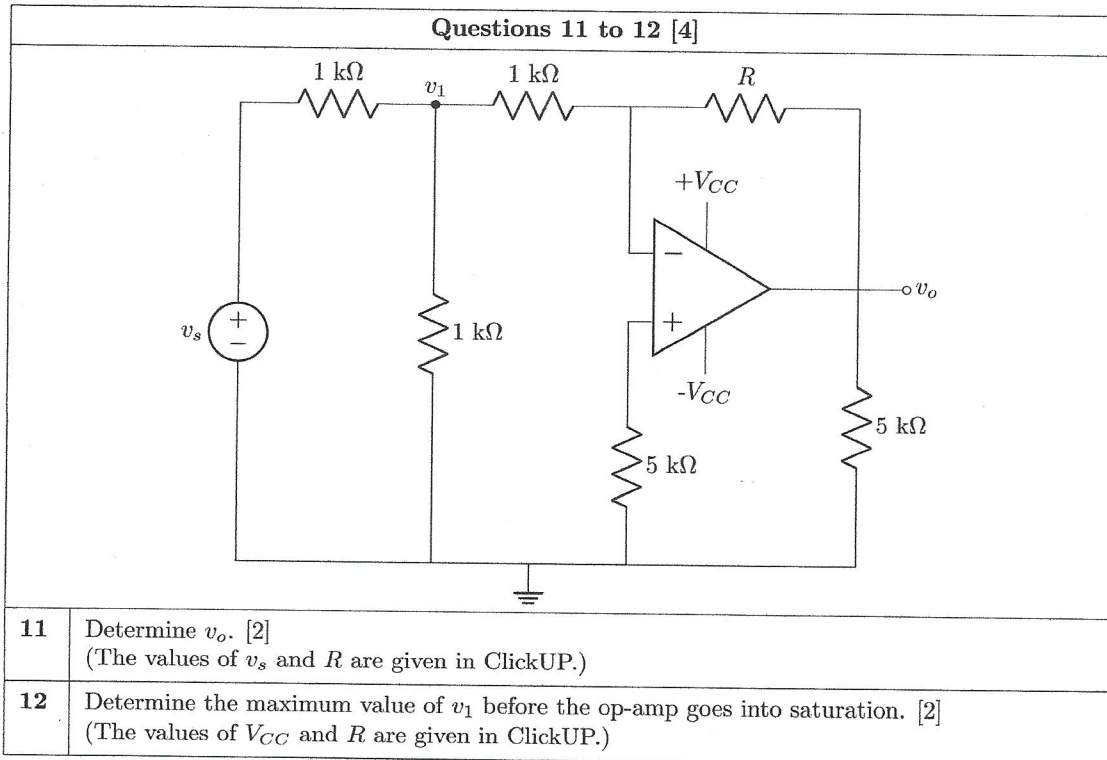11

$$\frac{V_s}{1k}$$

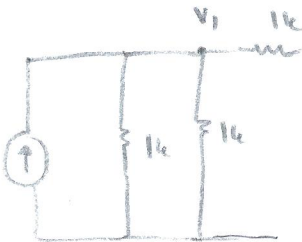

inverting Configuration:

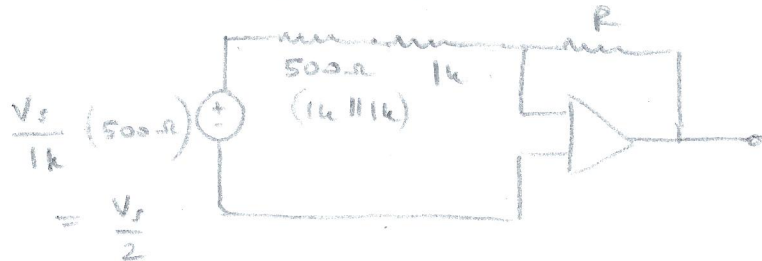

$$v_o = -\frac{V_s}{2} \left(\frac{R}{1.5} \right)$$

$$R = 10k\Omega$$

$$V_s = 3$$

$$v_o = -\frac{V_s R}{3} \quad [V] \quad (*)$$

$$v_o = -\frac{3}{2} \left(\frac{10}{1.5} \right) = -10V$$

12

$$-V_{CC} \leq v_o \leq V_{CC}$$

$$R = 2k\Omega$$


$$V_{CC} = 12V$$

$$-V_{CC} \leq -\frac{R}{1k} v_1 \leq V_{CC}$$


$$v_1 = \frac{V_{CC}}{R} \quad [V] \quad (*) \quad \text{max}$$

$$v_1 = \frac{12}{2} = 6V$$

Question 13 [2]

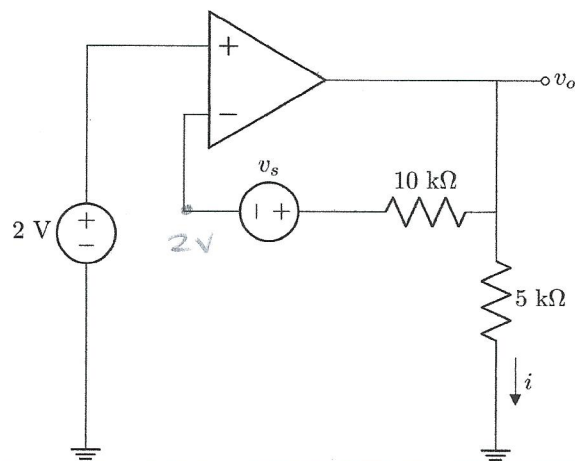

13

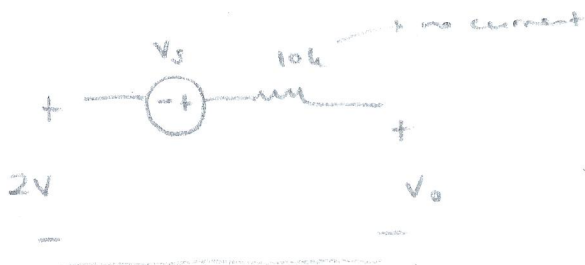Find i . [2](The value of v_s is given in ClickUP.)

$$-2V - V_s + V_o = 0$$

$$V_o = 2 + V_s$$


$$i = \frac{V_o}{5k} = \frac{2 + V_s}{5} \text{ [mA]} \text{ (*)}$$

$$V_s = 3V$$

$$V_o = 2 + 3 = 5$$

$$i = \frac{5}{5} = 1mA$$

Question 14 [2]

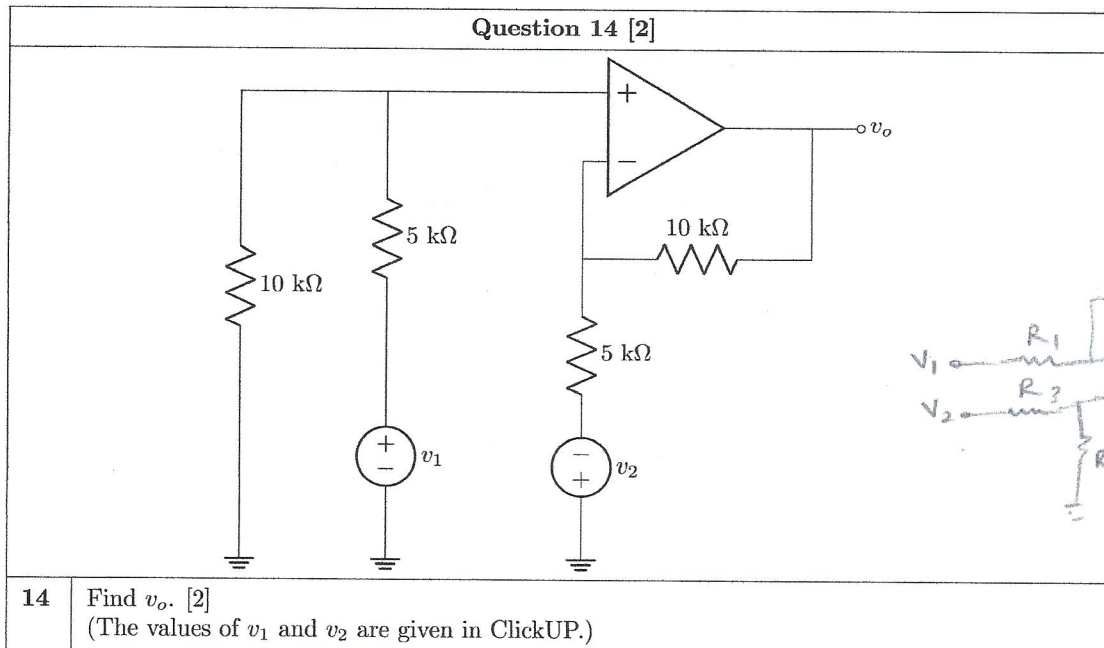

- 14 Find v_o . [2]
(The values of v_1 and v_2 are given in ClickUP.)

difference amplifier:

$$\Rightarrow V_o = 2(V_1 - (-V_2))$$

$$V_o = \frac{R_2}{R_1} (V_1 - (-V_2)) \text{ as } \frac{R_1}{R_2} = \frac{R_3}{R_4}$$

$$V_o = \frac{10k}{5k} (V_1 + V_2)$$


$$V_o = 2(V_1 + V_2) [V] (*)$$

$$\text{if } V_1 = 3V$$

$$V_2 = 2V$$

$$V_o = 10V$$

Questions 15 to 16 [4]

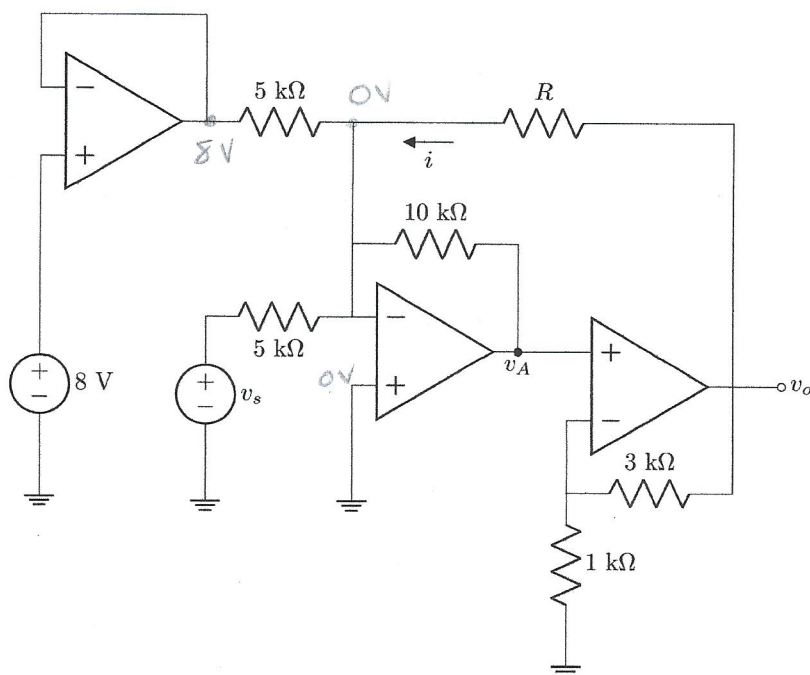

- 15 Determine v_A when $R \rightarrow \infty$. [2]
(The value of v_s is given in ClickUP.)
- 16 Determine i when $v_s = 6$ V. [2]
(The values of R and v_A are given in ClickUP.)

15 summing amp: $V_A = - \left(\frac{10k}{5k} v_s + \frac{10k}{5k} (8) \right)$ $v_s = 6V$

$$V_A = - (2v_s + 16)$$

$$V_A = -2(v_s + 8) [V] \text{ *}$$

$$V_A = - (2(6) + 16)$$

$$V_A = -28V$$

16 non-inverting: $V_o = \left(1 + \frac{3k}{1k} \right) V_A$

and $i = \frac{V_o - 0}{R} \therefore i = \frac{(1+3)V_A}{R} = \frac{4V_A}{R} [mA] \text{ *}$

Total Section 1 : [32]

Grand Total: [32]

$$V_A = 15V$$

$$R = 2k\Omega$$

$$V_o = 4(15)$$


$$= 60$$

$$i = \frac{60}{2} = 30mA$$

Section 3 / Afdeling 3

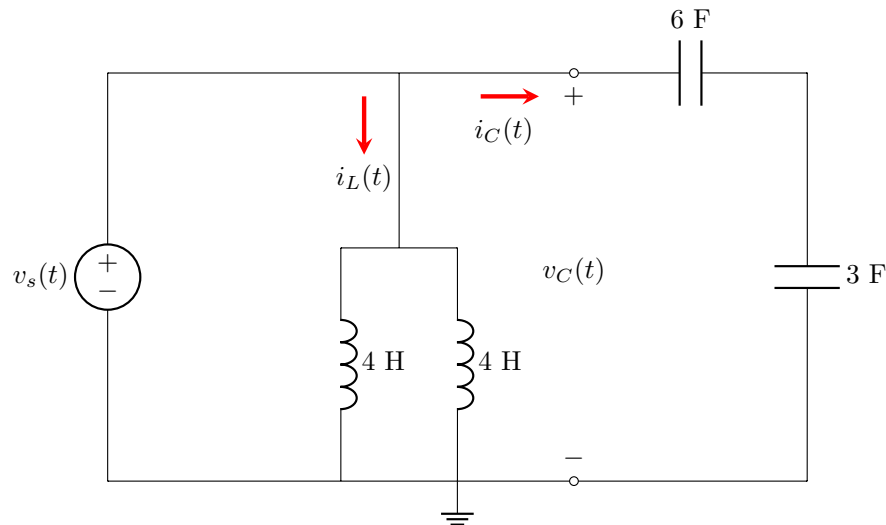Questions 33 to 35 [6]

In the circuit below, $v_s(t) = \alpha e^{-0.2t}$ V and $i_L(0) = 2$ A.
The value of α is given in ClickUP.



33 Determine $v_C(0)$. [2]

34 Determine $i_C(5)$. [2]

35 Determine $i_L(5)$. [2]

33. $v_s(0) = v_C(0) \Rightarrow v_C(0) = \alpha$ (V).


34. $i_C(t) = C \frac{dv}{dt}$, $C = 6F || 3F = 2F$. $v_C(t) = v_s(t)$
 $\Rightarrow i_C(t) = 2 \cdot [\alpha e^{-0.2t}]' = 2\alpha \cdot (-0.2)e^{-0.2t}$
 $= -0.4\alpha e^{-0.2t}$ A

$\Rightarrow i_C(5) = -0.4\alpha e^{-1}$ A.

35. $i_L(t) = \frac{1}{L} \int_0^5 \alpha e^{-0.2t} dt + i_L(0)$. $L = 4 || 4 = 2H$
 $= \frac{\alpha}{2} \cdot \frac{1}{-0.2} \int_0^5 e^{-0.2t} d(-0.2t) + 2$
 $= -2.5\alpha [e^{-0.2t}]_0^5 + 2$
 $= -2.5\alpha (e^{-1} - 1) + 2$
 $= 2.5\alpha - 2.5\alpha e^{-1} + 2$

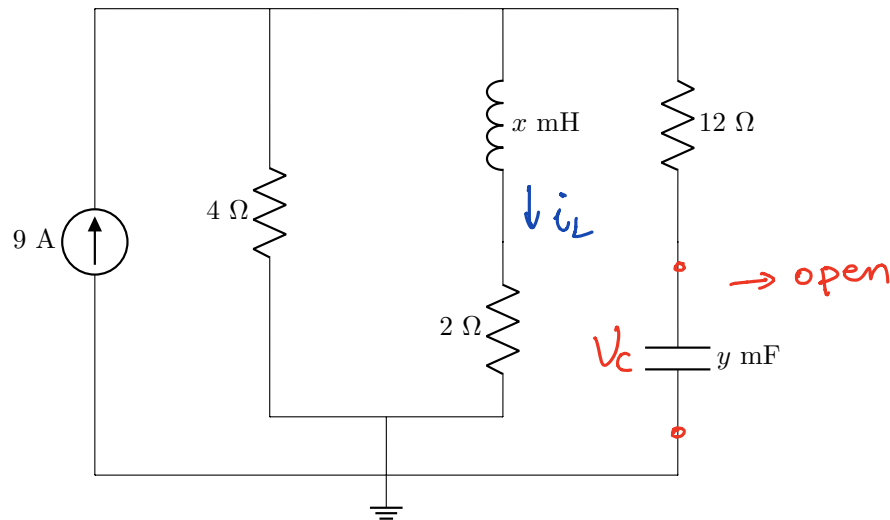Questions 36 to 37 [4]

The circuit below operates under steady-state DC conditions.
The values x and y are given in ClickUP.



36 Determine the energy stored in the inductor w_L . [2]

37 Determine the energy stored in the capacitor w_C . [2]

$$i_L = 9 \cdot \frac{4}{6} = 6A$$

$$V_C = 2 \times 6 = 12V$$

$$\textcircled{36} \Rightarrow w_L = \frac{1}{2} L i^2 = \frac{1}{2} x \cdot 10^{-3} \times 6^2 = 0.018x \text{ (J)}$$

$$\textcircled{37} w_C = \frac{1}{2} C V^2 = \frac{1}{2} y \cdot 10^{-3} \cdot 12^2 = 0.072y \text{ (J)}.$$

Question 38 [2]

Sinusoids $v_1(t)$ and $v_2(t)$ have the following general form: $A \cos(\omega t + \phi)$.


It is known that:

- v_2 leads v_1 by σ° .
- v_2 lags v_3 by 100° .

The value of σ is given in ClickUP.

38 What is the phase angle θ between v_1 and v_3 such that $0 \leq \theta \leq 180^\circ$. [2]
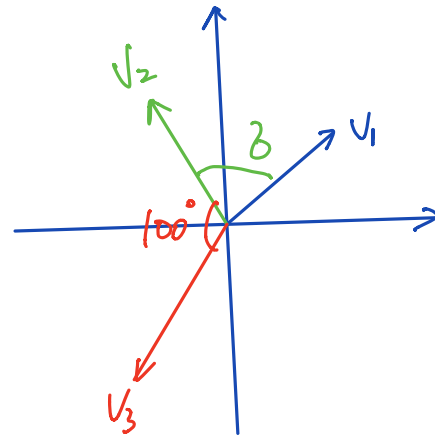
$$\begin{aligned} \theta + \sigma + 100 &= 360^\circ \\ \Rightarrow \theta &= 260^\circ - \sigma. \\ 0 &\leq 260^\circ - \sigma \leq 180^\circ \\ \Rightarrow 80^\circ &\leq \sigma \leq 260^\circ. \end{aligned}$$



Question 39 [2]

A current source of $i(t) = 2\cos(100t + 90^\circ)$ A is connected in parallel with a resistor of $R \Omega$, a capacitor of $C \mu\text{F}$, and an inductor of $L \text{ mH}$. Determine the phasor voltage $\mathbf{V}$ across the current source, assuming the sign of the voltage is positive. Values of R , C , and L are given in ClickUP.

39 (a) If $\mathbf{V} = A + jB$, what is the real part A ? [2]

39 (b) If $\mathbf{V} = A + jB$, what is the imaginary part B ? [2]

$$I = 2 \angle 90^\circ = j2. \quad \omega = 100.$$

$$Z_R = R$$

$$Z_L = j\omega L = j \cdot 100 \cdot L \times 10^{-3} = j0.1L$$

$$Z_C = -j \frac{1}{\omega C} = -j \frac{1}{100 \times C \times 10^{-6}} = -j \frac{10^4}{C}$$


$$Z_1 = Z_L || Z_C = \frac{j0.1L \cdot -j \frac{10^4}{C}}{j0.1L - j \frac{10^4}{C}} = \frac{\frac{10^3 L}{C}}{j(0.1L - \frac{10^4}{C})}$$

$$= \frac{10^3 L}{j(0.1LC - 10^4)}$$

$$Z_2 = Z_R || Z_1 \quad (\text{use matlab})$$

$$\Rightarrow V = j2 \cdot Z_2 \quad (\text{use matlab}).$$

39

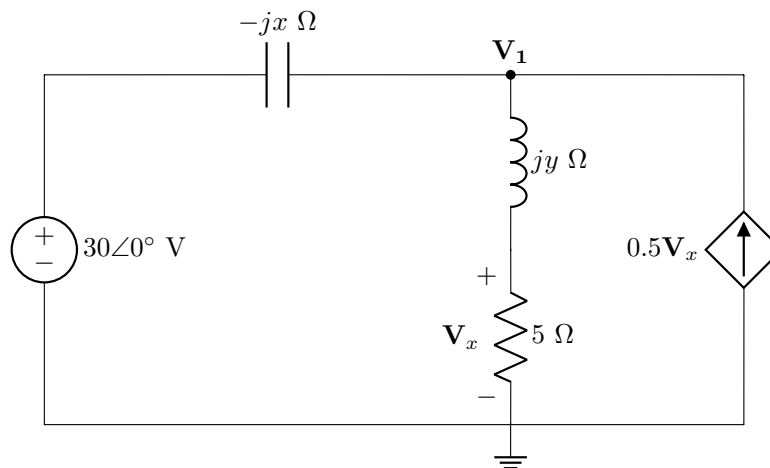Question 40 [2]Find $\mathbf{V}_1$ in the circuit below.The values x and y are given in ClickUP.40 (a) If $\mathbf{V}_1 = C + jD$, what is the real part C ? [2]40 (a) If $\mathbf{V}_1 = C + jD$, what is the imaginary part D ? [2]

$$\frac{V_1 - 30}{-jx} + \frac{V_1}{5+jy} - 0.5 \cdot V_1 \cdot \frac{5}{5+jy} = 0$$

$$\frac{V_1 - 30}{-jx} = \frac{1.5V_1}{5+jy}$$

$$\Rightarrow -j1.5x V_1 = (5+jy)V_1 - 30(5+jy)$$


$$(5+jy-j1.5x)V_1 = 30(5+jy)$$

$$\Rightarrow V_1 = \frac{30(5+jy)}{5+j(y-1.5x)}$$

40

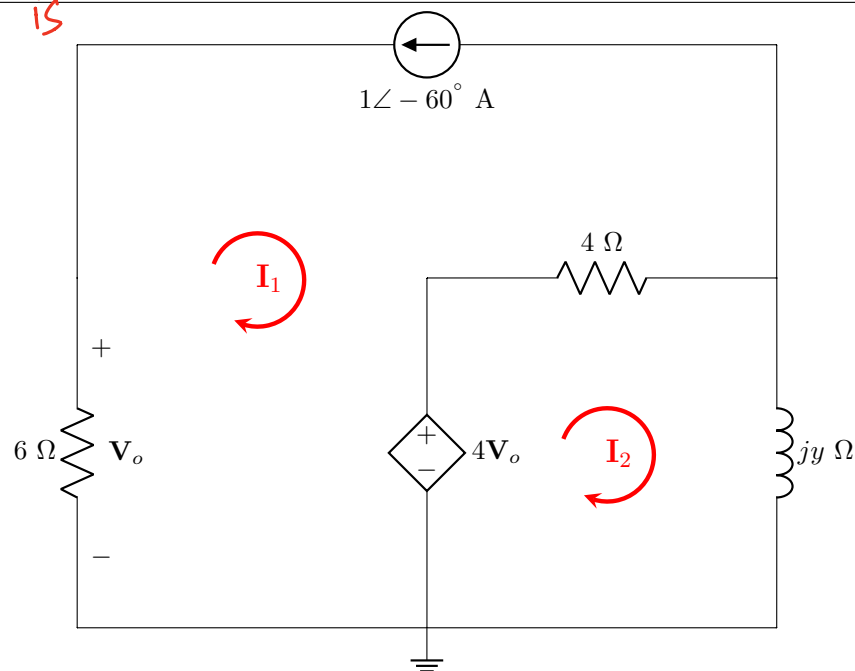Question 41 [2]

In the circuit below, use **mesh** analysis to find $\mathbf{I}_2$.
The value of y are given in ClickUP.



41 (a) If $\mathbf{I}_2 = E + jF$, what is the real part E ? [2]

41 (b) If $\mathbf{I}_2 = E + jF$, what is the imaginary part F . [2]

$$I_1 = -1 \angle -60^\circ, \quad V_o = 6 \angle -60^\circ$$

$$-4V_o + 4(I_2 - I_1) + jyI_2 = 0$$


$$\Rightarrow -24 \angle -60^\circ + (4 + jy)I_2 + 4 \angle -60^\circ = 0$$

$$\Rightarrow (4 + jy)I_2 = 20 \angle -60^\circ$$

$$(41) \quad I_2 = \frac{20 \angle -60^\circ}{4 + jy}$$

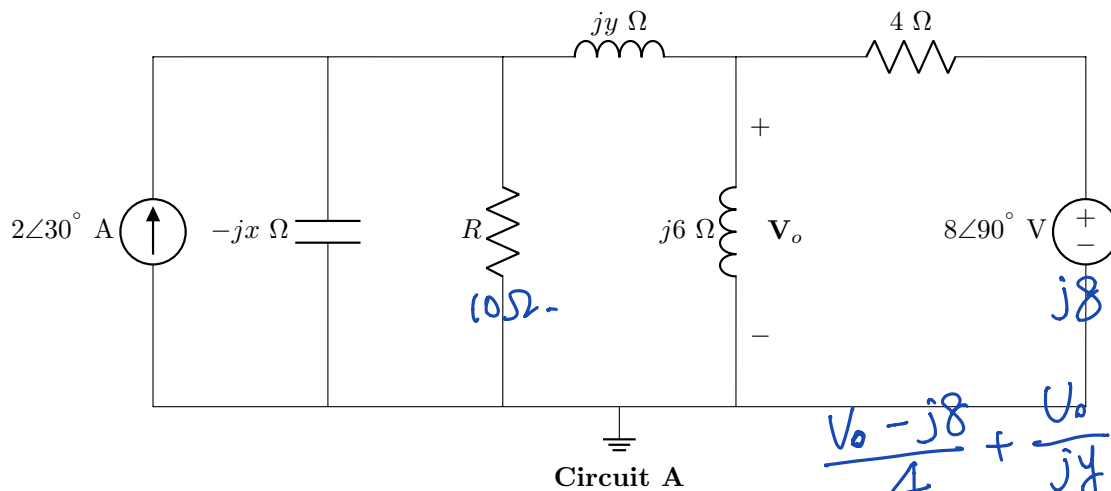Questions 42 to 44 [6]


In **Circuit A**, when $R = 0 \Omega$, find the exclusive contribution, $\mathbf{V}_o^1$ from the voltage source to $\mathbf{V}_o$. The values x and y are given in ClickUP.



42 (a) If $\mathbf{V}_o^1 = G + jH$, what is the real part G ? [2]

42 (b) If $\mathbf{V}_o^1 = G + jH$, what is the imaginary part H ? [2]

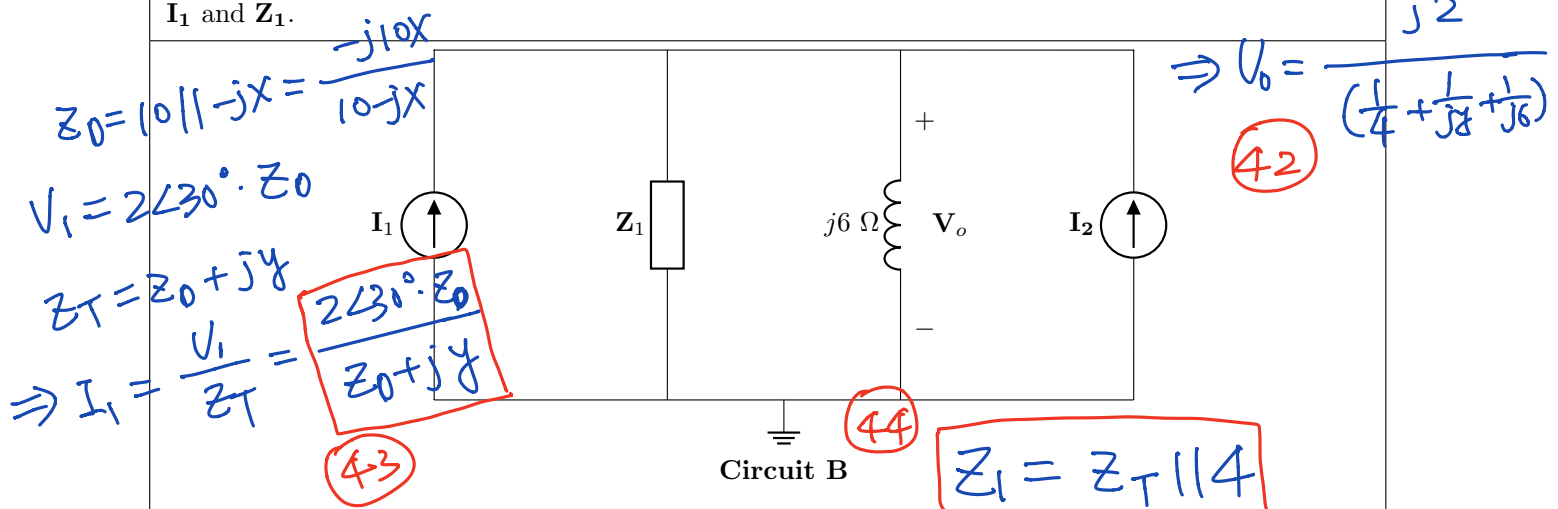When $R = 10 \Omega$, the Circuit A is transformed to **Circuit B** using source transformation. Determine $\mathbf{I}_1$ and $\mathbf{Z}_1$.



43 (a) If $\mathbf{I}_1 = K + jL$, what is the real part K ? [2]


43 (b) If $\mathbf{I}_1 = K + jL$, what is the imaginary part L ? [2]

44 (a) If $\mathbf{Z}_1 = P + jQ$, what is the real part P ? [2]

44 (b) If $\mathbf{Z}_1 = P + jQ$, what is the imaginary part Q ? [2]

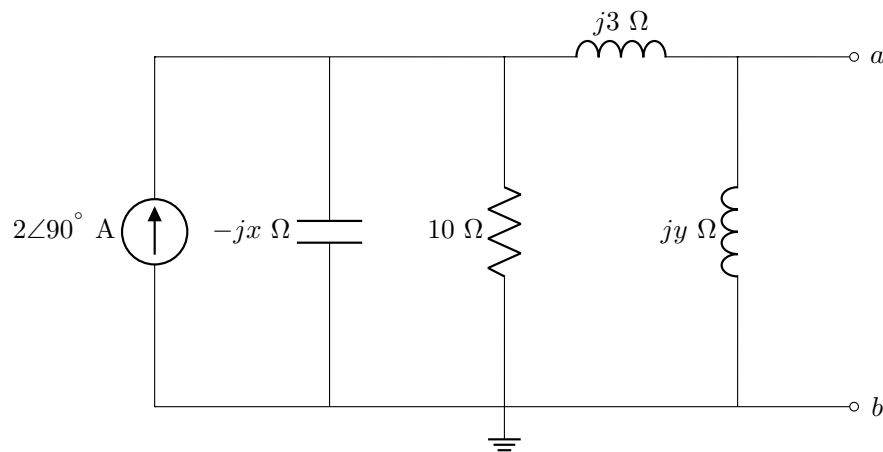Questions 45 to 46 [4]

In the circuit below, find the Norton equivalent current $\mathbf{I_N}$ and impedance $\mathbf{Z_N}$ at terminals a-b. The values x and y are given in ClickUP.



- | | |
|----|---|
| 45 | (a) If $\mathbf{I_N} = S + jT$, what is the real part S ? [2] |
| 45 | (b) If $\mathbf{I_N} = S + jT$, what is the imaginary part T ? [2] |
| 46 | (a) If $\mathbf{Z_N} = U + jV$, what is the real part U ? [2] |
| 46 | (b) If $\mathbf{Z_N} = U + jV$, what is the imaginary part V ? [2] |


(45)
$$Z_1 = -jx \parallel 10 = \frac{-j10x}{10 - jx}$$

$$Z_2 = Z_1 + j3, \quad Z_N = jy \parallel Z_2.$$

(46)
$$I_N = j2 \cdot \frac{Z_1}{Z_1 + j3}.$$

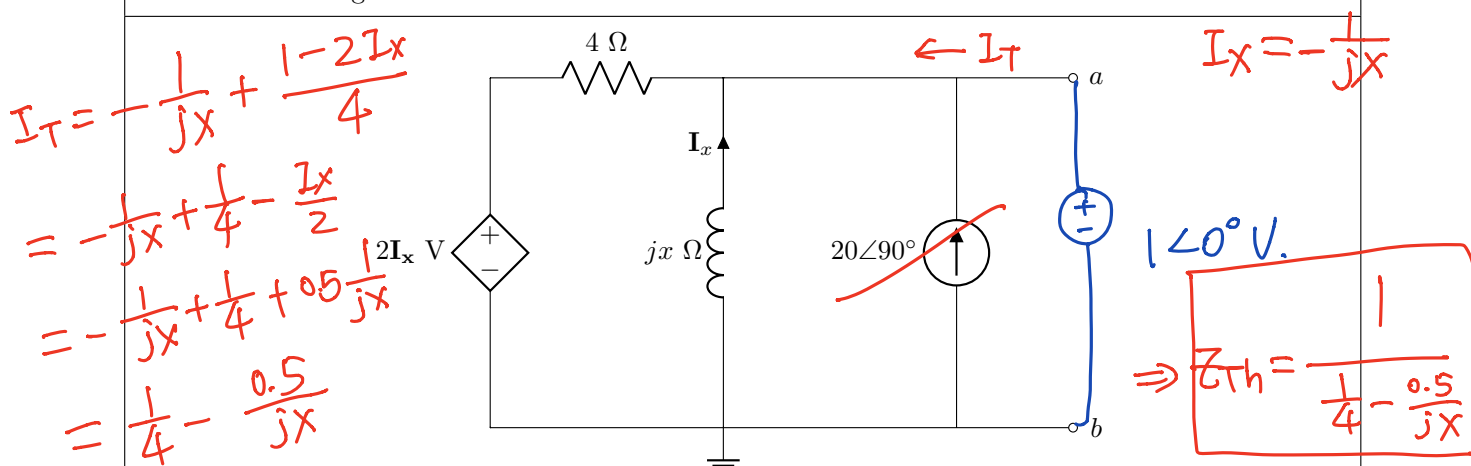Questions 47 to 48 [4]

In the circuit below, find the Thévenin equivalent voltage V_{Th} and impedance Z_{Th} at terminals a-b. The value of x is given in ClickUP.



- | | |
|----|---|
| 47 | (a) If $V_{Th} = X_1 + jY_1$, what is the real part X_1 ? [2] |
| 47 | (b) If $V_{Th} = X_1 + jY_1$, what is the imaginary part Y_1 ? [2] |
| 48 | (a) If $Z_{Th} = X_2 + jY_2$, what is the real part X_2 ? [2] |
| 48 | (b) If $Z_{Th} = X_2 + jY_2$, what is the imaginary part Y_2 ? [2] |

$$\frac{V_{Th} - 2I_x}{4} + \frac{V_{Th}}{jx} - j20 = 0$$

$$\Rightarrow \frac{V_{Th} - 2 \cdot (-\frac{V_{Th}}{jx})}{4} + \frac{V_{Th}}{jx} = j20$$

$$\frac{V_{Th}}{4} + 0.5 \frac{V_{Th}}{jx} + \frac{V_{Th}}{jx} = j20$$

$$(\frac{1}{4} + \frac{1.5}{jx}) V_{Th} = j20 \Rightarrow V_{Th} = \frac{j20}{\frac{1}{4} + \frac{1.5}{jx}}$$

(47)

Total Section 3 / Totaal Afdeling 3: [32]

Grand Total: [96]