
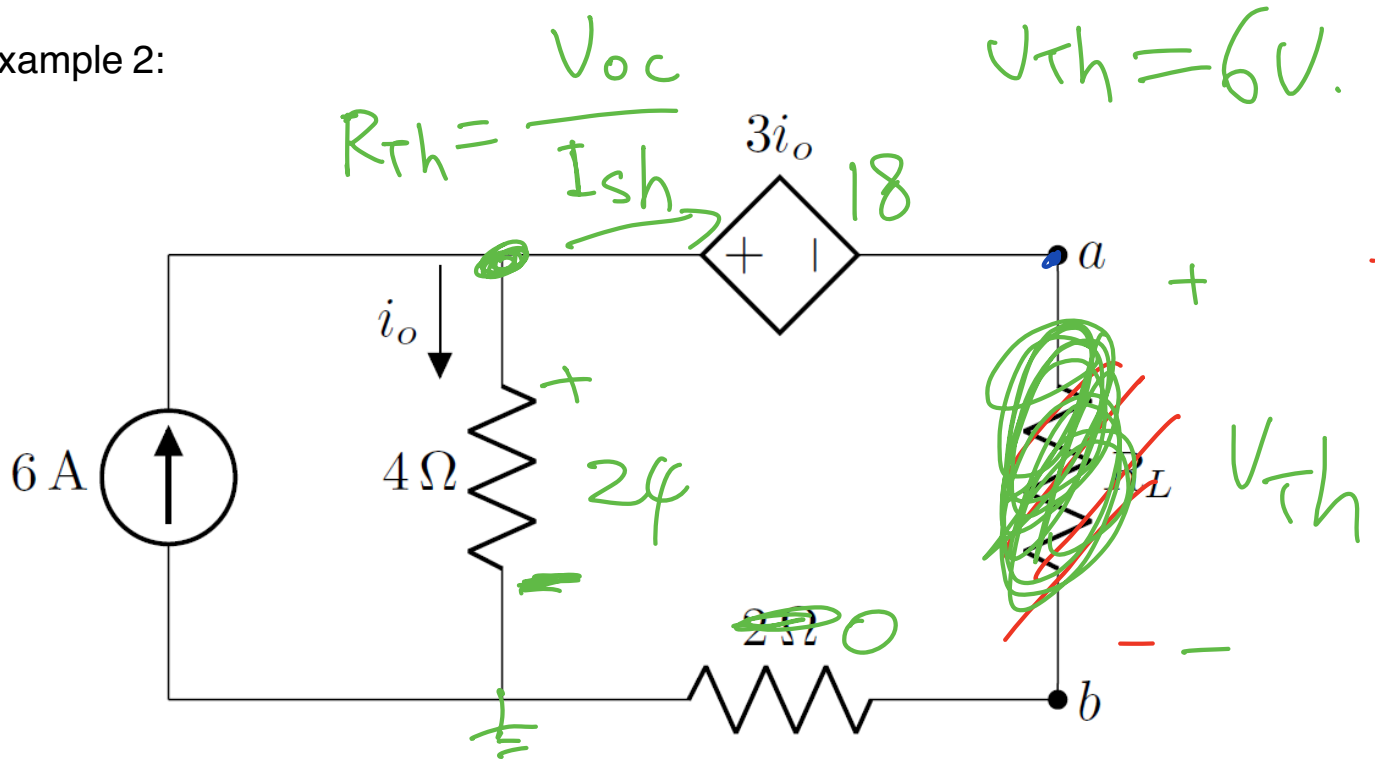


Example 2:

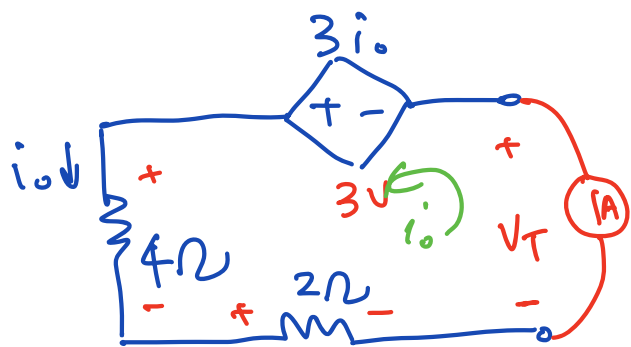

Find R_{th} in reference to terminals a-b across an unknown load R_L :




$$R_{Th} = \frac{V_T}{1A} = V_T$$

$$i_o = 1A.$$

$$-V_T - 3 + 4 + 2 = 0 \Rightarrow \underline{V_T = 3V.}$$

$$R_{Th} = 3\Omega.$$

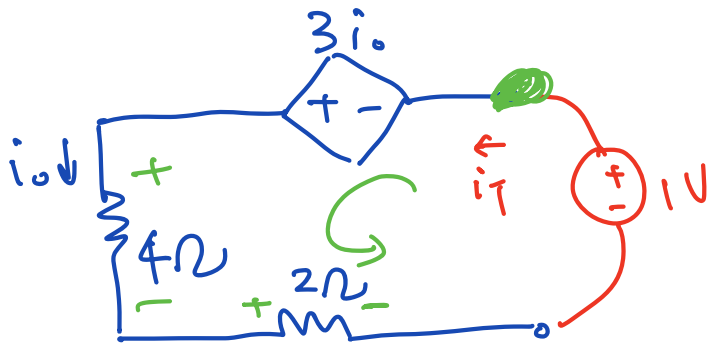

$$R_{Th} = \frac{1V}{i_T}$$

$$\underline{i_T = i_o.}$$

$$\underline{-3i_T + 6i_T - 1 = 0 \Rightarrow i_T = \frac{1}{3} \Rightarrow R_{Th} = 3\Omega}$$