

L#04: Kirchhoff's laws

2018-02-12

Kirchhoff's current law (KCL): algebraic sum of currents entering or leaving a node or (closed boundary) is zero.

Mathematical description:


$$\sum_{n=1}^N i_n = 0$$

i_n : current in n th branch.

N : number of currents.


Sign Convention:

i_n : + ; out: -



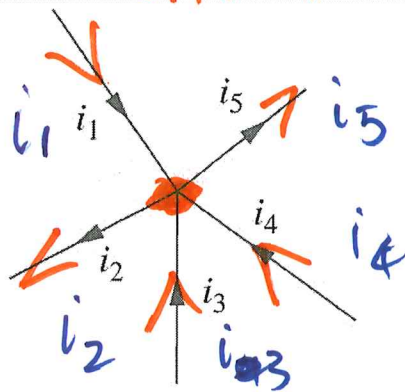


$$i_1 - i_2 + i_3 + i_4 - i_5 = 0$$
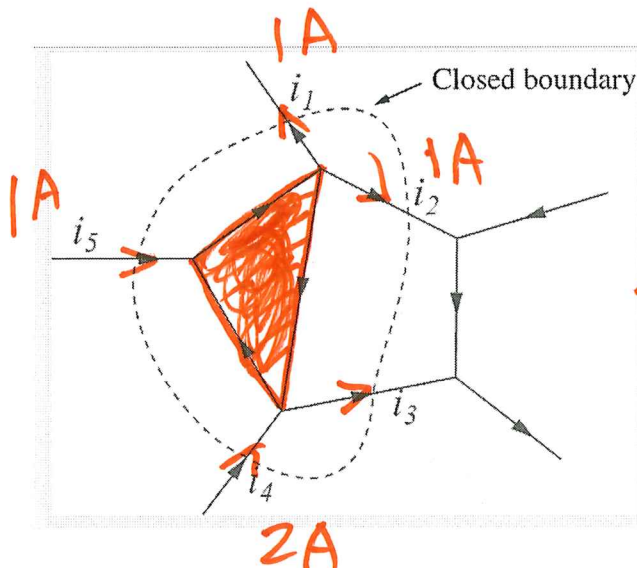
$$\frac{i_1 + i_3 + i_4}{\text{in}} = \frac{i_2 + i_5}{\text{out}}$$




Current sources in parallel

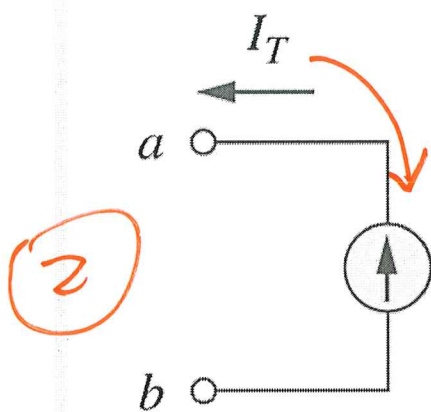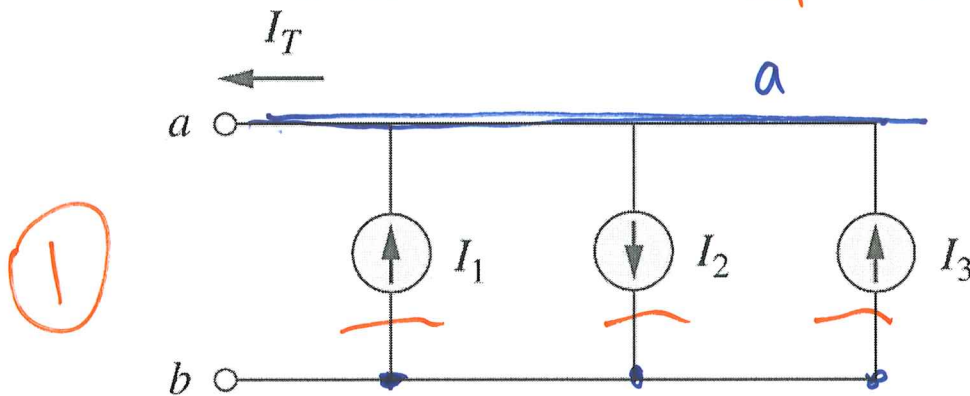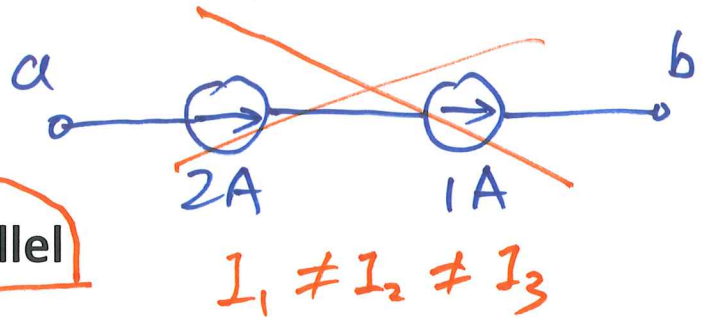

$$I_T^1 = I_1 - I_2 + I_3$$

I_T^1


$$\underline{I_T^1 = -I_T^2}$$

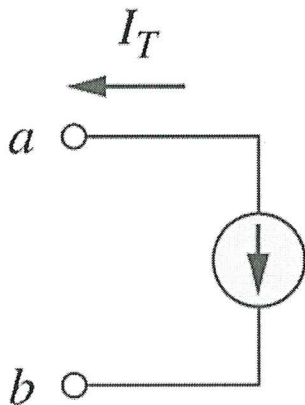

$$I_T^2 = -I_1 + I_2 - I_3$$

$$= -(I_1 - I_2 + I_3)$$

KCL: resistive networks

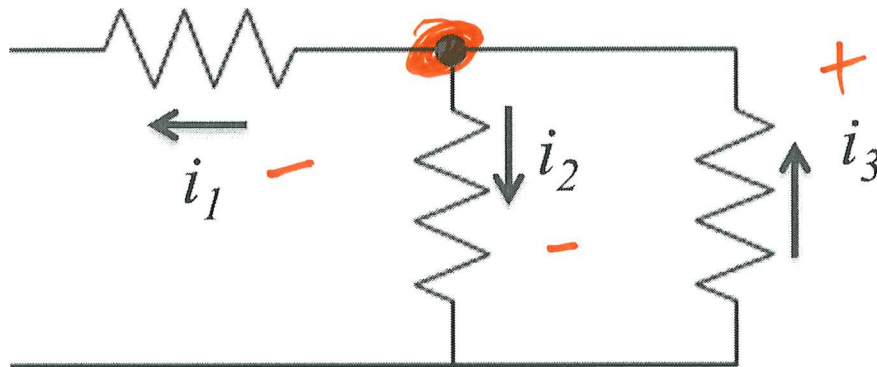


$$-i_1 - i_2 + i_3 = 0. \quad (1)$$

$$i_3 = i_1 + i_2 \quad (2)$$

Kirchhoff's voltage law (**KVL**): algebraic sum of voltages around a closed loop is 0.

$$-V_1 + V_2 + V_3 - V_4 + V_5 = 0$$

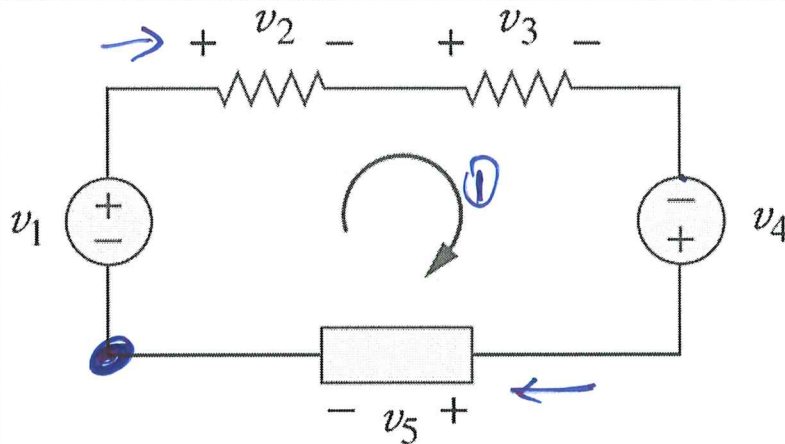

Sign Convention: ① we let current flows clockwise; ② current enters '+' polarity; ③ ~~if~~ when meet '-', note '-'.
Mathematical Description: when meet '+', note '+'.
 when meet '-', note '-'.


$$\sum_{i=1}^N V_i = 0$$

V_i : voltage across i th element.

N : number of elements.

Sign convention applies!

Voltage source in series

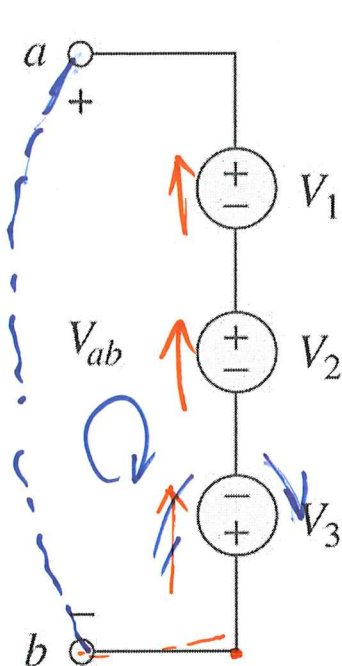


$$\textcircled{1} -V_{ab} + V_1 + V_2 - V_3 = 0.$$

$$V_{ab} = V_1 + V_2 - V_3$$


$$\textcircled{2} V_{ab} = V_a - V_b, \quad \underline{V_b = 0.}$$

$$V_a = -V_3 + V_2 + V_1.$$

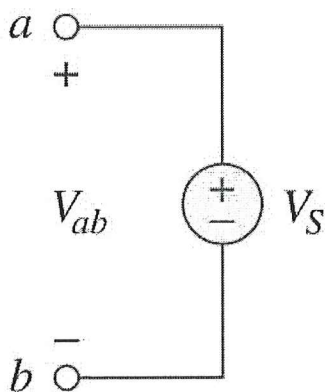

$$-V_{ab} + V_s = 0$$

$$\Rightarrow V_{ab} = \underline{V_s}$$

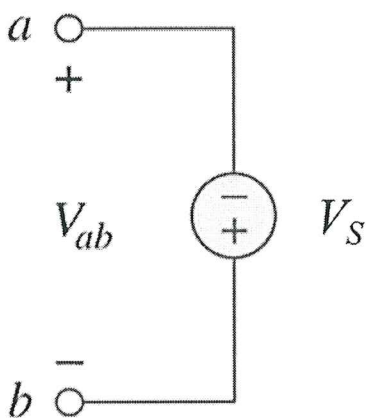


$$-V_{ab} - V_s = 0$$

$$\Rightarrow V_s = \underline{-V_{ab}.}$$

Example #1:

Find i , v_1 and v_2 .

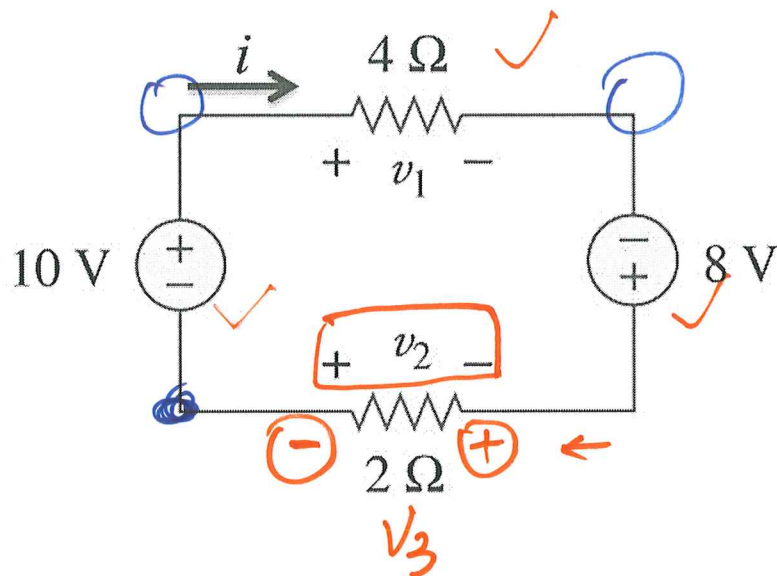

$$\text{KVL: } -10 + v_1 - 8 + v_3 = 0$$

$$v_1 + v_3 = 18$$

$$4i + 2i = 18 \Rightarrow \underline{i = 3\text{A}}$$


$$v_1 = 4i = 12\text{V.}$$

$$\textcircled{v_3} = 2i = 6\text{V.}$$

$$v_2 = -v_3 = -6\text{V.}$$

Example #2:

Find current i_o and voltage v_o .

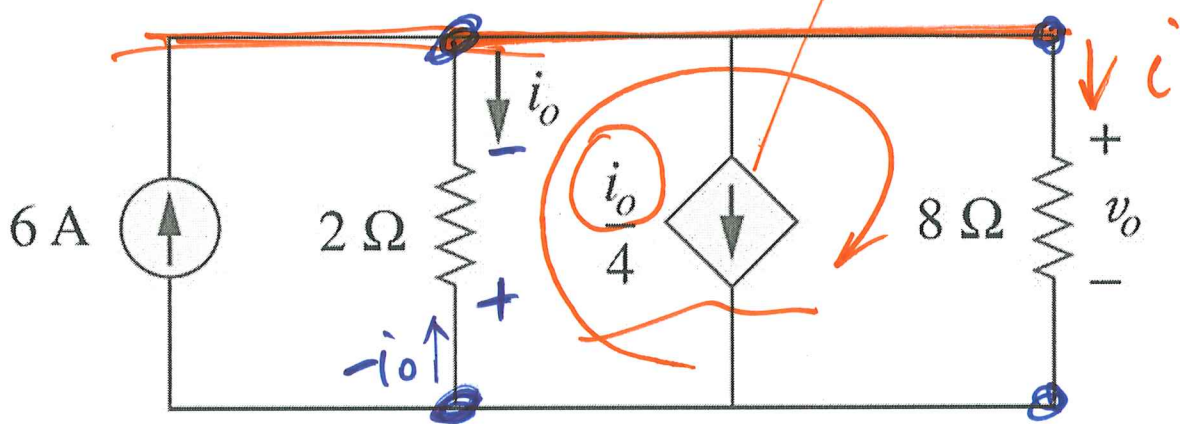

$$6A - i_o - \frac{i_o}{4} - \frac{V_o}{8} = 0$$

$$-2i_o + V_o = 0 \Rightarrow \underline{V_o = 2i_o}$$


$$6 - i_o - \frac{i_o}{4} - \frac{i_o}{4} = 0 \Rightarrow$$

$$1.5i_o = 6 \Rightarrow i_o = 4A$$

$$V_o = 8V.$$

Example #3:

Calculate V_1 and V_2 .

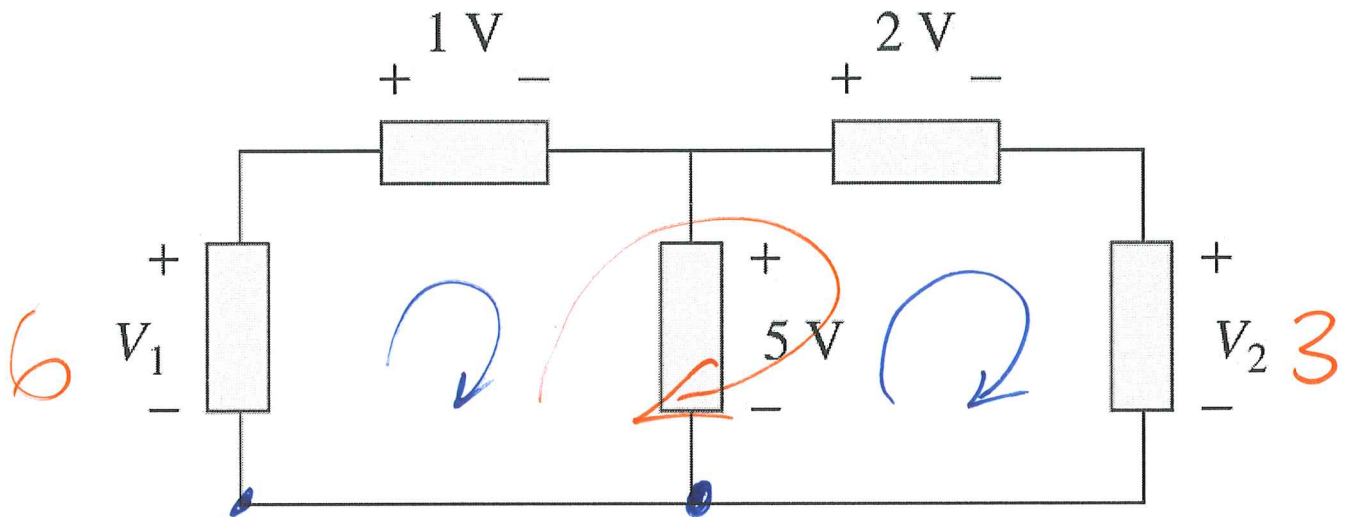


$$-V_1 + 1 + 5 = 0 \Rightarrow V_1 = 6V.$$

$$-5 + 2 + V_2 = 0 \Rightarrow V_2 = 3V.$$

$$\underline{-6 + 1 + 2 + 3 = 0} \quad \checkmark$$

Example #4:

Determine I and V_{ab} .

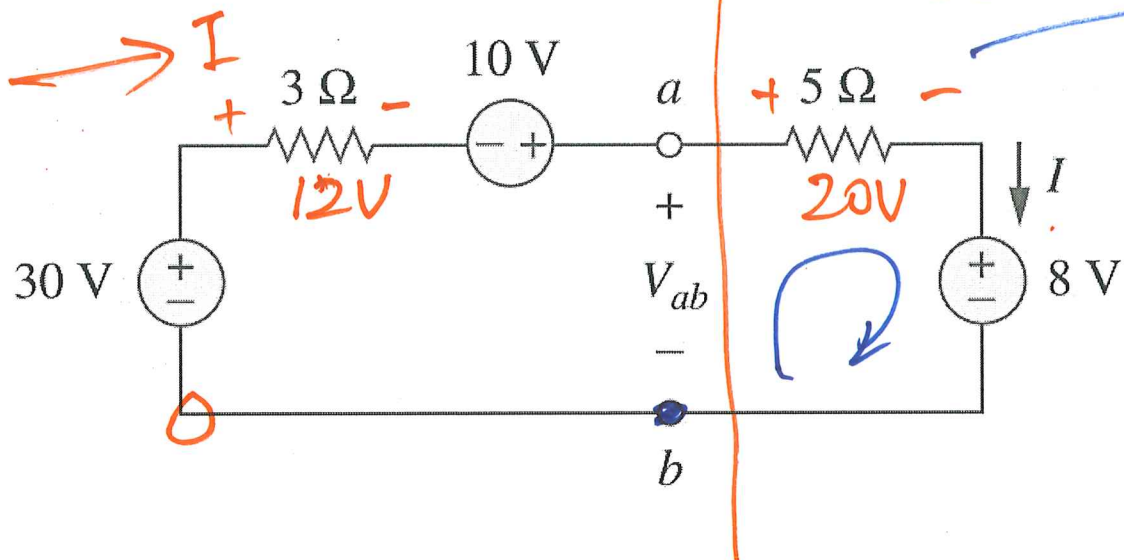

$$-30 + 3I - 10 + 5I + 8 = 0$$


$$8I = 32 \Rightarrow \underline{I = 4A}$$

$$-30 + 12 - 10 + V_{ab} = 0$$

$$\Rightarrow \underline{V_{ab} = 28V}$$

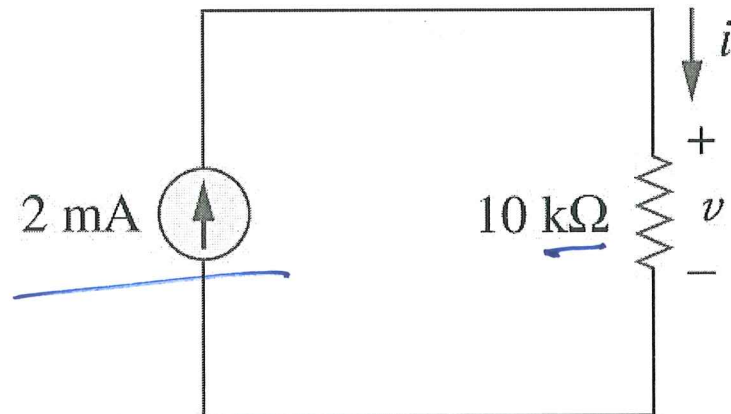Example #1:

For the circuit shown, calculate the voltage v , conductance G and power p .




$$V = i R = 2 \times 10^{-3} \text{ A} \times 10 \times 10^3 \Omega = 20 \text{ V}$$

$$G = \frac{1}{R} = \frac{1}{10 \times 10^3} = 0.1 \text{ mS}.$$


$$P = i^2 R = V \cdot i = 20 \text{ V} \cdot 2 \text{ mA} \\ = 40 \text{ mW}.$$

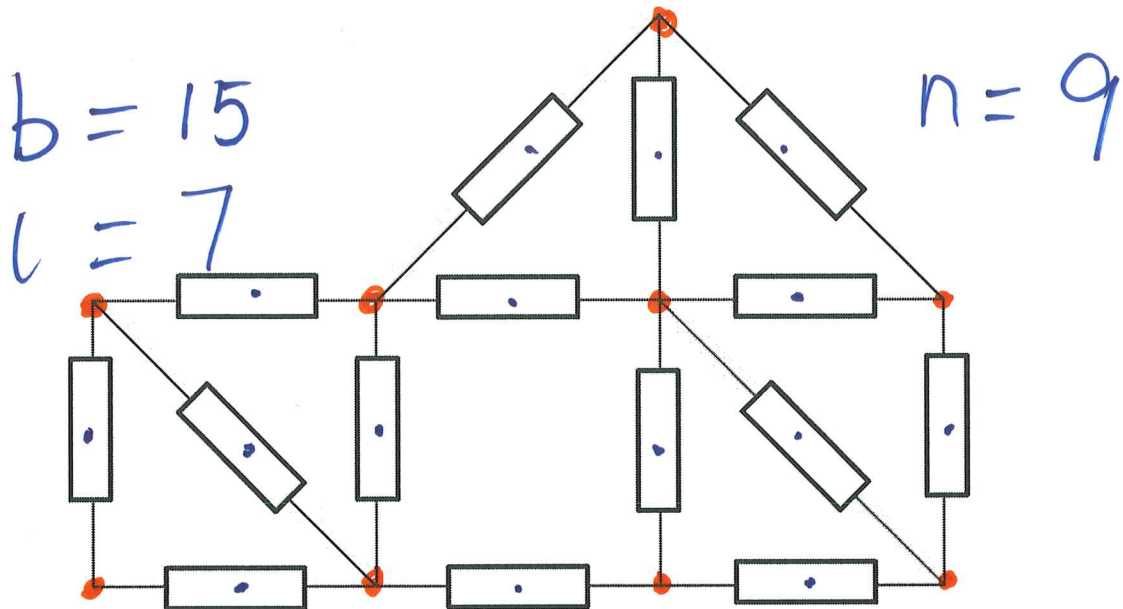Example #2:

Find the number of nodes, branches and independent loops.


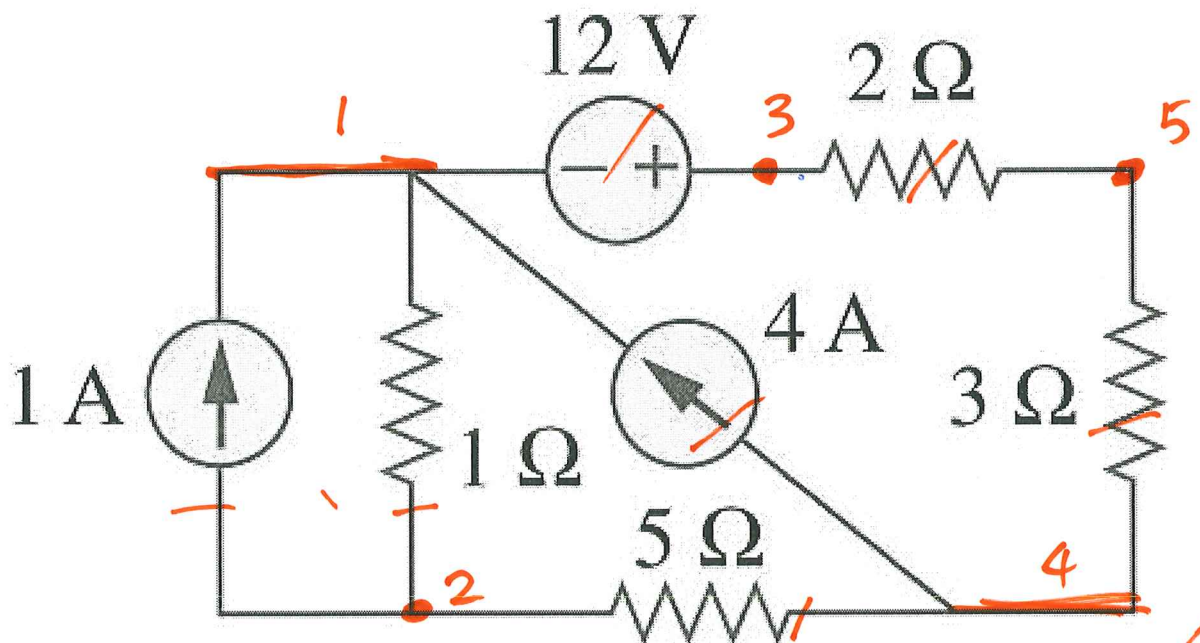
$$b = l + n - 1 \Rightarrow 15 = 7 + 9 - 1 \quad \checkmark$$



$$b = 7, \quad n = 5, \quad l = 3 \quad \checkmark$$