
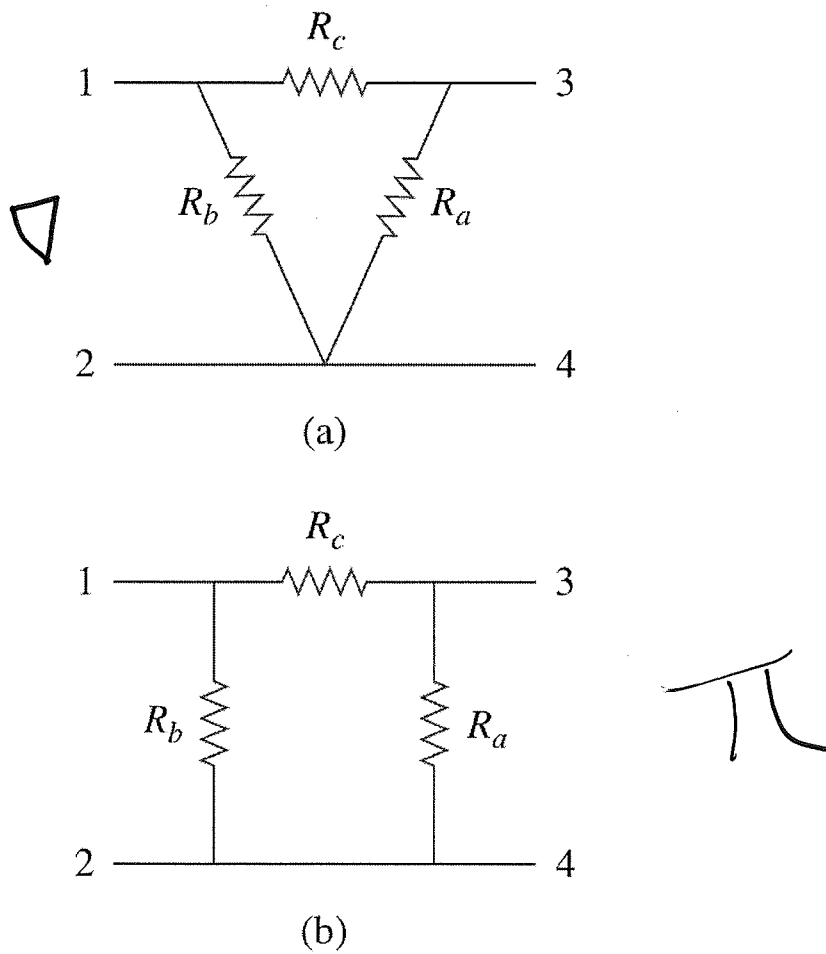


L#06: Wye-Delta transformations

2018-02-15

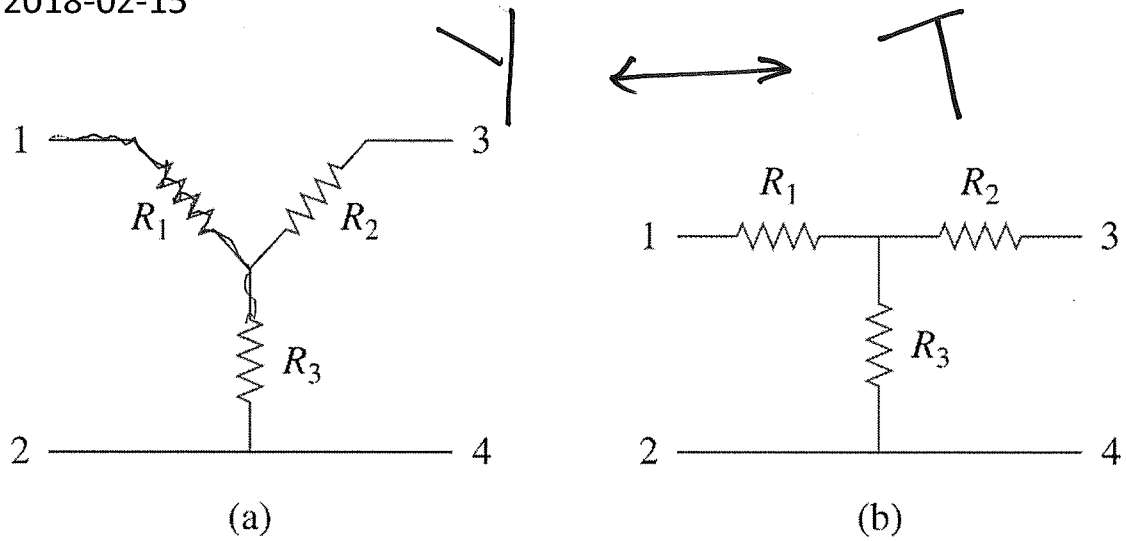

$$R_{bc} = R_a || (R_b + R_c) = R_2 + R_3$$

$$\Rightarrow R_2 + R_3 = \frac{R_a(R_b + R_c)}{R_a + R_b + R_c} \quad (1)$$

$$R_{ab} = R_c || (R_a + R_b) = R_1 + R_2$$

$$R_1 + R_2 = \frac{R_c(R_a + R_b)}{R_a + R_b + R_c} \quad (2)$$

$$R_1 + R_3 = \frac{R_b(R_a + R_c)}{R_a + R_b + R_c} \quad (3)$$


$$(2) + (3) - (1)$$

$$2R_1 = \frac{\cancel{R_a R_c} + R_b R_c + \cancel{R_a R_b} + \cancel{R_b R_c} - \cancel{R_a R_b} - \cancel{R_a R_c}}{R_a + R_b + R_c}$$

$$2R_1 = \frac{2R_b R_c}{R_a + R_b + R_c}$$



$$R_1 = \frac{R_b R_c}{R_a + R_b + R_c}$$

Notations

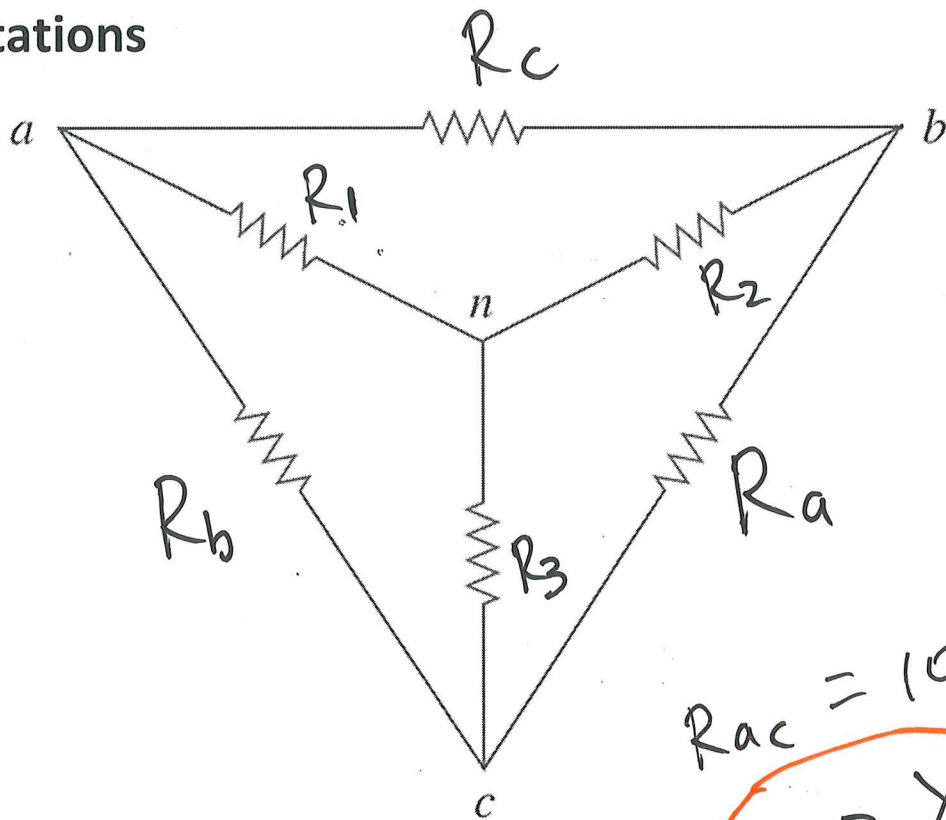

$$R_{ac} = 100 \Omega$$

$\Delta \rightarrow Y$

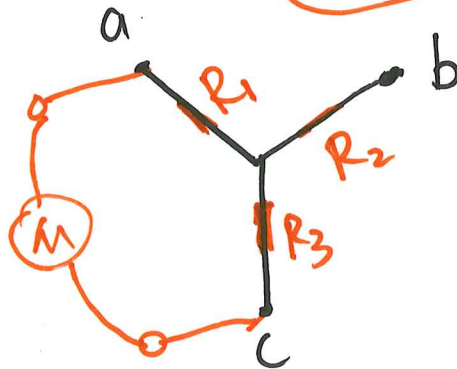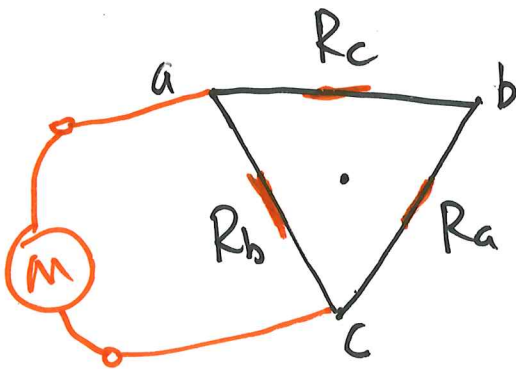

$$R_{ac} = R_b \parallel (R_a + R_c), \quad R_{ac} = R_1 + R_3$$

$$R_1 + R_3 = \frac{R_b(R_a + R_c)}{R_a + R_b + R_c}$$

$$R_1 = \frac{R_b R_c}{R_a + R_b + R_c} ; \quad R_2 = \frac{R_a R_c}{R_a + R_b + R_c}$$

$$R_3 = \frac{R_a R_b}{R_a + R_b + R_c}$$

$$R_1 R_2 = \frac{R_a R_b R_c^2}{(R_a + R_b + R_c)^2}$$

$$R_1 R_3 = \frac{R_a R_b^2 R_c}{(R_a + R_b + R_c)^2}$$

$$R_2 R_3 = \frac{R_a^2 R_b R_c}{(R_a + R_b + R_c)^2}$$

$$R_1 R_2 + R_2 R_3 + R_1 R_3 = \frac{R_a R_b R_c (R_a + R_b + R_c)}{(R_a + R_b + R_c)^2}$$

$$= R_c R_3$$


$$R_c = \frac{R_1 R_2 + R_2 R_3 + R_1 R_3}{R_3}$$

$$R_a = \frac{R_1 R_2 + R_2 R_3 + R_1 R_3}{R_1}$$

$Y \rightarrow \Delta$

$$R_b = \frac{R_1 R_2 + R_2 R_3 + R_1 R_3}{R_2}$$

Transformations

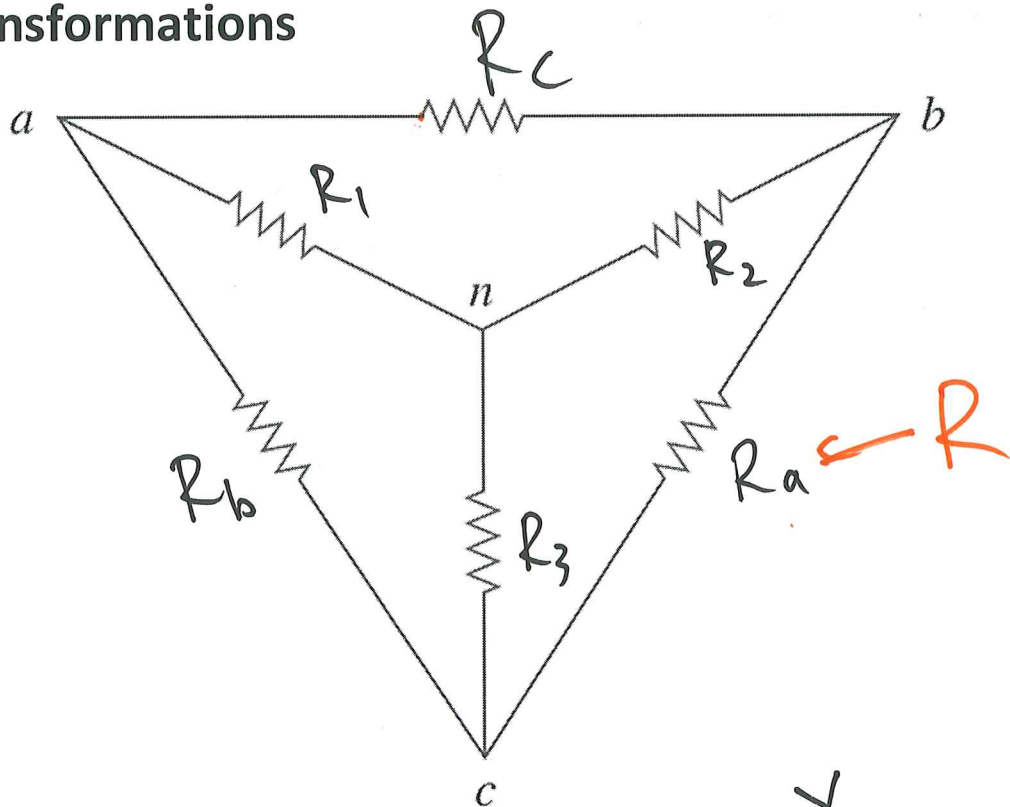

$$R_2 = \frac{R_a R_c}{R_a + R_b + R_c}$$


$\Delta \rightarrow Y$

$$R_3 = \frac{R_a R_b}{R_a + R_b + R_c} = \frac{R^2}{3R} = \frac{R}{3}$$


$$Y_R = \frac{\Delta R}{3} \Rightarrow \Delta R = 3 Y_R$$

Example #1:


Convert the circuits from Y to Δ :

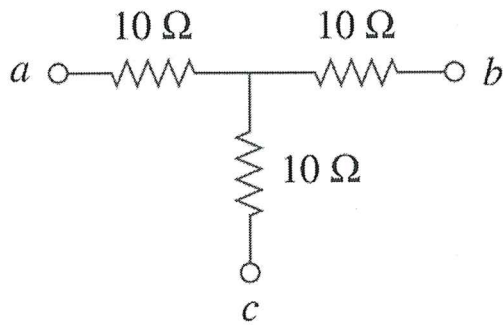

(a)

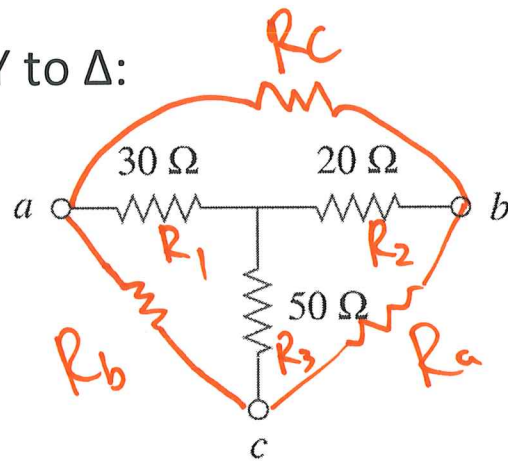

(b)

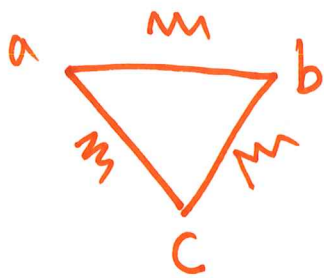


$$\Delta_R = 3 \Delta_Y = 30 \Omega.$$


$$\begin{aligned} R_a &= \frac{R_1 R_2 + R_2 R_3 + R_1 R_3}{R_1} \\ &= 70 + \frac{50 \times 20}{30} \\ &= 73.3 \Omega \end{aligned}$$

Example #2:

Convert the circuits from Δ to Y.

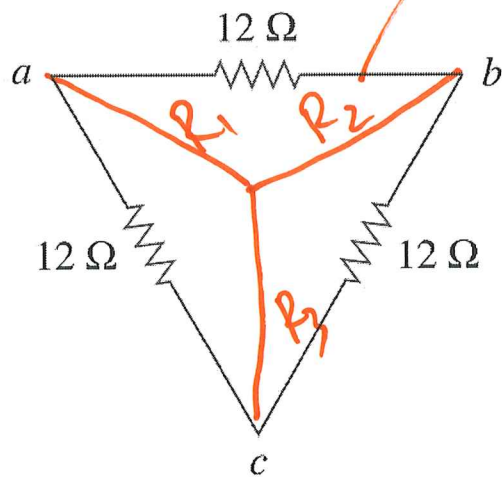

(a)

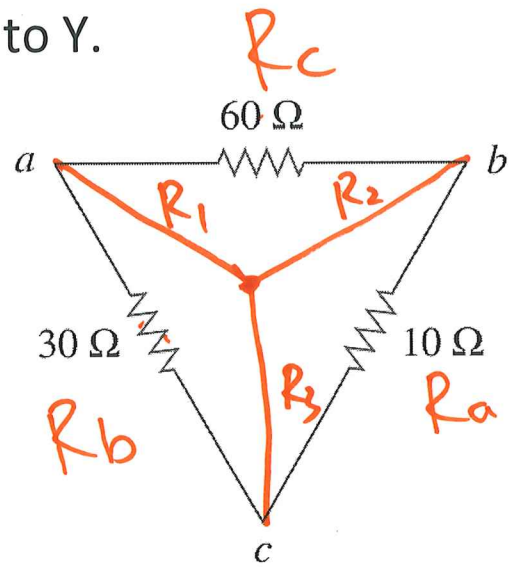

(b)


$$R_1 = \frac{30 \times 60}{30 + 60 + 10} = 18 \Omega$$

$$R_2 \dots R_3$$

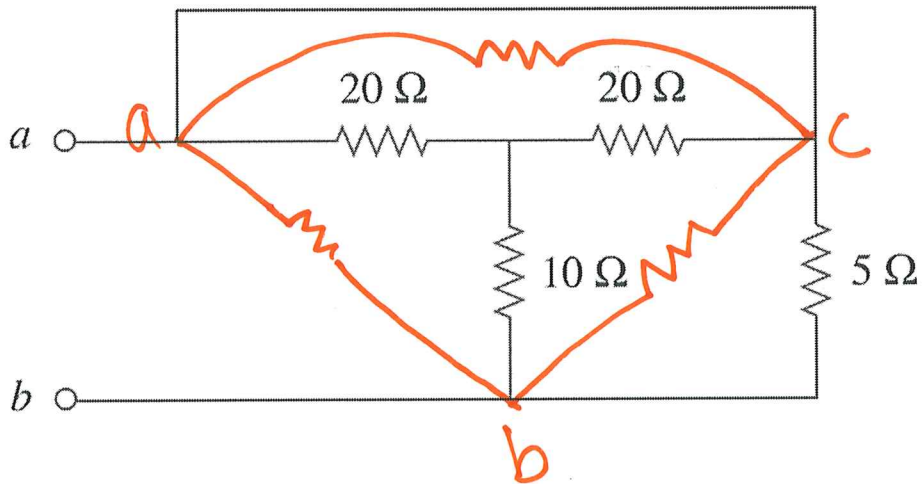Example #3:


homework

Determine R_{eq} between terminals a and b .



Example #4:

Calculate I_o in the circuit.

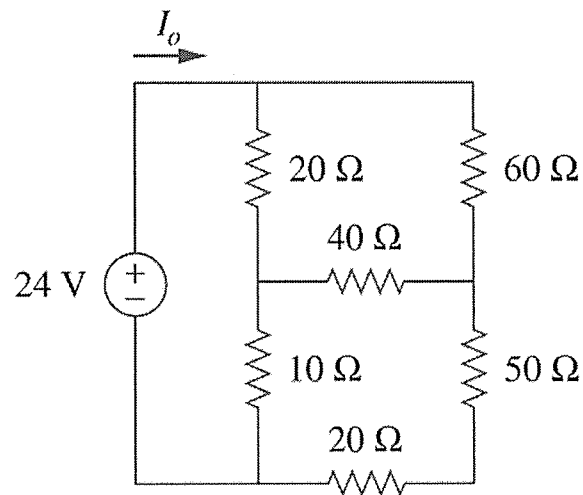

Example #3:

Determine i_1 to i_5 .

homework

