



EBN 122

Chapter 5: Operational Amplifiers (Op Amps)

Chapter 5 overview

5.2. Operational Amplifiers (Op Amps)

5.3. Ideal Op Amps

5.4. Inverting Amplifiers

5.5. Noninverting Amplifiers

5.6. Summing Amplifiers

5.7. Difference Amplifiers

5.8. Cascaded Amplifier Circuits




Video lecture 1




What is an Op Amp?



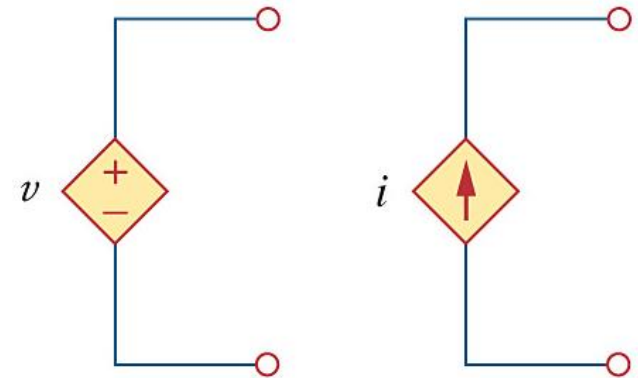
- Electronic unit that behaves like a **voltage-controlled voltage source**
- Active circuit element
- Designed to perform **mathematical operations**:
 - addition, subtraction, multiplication, division, differentiation, integration
- Consists of complex arrangement of components:
 - resistors, transistors, capacitors, diodes



What is an Op Amp?

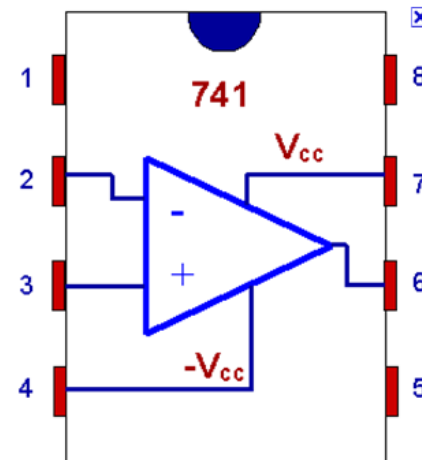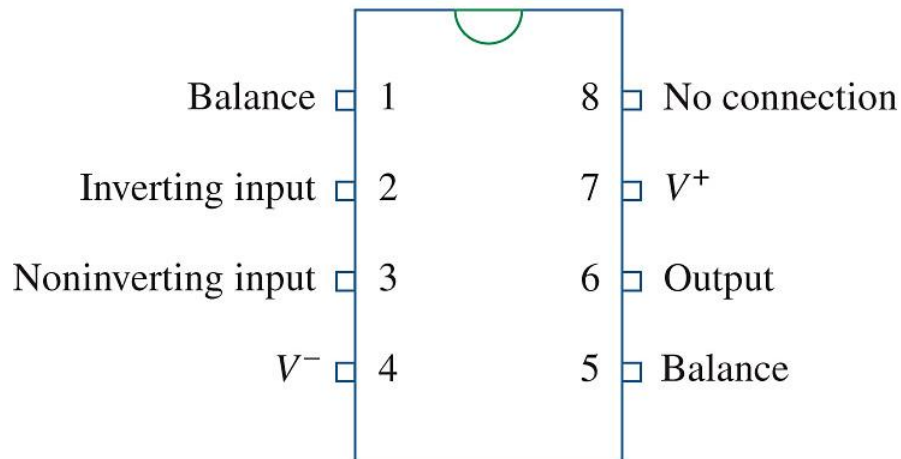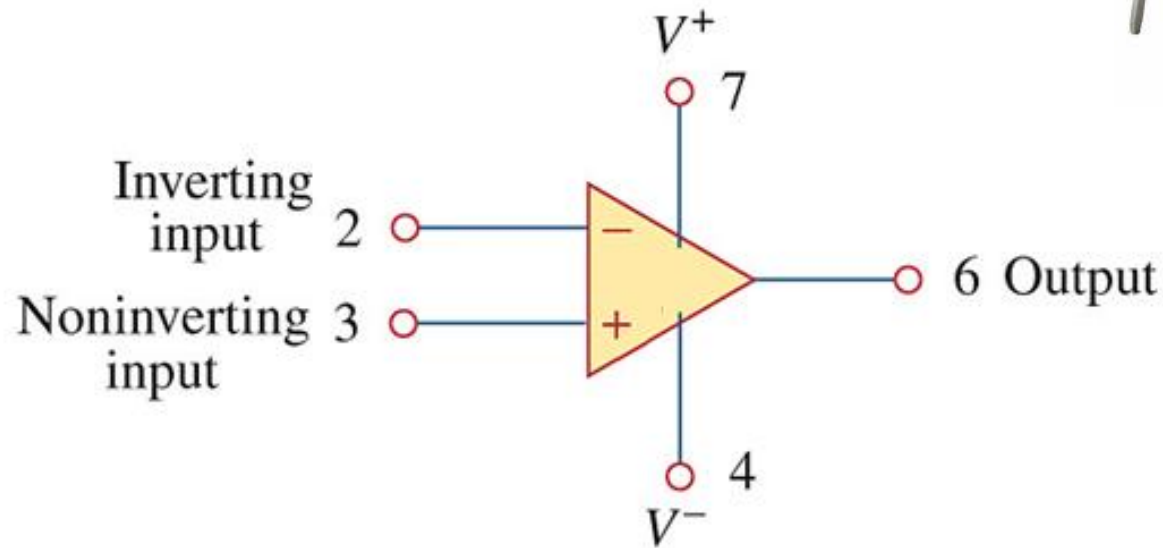

What is an Op Amp?


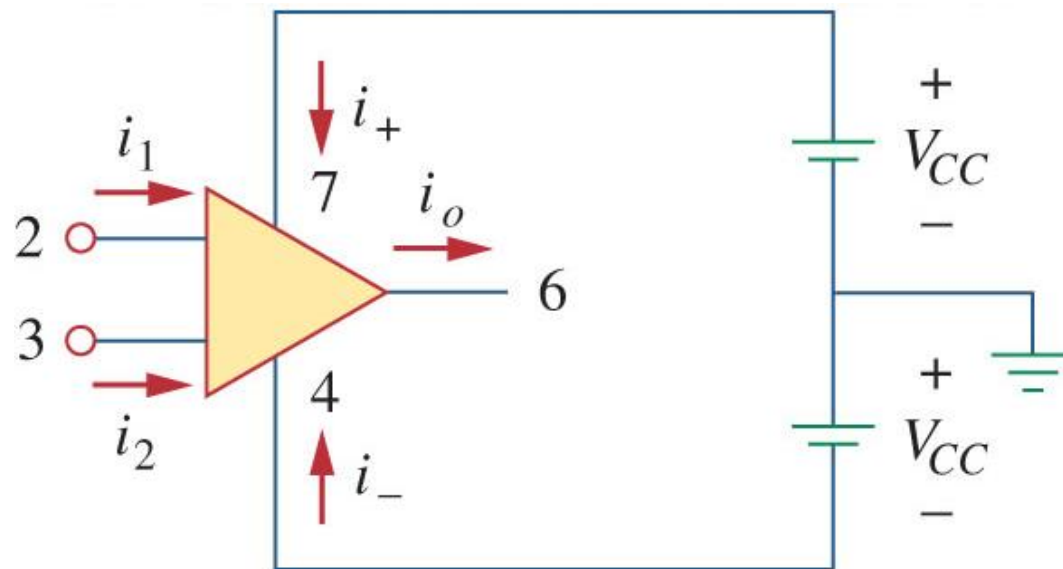


KCL:

$$i_o = i_1 + i_2 + i_+ + i_-$$

Maximum and minimum limits for output voltage of op-amp (v_o) as a result of power supply voltages

Equivalent circuit for op-amp

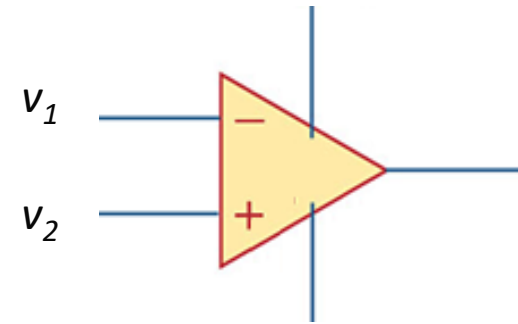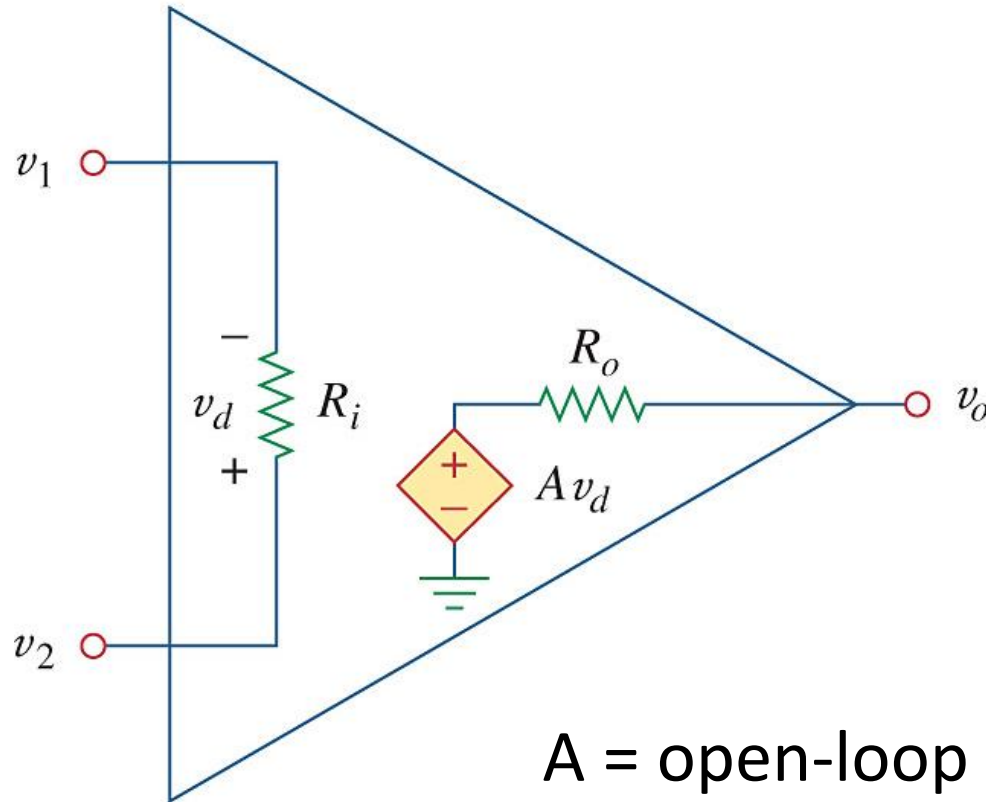

$$v_d = v_2 - v_1$$

$$v_o = A v_d = A(v_2 - v_1)$$

A = open-loop voltage gain
(no external feedback from
output v_o to input v_d)

Op-amp parameters and properties


Parameter	Range	Ideal
A	$10^5 - 10^8$	∞
R_i	$10^5 - 10^{13} \Omega$	$\infty \Omega$
R_o	$10 - 100 \Omega$	0Ω
V_{CC}	$5 - 24 \text{ V}$	

Supply voltage




FEEDBACK:

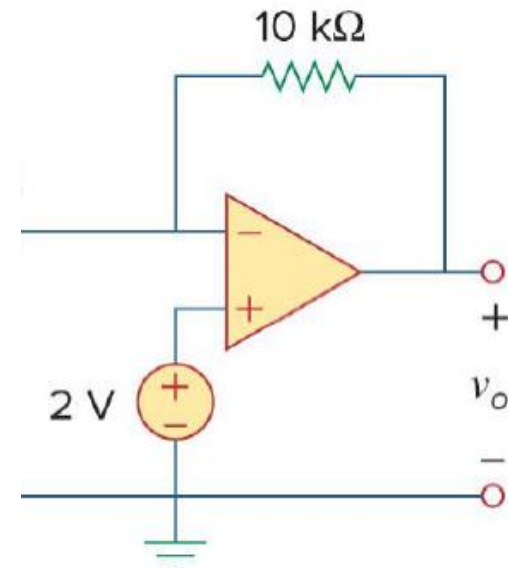- Negative feedback: output fed back to inverting input terminal
- Ratio of output voltage to input voltage = closed-loop gain





Practical limitations





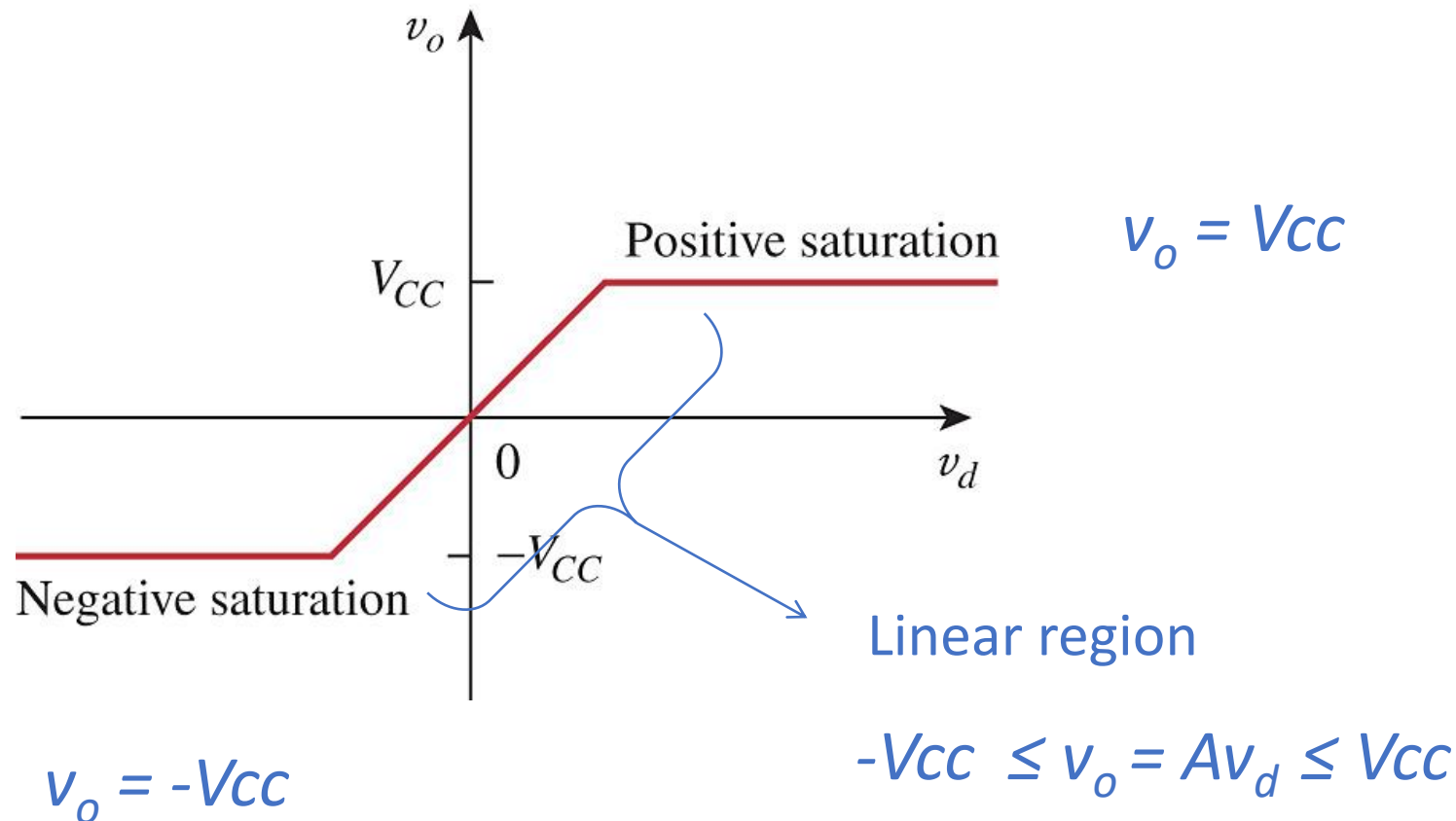


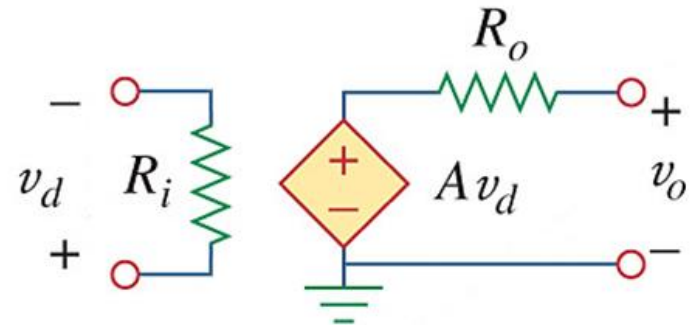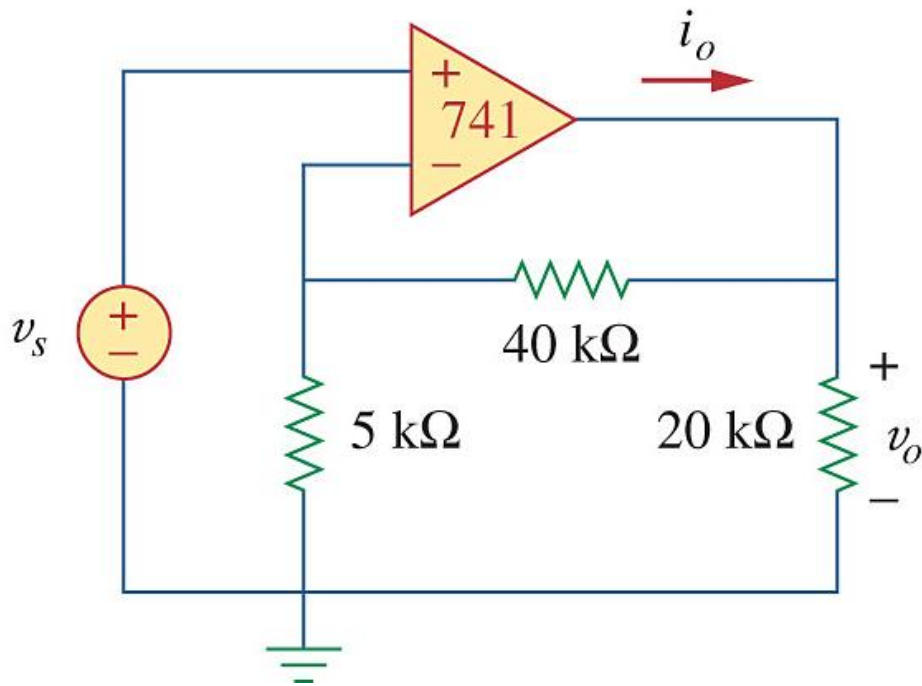Example

Use a 741 Op Amp with $A = 2 \times 10^5$, $R_i = 2 \text{ M}\Omega$, $R_o = 50 \Omega$.
Determine the closed-loop gain v_o/v_s




Example

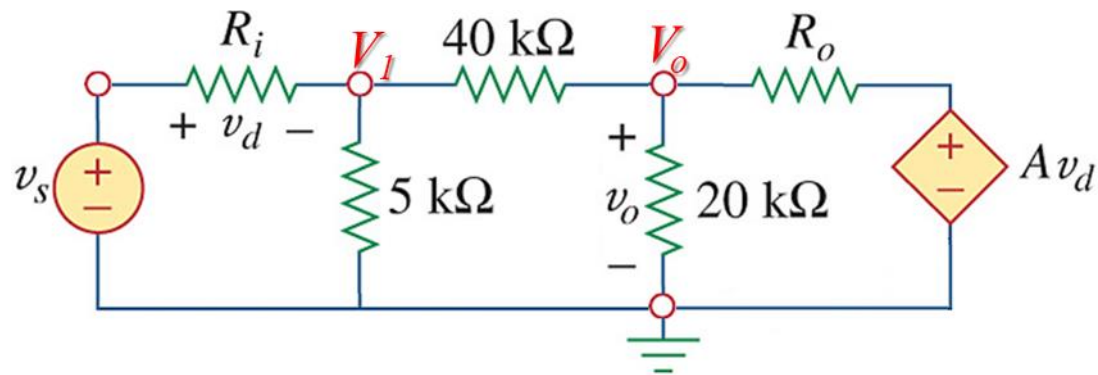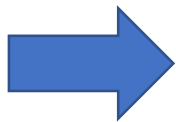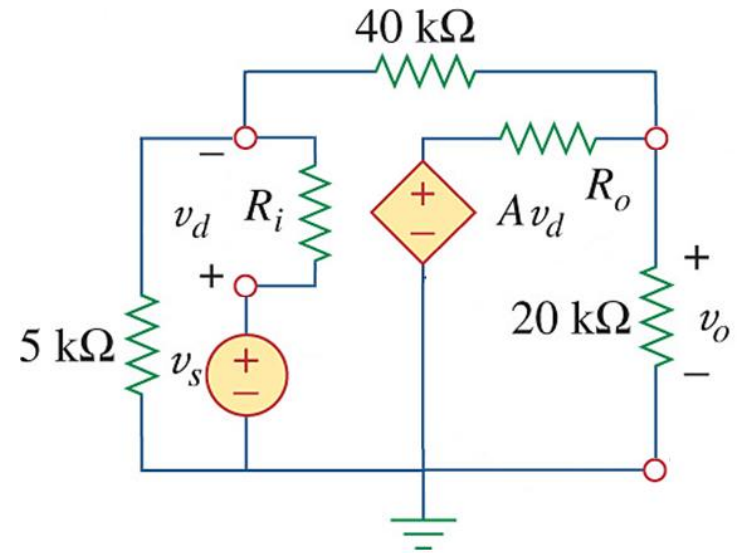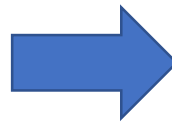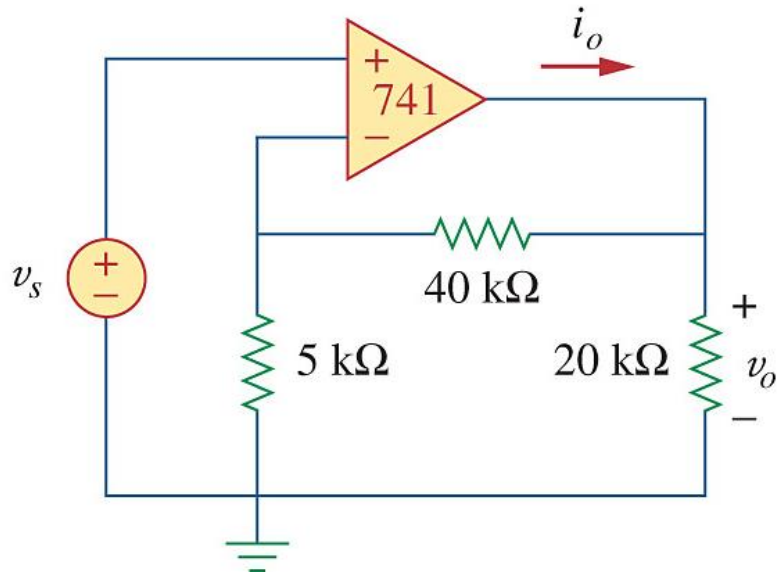

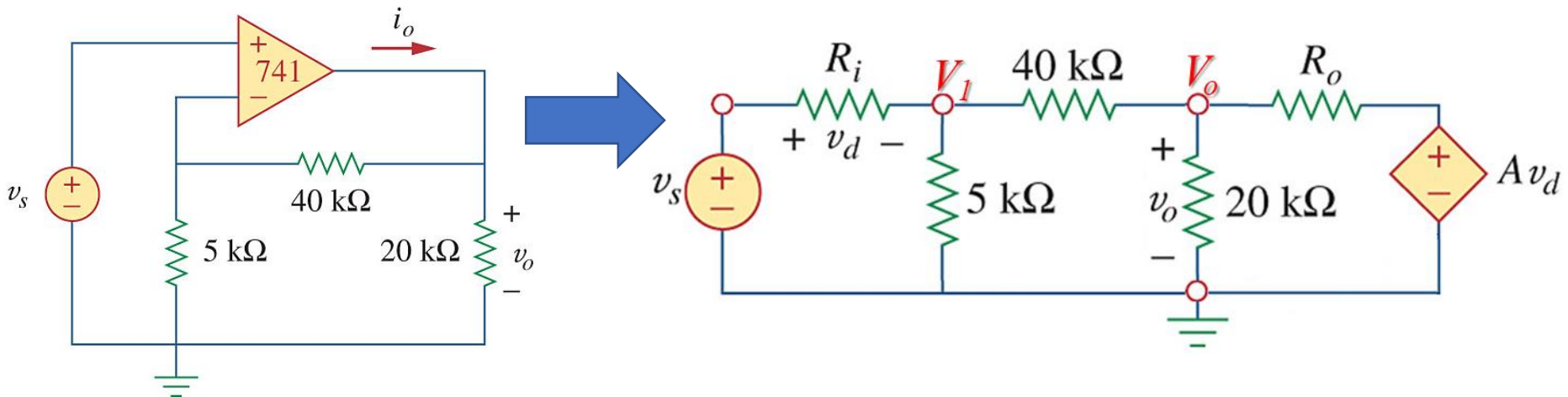
Example

Use a 741 Op Amp with $A = 2 \times 10^5$, $R_i = 2 \text{ M}\Omega$, $R_o = 50 \Omega$.
Determine the closed-loop gain v_o/v_s



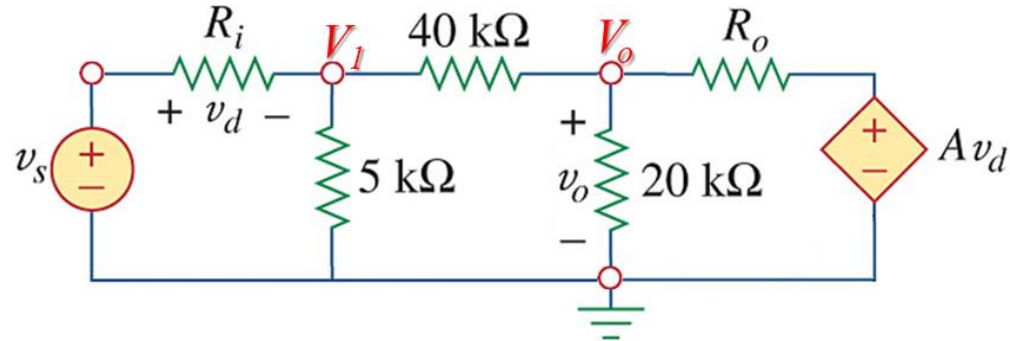Example

Use a 741 Op Amp with $A = 2 \times 10^5$, $R_i = 2 \text{ M}\Omega$, $R_o = 50 \text{ }\Omega$.
Determine the closed-loop gain v_o/v_s



KCL @ Node V_1

$$\frac{V_1 - V_s}{2 \times 10^6} + \frac{V_1}{5 \times 10^3} + \frac{V_1 - V_o}{40 \times 10^3} = 0$$

$$V_1 - V_s + 400V_1 + 50V_1 - 50V_o = 0$$

$$451V_1 - 50V_o = V_s \quad (1)$$

KCL @ Node V_o

$$\frac{V_o - V_1}{40 \times 10^3} + \frac{V_o}{20 \times 10^3} + \frac{V_o - Av_d}{50} = 0$$

$$V_o - V_1 + 2V_o + 800[V_o - A(V_s - V_1)] = 0$$

$$160 \times 10^6 V_1 + 803V_o = 160 \times 10^6 V_s$$

$$451V_1 + 2.263 \times 10^{-3} V_o = 451V_s \quad (2)$$


(1) - (2)

$$\begin{aligned} -50.00226 v_o &= -450V_s \\ \frac{v_o}{v_s} &= \frac{-450}{-50.00226} = 8.9996 \end{aligned}$$

Ideal Op Amps

An ideal op amp has the following characteristics:

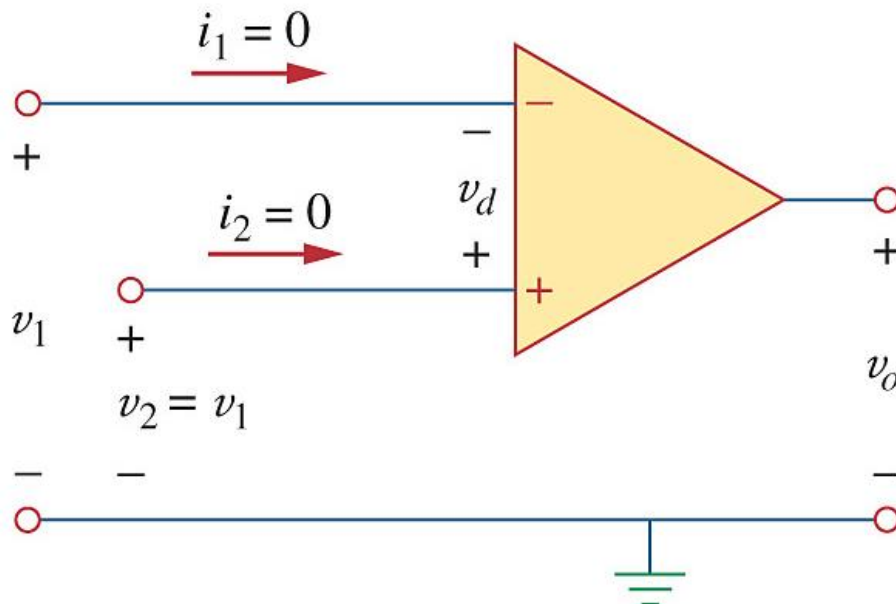1. Infinite open-loop gain, $A \approx \infty$
2. Infinite input resistance, $R_i \approx \infty$
3. Zero output resistance, $R_o \approx 0$



Since $R_i = \infty$:


$$i_1 = i_2 = 0$$

$$\therefore v_d = v_2 - v_1 = 0$$

$$\therefore v_2 = v_1$$

Ideal vs non-ideal op-amps

IDEAL:

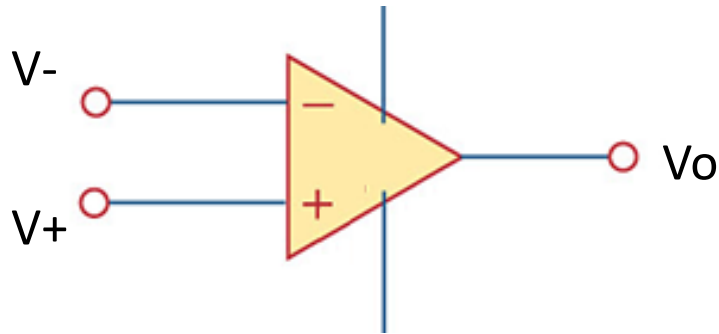


$$\begin{array}{lll} A & \rightarrow & \infty \quad \text{V/V} \\ R_i & \rightarrow & \infty \quad \Omega \\ R_o & \rightarrow & 0 \quad \Omega \end{array}$$

$$i_1 = i_2 = 0$$

$$V_2 = V_1$$

NON-IDEAL:

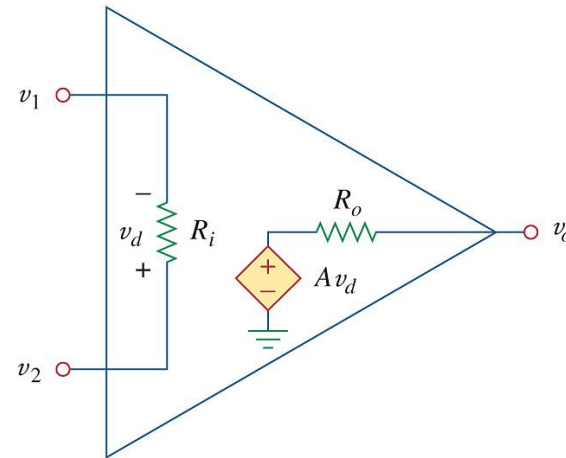

$$\begin{array}{lll} A & \rightarrow & 10^5 - 10^8 \quad \text{V/V} \\ R_i & \rightarrow & 10^5 - 10^{13} \quad \Omega \\ R_o & \rightarrow & 10 - 100 \quad \Omega \end{array}$$


Example using ideal op-amp

Assume $v_s = 1\text{ V}$ and determine v_o and i_o .

Remember:

$$i_1 = i_2 = 0$$

$$v_+ = v_-$$

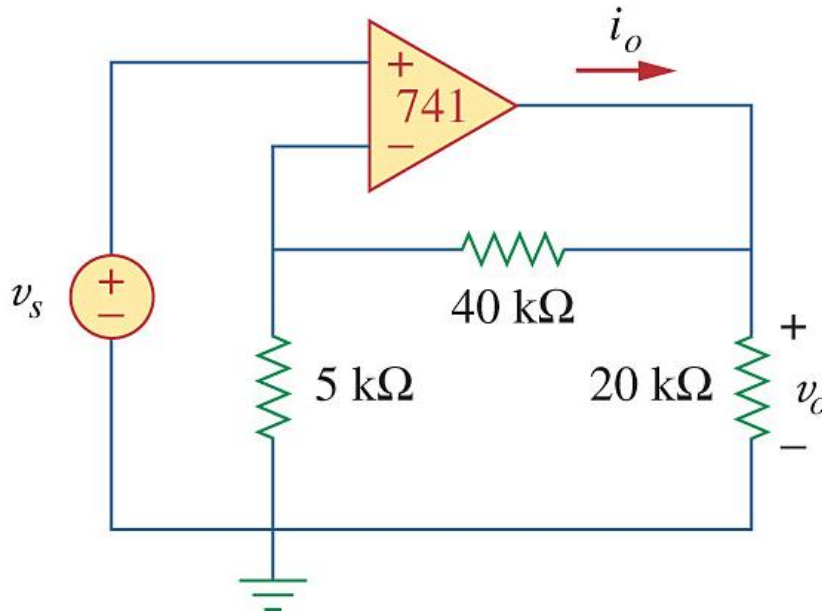

KCL @ Node v_- to get V_o :

$$\frac{1}{5 \times 10^3} + \frac{1 - V_o}{40 \times 10^3} = 0$$

$$8 + 1 - V_o = 0$$

$$V_o = 9\text{ V}$$


KCL @ Node V_o to get i_o :

$$i_o = \frac{9 - 1}{40 \times 10^3} + \frac{9}{20 \times 10^3}$$

$$i_o = 650\text{ }\mu\text{A}$$

Examples

Determine v_o

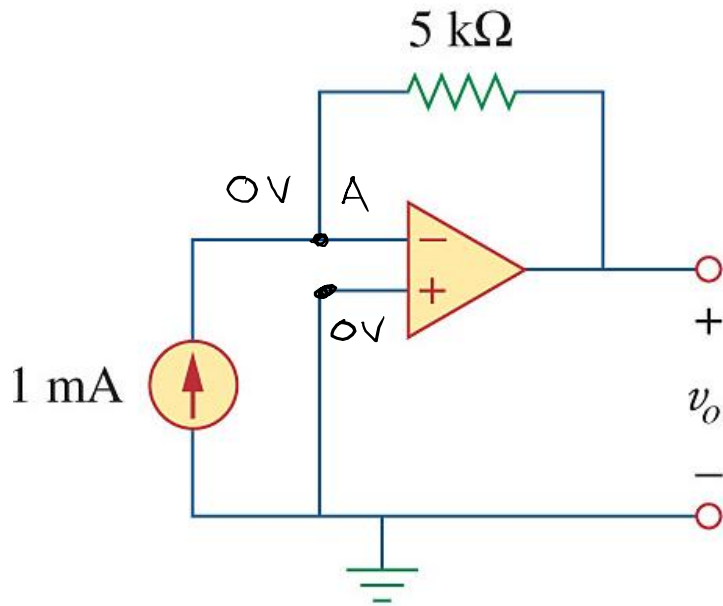

Node A: (KCL):



$$\frac{0 - v_o}{5k\Omega} + -1mA = 0$$

$$\therefore \frac{v_o}{5k\Omega} = -1mA$$

$$v_o = \underline{\underline{-5V}}$$

Examples

Determine v_o

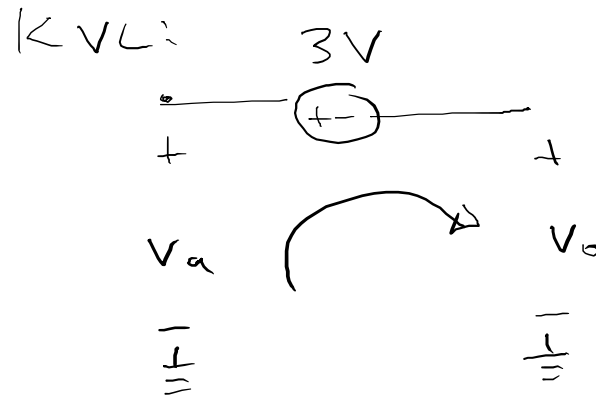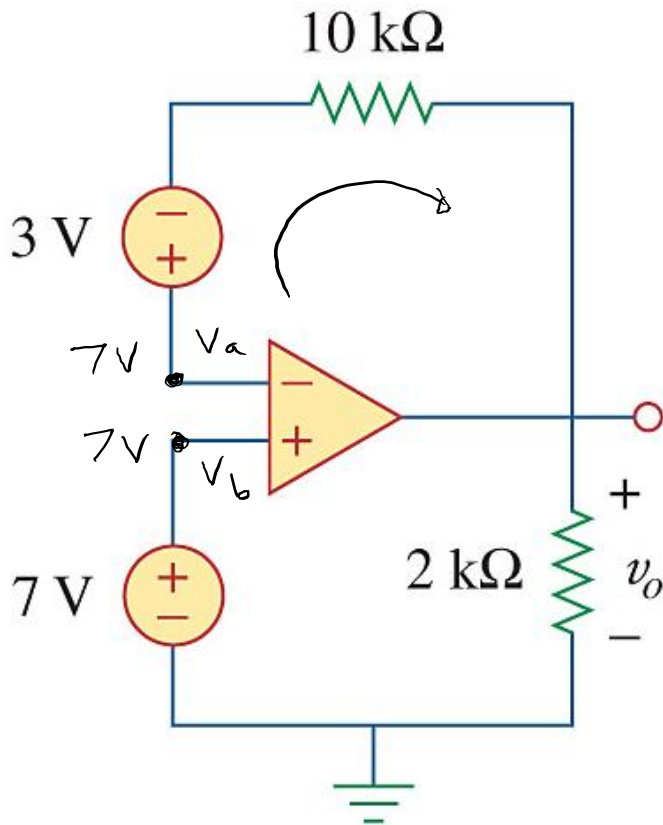



$$-v_a + 3 + v_o = 0$$


$$-7 + 3 + v_o = 0$$

$$\therefore v_o = 4V$$

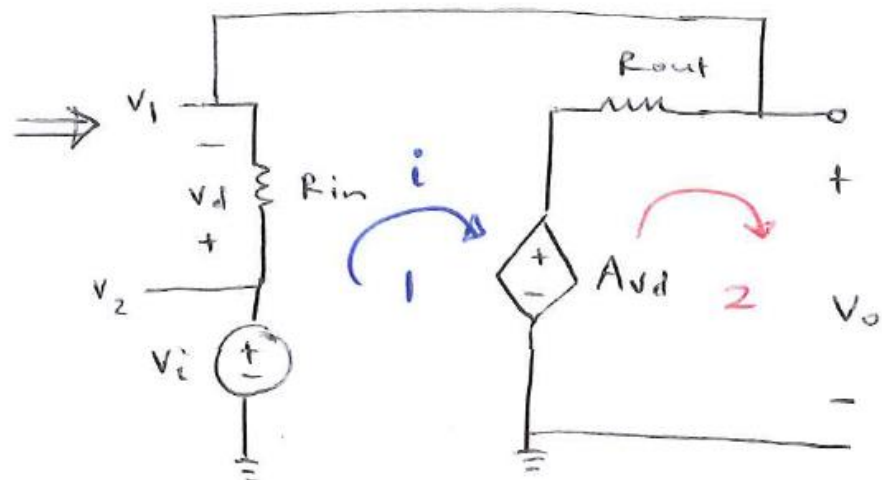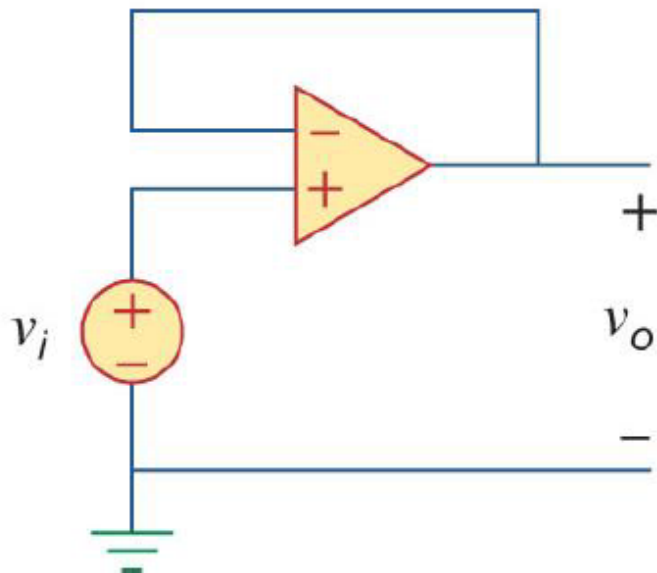Example 1: Non-ideal op amp

- The op amp has an open-loop gain of 100 000, an input resistance of 10 k Ω , and an output resistance of 100 Ω . Find the voltage gain $\frac{v_o}{v_i}$.



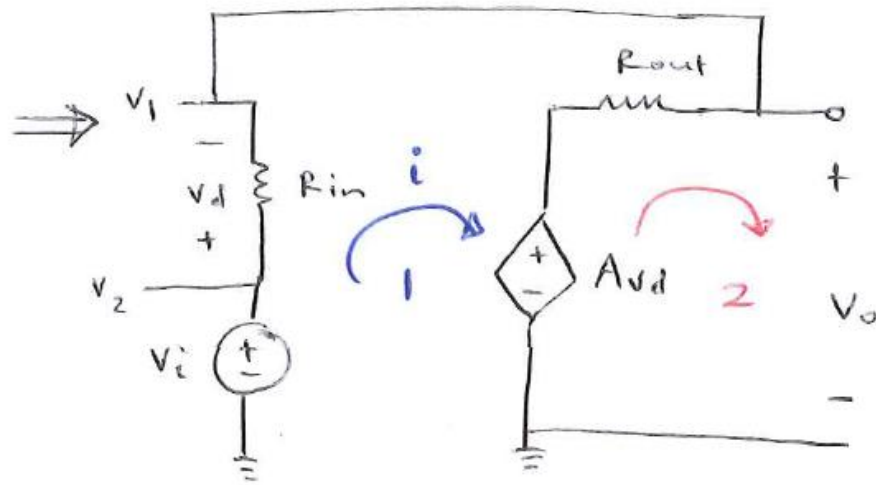

KVL loop 1: $-V_i + v_d + R_{out} i + A v_d = 0$

and $v_d = R_{in} i$

$\therefore -V_i + i (R_{in} + R_{out}) + A (R_{in} i) = 0$

$\therefore V_i = i (R_{in} + R_{out} + A R_{in})$


$i = \frac{V_i}{R_{in} (1+A) + R_{out}} \quad (1)$

KVL loop 2: $-A v_d + R_{out} (-i) + V_o = 0$

$\therefore V_o = A R_{in} i + R_{out} i = i (A R_{in} + R_{out}) \quad (2)$

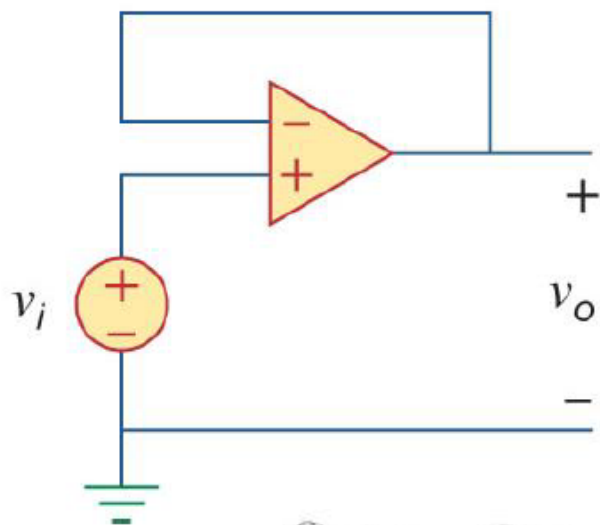Example 1: Non-ideal op amp

- The op amp has an open-loop gain of 100 000, an input resistance of 10 k Ω , and an output resistance of 100 Ω . Find the voltage gain $\frac{v_o}{v_i}$.



① into ②:
$$v_o = \frac{v_i (A R_{in} + R_{out})}{R_{in} (1 + A) + R_{out}}$$



$$\therefore \frac{V_o}{V_i} = \frac{((100 \times 10^3 - 10 \times 10^3) + 100)}{(10 \times 10^3 (1 + 100 \times 10^3) + 100)} = \frac{1 \times 10^9}{1.00001 \times 10^9}$$


$$\frac{V_o}{V_i} = 0.999$$

→

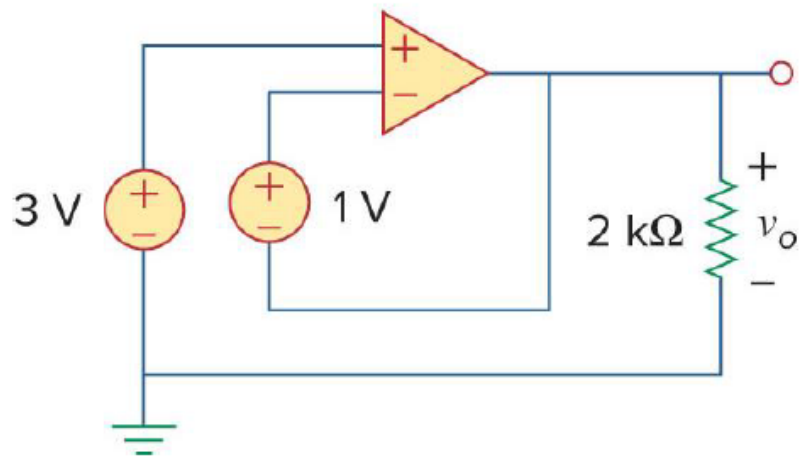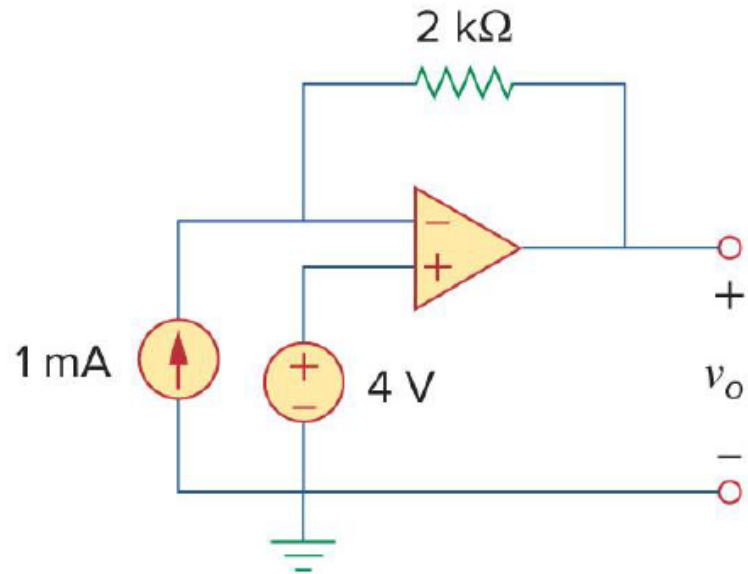Example 2: Ideal op amp

- Assume ideal op amps. Determine v_o for both circuits.



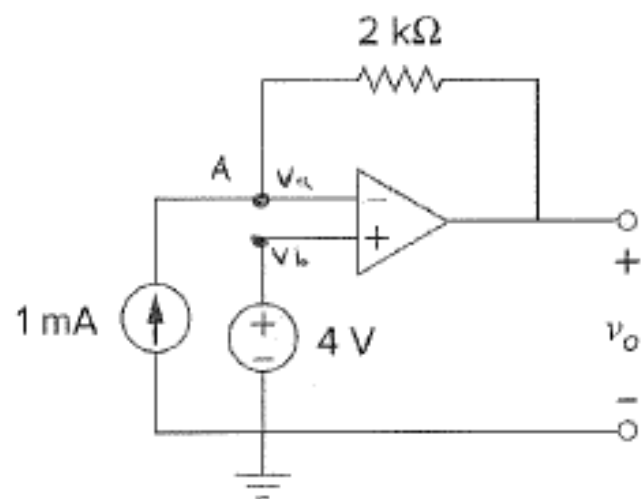


$$V_a = V_b = 4V$$

At node A:


$$1mA = \frac{4 - V_o}{2k\Omega}$$

$$\therefore -V_o = (2k\Omega)(1mA) - 4$$

$$V_o = 4 - 2 = 2V \rightarrow$$

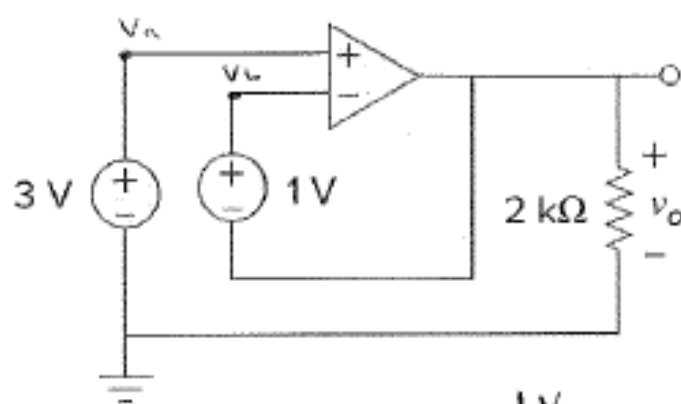

$$V_a = V_b = 3V$$

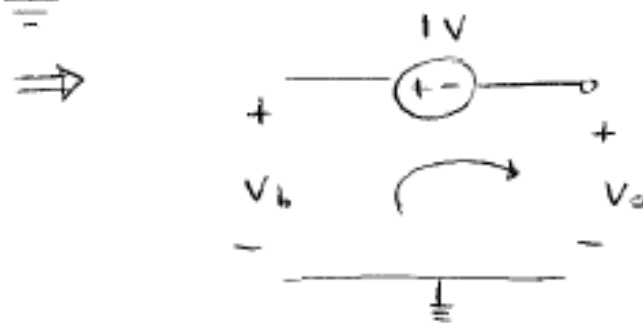

$$-V_b + 1 + V_o = 0$$


$$V_o = V_b - 1$$


$$V_o = 3 - 1$$

$$V_o = 2V \rightarrow$$

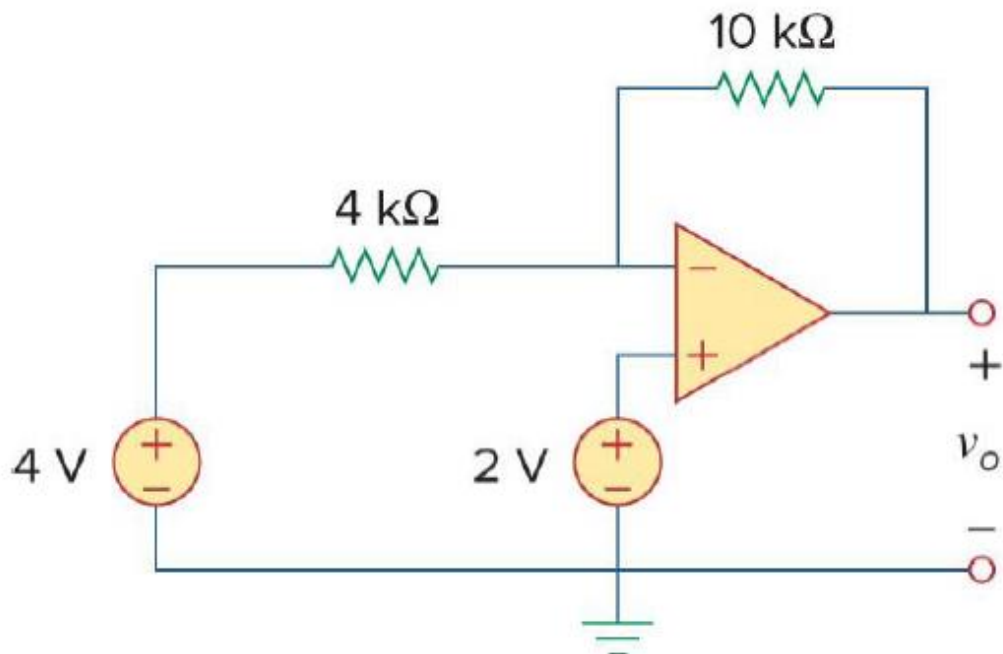Example 3: Ideal op amps

- Assume an ideal op amp. Determine v_o .



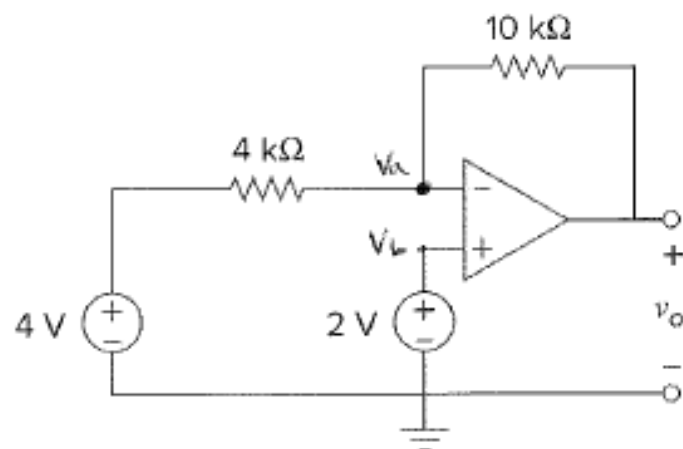

$$V_a = V_b = 2V$$

At node V_a :

$$\frac{V_a - 4}{4k} + \frac{V_a - V_o}{10k} = 0$$

$$(\times 20k): 5V_a - 20 + 2V_a - 2V_o = 0$$

and $V_a = 2V$:

$$\therefore 7(2) - 20 - 2V_o = 0$$

$$\therefore 2V_o = -6$$

$$V_o = -3V$$

