



EBN 122

Chapter 5: Operational Amplifiers (Op Amps)

Cascaded Op-Amp Circuits

Chapter 5 overview

- ✓ 5.2. Operational Amplifiers (Op Amps)
- ✓ 5.3. Ideal Op Amps
- ✓ 5.4. Inverting Amplifiers
- ✓ 5.5. Noninverting Amplifiers
- ✓ 5.6. Summing Amplifiers
- ✓ 5.7. Difference Amplifiers
- 5.8. Cascaded Amplifier Circuits


Recap of op-amps

IDEAL OP-AMPS:

$$i_+ = i_- = 0$$


$$v_+ = v_-$$

Inverting:

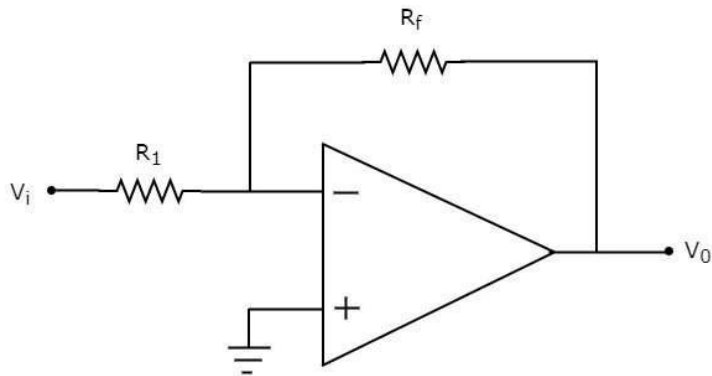


$$v_o = -\frac{R_f}{R_1} v_i$$

Non-inverting:

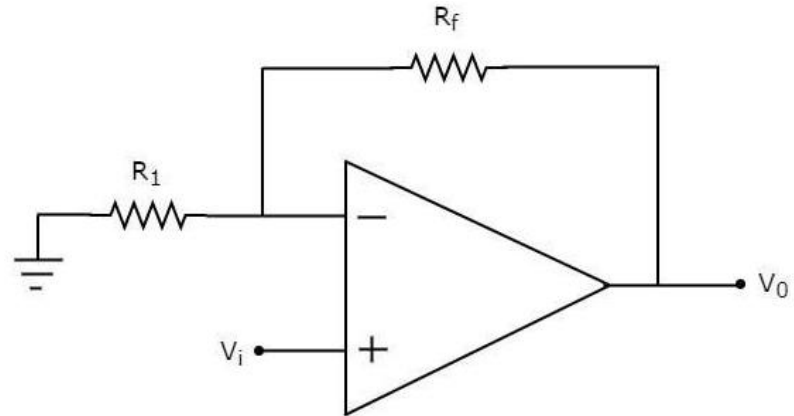

$$v_o = \left(1 + \frac{R_f}{R_1}\right) v_i$$

Buffer
(voltage follower):

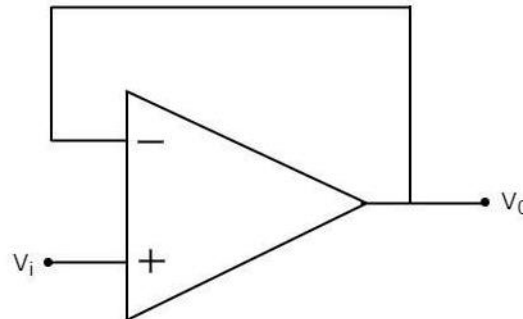

$$v_o = v_i$$


Re-cap of op-amps

IDEAL OP-AMPS:

$$i_+ = i_- = 0$$


$$v_+ = v_-$$

Summing amplifier:

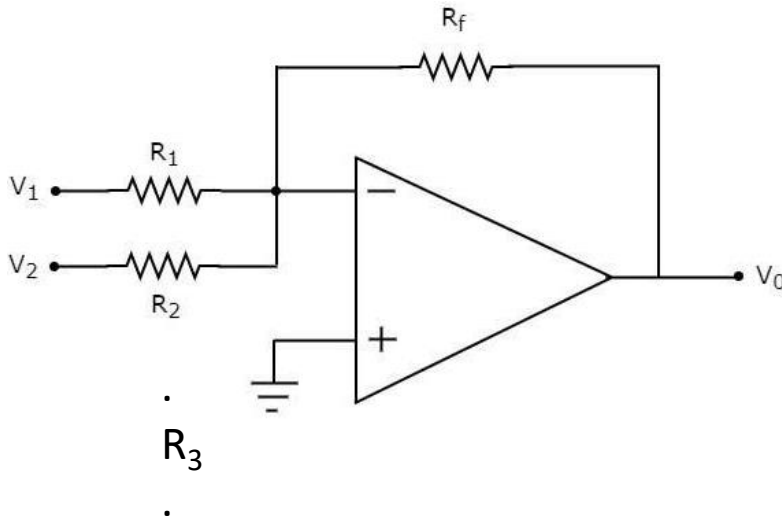

$$V_o = -\left(\frac{R_f}{R_1} V_1 + \frac{R_f}{R_2} V_2 + \frac{R_f}{R_3} V_3 \right)$$

Difference amplifier:

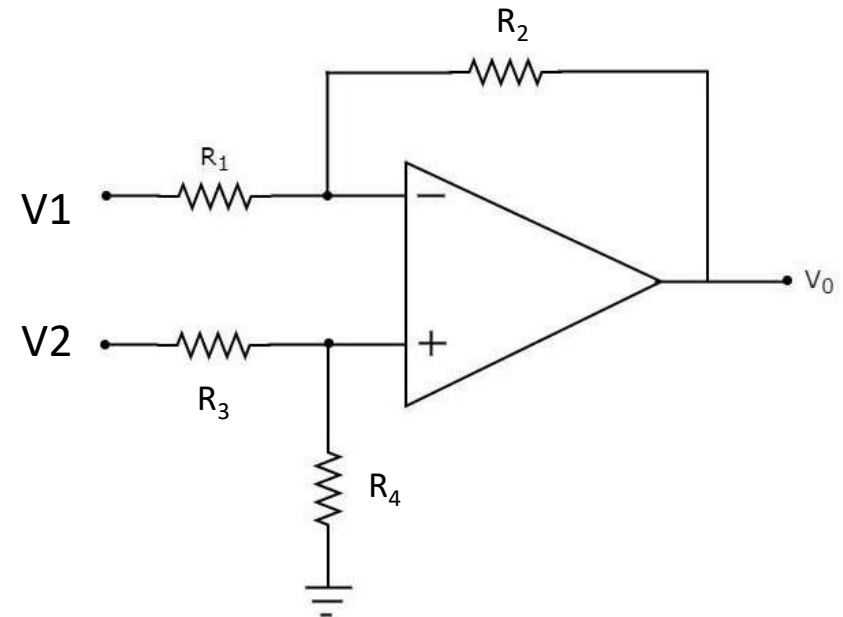


$$V_o = \frac{R_2(1 + R_1/R_2)}{R_1(1 + R_3/R_4)} V_2 - \frac{R_2}{R_1} V_1$$

Example 1: (Practice Problem 5.7)

Design an Op Amp circuit with inputs v_1 and v_2 such that $v_o = -5v_1 + 3v_2$

$v_o = 3v_2 - 5v_1 \rightarrow$ difference amplifier
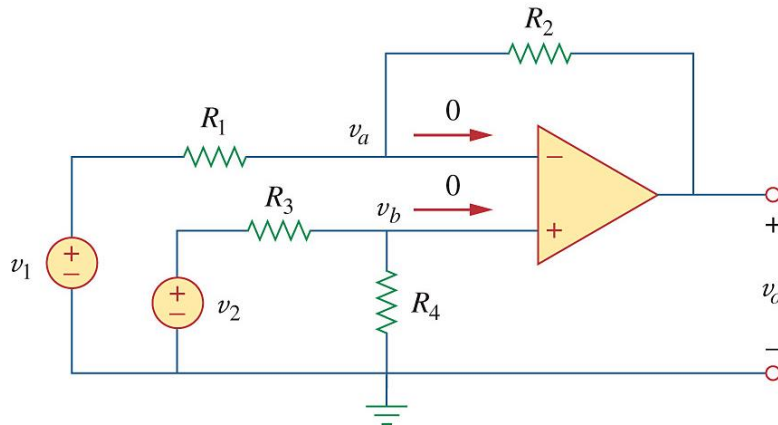
$$v_o = \frac{R_2(1 + R_1/R_2)}{R_1(1 + R_3/R_4)} v_2 - \frac{R_2}{R_1} v_1$$



$$\frac{R_2}{R_1} = 5$$

$$\frac{R_2(1 + R_1/R_2)}{R_1(1 + R_3/R_4)} = \frac{5(1 + 1/5)}{1(1 + R_3/R_4)} = 3$$

$$\frac{5(1 + 1/5)}{3} = (1 + R_3/R_4)$$

$$2 - 1 = 1 = R_3/R_4$$


Choose $R_3 = R_4 = 2 \text{ k}\Omega$

Example 1: (Practice Problem 5.7)

Design an Op Amp circuit with inputs v_1 and v_2 such that $v_o = -5v_1 + 3v_2$


- Can also use 2 op-amps:

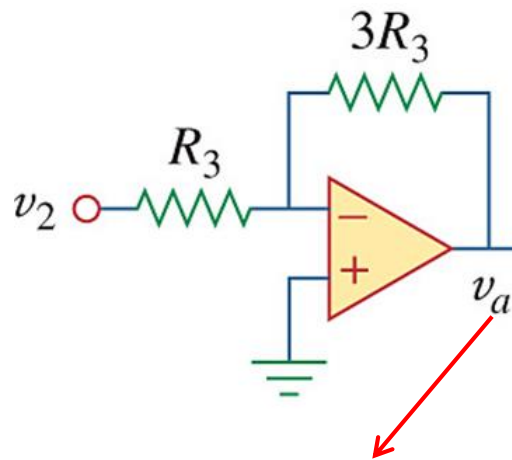1. Build an inverting amp to obtain $v_a = -3v_2$.



$$\begin{aligned} v_a &= -\frac{3R_3}{R_3} \times v_2 \\ &= -3v_2 \end{aligned}$$

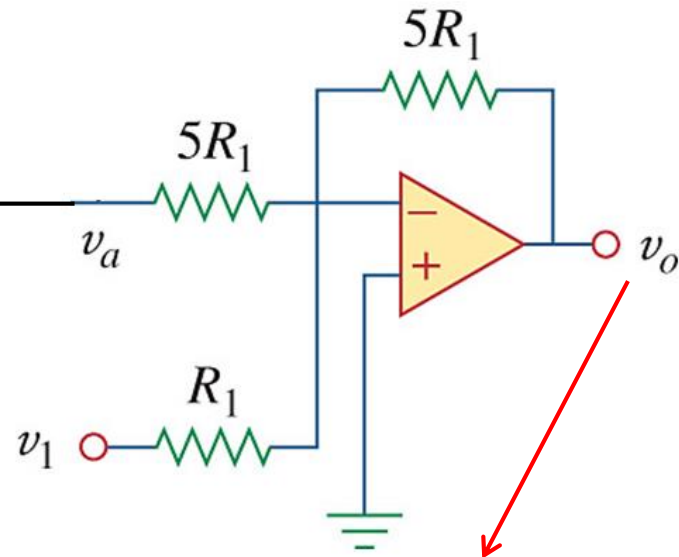
2. Feed the output v_a into a summing amplifier along with v_1 .



$$\begin{aligned} v_o &= -\left(\frac{5R_1}{R_1} \times v_1 + \frac{5R_1}{5R_1} \times v_a\right) \\ &= -5v_1 - v_a \\ &= -5v_1 - (-3v_2) \\ &= -5v_1 + 3v_2 \end{aligned}$$


Cascaded Op Amps

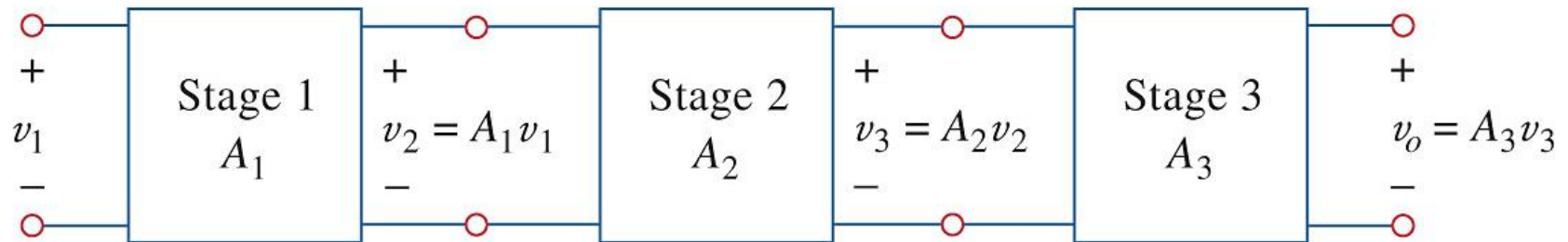- It is common to use multiple op-amp stages chained together – e.g. can increase overall gain
- This is called **cascading**
- Each amplifier is then called a **stage**



Cascaded Op Amps

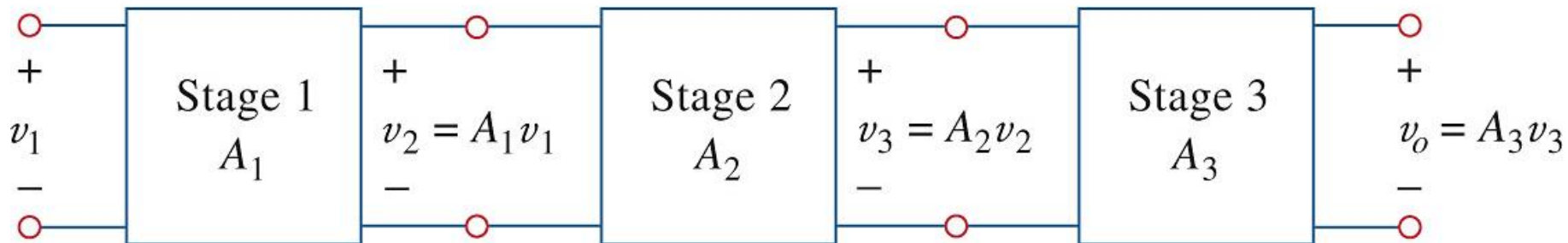- Cascaded op-amps: Head-to-tail arrangement of two or more op amp circuits such that the output to one is the input of the next




$$v_o = A_3 v_3 = A_3 (A_2 v_2) = A_3 A_2 (A_1 v_1)$$

$$\text{Total Amplification } A = A_1 A_2 A_3$$


Example 2:

Determine v_o and i_o

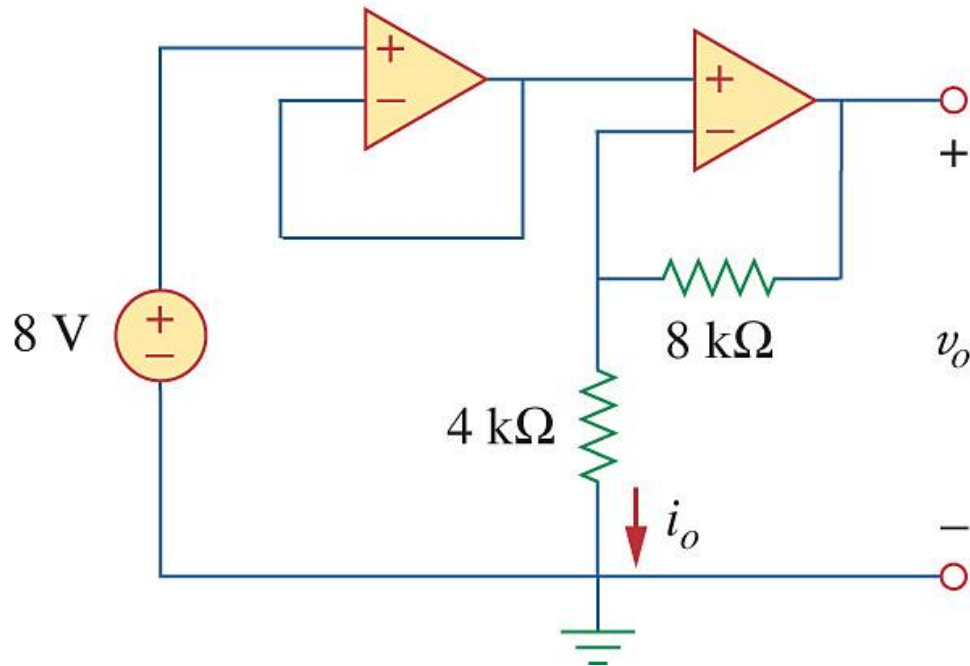

Example 2:

Determine v_o and i_o

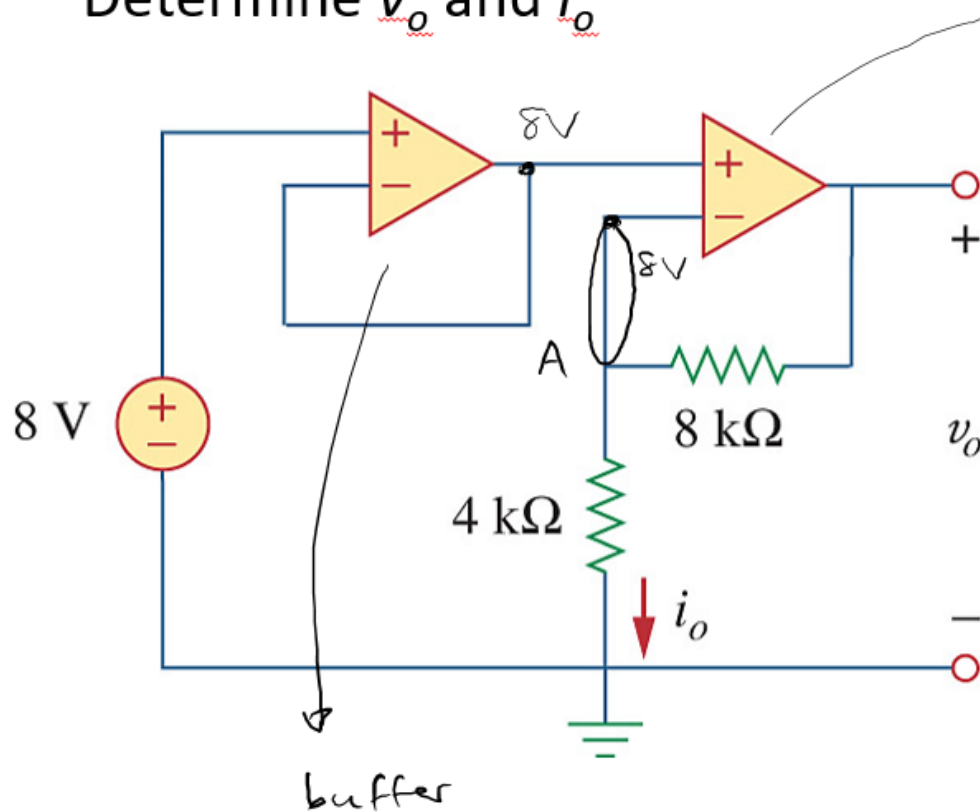

non-inverting amp

KCL at A:

$$\frac{8 - 0}{4k\Omega} + \frac{8 - v_o}{8k\Omega} = 0$$

$$\therefore v_o = 16 + 8$$


$$v_o = 24V$$

$$i_o = \frac{v_-}{4k\Omega} = \frac{8V}{4k\Omega}$$

$$i_o = 2mA$$


Example 3: (Practice Problem 5.10)

If $v_1 = 4\text{ V}$ and $v_2 = 3\text{ V}$, determine v_o

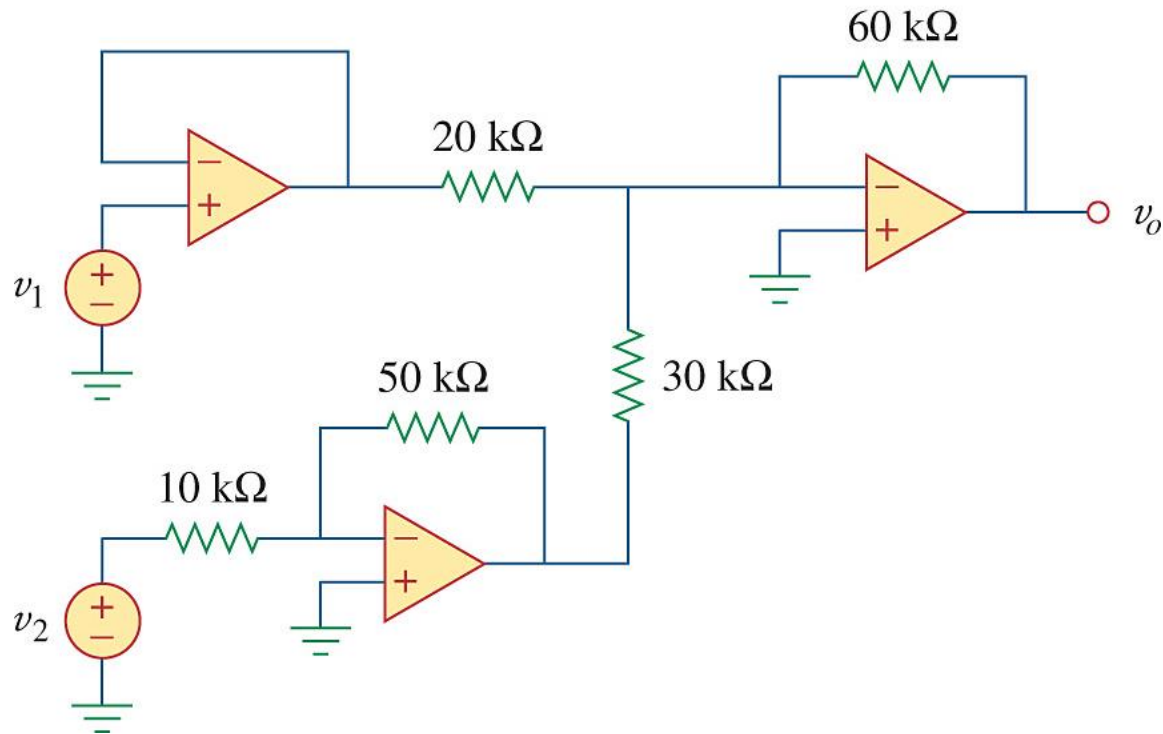

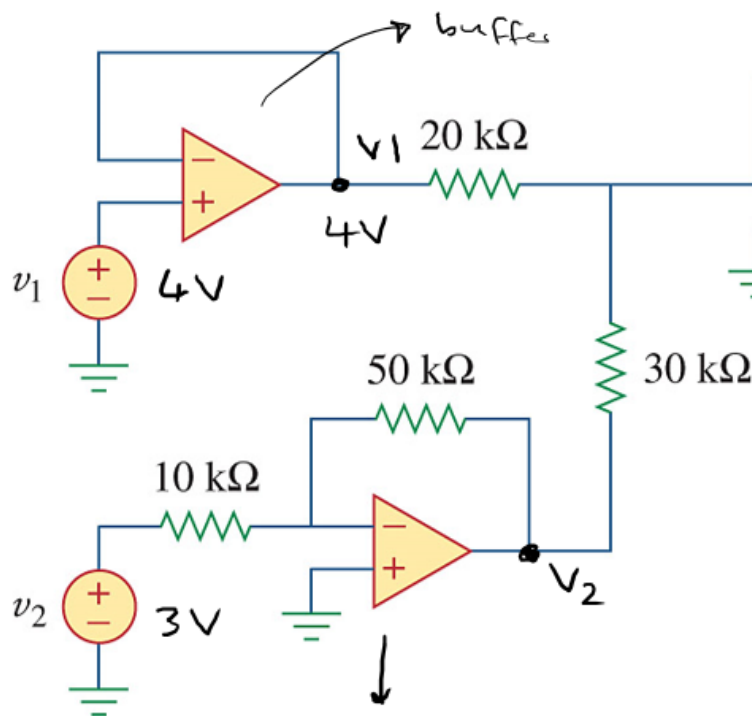Example 3: (Practice Problem 5.10)

If $v_1 = 4\text{ V}$ and $v_2 = 3\text{ V}$, determine v_o



summing amp:

$$V_o = - \left(\frac{R_F}{R_1} v_1 + \frac{R_F}{R_2} v_2 \right)$$

$$V_o = - \left(\frac{60k}{20k} (4V) \right.$$

$$\left. + \frac{60k}{30k} (-15V) \right)$$

$$\therefore V_o = -12 + 30$$

$$V_o = 18V \rightarrow$$


inverting

$$V_2 = - \frac{50k}{10k} (3V)$$

$$V_2 = -15V$$


Example 4:

Determine v_o/v_s if $R = 20\text{ k}\Omega$.

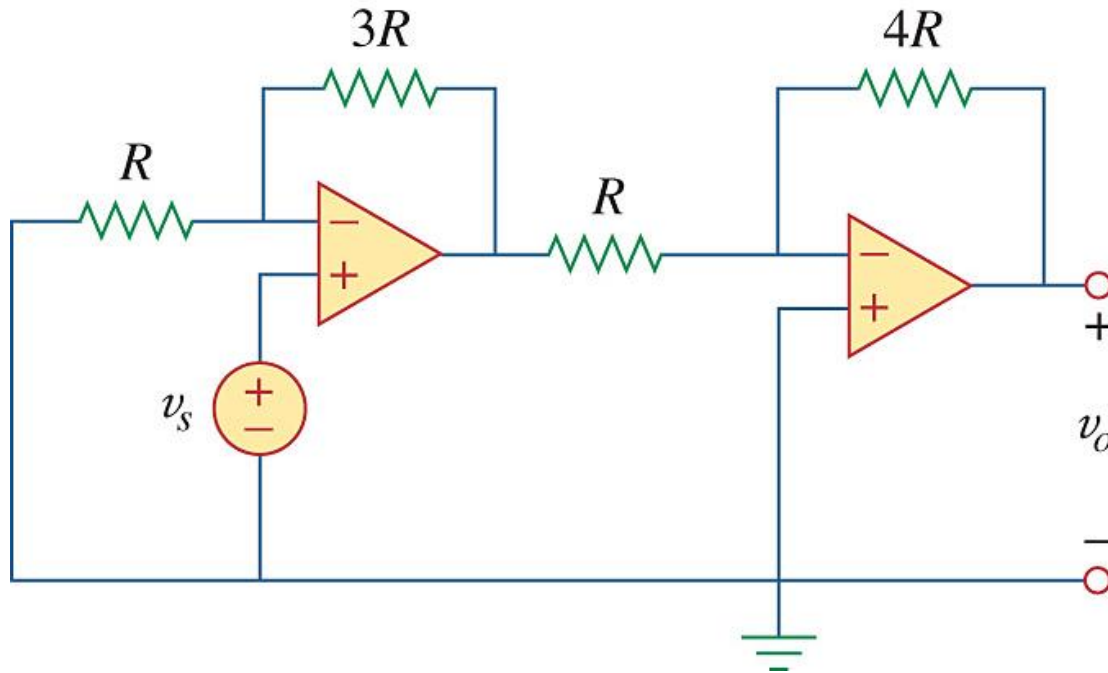

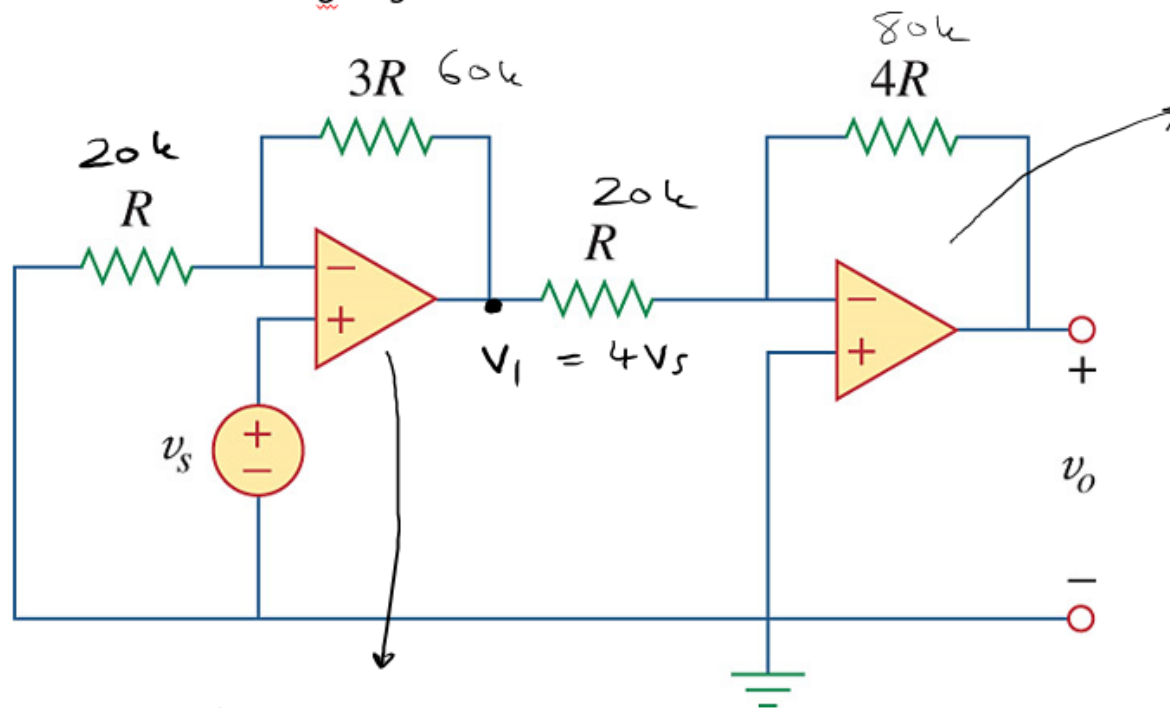Example 4:

Determine v_o/v_s if $R = 20 \text{ k}\Omega$.



inverting

$$V_o = -\frac{R_f}{R_i} V_i$$

$$V_o = -\left(\frac{80 \text{ k}}{20 \text{ k}}\right) 4V_s$$

$$V_o = -16 V_s$$

$$\therefore \frac{V_o}{V_s} = -16$$

non-inverting

$$V_1 = \left(1 + \frac{R_f}{R_i}\right) v_s$$


$$V_1 = \left(1 + \frac{3R}{R}\right) v_s$$


$$\therefore V_1 = 4V_s$$

CLASS PROBLEMS

Example 10: Cascade amplifier circuits

- Determine i_o .

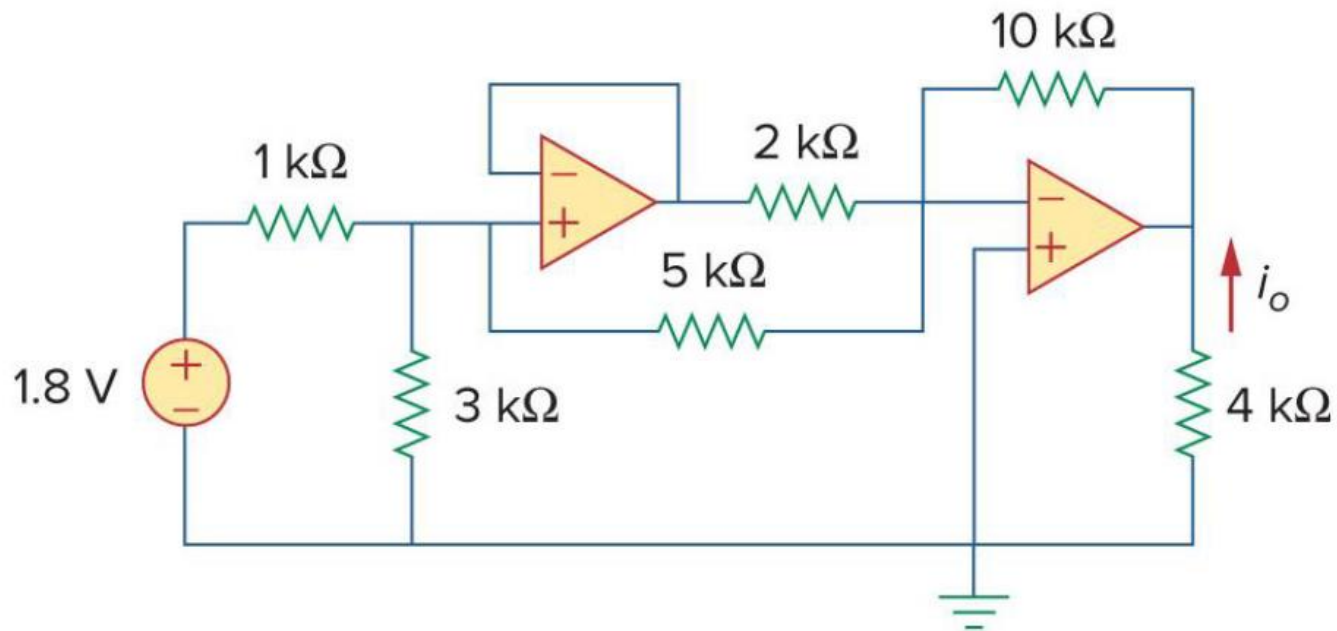

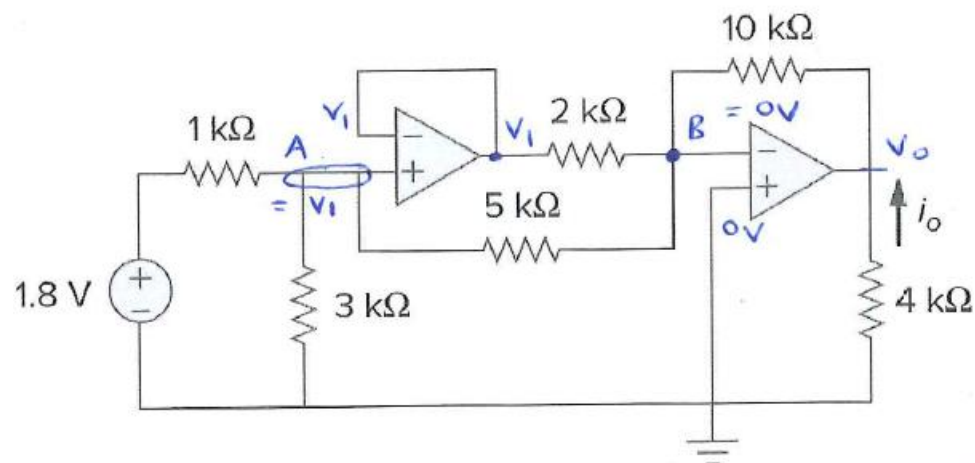

With V_1 the output of the first op-amp, the input voltages = V_1 $\therefore$ node A = V_1
 With V_0 the output of the second op-amp connected to 0V, node B = 0V

Node A: $\frac{V_1 - 1.8}{1k} + \frac{V_1}{3k} + \frac{V_1 - 0}{5k} = 0$

($\times 15k$): $15V_1 - 27 + 5V_1 + 3V_1 = 0$

$\therefore V_1 = 1.174 \text{ V}$

Node B: $\frac{0 - V_0}{10k} + \frac{0 - V_1}{2k} + \frac{0 - V_1}{5k} = 0$ and $V_1 = 1.174 \text{ V}$


$\therefore \frac{-V_0}{10} = 0.8218$


$\therefore V_0 = -8.218 \text{ V}$

$i_0 = \frac{-V_0}{4k\Omega} = \frac{-(-8.218)}{4k\Omega} = 0.2054 \text{ mA}$ 10

Example 11: Cascade amplifier circuits

- Determine v_o .

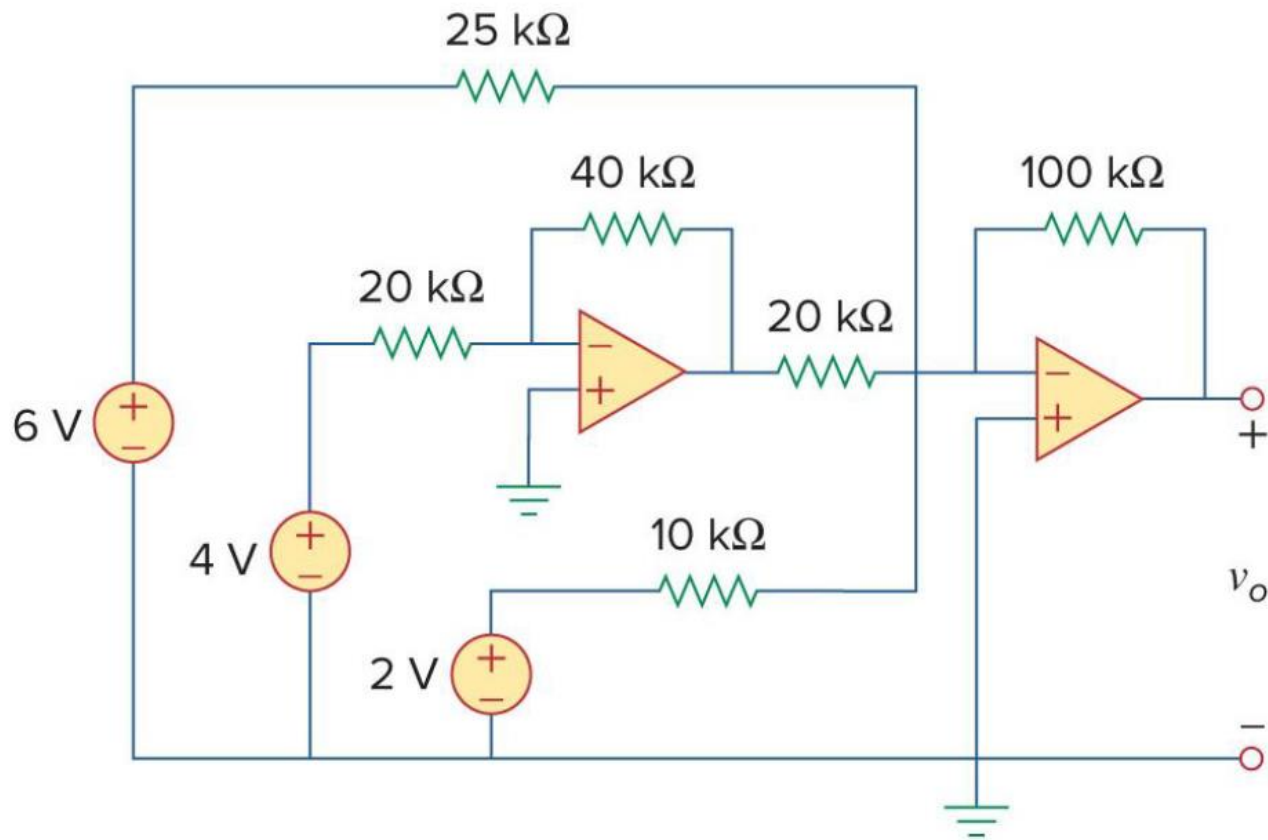

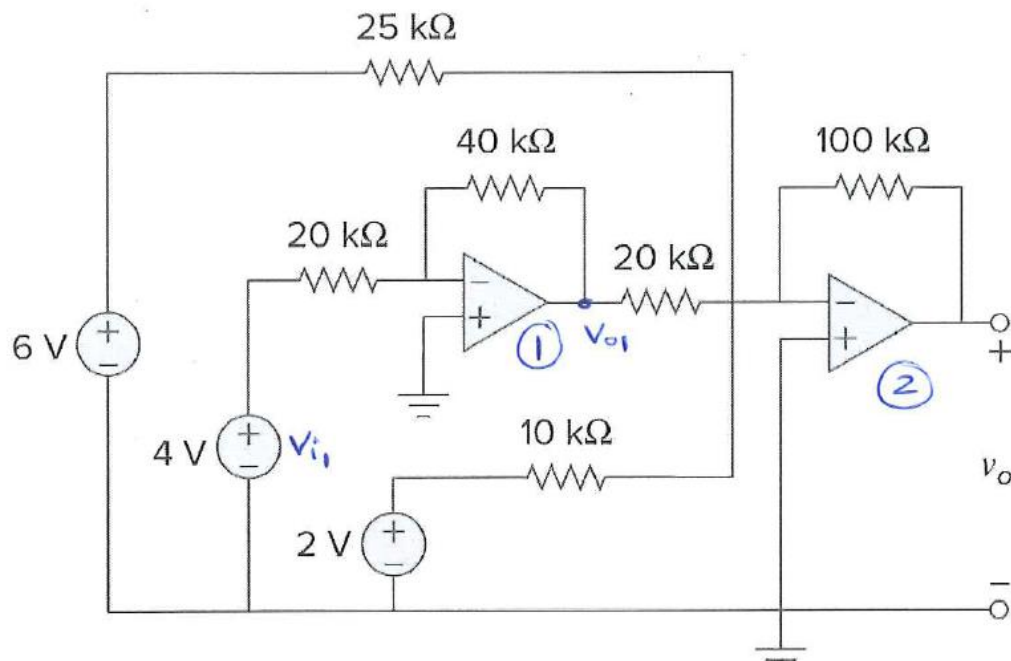

stage ① = inverting op-amp

stage ② = summing op-amp

① inverting:
$$V_{o1} = -\frac{R_f}{R_i} V_{i1} = -\frac{40k}{20k} (4V)$$

$$\therefore V_{o1} = -2(4) = -8V$$

② summing:
$$V_o = -\left(\frac{R_f}{R_1} V_1 + \frac{R_f}{R_2} V_2 + \frac{R_f}{R_3} V_3\right)$$


$$\therefore V_o = -\left(\frac{100k}{25k}(6) + \frac{100k}{20k}(\underset{\substack{\downarrow \\ -8}}{V_{o1}}) + \frac{100k}{10k}(2)\right)$$


$$\therefore V_o = -(24 - 40 + 20)$$

$$\therefore V_o = -4V$$

Example 12: Cascade amplifier circuits

- Determine v_o .

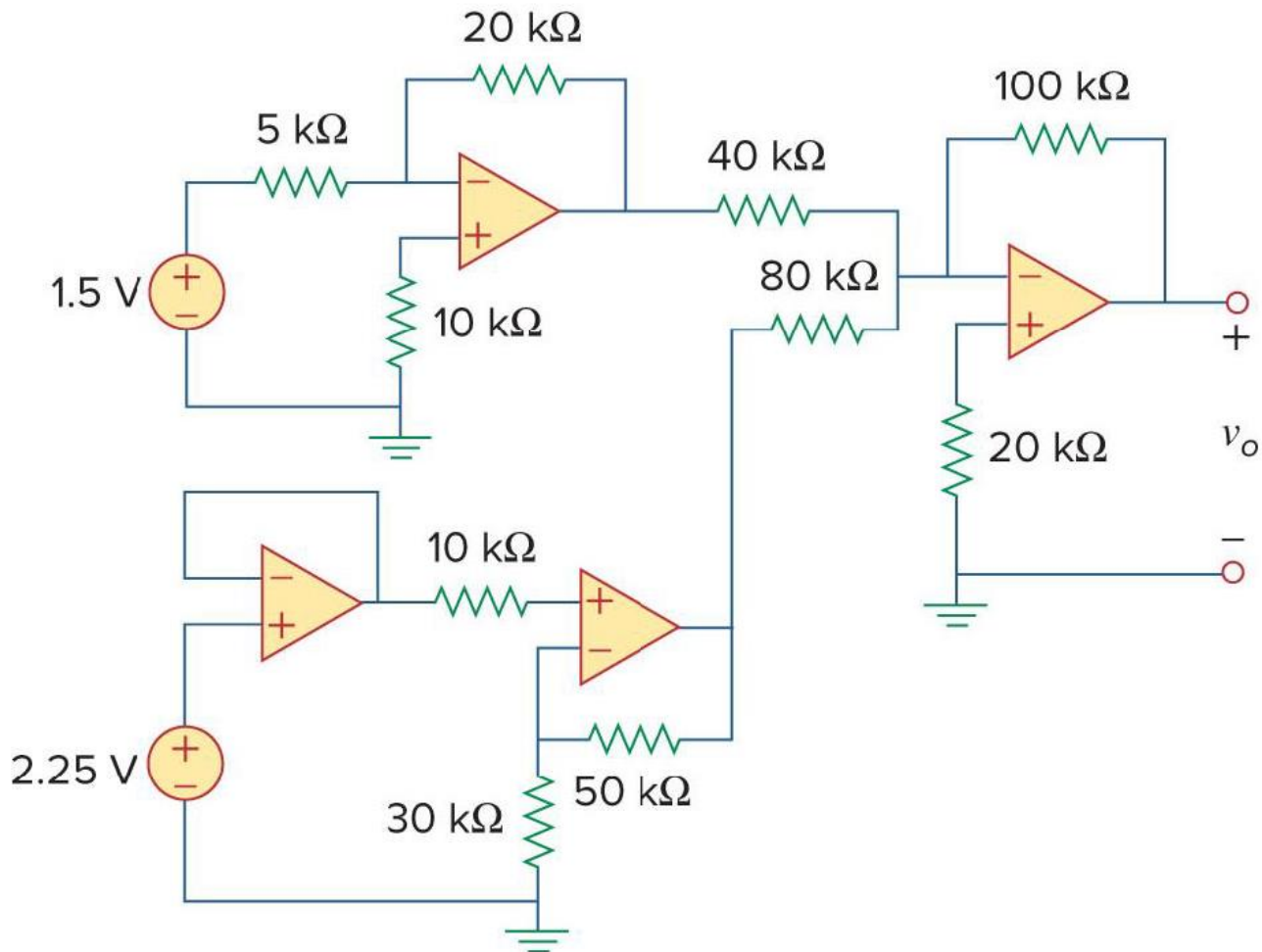

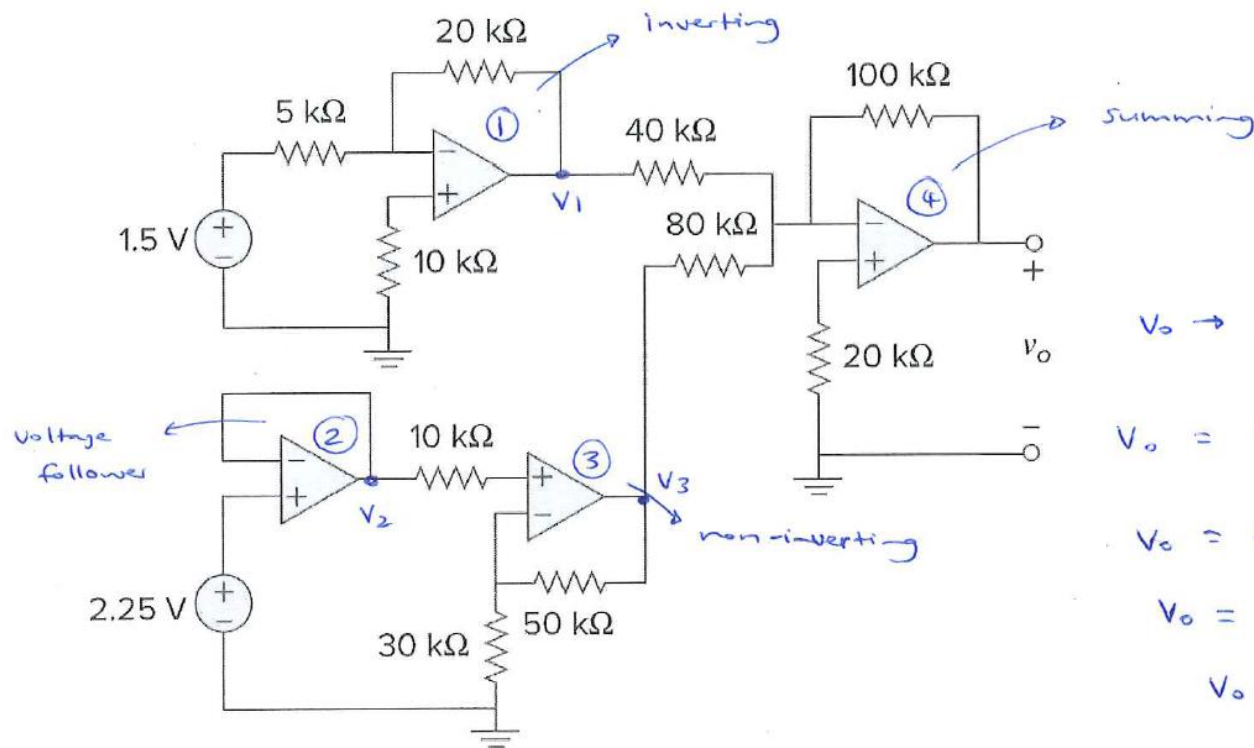

$V_o \rightarrow$ summing:

$$V_o = - \left(\frac{100k}{40k} V_1 + \frac{100k}{80k} V_3 \right)$$

$$V_o = - (2.5(-6) + 1.25(6))$$

$$V_o = - (-15 + 7.5)$$

$$V_o = -(-7.5) = \underline{\underline{7.5V}}$$

$$V_1 \rightarrow \text{inverting} : V_1 = -\frac{20k}{5k} (1.5V) = \underline{\underline{-6V}}$$

$$V_2 \rightarrow \text{follower} : V_2 = V_{in} = \underline{\underline{2.25V}}$$

$$V_3 \rightarrow \text{non-inverting} : V_3 = \left(1 + \frac{50k}{30k} \right) V_{in}$$

$$\text{and } V_{in} = V_2 = 2.25V$$


$$\therefore V_3 = (1 + 1.667)(2.25) = \underline{\underline{6V}}$$

Summary

- Ideal op-amps $i_+ = i_- = 0$


$$v_+ = v_-$$

- Inverting op-amps

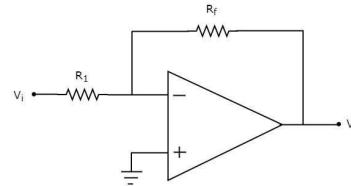


$$v_o = -\frac{R_f}{R_1} v_i$$

- Non-inverting op-amps

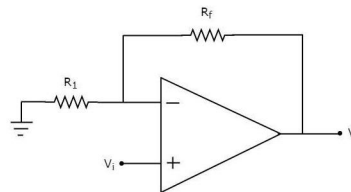


$$v_o = \left(1 + \frac{R_f}{R_1}\right) v_i$$

- Buffer/voltage follower

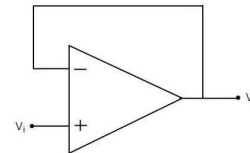


$$v_o = v_i$$

- Summing amplifier

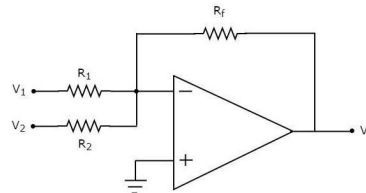

$$v_o = -\left(\frac{R_f}{R_1} v_1 + \frac{R_f}{R_2} v_2 + \frac{R_f}{R_3} v_3\right)$$

- Difference amplifier

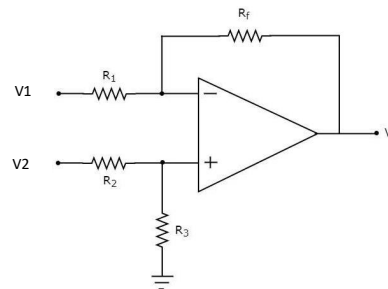

$$v_o = \frac{R_2(1 + R_1/R_2)}{R_1(1 + R_3/R_4)} v_2 - \frac{R_2}{R_1} v_1$$

- Cascaded op-amp circuits