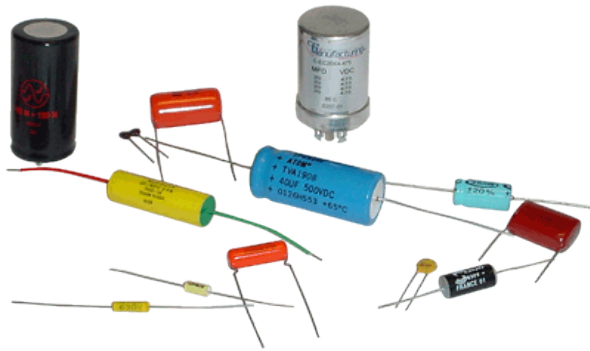




EBN 122

Chapter 6: Capacitors and Inductors

Inductors and Series and Parallel Inductors

Chapter 6 overview

✓ 6.2. Capacitors

✓ 6.3. Series and Parallel
Capacitors

6.4. Inductors

6.5. Series and Parallel
Inductors

Inductors

- Passive element that stores energy in its **magnetic field**
- Any conductor of electric current has inductive properties
- Consists of coil with many turns of conducting wire around a core (iron, steel, air)

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display



(a)




(b)



(c)

Courtesy of Tech America

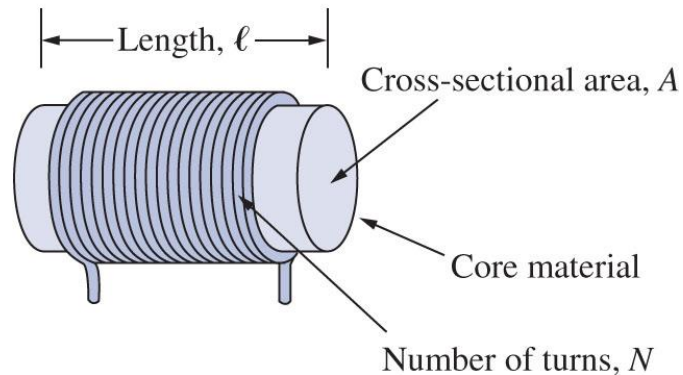Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display



Inductors

- If a current is allowed to pass through an inductor, the voltage v across the inductor is proportional to the time rate of change of current:

$$v = L \frac{di}{dt}$$

- **L = inductance** of inductor
- Inductance (L) is measured in henry (H)
- 1 henry = 1 volt-second per ampere

Inductors

- Inductance = opposition to the change of current flowing through an inductor
- L is dependent on **physical dimensions** of inductor, e.g. for solenoid:


$$L = \frac{N^2 \mu A}{l} [H]$$

N = number of turns

A = cross sectional area of the core [m²]

l = length of coil [m]


μ = permeability of the core [H/m]

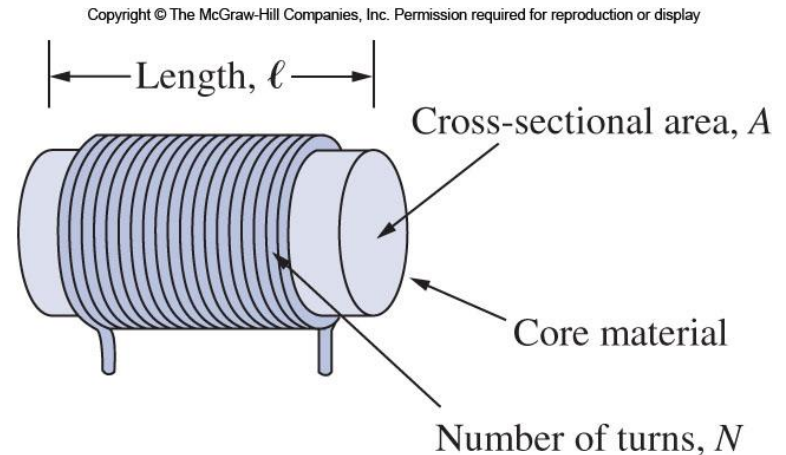

Inductors

- Typical values = microhenrys (μH) to henrys (H)
- Fixed or variable

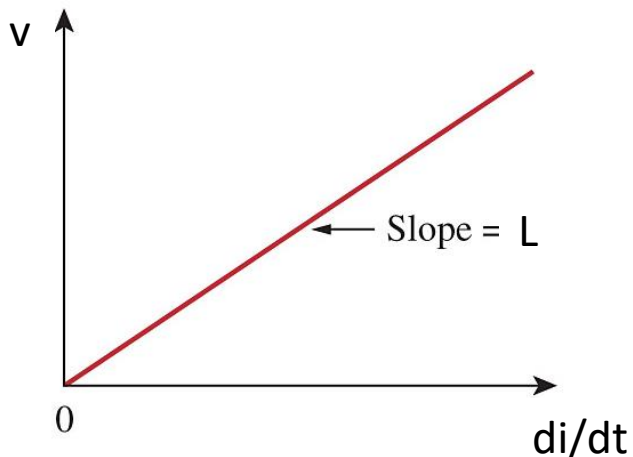
- **Voltage-current** relationship of inductor:



$$v = L \frac{di}{dt}$$

Linear inductors
→ independent of current

passive sign
convention

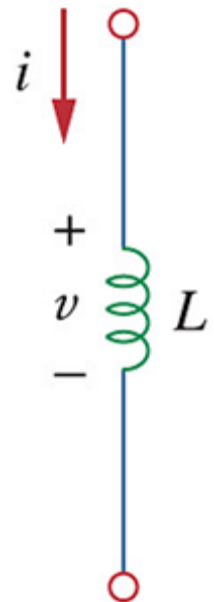

Inductors

- **Current-voltage** relationship for inductor:

$$v = L \frac{di}{dt} \longrightarrow di = \frac{1}{L} v dt$$

Integrating:

$$i = \frac{1}{L} \int_{t_0}^t v(t) dt + i(t_0)$$

$i(t_0)$ = total current for $-\infty < t < t_0$ and $i(-\infty) = 0$


→ $i(-\infty) = 0$ is reasonable as there was a time in the past when the inductor had no current

Inductors

- **Power (p)** delivered to inductor:

$$p = vi = L \frac{di}{dt} i$$

from $v = L \frac{di}{dt}$

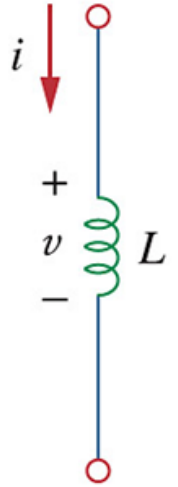

- **Energy (w)** stored in inductor:

$$w = \frac{1}{2} Li^2$$

from $w = \int_{-\infty}^t p dt$

Inductors

Important properties of inductors:


$$v = L \frac{di}{dt}$$

1. Inductor is a **short circuit** to dc
(dc $\rightarrow$ current constant $\rightarrow di/dt = 0$
 $\rightarrow v = 0$, thus short circuit)
2. **Current** through an inductor **cannot change instantaneously**
($di/dt = \infty \rightarrow v = \infty$, not possible)
3. Does not dissipate energy, but
stores energy when **taking** power
from circuit **(+p)**
or
returns previously stored energy
when **delivering** power to circuit **(-p)**



Inductors

- Current and voltage over time:

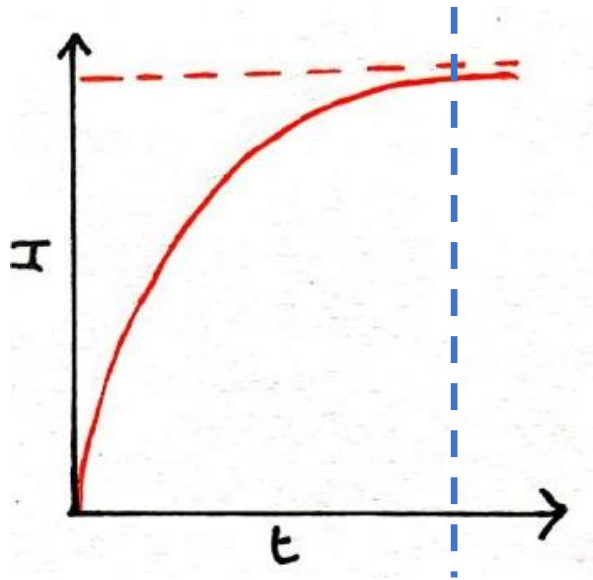


1. Current flows through inductor and magnetic field builds

DC

DC-state or steady-state

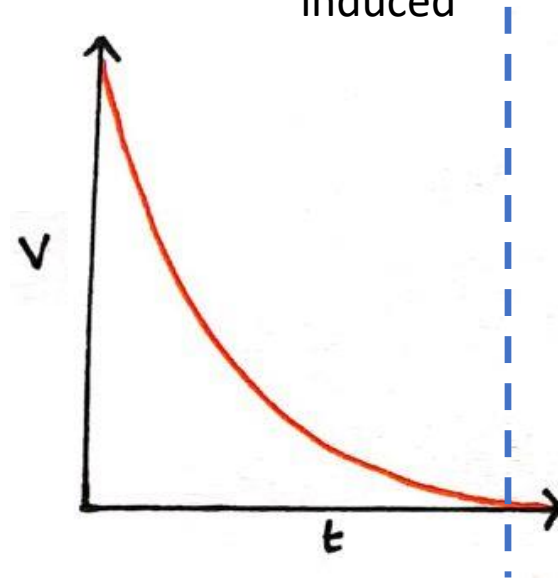2. When magnetic field at maximum, no more voltage is induced



DC

Inductors summary


$$L = \frac{N^2 \mu A}{l}$$

$$v = L \frac{di}{dt}$$

$$i = \frac{1}{L} \int_{t_0}^t v(t) dt + i(t_0)$$

$$p = vi = L \frac{di}{dt} i$$


$$w = \frac{1}{2} Li^2$$

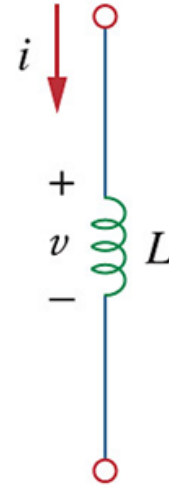

DC conditions:
short circuit

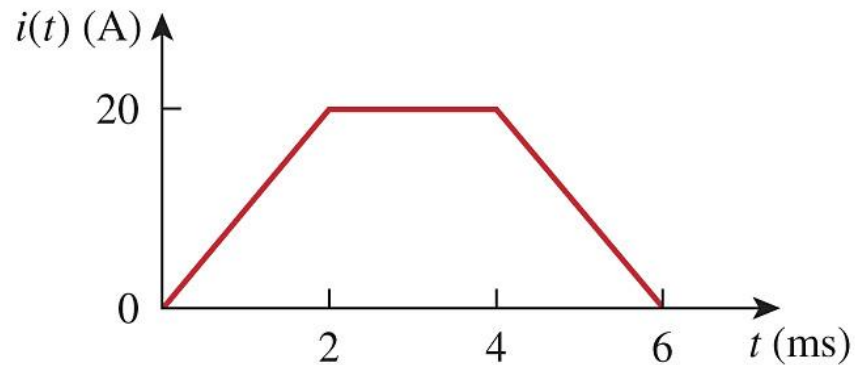
Example

The current through a 10 mH inductor is shown below. Determine the voltage across the inductor at $t = 1, 3$ and 5 ms.



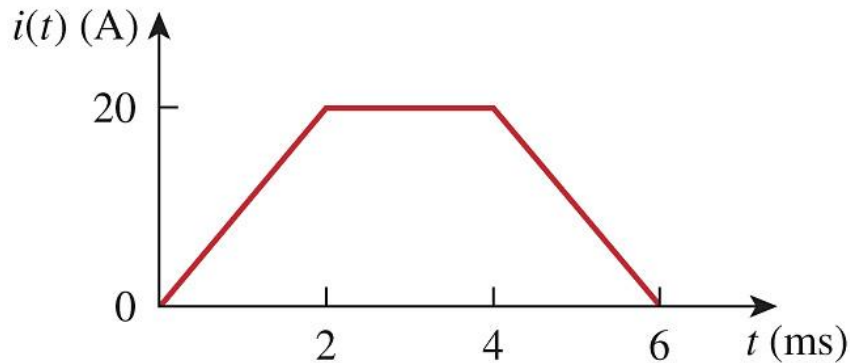Example

The current through a 10 mH inductor is shown below. Determine the voltage across the inductor at $t = 1, 3$ and 5 ms.



$$v(t) = 0.01 \frac{di}{dt} = 0.01 \frac{\Delta i}{\Delta t}$$

$$v(1\text{ms}) = 0.01 \frac{20 - 0}{0.002 - 0} = \underline{100 \text{ V}}$$

$$v(3\text{ms}) = \underline{0 \text{ V}} \text{ because } \frac{di}{dt} = 0$$

$$v(5\text{ms}) = \underline{-100 \text{ V}}$$

OR

$$i(t) = \frac{\Delta i}{\Delta t} t + c = \frac{20 - 0}{0.002 - 0} t + 0 = 10t \text{ kA}$$

$$v(t) = 0.01 \frac{di}{dt} = 0.01 \times 10000 = 100 \text{ V}$$

Example 5: Inductor – voltage and current

The voltage across a 2 H inductor is $v(t) = 10(1 - t)$ V. Determine the current through the inductor at $t = 4$ s if $i(0) = 2$ A.

Example 5: Inductor – voltage and current

The voltage across a 2 H inductor is $v(t) = 10(1 - t)$ V. Determine the current through the inductor at $t = 4$ s if $i(0) = 2$ A.

$$i(t) = \frac{1}{L} \int_{t_0}^t v(\tau) d\tau + i(t_0)$$

$\downarrow$
 $= 2 \text{ A}$

$$i(4) = \frac{1}{2} \int_0^4 [10(1-t)] dt + 2 \text{ A}$$

$$i(4) = 5 \left(t - \frac{t^2}{2} \right) \Big|_0^4 + 2 \text{ A}$$

$$= 5t - \frac{5}{2} t^2 \Big|_0^4 + 2 \text{ A}$$

$$= 5(4) - \frac{5}{2} (4^2) + 2 \text{ A}$$


$$\therefore i(4) = 20 - 2.5(16) + 2$$

$$= 20 - 40 + 2$$

$$\therefore i(4) = \underline{\underline{-18 \text{ A}}}$$


Example 6: Inductor – voltage, current and energy under DC condition

Determine v_C , i_L and the energy stored in both the capacitor and the inductor for the DC circuit below.

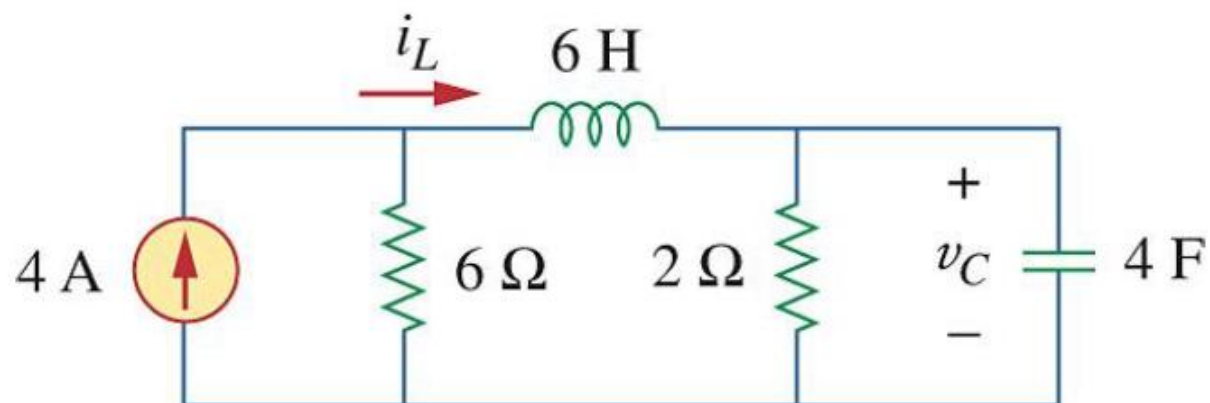


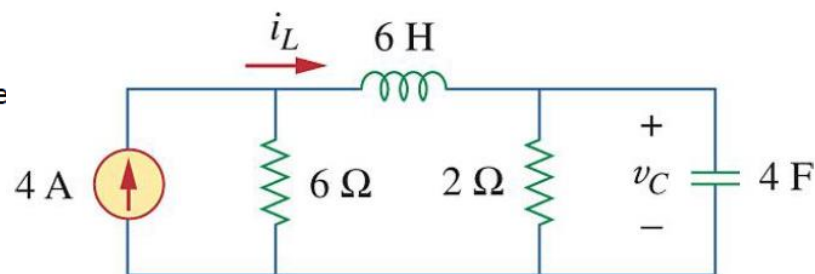Example 6: Inductor – voltage, current and energy under DC condition

Determine v_C , i_L and the energy stored in both the capacitor and the inductor for the DC circuit below.



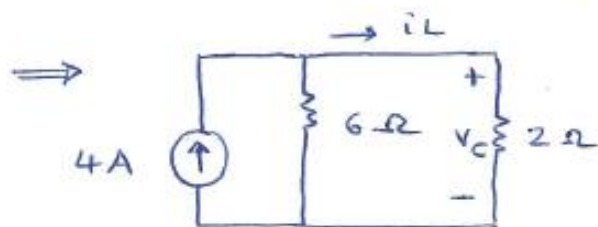DC $\Rightarrow$ capacitor = open circuit, inductor = short circuit



$$i_L = 4 \left(\frac{6}{6+2} \right) \text{ current division}$$

$$i_L = 3 \text{ A}$$

$$v_C = 2 \Omega \times i_L \\ = 2 \times 3 = 6 \text{ V}$$


$$W_{\text{capacitor}} = \frac{1}{2} C v^2 \\ = \frac{1}{2} (4 \text{ F}) (6^2) = 72 \text{ J}$$

$$W_{\text{inductor}} = \frac{1}{2} L i^2 \\ = \frac{1}{2} (6 \text{ H}) (3^2) = 27 \text{ J}$$

Example 7: Inductor – voltage and current

If $i_1(t) = 0.6e^{-2t}$ A and $i(0) = 1.4$ A, find:


- 1) $i_2(0)$
- 2) $i_2(t)$ and $i(t)$, and
- 3) $v_1(t)$, $v_2(t)$ and $v(t)$

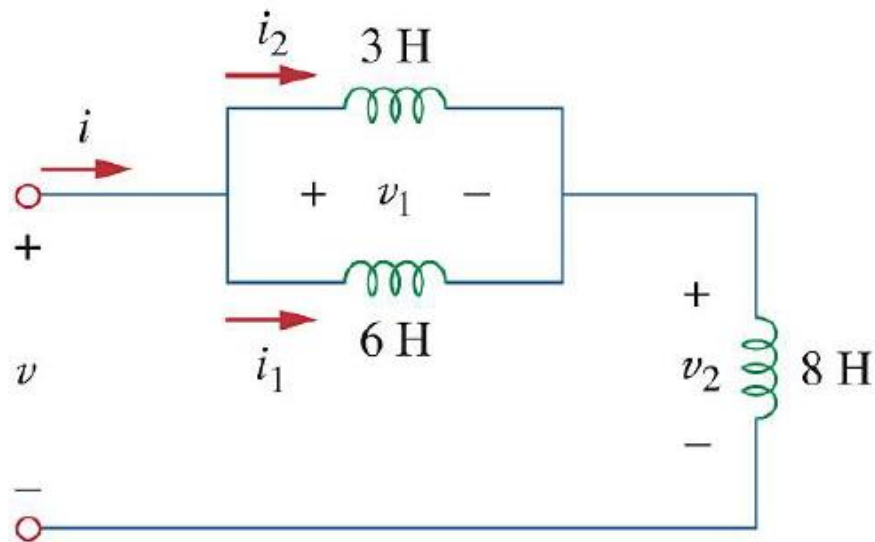

Example 7: Inductor – voltage and current

If $i_1(t) = 0.6e^{-2t}$ A and $i(0) = 1.4$ A, find:

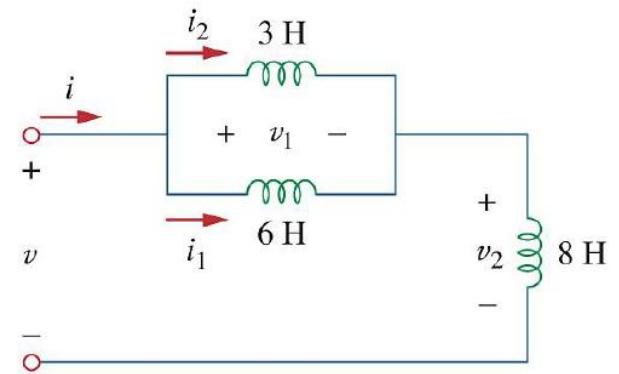- 1) $i_2(0)$
- 2) $i_2(t)$ and $i(t)$, and
- 3) $v_1(t)$, $v_2(t)$ and $v(t)$



$$1) \quad i_1(0) = 0.6e^{-2(0)} = 0.6 \quad \text{and KCL: } i(t) = i_1(t) + i_2(t)$$

$$\therefore i_2(0) = i(0) - i_1(0) \quad \therefore i_2(0) = 1.4 - 0.6 = 0.8 \text{ A}$$

$$2) \quad i_2(t) = \frac{1}{L} \int v_1 dt + i_2(0) \quad \text{and} \quad v_1(t) = L_1 \frac{di_1}{dt}$$

$$i_2(t) = \frac{1}{3} \int_0^t (-7.2 e^{-2t}) dt + 0.8$$

$$\therefore i_2(t) = \frac{-7.2}{3} \left(-\frac{e^{-2t}}{2} \right) \Big|_0^t + 0.8$$

$$v_1(t) = -7.2 e^{-2t} \text{ V}$$

$$i_2(t) = 1.2(e^{-2t} - 1) + 0.8 = 1.2e^{-2t} - 0.4 \text{ A}$$

$$i(t) = i_1(t) + i_2(t) = 0.6e^{-2t} + 1.2e^{-2t} - 0.4 = 1.8e^{-2t} - 0.4 \text{ A}$$

$$3) \quad v_2(t) = L \frac{di}{dt} = 8 \frac{d}{dt} (1.8e^{-2t} - 0.4)$$


$$= 8(-2(1.8)e^{-2t}) = -28.8e^{-2t}$$

$$\text{KVL: } v(t) = v_1(t) + v_2(t) = -7.2e^{-2t} + -28.8e^{-2t}$$


$$\therefore v(t) = -36e^{-2t} \text{ V}$$

Series and parallel inductors

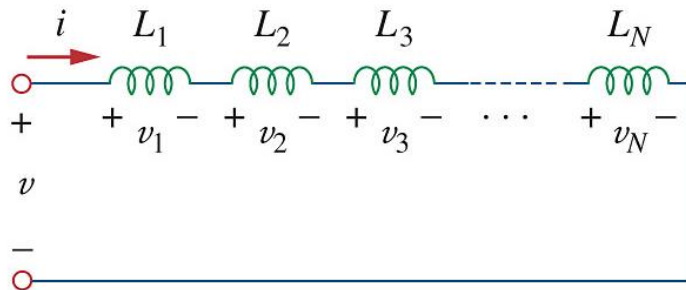
- Series and parallel combinations simplify circuits
- Equivalent inductance L_{eq} can be used




(a)

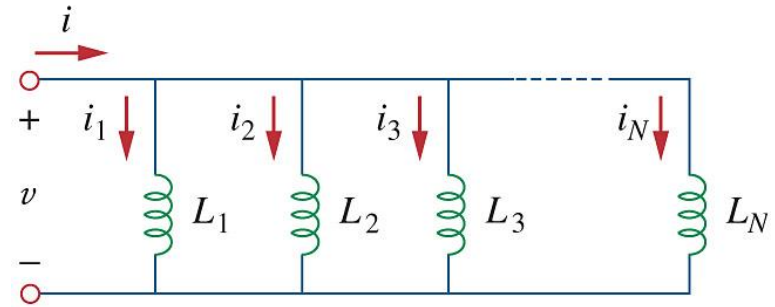

(a)

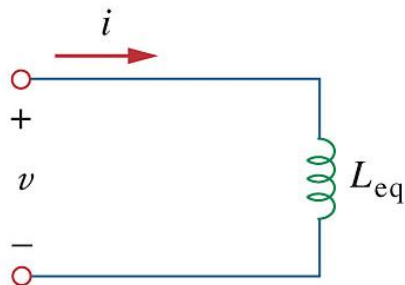

(b)

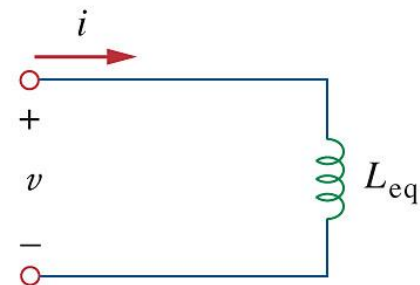

(b)


Series inductors

- Current through each inductor is the same
- Applying KVL:


$$v = v_1 + v_2 + v_3 + \dots + v_N$$

$$v = L_{eq} \frac{di}{dt} = L_1 \frac{di}{dt} + L_2 \frac{di}{dt} + L_3 \frac{di}{dt} + \dots + L_N \frac{di}{dt}$$

$$L_{eq} = L_1 + L_2 + \dots + L_N$$

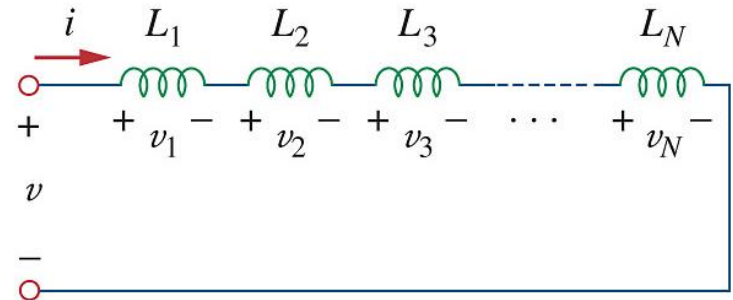

(a)

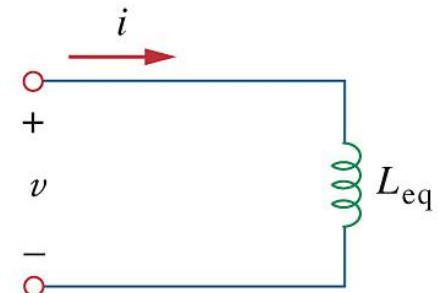

(b)

**Series inductors
= sum of inductors**

Parallel inductors



- Voltage across each inductor the same
- Applying KCL:

$$i = i_1 + i_2 + i_3 + \cdots + i_N$$

$$i = \frac{1}{L_{eq}} \int_{t_0}^t v dt + i(t_0) =$$


$$\frac{1}{L_1} \int_{t_0}^t v dt + i_1(t_0) + \dots + \frac{1}{L_N} \int_{t_0}^t v dt + i_N(t_0)$$
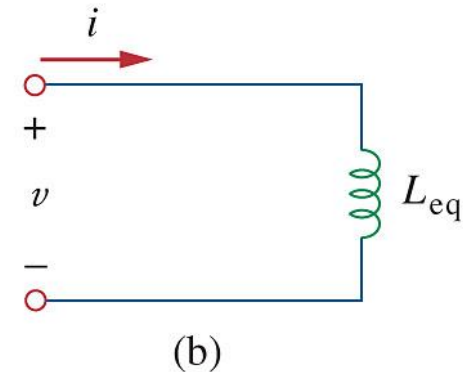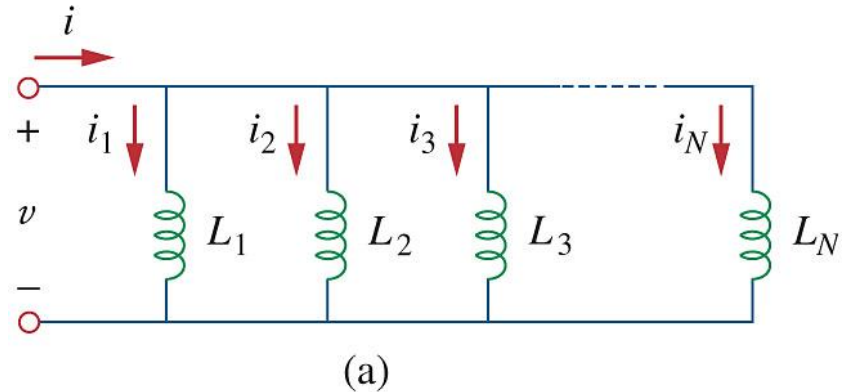
$$\frac{1}{L_{eq}} = \frac{1}{L_1} + \frac{1}{L_2} + \dots + \frac{1}{L_N}$$




Parallel inductors
→ similar to parallel resistors


Series and parallel inductors

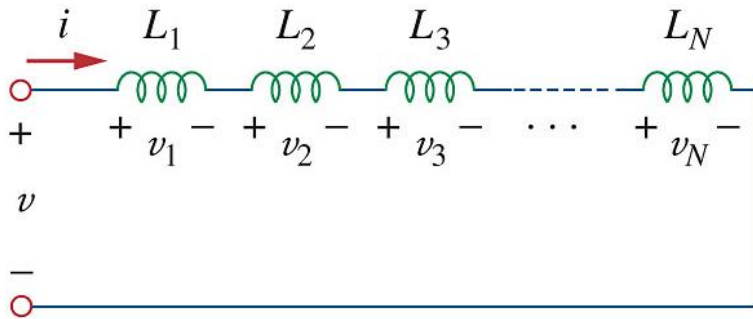

(a)

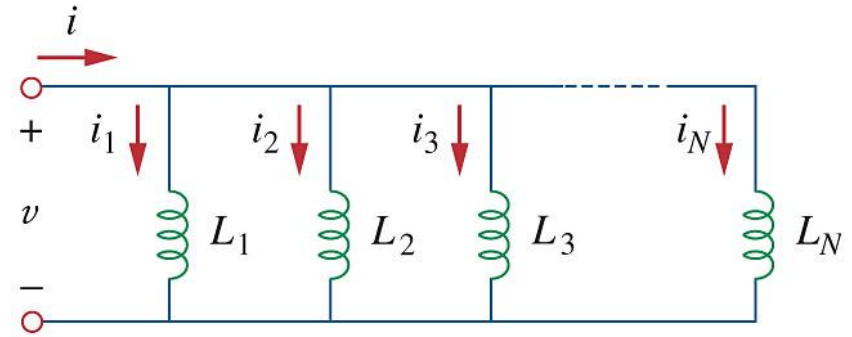


(a)

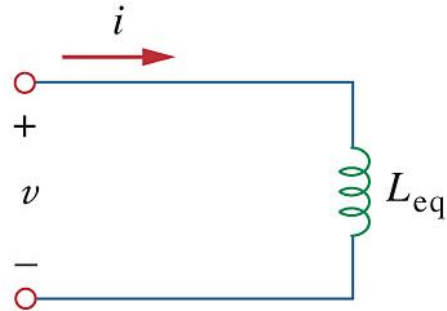

(b)

$$L_{eq} = L_1 + L_2 + \dots + L_N$$

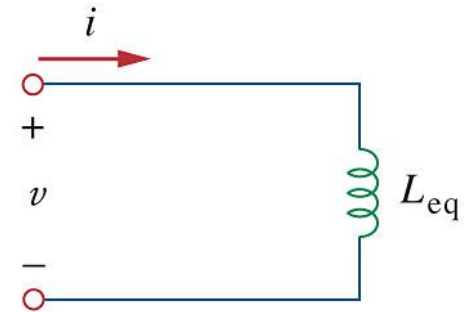

(b)

$$\frac{1}{L_{eq}} = \frac{1}{L_1} + \frac{1}{L_2} + \dots + \frac{1}{L_N}$$

Summary


Important characteristics of the basic elements

Relation	Resistor (R)	Capacitor (C)	Inductor (L)
$v - i$:	$v = iR$	$v = \frac{1}{C} \int_{t_0}^t i(\tau) d\tau + v(t_0)$	$v = L \frac{di}{dt}$
$i - v$:	$i = v/R$	$i = C \frac{dv}{dt}$	$i = \frac{1}{L} \int_{t_0}^t v(\tau) d\tau + i(t_0)$
P or w:	$p = i^2 R = \frac{v^2}{R}$	$w = \frac{1}{2} C v^2$	$w = \frac{1}{2} L i^2$
Series	$R_{eq} = R_1 + R_2$	$C_{eq} = \frac{C_1 C_2}{C_1 + C_2}$	$L_{eq} = L_1 + L_2$
Parallel	$R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$	$C_{eq} = C_1 + C_2$	$L_{eq} = \frac{L_1 L_2}{L_1 + L_2}$
At dc:	Same	Open circuit	Short circuit
Circuit variable that cannot change abruptly:	Not applicable	v	i

Example 8: Inductor – equivalent inductance


Practice Problem 6.11

Calculate L_{eq} .

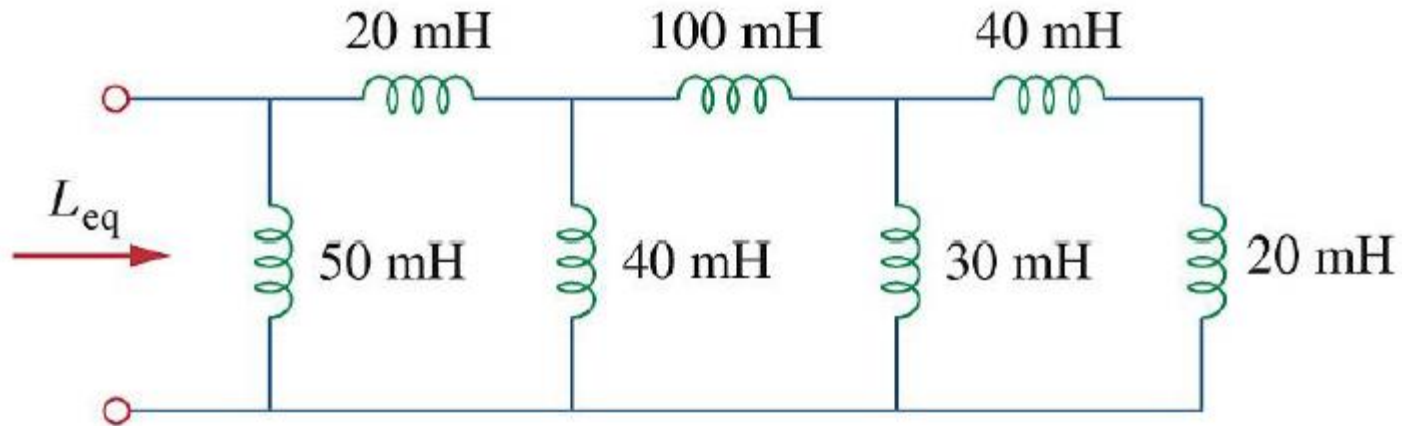

Example 8: Inductor – equivalent inductance

Calculate L_{eq} .

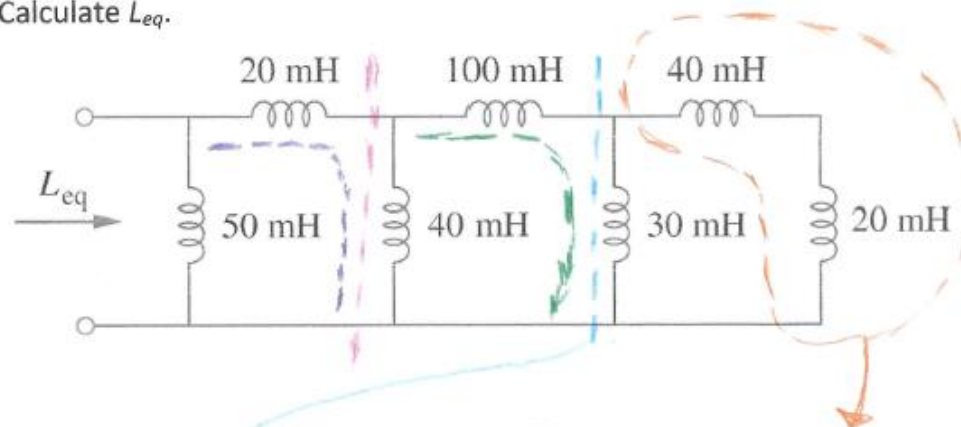

$$\textcircled{1} \quad 40 \text{ mH} + 20 \text{ mH} = \underline{60 \text{ mH}}$$

$$\textcircled{2} \quad 30 \text{ mH} \parallel \underline{60 \text{ mH}} = \frac{30 \times 60}{30 + 60} = \underline{20 \text{ mH}}$$

$$\textcircled{3} \quad 100 \text{ mH} + \underline{20 \text{ mH}} = \underline{120 \text{ mH}}$$

$$\textcircled{4} \quad 40 \text{ mH} \parallel \underline{120 \text{ mH}} = \frac{40 \times 120}{40 + 120} = \underline{30 \text{ mH}}$$

$$\textcircled{5} \quad 20 \text{ mH} + \underline{30 \text{ mH}} = \underline{50 \text{ mH}}$$

$$L_{eq} = 50 \text{ mH} \parallel \underline{50 \text{ mH}}$$

$$= \frac{50 \times 50}{50 + 50} \quad \therefore L_{eq} = \underline{25 \text{ mH}}$$