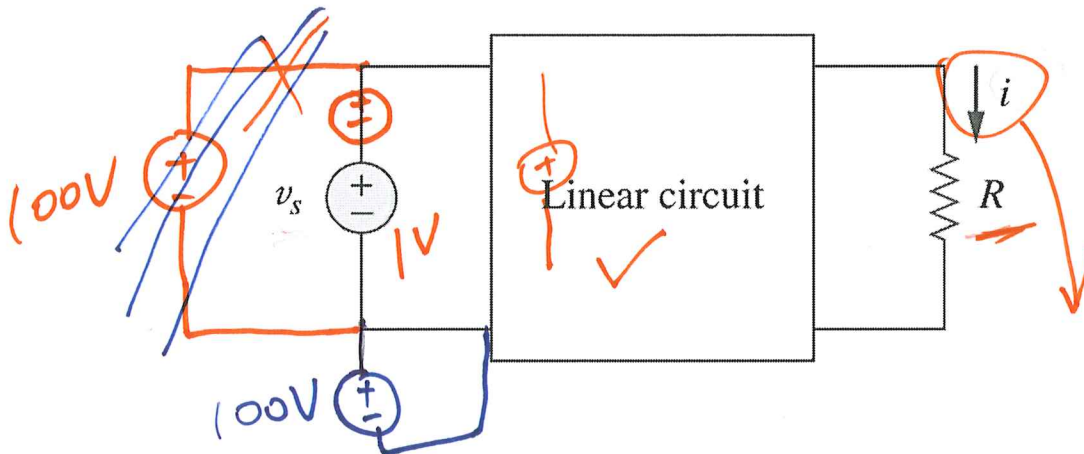


L#13: Linearity and superposition



If $v_s = 10V \Rightarrow i = 2 A$

then:

$v_s = 1V \Rightarrow i = \underline{0.2} A$

$v_s = 100V \Rightarrow i = \underline{20} A$

try add above two

$\underline{20.2}$

Two properties


➤ Homogeneity (scaling)

$\underline{V = i R} ; \underline{k V = k i R}$

➤ Additivity

$v_1 \text{ and } v_2 \quad \left. \begin{array}{l} V_1 = i_1 R \\ V_2 = i_2 R \end{array} \right\} \Rightarrow V_1 + V_2 = (i_1 + i_2) R$


Example #1: Determine I_o .

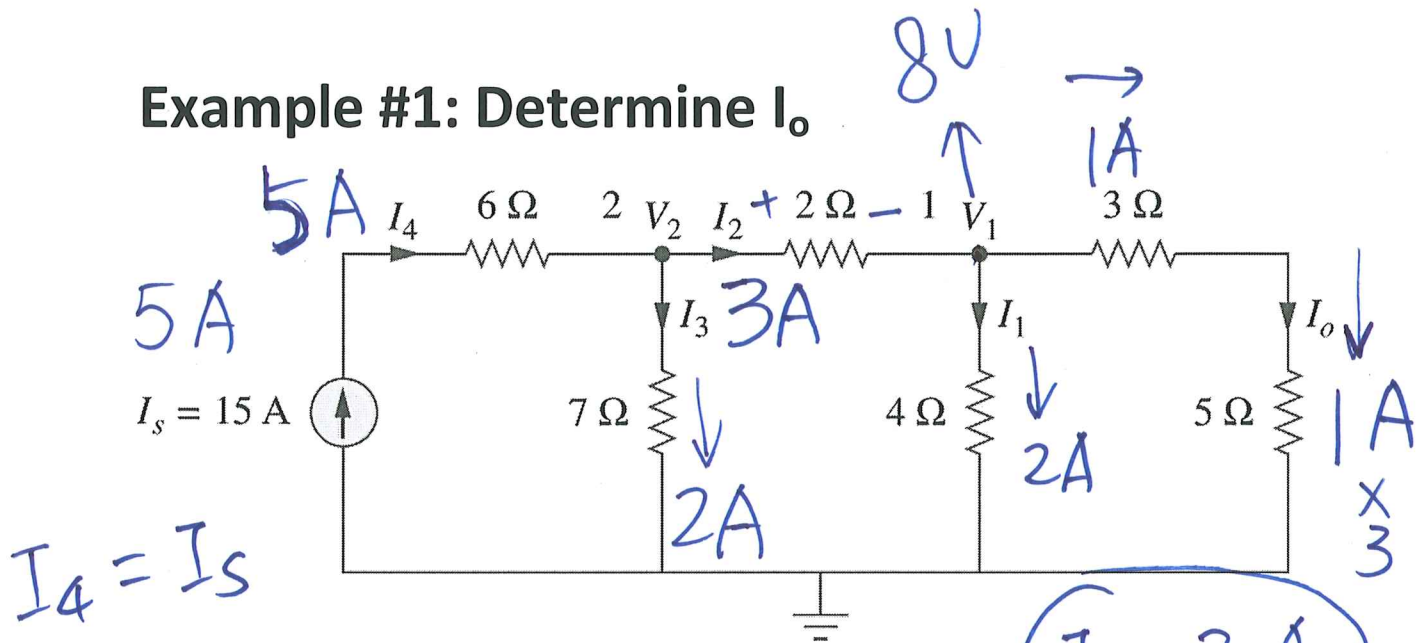


Assume $I_o = 1\text{ A}$

$V_1 = 8\text{ V}$, $I_1 = 2\text{ A}$, $V_2 = 14\text{ V}$

Example #2: Determine V_o .

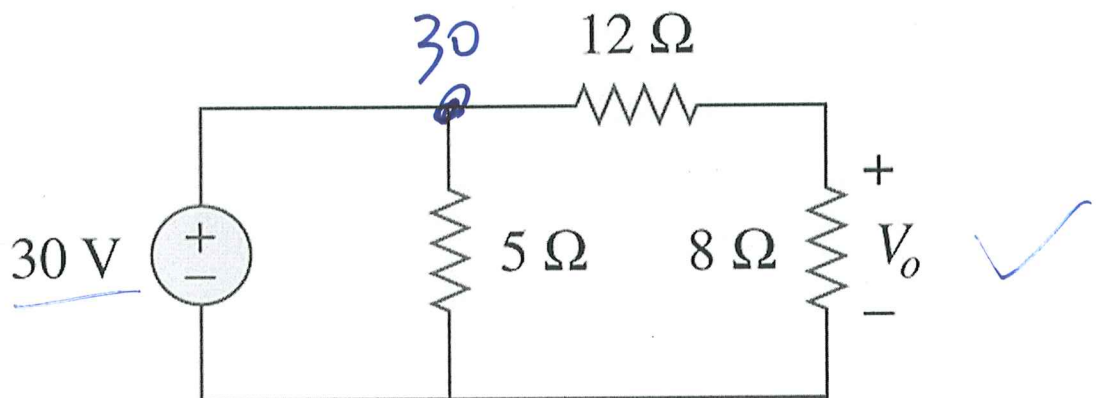

Superposition Theorem

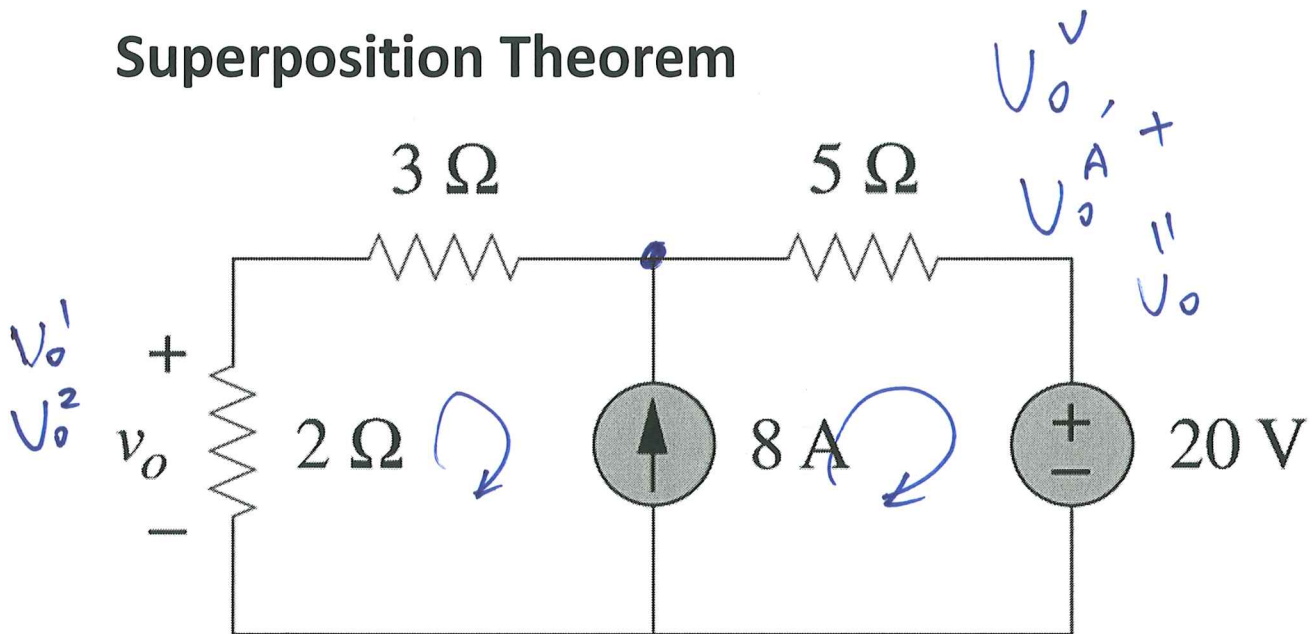

1. Turn off; 2. Repeat; 3. Sum.



1. Turn off **INDEPENDENT** sources

Voltage source $\rightarrow$ <u>Short circuit</u>	
Current source $\rightarrow$ <u>Open circuit</u>	
Dependent Source	Leave as it is

2. Repeat Step 1 with analysis


3. Summation *Additivity*

Example #1: Find I.

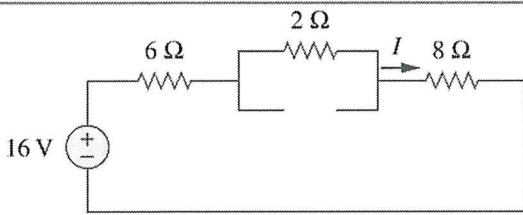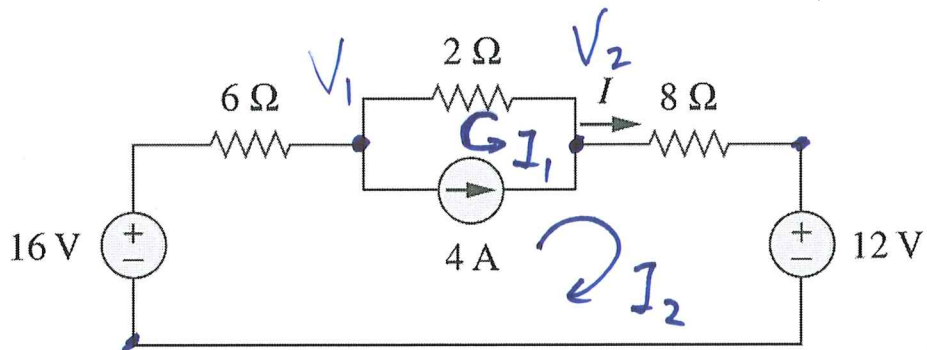

$$I_1 = \frac{16}{16} = 1A$$



$$I_1 = \frac{16}{16} = 1A$$

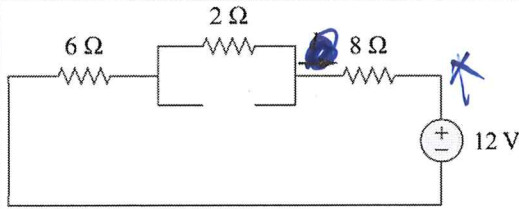

$$I_2 = -\frac{12}{16} = -0.75A$$

$$I_3 = 4A \cdot \frac{2}{16} = 2 + 14$$

$$= 0.5A$$

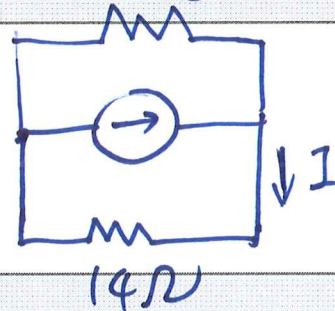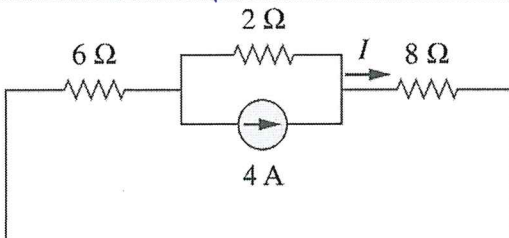

Total

$$I = I_1 + I_2 + I_3 = 1 - 0.75 + 0.5 = 0.75A$$

$$M1: I_1 + I_2 = 4$$




$$M2: -16 + 6I_2 - 2I_1 + 8I_2 + 12 = 0$$

$$\Rightarrow I = 4 - I_1 = 0.75A$$

$$V_2: I = \frac{8}{V_2 - 12} = 4 + \frac{2}{V_1 - V_2} = 0.75A$$

$$V_1: \frac{6}{V_1 - 16} + 4 + \frac{2}{V_1 - V_2} = 0$$

Example #2: Find v_x .

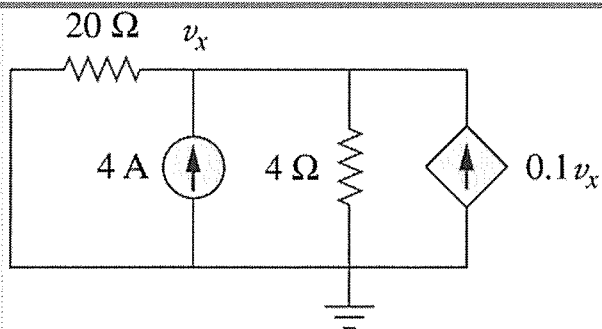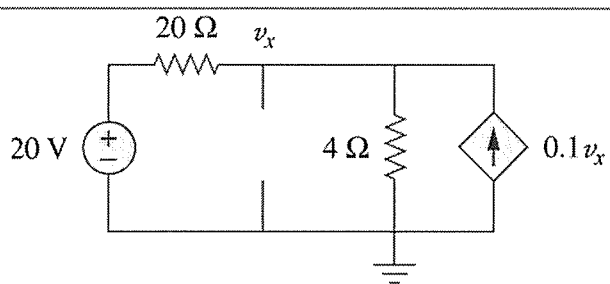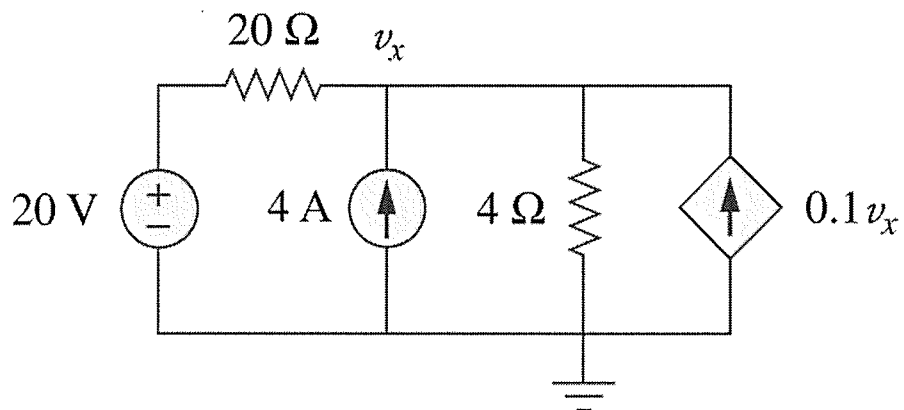

Total