
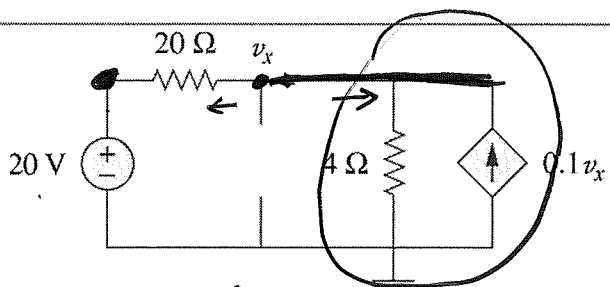


Example #2: Find v_x .

VCCS

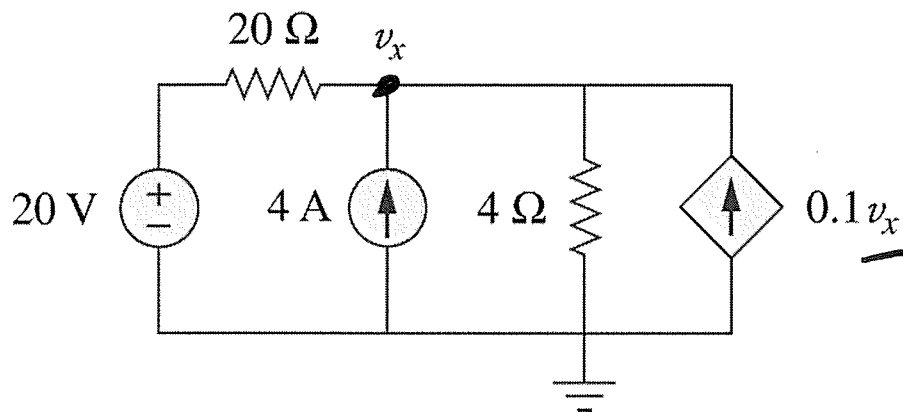


$$4V_x = 20$$

$$\Rightarrow V_x^V = 5V$$

$$\frac{V_x - 20}{20} + \frac{V_x}{4} - 0.1V_x = 0$$

$$V_x - 20 + 5V_x - 2V_x = 0$$

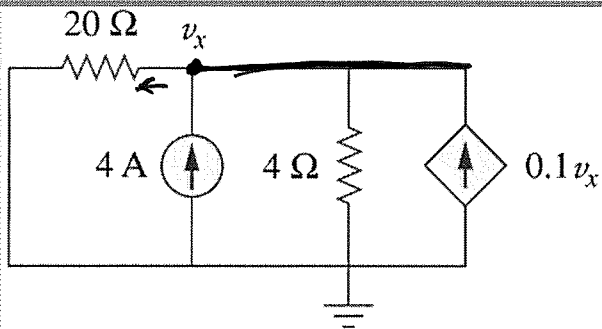

$$V_x^A = 20V$$

$$\frac{V_x}{20} + \frac{V_x}{4} = 4 + 0.1V_x$$



$$V_x + 5V_x = 80 + 2V_x$$

Total

$$V_x = V_x^A + V_x^V = 20V + 5V = \underline{25V}$$

L#14: Source transformation

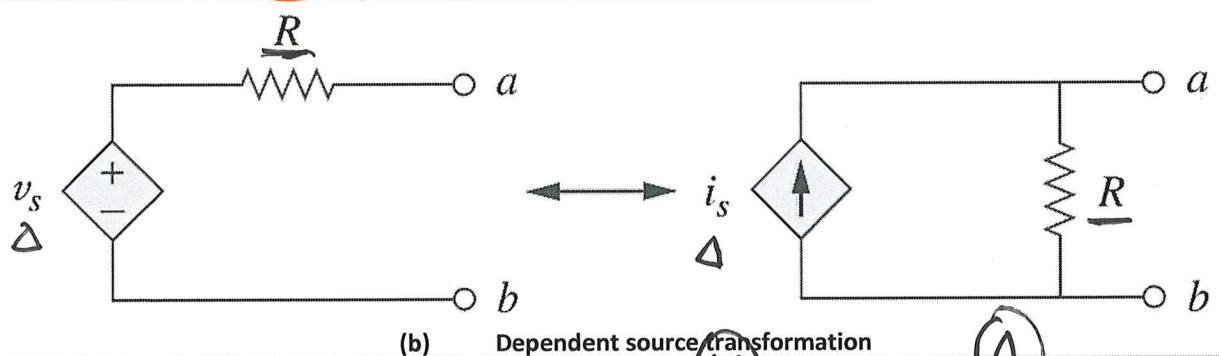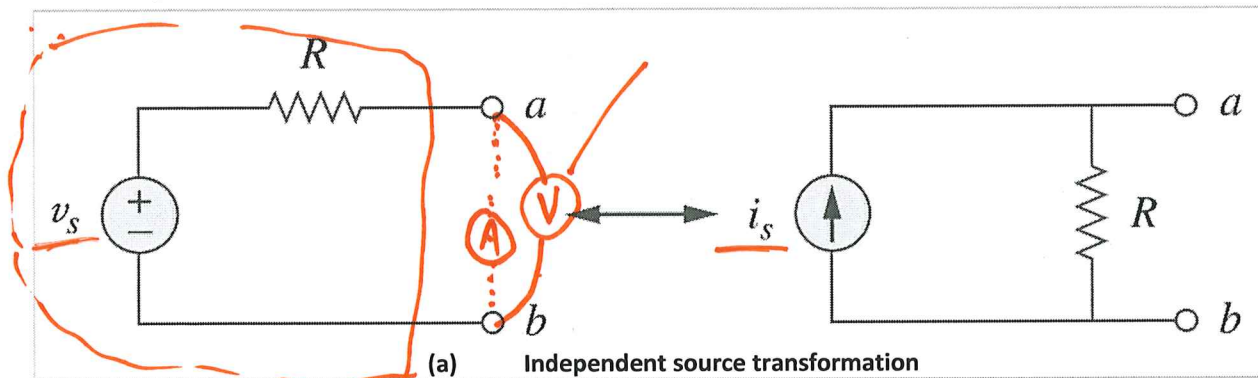Equivalent circuit: a new circuit whose V-I characteristics are identical with the original circuit.





Value:

- ① change configuration, $S \rightarrow P$
- ② R : value not change
- ③ $\text{V} \Rightarrow \text{A}$: $I_s = \frac{V_s}{R}$; $\text{A} \Rightarrow \text{V}$: $V_s = I_s R$






Direction:

Arrow of A always points to positive end of V


Applicability:

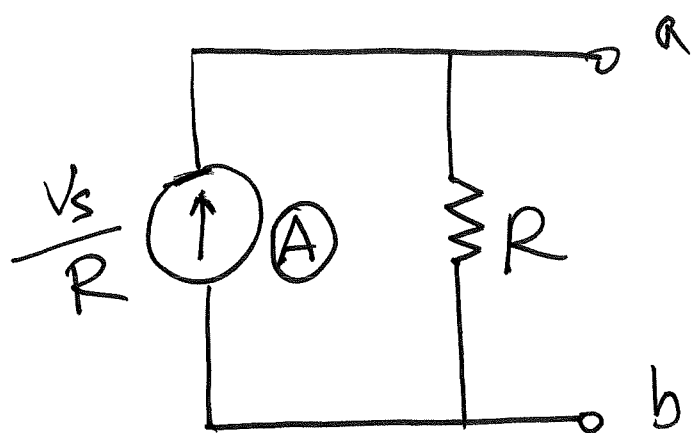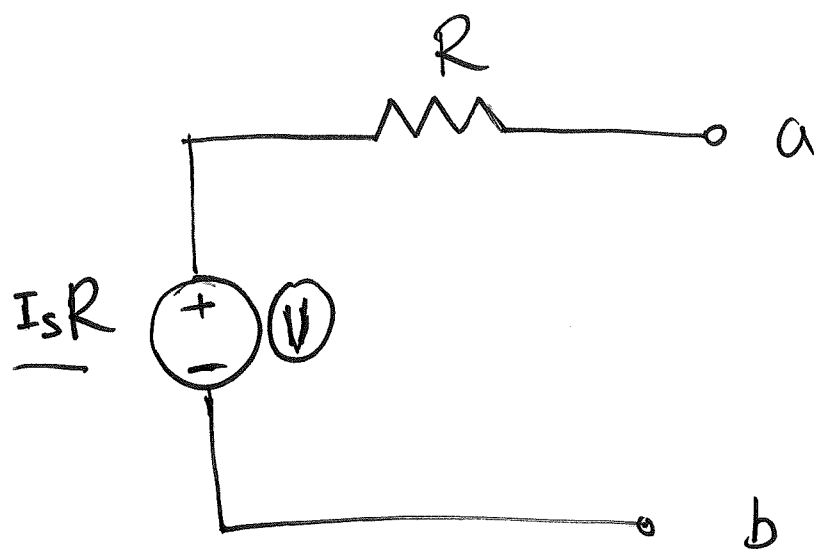

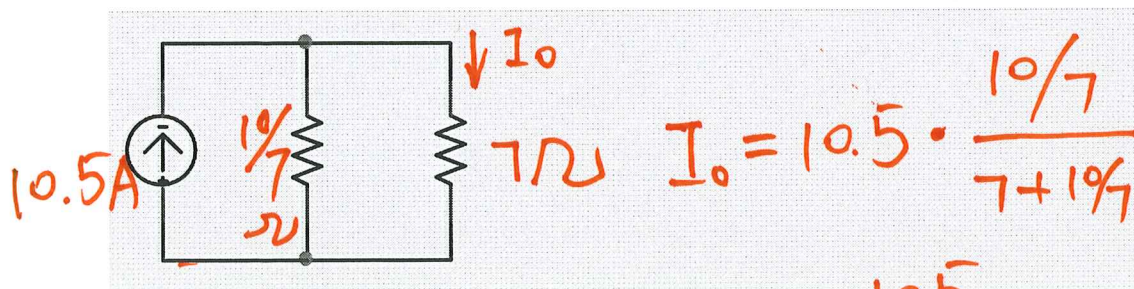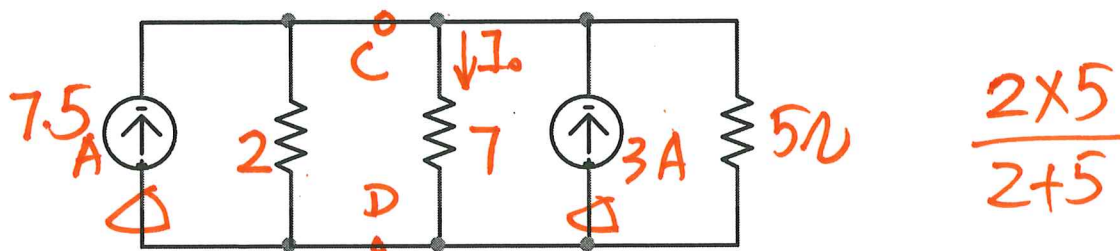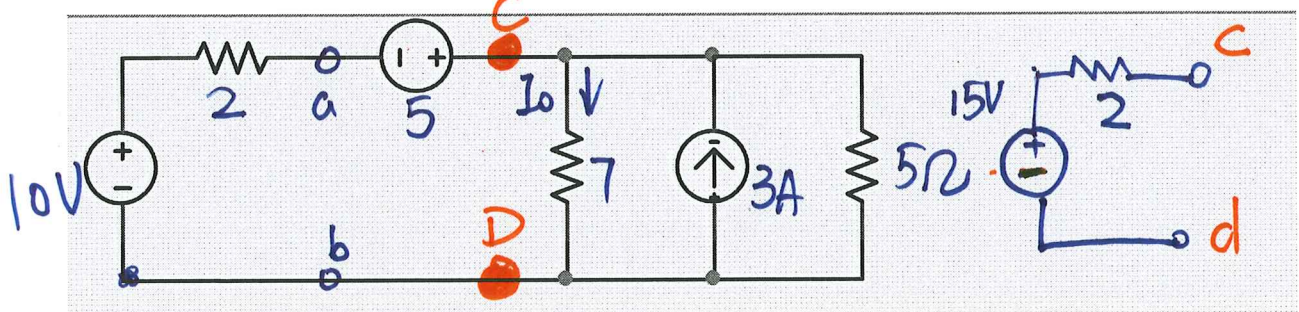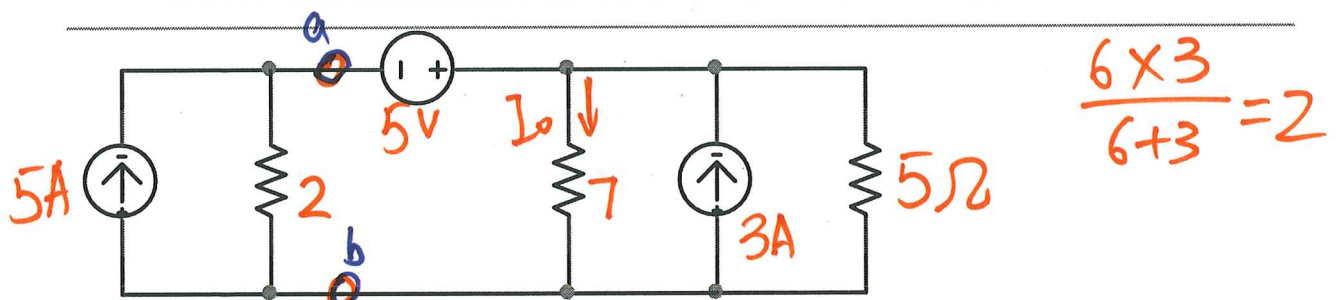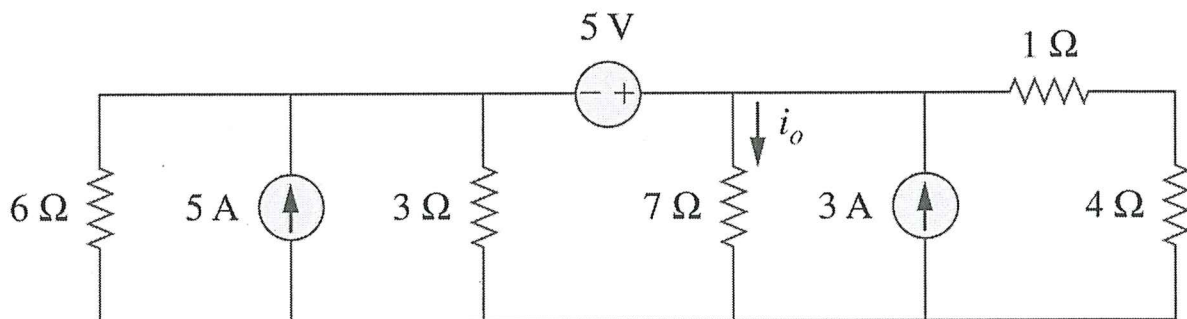Example #1: Use source transformation and determine i_o .



$$= \frac{105}{59} \text{ A}$$

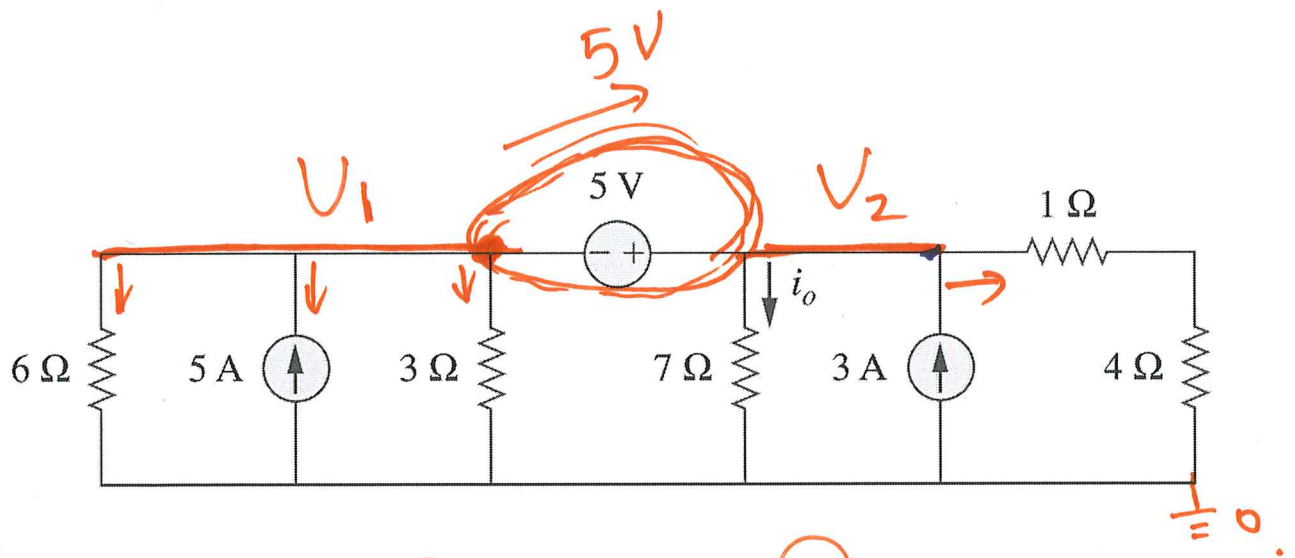

$$V_1 + 5 = V_2 \rightarrow \textcircled{1}$$

$$\frac{V_1}{6} - 5 + \frac{V_1}{3} + \frac{V_2}{7} - 3 + \frac{V_2}{5} = 0$$

$$\frac{1}{2}V_1 + \frac{V_2}{7} + \frac{V_2}{5} = 8 \quad \times 70 \rightarrow$$

$$35V_1 + 24V_2 = 8 \times 70 = 560$$

$$V_1 = V_2 - 5$$



$$35(V_2 - 5) + 24V_2 = 560$$

$$59V_2 = 560 + 175$$

$$\boxed{V_2 = \frac{560 + 175}{59}}$$

$$I_o = \frac{V_2}{7} = \frac{80 + 25}{59} = \frac{105}{59}$$

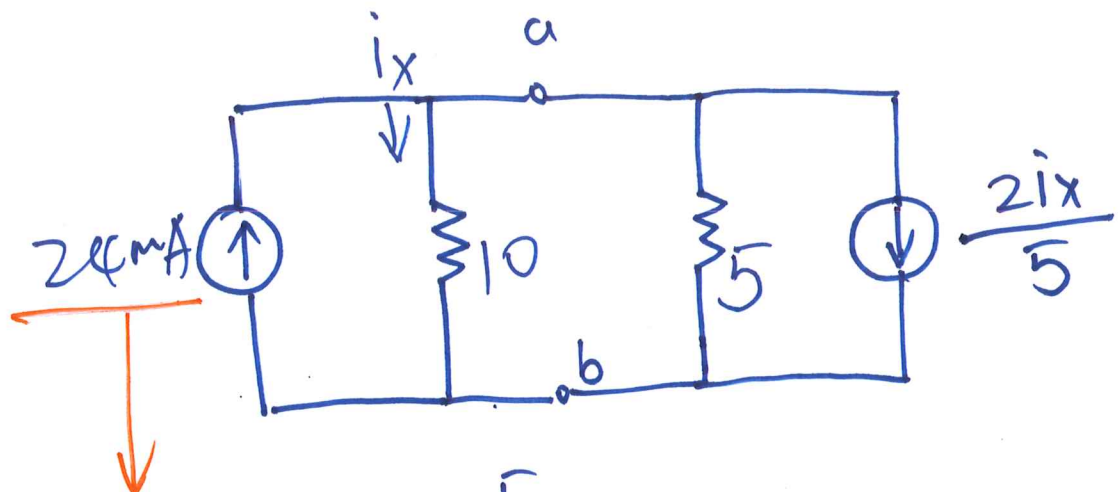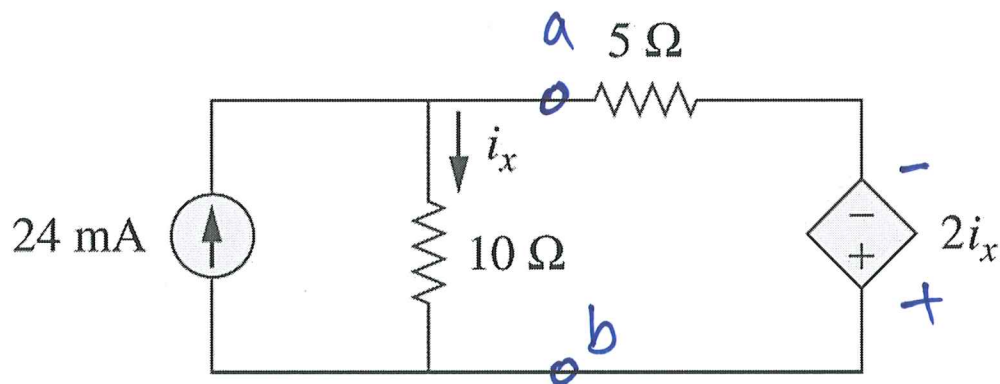Example #2: Use source transformation and determine i_x .





$$\left(24 - \frac{2i_x}{5}\right) \cdot \frac{5}{10+5} = i_x$$

$$24 \text{ mA} - 0.4i_x = 3i_x$$

$$\Rightarrow \underline{3.4i_x = 24 \text{ mA}} \rightarrow$$

Do NOT transform the part of the circuit with the unknown variable!

Example #3: Determine V_x .

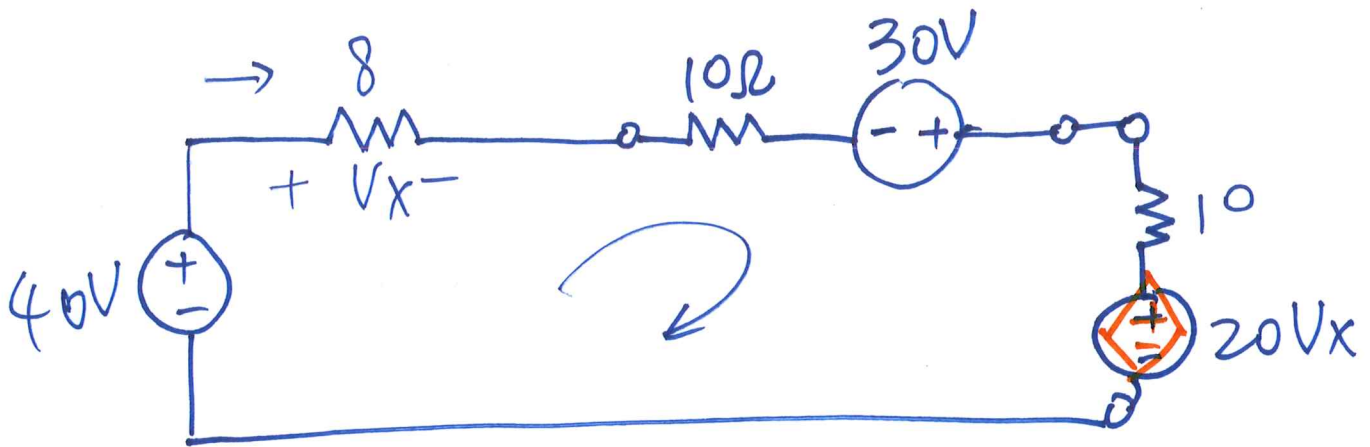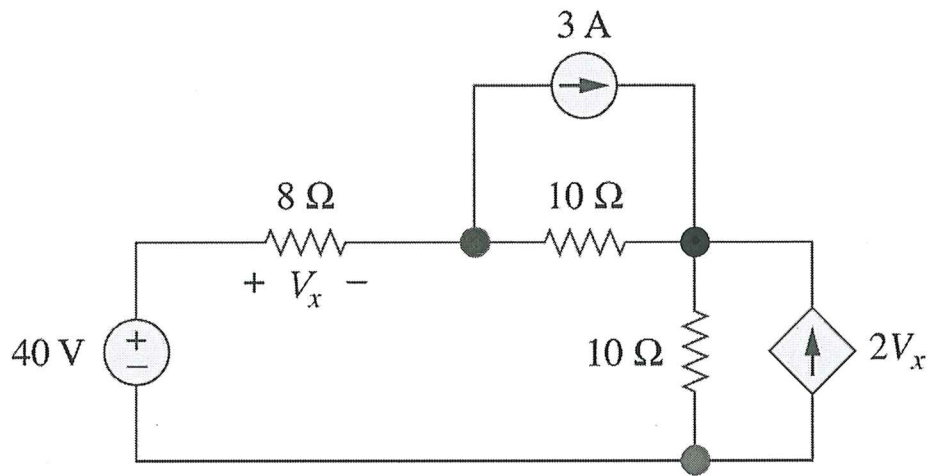

$$(40 + 30 - 20V_x) \cdot \frac{8}{8 + 10 + 10} = V_x$$