
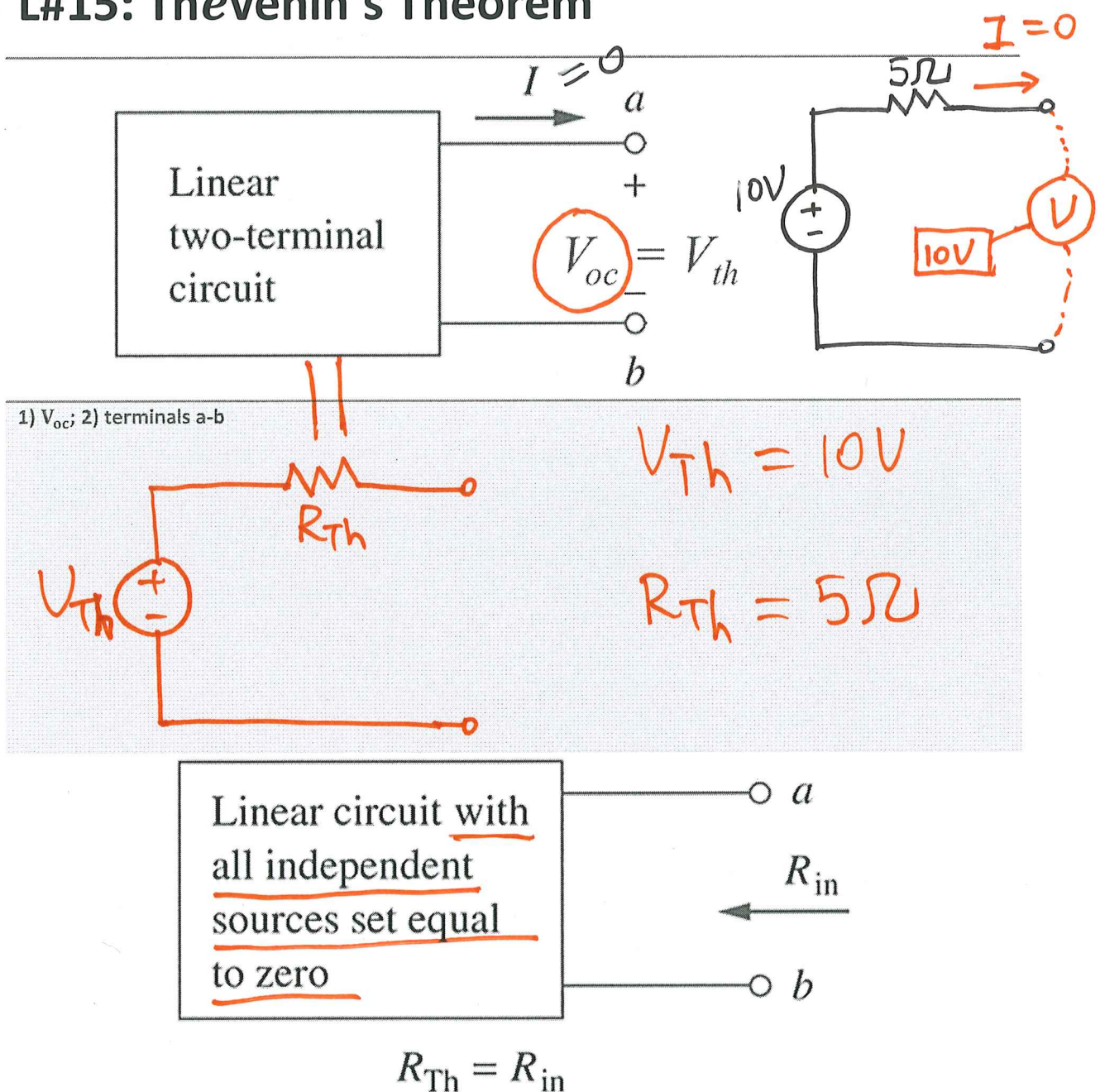


L#15: Thévenin's Theorem

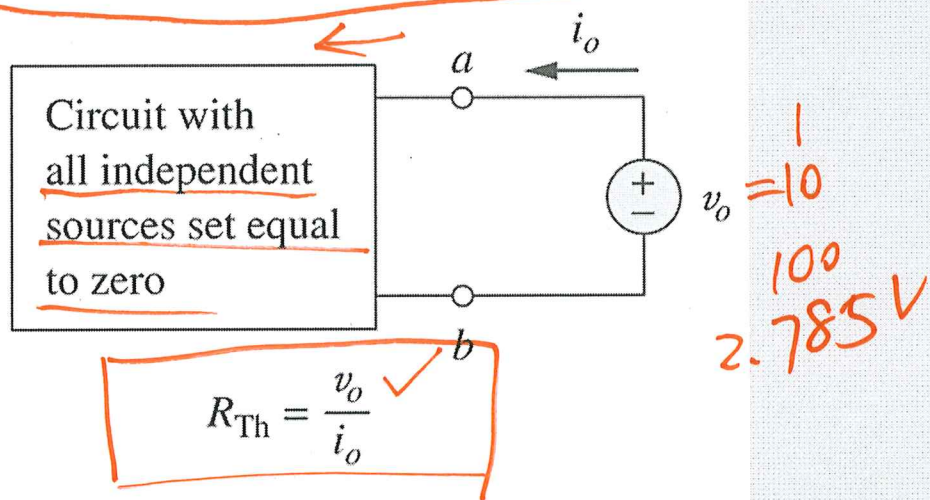


Method #1: Zeroing of Sources:
If the circuit contains no dependent sources.

Method #2: Application of test sources, if the circuit does contain dependent sources.




(a)

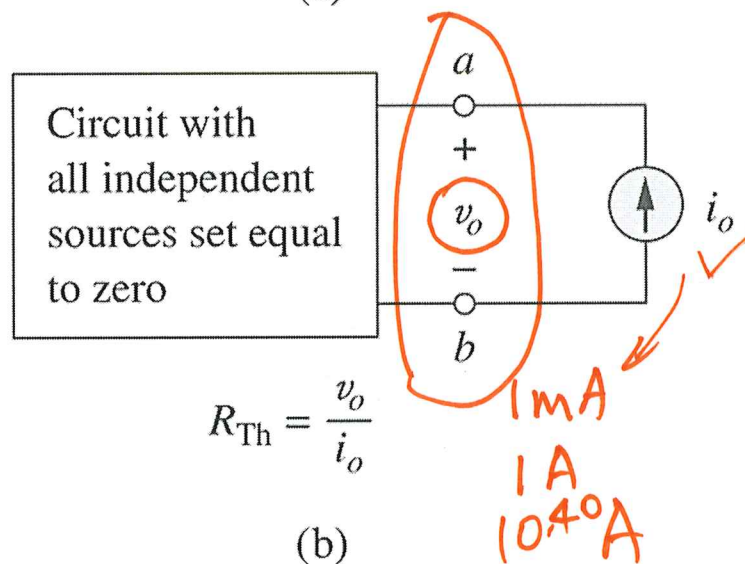


(b)

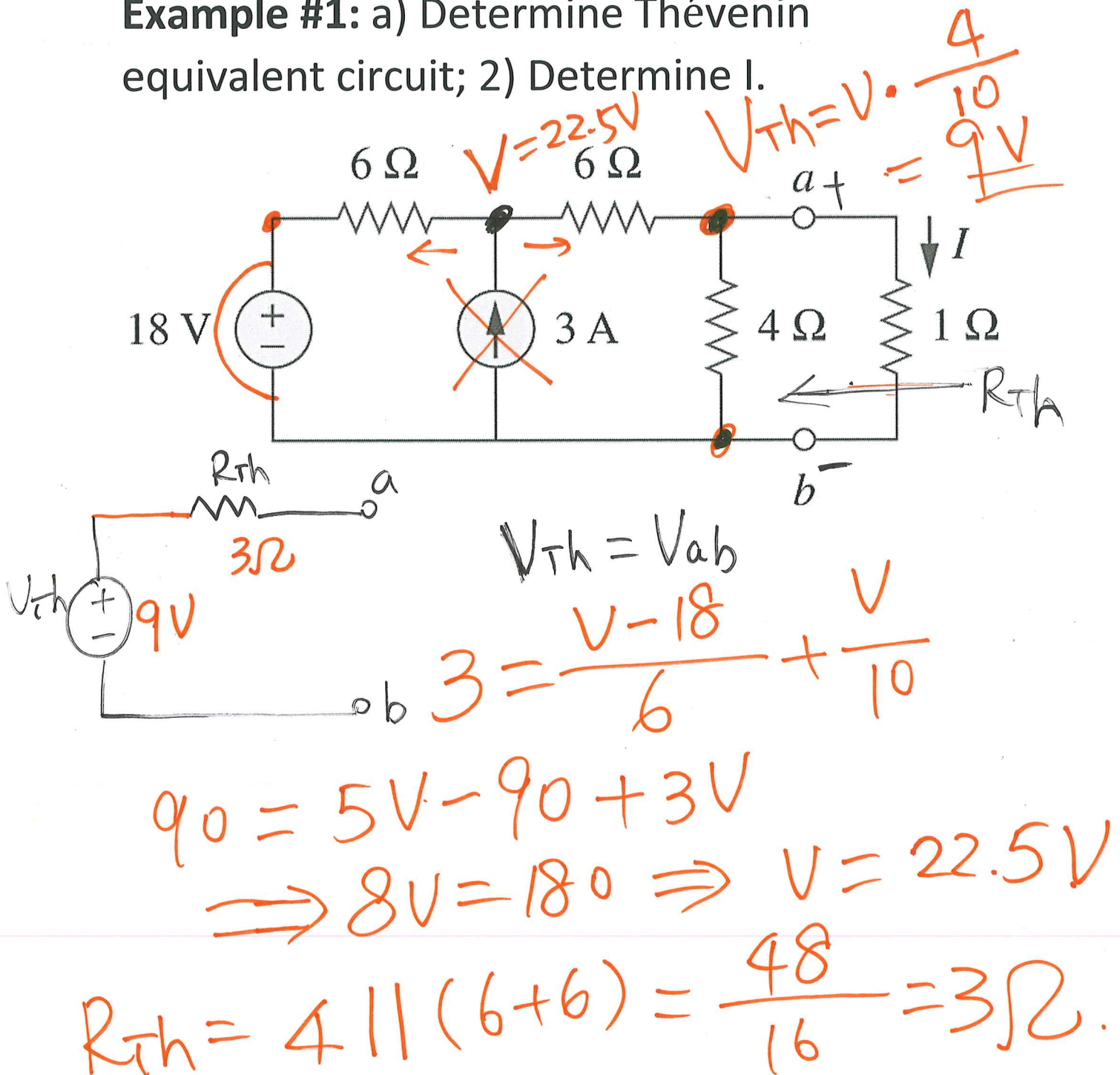Example #1: a) Determine Thévenin equivalent circuit; 2) Determine I .



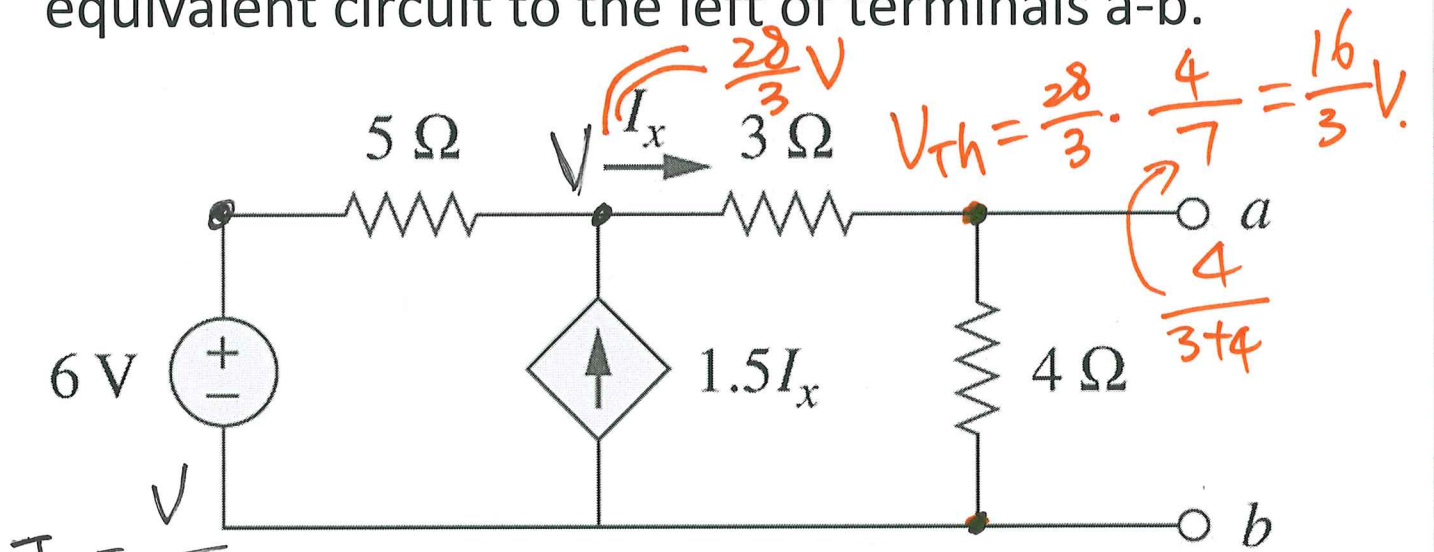Example #2: Determine the Thévenin equivalent circuit to the left of terminals a-b.



Use 3 approaches for R_{th}


$$V_{Th} = V_{ab}, \quad \frac{V-6}{5} + \frac{V}{7} = 1.5 I_x = 1.5 \frac{V}{7}$$

$$\frac{V-6}{5} = -\frac{V}{14} \Rightarrow 14V - 84 = -5V$$

$$\Rightarrow 9V = 84$$

$$V = \frac{84}{9} = \boxed{\frac{28}{3}} = 9.\bar{3}V$$

$$V_{Th} = \frac{16}{3} V.$$

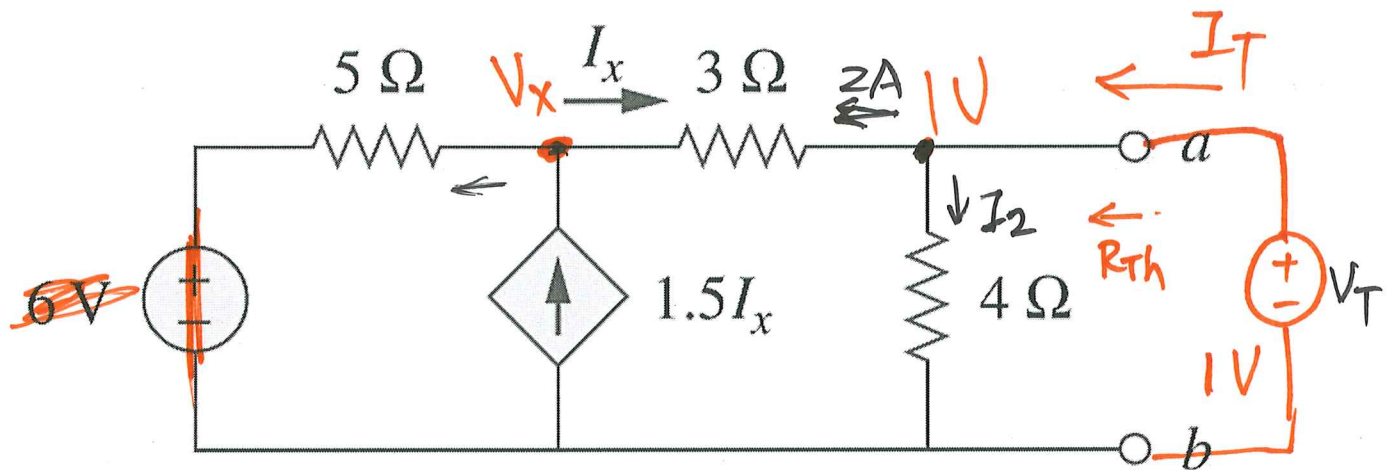

$$1.5 I_x = \frac{V_x}{5} + \left(\frac{V_x - 1}{3} \right), \quad I_x = \frac{V_x - 1}{3}$$

$$0.5 \frac{V_x - 1}{3} = \frac{V_x}{5}$$


$$6 V_x = 5 V_x - 5$$

$$V_x = -5 V.$$

$$I_x = \frac{-5 - 1}{3} = -2 A, \quad I_2 = \frac{1}{4} = 0.25 A$$

$$I_T = 2 A + 0.25 A = 2.25 A = \frac{9}{4} A.$$
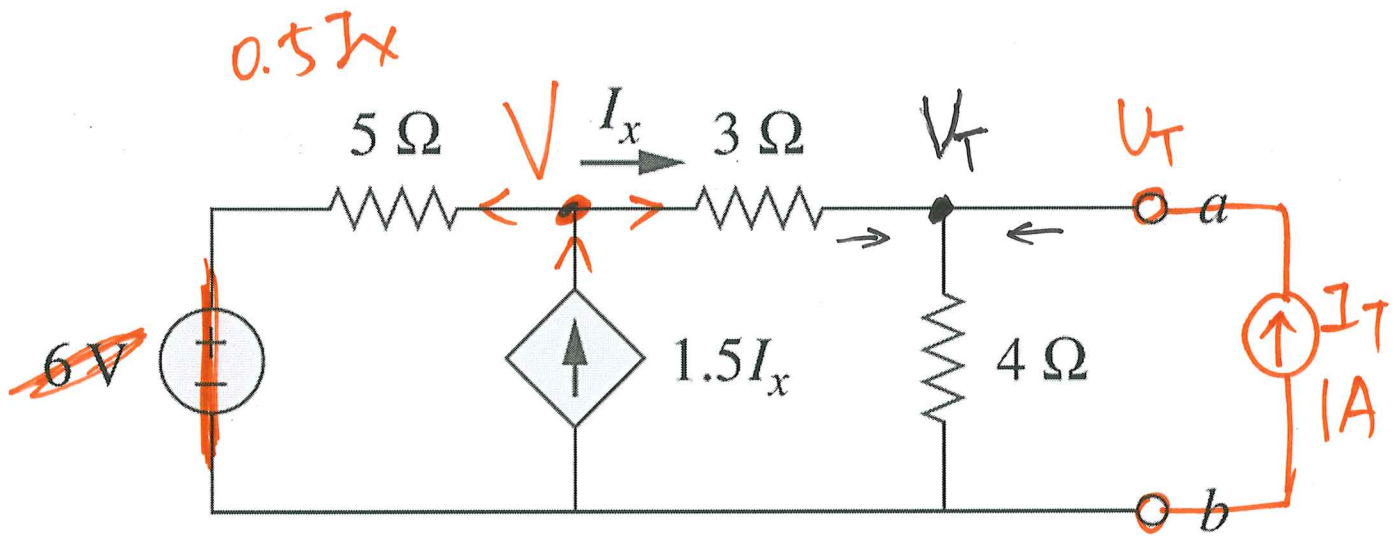
$$R_{Th} = \frac{V_T}{I_T} = \frac{1 V}{9/4 A} = \frac{4}{9} \Omega.$$



Add current source

$$0.5I_x = \frac{V}{5} = 0.5 \cdot \frac{V - V_T}{3}$$

$$\frac{V}{5} = \frac{V - V_T}{6}$$

$$\textcircled{1} \Rightarrow 6V = 5V - 5V_T$$

$$\Rightarrow V = -5V_T$$

$$\frac{V - V_T}{3} + 1 = \frac{V_T}{4}$$

$\textcircled{2}$


$$\frac{-5V_T - V_T}{3} + 1 = \frac{V_T}{4}$$

$$1 = \frac{V_T}{4} + 2V_T = \frac{9}{4}V_T$$


$$\Rightarrow V_T = \frac{4}{9}V$$

$$R_{Th} = \frac{V_T}{I_T} = \frac{4/9V}{1A} = \frac{4}{9}\Omega$$

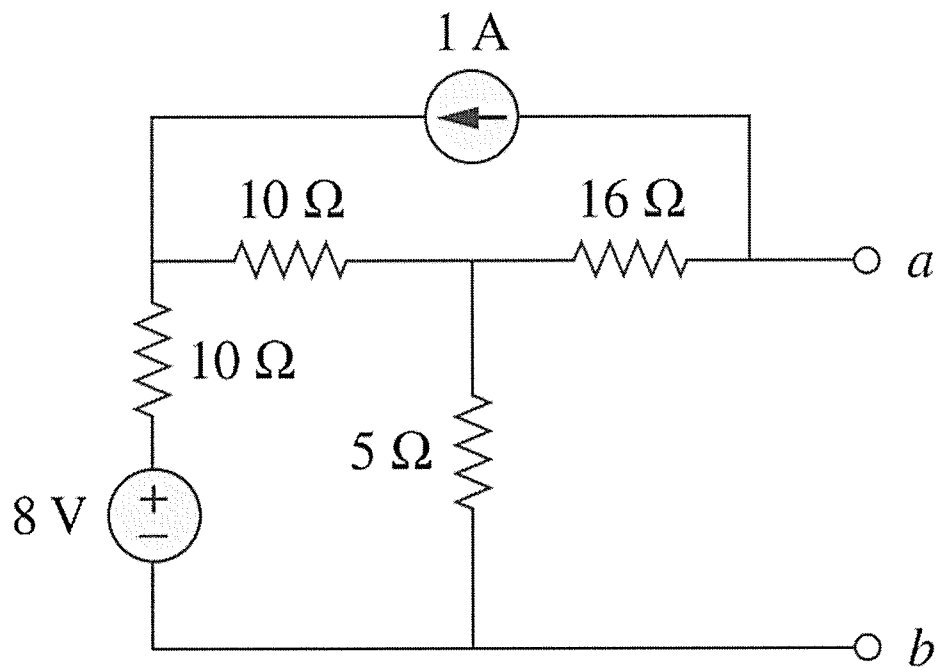
Example #3: Determine the Thévenin equivalent circuit.



L#16: Norton's Theorem

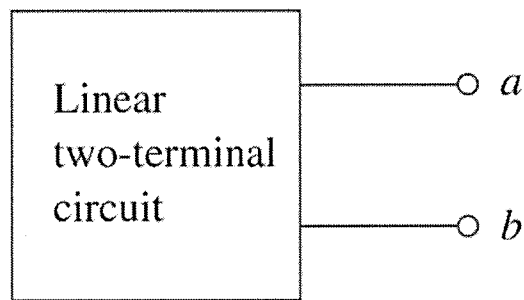

(a)



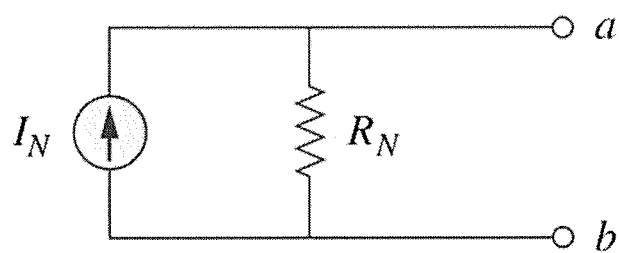


(b)

I_N : Norton equivalent current


R_N : Norton equivalent Resistance

Norton's Theorem and Thévenin's Theorem

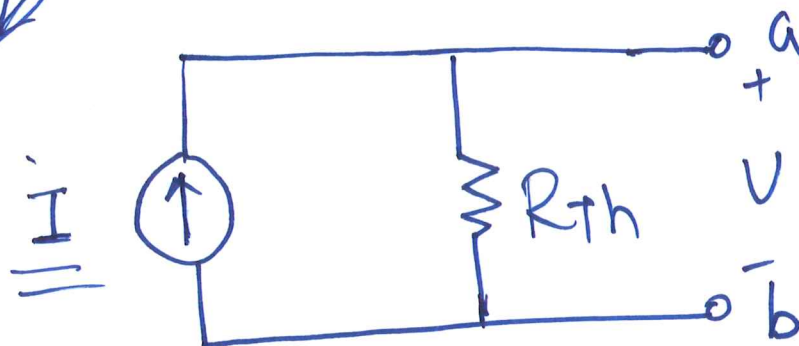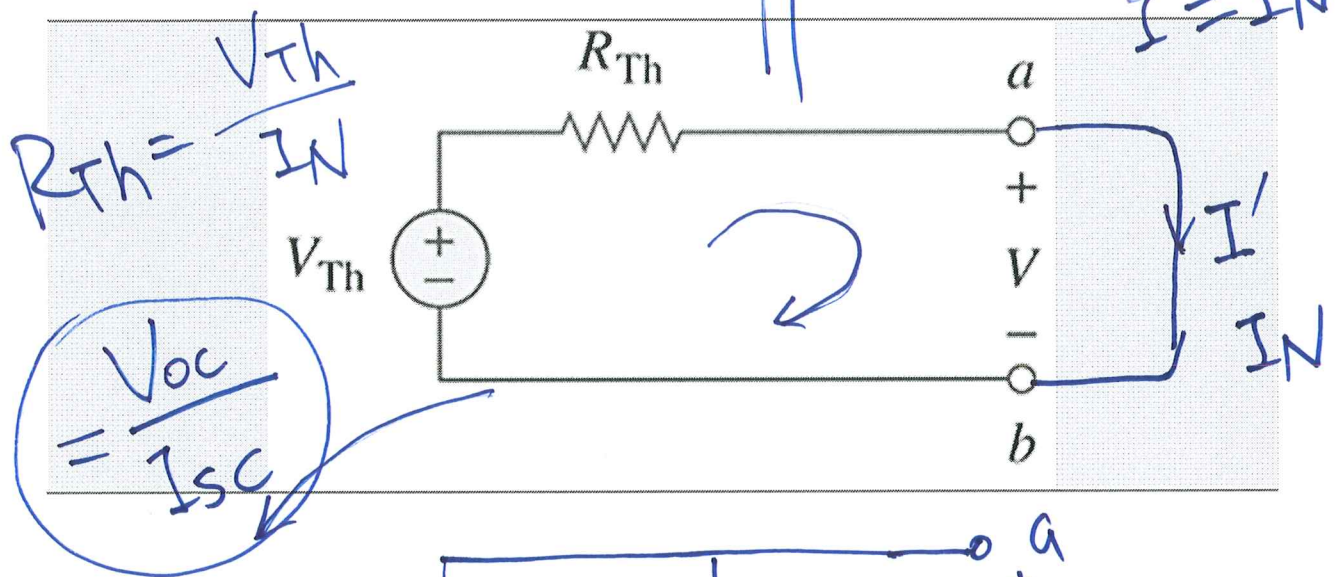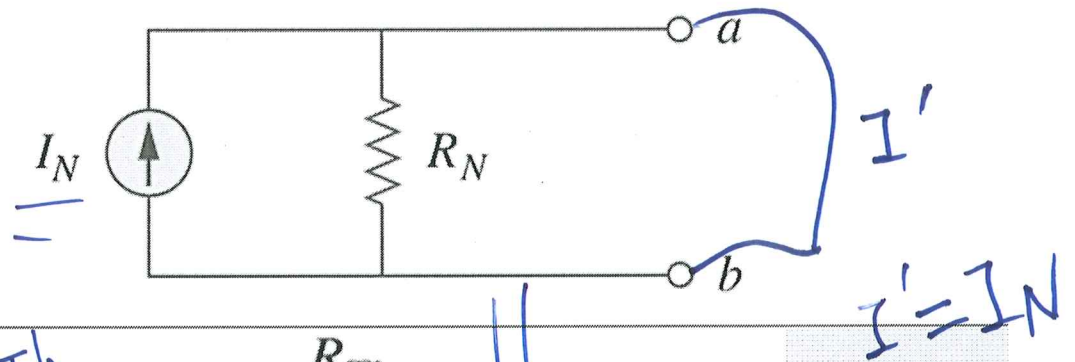

$$I = \frac{V_{Th}}{R_{Th}}, \quad I = I_N, \quad R_{Th} = R_N$$

Determine I_N

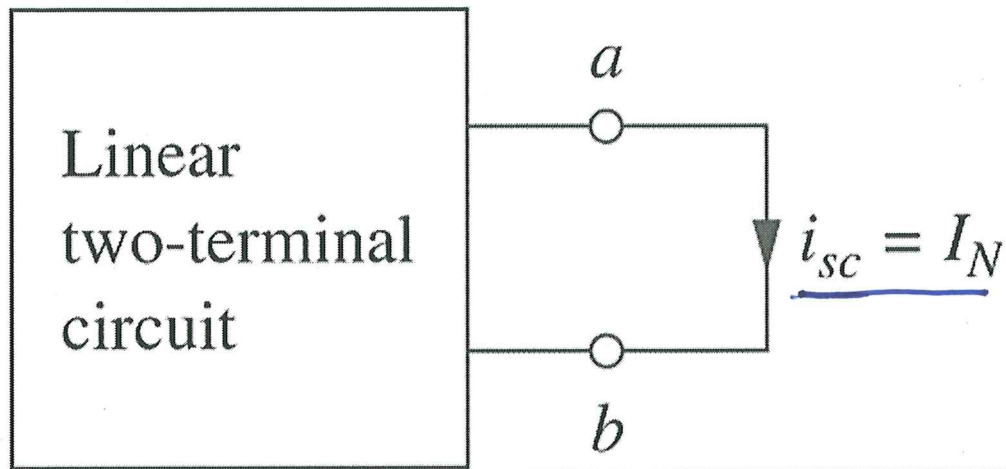

Norton equivalent current is the short circuit current

Determine R_N

Method #1:

Zero ind. sources.

Method #2:

by testing


(A)

(V)

Method #3:

- $R_N = R_{th} = V_{oc} / i_{sc} = V_{Th} / I_N$
- Works for circuits with or without dependent sources.

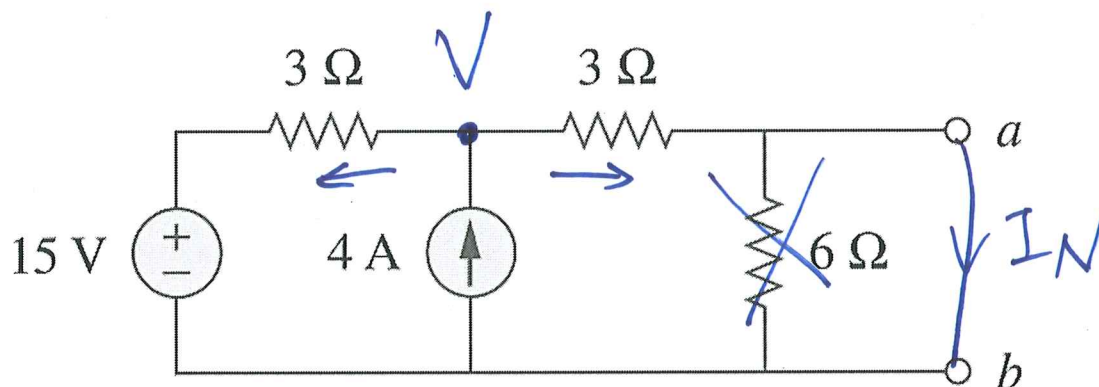Example #1: Determine the Norton equivalent circuit to the left of terminals a-b.





$$R_N = 6 \parallel (3+3) = 3\Omega$$


$$4A = \frac{V-15}{3} + \frac{V}{3}$$

$$12 = 2V - 15 \Rightarrow V = 13.5$$

$$I_N = \frac{V}{3} = 4.5A$$

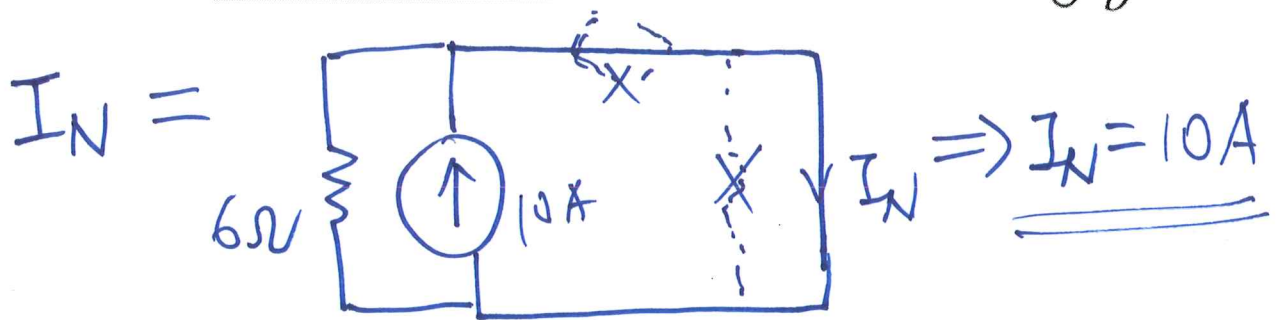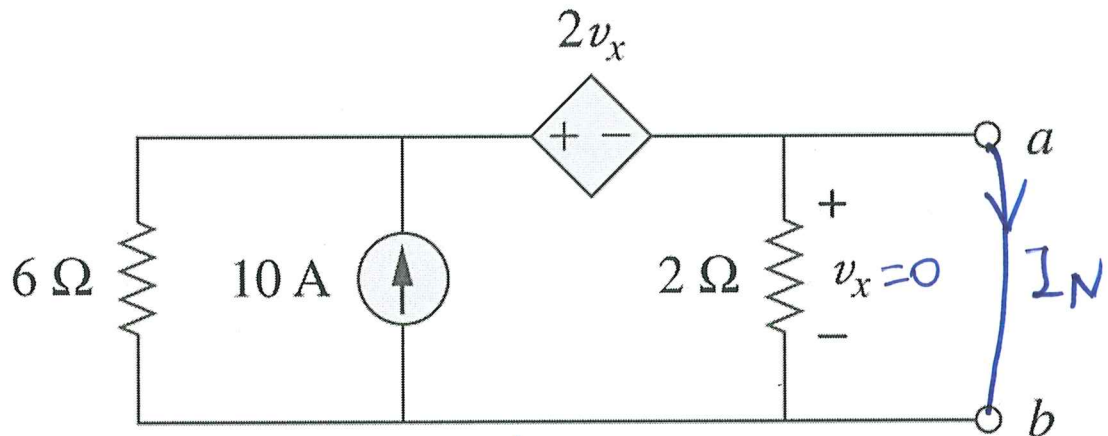Example #2: Determine the Norton equivalent circuit to the left of terminals a-b.




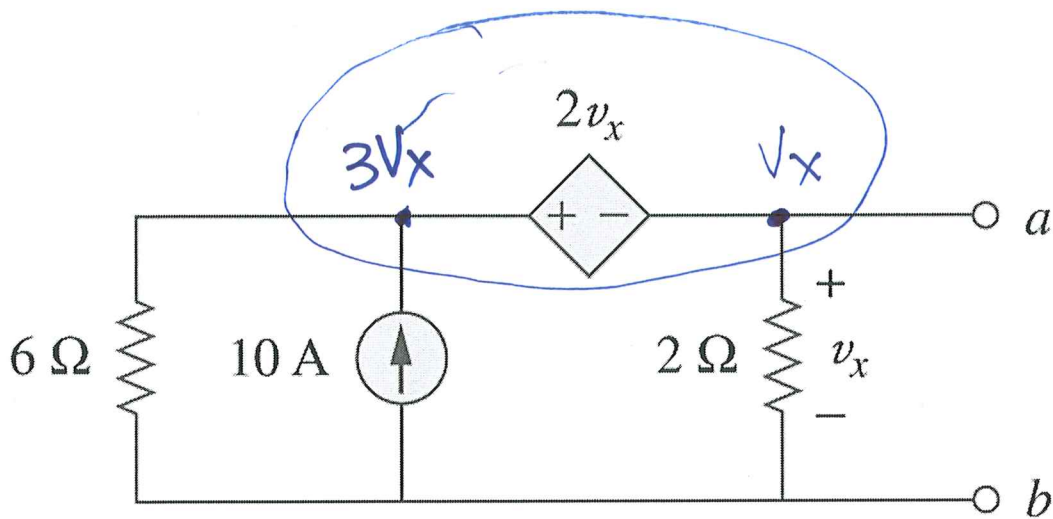



$$R_N = \frac{V_{oc}}{I_N}, \quad I_N = 10A.$$

$$10 = \frac{3V_x}{6} + \frac{V_x}{2} \Rightarrow V_x = 10V.$$
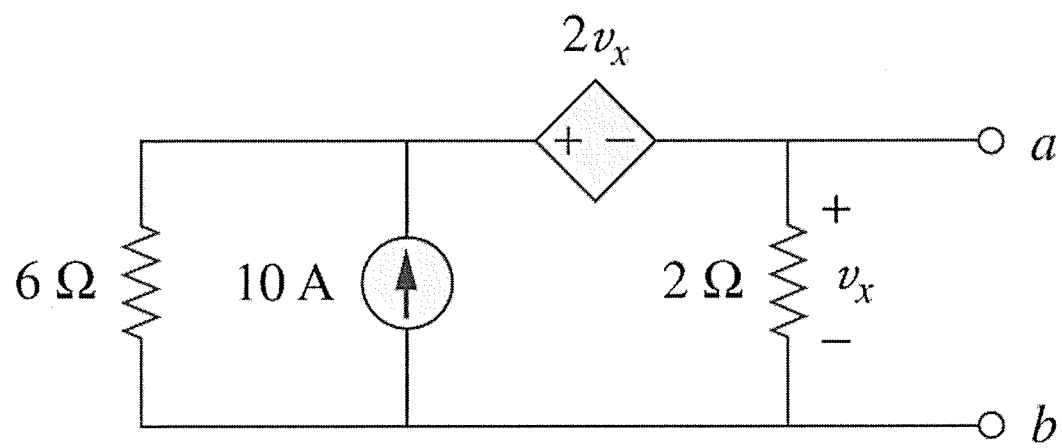
$$R_N = \frac{V_{oc}}{I_N} = \frac{V_x}{I_N} = \frac{10V}{10A} = 1\Omega.$$



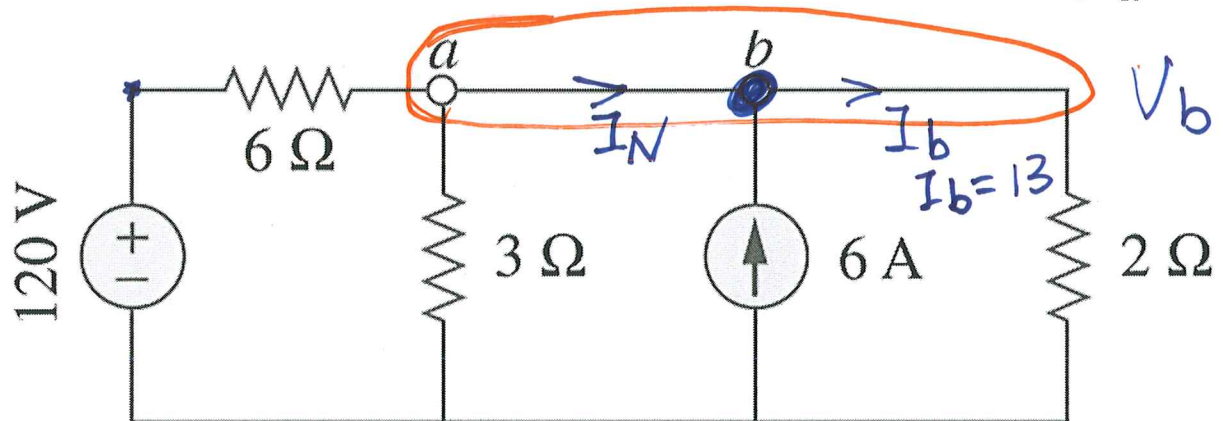
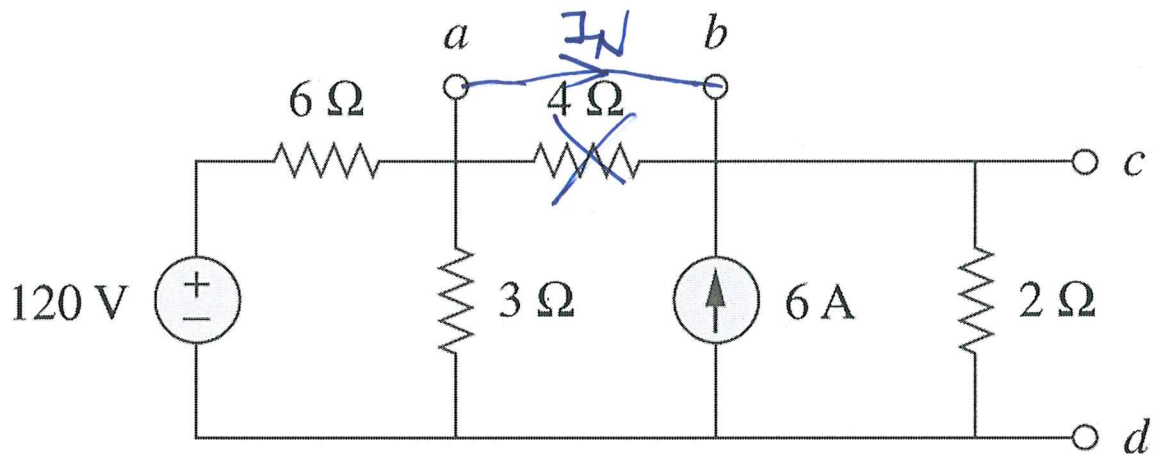
Example #3: Determine the Norton equivalent circuit. *from a-b*



$$\frac{V_b - 120}{6} + \frac{V_b}{3} + \frac{V_b}{2} = 6$$

$$\frac{V_b}{6} + \frac{V_b}{3} + \frac{V_b}{2} = 26 \Rightarrow V_b = 26$$

$$I_N = I_b - 6 = 7\text{ A}$$

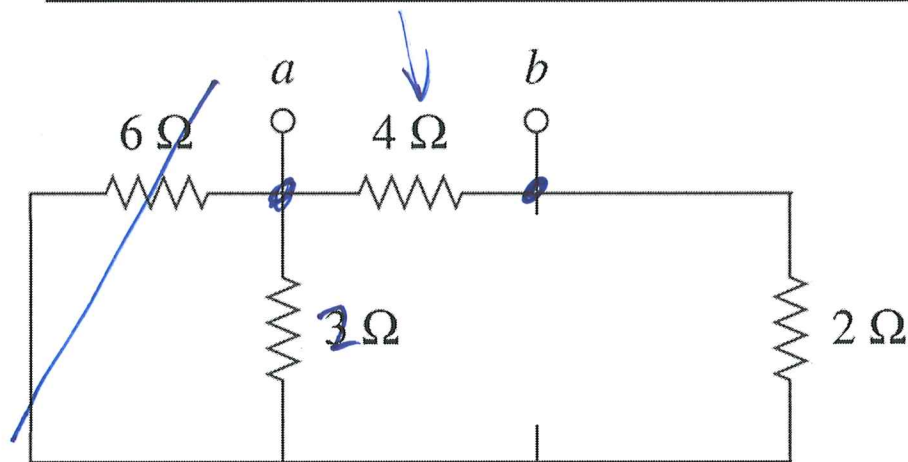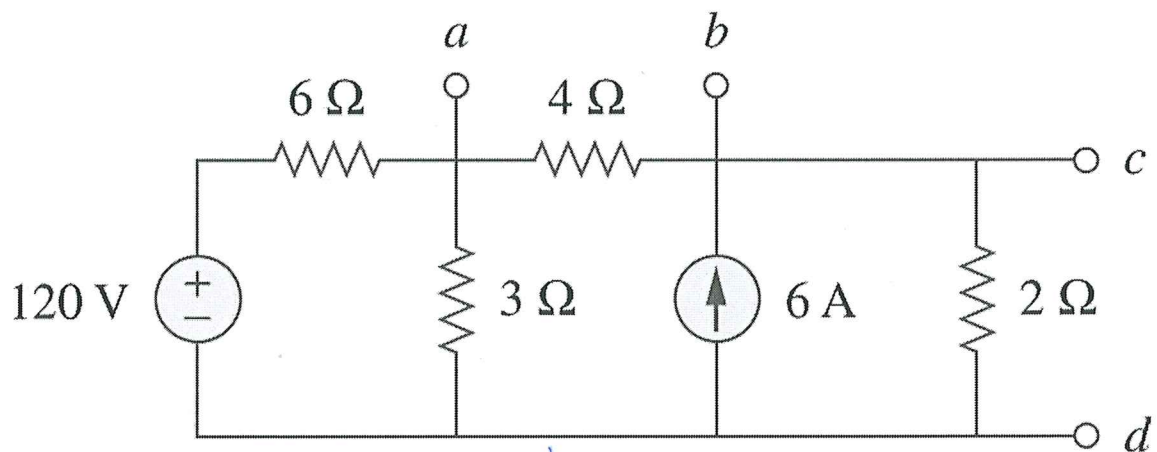

$$\frac{6 \times 3}{6 + 3} = 2$$

$$R_N = 4 \parallel (2 + 2) = 2\Omega.$$