

Methods of Analysis

Ch 3


L#1 3.2	Nodal analysis.
L#2 3.3	Nodal analysis with voltage sources.
L#3 3.4	Mesh analysis.
L#4 3.5	Mesh analysis with current sources.
L#5 3.6	Nodal and mesh analysis by inspection.
L#6 3.7	Nodal versus mesh analysis.
L#7 3.6	Transistors



Department of Electrical, Electronic and Computer Engineering

1

3.1 Motivation (1)

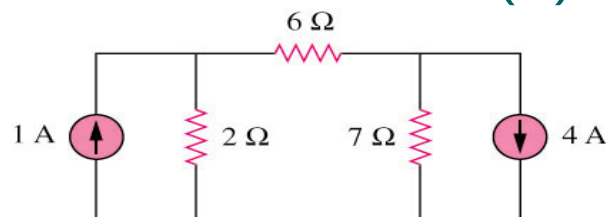

If you are given the following circuit, how can we determine

- 1) the voltage across each resistor,
- 2) current through each resistor.
- 3) power generated by each current source, etc.

What are the things which we need to know in order to determine the answers?



Department of Electrical, Electronic and Computer Engineering

2

3.1 Motivation (2)

The LAWS

Things we need to know in solving any resistive circuit with current and voltage sources only:

- Kirchhoff's Current Laws (KCL)
- Kirchhoff's Voltage Laws (KVL)
- Ohm's Law

How should we apply these laws to determine the answers?



Department of Electrical, Electronic and Computer Engineering

3

3.1 Motivation (3)

THESE TWO TECHNIQUES

KCL → Nodal Analysis
aka (Voltage Node Analysis)

KVL → Mesh (Current) Analysis

- Can be used in any linear circuit
- To obtain a set of simultaneous equations
- Equations solved using:
 - Substitution
 - Cramer's rule (Appendix A)




Department of Electrical, Electronic and Computer Engineering

4

3.2 Nodal Analysis

Why?

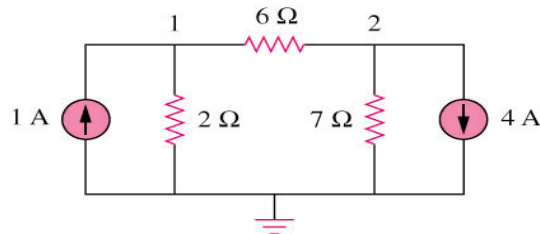

- It provides a general procedure for analyzing circuits using node voltages as opposed to element voltages as the circuit variables.
- Reduces the number of equations required to solve a circuit.

3.2 Nodal Analysis

STEPS


Steps to determine the node voltages:

1. Select a node as the reference node (*ground*).
2. Assign voltages $V_1, V_2, \dots, V_{n-1}$ to the remaining "critical" nodes.
 - "Critical node" = node with more than 2 branches attached.
 - The voltages are referenced with respect to the reference node. I.e. Measured between Node and Ground.
3. Apply KCL to each of the non-reference nodes. Use Ohm's law to express the branch currents in terms of node voltages.
4. Solve the resulting simultaneous equations to obtain the unknown node voltages.

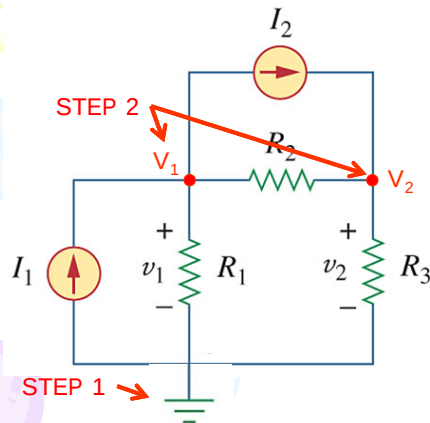3.2 Nodal Analysis: **EXAMPLE 1**

Calculate v_1 & v_2

Two unknown: v_1, v_2 ; requires two algebraic expression to calculate
Using Nodal voltage analysis we will obtain these two algebraic expressions



STEP 1:

Select a Reference Node
WHERE??

- Negative terminal of V-source
- Entry terminal of I-source
- Node with many branches
- Bottom node (many cases)



STEP 2:

Name critical nodes: $V_1, V_2, \dots, V_n$




UNIVERSITEIT VAN PRETORIA
UNIVERSITY OF PRETORIA
YUNIBESITHI YA PRETORIA

Department of Electrical, Electronic and Computer Engineering

7

3.2 Nodal Analysis


EXAMPLE 1

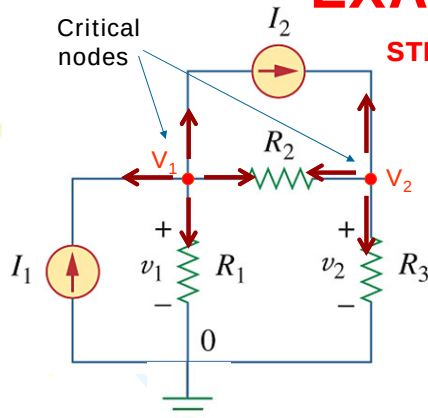

STEP 3: Apply KCL to each node

- Assign a current to each branch at each critical node.
- All currents to point **OUT** of the node.
- Remember: Current flows from **HIGH** to **LOW** voltage $\therefore$
- All branch currents to be written ito
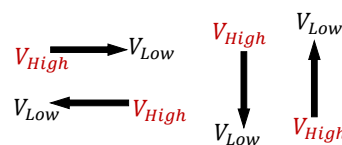
$$\text{Ohm's law: } i = \frac{V_{\text{High}} - V_{\text{Low}}}{R_{\text{Branch}}}$$



- Number of critical nodes = number of equations.
- Number of branches = number of terms.



UNIVERSITEIT VAN PRETORIA
UNIVERSITY OF PRETORIA
YUNIBESITHI YA PRETORIA

Department of Electrical, Electronic and Computer Engineering

8

EXAMPLE 1

STEP 3: Apply KCL to each node

$i = \frac{V_{High} - V_{Low}}{R_{Branch}}$

KCL@ Node 1
(4 Branches):
 $i_w + i_x + i_y + i_z$
 Replace the branch current using Ohm's law
 $i_w = -I_1$;
 $i_x = I_2$;
 $i_y = \frac{V_1 - V_2}{R_2}$; $i_z = \frac{V_1}{R_1}$
 $(-I_1) + (I_2) + \frac{V_1 - V_2}{R_2} + \frac{V_1 - 0}{R_1} = 0$

$i_{branch} = \frac{V_{n_from} - V_{n_to}}{R_{branch}}$

KCL@ Node 2
(3 Branches):
 $i_a + i_b + i_c = 0$
 Replace the branch current using Ohm's law
 $(-I_2) + \frac{V_2 - 0}{R_3} + \frac{V_2 - V_1}{R_2} = 0$

Negative because outgoing branch current is opposite to the source's current

Department of Electrical, Electronic and Computer Engineering

9

3.2 Nodal Analysis

EXAMPLE 2

Step 2
Critical nodes

Step 1
Ground

$4V_1 + (-1)V_2 = 6 \quad (1)$
 $(-7)V_1 + 13V_2 = -168 \quad (2)$

$a_1 = 4; \quad b_1 = -1$
 $a_2 = -7; \quad b_2 = 13$

Step 3:
 • apply KCL @ each node
 • Use Ohm's law and replace branch current


Node 1: $i_{1A} + i_{2\Omega} + i_{6\Omega} = 0$
 $1 + \frac{V_1 - 0}{2} + \frac{V_1 - V_2}{6} = 0$
 $-6 + 3V_1 + V_1 - V_2 = 0$
 Write it to: $a_1V_1 + b_1V_2 = k_1$
 $4V_1 + (-1)V_2 = 6 \quad (1)$

Node 2: $i_{6\Omega} + i_{7\Omega} + i_{4A} = 0$
 $\frac{V_2 - V_1}{6} + \frac{V_2 - 0}{7} + 4 = 0$
 $7V_2 - 7V_1 + 6V_2 + 168 = 0$
 Write it to: $a_2V_1 + b_2V_2 = k_2$
 $(-7)V_1 + 13V_2 = -168 \quad (2)$

Department of Electrical, Electronic and Computer Engineering

10

Ex. 2 – Method 1: Elimination

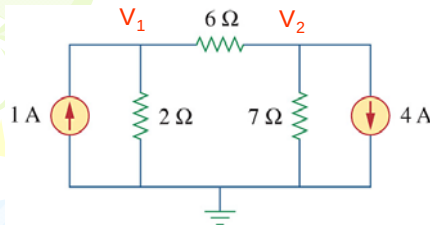

$$\begin{aligned} 4V_1 + (-1)V_2 &= 6 & (1) \\ (-7)V_1 + 13V_2 &= -168 & (2) \end{aligned}$$

From (1): $V_2 = 4V_1 - 6$ (3)

(3) in (2): $(-7)V_1 + 13(4V_1 - 6) = -168$
 $45V_1 - 78 = -168$
 $45V_1 = -90 \quad V_1 = -2 \text{ V}$

From (3): $V_2 = 4(-2) - 6$
 $V_2 = -14 \text{ V}$




UNIVERSITEIT VAN PRETORIA
UNIVERSITY OF PRETORIA
YUNIBESITHI YA PRETORIA

Department of Electrical, Electronic and Computer Engineering

11

Ex. 2 – Method 2: Cramer's Rule

See Appendix A

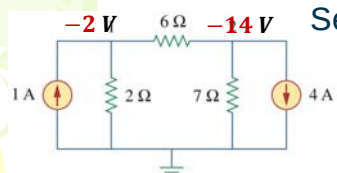

$$\begin{aligned} 4V_1 + (-1)V_2 &= 6 & (1) \\ (-7)V_1 + 13V_2 &= -168 & (2) \end{aligned}$$

$$\begin{bmatrix} 4 & -1 \\ -7 & 13 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 6 \\ -168 \end{bmatrix}$$

$$\Delta = \begin{vmatrix} 4 & -1 \\ -7 & 13 \end{vmatrix} = (4 \times 13) - (-1 \times -7) = 52 - 7 = 45$$

$$V_1 = \frac{\Delta_1}{\Delta} \quad \Delta_1 = \begin{vmatrix} 6 & 1 \\ -168 & 13 \end{vmatrix} = (6 \times 13) - (-1 \times -168) = 78 - 168 = -90$$

$$V_1 = \frac{-90}{45} = -2 \text{ V}$$

$$V_2 = \frac{\Delta_2}{\Delta} \quad \Delta_2 = \begin{vmatrix} 4 & 6 \\ -7 & -168 \end{vmatrix} = (4 \times -168) - (-7 \times 6) = -672 + 42 = -630$$

$$V_2 = \frac{-630}{45} = -14 \text{ V}$$



UNIVERSITEIT VAN PRETORIA
UNIVERSITY OF PRETORIA
YUNIBESITHI YA PRETORIA

Department of Electrical, Electronic and Computer Engineering

12

PP 3-2: Determine the node voltages.

Three unknown: V_1 , V_2 & V_3 ; requires three algebraic expression

Apply KCL @ each node

Using Ohm's law replace the branch currents with node voltages

KCL@ node 1:

$$i_{10A} + i_{3\Omega} + i_{2\Omega} = 0;$$

Ohm's law: replace current with voltages


$$\begin{aligned} \times 6 \left\{ -10 + \frac{V_1 - V_2}{3} + \frac{V_1 - V_3}{2} \right. &= 0 \\ -60 + 2V_1 - 2V_2 + 3V_1 - 3V_3 &= 0 \\ 5V_1 - 2V_2 - 3V_3 &= 60 \quad (1) \end{aligned}$$

KCL@ 2:

$$i_{3\Omega} + i_{4\Omega} + i_d = 0$$

Ohm's law: replace current with voltages
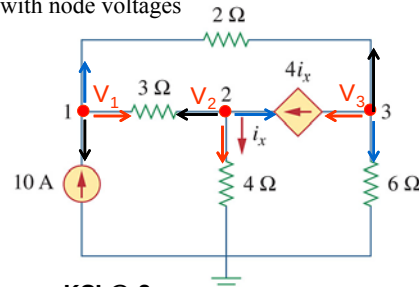
$$\begin{aligned} \times 12 \left\{ \frac{V_2 - V_1}{3} + \frac{V_2 - 0}{4} - 4i_x \right. &= 0 \\ 4V_2 - 4V_1 + 3V_2 - 48 \frac{V_2}{4} &= 0 \\ -4V_1 - 5V_2 + 0V_3 &= 0 \quad (2) \end{aligned}$$



KCL@ 3:

$$i_d + i_{2\Omega} + i_{6\Omega} = 0$$

Ohm's law: replace current with voltages

$$\begin{aligned} \times 6 \left\{ 4i_x + \frac{V_3 - V_1}{2} + \frac{V_3 - 0}{6} \right. &= 0 \\ 24 \frac{V_2}{4} + 3V_3 - 3V_1 + V_3 &= 0 \\ -3V_1 + 6V_2 + 4V_3 &= 0 \quad (3) \end{aligned}$$




UNIVERSITEIT VAN PRETORIA
UNIVERSITY OF PRETORIA
YUNIBESITHI YA PRETORIA

Department of Electrical, Electronic and Computer Engineering

13

PP 3-2: Determine the node voltages.

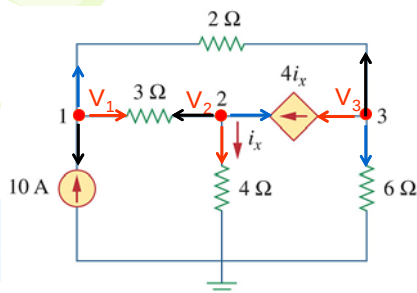

$$5V_1 - 2V_2 - 3V_3 = 60 \quad (1)$$

$$-4V_1 - 5V_2 + 0V_3 = 0 \quad (2)$$

$$-3V_1 + 6V_2 + 4V_3 = 0 \quad (3)$$

$$\begin{bmatrix} 5 & -2 & -3 \\ -4 & -5 & 0 \\ -3 & 6 & 4 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} 60 \\ 0 \\ 0 \end{bmatrix}$$

$$V_1 = \frac{\Delta_1}{\Delta} \quad V_2 = \frac{\Delta_2}{\Delta} \quad V_3 = \frac{\Delta_3}{\Delta}$$



UNIVERSITEIT VAN PRETORIA
UNIVERSITY OF PRETORIA
YUNIBESITHI YA PRETORIA

Department of Electrical, Electronic and Computer Engineering

14

PP 3-2 ... Calculating Δ

$$\begin{bmatrix} 5 & -2 & -3 \\ -4 & -5 & 0 \\ -3 & 6 & 4 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} 60 \\ 0 \\ 0 \end{bmatrix}$$

$$\Delta = \begin{vmatrix} +5 & -2 & -3 \\ -4 & -5 & 0 \\ -3 & 6 & 4 \end{vmatrix}$$

$(-3 \cdot -5 \cdot -3) = -45$ $(5 \cdot -5 \cdot 4) = -100$
 $(0 \cdot 6 \cdot 5) = 0$ $(-4 \cdot 6 \cdot -3) = 72$
 $(4 \cdot -2 \cdot -4) = -32$ $(-3 \cdot -2 \cdot 0) = 0$

$$\begin{aligned} \Delta &= (-100 + 72 + 0) - (-45 + 0 + 32) \\ &= (-28) - (-13) \\ \Delta &= -15 \end{aligned}$$



UNIVERSITEIT VAN PRETORIA
UNIVERSITY OF PRETORIA
YUNIBESITHI YA PRETORIA

Department of Electrical, Electronic and Computer Engineering

15

PP 3-2 ... Calculating Δ_1

$$\Delta = -15 \quad \begin{bmatrix} 5 & -2 & -3 \\ -4 & -5 & 0 \\ -3 & 6 & 4 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} 60 \\ 0 \\ 0 \end{bmatrix}$$

$$\Delta_1 = \begin{vmatrix} 60 & -2 & -3 \\ 0 & -5 & 0 \\ 0 & 6 & 4 \end{vmatrix}$$

$(-3 \cdot -5 \cdot 0) = 0$ $(60 \cdot -5 \cdot 4) = -1200$
 $(0 \cdot 6 \cdot 0) = 0$ $(0 \cdot 6 \cdot -3) = 0$
 $(4 \cdot -2 \cdot 0) = 0$ $(0 \cdot -2 \cdot 0) = 0$

$$\begin{aligned} \Delta_1 &= (-1200 + 0 + 0) - (0 + 0 + 0) \\ \Delta_1 &= -1200 \end{aligned}$$

$$V_1 = \frac{\Delta_1}{\Delta} = \frac{-1200}{-15} = 80 \text{ V}$$



UNIVERSITEIT VAN PRETORIA
UNIVERSITY OF PRETORIA
YUNIBESITHI YA PRETORIA

Department of Electrical, Electronic and Computer Engineering

16

PP 3-2 ... Calculating Δ_2

$$\Delta = -15$$

$$\begin{bmatrix} 5 & -2 & -3 \\ -4 & -5 & 0 \\ -3 & 6 & 4 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} 60 \\ 0 \\ 0 \end{bmatrix}$$

$$\Delta_2 = \begin{vmatrix} 5 & 60 & -3 \\ -4 & 0 & 0 \\ -3 & 0 & 4 \end{vmatrix}$$

$(-3 \cdot 0 \cdot 0) = 0$
 $(0 \cdot 0 \cdot 5) = 0$
 $(4 \cdot 60 \cdot -4) = -960$

$+ (5 \cdot 0 \cdot 4) = 0$
 $+ (-4 \cdot 0 \cdot -3) = 0$
 $+ (-3 \cdot 60 \cdot 0) = 0$

$$\Delta_2 = (0 + 0 + 0) - (0 + 0 - 960)$$

$$\Delta_2 = -960$$

$$V_2 = \frac{\Delta_2}{\Delta} = \frac{-960}{-15} = 64 \text{ V}$$



Department of Electrical, Electronic and Computer Engineering

17

PP 3-2 ... Calculating Δ_3

$$\Delta = -15$$

$$\begin{bmatrix} 5 & -2 & -3 \\ -4 & -5 & 0 \\ -3 & 6 & 4 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} 60 \\ 0 \\ 0 \end{bmatrix}$$

$$\Delta_3 = \begin{vmatrix} 5 & -2 & 60 \\ -4 & -5 & 0 \\ -3 & 6 & 0 \end{vmatrix}$$

$(60 \cdot -5 \cdot -3) = 900$
 $(0 \cdot 6 \cdot 5) = 0$
 $(0 \cdot -2 \cdot -4) = 0$

$+ (5 \cdot -5 \cdot 0) = 0$
 $+ (-4 \cdot 6 \cdot 60) = -1440$
 $+ (-3 \cdot -2 \cdot 0) = 0$

$$\Delta_3 = (0 - 1440 + 0) - (900 + 0 + 0)$$

$$\Delta_3 = -2340$$

$$V_3 = \frac{\Delta_3}{\Delta} = \frac{-2340}{-15} = 156 \text{ V}$$



Department of Electrical, Electronic and Computer Engineering

18

L#2: 3.3 Nodal Analysis With Voltage sources

Case 1: V_s between a node and GND:
 $V_1 - 0 = 10 \text{ V}$

Case 2: V_s between two nodes:
 $V_2 - V_3 = 5 \text{ V}$
SUPERNODE

Department of Electrical, Electronic and Computer Engineering

3.3 Nodal Analysis with Voltage sources

SUPERNODE

Formed by enclosing a (dependent or independent) voltage source connected between two non-reference nodes along with any elements connected in parallel with that voltage source.

Note:

$$i_1 = -i_{2\Omega} = \frac{V_1 - V_2}{2}$$

$$i_2 = +i_{8\Omega} = \frac{V_2}{8}$$

$$i_3 = +i_{6\Omega} = \frac{V_3}{6}$$

$$i_4 = -i_{4\Omega} = \frac{V_1 - V_3}{4}$$


KCL at SUPERNODE:

$$i_{2\Omega} + i_{8\Omega} + i_{6\Omega} + i_{4\Omega} = 0$$

$$\frac{V_2 - 10}{2} + \frac{V_2 - 0}{8} + \frac{V_3 - 0}{6} + \frac{V_3 - 10}{4} = 0$$

Solve for V_2 and V_3 from (1) and (2)

Department of Electrical, Electronic and Computer Engineering

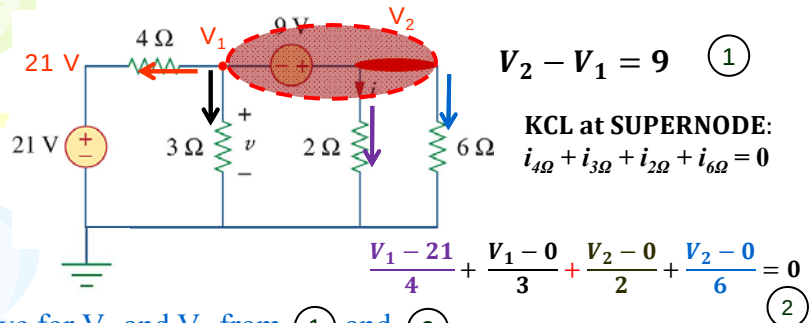PP 3-3: Find v and i in the circuit.Solve for V_2 and V_3 from (1) and (2)

$$\begin{aligned} -V_1 + V_2 &= 9 & (1) \\ 7V_1 + 8V_2 &= 63 & (2) \end{aligned}$$

$$\begin{aligned} V_1 &= V_2 - 9 \\ &= 8.4 - 9 \\ \therefore V_1 &= v = -0.6 \text{ V} \end{aligned}$$

$$\begin{aligned} x7\{ & -7V_1 + 7V_2 = 63 \\ & 7V_1 + 8V_2 = 63 \\ \hline & 15V_2 = 126 \\ & V_2 = 8.4 \text{ V} \end{aligned}$$

$$i = \frac{8.4}{2} = 4.2 \text{ A}$$

Cramer's rule

$$\begin{bmatrix} -1 & 1 \\ 7 & 8 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 9 \\ 63 \end{bmatrix}$$

UNIVERSITEIT VAN PRETORIA
UNIVERSITY OF PRETORIA
YUNIBESITHI YA PRETORIA

Department of Electrical, Electronic and Computer Engineering

21

PP 3-3: ...

$$\begin{bmatrix} -1 & 1 \\ 7 & 8 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 9 \\ 63 \end{bmatrix}$$

$$V_1 = \frac{\Delta_1}{\Delta}$$

$$\Delta_1 = \begin{vmatrix} 9 & 1 \\ 63 & 8 \end{vmatrix} = (1 \times 63) - (9 \times 8) = 63 - 72 = -9$$

$$\Delta_1 = 72 - 63 = 9$$

$$V_1 = \frac{9}{-15} = -0.6 \text{ V}$$

$$\Delta = \begin{vmatrix} -1 & 1 \\ 7 & 8 \end{vmatrix} = (1 \times 7) - (-1 \times 8) = 7 + 8 = 15$$

$$\Delta = -8 - 7 = -15$$

$$V_2 = \frac{\Delta_2}{\Delta}$$

$$\Delta_2 = \begin{vmatrix} -1 & 9 \\ 7 & 63 \end{vmatrix} = (9 \times 7) - (-1 \times 63) = 63 + 63 = 126$$


$$\Delta_2 = -63 - (63) = -126$$

$$V_2 = \frac{-126}{-15} = 8.4 \text{ V}$$

UNIVERSITEIT VAN PRETORIA
UNIVERSITY OF PRETORIA
YUNIBESITHI YA PRETORIA

Department of Electrical, Electronic and Computer Engineering

22

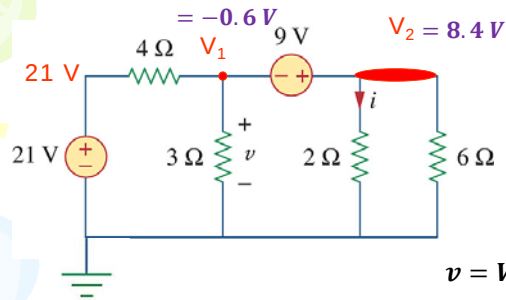PP 3-3: Find v and i 

$$v = V_1 = -0.6 \text{ V}$$

$$i = \frac{V_2}{2} = \frac{8.4}{2} = 4.2 \text{ A}$$

$$\begin{bmatrix} -1 & 1 \\ 7 & 8 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 9 \\ 63 \end{bmatrix}$$

$$V_1 = -0.6 \text{ V} \quad V_2 = 8.4 \text{ V}$$



UNIVERSITEIT VAN PRETORIA
UNIVERSITY OF PRETORIA
YUNIBESITHI YA PRETORIA

Department of Electrical, Electronic and Computer Engineering

23

PP 3-4 Find v_1 , v_2 , v_3 and i .

$$v_1 - v_2 = 10 \quad (1)$$

$$v_3 - v_2 = 5i$$

$$v_3 - v_2 = 5 \frac{v_1}{2}$$

$$-5v_1 - 2v_2 + 2v_3 = 0 \quad (2)$$


Two supernode can be merged

KCL@SN

$$i_6 + i_2 + i_4 + i_3 + i_6 = 0$$

$$\frac{v_1 - v_3}{6} + \frac{v_1}{2} + \frac{v_2}{4} + \frac{v_3}{3} + \frac{v_3 - v_1}{6} = 0 \quad \text{ } \times 12$$

$$6v_1 + 3v_2 + 4v_3 = 0 \quad (3)$$

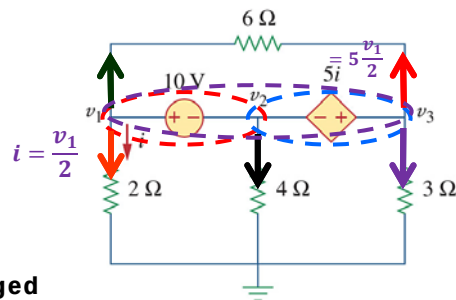

$$\begin{bmatrix} 1 & -1 & 0 \\ -5 & -2 & 2 \\ 6 & 3 & 4 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} 10 \\ 0 \\ 0 \end{bmatrix}$$



UNIVERSITEIT VAN PRETORIA
UNIVERSITY OF PRETORIA
YUNIBESITHI YA PRETORIA

Department of Electrical, Electronic and Computer Engineering

24

PP 3-4 ... Calculating Δ

$$\begin{bmatrix} 1 & -1 & 0 \\ -5 & -2 & 2 \\ 6 & 3 & 4 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} 10 \\ 0 \\ 0 \end{bmatrix}$$

$$\Delta = \begin{vmatrix} 1 & -1 & 0 \\ -5 & -2 & 2 \\ 6 & 3 & 4 \end{vmatrix}$$

$(0) = 0$
 $(2 \cdot 3 \cdot 1) = 6$
 $(4 \cdot -1 \cdot -5) = 20$
 $(1 \cdot -2 \cdot 4) = -8$
 $(-5 \cdot 3 \cdot 0) = 0$
 $(6 \cdot -1 \cdot 2) = -12$

$$\begin{aligned} \Delta &= (-8 - 12) - (6 + 20) \\ &= (-20) - (26) \\ \Delta &= -46 \end{aligned}$$



UNIVERSITEIT VAN PRETORIA
UNIVERSITY OF PRETORIA
YUNIBESITHI YA PRETORIA

Department of Electrical, Electronic and Computer Engineering

25

PP 3-4 ... Calculating v_1 using Δ_1


$$\begin{bmatrix} 1 & -1 & 0 \\ -5 & -2 & 2 \\ 6 & 3 & 4 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} 10 \\ 0 \\ 0 \end{bmatrix} \quad \Delta = -46$$

$$\Delta_1 = \begin{vmatrix} 10 & -1 & 0 \\ 0 & -2 & 2 \\ 0 & 3 & 4 \end{vmatrix}$$

$(0) = 0$
 $(2 \cdot 3 \cdot 10) = 60$
 $(4 \cdot -1 \cdot 0) = 0$
 $(10 \cdot -2 \cdot 4) = -80$
 $(0) = 0$
 $(0 \cdot \cdot) = 0$

$$\begin{aligned} \Delta_1 &= (-80) - (60) \\ \Delta_1 &= -140 \end{aligned}$$
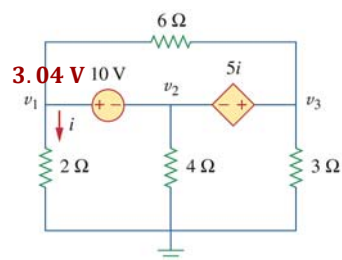
$$V_1 = \frac{\Delta_1}{\Delta} = \frac{-140}{-46} = 3.044 \text{ V}$$



$$i = \frac{3.04}{2} = 1.522 \text{ A}$$



UNIVERSITEIT VAN PRETORIA
UNIVERSITY OF PRETORIA
YUNIBESITHI YA PRETORIA

Department of Electrical, Electronic and Computer Engineering

26

PP 3-2 ... Calculating v_2 using Δ_2


$$\begin{bmatrix} 1 & -1 & 0 \\ -5 & -2 & 2 \\ 6 & 3 & 4 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} 10 \\ 0 \\ 0 \end{bmatrix}$$

$$\Delta = -46$$

$$v_1 = 3.04 \text{ V}$$

$$i = 1.52 \text{ A}$$

Method #2 for calculating v_2

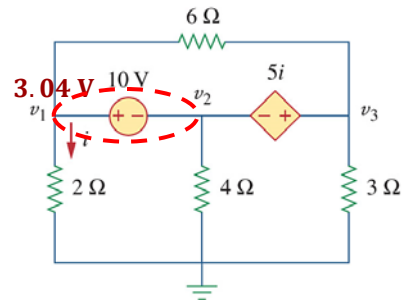

$$v_1 - v_2 = 10$$

$$v_2 = v_1 - 10$$

$$= 3.04 - 10$$

$$v_2 = -6.96 \text{ V}$$

$$\Delta_2 = \begin{vmatrix} 1 & 10 & 0 \\ -5 & 0 & 2 \\ 6 & 0 & 4 \end{vmatrix}$$

$(0) = 0$
 $(0) = 0$
 $(4 \cdot 10 \cdot -5) = -200$
 $(6 \cdot 10 \cdot 2) = 120$

$$\Delta_2 = (120) - (-200)$$

$$\Delta_2 = +320$$

$$v_2 = \frac{\Delta_2}{\Delta} = \frac{+320}{-46} = -6.96 \text{ V}$$



UNIVERSITEIT VAN PRETORIA
UNIVERSITY OF PRETORIA
YUNIBESITHI YA PRETORIA

Department of Electrical, Electronic and Computer Engineering


27

PP 3-2 ... Calculating v_3 using Δ_3

$$\begin{bmatrix} 1 & -1 & 0 \\ -5 & -2 & 2 \\ 6 & 3 & 4 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} 10 \\ 0 \\ 0 \end{bmatrix}$$

$$\Delta = -46$$

Method #2 for calculating v_3

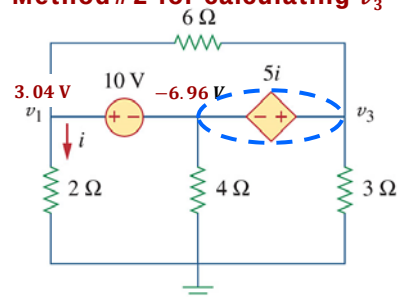

$$v_3 = 5i + v_2$$

$$i = \frac{3.04}{2} = 1.52 \text{ A}$$

$$v_3 = 5(1.52) - 6.96$$

$$v_3 = 0.65 \text{ V}$$

$$\Delta_3 = \begin{vmatrix} 1 & -1 & 10 \\ -5 & -2 & 0 \\ 6 & 3 & 0 \end{vmatrix}$$

$(10 \cdot -2 \cdot 6) = -120$
 $(0) = 0$
 $(0) = 0$
 $(-5 \cdot 3 \cdot 10) = -150$

$$\Delta_3 = (-150) - (-120)$$

$$\Delta_3 = -30$$

$$v_3 = \frac{\Delta_3}{\Delta} = \frac{-30}{-46} = 0.65 \text{ V}$$




UNIVERSITEIT VAN PRETORIA
UNIVERSITY OF PRETORIA
YUNIBESITHI YA PRETORIA

Department of Electrical, Electronic and Computer Engineering

28

Problem 3-4 Find I_1 through I_4 .

$$I_1 = \frac{V_1}{5}$$

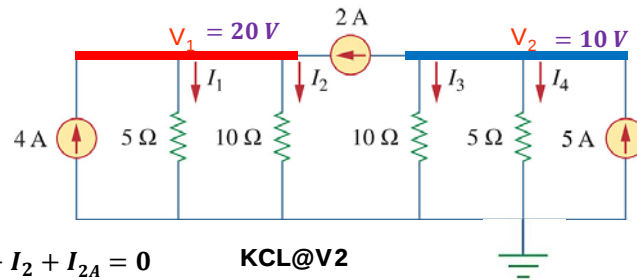**KCL@V1**

$$I_{4A} - I_1 - I_2 + I_{2A} = 0$$

$$4 - \frac{V_1}{5} - \frac{V_1}{10} + 2 = 0$$

$$V_1 = 20 \text{ V}$$

$$I_1 = \frac{20}{5} = 4 \text{ A}$$

$$I_2 = \frac{20}{10} = 2 \text{ A}$$

KCL@V2

$$-2 - I_3 - I_4 + 5 = 0$$

$$-\frac{V_2}{10} - \frac{V_2}{5} + 3 = 0$$

$$V_2 = 10 \text{ V}$$

$$I_3 = \frac{10}{10} = 1 \text{ A}$$

$$I_4 = \frac{10}{5} = 2 \text{ A}$$

$$I_3 = \frac{V_2}{5}$$


 UNIVERSITEIT VAN PRETORIA
 UNIVERSITY OF PRETORIA
 YUNIBESITHI YA PRETORIA

Department of Electrical, Electronic and Computer Engineering

29

Problem 3-16 Find v_1 , v_2 and v_3 .

$$v_1 - v_2 = 2v_o$$

$$v_1 - v_2 = 2(v_2)$$

$$v_1 = 3v_2 \quad (1)$$

KCL@SN

$$i_2 + i_{2A} + i_1 + i_4 + i_8 = 0$$

$$(v_1 - 13)2 - 2 + (v_1)1 + (v_2)4 + (v_2 - 13)8 = 0$$


$$3v_1 + 12v_2 = 132 \quad (2)$$

Substitute $v_1 = 3v_2$ into (2)

$$9v_2 + 12v_2 = 132$$

$$\rightarrow v_2 = 6.29 \text{ V}$$

$$v_1 = 3 \times 6.29 = 18.87 \text{ V}$$

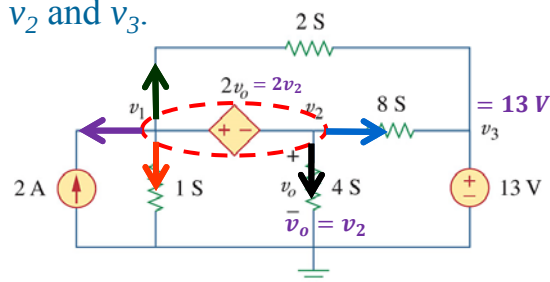
 UNIVERSITEIT VAN PRETORIA
 UNIVERSITY OF PRETORIA
 YUNIBESITHI YA PRETORIA

Department of Electrical, Electronic and Computer Engineering

30

Class Test #1

Date: 19 February
 Time: 7:30
 Scope: Ch01 & Ch02
 Venue: Eng 3-1 Surnames: A – K
 Eng 3-6 Surnames: L – O
 IT 2-23 Surnames: P – Z



Department of Electrical, Electronic and Computer Engineering

31

L#3: 3.4 Mesh Analysis

Why?


1. Mesh analysis provides another general procedure for analyzing circuits using mesh currents as the circuit variables.
2. Nodal analysis applies KCL to find unknown voltages in a given circuit, while mesh analysis applies KVL to find unknown currents.
3. A mesh is a loop which does not contain any other loops within it.



Department of Electrical, Electronic and Computer Engineering

32

3.4 Mesh Analysis STEPS

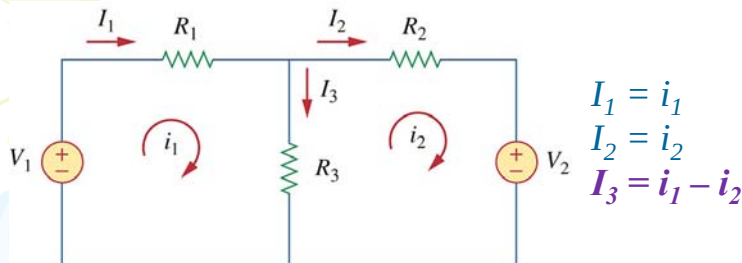

Steps to determine the mesh currents:

1. Assign mesh currents $i_1, i_2, \dots$, in to the n meshes – clock wise.
2. Apply KVL to each of the n meshes. Use Ohm's law to express the voltages in terms of the mesh currents.
3. Solve the resulting n simultaneous equations to get the mesh currents.




UNIVERSITEIT VAN PRETORIA
UNIVERSITY OF PRETORIA
YUNIBESITHI YA PRETORIA

Department of Electrical, Electronic and Computer Engineering

33

3.4 Mesh Analysis STEPS: KVL in Loops

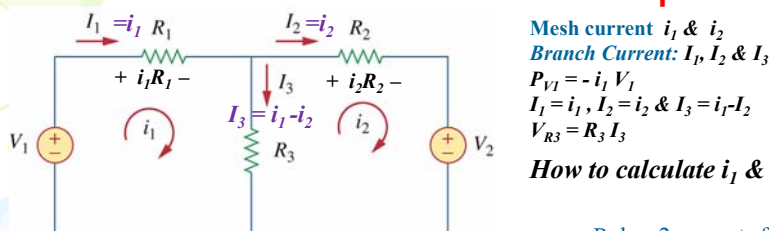

KVL@Loop 1: $-V_1 + V_{R1} + V_{R3} = 0$
 $-V_1 + R_1 i_1 + R_3 (i_1 - i_2) = 0$
 Write ito: $a_1 i_1 + b_1 i_2 = k_1$
 $(R_1 + R_3) i_1 + (-R_3) i_2 = V_1$

R_3 has 2 currents flowing through it: i_1 and i_2

I_{net} through R_3 wrt loop 1

$$R(i_{loop} - i_{opposing_loop})$$

KVL@Loop 2: $V_2 + V_{R3} + V_{R2} = 0$
 $V_2 + R_3 (i_2 - i_1) + R_2 i_2 = 0$
 Write ito: $a_2 i_1 + b_2 i_2 = k_2$
 $(-R_3) i_1 + (R_2 + R_3) i_2 = -V_2$


I_{net} through R_3 wrt loop 2



UNIVERSITEIT VAN PRETORIA
UNIVERSITY OF PRETORIA
YUNIBESITHI YA PRETORIA

Department of Electrical, Electronic and Computer Engineering

34

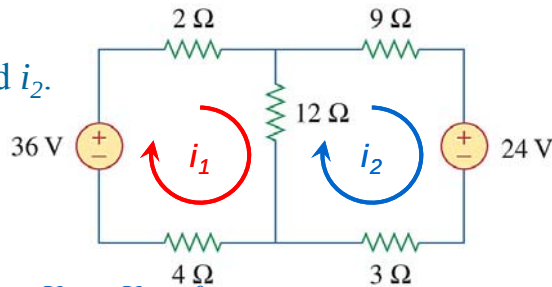PP 3-5Determine i_1 and i_2 .**KVL@Loop 1:**

$$\begin{aligned} V_{36V} + V_{2\Omega} + V_{12\Omega} + V_{4\Omega} &= 0 \\ -36 + 2i_1 + 12(i_1 - i_2) + 4i_1 &= 0 \\ (2+12+4)i_1 + (-12)i_2 &= 36 \\ 18i_1 - 12i_2 &= 36 \end{aligned} \quad (1)$$

KVL@Loop 2:

$$\begin{aligned} V_{24V} + V_{3\Omega} + V_{12\Omega} + V_{9\Omega} &= 0 \\ 24 + 3i_2 + 12(i_2 - i_1) + 9i_2 &= 0 \\ -12i_1 + (3+12+9)i_2 &= -24 \\ -12i_1 + 24i_2 &= -24 \end{aligned} \quad (2)$$

$$\text{Matrix: } \begin{bmatrix} 18 & -12 \\ -12 & 24 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} 36 \\ -24 \end{bmatrix}$$

$$\Delta = \begin{vmatrix} 18 & -12 \\ -12 & 24 \end{vmatrix} = 288$$

$$\Delta_1 = \begin{vmatrix} 36 & -12 \\ -24 & 24 \end{vmatrix} = 576$$

$$i_1 = \frac{\Delta_1}{\Delta} = \frac{576}{288} = 2 \text{ A}$$


$$\Delta_2 = \begin{vmatrix} 18 & 36 \\ -12 & -24 \end{vmatrix} = 0$$

$$i_2 = \frac{\Delta_2}{\Delta} = \frac{0}{288} = 0 \text{ A}$$

UNIVERSITEIT VAN PRETORIA
UNIVERSITY OF PRETORIA
YUNIBESITHI YA PRETORIA

Department of Electrical, Electronic and Computer Engineering

35

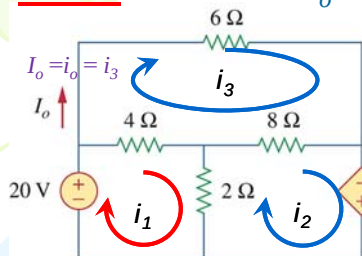PP 3-6 Determine I_o .**KVL@
Loop 3:**

$$\begin{aligned} V_{6\Omega} + V_{8\Omega} + V_{4\Omega} &= 0 \\ 6i_3 + 8(i_3 - i_2) + 4(i_3 - i_1) &= 0 \\ (-4)i_1 + (-8)i_2 + (18)i_3 &= 0 \end{aligned} \quad (3)$$

**KVL@
Loop 1:**

$$\begin{aligned} V_{20V} + V_{4\Omega} + V_{2\Omega} &= 0 \\ -20 + 4(i_1 - i_3) + 2(i_1 - i_2) &= 0 \\ (4+2)i_1 + (-2)i_2 + (-4)i_3 &= 20 \\ 6i_1 + (-2)i_2 + (-4)i_3 &= 20 \end{aligned} \quad (1)$$

**KVL@
Loop 2:**

$$\begin{aligned} V_{10i_o} + V_{2\Omega} + V_{8\Omega} &= 0 \\ -10i_o + 2(i_2 - i_1) + 8(i_2 - i_3) &= 0 \\ -10i_3 + 2(i_2 - i_1) + 8(i_2 - i_3) &= 0 \\ (-2)i_1 + (10)i_2 + (-18)i_3 &= 0 \end{aligned} \quad (2)$$

$$\begin{bmatrix} 6 & -2 & -4 \\ -2 & 10 & -18 \\ -4 & -8 & 18 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} 20 \\ 0 \\ 0 \end{bmatrix}$$

UNIVERSITEIT VAN PRETORIA
UNIVERSITY OF PRETORIA
YUNIBESITHI YA PRETORIA

Department of Electrical, Electronic and Computer Engineering

36

PP 3-6 Determine I_o cont. ... calculate Δ

$$\begin{bmatrix} 6 & -2 & -4 \\ -2 & 10 & -18 \\ -4 & -8 & 18 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} 20 \\ 0 \\ 0 \end{bmatrix}$$

$$\Delta = \begin{vmatrix} 6 & -2 & -4 \\ -2 & 10 & -18 \\ -4 & -8 & 18 \end{vmatrix}$$

$(-4 \cdot 10 \cdot -4) = 160$
 $(-18 \cdot -8 \cdot 6) = 864$
 $(18 \cdot -2 \cdot -2) = 72$
 $(6 \cdot 10 \cdot 18) = 1080$
 $(-2 \cdot -8 \cdot -4) = -64$
 $(-4 \cdot -2 \cdot -18) = -144$

$$\Delta = (1080 - 64 - 144) - (160 + 864 + 72) = -224$$

PP 3-6 Determine I_o cont. ... calculate Δ_3

$$\begin{bmatrix} 6 & -2 & -4 \\ -2 & 10 & -18 \\ -4 & -8 & 18 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} 20 \\ 0 \\ 0 \end{bmatrix}$$

Only I_o is asked so calculate Δ_3


$$\Delta_3 = \begin{vmatrix} 6 & -2 & 20 \\ -2 & 10 & 0 \\ -4 & -8 & 0 \end{vmatrix}$$

$(20 \cdot 10 \cdot -4) = -800$
 $(0) = 0$
 $(0) = 0$
 $(6 \cdot 10 \cdot 0) = 0$
 $(-2 \cdot -8 \cdot 20) = 320$
 $(0) = 0$

$$\Delta_3 = (320) - (-800) = 1120$$

$$I_o = i_3 = \frac{\Delta_3}{\Delta} = \frac{1120}{-224} = -5 \text{ A}$$

Problem 3-39 Determine i_1 and i_2 (Mesh Analysis)

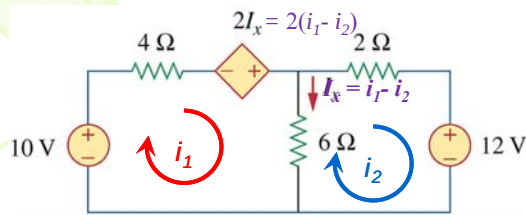

Loop 1: $V_{10V} + V_{4\Omega} + V_{2I_x} + V_{6\Omega} = 0$
 $-10 + 4i_1 - 2I_x + 6(i_1 - i_2) = 0$
 $4i_1 - 2(i_1 - i_2) + 6(i_1 - i_2) = 10$
 $8i_1 + (-4)i_2 = 10 \quad (1)$

Loop 2: $V_{12V} + V_{6\Omega} + V_{2\Omega} = 0$
 $12 + 6(i_2 - i_1) + 2i_2 = 0$
 $(-6)i_1 + 8i_2 = -12 \quad (2)$

$$2 \times (1) + (2)$$

$$\begin{aligned} 16i_1 + (-8)i_2 &= 20 \\ (-6)i_1 + 8i_2 &= -12 \\ \hline 10i_1 &= 8 \\ \therefore i_1 &= 0.8 \text{ A} \quad (3) \end{aligned}$$

$$(3) \text{ in } (2):$$

$$\begin{aligned} (-6)(0.8) + 8i_2 &= -12 \\ \therefore i_2 &= -0.9 \text{ A} \end{aligned}$$




UNIVERSITEIT VAN PRETORIA
UNIVERSITY OF PRETORIA
YUNIBESITHI YA PRETORIA

Department of Electrical, Electronic and Computer Engineering

39

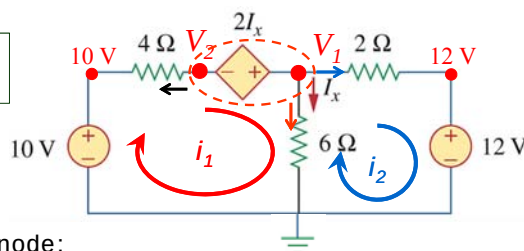Problem 3-39 Determine i_1 and i_2 (Method#2 Supernode)

$$\begin{aligned} i_1 &= \frac{10 - V_2}{4} \\ &= \frac{3.2}{4} \\ i_1 &= 0.8 \text{ A} \end{aligned}$$



$$\begin{aligned} i_2 &= \frac{V_1 - 12}{2} \\ &= \frac{10.2 - 12}{2} \\ i_2 &= -0.9 \text{ A} \end{aligned}$$

KVL@Supernode:

$$V_1 - V_2 = 2I_x$$

$$I_x = V_1/6$$

$$2V_1 - 3V_2 = 0 \quad (1)$$

KCL @ SN:

$$i_{4\Omega} + i_{6\Omega} + i_{4\Omega} = 0$$

$$\times 12 \left\{ \frac{V_2 - 10}{4} + \frac{V_1}{6} + \frac{V_1 - 12}{2} = 0 \right.$$

$$3V_2 - 30 + 2V_1 + 6V_1 - 72 = 0$$

$$8V_1 + 3V_2 = 102 \quad (2)$$

$$(1) + (2):$$

$$\begin{aligned} (8 + 2)V_1 + (3 - 3)V_2 &= 102 \\ \therefore V_1 &= 10.2 \text{ V} \end{aligned}$$

$$\therefore V_2 = 6.8 \text{ V}$$




UNIVERSITEIT VAN PRETORIA
UNIVERSITY OF PRETORIA
YUNIBESITHI YA PRETORIA

Department of Electrical, Electronic and Computer Engineering

40

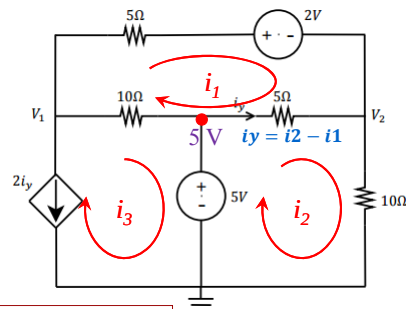2014: Use mesh analysis to find V_1 , V_2 and i_y



Solve

$$\begin{aligned} i_1 &= -1.4 \text{ A} \\ i_2 &= -0.13 \text{ A} \\ i_3 &= -2.53 \text{ A} \end{aligned}$$

$$\begin{aligned} i_y &= -0.13 - (-1.4) \\ &= 1.27 \text{ A} \end{aligned}$$

V_1 ?

Using Ohms Law ($V=RI$) at 10Ω branch

$$\begin{aligned} V_1 - 5 &= 10(i_3 - i_1) \\ V_1 &= 5 + 10(-2.53 - (-1.4)) \\ &= 5 - 11.3 = -6.3 \text{ V} \end{aligned}$$

KVL@i3

$$\begin{aligned} i_3 &= -2i_y = -2(i_2 - i_1) \\ 2i_1 - 2i_2 - i_3 &= 0 \quad (1) \end{aligned}$$

KVL@i1

$$\begin{aligned} (5 + 5 + 10)i_1 - 5i_2 - 10i_3 + 2 &= 0 \\ 20i_1 - 5i_2 - 10i_3 &= -2 \quad (2) \end{aligned}$$

KVL@i2

$$\begin{aligned} (5 + 10)i_2 - 5i_1 - 5 &= 0 \\ -5i_1 + 15i_2 &= 5 \quad (3) \end{aligned}$$

V_2 ?

Using Ohms Law ($V=RI$) at 5Ω branch

$$\begin{aligned} 5 - V_2 &= 5i_y \\ V_2 &= 5 - 5(1.27) \\ &= -1.35 \text{ V} \end{aligned}$$




UNIVERSITEIT VAN PRETORIA
UNIVERSITY OF PRETORIA
YUNIBESITHI YA PRETORIA

Department of Electrical, Electronic and Computer Engineering

41

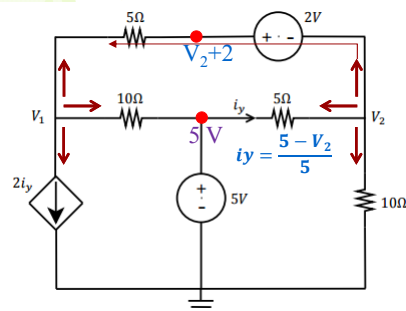2014: Use Nodal analysis to find V_1 , V_2 and i_y



KCL@V1

$$\begin{aligned} 2i_y + i_{10\Omega} + i_{5\Omega} &= 0 \\ 2i_y + \frac{V_1 - 5}{10} + \frac{V_1 - (V_2 + 2)}{5} &= 0 \\ 2\left(\frac{5 - V_2}{5}\right) + \frac{V_1 - 5}{10} + \frac{V_1 - (V_2 + 2)}{5} &= 0 \\ 3V_1 - 6V_2 &= -11 \quad (1) \end{aligned}$$

KCL@V2

$$\begin{aligned} i_{10\Omega} + i_{5\Omega} + i_{2V} &= 0 \\ \left(\frac{V_2}{10}\right) + \frac{V_2 - 5}{5} + \frac{(V_2 + 2) - V_1}{5} &= 0 \\ -2V_1 + 5V_2 &= 6 \quad (2) \end{aligned}$$

Solve

$$\begin{aligned} V_1 &= -6.33 \text{ A} \\ V_2 &= -1.33 \text{ A} \end{aligned}$$

$$\begin{aligned} i_y &= \frac{5 - (-1.33)}{5} \\ &= 1.27 \text{ A} \end{aligned}$$




UNIVERSITEIT VAN PRETORIA
UNIVERSITY OF PRETORIA
YUNIBESITHI YA PRETORIA

Department of Electrical, Electronic and Computer Engineering

42

L# 4: 3.5 Mesh Analysis With Current Sources

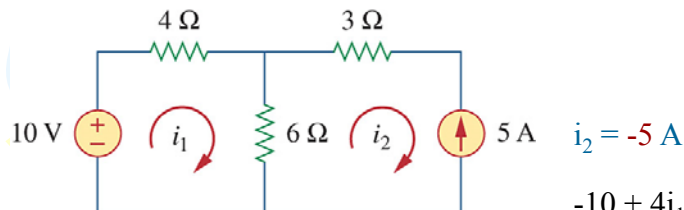CASE #1: A current source exists only in one mesh:
That loop current is then known.



$$\begin{aligned} i_2 &= -5 \text{ A} \\ -10 + 4i_1 + 6(i_1 - i_2) &= 0 \\ -10 + 10i_1 - 6(-5) &= 0 \\ 10i_1 &= -20 \\ i_1 &= -2 \text{ A} \end{aligned}$$



UNIVERSITEIT VAN PRETORIA
UNIVERSITY OF PRETORIA
YUNIBESITHI YA PRETORIA

Department of Electrical, Electronic and Computer Engineering

43

Problem 3-46

Solve for the mesh currents.


KVL@Loop 1:

$$\begin{aligned} -60 + 2i_1 + 1(i_1 - i_2) &= 0 \\ 3i_1 - i_2 &= 60 \quad (1) \end{aligned}$$

KVL@Loop 2:

$$\begin{aligned} 1(i_2 - i_1) + 3(i_2 - 2) + 1(i_2 - i_3) &= 0 \\ -i_1 + 5i_2 - i_3 &= 6 \quad (2) \end{aligned}$$

Solve for i_1, i_2 & i_3

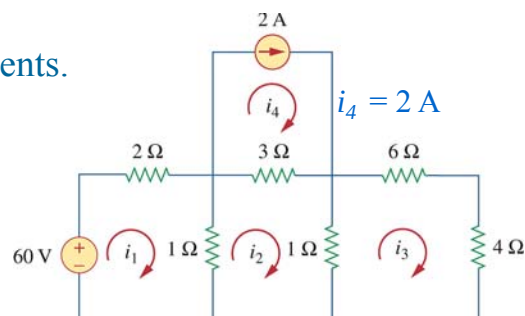

KVL@Loop 3:

$$\begin{aligned} 1(i_3 - i_2) + 10i_3 &= 0 \\ -i_2 + 11i_3 &= 0 \quad (3) \end{aligned}$$

Solve

$$\begin{aligned} i_1 &= 21.9 \text{ A} \\ i_2 &= 5.68 \text{ A} \\ i_3 &= 0.52 \text{ A} \end{aligned}$$



UNIVERSITEIT VAN PRETORIA
UNIVERSITY OF PRETORIA
YUNIBESITHI YA PRETORIA


Department of Electrical, Electronic and Computer Engineering

44

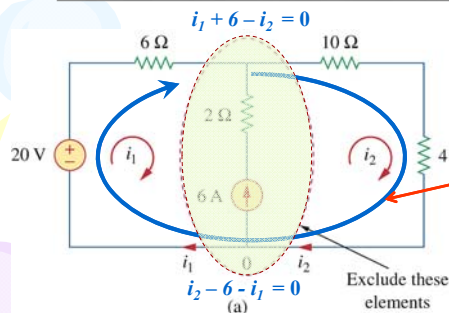3.5 Mesh Analysis With Current Sources

CASE #2: A current source exists between two meshes: SUPERMESH

A *SUPERMESH* results when two meshes have a current source (dependent or independent), with or without other elements in series, in common.



Common source:

Note: i_2 flows in the same direction as the 6A source.

$$i_2 - i_1 = 6 \quad i_1 = 2.8 - 6$$

$$i_1 = i_2 - 6 \quad (1) \quad \therefore i_1 = -3.2 \text{ A}$$

SUPERMESH:

$$-20 + 6i_1 + 10i_2 + 4i_2 = 0 \quad (2)$$

$$(1) \text{ in } (2)$$

$$-20 + 6(i_2 - 6) + 10i_2 + 4i_2 = 0$$

$$i_2 = 2.8 \text{ A}$$




UNIVERSITEIT VAN PRETORIA
UNIVERSITY OF PRETORIA
YUNIBESITHI YA PRETORIA

Department of Electrical, Electronic and Computer Engineering

45

PP 3-7 Determine i_1 , i_2 and i_3 .

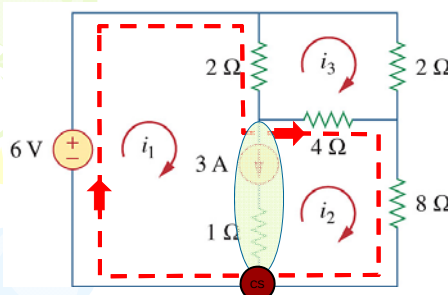

Note: 3A current source common to mesh i_1 & i_2

Common source:

$$i_1 - i_2 - 3 = 0 \quad (1)$$

Supermesh:

$$-6 + 2(i_1 - i_3) + 4(i_2 - i_3) + 8i_2 = 0$$

$$2i_1 + 12i_2 - 6i_3 = 6 \quad (2)$$

Loop 3:

$$2(i_3 - i_1) + 2i_3 + 4(i_3 - i_2) = 0$$

$$-2i_1 - 4i_2 + 8i_3 = 0 \quad (3)$$

Solve for i_1 , i_2 & i_3

Solve

$$i_1 = 3.47 \text{ A}$$

$$i_2 = 0.47 \text{ A}$$

$$i_3 = 1.11 \text{ A}$$



UNIVERSITEIT VAN PRETORIA
UNIVERSITY OF PRETORIA
YUNIBESITHI YA PRETORIA

Department of Electrical, Electronic and Computer Engineering

46

Problem 3-46Find v_o and i_o **Supermesh:**

$$\begin{aligned} 2i_1 + 1(i_1 - i_3) + 2(i_2 - i_3) + 16 &= 0 \\ 3i_1 + 2i_2 - 3i_3 &= -16 \quad (2) \end{aligned}$$

Loop 3:

$$\begin{aligned} 1(i_3 - i_1) + 3i_3 + 2(i_3 - i_2) &= 0 \\ -i_1 - 2i_2 + 6i_3 &= 0 \quad (3) \end{aligned}$$

Solve

$$i_1 = -10.67 \text{ A}$$

$$i_2 = 10.67 \text{ A}$$

$$i_3 = 1.78 \text{ A}$$


$$i_o = 10.67 \text{ A}$$

Common source:

$$i_2 = 2i_o + i_1$$

$$i_2 = 2(-i_1) + i_1$$

$$i_1 + i_2 = 0 \quad (1)$$

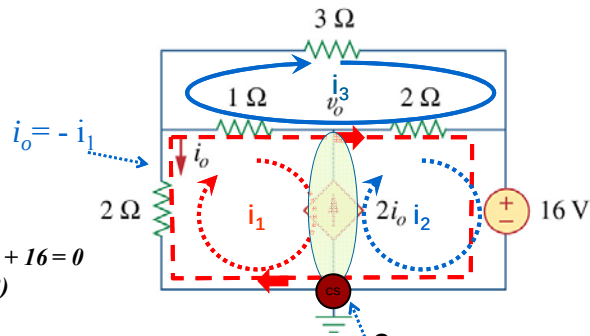
 UNIVERSITEIT VAN PRETORIA
 UNIVERSITY OF PRETORIA
 YUNIBESITHI YA PRETORIA

Department of Electrical, Electronic and Computer Engineering

47

Problem 3-46Find v_o

$$i_1 = -10.67 \text{ A}$$

$$i_2 = 10.67 \text{ A}$$

$$i_3 = 1.78 \text{ A}$$

$$i_o = 10.67 \text{ A}$$

**KVL:**

$$2i_1 + 1(i_1 - i_3) + v_o = 0$$

$$v_o = -3i_1 + i_3$$

$$v_o = 33.78 \text{ V}$$

KVL:

$$-v_o + 2(i_2 - i_3) + 16 = 0$$

$$v_o = 2(10.67 - 1.78) + 16$$

$$v_o = 33.78 \text{ V}$$


 UNIVERSITEIT VAN PRETORIA
 UNIVERSITY OF PRETORIA
 YUNIBESITHI YA PRETORIA

Department of Electrical, Electronic and Computer Engineering

48

L#5: 3.6 Nodal and Mesh Analysis by inspection

Special case #1: All sources = independent **current** sources

KCL@ V1 $G = \frac{1}{R}$

$$I_1 - I_2 - i_{G1} - i_{G2} = 0$$

$$G_1 V_1 + G_2 (V_1 - V_2) = I_1 - I_2$$

$$(G_1 + G_2) + (-G_2)V_2 = I_1 - I_2$$

Matrix

$$\begin{bmatrix} G_1 + G_2 & -G_2 \\ -G_2 & G_2 + G_3 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} I_1 - I_2 \\ I_2 \end{bmatrix}$$

$$\begin{bmatrix} G_{11} & -G_{12} \\ -G_{21} & G_{22} \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} I_{in} - I_{out} \\ I_{in} - I_{out} \end{bmatrix}$$

KCL@ V2

$$I_2 = i_{G3} + i_{G2}$$

$$G_3 V_2 + G_2 (V_2 - V_1) = I_2$$


$$(-G_2)V_1 + (G_2 + G_3)V_2 = I_2$$

Note:

$$G_{12} = G_{21}$$

$$G_{13} = G_{31}$$

$$G_{23} = G_{32}$$

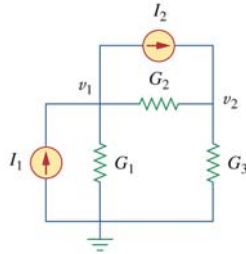

Conductance Matrix

$\begin{bmatrix} \blacksquare & \\ & \blacksquare \end{bmatrix}$ - Diagonal elements ($G_{11}, G_{22}, \dots$) = sum of all G 's connected to that node.

$\begin{bmatrix} & \blacksquare \\ \blacksquare & \end{bmatrix}$ - Off-diagonal elements ($G_{12}, G_{21}, \dots$) = $-G$ connected between the two nodes.



UNIVERSITEIT VAN PRETORIA
UNIVERSITY OF PRETORIA
YUNIBESITHI YA PRETORIA


Department of Electrical, Electronic and Computer Engineering

49

PP 3-8 By inspection, obtain the node voltage equations for the circuit in matrix form.

Current only source, use $\bar{G} \cdot \bar{V} = \bar{I}$

Convert all R 's into G 's

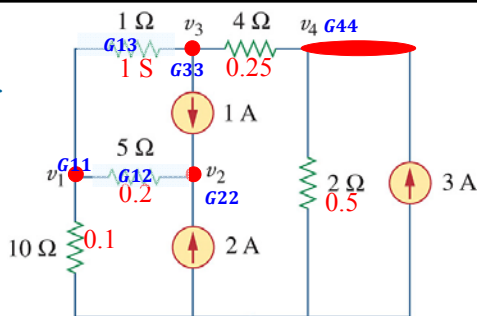

$$\begin{bmatrix} (1 + 0.2 + 0.1) & -0.2 & -1 & 0 \\ -0.2 & 0.2 & 0 & 0 \\ -1 & 0 & (1 + 0.25) & -0.25 \\ 0 & 0 & -0.25 & (0.25 + 0.5) \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \\ v_4 \end{bmatrix} = \begin{bmatrix} 0 \\ 2 + 1 \\ -1 \\ 3 \end{bmatrix}$$

Note:

$$\begin{bmatrix} G_{11} & -G_{12} & -G_{13} & -G_{14} \\ -G_{21} & G_{22} & -G_{23} & -G_{24} \\ -G_{31} & -G_{32} & G_{33} & -G_{34} \\ -G_{41} & -G_{42} & -G_{43} & G_{44} \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \\ v_4 \end{bmatrix} = \begin{bmatrix} I_{in} - I_{out} \\ I_{in} - I_{out} \\ I_{in} - I_{out} \\ I_{in} - I_{out} \end{bmatrix}$$




UNIVERSITEIT VAN PRETORIA
UNIVERSITY OF PRETORIA
YUNIBESITHI YA PRETORIA

Department of Electrical, Electronic and Computer Engineering

50

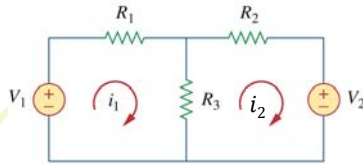3.6 Nodal and Mesh Analysis by inspection

Special case #2: All sources = independent **voltage** sources



KVL@ i_1

$$-V_1 + R_1 i_1 + R_3 (i_1 - i_2) = 0$$

$$(R_1 + R_3) i_1 + (-R_3) i_2 = V_1$$

KVL@ i_2

$$V_2 + R_2 i_2 + R_3 (i_2 - i_1) = 0$$

$$(-R_3) i_1 + (R_2 + R_3) i_2 = -V_2$$

Note:

$$R_{12} = R_{21}$$

$$R_{13} = R_{31}$$

$$R_{14} = R_{41}$$

$$R_{23} = R_{32}$$

$$R_{24} = R_{42}$$

$$R_{34} = R_{43}$$

$$\begin{bmatrix} R_{11} & -R_{12} \\ -R_{21} & R_{22} \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} \Sigma V \\ \Sigma V \end{bmatrix}$$

$$\begin{bmatrix} R_1 + R_3 & -R_3 \\ -R_3 & R_2 + R_3 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} V_1 \\ -V_2 \end{bmatrix}$$

Resistance Matrix

$\begin{bmatrix} \blacksquare & \\ & \blacksquare \end{bmatrix}$ - Diagonal elements ($R_{11}, R_{22}, \dots$)
= sum of all R 's in the loop.

$\begin{bmatrix} & \blacksquare \\ \blacksquare & \end{bmatrix}$ - Off-diagonal elements ($R_{12}, R_{21}, \dots$)
= $-R$ common to two loop between the two MESH

Sum of all the voltage increases in the loop:

In @ $- = +$

In @ $+ = -$

Remember: V is taken to the other side in the KVL equation.




UNIVERSITEIT VAN PRETORIA
UNIVERSITY OF PRETORIA
YUNIBESITHI YA PRETORIA

Department of Electrical, Electronic and Computer Engineering

51

PP 3-9 By inspection, obtain the mesh-current equations for the circuit in matrix form.

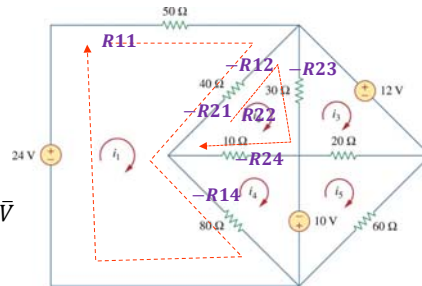ONLY voltage source, use $\bar{R} \cdot \bar{I} = \bar{V}$



Note:

$$R_{12} = R_{21}$$

$$R_{13} = R_{31}$$

$$R_{14} = R_{41}$$

$$R_{23} = R_{32}$$

$$R_{24} = R_{42}$$

$$R_{34} = R_{43}$$

$$\begin{bmatrix} (50+40+80) & -40 & 0 & -80 & 0 \\ -40 & (40+30+10) & -30 & -10 & 0 \\ 0 & -30 & (30+20) & 0 & -20 \\ -80 & -10 & 0 & (10+80) & 0 \\ 0 & 0 & -20 & 0 & (20+60) \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \\ i_5 \end{bmatrix} = \begin{bmatrix} 24 \\ 0 \\ -12 \\ 10 \\ -10 \end{bmatrix}$$

$$\begin{bmatrix} 170 & -40 & 0 & -80 & 0 \\ -40 & 80 & -30 & -10 & 0 \\ 0 & -30 & 50 & 0 & -20 \\ -80 & -10 & 0 & 90 & 0 \\ 0 & 0 & -20 & 0 & 80 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \\ i_5 \end{bmatrix} = \begin{bmatrix} 24 \\ 0 \\ -12 \\ 10 \\ -10 \end{bmatrix}$$

$$\begin{bmatrix} R_{11} & -R_{12} & -R_{13} & -R_{14} \\ -R_{21} & R_{22} & -R_{23} & -R_{24} \\ -R_{31} & -R_{32} & R_{33} & -R_{34} \\ -R_{41} & -R_{42} & -R_{43} & R_{44} \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \end{bmatrix} = \begin{bmatrix} \Sigma V \\ \Sigma V \\ \Sigma V \\ \Sigma V \end{bmatrix}$$




UNIVERSITEIT VAN PRETORIA
UNIVERSITY OF PRETORIA
YUNIBESITHI YA PRETORIA

Department of Electrical, Electronic and Computer Engineering

52

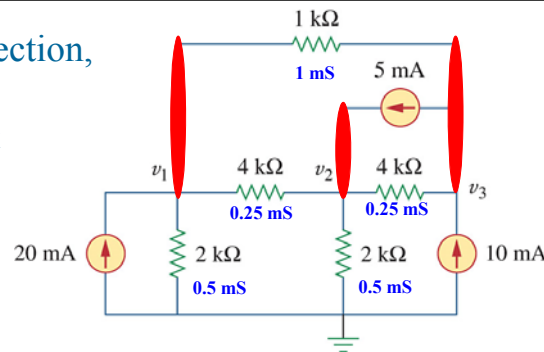Problem 3-69 By inspection, obtain the node voltage equations for the circuit

Current only source, use $\vec{G} \cdot \vec{V} = \vec{I}$
Convert all R's into G's



$$\begin{bmatrix} (0.25+0.5)\text{m} & -0.25\text{m} & -1\text{m} \\ -0.25\text{m} & (0.25+0.5+0.25)\text{m} & -0.25\text{m} \\ -1\text{m} & -0.25\text{m} & (0.25+1)\text{m} \end{bmatrix} \cdot \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} 20\text{m} \\ 5\text{m} \\ (10-5)\text{m} \end{bmatrix}$$

X 1000

$$\begin{bmatrix} 0.75 & -0.25 & -1 \\ -0.25 & 1 & -0.25 \\ -1 & -0.25 & 1.25 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} 20 \\ 5 \\ 5 \end{bmatrix}$$



UNIVERSITEIT VAN PRETORIA
UNIVERSITY OF PRETORIA
YUNIBESITHI YA PRETORIA

Department of Electrical, Electronic and Computer Engineering

53

L#6:

3.7 Nodal versus Mesh Analysis

To select the method that results in the smaller number of equations. For example:

1. Choose nodal analysis for circuit with fewer nodes than meshes.
 * Choose mesh analysis for circuit with fewer meshes than nodes.
 * Networks that contain many series connected elements, voltage sources, or supermeshes are more suitable for mesh analysis.
 * Networks with parallel-connected elements, current sources, or supernodes are more suitable for nodal analysis.
2. If node voltages are required, it may be expedient to apply nodal analysis. If branch or mesh currents are required, it may be better to use mesh analysis.



UNIVERSITEIT VAN PRETORIA
UNIVERSITY OF PRETORIA
YUNIBESITHI YA PRETORIA

Department of Electrical, Electronic and Computer Engineering

54

Revision




Department of Electrical, Electronic and Computer Engineering

55

2012: Answer the questions

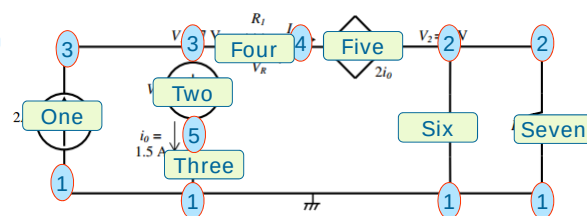- How many nodes are there in the circuit? [1]
- How many branches are there in the circuit? [1]
- Determine the voltage V_S . [1]
- Determine the voltage V_R over resistor R_1 . [2]
- Determine the current I_X . [2]




Department of Electrical, Electronic and Computer Engineering

56

2012: Source voltage V_S and resistors R_1 , R_2 and R_3 are unknown:

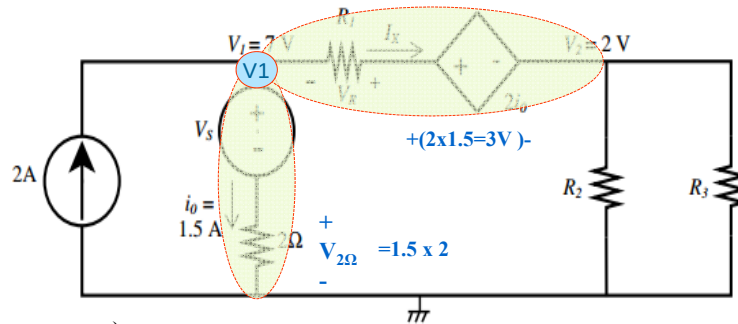- c) Determine the voltage V_S . [1]
 d) Determine the voltage V_R over resistor R_1 . [2]
 e) Determine the current I_X . [2]



c)
 $V_1 - 0 = V_S + V_{2\Omega}$
 $7 = V_S + 3$
 $V_S = 4 \text{ V}$

d)
 $V_1 - V_2 = -V_R + 2i_o$
 $V_R = 2i_o - 7 + 2$
 $= 3 - 7 + 2$
 $V_R = -2 \text{ V}$

e) KCL @ V1
 $I_{in} = I_{out}$
 $2 = I_X + 1.5$
 $I_X = 0.5 \text{ A}$




UNIVERSITEIT VAN PRETORIA
 UNIVERSITY OF PRETORIA
 YUNIBESITHI YA PRETORIA

Department of Electrical, Electronic and Computer Engineering

57

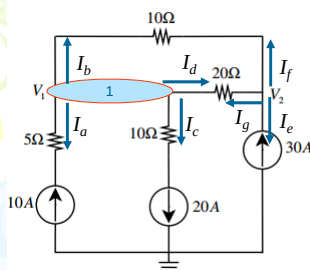2012: Use node analysis to set up two equations of the following form for the circuit: $a V_1 + b V_2 = -200$ $c V_1 + d V_2 = 600$



KCL @ V1

$I_a + I_b + I_c + I_d = 0$
 $-10 + \frac{V_1 - V_2}{10} + 20 + \frac{V_1 - V_2}{20} = 0$
 $-200 + 2V_1 - 2V_2 + 400 + V_1 - V_2 = 0$
 $3V_1 - 3V_2 = -200 \quad (1)$

KCL @ V2

$I_e + I_f + I_g = 0$
 $-30 + \frac{V_2 - V_1}{10} + \frac{V_2 - V_1}{20} = 0$
 $-600 + 2V_2 - 2V_1 + V_2 - V_1 = 0$
 $-3V_1 + 3V_2 = 600 \quad (2)$




UNIVERSITEIT VAN PRETORIA
 UNIVERSITY OF PRETORIA
 YUNIBESITHI YA PRETORIA

Department of Electrical, Electronic and Computer Engineering

58

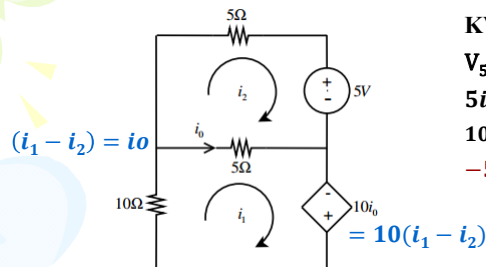2012: Use mesh analysis to set up two equations of the following form for the circuit: $a i_1 + b i_2 = 0$ $c i_1 + d i_2 = -5$ Solve for i_o and power associated with dependable source



KVL@ i_1

$$\begin{aligned} V_{10\Omega} + V_{5\Omega} + V_{10i_o} &= 0 \\ 10i_1 + 5(i_1 - i_2) - 10i_o &= 0 \\ 10i_1 + 5(i_1 - i_2) - 10(i_1 - i_2) &= 0 \\ \mathbf{5i_1 + 5i_2 = 0} \quad (1) \end{aligned}$$

KVL@ i_2

$$\begin{aligned} V_{5\Omega} + V_{5V} + V_{5\Omega} &= 0 \\ 5i_2 + 5 + 5(i_2 - i_1) &= 0 \\ 10i_2 + 5 - 5i_1 &= 0 \\ \mathbf{-5i_1 + 10i_2 = -5} \quad (2) \end{aligned}$$

$$(1) + (2)$$

$$\begin{aligned} 5i_1 + 5i_2 &= 0 \\ \mathbf{-5i_1 + 10i_2 = -5} \end{aligned}$$

$$15i_2 = -5$$

$$i_2 = \mathbf{-0.33 \text{ A}}$$

From (1)

$$i_1 = -i_2 = \mathbf{0.33 \text{ A}}$$

$$i_o = i_1 - i_2 = \mathbf{0.66 \text{ A}}$$

$$\begin{aligned} P_d &= -i_1 \times 10i_o \\ &= \mathbf{-(0.33) \times 10 \times 0.66} \\ &= \mathbf{-2.178 \text{ W}} \end{aligned}$$




UNIVERSITEIT VAN PRETORIA
UNIVERSITY OF PRETORIA
YUNIBESITHI YA PRETORIA

Department of Electrical, Electronic and Computer Engineering

59

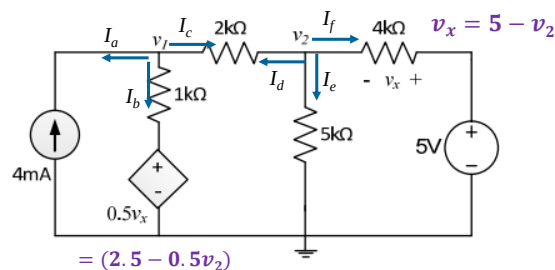2014: Use nodal analysis to set up two equations of the following form: $a v_1 + b v_2 = 13$ $c v_1 - 19 v_2 = d$



KCL@ v_1

$$\begin{aligned} I_a + I_b + I_c &= 0 \\ -4m + \frac{v_1 - 0.5v_x}{1k} + \frac{v_1 - v_2}{2k} &= 0 \\ -8 + 2v_1 - (5 - v_2) + v_1 - v_2 &= 0 \\ \mathbf{3v_1 - 0v_2 = 13} \quad (1) \end{aligned}$$

KCL@ v_2

$$\begin{aligned} I_d + I_e + I_f &= 0 \\ \frac{v_2 - v_1}{2k} + \frac{v_2}{5k} + \frac{v_2 - 5}{4k} &= 0 \\ 10v_2 - 10v_1 + 4v_2 + 5v_2 - 25k &= 0 \\ -10v_1 + 19v_2 &= 25k \\ \mathbf{10v_1 - 19v_2 = -25k} \quad (2) \end{aligned}$$




UNIVERSITEIT VAN PRETORIA
UNIVERSITY OF PRETORIA
YUNIBESITHI YA PRETORIA

Department of Electrical, Electronic and Computer Engineering

60

Calculate i_x and V_x

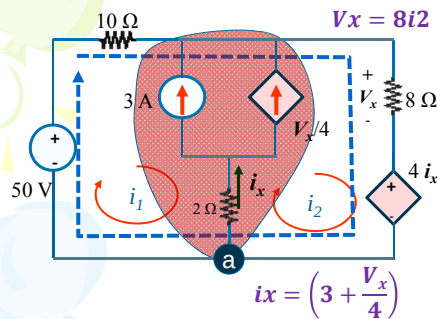

KCL @ common node (a)

$$i_2 = i_1 + i_x$$

$$i_2 = i_1 + \left(3 + \frac{V_x}{4}\right)$$

$$i_2 = i_1 + 3 + \frac{8i_2}{4}$$

$$-i_1 - i_2 = 3 \quad (1)$$

KVL @ Supermesh

$$-50 + 10i_1 + 8i_2 + 4i_x = 0$$

$$10i_1 + 16i_2 = 38 \quad (2)$$

$$(2) + 10(1)$$

$$10i_1 + 16i_2 = 38$$

$$\underline{-10i_1 - 10i_2 = 30}$$

$$6i_2 = 68$$

$$i_2 = 11.38 \text{ A}$$

$$-i_1 - (11.38) = 3 \quad (1)$$

$$i_1 = -14.33 \text{ A}$$

$$V_x = 8i_2 = 8 \times 11.38$$

$$= 90.67 \text{ V}$$

$$i_x = \left(3 + \frac{90.67}{4}\right) = 25.67 \text{ A}$$




UNIVERSITEIT VAN PRETORIA
UNIVERSITY OF PRETORIA
YUNIBESITHI YA PRETORIA

Department of Electrical, Electronic and Computer Engineering

61

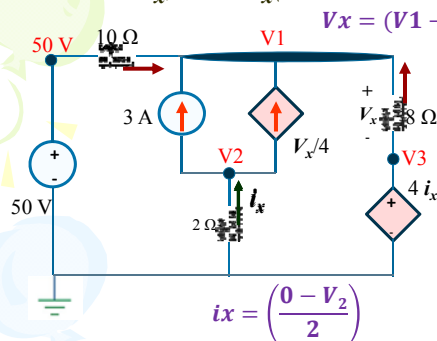Calculate i_x and V_x (use Nodal Analysis)



KVL @ V3

$$V_3 = 4i_x = 4\left(\frac{-V_2}{2}\right)$$

$$2V_2 + V_3 = 0 \quad (3)$$

$$i_x = \left(\frac{-V_2}{2}\right) = \left(\frac{-(-51.33)}{2}\right)$$

$$= 25.67 \text{ A}$$

$$V_x = (V_1 - V_3) = 193.33 - 102.67$$

$$= 90.67 \text{ V}$$

KCL @ V1

$$i_{10\Omega} + 3 + \left(\frac{V_x}{4}\right) + i_{8\Omega} = 0$$

$$\frac{50 - V_1}{10} + 3 + \frac{V_1 - V_3}{4} + \frac{V_3 - V_1}{8} = 0$$

$$2V_1 - 10V_3 = -640 \quad (1)$$

KCL @ V2

$$i_x = 3 + \left(\frac{V_x}{4}\right)$$

$$\frac{0 - V_2}{2} = 3 + \frac{V_1 - V_3}{4}$$

$$-V_1 - 2V_2 + V_3 = 12 \quad (2)$$

Solve

$$V_1 = 193.33 \text{ V}$$

$$V_2 = -51.33 \text{ V}$$

$$V_3 = 102.67 \text{ V}$$



UNIVERSITEIT VAN PRETORIA
UNIVERSITY OF PRETORIA
YUNIBESITHI YA PRETORIA

Department of Electrical, Electronic and Computer Engineering

62

L#7:

3.9 Transistor Circuits

BJT = Bipolar Junction Transistor

Collector = C

Base B

Emitter = E

npn transistor

Voltage

KVL: $V_{CE} = V_{CB} + V_{BE}$
 $V_{BE} = 0.7 \text{ V}$

Currents

KCL: $I_E = I_C + I_B$


UNIVERSITEIT VAN PRETORIA
 UNIVERSITY OF PRETORIA
 YUNIBESITHI YA PRETORIA
 SITHUNYENSI YA PRETORIA

Department of Electrical, Electronic and Computer Engineering

63

3.9 Transistor Circuits

Currents

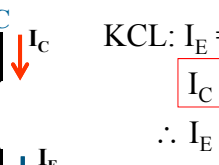


KCL: $I_E = I_C + I_B$

$I_C = \beta I_B$

$\therefore I_E = (1 + \beta) I_B$

β = “Common-emitter current gain”

β ranges between $50 \rightarrow 100$

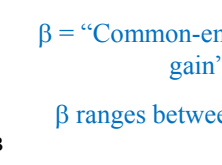


$I_C = \alpha I_E$

α = “Common-base current gain”

α ranges between $0.98 \rightarrow 0.999$

$$\beta = \frac{\alpha}{1 - \alpha}$$

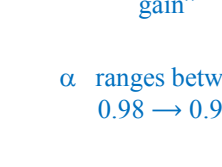

UNIVERSITEIT VAN PRETORIA
UNIVERSITY OF PRETORIA
Pretoria • Learning Matters • Department of Electrical Engineering

Department of Electrical, Electronic and Computer Engineering

64

3.9 Transistor Circuits

Equivalent network model

A transistor is equivalent to a current controlled current source.

How does one analyse a circuit with a transistor in it?

- Method #1: Mesh Analysis**
- Method #2: Node Analysis**
Only applicable if the equivalent network model is used.

UNIVERSITEIT VAN PRETORIA
UNIVERSITY OF PRETORIA
YUNIBESITHI YA PRETORIA

Department of Electrical, Electronic and Computer Engineering

65

PP 3-12 Determine v_o and V_{CE} for the transistor circuit in which $V_{BE} = 0.7$ V and $\beta = 100$. **METHOD #1**

Identify Base, collector & Emitter
Indicate the currents: I_B , I_E and I_C
Use $I_E = (1 + \beta)I_B$ and $I_C = \beta I_B$

Draw the input & output loops
 $v_o = 200 I_E$
 $v_o = 200 (1 + \beta)I_B$ (1)

KVL at outer loop:
 $12 - v_o - V_{CE} - 500 \times I_C = 0$
 $12 - v_o - V_{CE} - 500 \times \beta I_B = 0$ (2)
Solve for I_B from Input loop.

KVL for Input Loop:
 $-5 + 10000 \times I_B + V_{BE} + v_o = 0$
 $-5 + 10000 \times I_B + 0.7 + 200 (1 + \beta)I_B = 0$
 $\therefore I_B = 0.1424 \text{ mA} = 142.4 \mu\text{A}$
 $v_o = 200 (100 + 1) \times 142.4 \mu =$ (1)
 $= 2.87 \text{ V}$


$12 - v_o - V_{CE} - 500 \times \beta I_B = 0$ (2)
 $12 - 2.87 - V_{CE} - 500 \times (100 \times 142.4 \mu) = 0$
 $V_{CE} = 12 - 2.87 - 7.12 = 2 \text{ V}$

UNIVERSITEIT VAN PRETORIA
UNIVERSITY OF PRETORIA
YUNIBESITHI YA PRETORIA

Department of Electrical, Electronic and Computer Engineering

66

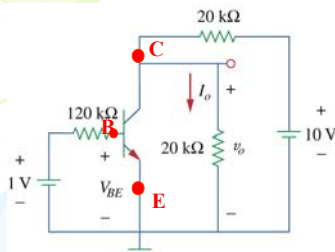PP 3-13 Determine v_o and I_o for the transistor circuit in which $V_{BE} = 0.7\text{ V}$ and $\beta = 80$. – **Node Analysis**



KCL @ Collector (C):

$$I_C + I_o + I_S = 0$$


$$80I_B + \frac{v_o}{20000} + \frac{v_o - 10}{20000} = 0$$

$$20000 \times 80I_B + 2v_o - 10 = 0$$

$$1600k I_B + 2v_o = 10 \quad (1)$$

$$I_B = \frac{1 - V_B}{120k} \quad (2)$$
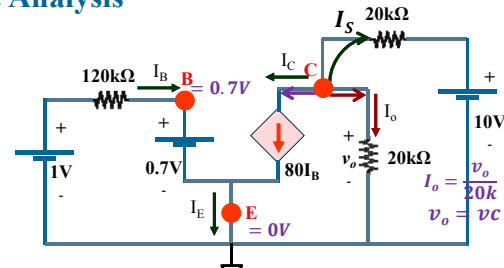
$$I_B = \frac{1 - 0.7}{120k} = 2.5 \mu\text{A}$$



- $V_{BE} = V_B - V_E$
- $V_B = V_{BE} + V_E = 0.7 + 0$
- $V_B = 0.7\text{ V} \quad (3)$

$$1600k \times 2.5 \mu + 2v_o = 10 \quad (1)$$

$$2v_o = 10 - 4$$

$$v_o = 3\text{ V}$$

$$I_o = \frac{v_o}{20k} = \frac{3}{20k} = 150 \mu\text{A}$$




UNIVERSITEIT VAN PRETORIA
UNIVERSITY OF PRETORIA
YUNIBESITHI YA PRETORIA

Department of Electrical, Electronic and Computer Engineering

67

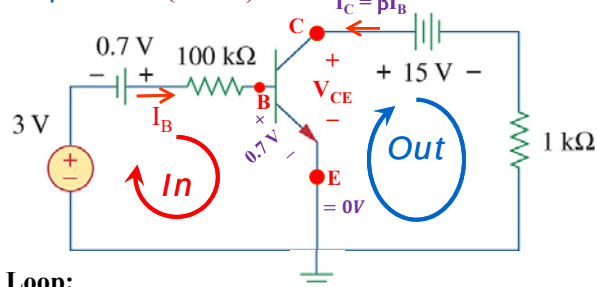Problem 3-89 Determine V_{CE} and I_B for the transistor circuit in which $V_{BE} = 0.7\text{ V}$ and $\beta = 100$. (Mesh)



KVL for Input Loop:

$$-3 - 0.7 + 100k \cdot I_B + 0.7 = 0$$

$$I_B = 3 / 100k$$

$$= 30 \mu\text{A}$$

KVL for Output Loop:

$$-V_{CE} + 15 + 1000 \cdot I_{out} = 0$$

$$15 + 1000 \cdot (-I_C) - V_{CE} = 0$$

$$V_{CE} = 15 + 1000 \cdot (-100 \cdot 30 \mu)$$

$$V_{CE} = 15 - 1000 \cdot (100 \cdot 30 \mu)$$

$$= 12\text{ V}$$



UNIVERSITEIT VAN PRETORIA
UNIVERSITY OF PRETORIA
YUNIBESITHI YA PRETORIA

Department of Electrical, Electronic and Computer Engineering

68