

Hoofdstuk 3

Lesing 3.2

①

Recap: → Doelwit: Los op voor V of I .


→ Methode: ① Ω -wet $\Rightarrow V = \pm IR$

② KVL $\Rightarrow \sum V = 0$

③ KCL $\Rightarrow \sum I_{\text{in}} = \sum I_{\text{out}}$

↳ Node analyse.

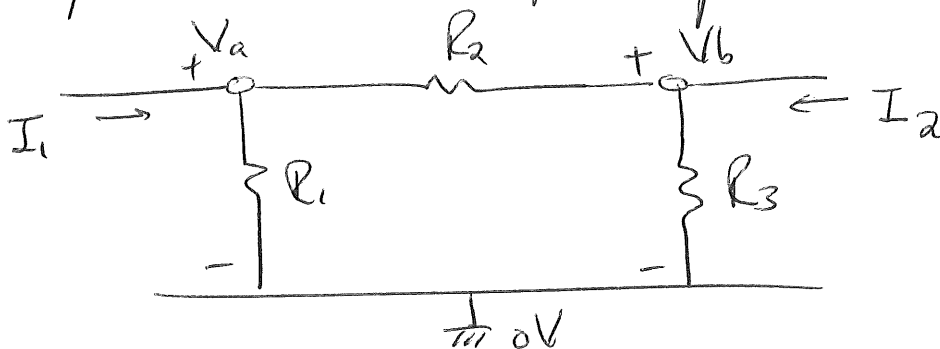* Schryf strome in spanningen en weerstanden.



$$\textcircled{1} \quad I_1 = \frac{V_a}{R_1} + \frac{V_a - V_b}{R_2}$$

$$\textcircled{2} \quad I_2 = \frac{V_b}{R_3} + \frac{V_b - V_a}{R_2}$$

$$i = \frac{V_{\text{FROM}} - V_{\text{TO}}}{R}$$

Stappen:

① Kies 0V.

② Definiceer node-spannings

③ Stel vergelijkingen op.

④ Los op mbw: → Substitutie


→ Cramer se Wkt.

⊕ by node.
⊖ by 0V.

* Supernodusse

(2)

V_b

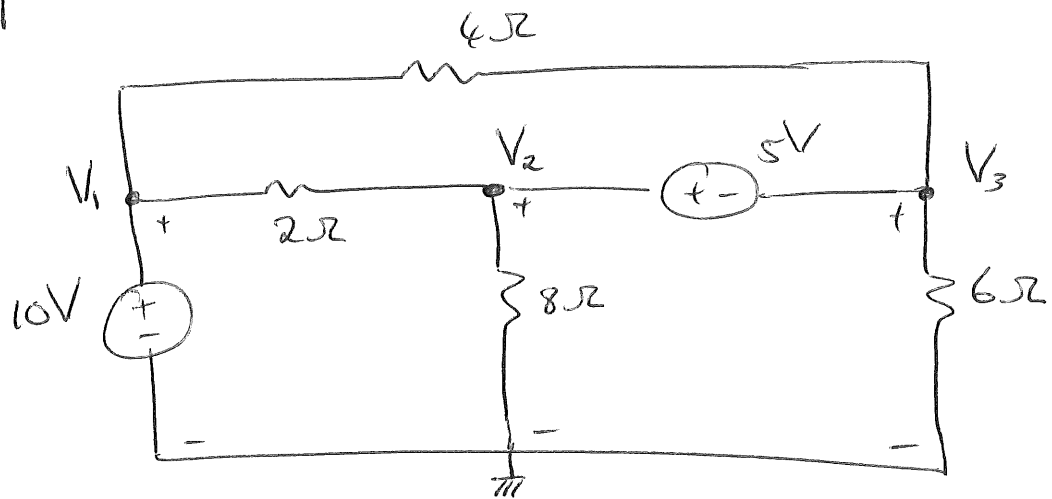

1 → $V_1 = ?$


2 → Hoe word KCL by V_2 en V_3 gedaan?

(Ω -Wet nie van toepassing op)
bronne nie.

Supernodes: • vorm geslote grens rondom
V-bron en enige elemente || tot
bronne

• Geslote grens word nuwe "node."

• KCL:

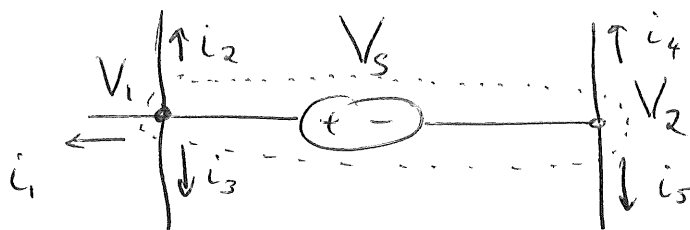

$$i_1 + i_2 + i_3$$

$$+ i_4 + i_5 = 0$$




• KCL word by supernode gedoen.

(3)

• Nog 'n vergelyking word benodig.

(Node analyse son gewoontlik 2 vgl's vir 2 nodusse gee.)

Doen KVL rondom bron in supernode.

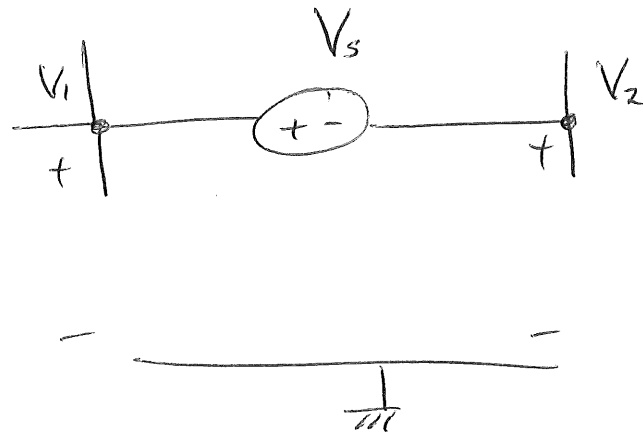

$$-V_1 + V_s + V_2 = 0$$

$$\therefore V_s = V_1 - V_2.$$

* Node-analise se vgl's vir voorbeeld.

① $V_1 = 10V$

KVL: ② $V_s = V_1 - V_2.$


KCL: ③ $\frac{V_2 - V_1}{2\Omega} + \frac{V_2}{8\Omega} + \frac{V_3}{6\Omega} + \frac{V_3 - V_1}{4\Omega} = 0$

V6

$u = ?$

$i = ?$

④

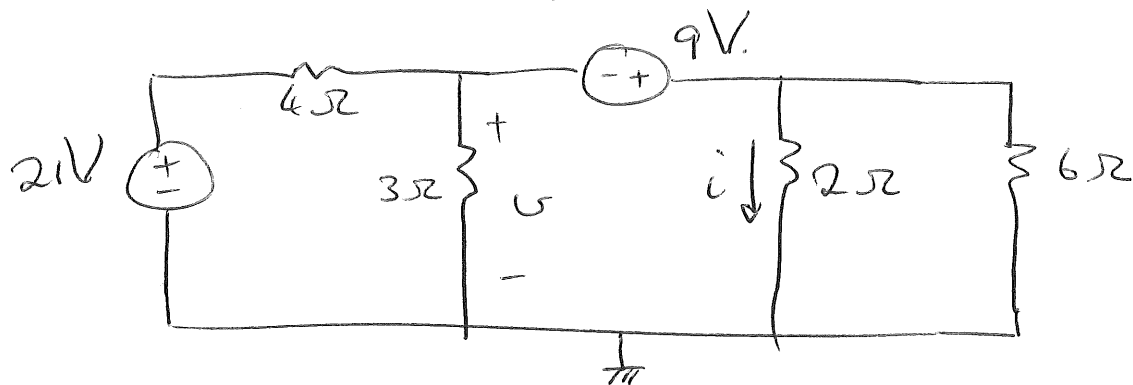

V6

