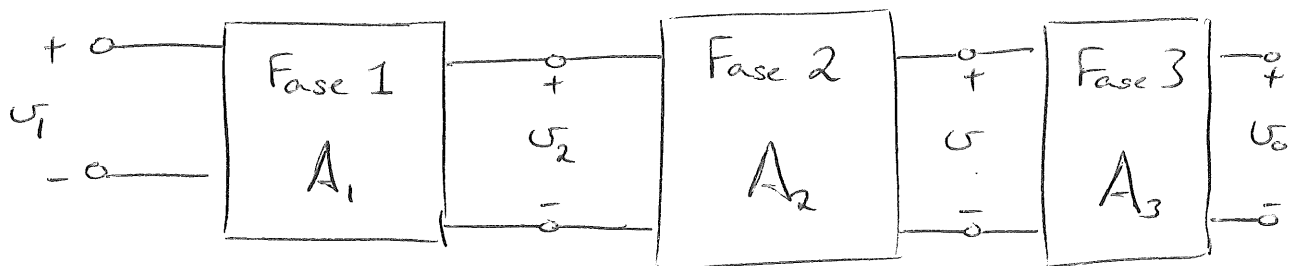


Kringbane en Kaskade.




- * Kop-aan-ster rangstelling van twee of meer versterker kringbane.



$$\begin{aligned} U_0 &= A_3 U_3 \\ &= A_3 (A_2 U_2) \\ &= A_3 \cdot A_2 (A_1 U_1) \\ &= A_3 \cdot A_2 \cdot A_1 \cdot U_1 \end{aligned}$$

Voorbeelde

②

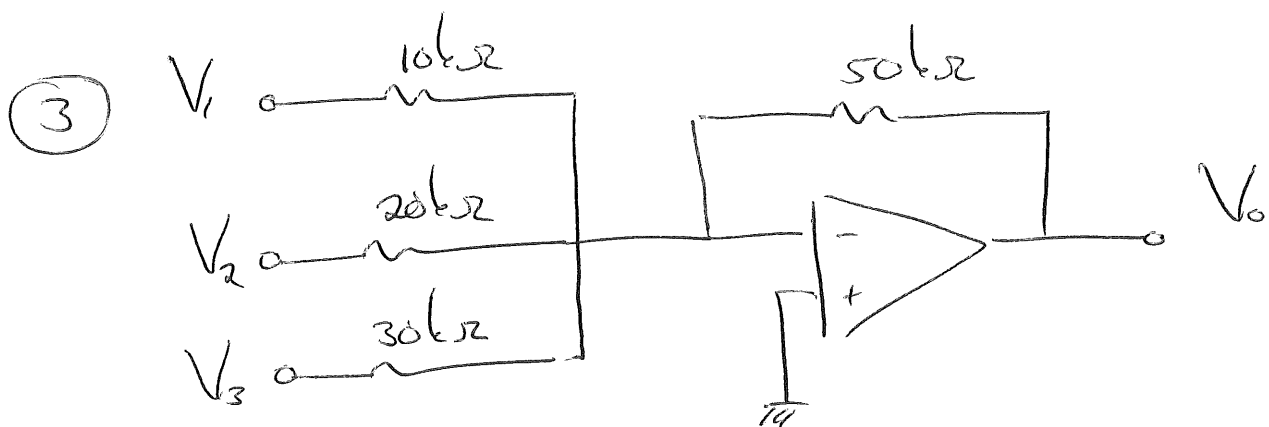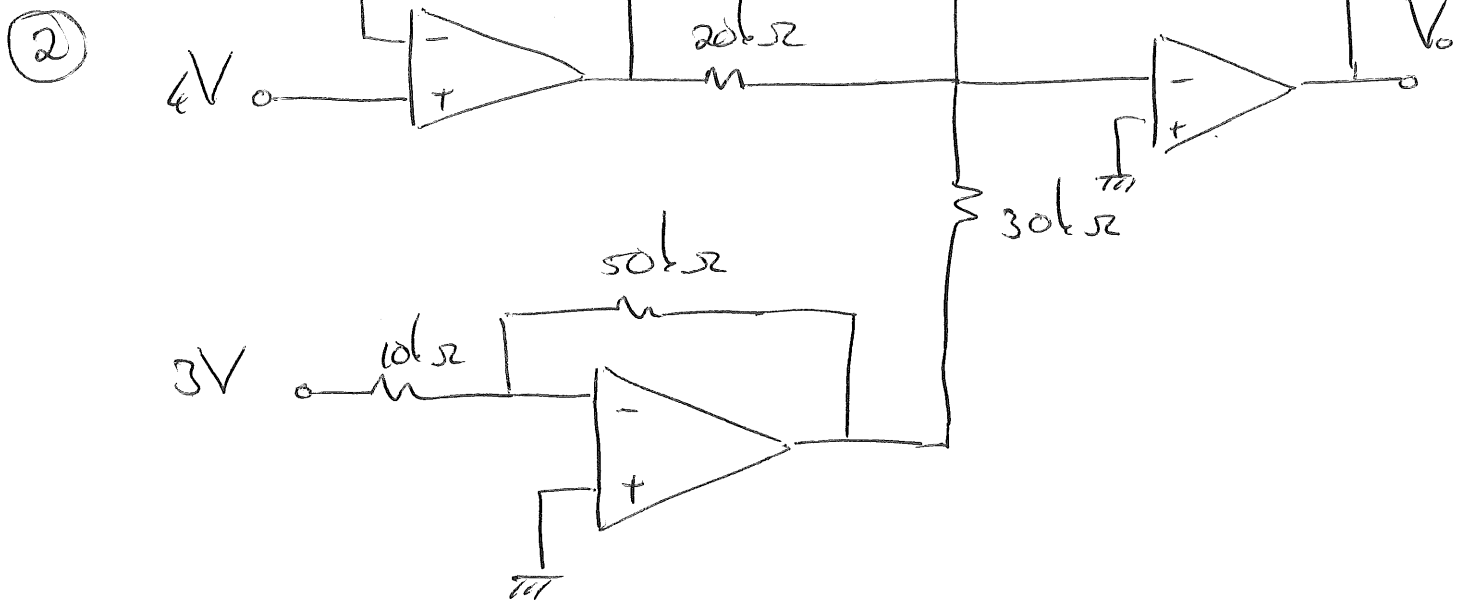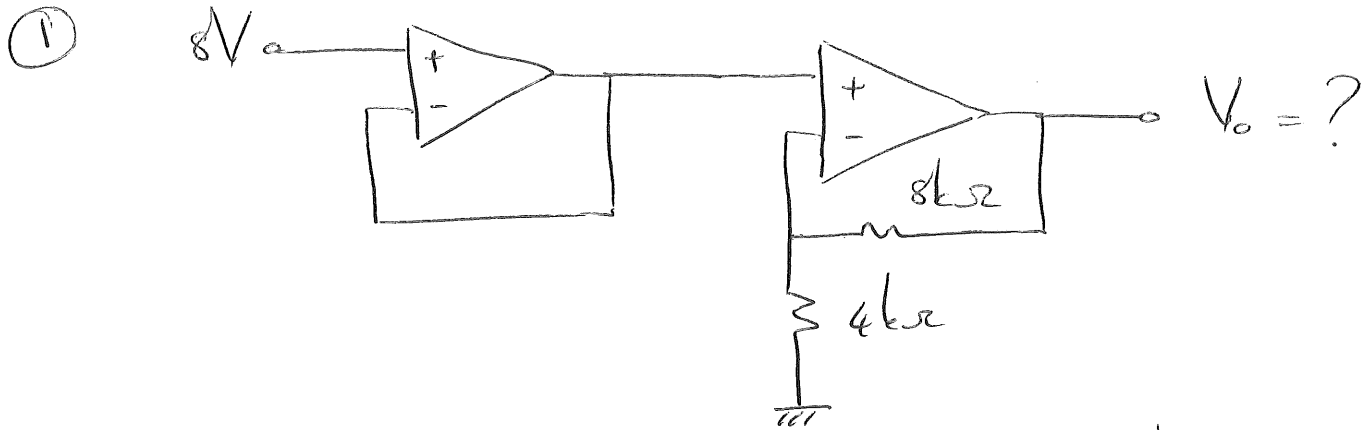

$$V_1 = 2V$$


$$V_3 = -1V$$

$$V_o = -16.5V$$

$$V_2 = ?$$

④

③

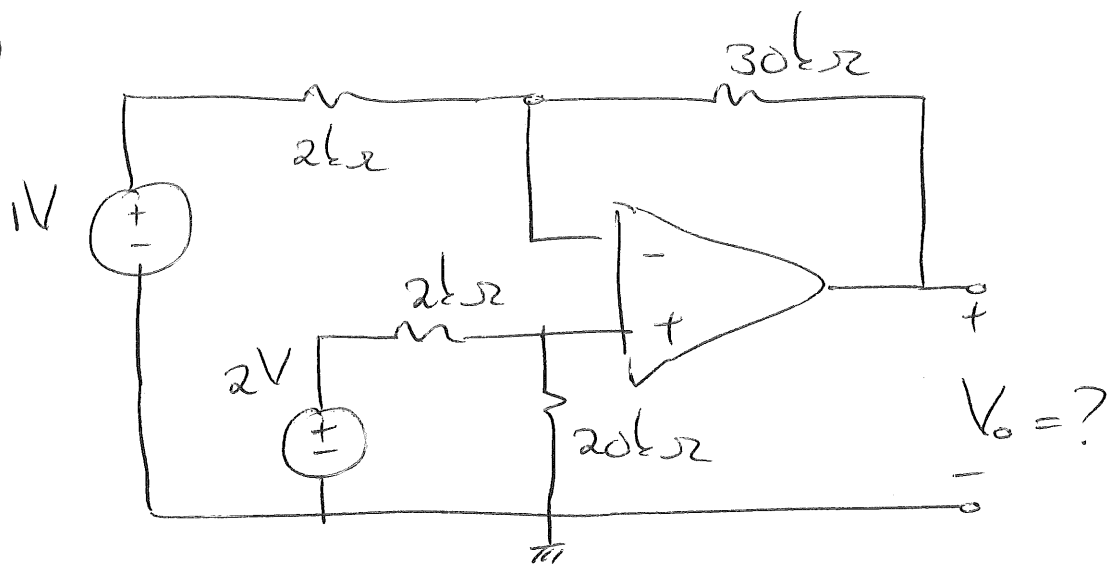

⑤

$V_o/V_s = ?$ inden $R = 20k\Omega$

