
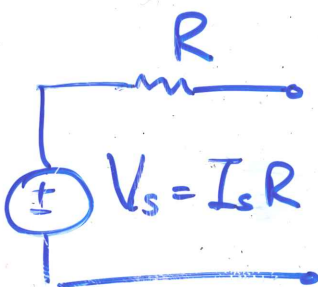
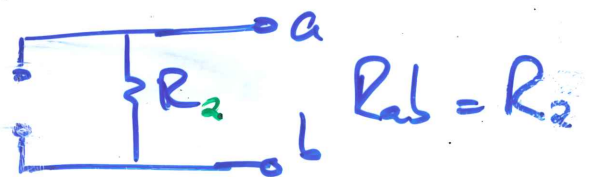
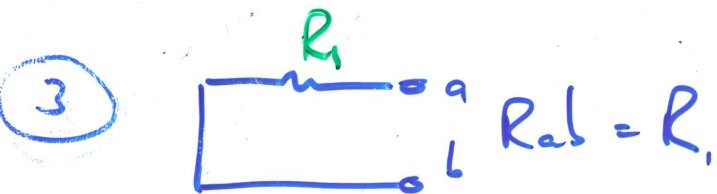
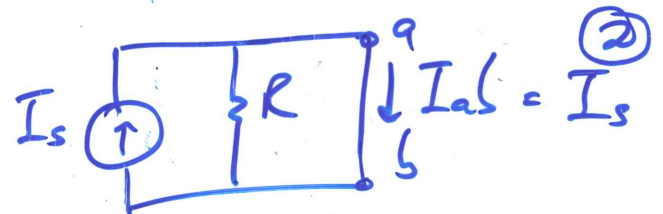
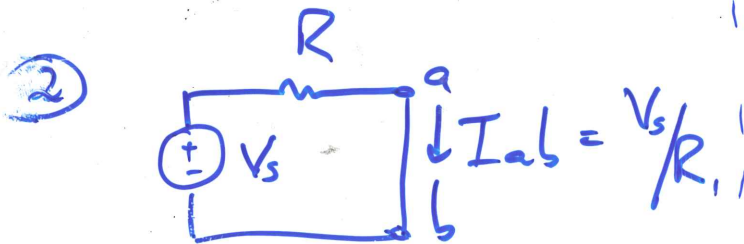
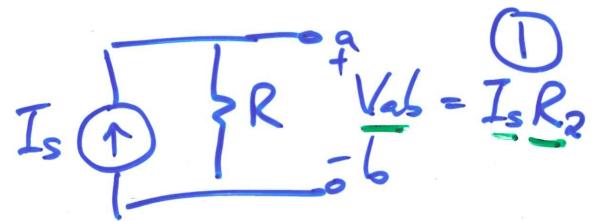
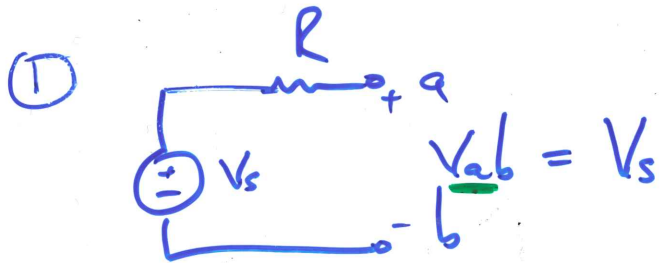
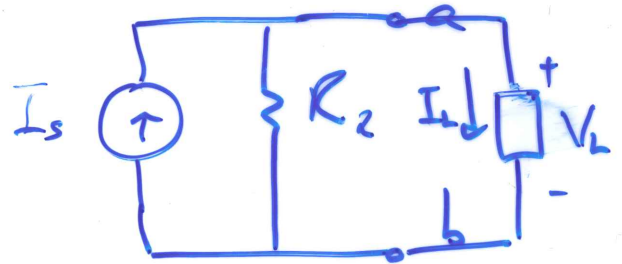


Source Transformation

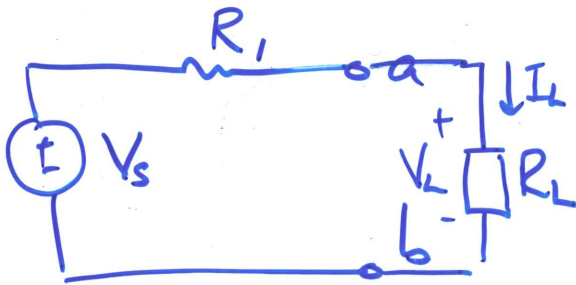
- ① V_{ab} for a-b Open Circuit?
($I_{ab} = 0$)
- ② I_{ab} for a-b Short Circuit?
($V_{ab} = 0$)
- ③ R_{ab} for all sources off?



For equivalence:



* $R_1 = R_2 = R$

* $V_s = I_s R$

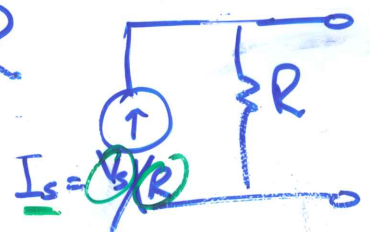

PP 4.7

$(i_x = 7.06 \text{ mA})$

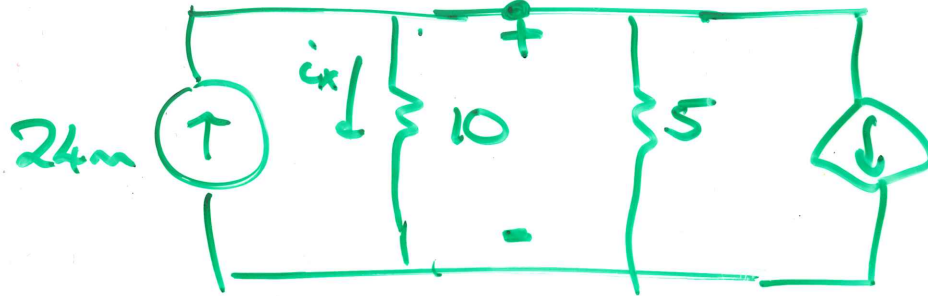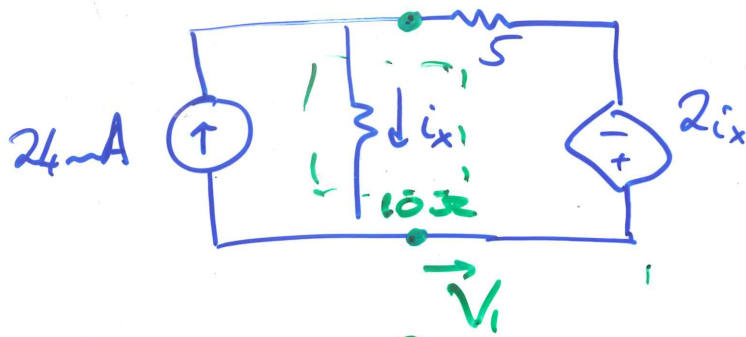

$V_s = 2i_x$
 $I_s = 2i_x/5$

$\rightarrow \sum I_{out} = \sum I_{in}$



① $\frac{V_1}{10} + \frac{V_1}{5} + \frac{2i_x}{5} = 24 \text{ mA}$

② $V_1 = 10 i_x$


$\frac{10 i_x}{10} + \frac{10 i_x}{5} + \frac{2 i_x}{5} = 24 \text{ mA}$

$i_x = ?$

Thevenin / Norton

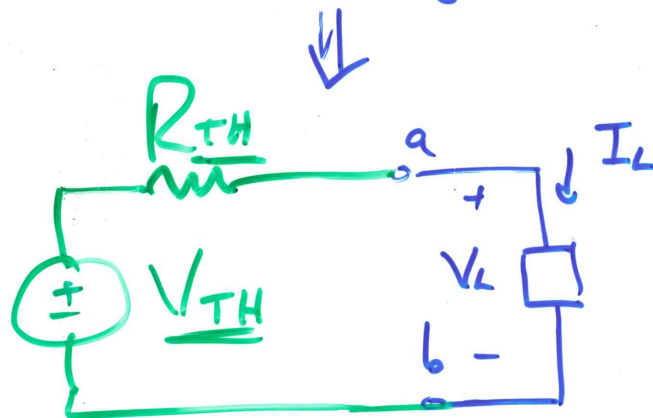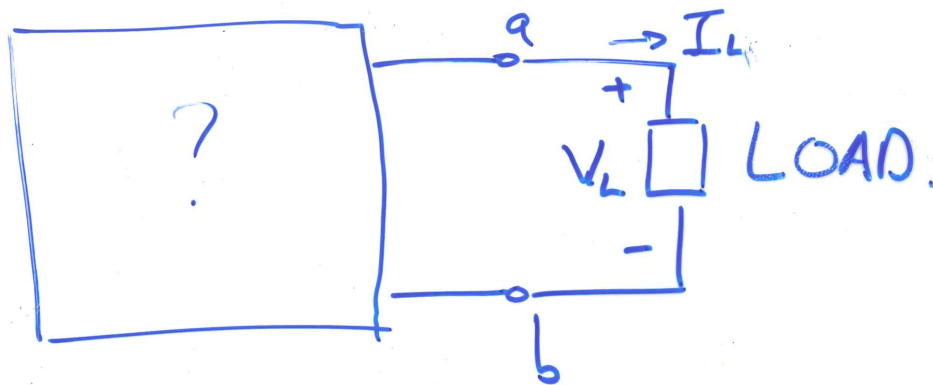


Thevenin equivalent.

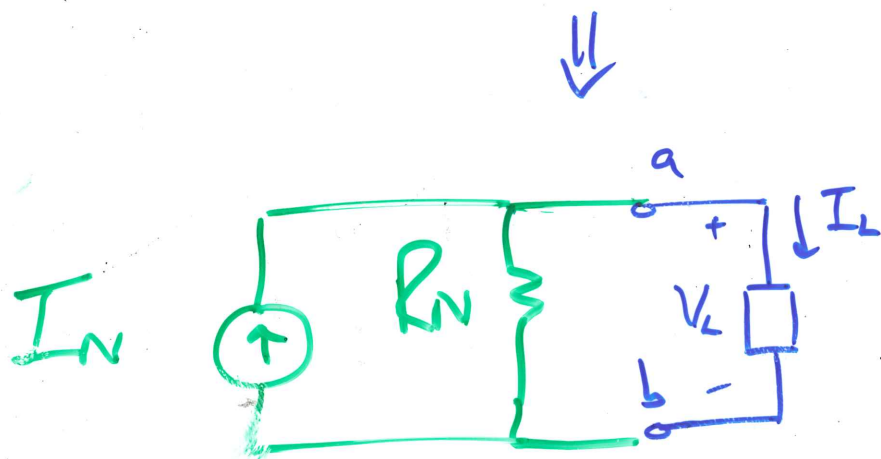


Norton equivalent.


We can replace $\boxed{?}$ with:

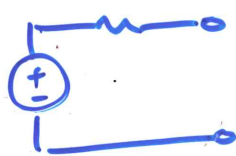

or

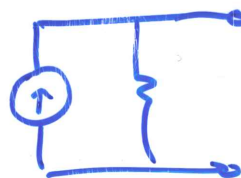

Thevenin:

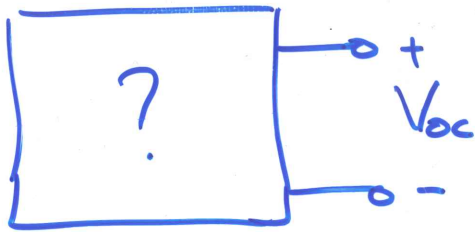

① V_{TH} is open circuit voltage of $\boxed{?}$



② R_{TH} is resistance of $\boxed{?}$ if sources are off.
(Keep  sources on!)

R_{TH}


① No  in circuit

②  is in circuit


* Use series and || theory to simplify circuit to one resistor.

* Simplify series + || if possible.

* Apply test source

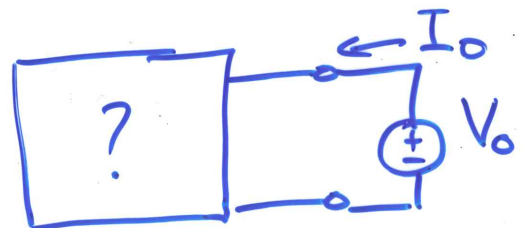

or

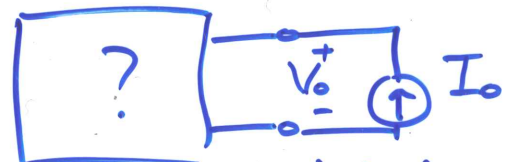


$$\therefore R_{TH} = V_0 / I_0$$





PP 4.8:

a) Determine V_{TH} and R_{TH} for the circuit to the left of a-b.

b) Determine I .


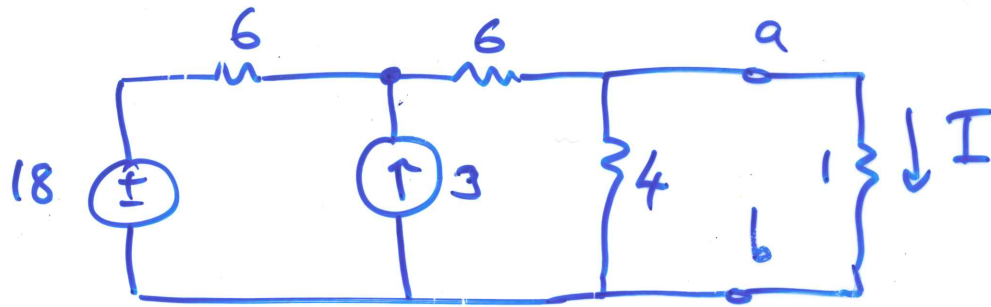


① V_{TH} .

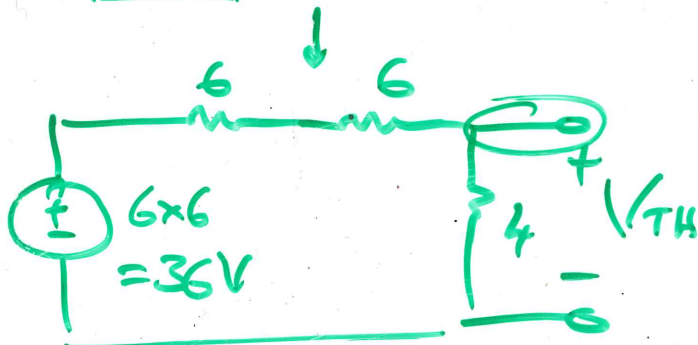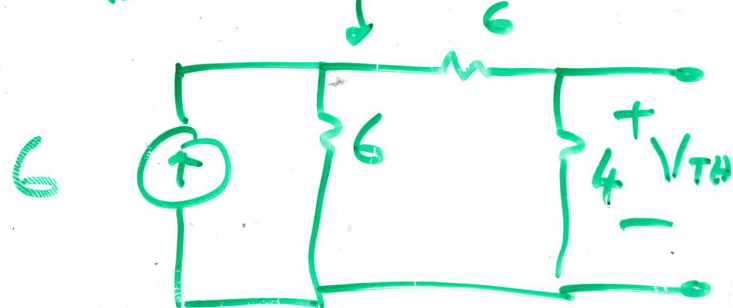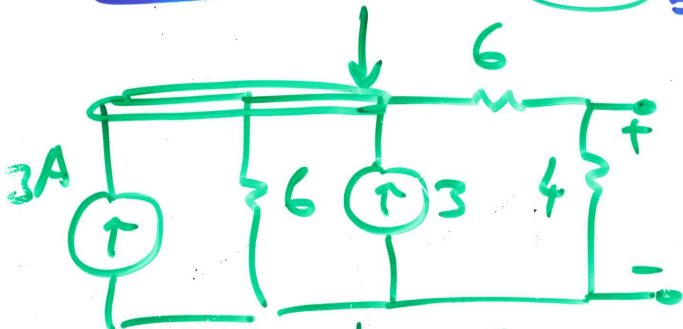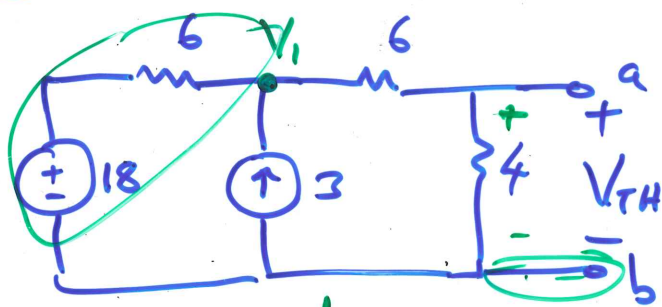


$$V_{TH} = \frac{36 \times 4}{4 + 6 + 6} = \underline{\underline{9V}}$$

② R_{TH}

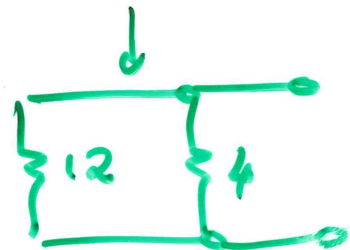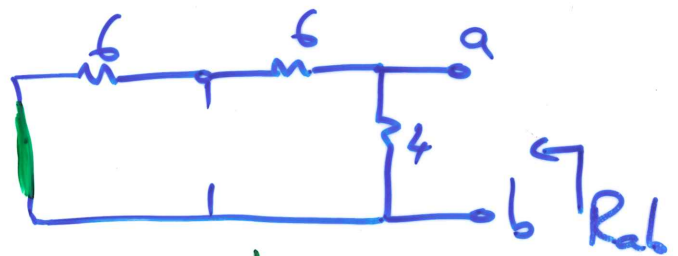


$$R_{TH} = 12 || 4$$


$$R_{TH} = \frac{12 \times 4}{16} = \underline{\underline{3\Omega}}$$

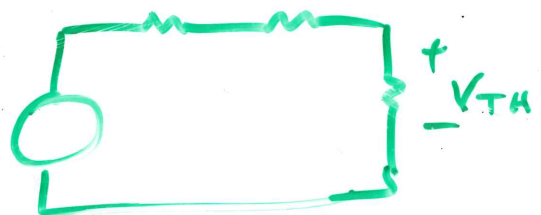


PP 4-9

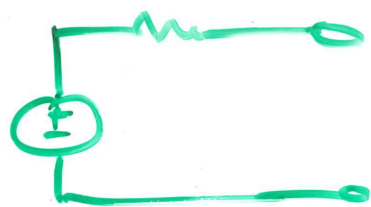

① V_{TH}

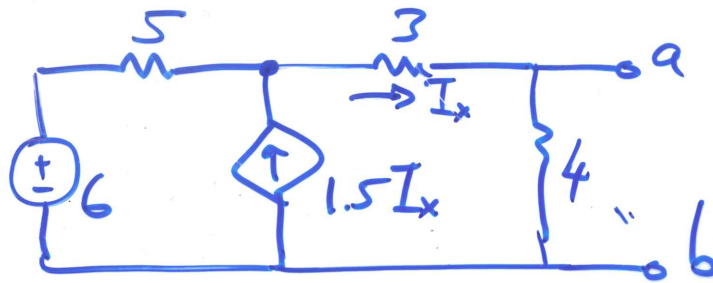

Find Theo
equivalent
circuit.

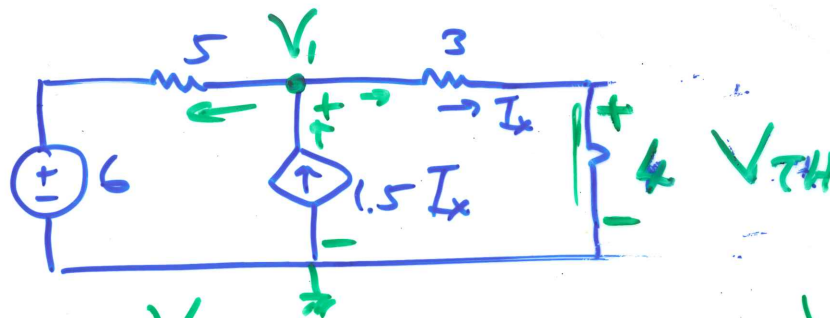

$$* I_x = \frac{V_1}{3+4}$$


$$* V_{TH} = \frac{V_1 \times 4}{3+4} = \underline{5.3V}$$

$$* \frac{V_1 - 6}{5} + \frac{V_1 - 0}{7} = 1.5 \underline{I_x}$$


$$\frac{V_1}{5} - \frac{6}{5} + \frac{V_1}{7} = \frac{3}{2} \left(\frac{V_1}{7} \right)$$

$$V_1 = \underline{9.3V}$$

② R_{TH}

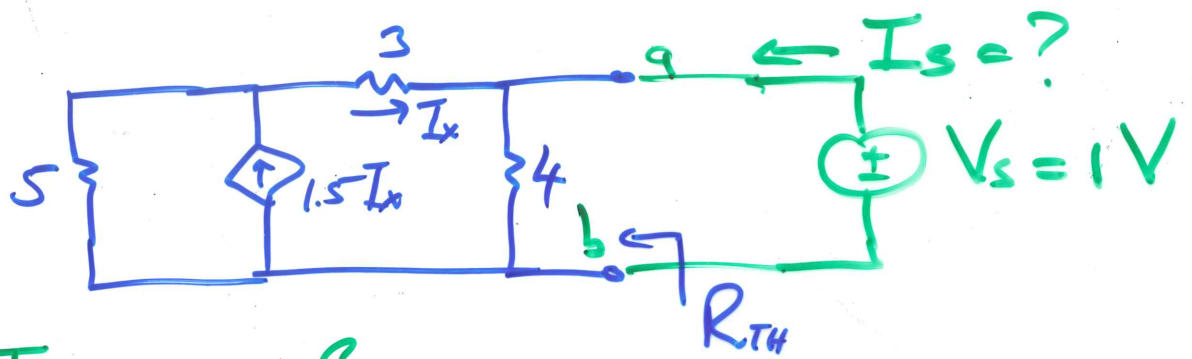


Test Source.

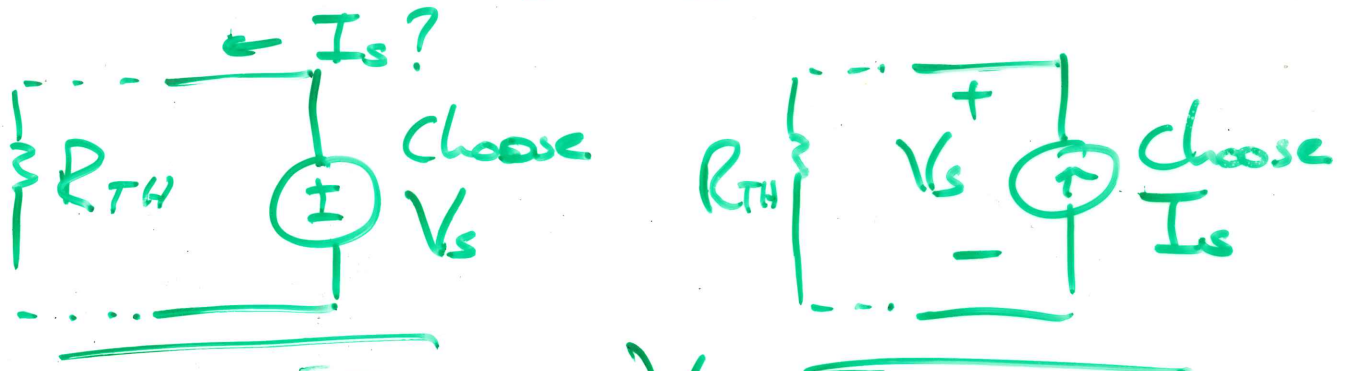

$$R = \frac{V_s}{I_s}$$

* Test Source: $V_s = 1V$ $I_s = ?$

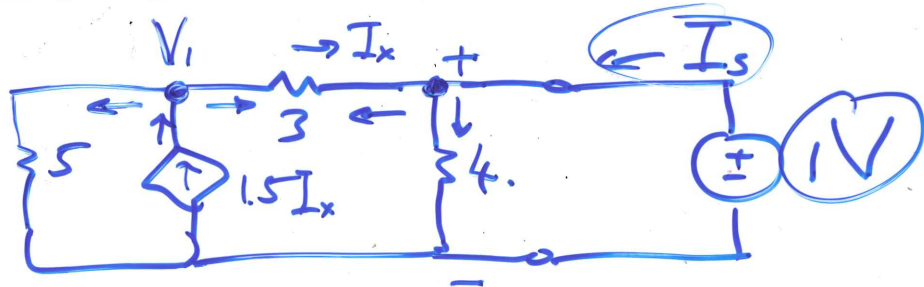

$$\frac{V_1}{5} + \frac{V_1 - 1}{3} = 1.5 I_x \quad (1)$$

$$I_x = \frac{V_1 - 1}{3} \quad (2)$$

$$V_1 = -5V \text{ (from (1) and (2))}$$

$$I_s = \frac{1}{4} + \frac{1 - V_1}{3}$$

$$I_s = \underline{2.25A}$$

$$\underline{R_{TH}} = V / I_s = 1 / 2.25 = 0.4 \Omega$$

