

Can you read this?

* Recap:

→ Ohm's Law


$$\begin{array}{c} + \quad V_1 \quad - \\ \text{---} m \text{---} \\ \rightarrow i_1 \end{array} \quad V_1 = +i_1 R$$

$$\begin{array}{c} - \quad V_2 \quad + \\ \text{---} m \text{---} \\ \rightarrow i_2 \end{array} \quad V_2 = -i_2 R$$

* Series:

* share same I

* share single node

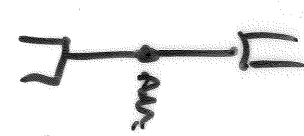
exclusively. 

* $\parallel$: * share same V

* share same two nodes at either ends of the branches.

* KCL: (~~two~~ nodes)


$$\sum I_{IN} = \sum I_{OUT}$$

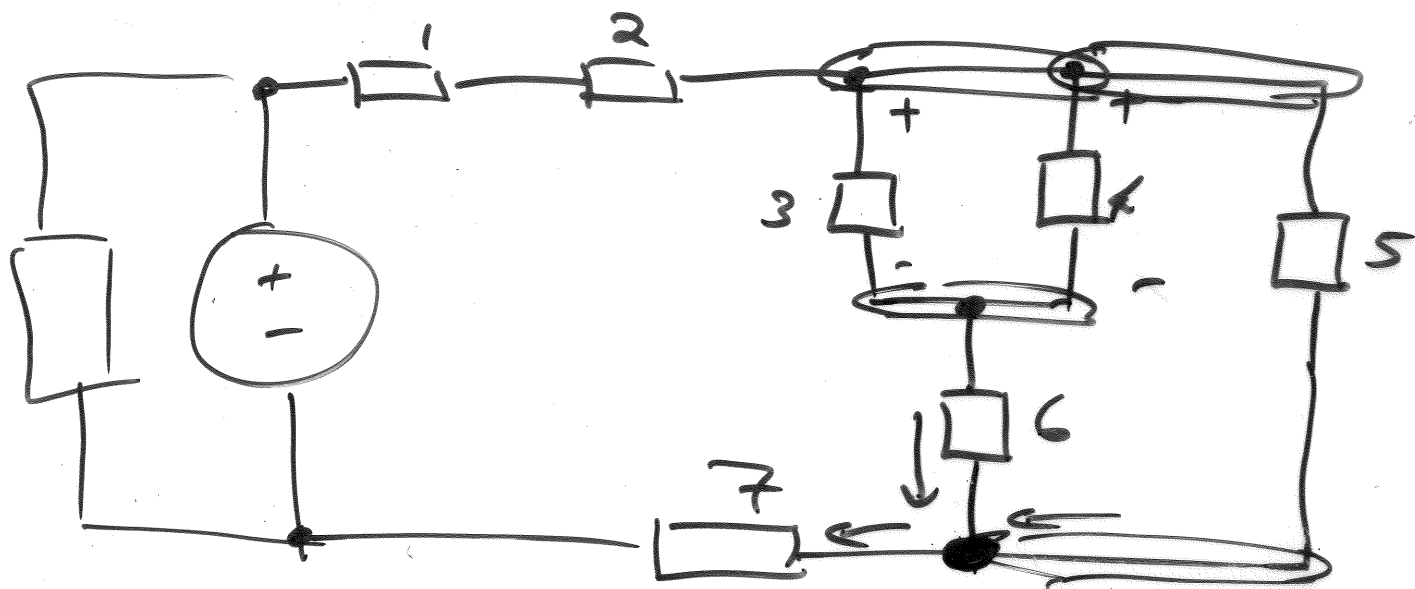


1 series 2.

4 // 5


3 || 4

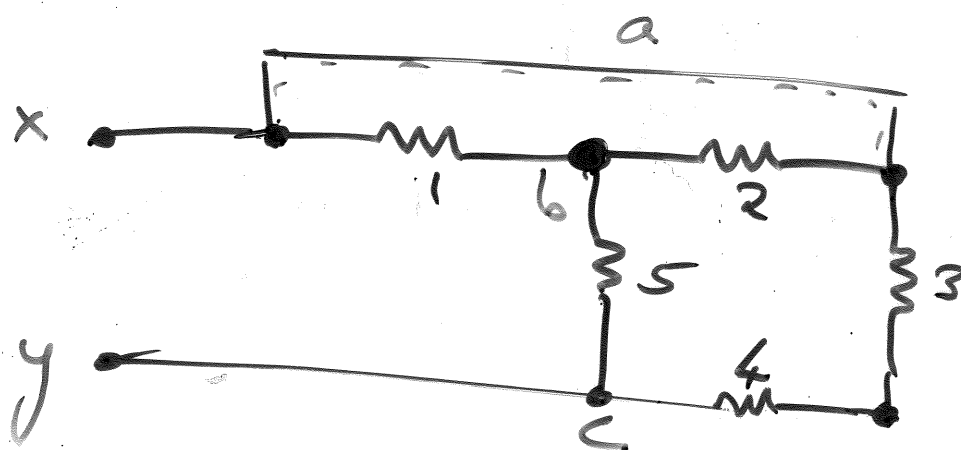


3 s 4
1 || 2

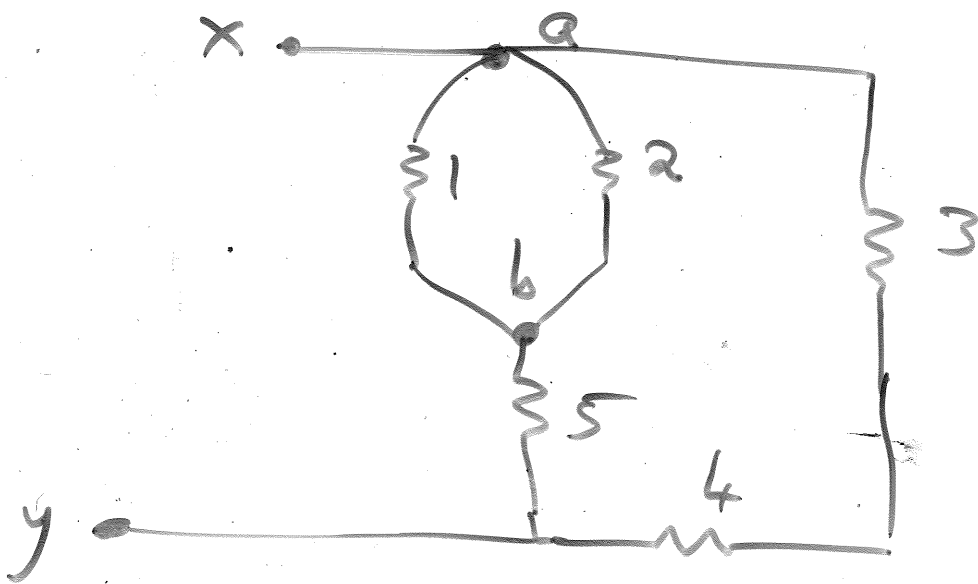


$$\sum I_{IN} = \sum I_{OUT}$$

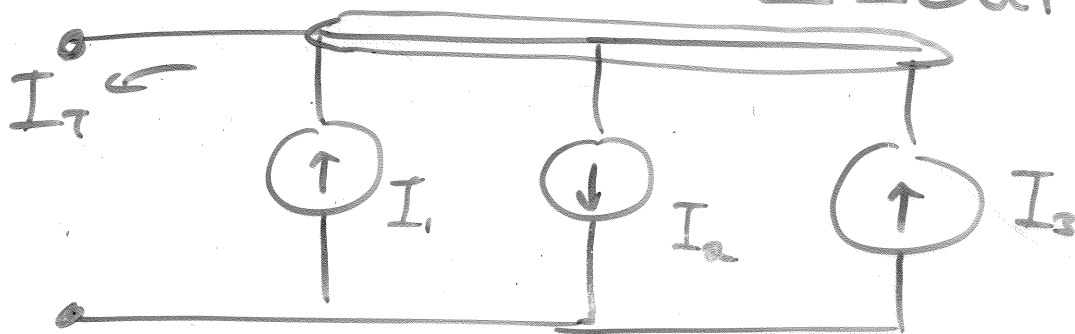

$$I_1 + I_3 = I_T + I_2$$

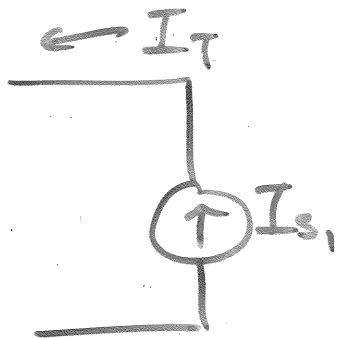


$$I_T = +I_{s1}$$

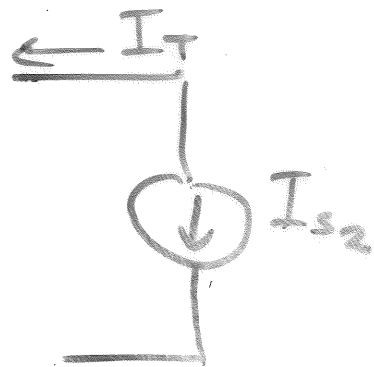


$$I_T = -I_{s2}$$

$$= I_1 + I_3 - I_2$$

$$= I_2 - I_1 - I_3$$

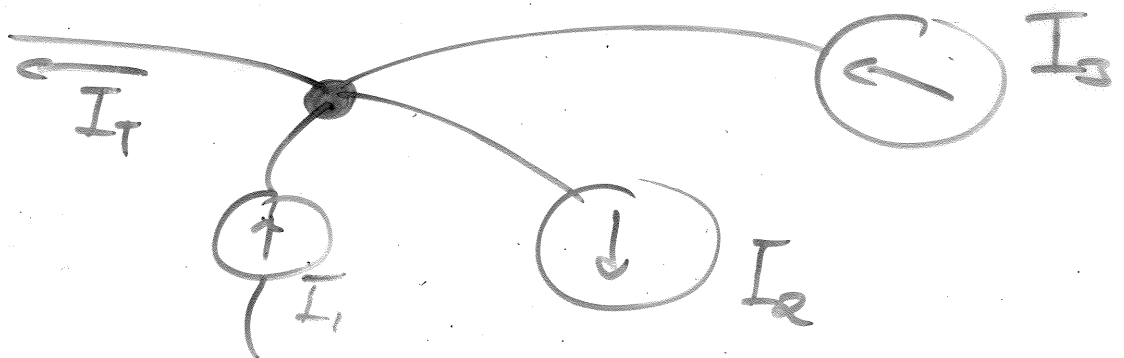


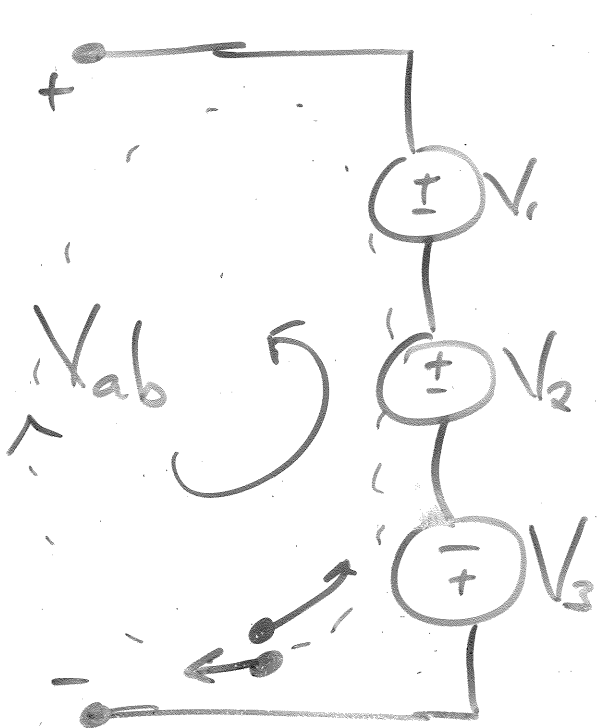


$$\sum V_{\text{LOOP}} = 0$$

$$-V_{ab} + V_1 + V_2 - V_3 = 0$$

$$+V_3 - V_2 - V_1 + V_{ab} = 0$$

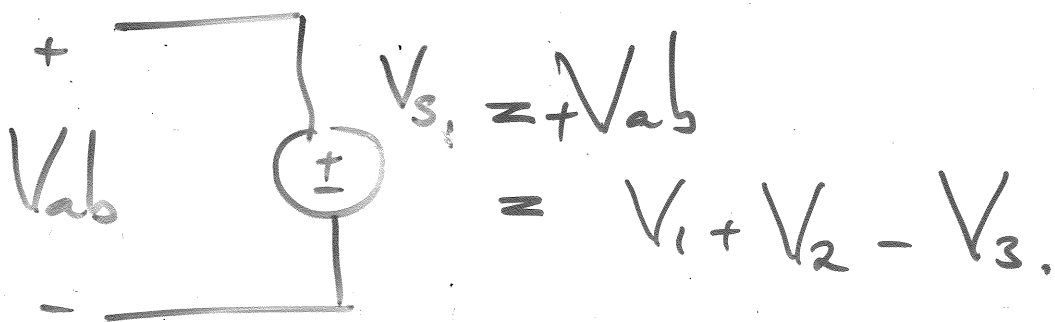

* Series R's & Voltage Div

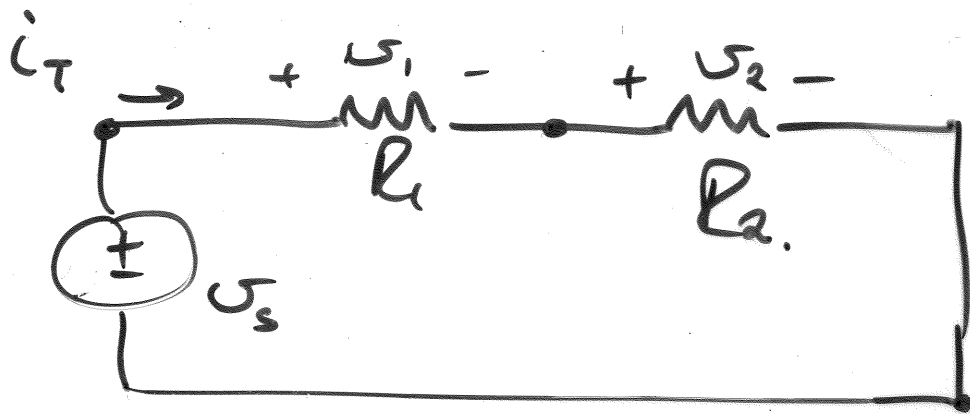

* Ohm: $V_1 = i_T R_1$ $V_2 = i_T R_2$


* KVL: $-V_s + V_1 + V_2 = 0.$

$$V_s = i_T (R_1 + R_2)$$

$$\rightarrow \boxed{i_T = \frac{V_s}{R_1 + R_2}}$$

*
$$V_1 = \frac{V_s R_1}{R_1 + R_2}$$
$$= \frac{V_s R_1}{R_{eq}}$$

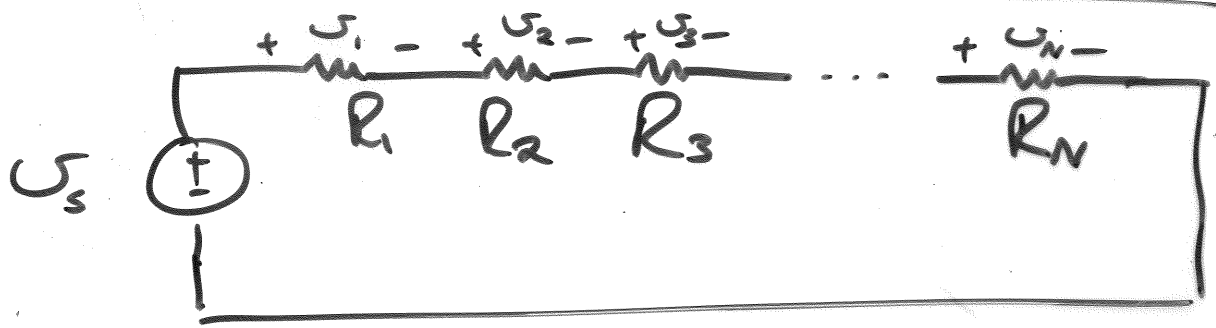
$$V_2 = \frac{V_s R_2}{R_1 + R_2}$$
$$= \frac{V_s R_2}{R_{eq}}$$



$$R_{\text{eq series}} = \sum_{i=1}^N R_i \leftarrow \text{Series R}$$

$$V_3 = \frac{V_s \times R_3}{R_{\text{eq}}} \leftarrow \text{Voltage Division}$$

* Parallel R's & Current Division

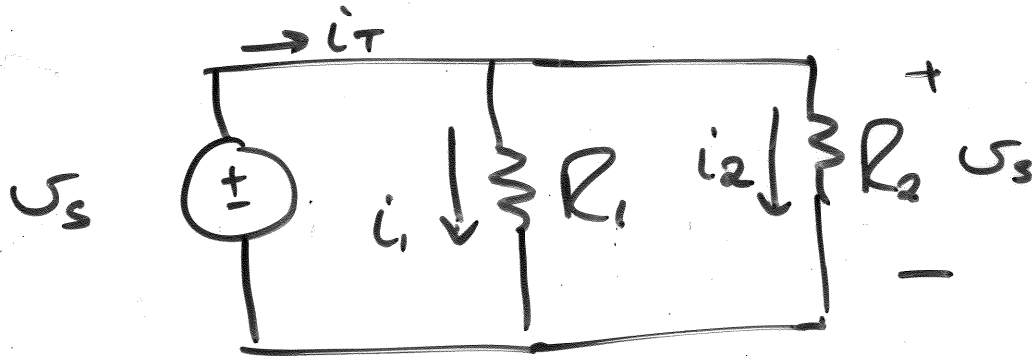

* Ohm's Law:

$$V_s = \underline{i_1} R_1 \quad V_s = \underline{i_2} R_2$$

* KCL: $i_T = i_1 + i_2$

$$i_T = \frac{V_s}{R_1} + \frac{V_s}{R_2} = V_s \left(\frac{1}{R_1} + \frac{1}{R_2} \right)$$


$$\boxed{i = \frac{V}{R}} \Rightarrow i_T = \frac{V_s}{R_{\text{eq}}}$$

$$\Rightarrow \frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$\frac{1}{R_{eq}} = \frac{R_1 + R_2}{R_1 R_2}$$

R_{eq}
(2 R's)

$$R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$$

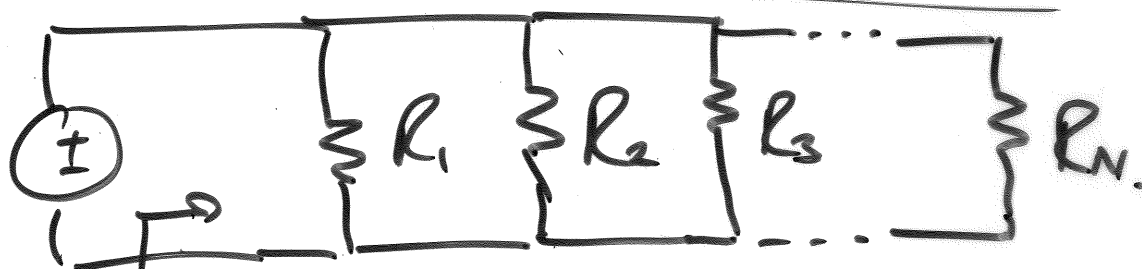


$$R_{eq} = \frac{R_1 \times R_2 \times R_3 \times \dots \times R_N}{\sum R}$$

$$= \left(\frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_N} \right)^{-1}$$

$$+\sum I_N = +\sum I_{out}$$

$$i_T = i_1 + i_2$$

Current

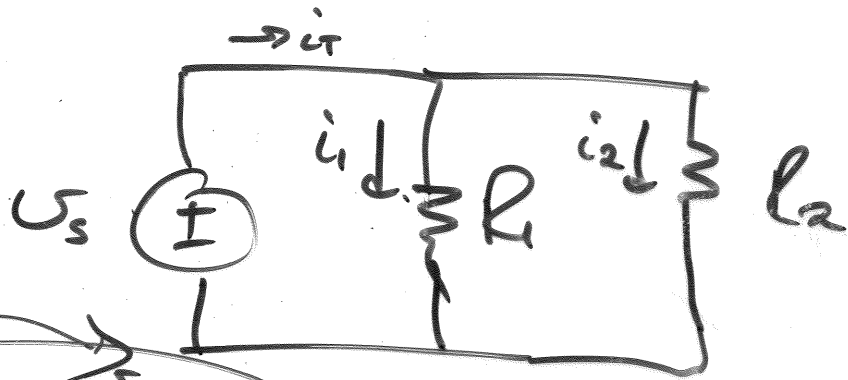

$$i_1 = U_s / R_1$$

$$i_2 = U_s / R_2$$

$$i_T = i_1 + i_2 = U_s / R_{eq}$$

$$i_T = U_s \times \left(\frac{1}{R_1} + \frac{1}{R_2} \right)$$

$$R_{eq} = \left(\frac{1}{R_1} + \frac{1}{R_2} \right)^{-1} = \frac{R_1 R_2}{R_1 + R_2}$$


$$i_T = U_s \times \left(\frac{1}{R_1} + \frac{1}{R_2} \right)$$

$$U_s = i_T / \left(\frac{1}{R_1} + \frac{1}{R_2} \right)$$


$$U_s = \frac{i_T R_1 R_2}{R_1 + R_2}$$

$$i_1 = U_s / R_1 = \frac{i_T R_1 R_2}{R_1 + R_2} / R_1$$

$$\rightarrow \underline{i_1} = \frac{i_T R_2}{R_1 + R_2} \quad | \quad i_2 = \frac{i_T R_1}{R_1 + R_2}$$

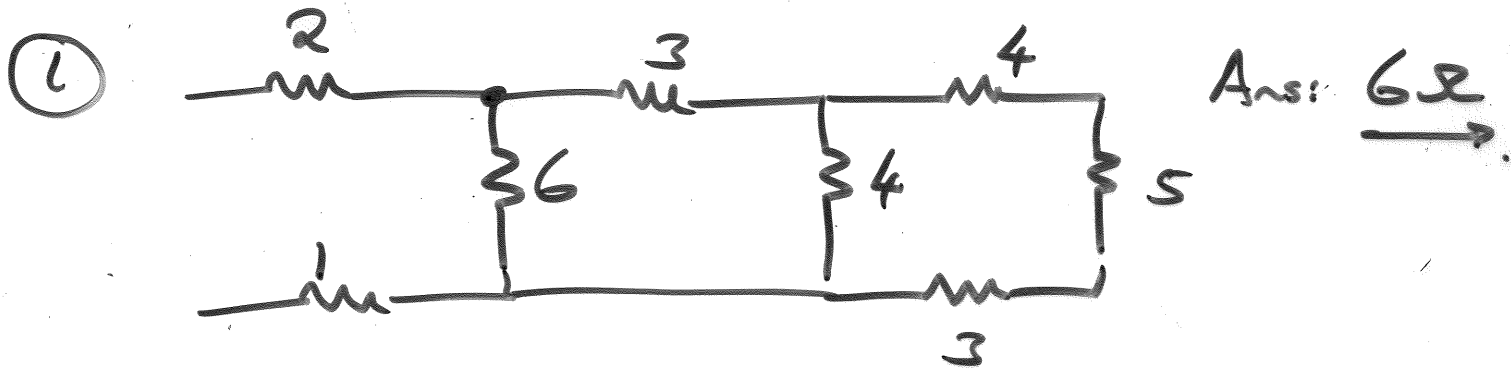

→ $R_{s1} = 4 + 5 + 3 = 12\Omega$

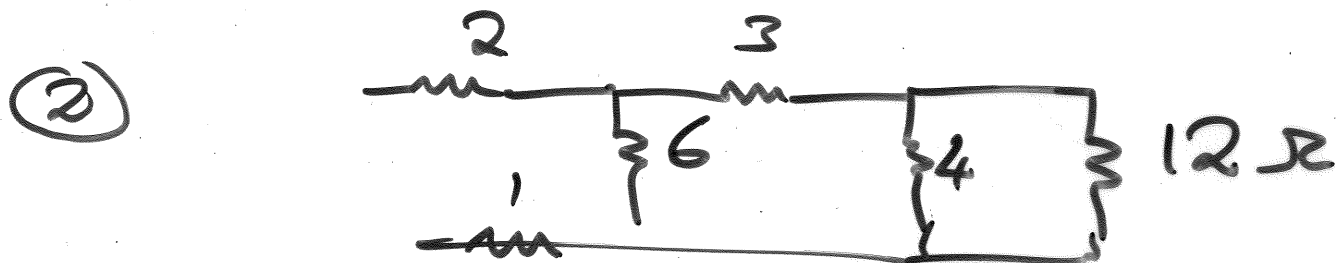

$$R_{u1} = 4 \parallel 12 = \left(\frac{1}{4} + \frac{1}{12} \right)^{-1}$$

$$= \frac{4 \times 12}{4 + 12} = 3\Omega$$




$$R_{s2} = 3 + 3 = 6\Omega$$

$$R_{u2} = R_{s2} \parallel 6 = 6 \parallel 6$$

$$= \frac{6 \times 6}{6 + 6} = 3\Omega$$



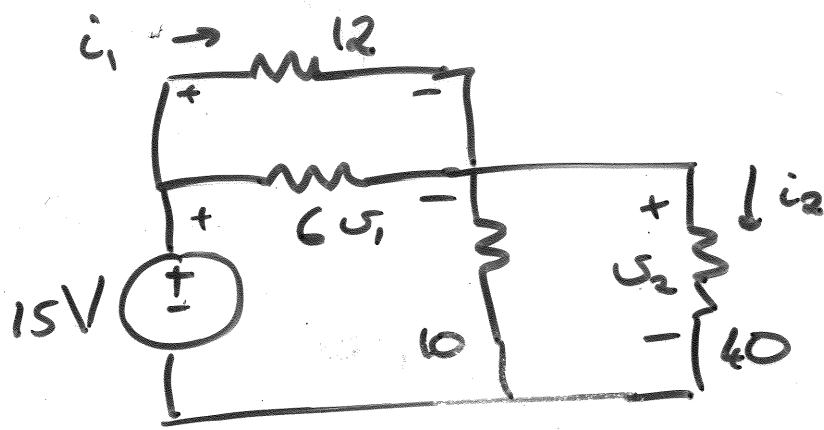


$$\begin{aligned} U_1 &= 5V \\ U_2 &= 10V \end{aligned}$$

* Ohm: $U_2 = i_2 \times 40$
 $U_1 = i_1 \times 12$

* Series & ||.


$$R_{||1} = 12 || 6 = 4\Omega$$

$$R_{||2} = 10 || 40 = 8\Omega$$

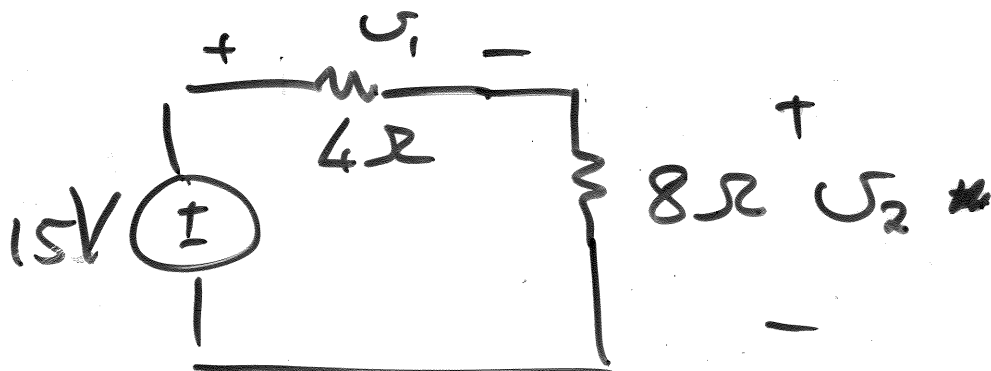

→ Voltage Div:
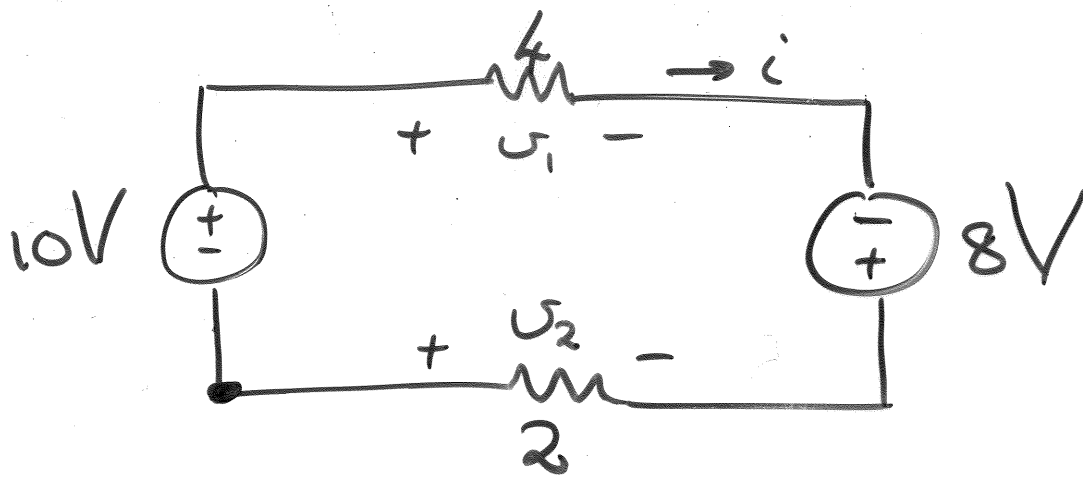
$$\begin{aligned} U_1 &= \frac{15 \times R_1}{R_{eq}} = \frac{15 \times 4}{4 + 8} \\ &= \underline{5V} \end{aligned}$$



* Ohm's Law

$$U_1 = \underline{+4} \times i =$$

$$U_2 = \underline{-2} \times i$$

* KVL:

$$-10 + U_1 - 8 - U_2 = 0$$

$$-10 + 4i - 8 - (-2i) = 0$$


$$-18 + 4i + 2i = 0$$

$$6i = 18$$

$$\underline{i = 3A}$$

$$U_1 = 4 \times 3 = \underline{12V}$$

$$U_2 = -2 \times 3 = \underline{-6V}$$

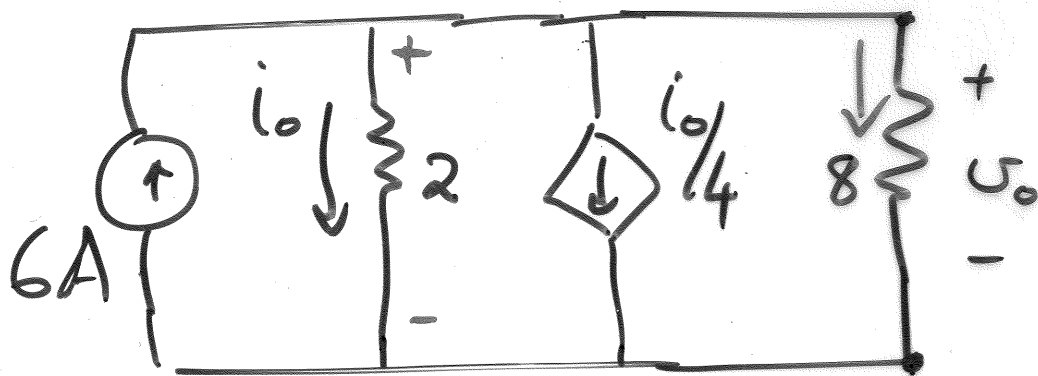

$$b = 4 \quad n = 2 \quad l = 3$$

* Ohm $i_{8\Omega} = +V_o/8$

$$V_o = V_{2\Omega} = i_o \times 2.$$

* KCL: $\sum I_{IN} = \sum I_{OUT}$

$$6 = i_o + \frac{i_o}{4} + i_8$$

~~Subst~~ Subs: $6 = i_o + \frac{i_o}{4} + \frac{V_o}{8}$


$$\rightarrow 6 = i_o + \frac{i_o}{4} + \frac{2i_o}{8}$$

$$6 = i_o + \frac{i_o}{4} + \frac{i_o}{4}$$

$$6 = i_o + \frac{1}{2} i_o$$

$$6 = \frac{3}{2} i_o$$

$$i_o = \underline{4A}$$

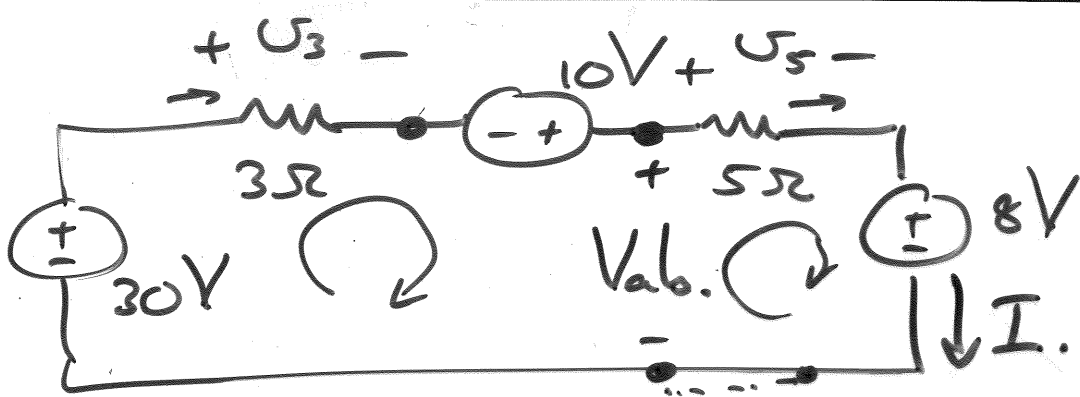

Ohm's Law: $U_3 = +3I$ $U_5 = +5I$.

KVL: $-30 + U_3 - 10 + U_5 + 8 = 0$

$-32 + 3I + 5I = 0$

$I = \underline{4A}$


KVL: $-V_{ab} + U_5 + 8 = 0$

$-V_{ab} + 5 \times 4 + 8 = 0$

$V_{ab} = \underline{28V}$

* KVL:

$$\sum V_{\text{LOOP}} = 0$$

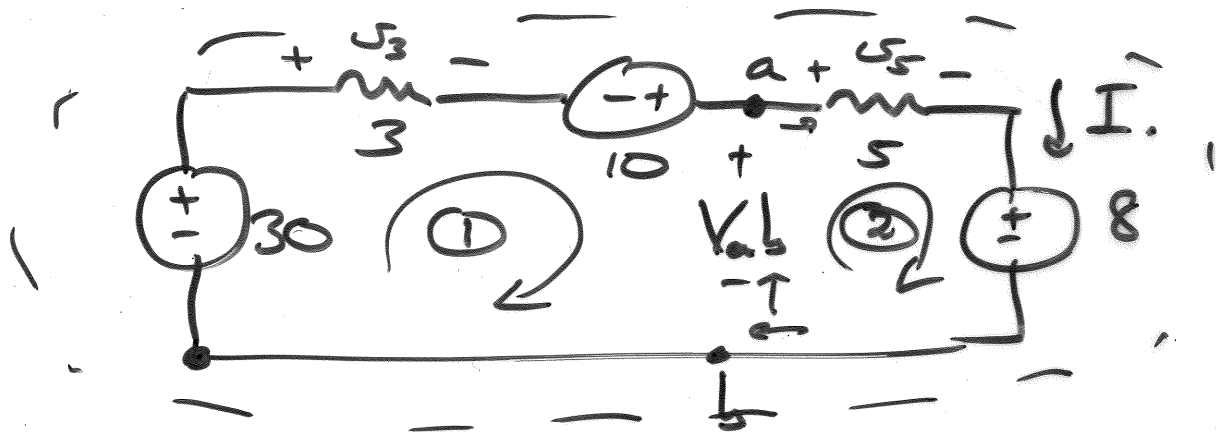

$$U_3 = +3I$$

$$U_5 = +5I$$

① KVL: $-30 + 3I - 10 + V_{ab} = 0$

② KVL: $+5I + 8 - V_{ab} = 0$

③ KVL: $-30 + 3I - 10 + 5I + 8 = 0$

$$I = \underline{4A}$$

$$V_{ab} = \underline{28V}$$