

Departement Elektriese, Elektroniese en
Rekenaar-Ingenieurswese

Department of Electrical, Electronic and
Computer Engineering

Eksamen

Kopiereg voorbehou

Examination

Copyright reserved

Module EBN111
Elektrisiteit en Elektronika
4 Junie 2010

Module EBN111
Electricity and Electronics
4 June 2010



UNIVERSITEIT VAN PRETORIA
UNIVERSITY OF PRETORIA
YUNIBESITHI YA PRETORIA

Eksamensinligting:

Exam information:

Maksimum punte: <i>Maximum marks:</i>	90	Volpunte: <i>Full marks:</i>	90
Duur van vraestel: <i>Duration of paper:</i>	180 minute <i>180 minutes</i>	Oopboek / toeboek: <i>Open / closed book:</i>	Toe <i>Closed</i>
Totale aantal bladsye (hierdie blad ingesluit): <i>Total number of pages (including this page):</i>		31	

BELANGRIK- IMPORTANT

- Die eksamenregulasies van die Universiteit van Pretoria geld.
The examination regulations of the University of Pretoria apply.
- Alle vrae moet op die ANTWOORDBLAD beantwoord word.
All Questions must be answered on the ANSWER SHEET.
- Studente mag hul eie rowwe berekeninge op die vraestel doen – die vraestel word nie ingeneem nie.
Students may do their own rough calculations on the question paper – the question paper will not be taken in.
- Polêre vorm: $A\angle\theta$; Reghoekige vorm: $a + jb$
Polar form: $A\angle\theta$; Rectangular form: $a + jb$

Dosent(e): <i>Lecturer(s):</i>	1 J Joubert
	2 D Bhatt
	3 B Mabuza

Groephoof: Ek bevestig dat die vraestel die uitkomstes toets soos gespesifiseer in die studiehandleiding.
Group head: I confirm that the question paper evaluates the outcomes as specified in the study guide.

Groephoof: <i>Group Head:</i>	Prof J Joubert	Handtekening: <i>Signature:</i>	
----------------------------------	----------------	------------------------------------	--


VRAAG/QUESTION 1 [30]

Vraag 1.1	Question 1.1
'n Klein elektriese voertuig is toegerus met 'n 25 kW elektriese motor. (a) Hoeveel energie (in MJ) word gebruik as die motor volspoed vir 3 ure lank loop. [1] (b) As 'n enkele battery 15 kWh stoorkapasiteit het, hoeveel batterye word benodig om die kar vir 6 ure teen volspoed te laat loop. [1]	A small electric car is fitted with a 25 kW electric motor. (a) How much energy (in MJ) is required for the motor to operate at full speed for 3 hours. [1] (b) If a single battery has a store capacity of 15 kWh, how many batteries are needed for the motor to operate full speed for 6 hours. [1]

Vraag 1.2	Question 1.2
(a) 'n Herlaaibare flitslig is in staat om 60 mA vir omtrent 10 ure lank te voorsien. Hoeveel lading word gelewer in daardie tyd. [1] (b) Die lading wat by die positiewe terminaal van 'n element ingaan is $q = 100 \sin(5t)$ mC, as die spanning oor die element $v = 2 \cos(5t)$ V is. Bepaal die drywing geassosieer met die element by $t = 0.2$ s. [2]	(a) A rechargeable flashlight is capable of delivering 60 mA for about 10 hours. How much charge can it release during that time. [1] (b) The charge entering the positive terminal of an element is given by $q = 100 \sin(5t)$ mC, while the voltage across the element is $v = 2 \cos(5t)$ V. Find the power associated with the element at $t = 0.2$ s. [2]

Vraag 1.3

Question 1.3

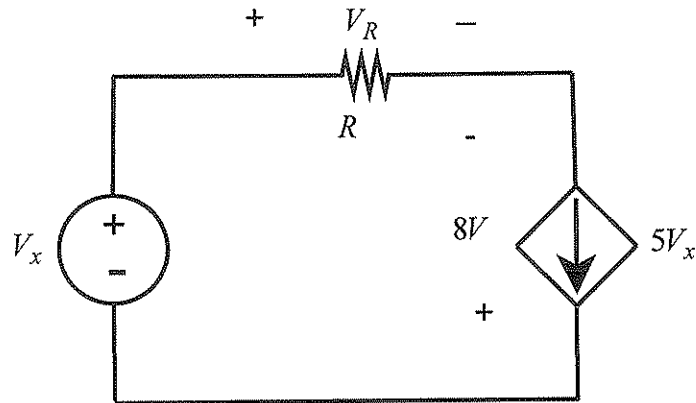

Indien $V_x = 1\text{V}$;


- (a) Bepaal die drywing ge-assosieer met die spanningsbron. [1]
- (b) Bepaal die drywing ge-assosieer met die stroombron. [1]

If $V_x = 1\text{V}$;

- (a) Determine the power associated with the voltage source. [1]
- (b) Determine the power associated with the current source. [1]


Vraag 1.4

Question 1.4

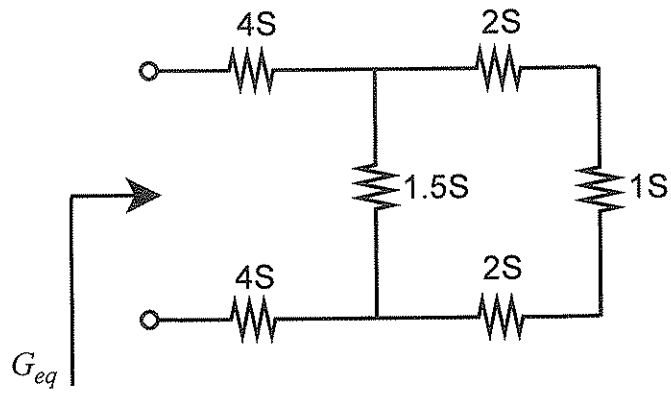


Bepaal G_{eq} . [2]

Determine G_{eq} . [2]

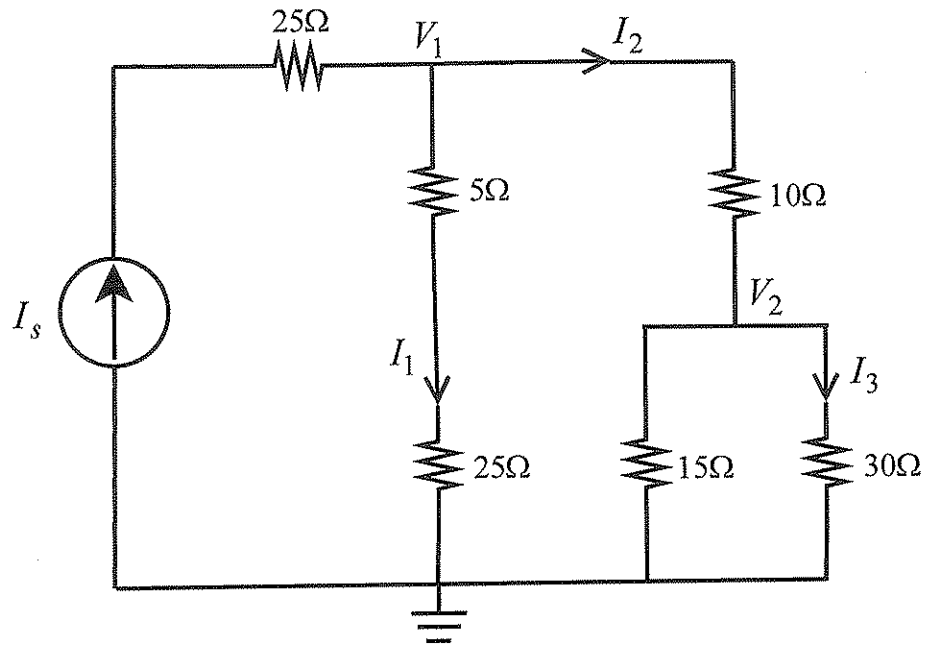

- (a) Bepaal I_3 as $I_2 = 12$ mA. [1]
 (b) Bepaal V_2 as $V_1 = 30$ V. [1]
 (c) Bepaal I_3 as $I_s = 60$ mA. [2]

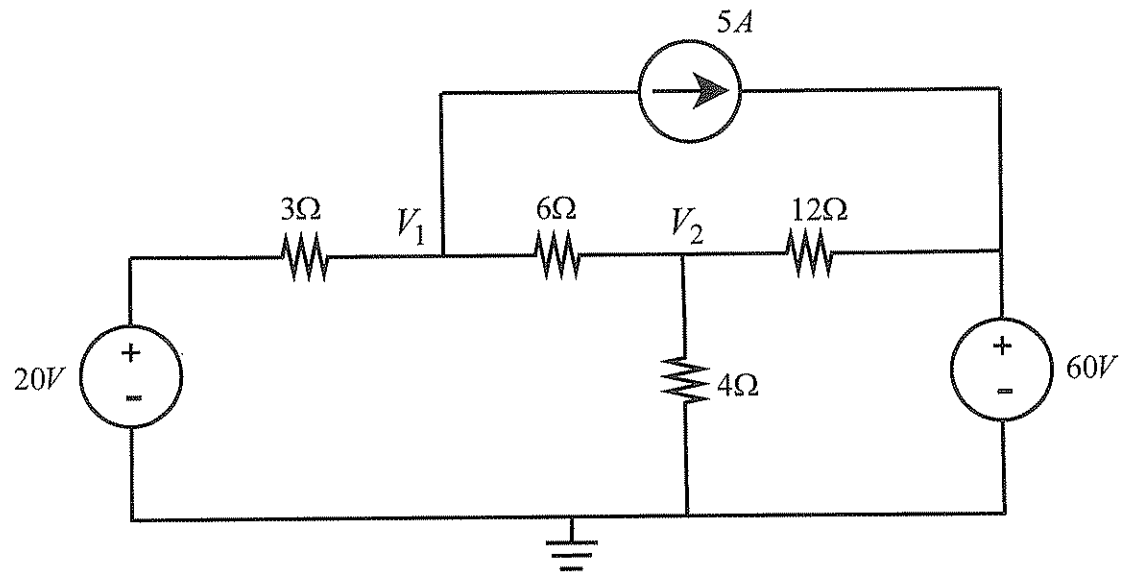- (a) Determine I_3 if $I_2 = 12$ mA. [1]
 (b) Determine V_2 if $V_1 = 30$ V. [1]
 (c) Determine I_3 if $I_s = 60$ mA. [2]




Gebruik node-analise om twee vergelykings van die volgende vorm op te stel:

$$\begin{aligned} aV_1 - V_2 &= b \\ -2V_1 + cV_2 &= d \end{aligned} \quad [4]$$

Use nodal analysis to formulate two equations of the following form:
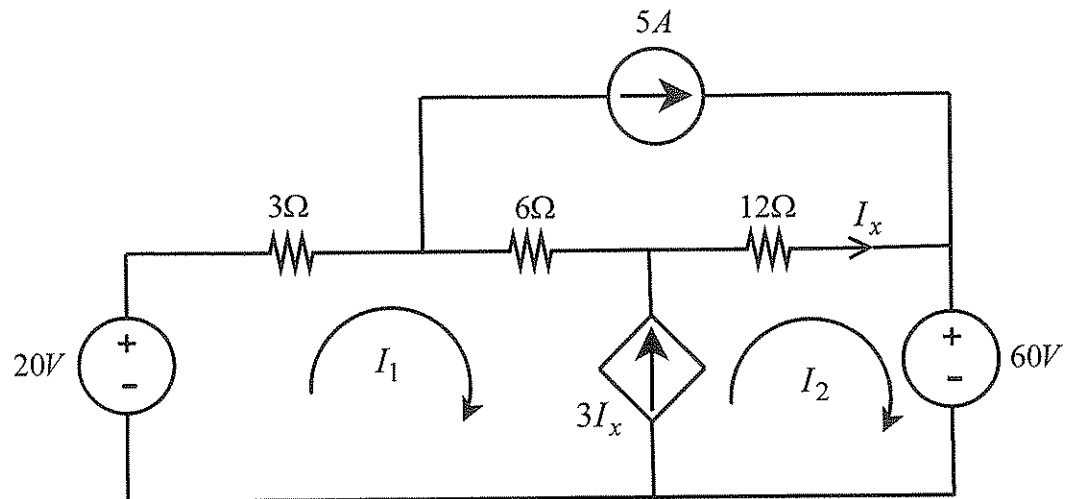
$$\begin{aligned} aV_1 - V_2 &= b \\ -2V_1 + cV_2 &= d \end{aligned} \quad [4]$$




Gebruik lus-analise om twee vergelykings van die volgende vorm op te stel:

$$\begin{aligned} I_1 + eI_2 &= f \\ 9I_1 + gI_2 &= h \end{aligned} \quad [4]$$

Use mesh analysis to formulate two equations of the following form:

$$\begin{aligned} I_1 + eI_2 &= f \\ 9I_1 + gI_2 &= h \end{aligned} \quad [4]$$

Vraag 1.8	Question 1.8
Bepaal die determinant Δ en los die matriksvegelyking op om v_2 te bepaal. [2] $\begin{bmatrix} 2 & 0 & -2 \\ -1 & 3 & 0 \\ 2 & 1 & 0 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \end{bmatrix} = \begin{bmatrix} 5 \\ 0 \\ 10 \end{bmatrix}$	Find the determinant Δ and solve the matrix equation to find v_2. [2] $\begin{bmatrix} 2 & 0 & -2 \\ -1 & 3 & 0 \\ 2 & 1 & 0 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \end{bmatrix} = \begin{bmatrix} 5 \\ 0 \\ 10 \end{bmatrix}$

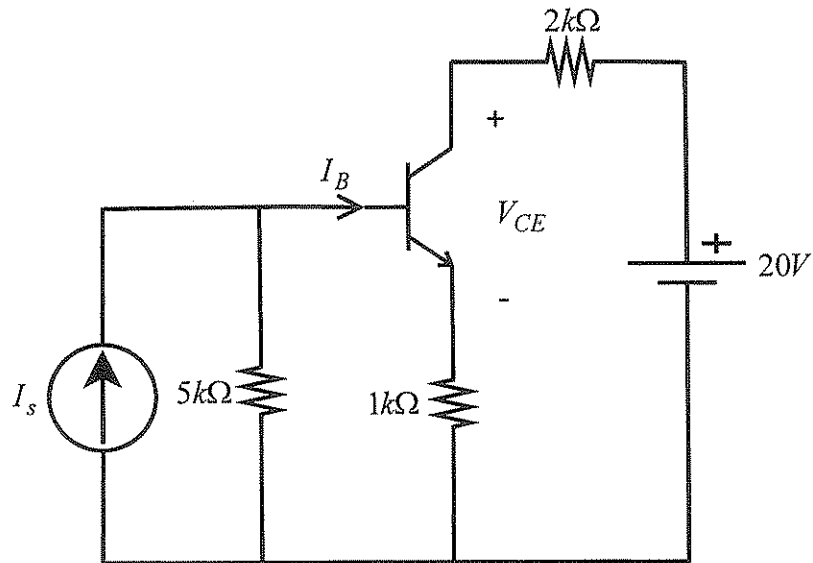


- (a) Bereken I_B (in μA) as $I_s = 1\text{mA}$, $\beta = 100$ en $V_{BE} = 0.7\text{V}$. [2]
 (b) Bereken V_{CE} as $I_B = 25\text{ }\mu\text{A}$, $\beta = 100$ en $V_{BE} = 0.7\text{V}$. [2]

- (a) Calculate I_B (in μA) if $I_s = 1\text{mA}$, $\beta = 100$ and $V_{BE} = 0.7\text{V}$. [2]
 (b) Calculate V_{CE} if $I_B = 25\text{ }\mu\text{A}$, $\beta = 100$ and $V_{BE} = 0.7\text{V}$. [2]

Vraag 1.10

Question 1.10

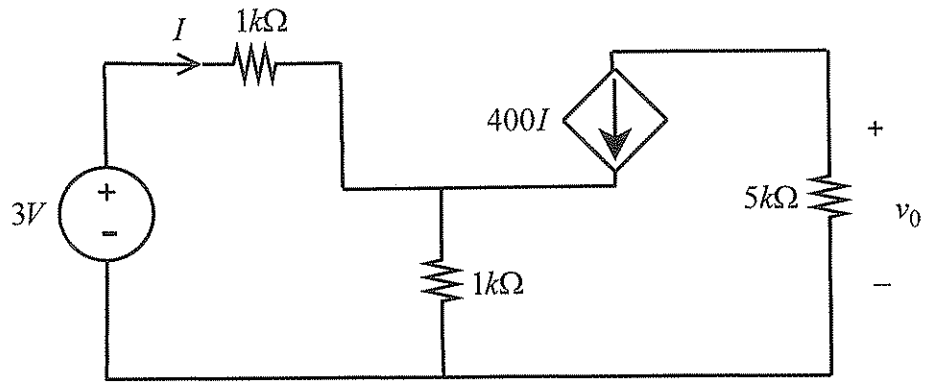


Bereken I en v_0 in die vereenvoudigde transistor-baan.
[3]

Calculate I and v_0 in the simplified transistor circuit. [3]

VRAAG/QUESTION 2 [25]


Vraag 2.1

Question 2.1

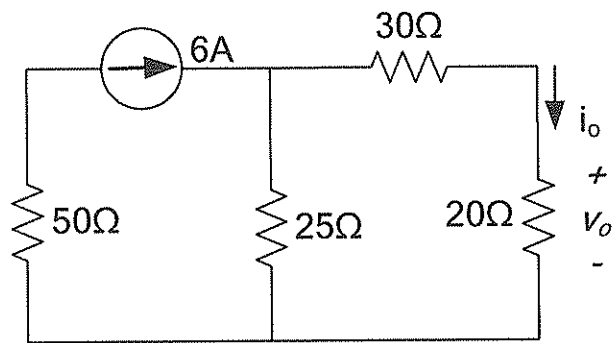

Gebruik lineariteit om die spanning v_o in die stroombaan te bereken (aanvaar aanvanklik $v_o = 20V$). [2]

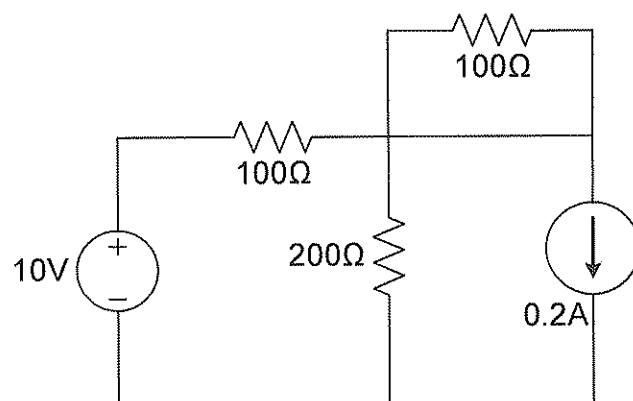Use linearity to calculate the voltage v_o in the circuit (initially assume $v_o = 20V$). [2]




Vereenvoudig die stroombaan tot 'n enkele spanningsbron en 'n enkele weerstand. [2]

Reduce the circuit to a single voltage source and a single resistor. [2]

Vraag 2.3

Question 2.3

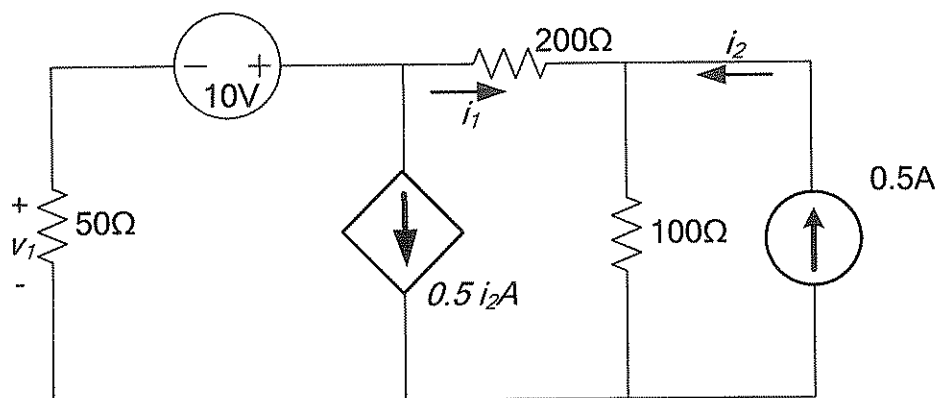


Bereken:

- (a) v_i as gevolg van die 10V bron. [2]
(b) i_1 as gevolg van die 0.5A bron. [2]

Calculate:

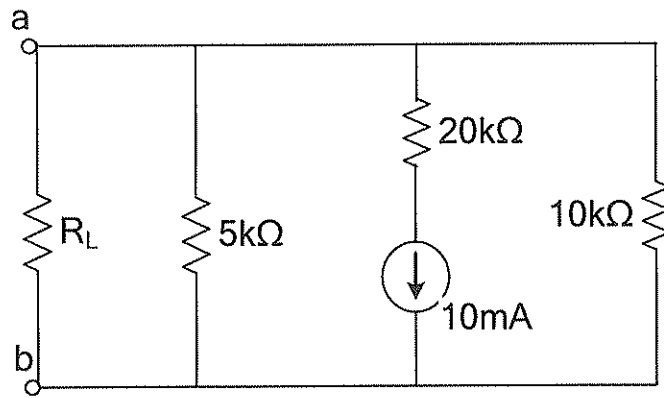- (a) v_i due to 10V source. [2]
(b) i_1 due to 0.5A source. [2]




Wat is die optimum waarde van R_L vir maksimum drywingsoordrag, en wat is die waarde van die maksimum drywing (in mW). [3]

What is the optimum value of R_L for maximum power transfer, and what is the value of the maximum power (in mW). [3]


Vraag 2.5

Question 2.5

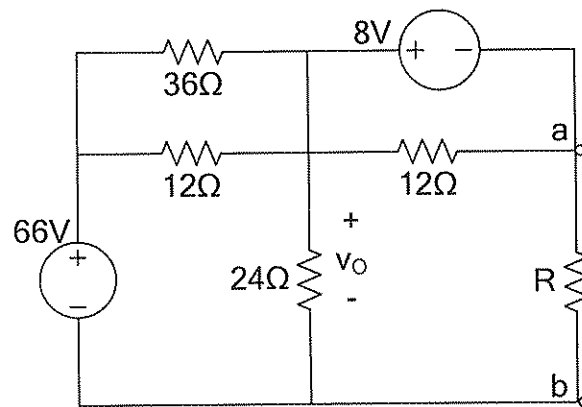

Bereken die Thévenin ekwivalente weerstand R_{TH} oor die las R (terminale a-b). [2]

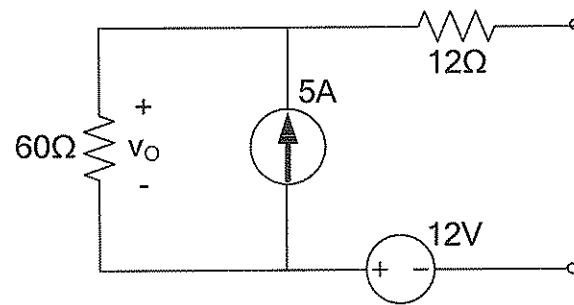Calculate the Thévenin equivalent resistance R_{TH} across load R (terminal a-b). [2]




Bepaal die Thévenin ekwivalent. [4]

Determine the Thévenin equivalent. [4]

Vraag 2.7

Question 2.7

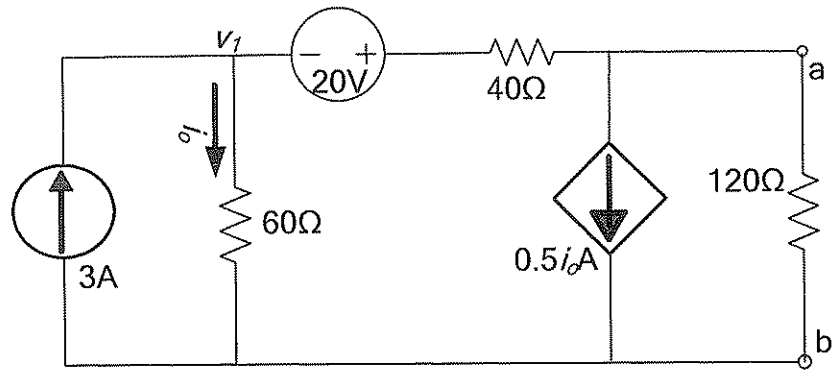


Bepaal die Thévenin ekwivalent R_{TH} ten opsigte van terminale a–b (verwyder die 120Ω). [2]

Find the Thévenin equivalent R_{TH} with respect to terminals a–b (remove the 120Ω). [2]


Vraag 2.8

Question 2.8

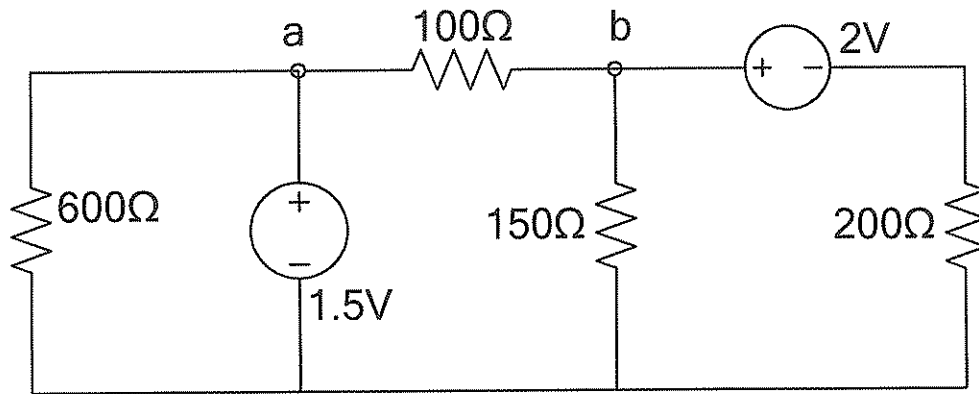

Bepaal die Norton ekwivalent I_N and R_N met verwysing tot terminale a-b (verwyder die 100Ω las). [4]

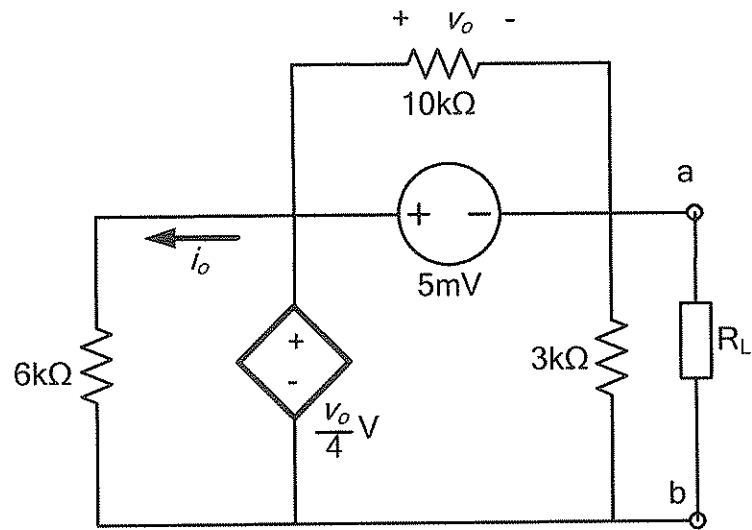Find the Norton equivalent I_N and R_N with respect to terminals a-b (remove the 100Ω load). [4]




Bepaal die Norton ekwivalente weerstand R_N met verwysing tot terminale a-b. [2]

Determine the Norton equivalent resistance R_N with respect to terminals a-b. [2]

VRAAG 3 – QUESTION 3 [15]

Vraag 3.1

Question 3.1

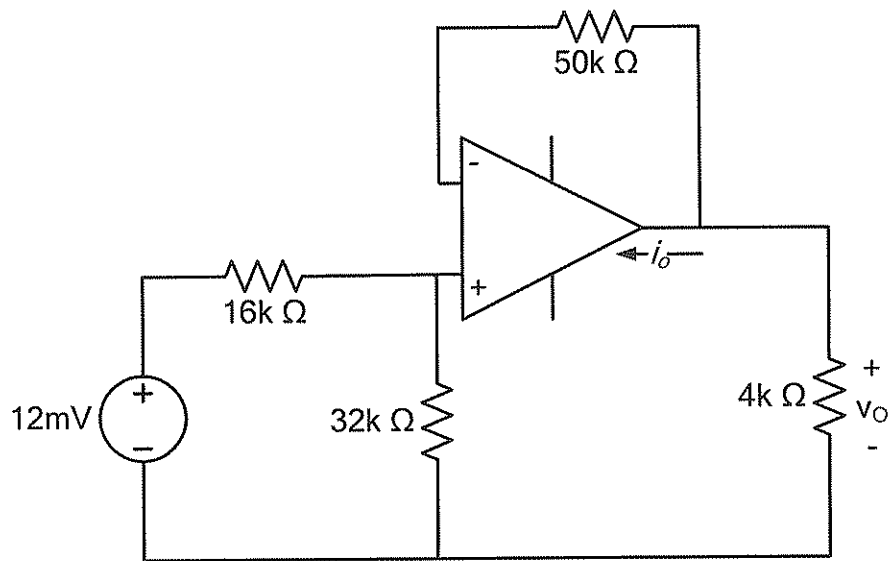


Bepaal die waarde van v_O and i_o . [3]

Calculate the value of v_O and i_o . [3]

Vraag 3.2


Question 3.2

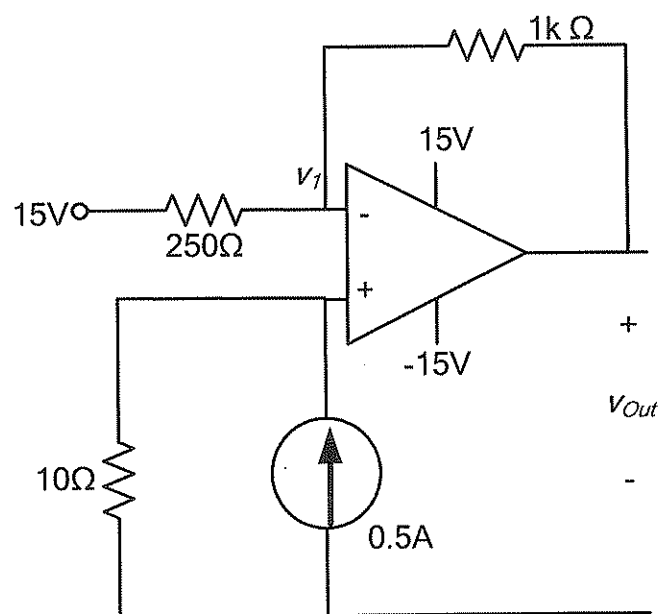
Bepaal V_{out} . [2]

Determine V_{out} . [2]


Vraag 3.3

Question 3.3

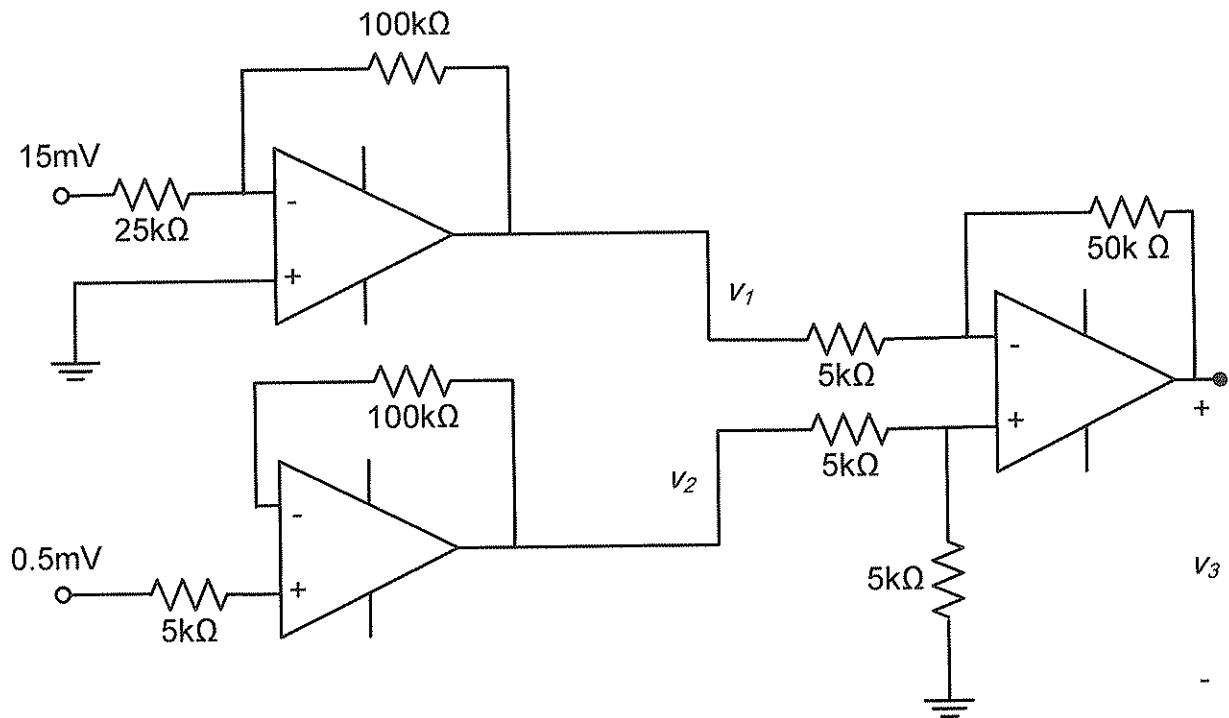

Bepaal V_1 , V_2 , en V_3 . [3]

Determine V_1 , V_2 , and V_3 . [3]

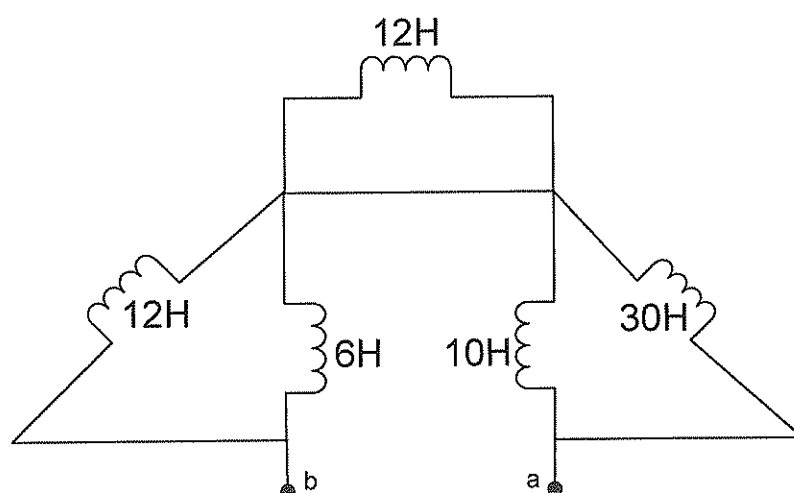


Bereken die ekwivalente induktansie tussen terminale *a* en *b*. [2]

Calculate the equivalent inductance between terminals *a* and *b*. [2]

Vraag 3.5

Question 3.5

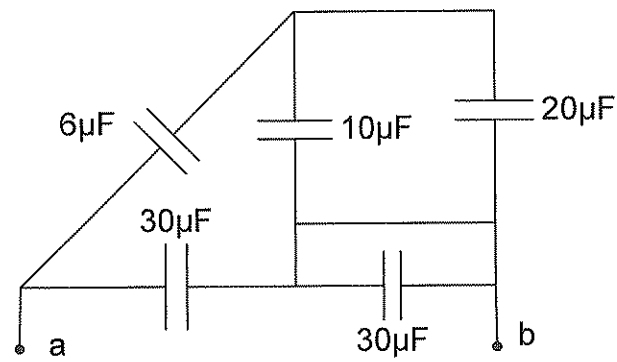


Bereken die ekwivalente kapasitansie tussen terminale a en b . [2]

Calculate the equivalent capacitance between terminals a and b . [2]

Vraag 3.6

Question 3.6

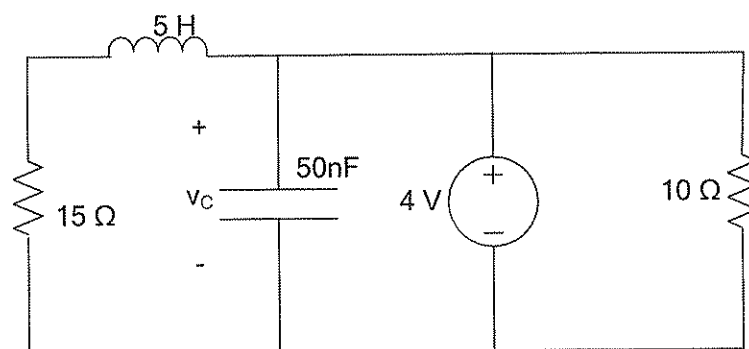

Bepaal energiewaardes:

- (a) gestoor in die kapasitor, [1]
- (b) gestoor in die induktor, en [1]
- (c) ge-assosieer met die $10\ \Omega$ weerstand in een uur. [1]


Determine the energy:

- (a) stored in the capacitor, [1]
- (b) stored in the inductor, and [1]
- (c) associated with the $10\ \Omega$ resistor in one hour. [1]

VRAAG 4 – QUESTION 4 [20]

Vraag 4.1	Question 4.1
(a) Skryf as 'n enkele cosinus uitdrukking: $v(t) = 15 \cos(\omega t + 30^\circ) - 10 \sin(\omega t - 45^\circ) \text{ V}$ [2]	(a) Write as a single cosine expression: $v(t) = 15 \cos(\omega t + 30^\circ) - 10 \sin(\omega t - 45^\circ) \text{ V}$ [2]
(b) Watter van die volgende fasors loop voor, en met hoeveel grade? $\bar{V}_1 = 10 \angle -30^\circ$, $\bar{V}_2 = 15 \angle 170^\circ$ [2]	(b) Which of the following phasors is leading, and with how many degrees? $\bar{V}_1 = 10 \angle -30^\circ$, $\bar{V}_2 = 15 \angle 170^\circ$ [2]
(c) Bepaal $\bar{V}_2$ (in reghoekige vorm): $\begin{bmatrix} 1+j1 & -j \\ -j & 2-j2 \end{bmatrix} \begin{bmatrix} \bar{V}_1 \\ \bar{V}_2 \end{bmatrix} = \begin{bmatrix} 10 \\ 0 \end{bmatrix} \quad [2]$	(c) Determine $\bar{V}_2$ (in rectangular form): $\begin{bmatrix} 1+j1 & -j \\ -j & 2-j2 \end{bmatrix} \begin{bmatrix} \bar{V}_1 \\ \bar{V}_2 \end{bmatrix} = \begin{bmatrix} 10 \\ 0 \end{bmatrix} \quad [2]$

Vraag 4.2	Question 4.2
(a) Evalueer die volgende (skryf antwoord in reghoekige vorm): $\frac{\sqrt{(20 + j10)}}{(3 + j4)^*} \quad [2]$ (b) Evalueer die volgende (skryf antwoord in polêre vorm): $\frac{(14 - j9)}{(-2 - j8)} + 2e^{j30^\circ} \quad [2]$	(a) Evaluate the following (write the answer in rectangular form): $\frac{\sqrt{(20 + j10)}}{(3 + j4)^*} \quad [2]$ (b) Evaluate the following (write the answer in polar form): $\frac{(14 - j9)}{(-2 - j8)} + 2e^{j30^\circ} \quad [2]$

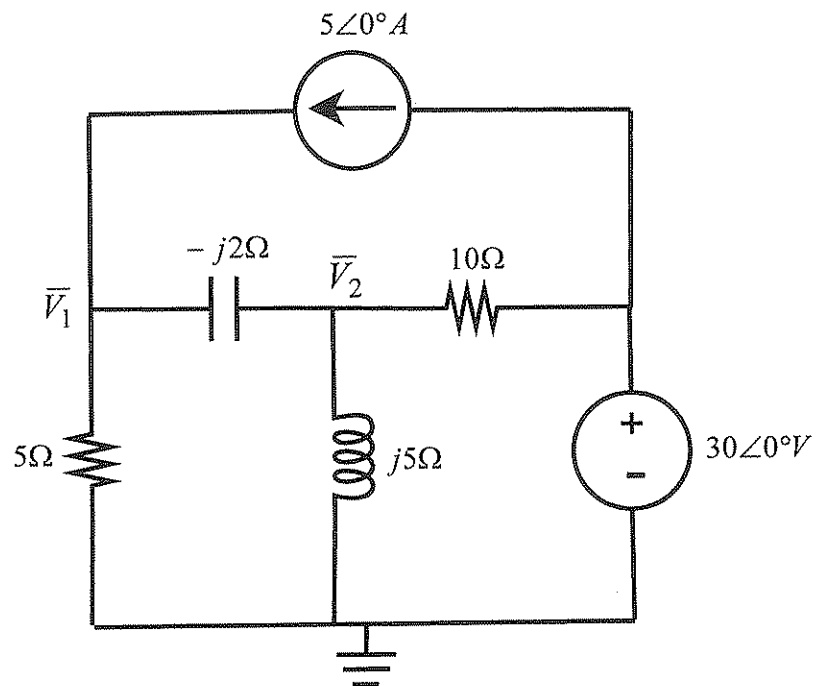

Gebruik node-analise om twee gelyktydige vergelykings vir fasors $\bar{V}_1$ en $\bar{V}_2$ op te stel. Skryf in die vorm

$$\bar{a}\bar{V}_1 + \bar{b}\bar{V}_2 = 50$$

$$\bar{c}\bar{V}_1 + \bar{d}\bar{V}_2 = 30$$


met $\bar{a}$, $\bar{b}$, $\bar{c}$, and $\bar{d}$ komplekse koëffisiënte in reghoekige vorm. [4]

Use nodal analysis to set up two simultaneous equations for phasors $\bar{V}_1$ and $\bar{V}_2$. Write in the form

$$\bar{a}\bar{V}_1 + \bar{b}\bar{V}_2 = 50$$

$$\bar{c}\bar{V}_1 + \bar{d}\bar{V}_2 = 30$$

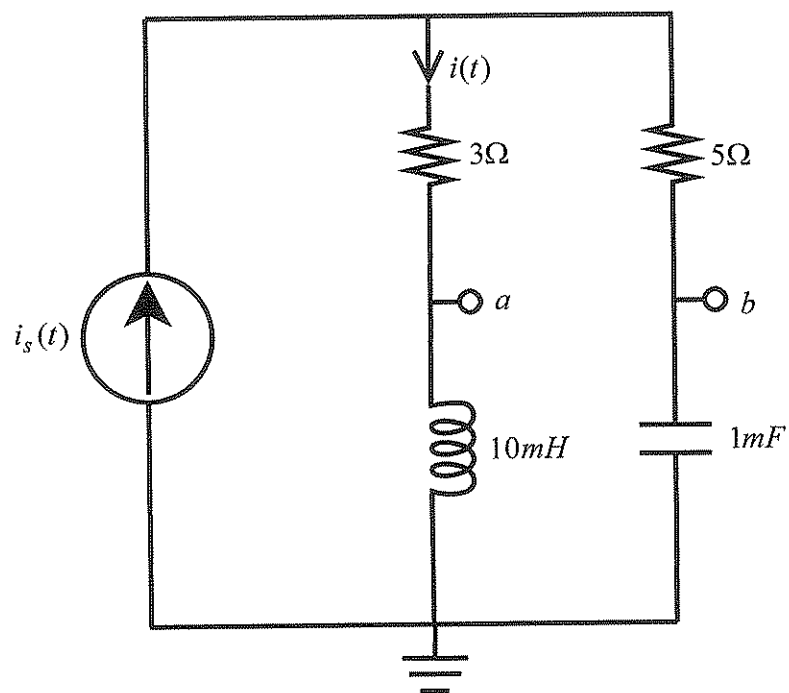with $\bar{a}$, $\bar{b}$, $\bar{c}$, and $\bar{d}$ complex coefficients in rectangular form. [4]




Indien $i_s(t) = 3\cos(400t)$ A:

- (a) Bereken $i(t)$. [2]
- (b) Bereken Z_{ab} (in polêre vorm), die Thevenin impedansie t.o.v. terminale a-b. [2]

If $i_s(t) = 3\cos(400t)$ A:

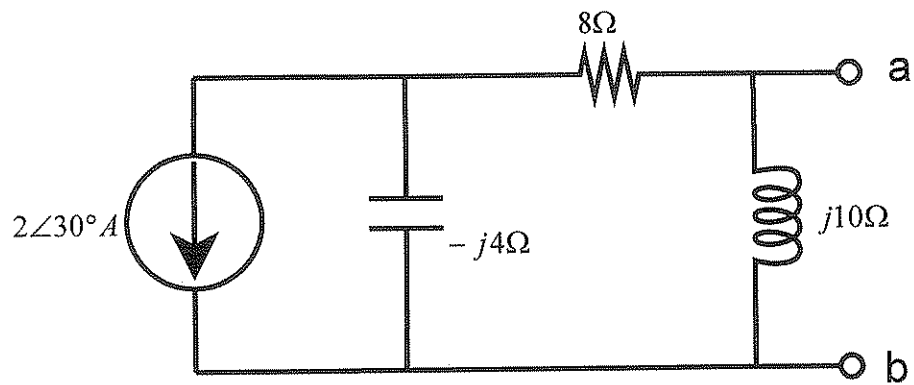- (a) Determine $i(t)$. [2]
- (b) Determine Z_{ab} (in polar form), the Thevenin impedance w.r.t. terminals a-b. [2]



Bepaal $\bar{V}_{th}$ (die Thevenin spanning) t.o.v. terminale a-b.
Skryf die antwoord in polêre vorm. [2]

Find $\bar{V}_{th}$ (the Thevenin voltage) w.r.t. terminals a-b.
Write the answers in polar form. [2]

EINDE - END