

Departement Elektriese, Elektroniese en
Rekenaar-Ingenieurswese

Semestertoets 1

Kopiereg voorbehou

Module EBN111

Elektrisiteit en Elektronika

15 Maart 2012



UNIVERSITEIT VAN PRETORIA
UNIVERSITY OF PRETORIA
YUNIBESITHI YA PRETORIA

Department of Electrical, Electronic and
Computer Engineering

Semester Test 1

Copyright reserved

Module EBN111

Electricity and Electronics

15 March 2012

Eksamensinligting:

Exam information:

Memo.

Maksimum punte: <i>Maximum marks:</i>	45	Volpunte: <i>Full marks:</i>	45
Duur van vraestel: <i>Duration of paper:</i>	90 minute <i>90 minutes</i>	Oopboek / toeboek: <i>Open / closed book:</i>	Toe <i>Closed</i>
Totale aantal bladsye (hierdie blad ingesluit): <i>Total number of pages (including this page):</i>		13	

BELANGRIK- IMPORTANT

- Die eksamenregulasies van die Universiteit van Pretoria geld.
The examination regulations of the University of Pretoria apply.
- Alle vrae moet op die ANTWOORDBLAD beantwoord word.
All questions must be answered on the ANSWER SHEET.
- Studente mag hul eie rowwe berekeninge op die vraestel doen – die vraestel word nie ingeneem nie.
Students may do their own rough calculations on the question paper – the question paper will not be taken in.
- Antwoorde moet eenhede insluit!
Answers must include units!
- Finale antwoorde moet as reële getalle geskryf word, en nie as breuke nie.
Final answers must be written as real numbers, and not as fractions.

Dosent(e): <i>Lecturer(s):</i>	1 J Joubert
	2 JD le Roux

Groephoof: Ek bevestig dat die vraestel die uitkomstes toets soos gespesifiseer in die studiehandleiding.

Group head: I confirm that the question paper evaluates the outcomes as specified in the study guide.

Groephoof: <i>Group Head:</i>	Prof J Joubert	Handtekening: <i>Signature:</i>	
----------------------------------	----------------	------------------------------------	--


VRAAG/QUESTION 1 [22]

Vraag 1.1 [2]

Die grafiek dui die drywing van 'n element teenoor tyd aan. Bepaal die hoeveelheid energy wat die element verbruik tussen 4 en 10 sekondes.

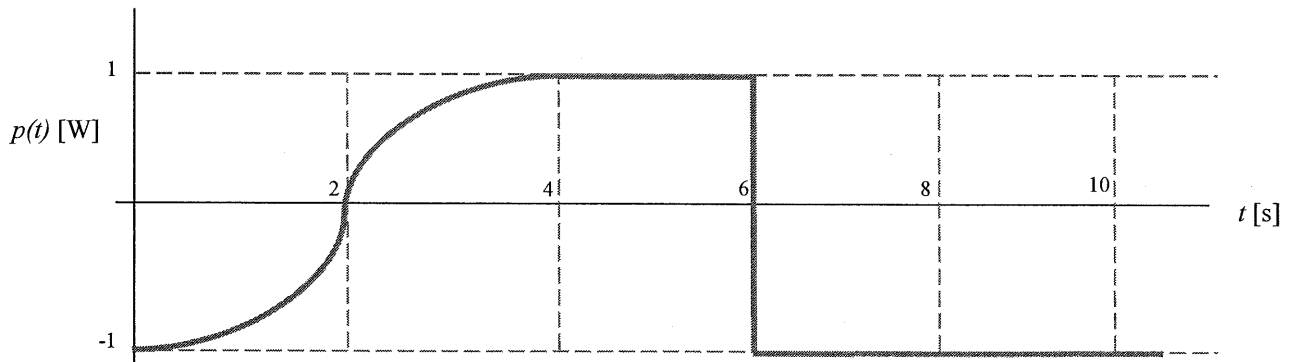Question 1.1 [2]

The graph shows the power of an element over time. Determine the energy used by the element between 4 and 10 seconds.



$$\begin{aligned} p &= \frac{dw}{dt} \\ \therefore W &= \int_{t_0}^{t_1} p \, dt \\ &= (6-4) \times 1 + (10-6) \times -1 \\ &= 2 - 4 \\ &= -2 \, \text{J} \end{aligned}$$

(2 marks for correct sign (-) and size (2))
(0 marks for any other answer.)

Vraag 1.2 [2]

Dit verg 600 mJ om -60 nC in 6 μ s deur 'n element te beweeg. Bepaal die spanning oor die element en die stroom deur die element. (Skryf die antwoorde deur gebruik te maak van die SI voorvoegsels: M, k, m, μ , n, of p.)

Question 1.2 [2]

To move -60 nC in 6 μ s through an element requires 600 mJ. Determine the voltage across the element and the current through the element. (Write the answers using the SI prefixes: M, k, m, μ , n, or p.)

$$* \quad i = \Delta q / \Delta t$$

$$= \frac{-60 \text{ nC}}{6 \mu\text{s}}$$

$$= \underline{-10 \text{ mA}} \quad \checkmark$$


$$* \quad U = dw / dq$$

$$= \frac{600 \text{ mJ}}{-60 \text{ nC}}$$

$$= \underline{-10 \text{ MV}} \quad \checkmark$$

(1 mark if answer has

- correct sign
- correct size
- SI pretix)

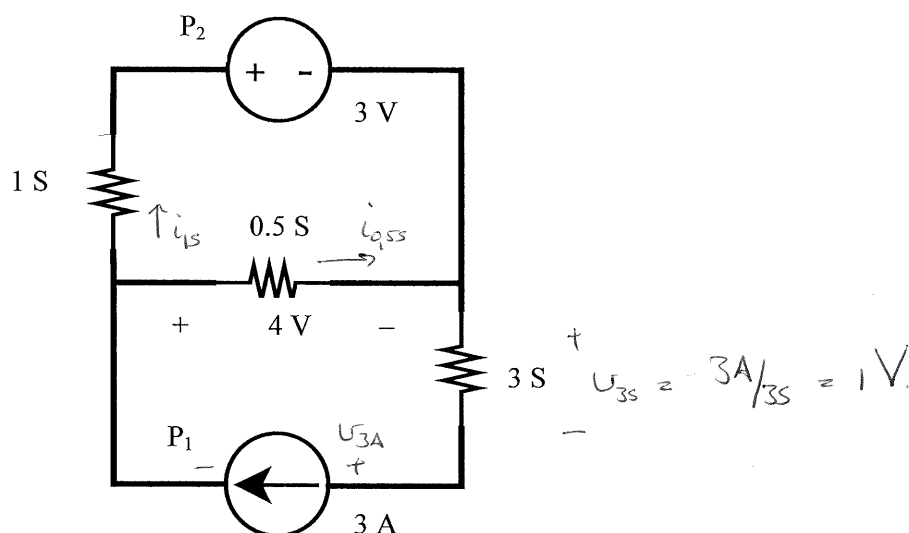Vraag 1.3 [3]a) Bepaal die drywing P_1 en P_2 .b) Vir P_2 , word drywing geabsorbeer of gelever?**Question 1.3 [3]**a) Determine the power P_1 and P_2 .b) For P_2 , is power absorbed or provided?

$$* i_{0.5S} = 0.5 \times 4 = 2A$$

$$* i_{1S} = 3 - 2 = 1A$$

$$* P_2 = 3V \times 1A = 3W \checkmark$$

$$KVL: 4V + 3A / 3S + U_{3A} = 0$$

$$U_{3A} = -5V$$

$$* P_1 = -5V \times 3A = -15W \checkmark$$

→ P_2 absorbs power.
 ✓ (Marked according to value given for P_2 .)

→ If answer of P_2 was given as negative,
 then student must write: P_2 delivers power.

Vraag 1.4 [7]


Weerstande R_1 , R_2 en R_3 en bronspanning V_S is onbekend.

- Hoeveel nodusse is daar in die stroombaan? [1]
- Hoeveel takke is daar in die stroombaan? [1]
- Bepaal die spanning V_S . [1]
- Bepaal die spanning V_R oor weerstand R_1 . [2]
- Bepaal stroom I_X . [2]

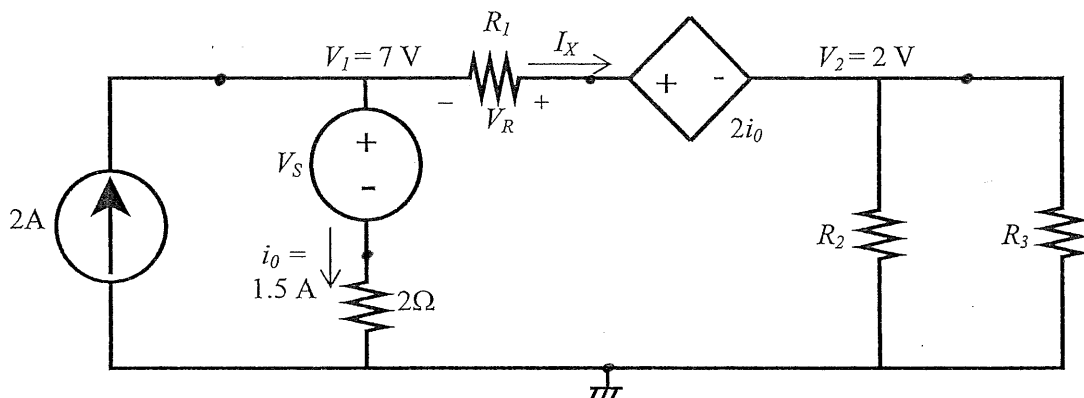Question 1.4 [7]

Source voltage V_S and resistors R_1 , R_2 and R_3 are unknown.

- How many nodes are there in the circuit? [1]
- How many branches are there in the circuit? [1]
- Determine the voltage V_S . [1]
- Determine the voltage V_R over resistor R_1 . [2]
- Determine the current I_X . [2]



a) 5 ✓ nodes

b) 7 ✓ branches.

Remember $b = n + (\text{independent loops}) - 1$

$$7 = 5 + 3 - 1.$$

c) KVL: $-V_1 + V_S + i_0 \times 2 = 0$

$$-7 + V_S + 3 = 0$$

$$V_S = \underline{4V} \quad \checkmark$$


d) KVL: $-V_1 + 2i_0 + V_2 - V_R = 0$

$$V_R = -7 + 2 + 2(1.5)$$

$$= \underline{-2V} \quad \checkmark \checkmark$$

(If sign correct, but sign wrong, 1 mark)

e) KCL: $I_X = 2 - 1.5 = \underline{0.5A} \quad \checkmark \checkmark$

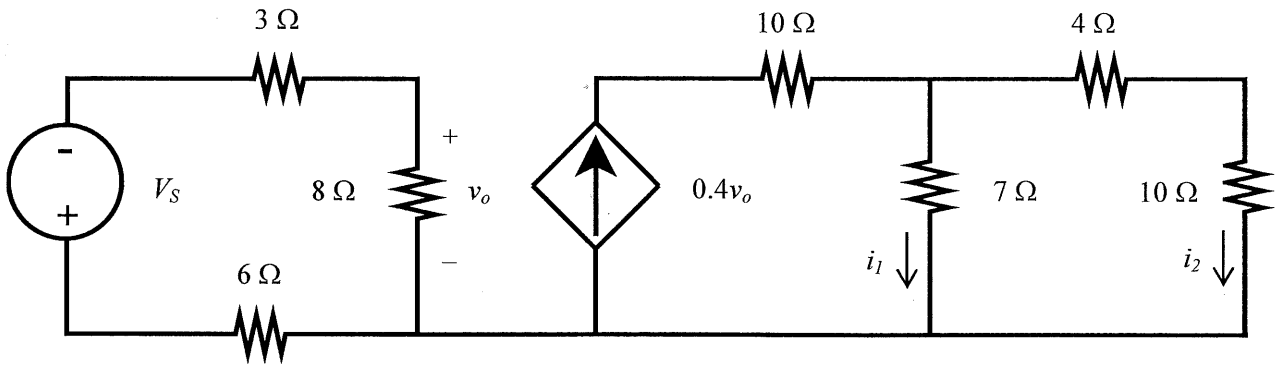
Vraag 1.5 [4]a) Bereken v_o indien $V_S = 21.25$ V.b) Bereken i_2 indien $v_o = 5$ V.**Question 1.5 [4]**a) Determine v_o if $V_S = 21.25$ V.b) Determine i_2 if $v_o = 5$ V.

$$\begin{aligned}
 \text{a) } * \quad v_o &= \frac{-V_S}{6 + 3 + 8} \times 8 \\
 &= \underline{-10\text{V}} \quad \checkmark \checkmark \quad (\text{If size is correct but sign is wrong, then one mark.})
 \end{aligned}$$

$$\begin{aligned}
 \text{b) } i_2 &= \frac{0.4(5) \times 7}{4 + 10 + 7} \\
 &= \underline{0.6667\text{ A}} \quad \checkmark \checkmark \quad (\text{Two marks for right answer.})
 \end{aligned}$$

Vraag 1.6 [4]


Bepaal die ekwivalente weerstand by terminale a - b vir kringbaan (1) en (2). Alle resistors is $2\ \Omega$.

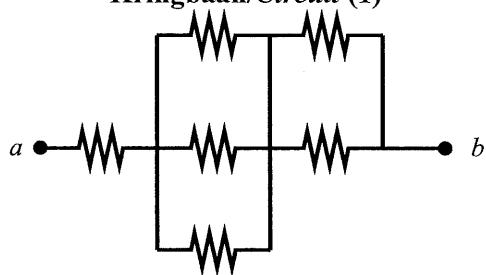Kringbaan/Circuit (1)

$$\begin{aligned}
 R_{eq} &= 2 + 2 \parallel 2 \parallel 2 + 2 \parallel 2 \\
 &= 2 + \frac{2}{3} + 1 \\
 &= \underline{3,667\ \Omega} \quad \checkmark\checkmark
 \end{aligned}$$

Question 1.6 [4]

Determine the equivalent resistance at terminals a - b for circuit (a) and (b). All resistors are $2\ \Omega$.

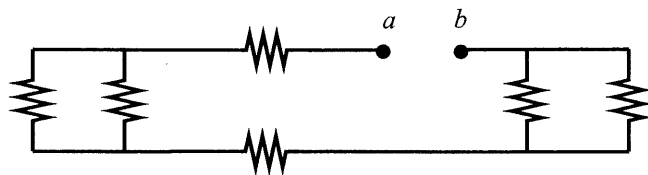Kringbaan/Circuit (2)

$$\begin{aligned}
 R_{eq} &= 2 + 2 \parallel 2 + 2 + 2 \parallel 2 \\
 &= 4 + 1 + 1 \\
 &= \underline{6\ \Omega} \quad \checkmark\checkmark
 \end{aligned}$$

VRAAG/QUESTION 2 [23]

Vraag 2.1[4]

Gebruik node-analise om twee vergelykings van die volgende vorm op te stel vir die stroombaan:

$$aV_1 + bV_2 = -200$$


$$cV_1 + dV_2 = 600$$

Question 2.1[4]

Use node analysis to set up two equations of the following form for the circuit:

$$aV_1 + bV_2 = -200$$

$$cV_1 + dV_2 = 600$$

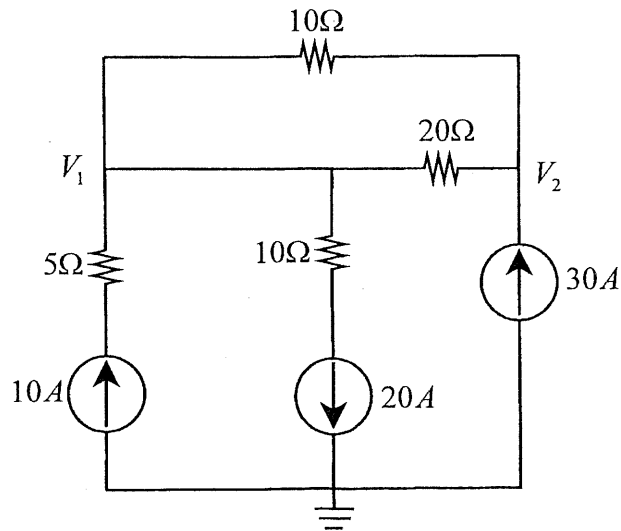

node 1: $-10 + 20 + \frac{V_1 - V_2}{20} + \frac{V_1 - V_2}{10} = 0$

$\times 20:$ $200 + V_1 - V_2 + 2V_1 - 2V_2 = 0$

$$3V_1 - 3V_2 = -200 \rightarrow$$

node 2: $-30 + \frac{V_2 - V_1}{20} + \frac{V_2 - V_1}{10} = 0$

$\times 20:$ $-600 + V_2 - V_1 + 2V_2 - 2V_1 = 0$

$$-3V_1 + 3V_2 = 600 \rightarrow$$

Vraag 2.2[4]

Gebruik lus-analise om twee vergelykings van die volgende vorm op te stel vir die stroombaan:

$$ai_1 + bi_2 = 0$$


$$ci_1 + di_2 = -5$$

Question 2.2 [4]

Use mesh analysis to set up two equations of the following form for the circuit:

$$ai_1 + bi_2 = 0$$

$$ci_1 + di_2 = -5$$

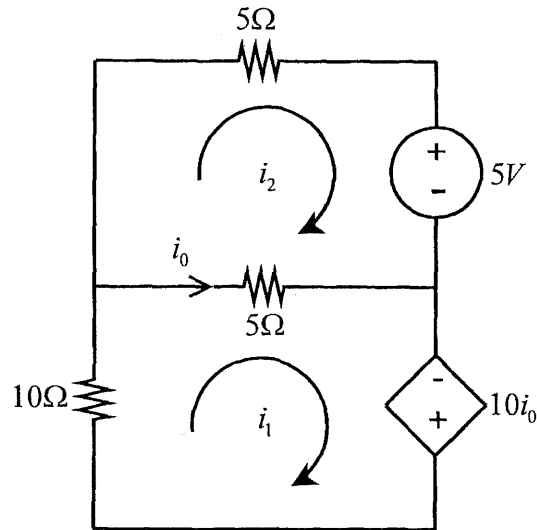

mesh 1:

$$10i_1 + 5(i_1 - i_2) - 10i_0 = 0$$

$$\text{but } i_0 = i_1 - i_2$$

$$\cancel{10i_1} + 5i_1 - 5i_2 - \cancel{10i_1} + 10i_2 = 0$$

$$\underline{5i_1 + 5i_2 = 0}$$

mesh 2:

$$5i_2 + 5 + 5(i_2 - i_1) = 0$$

$$\underline{-5i_1 + 10i_2 = -5}$$

Vraag 2.3 [4](a) Bepaal V_1 .

$$\begin{bmatrix} 5 & -3 \\ -3 & 6 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} -1 \\ 2 \end{bmatrix}$$

(b) Bepaal i_2 .

$$\begin{bmatrix} 5 & -5 & 0 \\ -2 & 20 & 0 \\ 0 & 0 & 10 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} 20 \\ 10 \\ -10 \end{bmatrix}$$

Question 2.3 [4](a) Determine V_1 .

$$\begin{bmatrix} 5 & -3 \\ -3 & 6 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} -1 \\ 2 \end{bmatrix}$$

(b) Determine i_2 .

$$\begin{bmatrix} 5 & -5 & 0 \\ -2 & 20 & 0 \\ 0 & 0 & 10 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} 20 \\ 10 \\ -10 \end{bmatrix}$$

$$(a) \quad \frac{\begin{vmatrix} -1 & -3 \\ 2 & 6 \end{vmatrix}}{\begin{vmatrix} 5 & -3 \\ -3 & 6 \end{vmatrix}} = \frac{-6+6}{30-9} = \frac{0}{21} = 0 \quad \checkmark \checkmark$$

$$(b) \quad \Delta = \begin{vmatrix} 5 & -5 & 0 \\ -2 & 20 & 0 \\ 0 & 0 & 10 \end{vmatrix} = (5 \times 20 \times 10) - (-2 \times (-5) \times 10) = 1000 - 100 = 900$$

$$\Delta_2 = \begin{vmatrix} 5 & 20 & 0 \\ -2 & 10 & 0 \\ 0 & -10 & 10 \end{vmatrix} = (5 \times 10 \times 10) - (-2 \times 20 \times 10) = 500 + 400 = 900$$

$$i_2 = \frac{\Delta_2}{\Delta} = \frac{900}{900} = 1 \quad \checkmark \checkmark$$

Vraag 2.4 [4]

Gebruik node-analise om twee vergelykings van die volgende vorm op te stel vir die stroombaan:

$$aV_1 + bV_2 = 10$$


$$cV_1 + dV_2 = -60$$

Question 2.4 [4]

Use node analysis to set up two equations of the following form for the circuit:

$$aV_1 + bV_2 = 10$$

$$cV_1 + dV_2 = -60$$

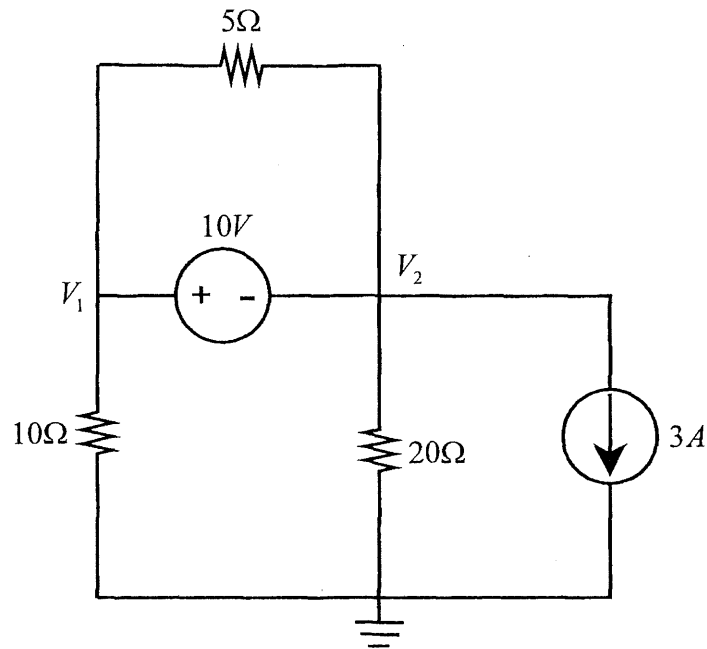

Supernode: $V_2 + 10 = V_1$

$$\checkmark V_1 - \checkmark V_2 = 10$$

KCL: $\frac{V_1}{10} + \frac{V_2}{20} + 3 = 0$

$\times 20$: $\checkmark 2V_1 + \checkmark V_2 = -60$

Vraag 2.5 [4]

Gebruik lus-analise om twee vergelijkingen van die volgende vorm op te stel vir die stroombaan:

$$ai_1 + bi_2 = 10$$


$$ci_1 + di_2 = 0$$

Question 2.5 [4]

Use mesh analysis to set up two equations of the following form for the circuit:

$$ai_1 + bi_2 = 10$$

$$ci_1 + di_2 = 0$$

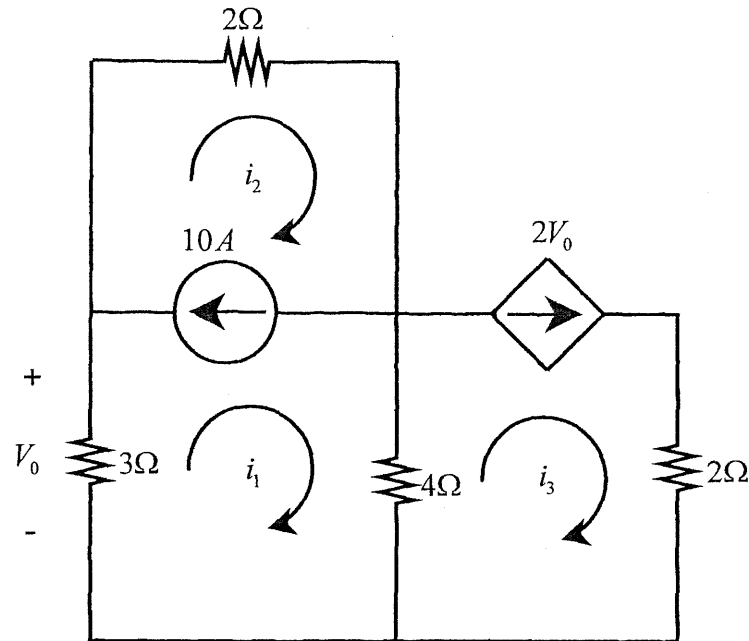

$$i_3 = 2V_0 = 2(-3i_1) = -6i_1$$

KVL: $3i_1 + 2i_2 + 4(i_1 - i_3) = 0$

$$3i_1 + 2i_2 + 4i_1 - 4(-6i_1) = 0$$

$$31i_1 + 2i_2 = 0$$

Supermesh: $i_2 - i_1 = 10$


$$-i_1 + i_2 = 10$$

Vraag 2.6 [3]

Bepaal die node-spannings vergelykings deur inspeksie.

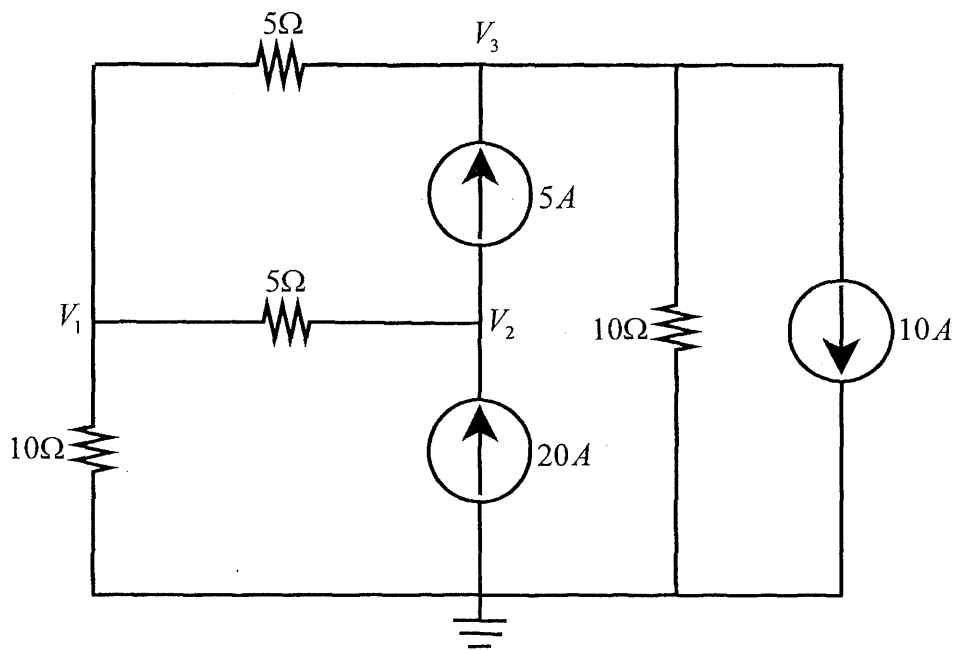Question 2.6 [3]

Determine the node-voltage equations by inspection.



$$\begin{bmatrix} 0.5 & -0.2 & -0.2 \\ -0.2 & 0.2 & 0 \\ -0.2 & 0 & 0.3 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} 0 \\ 15 \\ -5 \end{bmatrix}$$

✓ for diagonal self terms

✓ for off-diagonal coupling terms

✓ for right hand excitation matrix