

Departement Elektriese, Elektroniese en
Rekenaar-Ingenieurswese

Semestertoets 1

Kopiereg voorbehou

Module EBN111

Elektrisiteit en Elektronika

3 Maart 2016

Department of Electrical, Electronic and
Computer Engineering

Semester Test 1

Copyright reserved

Module EBN111

Electricity and Electronics

3 March 2016



UNIVERSITEIT VAN PRETORIA
UNIVERSITY OF PRETORIA
YUNIBESITHI YA PRETORIA

Eksamensinligting:

Exam information:

Maksimum punte: <i>Maximum marks:</i>	46	Volpunte: <i>Full marks:</i>	45
Duur van vraestel: <i>Duration of paper:</i>	90 minute <i>90 minutes</i>	Oopboek / toeboek: <i>Open / closed book:</i>	Toe <i>Closed</i>
Totale aantal bladsye (hierdie blad ingesluit): <i>Total number of pages (including this page):</i>		16 + Answer sheet	

BELANGRIJK- IMPORTANT

- Die eksamenregulasies van die Universiteit van Pretoria geld.
The examination regulations of the University of Pretoria apply.
- Alle vrae moet op die ANTWOORDBLAD beantwoord word.
All questions must be answered on the ANSWER SHEET.
- Studente mag hul eie rowwe berekeninge op die vraestel doen – die vraestel word nie ingeneem nie.
Students may do their own rough calculations on the question paper – the question paper will not be taken in.
- Antwoorde moet eenhede insluit!
Answers must include units!
- Finale antwoorde moet as reële getalle geskryf word, en nie as breuke nie.
Final answers must be written as real numbers, and not as fractions.

Dosent(e): <i>Lecturer(s):</i>	1. G Hancke
	2. D. Bhatt
	3. D. le Roux


VRAAG/QUESTION 1 [12]

Vraag 1.1 [2]

Die lading wat in 'n geleier vloei word onder getoon. Bepaal die stroom by: a) $t = 10$ s en b) $t = 20$ s. (Die kurwe bereik sy maksimumwaarde by $t = 20$ s.)

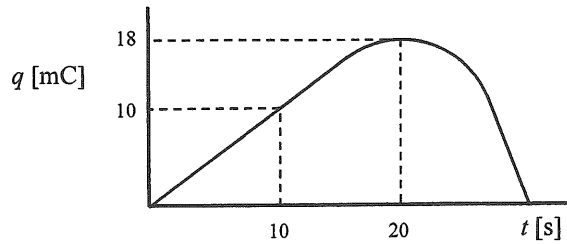Question 1.1 [2]

The charge flowing in a conductor is shown below. Determine the current at: a) $t = 10$ s en b) $t = 20$ s. (The curve reaches its maximum value at $t = 20$ s.)



$$i(10s) = \frac{dq}{dt} = \frac{10mC}{10s} = 1mA$$

$$i(20s) = \frac{dq}{dt} = 0 \text{ (Slope} = 0 \text{)}$$

Vraag 1.2 [2]

Die spanning oor 'n 5Ω weerstand neem liniêr toe van 0 mV tot 15 mV tussen $t = 0$ s en $t = 20$ s. Bereken

- a) Die waarde van die lading wat deur die weerstand vloei tussen $t = 5$ s en $t = 15$ s.
b) Die drywing in die weerstand geabsorbeer by $t = 12$ s.

Question 1.2 [2]

The voltage across a 5Ω resistor increases linearly from 0 mV to 15 mV between $t = 0$ s and $t = 20$ s. Calculate

- a) The value of the charge flowing through the resistor between $t = 5$ s and $t = 15$ s.
b) The power absorbed by the resistor at $t = 12$ s.


(b) At $t = 12s$

$$i = \frac{12}{20} \times 3mA$$

$$= 1.8mA$$

$$P(12s) = (1.8 \times 10^{-3})^2 \times 5$$

$$= 16.2 \mu W$$

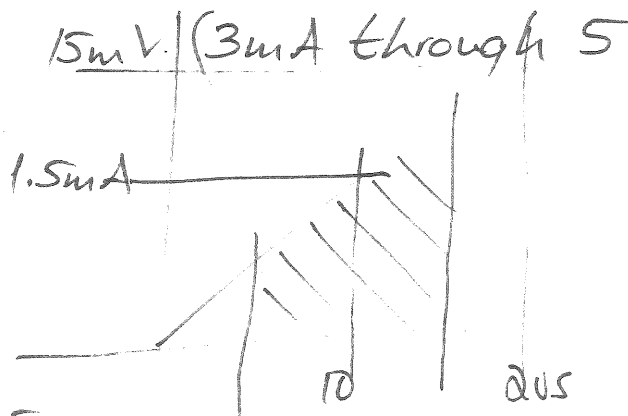

←→

$$(a) \text{ area} = 1.5mA \times 10$$

$$= 15mC$$

Vraag 1.3 [3]

'n Elektriese verwarmer is gespesifiseer as 240 V; 3 kW.

- a) Hoeveel stroom trek die verwarmer?
- b) Hoeveel lading vloei deur dit in 1 minuut?
- c) Elektrisiteit kos R3/kWh. Bereken die totale koste oor een maand (30 dae) indien die verwarmer elke oggend vir 80 minute aangeskakel word?

Question 1.3 [3]

An electric heater is specified as 240 V; 3 kW.

- a) What is the current flowing through the heater?
- b) How much charge flows through the heater in 1 minute?
- c) Electricity cost R3/kWh. Calculate the total cost if the heater is switched on for 80 minutes every morning for 1 month (30 days).

$$(a) \quad i = \frac{3000}{240} = 12.5 \text{ A}$$

$$(b) \quad q(\text{minute}) = 12.5 \times 60 \\ = 750 \text{ C}$$

$$(c) \quad \text{Total energy} = \frac{30 \times 80}{60} \times 3 \\ = 120 \text{ kWh}$$


$$\text{Total Cost} = 120 \times 3 \\ = \underline{\underline{R360}}$$

Vraag 1.4 [5]

Bepaal P_1 , P_2 , P_3 , R_1 en R_2

Question 1.4 [5]

Determine P_1 , P_2 , P_3 , R_1 en R_2 .

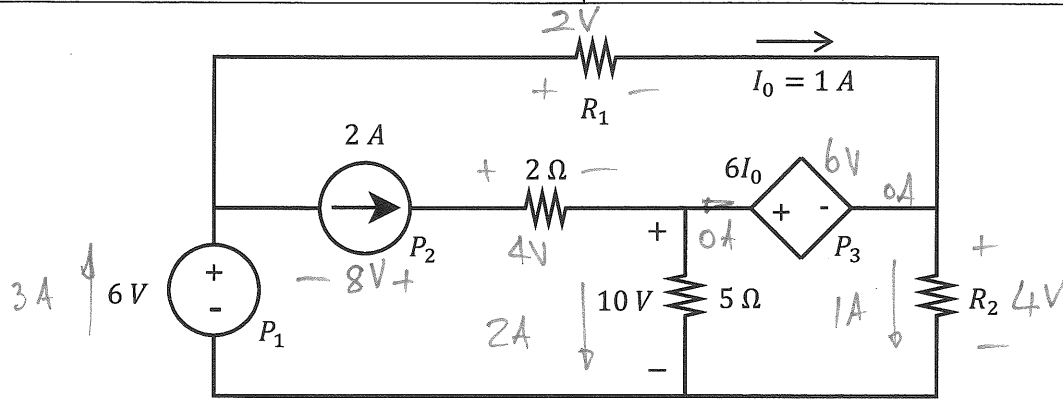

$$P_1 = -18W (-3 \times 6)$$

$$P_2 = -16W (-2 \times 8)$$

$$P_3 = 0W \text{ (zero current)}$$

$$\sum P_{\text{source}} = -34W$$

$$R_1 = 2\Omega$$

$$R_2 = 4\Omega$$

$$P_{R1} = 2W$$

$$P_{R2} = 4W$$

$$P_{2\Omega} = 8W$$

$$P_{5\Omega} = 20W$$

$$\sum P_R = +34W$$

VRAAG/QUESTION 2 [18]

Vraag 2.1 [4]


Vir onderstaande kringbaan, bereken die volgende:

- die stroom I_I ,
- die stroom I_x ,
- die spanning oor die 5 A stroombron, V_{5A} , en
- die waarde van die resistor R wat sal veroorsaak dat 'n stroom van 3.5 A daardeur vloei.

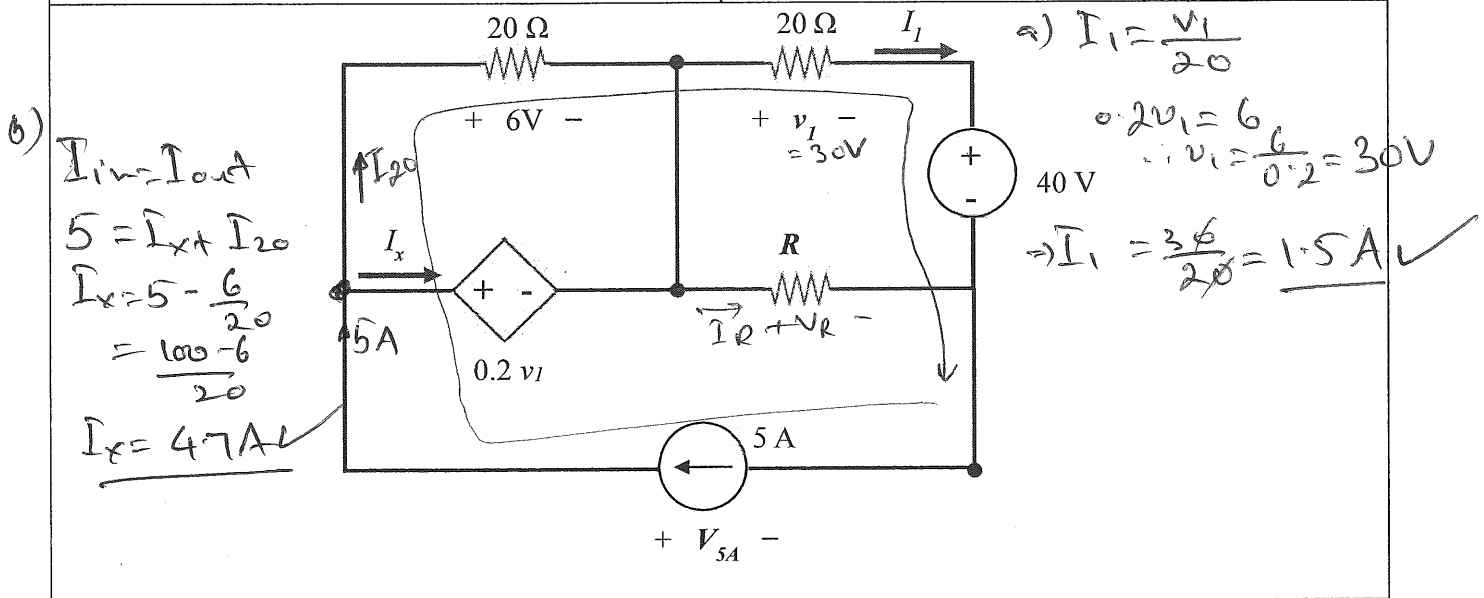Question 2.1 [4]

Consider the circuit diagram shown below and calculate the following:

- the current I_I ,
- the current I_x ,
- the voltage across 5 A current source, V_{5A} , and
- the value of resistor R , that will allow a current of 3.5 A to flow through it.



c) KVL: $-V_{5A} + 6 + V_1 + 40 = 0$

$$V_{5A} = 6 + 30 + 40$$

$$V_{5A} = 76V$$

d) $R = \frac{V_R}{I_R} = \frac{V_R}{3.5}$

$$-V_5 + 0.2V_1 + V_R = 0$$

$$V_R = 76 - 0.2 \times 30$$

$$= 70V$$

$$R = \frac{700}{35} = 20\Omega$$

Vraag 2.2 [4]


Bepaal die:

- a) spanning oor $4\text{ k}\Omega$ resistor, v_4 .
- b) stroom I .

Question 2.2 [4]

Determine the:

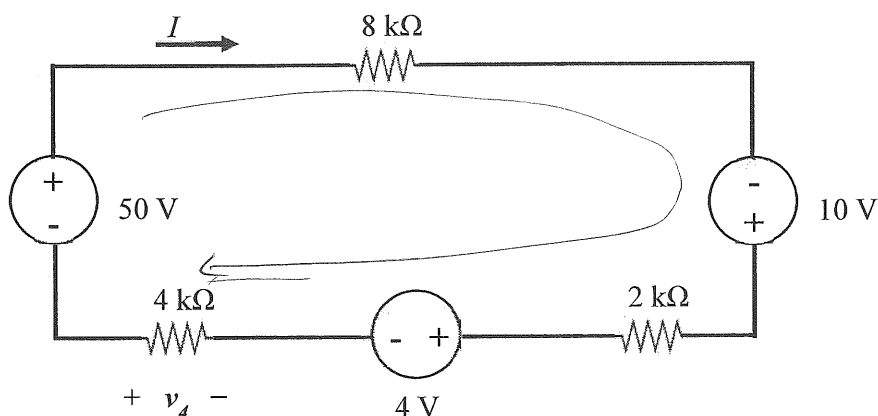- a) voltage across $4\text{ k}\Omega$ resistor, v_4 .
- b) current I .



(a) using voltage divider

$$v_4 = - (50 + 10 - 4) \left(\frac{4\text{k}}{(4 + 8 + 2)\text{k}} \right)$$

$$v_4 = \underline{-16\text{ V}}$$

$$(b) I = \frac{V}{R}$$

$$= \frac{50 + 10 - 4}{(8 + 2 + 4)\text{k}}$$

$$I = \frac{56}{14\text{k}}$$

$$= \underline{4\text{ mA}}$$

Vraag 2.3 [4]


Bepaal die stroom deur

- a) die 40 kΩ resistor, I_{40} and
b) die 10 kΩ resistor, I_{10} .


Question 2.3 [4]

Determine the current flowing through

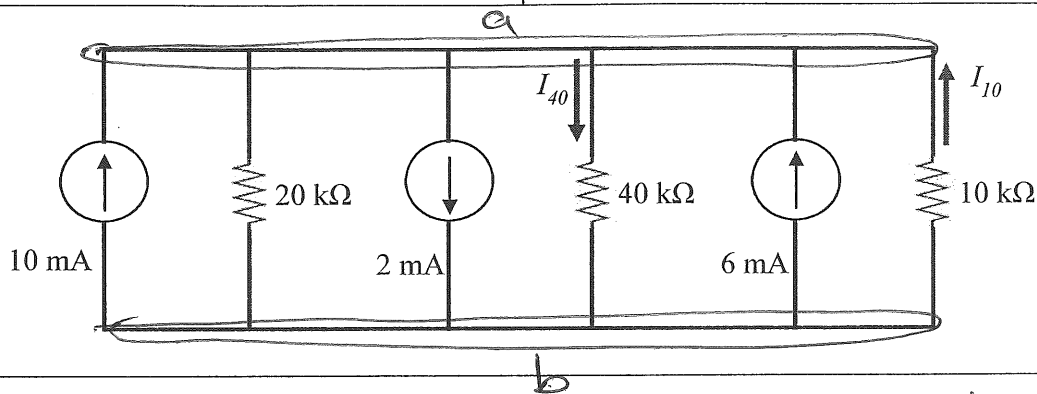- a) the 40 kΩ resistor, I_{40} and
b) the 10 kΩ resistor, I_{10} .



Note all elements are parallel.

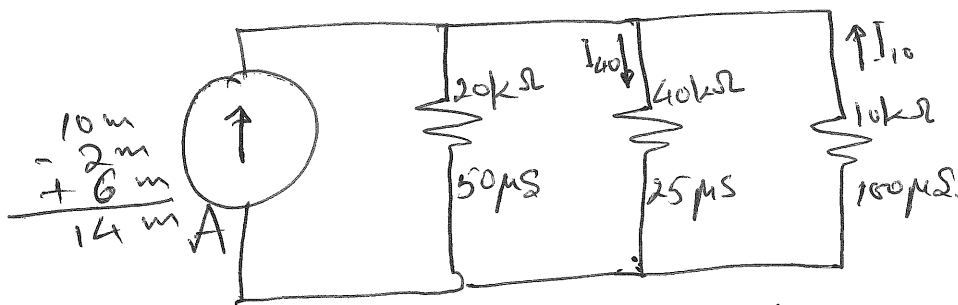

Using current divider

$$a) \quad I_{40} = \frac{G_{40}}{G_{eq}} \times I = \frac{1/40k}{1/40k + \frac{1}{20k} + \frac{1}{10k}} \times I = \frac{25 \mu}{(50 + 25 + 100) \mu} \times 14 \text{ mA}$$

$$I_{40} = \frac{25}{175} \times 14 \text{ mA} = \underline{2 \text{ mA}} \quad \checkmark \checkmark$$

$$b) \quad I_{10} = -I \times \frac{G_{10}}{G_{eq}} = -14 \text{ mA} \times \frac{100 \mu}{175 \mu}$$

$$I_{10} = \underline{-8 \text{ mA}} \quad \checkmark \checkmark$$


Vraag 2.4 [2]

Bepaal die ekwivalente weerstand R_{ab} .

Question 2.4 [2]


Calculate the equivalent resistance R_{ab} .

$$30 + 60 + 30 = 120 \Omega$$

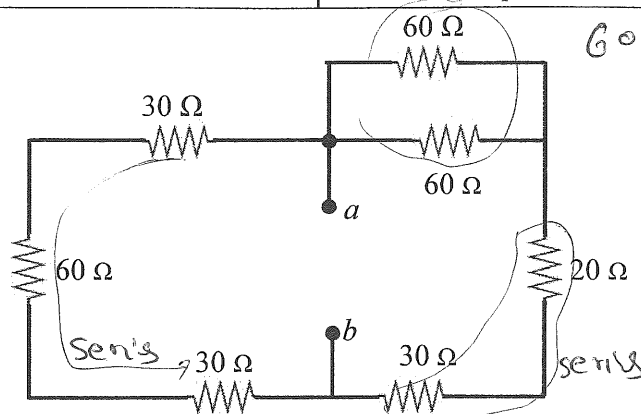


$$60 \parallel 60 = \frac{60 \times 60}{60 + 60} = 30 \Omega$$

$$30 + 20 = 50 \Omega$$

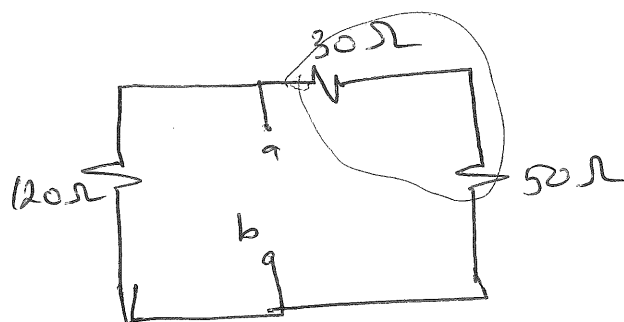

$$30 + 50 = 80 \Omega$$

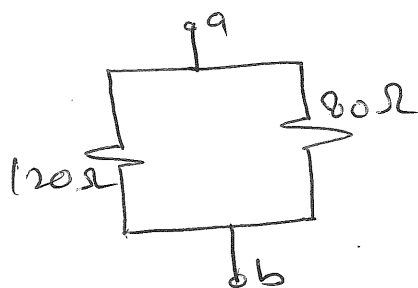

$$R_{ab} = 80 \parallel 120$$

$$= \frac{80 \times 120}{80 + 120}$$



$$= \underline{48 \Omega}$$

Vraag 2.5 [2]

Bepaal die ekwivalente geleiding, G_{ab} , tussen die nodes a - b vir onderstaande kringbaan.

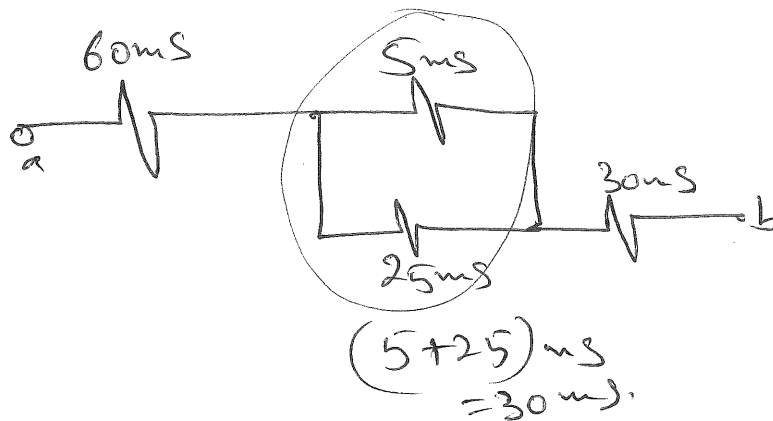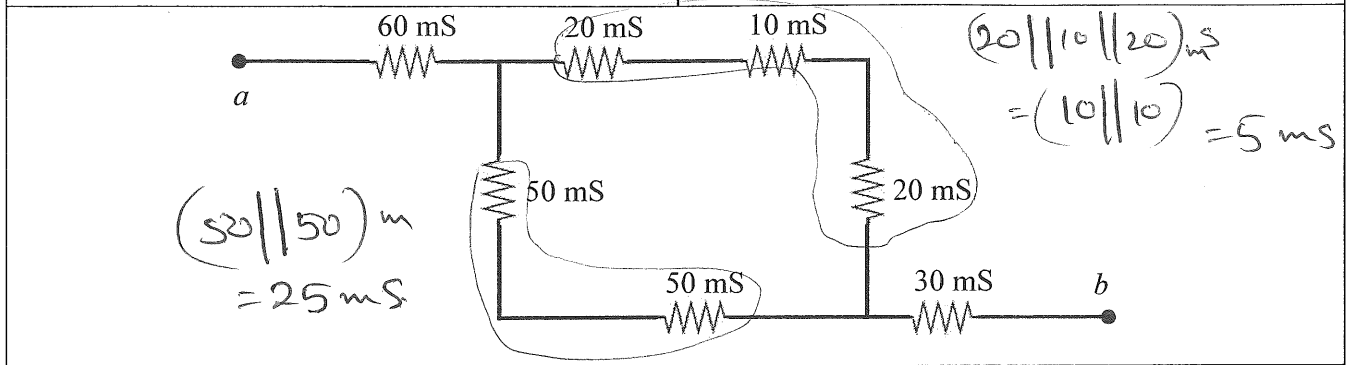Question 2.5 [2]

Calculate the equivalent conductance, G_{ab} , across the nodes a - b of the circuit below.




$$\begin{aligned}
 \Rightarrow G_{ab} &= (60 \text{ m} \parallel 30 \text{ m} \parallel 30 \text{ m}) \text{ S} \\
 &= (60 \text{ m} \parallel 15 \text{ m}) \text{ S} \\
 &= \left(\frac{60 \times 15}{60 + 15} \right) \text{ mS} \\
 &= \underline{12 \text{ mS}} \quad \checkmark \checkmark
 \end{aligned}$$

Vraag 2.6 [2]

Bepaal die ekwivalente weerstand R_{eq} .

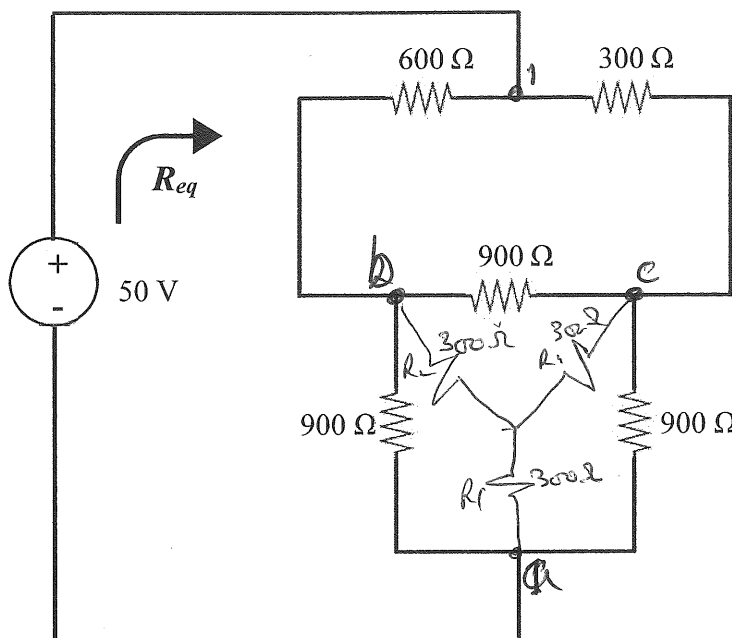Question 2.6 [2]

Calculate the equivalent resistance, R_{eq} .





Balanced load

$$R_Y = \frac{R_A}{3} = \frac{900}{3}$$

$$R_Y = 300\Omega$$

$$R_1 = R_2 = R_3$$

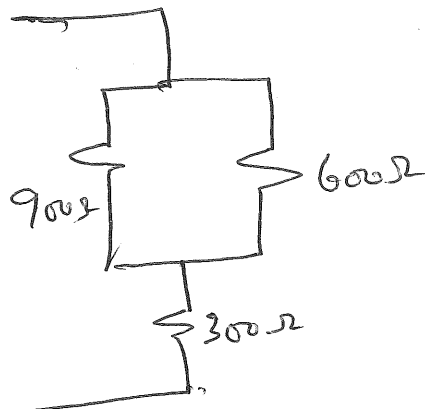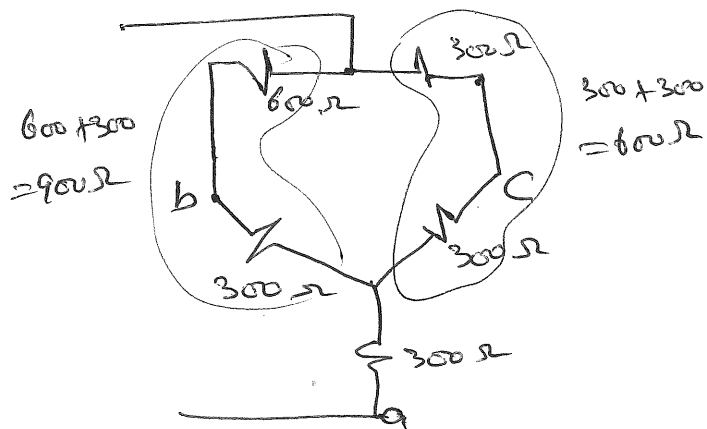

$$\therefore R_{eq} = 300 + (900 \parallel 600)$$

$$= 300 + \frac{900 \times 600}{900 + 600}$$

$$= 300 + 360$$

$$= 660\Omega$$


VRAAG/QUESTION 3 [16]

Vraag 3.1 [2]

Gebruik of node of lusanalyse en bepaal I_x .

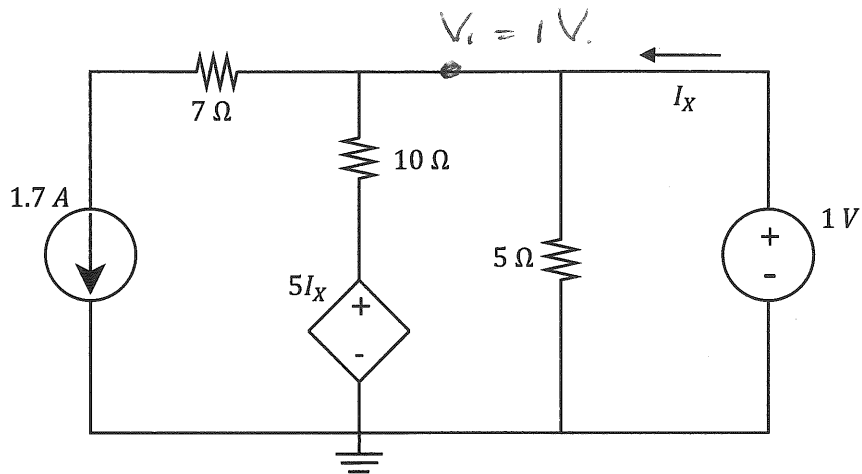Question 3.1 [2]

Use either nodal or mesh analysis to determine I_x .




$$\textcircled{1} \quad I_x = \frac{1}{5} + \frac{1 - 5I_x}{10} + 1.7.$$

$$10I_x = 2 + 1 - 5I_x + 17.$$

$$15I_x = 20$$

$$3I_x = 4$$

$$I_x = \frac{4}{3} = 1.333 \text{ A}$$

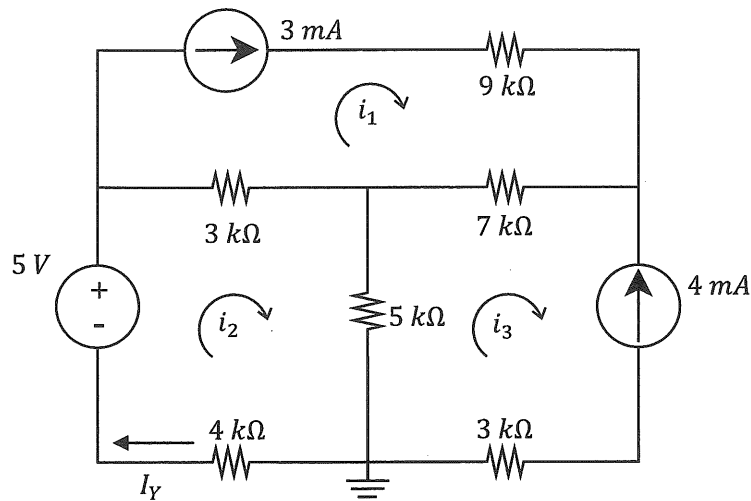Vraag 3.2 [2]Gebruik lusanalyse en bepaal I_Y .(Wenk: $i_1 = 3 \text{ mA}$, $i_2 = I_Y$, en $i_3 = -4 \text{ mA}$.)**Question 3.2 [2]**Use mesh analysis to determine I_Y .(Hint: $i_1 = 3 \text{ mA}$, $i_2 = I_Y$, and $i_3 = -4 \text{ mA}$.)


$$\textcircled{1} \quad -5 + i_2 (3k + 5k + 4k) - 3k i_1 - 5k i_3 = 0.$$

$$12k i_2 = 5 + 3k(3m) + 5(-4m)$$

$$12k i_2 = 5 + 9 - 20$$

$$12k i_2 = -6$$

$$i_2 = \underline{-0.5 \text{ mA}} \quad \checkmark$$

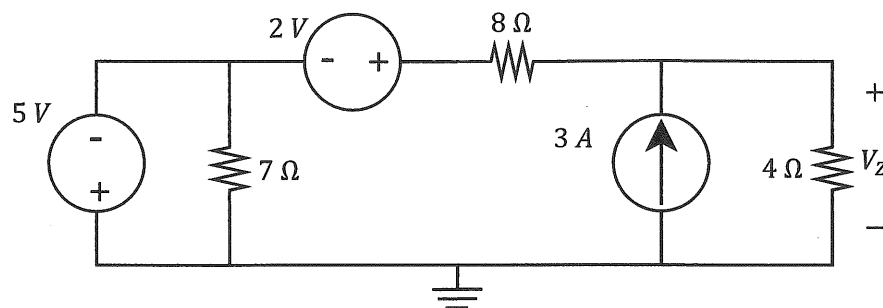Vraag 3.3 [2]Gebruik node analyse en bepaal V_Z .**Question 3.3 [2]**Use nodal analysis to determine V_Z .

$$\textcircled{1} \quad \frac{V_Z}{4} + \frac{V_Z - 2 - (-5)}{8} = 3.$$

$$2V_Z + V_Z + 3 = 24.$$

$$3V_Z = 21$$


$$V_Z = 7V \quad \checkmark$$

Vraag 3.4 [2]

Indien gegee dat $i_2 = -1.8$ A, bepaal i_0 deur gebruik te maak van lusanalise.

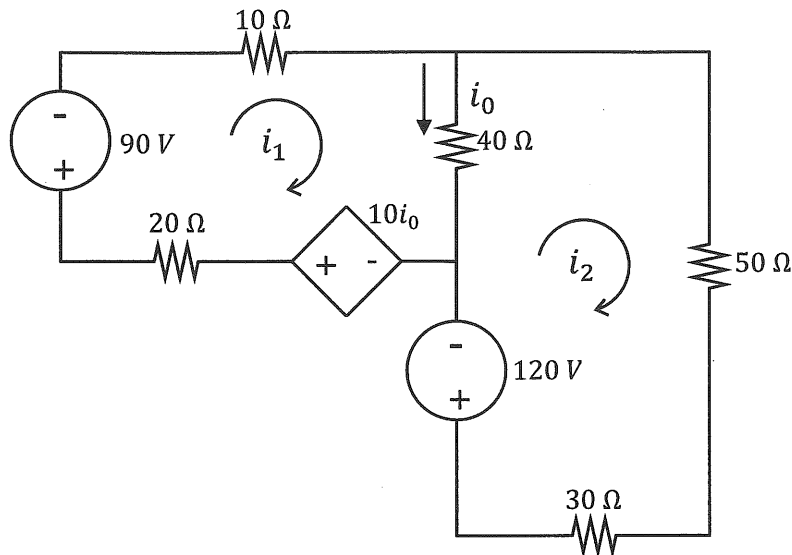Question 3.4 [2]

If given that $i_2 = -1.8$ A, determine i_0 using mesh analysis.



① $i_0 = i_1 - i_2$

② $+90 + i_1(10 + 40 + 20) - 40i_2 - 10i_0 = 0$

$$90 + 70i_1 - 40i_2 - 10i_1 + 10i_2 = 0$$

$$90 + 60i_1 - 30(-1.8) = 0$$

$$60i_1 = -90 - 54$$

$$60i_1 = -144$$

$$i_1 = -2.4$$

$$i_0 = -2.4 + 1.8$$

$$= -0.6 \text{ A}$$

Vraag 3.5 [4]a) Bepaal α indien $I_1 = 0.75$ A.

$$\begin{bmatrix} 4 & \alpha \\ -8 & 2 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 6 \\ -4 \end{bmatrix}$$

b) Bepaal β indien $v_1 = -3$ V en $v_3 = -1.8$ V.

$$\begin{bmatrix} 6 & 3 & -10 \\ -3 & 0 & \beta \\ 2 & -8 & 0 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \end{bmatrix} = \begin{bmatrix} -3 \\ 0 \\ 2 \end{bmatrix}$$

Question 3.5 [4]a) Determine α if $I_1 = 0.75$ A.

$$\begin{bmatrix} 4 & \alpha \\ -8 & 2 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 6 \\ -4 \end{bmatrix}$$

b) Determine β if $v_1 = -3$ V en $v_3 = -1.8$ V.

$$\begin{bmatrix} 6 & 3 & -10 \\ -3 & 0 & \beta \\ 2 & -8 & 0 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \end{bmatrix} = \begin{bmatrix} -3 \\ 0 \\ 2 \end{bmatrix}$$

$$a) \Delta = 4 \times 2 - (-8)\alpha = 8 + 8\alpha$$

$$\Delta_1 = \begin{vmatrix} 6 & \alpha \\ -4 & 2 \end{vmatrix} = 12 - (-4)\alpha = 12 + 4\alpha$$

$$\nabla I_1 = 0.75 = \frac{12 + 4\alpha}{8 + 8\alpha} \Rightarrow 6 + 6\alpha = 12 + 4\alpha$$

$$2\alpha = 6$$

$$\underline{\alpha = 3} \quad \checkmark$$

$$b) -3v_1 + \beta v_3 = 0$$

$$-3(-3) + \beta(-1.8) = 0$$

$$\beta = \frac{-9}{-1.8} = 5 \quad \checkmark$$

Vraag 3.6 [4]

Gebruik node-analise om twee vergelykings van die volgende vorm op te stel:

$$aV_1 + bV_2 = 30$$


$$cV_1 + dV_2 = -7.5$$

Question 3.6 [4]

Use nodal analysis to set up two equations of the following form:

$$aV_1 + bV_2 = 30$$

$$cV_1 + dV_2 = -7.5$$

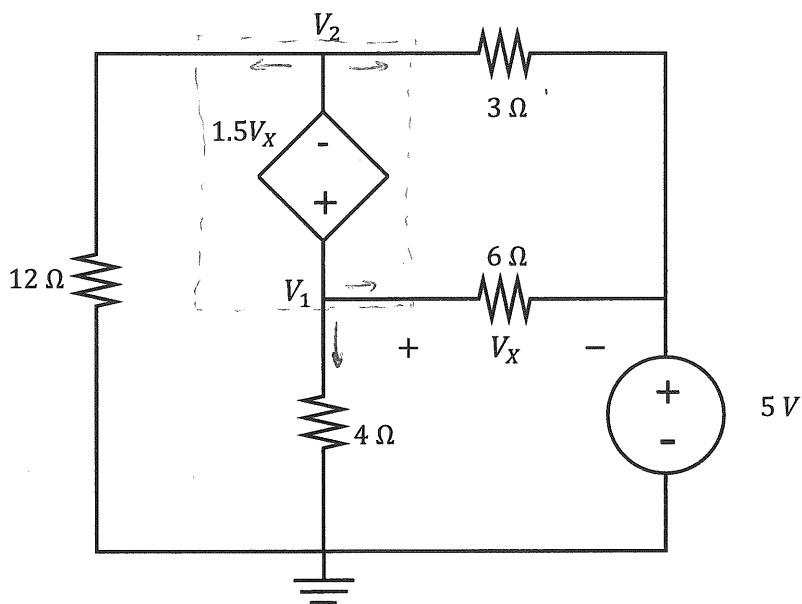

$$\textcircled{1} \quad \frac{V_1}{4} + \frac{V_1 - 5}{6} + \frac{V_2 - 5}{3} + \frac{V_2}{12} = 0$$

$$3V_1 + 2V_1 - 10 + 4V_2 - 20 + V_2 = 0.$$

$$\checkmark \quad 5V_1 + 5V_2 = 30$$

$$\textcircled{2} \quad V_1 - V_2 = 1.5V_x \quad \text{but } V_x = V_1 - 5.$$

$$\therefore V_1 - V_2 = 1.5V_1 - 7.5$$

$$\checkmark \quad -0.5V_1 - V_2 = -7.5$$