

Semester Test 1

Copyright reserved

Electricity and Electronics EBN 111

22 April 2021

Test Information

Maximum marks:	46	Full marks:	45
Duration of test:	100 min	Open/Closed book:	Open
Total number of pages (this page included)		17	

Lecturers: Dr D. le Roux, Dr S. Smith, Dr X. Ye**Assistant Lecturers:** M. Maritz, J. Masela, J. Thiselton, M. Trivedi, D. Wepener**Important**

1. The examination regulations of the University of Pretoria apply.
2. Write your answers on the Excel spreadsheet found on the AMS system. The spreadsheet contains unique parameter values for each student. Therefore, you must download the Excel spreadsheet from your own AMS account. Follow the instructions on the AMS spreadsheet carefully.
3. Final answers must be written as real numbers and not as fractions. Use at least 5 significant figures to write irrational numbers. Use decimal points and NOT decimal commas.
4. Answers must include units where applicable. (Refer to the EECE Rules for Electronic Assessments of tests and examinations for guidelines on how to enter units. Also refer to the example list of units on the Excel spreadsheet.)
5. **By uploading your class test, you declare the following:**


The University of Pretoria commits itself to produce academic work of integrity. I affirm that I am aware of and have read the Rules and Policies of the University, more specifically the Disciplinary Procedure and the Tests and Examinations Rules, which prohibit any unethical, dishonest or improper conduct during tests, examinations and/or any other forms of assessment. I am aware that no student or any other person may assist or attempt to assist another student, or obtain help, or attempt to obtain help from another student or any other person during tests, examinations and/or any other forms of assessment.

Online assessment submission rules and time-line

The following rules and time-line apply for all tests for EBN111/122 as illustrated by the figure below:

1. The Download Grace Period (DGP) is a 15 minute period before the official start of the test for students to download all documents related to the test and read all the necessary instructions.
2. The start of the green section after the DGP indicates the official start of the test. Students must work through the test at an average rate of at least 2 minutes per mark.
3. The upward green arrow at the end of the green section indicates the official submission deadline for the test.
4. Students must aim to submit their Excel spreadsheet with their answers on the AMS before the official submission deadline.
5. Students can request assistance via **e-mail** ebn2021.ams@gmail.com if they experience any technical issues with respect to uploading their Excel spreadsheets on the AMS.
6. An Upload Grace Period (UGP) of 15 minutes follows the official submission deadline. Students may submit their Excel spreadsheets with answers during this period without incurring any penalties. No email submissions will be accepted during the UGP.
7. A Penalty Period (PP) of 10 minutes follows the UGP. If a student submits an Excel spreadsheets during this period, the student incurs a 10% penalty to their final test mark.
8. No late submissions is accepted after the PP.

Late submissions of session-based assessments, e.g. tests and online practicals

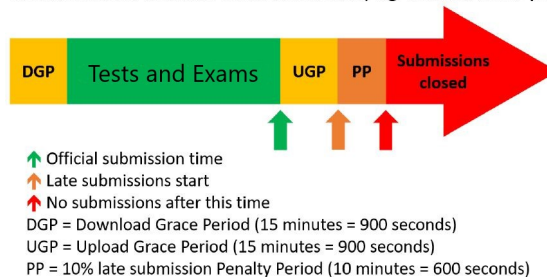

Section 1

Question 1 [2]


Given: x , y , z .


You have an old desk lamp which you use for studying. You decide to replace the old filament globe of x W with a new generation LED globe of y W. If you use your desk lamp for z h per day, and electricity costs R2/kWh, how much money do you save in a month (30 days) by using the new globe?
--


01	Savings [2]
-----------	-------------

Question 2 [2]Given: a , b


A 9 V battery is connected to a variable resistor. The resistance of the variable resistor is changed to produce a current response $i(t)$ through the variable resistor as shown in the graph below. Assuming the battery voltage remains constant, what is the total energy consumed by the variable resistor between $t = a$ s and $t = b$ s?

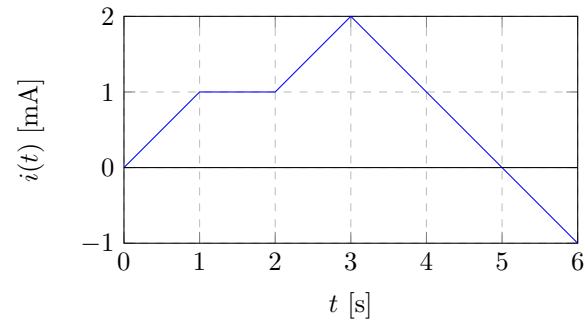
**02** | W [2]

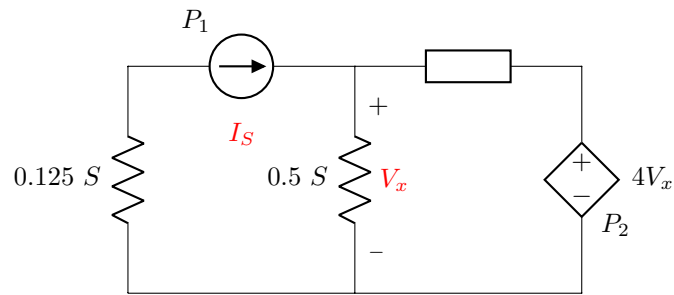
Questions 3 to 4 [4]Given: V_x , I_S .**03** Determine P_1 . [2]**04** Determine P_2 . [2]**Total Section 1: [8]**

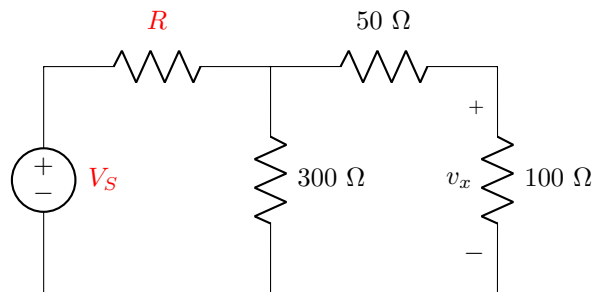Section 2**Question 5 [2]**Given: V_S , R .**05** Determine v_x . [2]


Questions 6 to 7 [4]

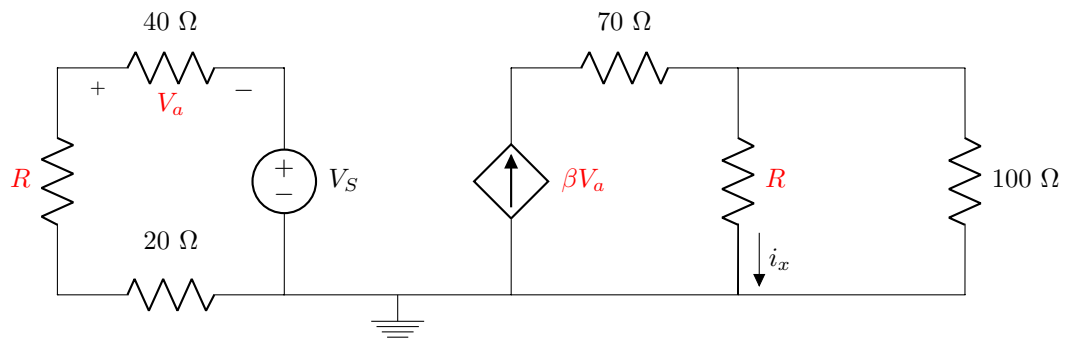
Given: β , V_a , R .**06** Determine V_S . [2]**07** Determine i_x . [2]

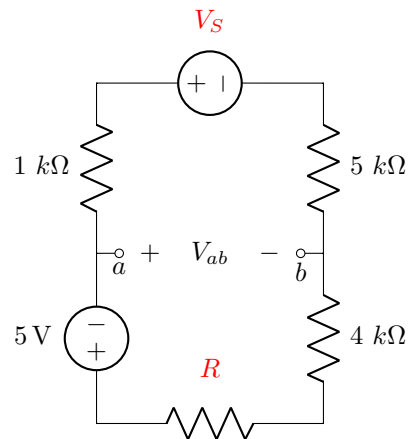
Question 8 [2]Given: V_S , R .**08** Determine V_{ab} . [2]

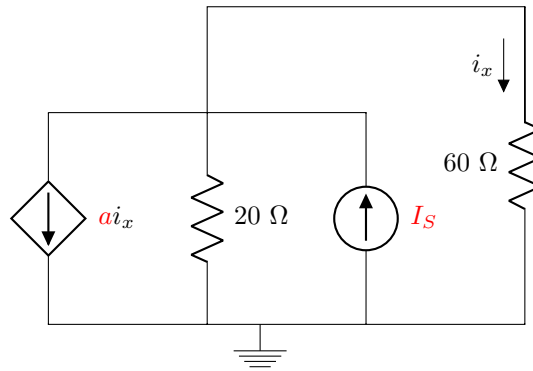Question 9 [2]Given: a , I_S .**09** Determine i_x . [2]


Questions 10 to 11 [4]

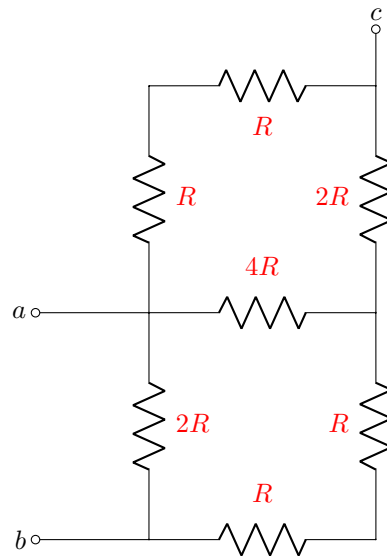Given: R **10** Determine R_{ab} [2]**11** Determine R_{cb} [2]**Total Section 2: [14]**

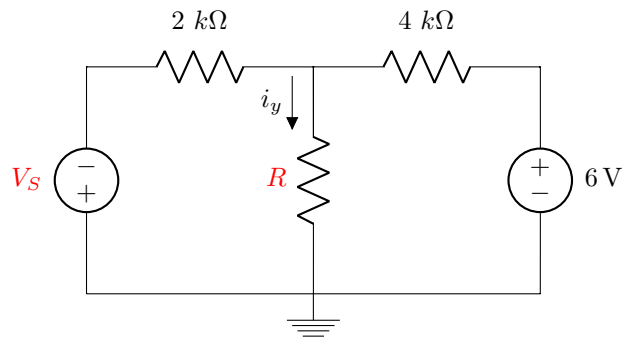Section 3**Question 12 [2]**Given: V_S , R .**12** Use either nodal or mesh analysis to determine i_y . [2]

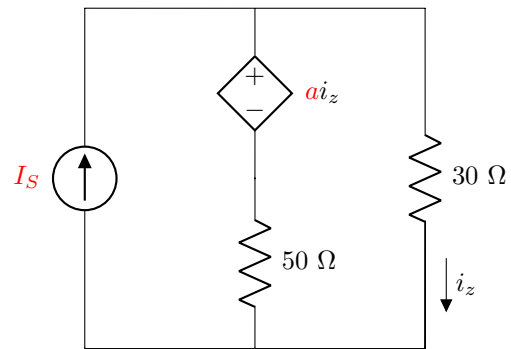Question 13 [2]Given: a , I_S .**13** Use either nodal or mesh analysis to determine i_z . [2]

Questions 14 to 17 [4]

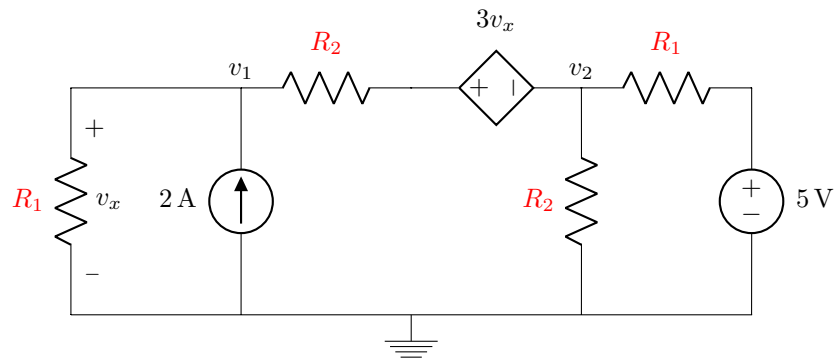Given: R_1 , R_2 .

Use nodal analysis to set up the following two equations of the form:


$$av_1 - R_1v_2 = b$$

$$2R_1v_1 + cv_2 = d.$$

Calculate the unknown coefficients a , b , c and d .

14	a [1]	15	b [1]	16	c [1]	17	d [1]
----	---------	----	---------	----	---------	----	---------

Questions 18 to 21 [4]

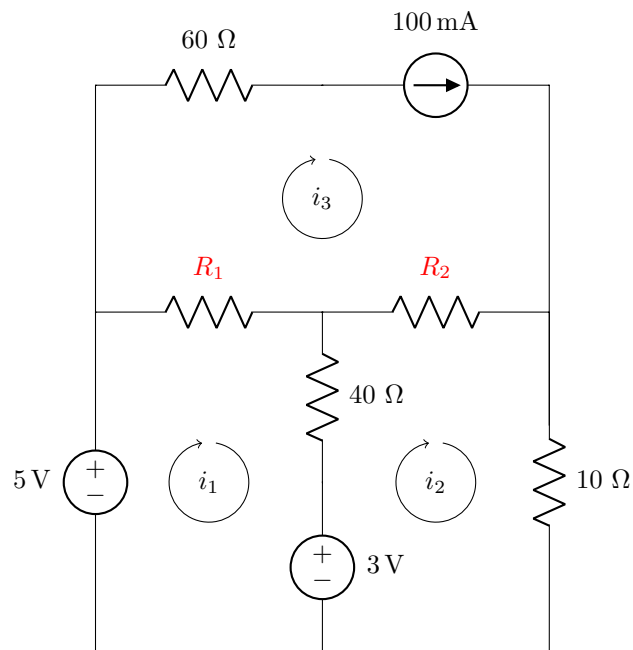Given: R_1 , R_2 .

Use mesh analysis to set up the following two equations of the form:

$$\begin{aligned} ei_1 - 40i_2 &= f \\ -40i_1 + gi_2 &= h \end{aligned}$$

Calculate the unknown coefficients e , f , g and h .

18	e [1]	19	f [1]	20	g [1]	21	h [1]
----	---------	----	---------	----	---------	----	---------


Questions 22 to 23 [4]	
Given: v_2 , a .	
22	Since v_2 is known, determine θ . [2] $\begin{bmatrix} a & -4 \\ 5 & 3 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} 2 \\ \theta \end{bmatrix}$
Given: i_1 .	
23	Since i_1 is known, determine σ . [2] $\begin{bmatrix} 2 & \sigma & -4 \\ -3 & 1 & 0 \\ 0 & 4 & 1 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} 0 \\ -2 \\ 1 \end{bmatrix}$


Questions 24 to 27 [4]

Given: G_1 , G_2 , G_3 .

Use inspection to compile a matrix equation of the form below

$$\begin{bmatrix} G_1 + 10 & -G_1 & -4 & 0 \\ -G_1 & \mathbf{v} & 0 & \mathbf{w} \\ -4 & 0 & G_3 + 4 & -G_3 \\ 0 & \mathbf{w} & -G_3 & \mathbf{x} \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \\ v_4 \end{bmatrix} = \begin{bmatrix} 0 \\ 5 \\ \mathbf{y} \\ -3 \end{bmatrix}$$

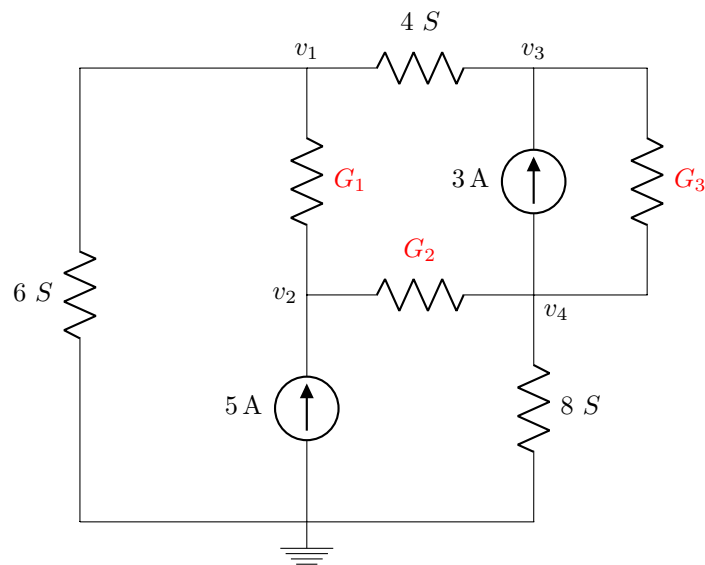and provide the values of the matrix elements $\mathbf{v}$, $\mathbf{w}$, $\mathbf{x}$ and $\mathbf{y}$.24 $\mathbf{v}$ [1]25 $\mathbf{w}$ [1]26 $\mathbf{x}$ [1]27 $\mathbf{y}$ [1]

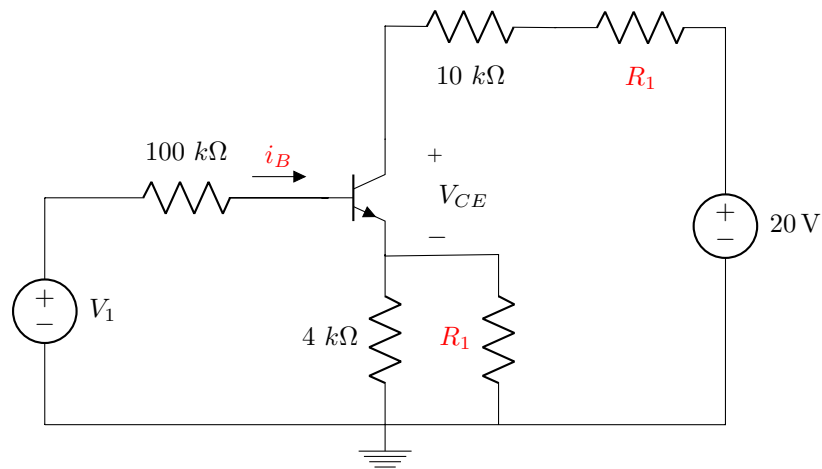Questions 28 to 29 [4]Given: i_B , R_1 .It is known that $\beta = 99$, and $V_{BE} = 0.7$ V.**28** Determine V_1 . [2]**29** Determine V_{CE} . [2]**Total Section 3: [24]****Grand Total : [46]**