
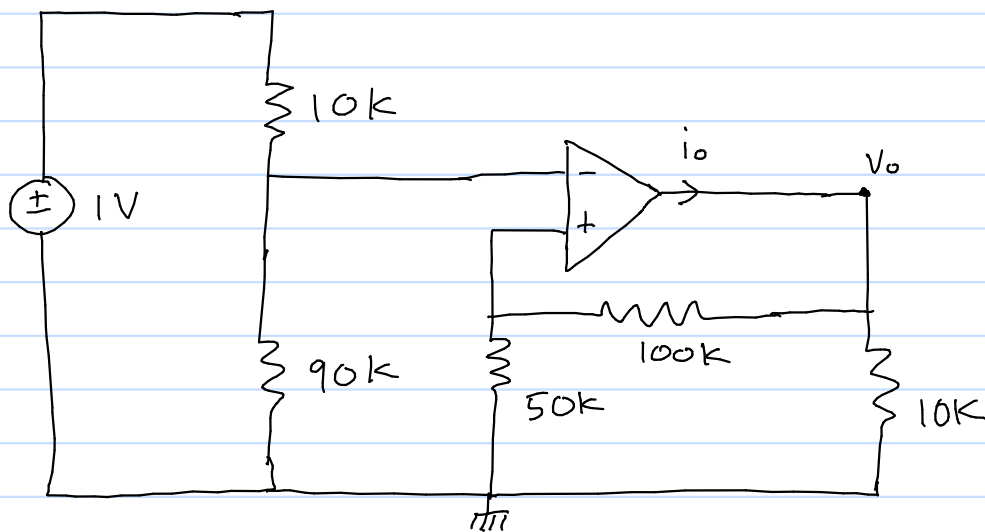




5.13 Find V_o and i_o in the circuit

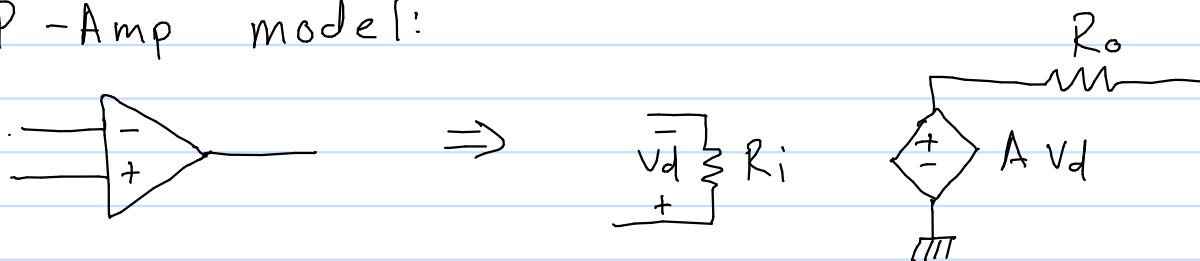

OP -Amp model:




Redraw Circuit :

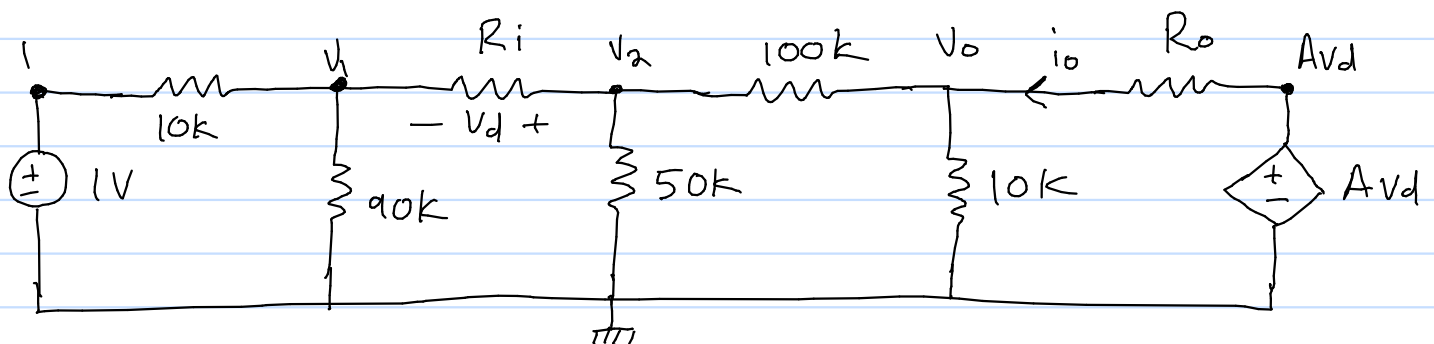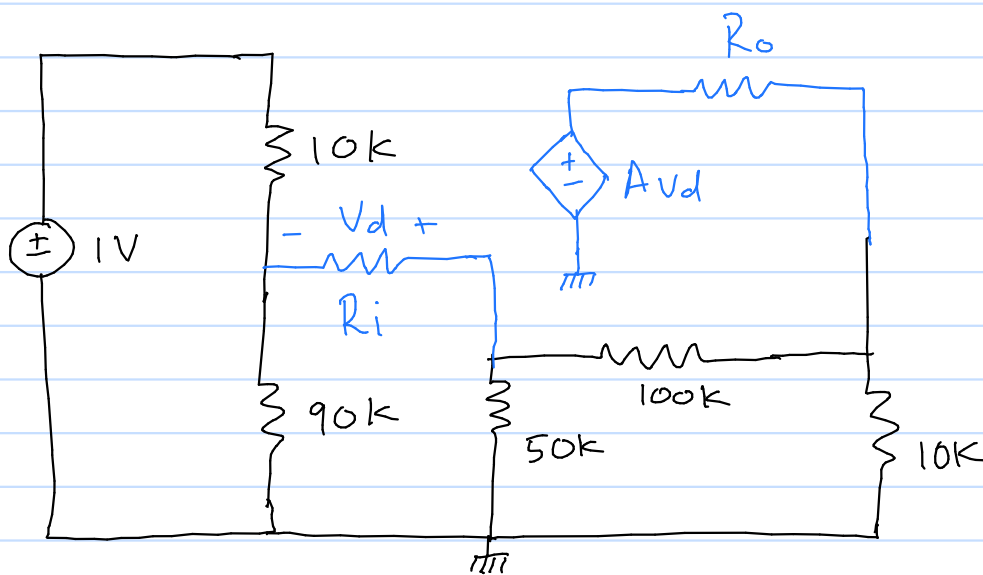

using parameters from 741 op-amp:
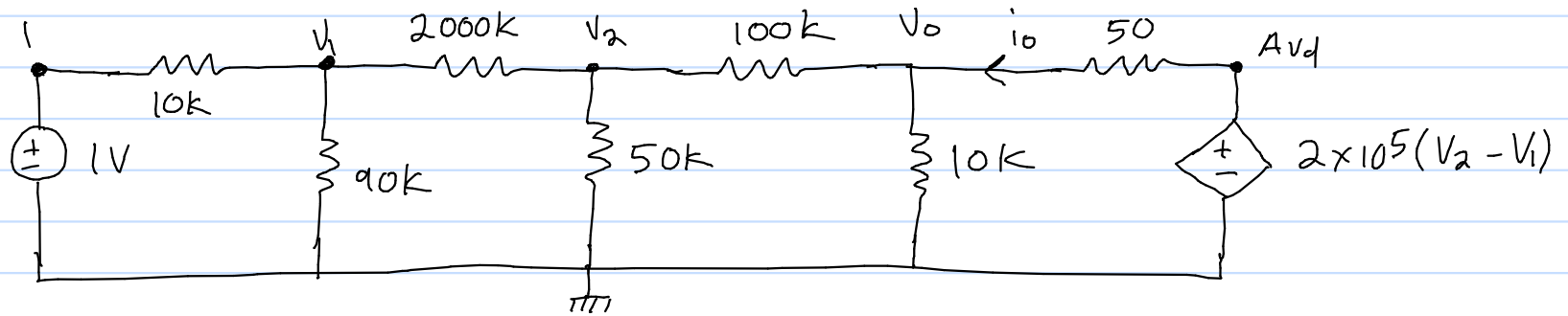
$$A = 2 \times 10^5 \quad R_i = 2 \times 10^6 \Omega \quad R_o = 50$$



Nodal analysis:

$$\textcircled{a} V_1: \frac{V_1 - 1}{10 \times 10^3} + \frac{V_1}{90 \times 10^3} + \frac{V_1 - V_2}{2 \times 10^6} = 0$$

$$200V_1 + \frac{200V_1}{9} + V_1 - V_2 = 200$$

$$\frac{2009V_1}{9} - V_2 = 200$$

$$\textcircled{a} V_2: \frac{V_1 - V_2}{2 \times 10^6} + \frac{V_2}{50 \times 10^3} + \frac{V_2 - V_0}{100 \times 10^3} = 0$$

$$V_1 - V_2 + 40V_2 + 20V_2 - 20V_0 = 0$$

$$V_1 + 59V_2 - 20V_0 = 0$$

$$\textcircled{a} V_0: \frac{V_0 - V_2}{100 \times 10^3} + \frac{V_0}{10 \times 10^3} + \frac{V_0 - A_{vd}}{50} = 0$$

$$\frac{V_0 - V_2}{100 \times 10^3} + \frac{V_0}{10 \times 10^3} + \frac{V_0 - 2 \times 10^5 (V_2 - V_1)}{50} = 0$$

$$V_0 - V_2 + 10V_0 + 2000V_0 - 400 \times 10^6 (V_2 - V_1) = 0$$

$$400 \times 10^6 V_1 - 400000001 V_2 + 2011 V_0 = 0$$

$$\frac{2009V_1}{9} - V_2 = 200$$

$$V_1 + 59V_2 - 20V_0 = 0$$

$$400 \times 10^6 V_1 - 400000001 V_2 + 2011 V_0 = 0$$


Using a calculating to solve equations:

$$V_1 = 0.9000000611$$

$$V_2 = 0.9000136333$$

$$V_0 = 2.700040221$$

5.13 Find V_o and i_o in circuit:

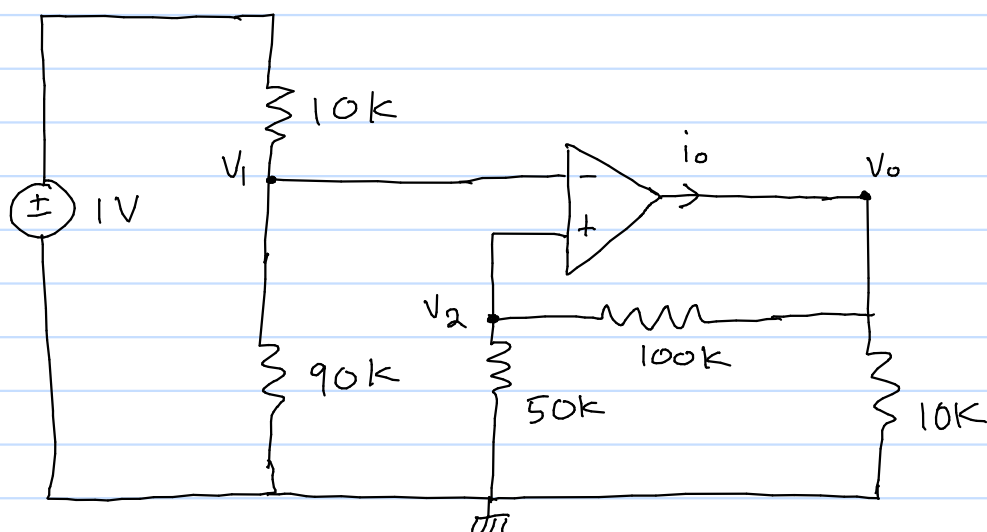

ideal op-amp $V_1 = V_2$ $i_1 = i_2 = 0$

V_1 using voltage division:

$$V_1 = \frac{1 \times 90 \times 10^3}{10 \times 10^3 + 90 \times 10^3} = 0.9 \text{ V}$$

V_2 using voltage division:

$$V_2 = \frac{V_o \times 50 \times 10^3}{50 \times 10^3 + 100 \times 10^3}$$

$$V_2 = \frac{V_o}{3}$$

since $V_2 = V_1$

$$0.9 = \frac{V_o}{3}$$

$$V_o = 2.7$$

OP-Amp model vs ideal model:

$$2.700040221 - 2.7 = 0.000040221 \approx 0$$