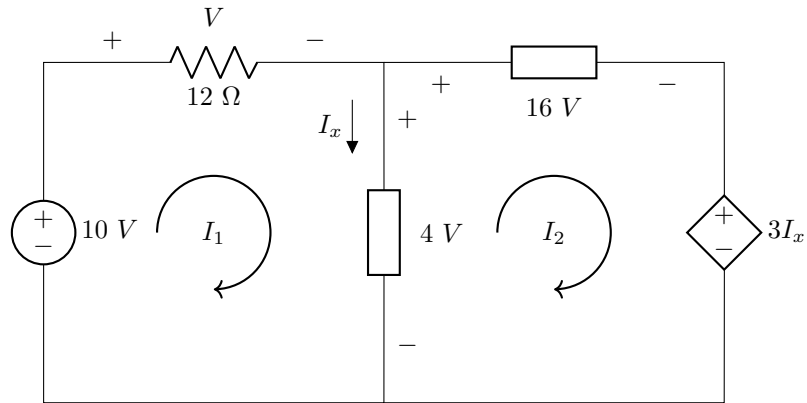



Tutorial 2

Question 2.15

Find V and I_x 


Question 2.22

Find V_o and power over the $2V_o$ source

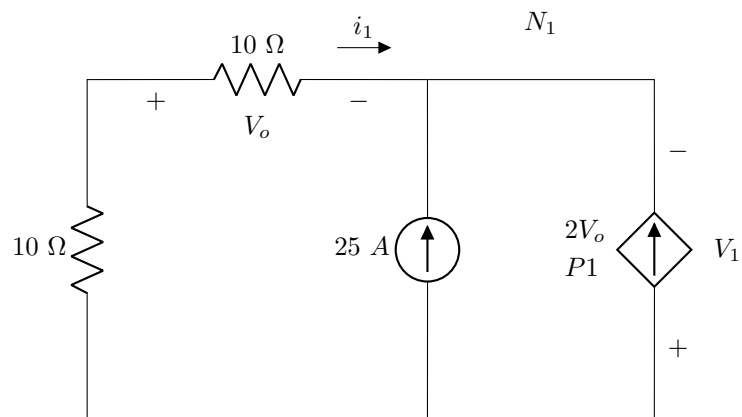


Question 2.23

In the circuit below, determine V_x and the power absorbed by the $12\ \Omega$ resistor.

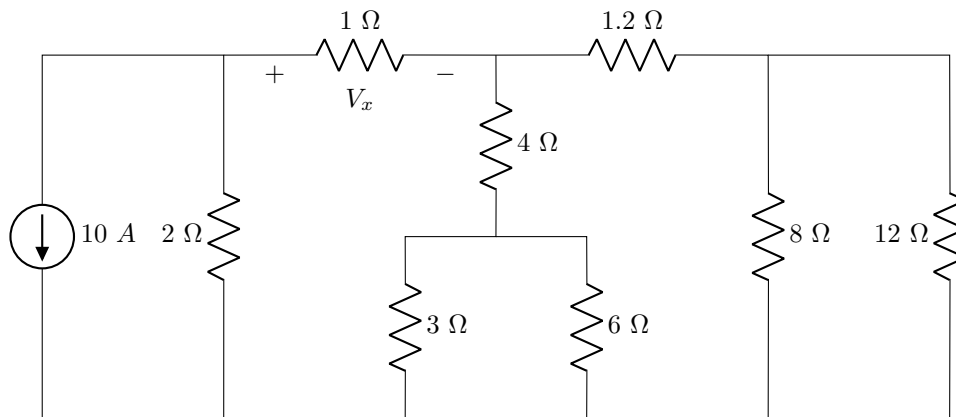


Question 2.25

Find $V_{20k\Omega}$, $i_{20k\Omega}$ and $P_{20k\Omega}$

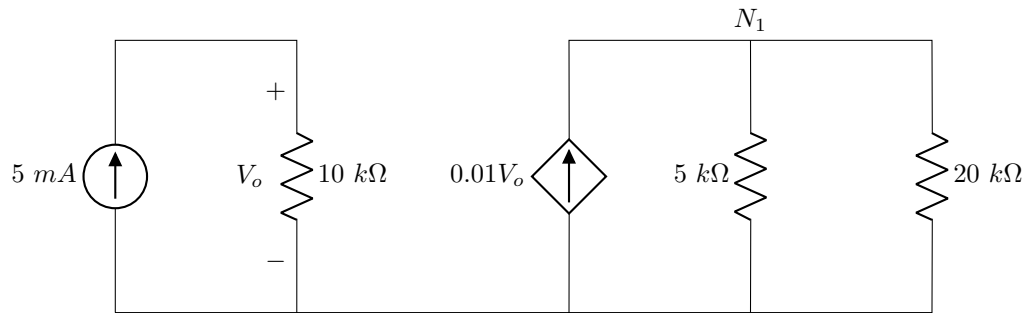


Question 2.32

Find i_1, i_2, i_3 and i_4 .

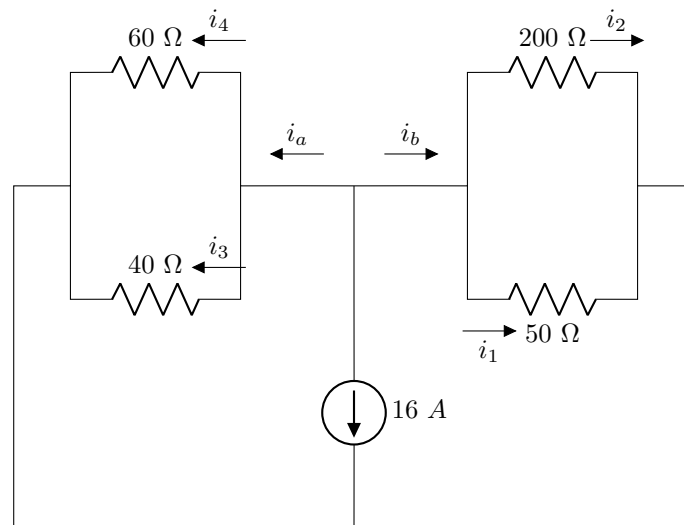


Question 2.45b

Find R_{eq} between terminals $a - b$

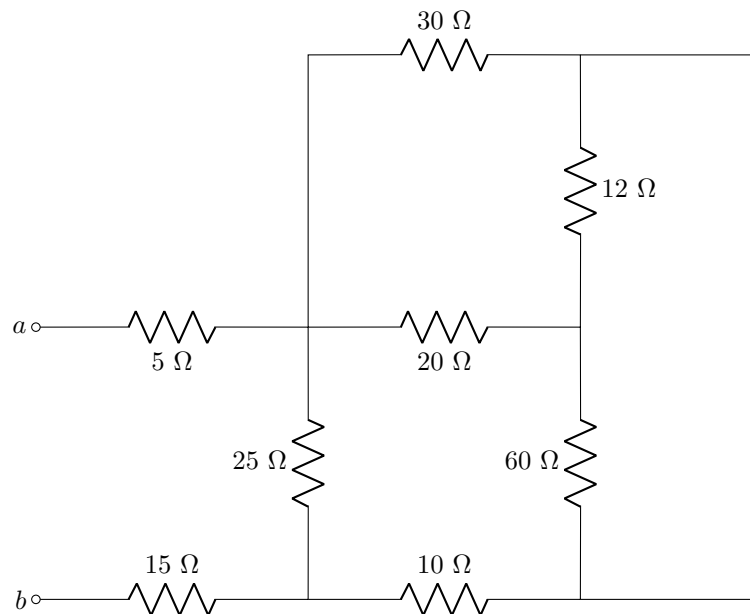

Question 2.51b

Determine the equivalent resistance across $a - b$.

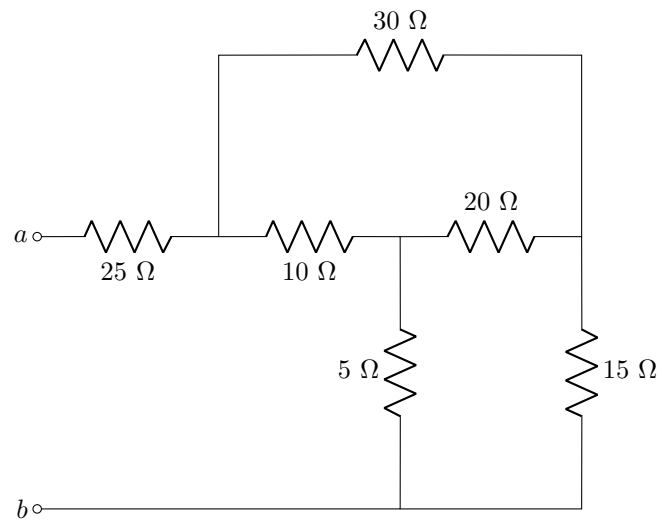

Question 2.53b

Determine the equivalent resistance across $a - b$ if all the elements are $30\ \Omega$.

