
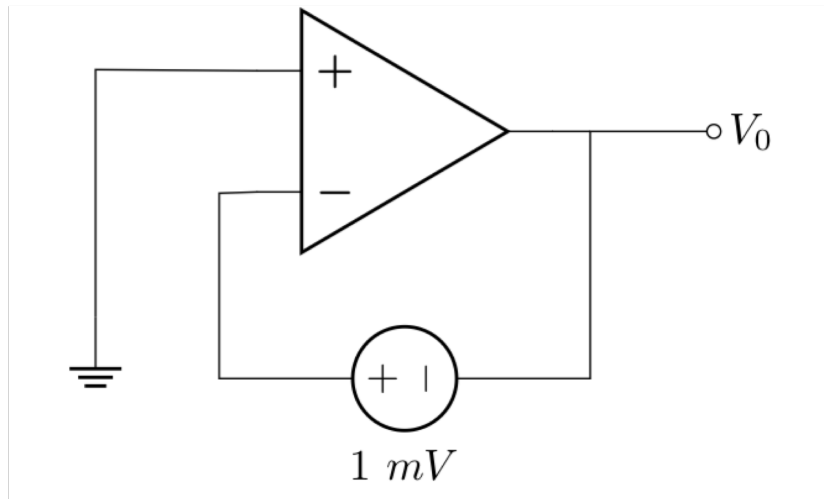


Tutorial 6

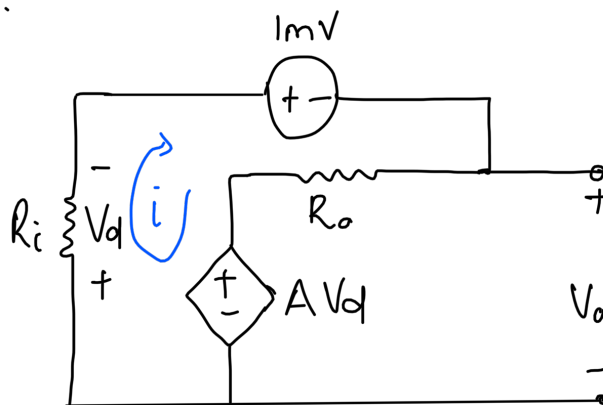5.6 Determine V_o if this is a 741 Opamp (it is not ideal)



Redraw as:



$$A = 2 \times 10^5$$

$$R_i = 2 \text{ M}\Omega$$

$$R_o = 50 \Omega$$

$$V_d = R_i \cdot i$$
$$= 2 \times 10^6 i$$

KVL:

$$2 \times 10^6 i + 1 \times 10^{-3} + 50 i + 2 \times 10^5 V_d = 0$$

$$i [2 \times 10^6 + 50 + (2 \times 10^5)(2 \times 10^6)] = -1 \times 10^{-3}$$

$$i = -24.99987 \times 10^{-16}$$


$$= -2.5 \text{ fA}$$

$$-A V_d + i R_o + V_o = 0$$

$$V_o = (2 \times 10^5)(2 \times 10^6)(-2.5 \times 10^{-15}) - (-2.5 \times 10^{-15})(50) \\ = -1 \text{ mV}$$

5.8 Determine V_o

(a)

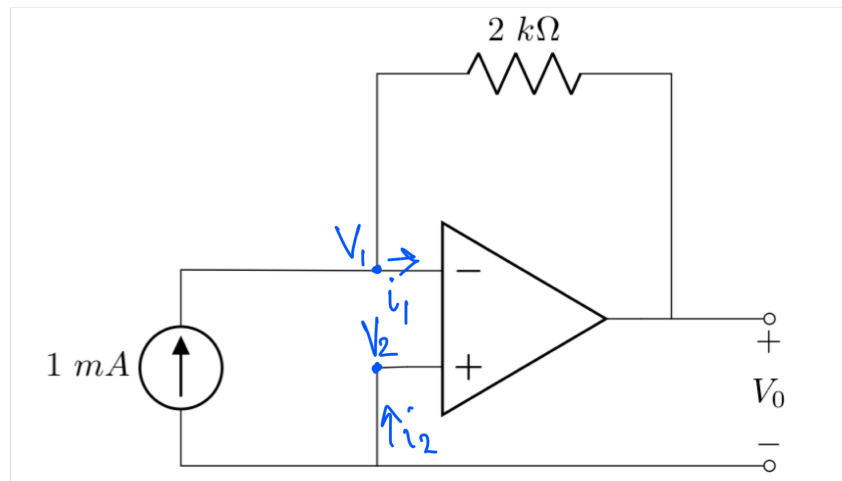

⇒ Ideal op-amp

$$i_1 = 0 ; i_2 = 0$$

$$V_1 = V_2$$

$$V_1 = V_2 = 0\text{ V}$$


@ Node V_1

$$-1 \times 10^{-3} + \frac{V_1 - V_o}{2000} = 0$$

$$\frac{-V_o}{2000} = 1 \times 10^{-3}$$

$$V_o = -2\text{ V}$$

(b)

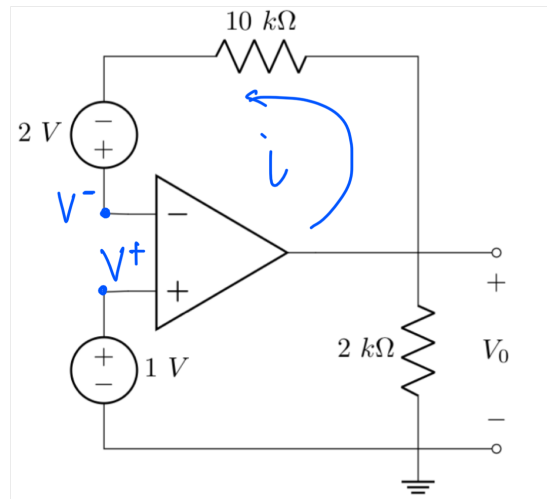

$$V_1 = V_2 = 1V$$

For an ideal op-amp $i = 0A$


$$\therefore V_{10k\Omega} = 0 \text{ (10 000)} \\ = 0V$$

$$V^- = V_0 + 2$$

$$V_0 = 1 - 2 \\ = -1V$$

5.9 Determine V_o

(a)

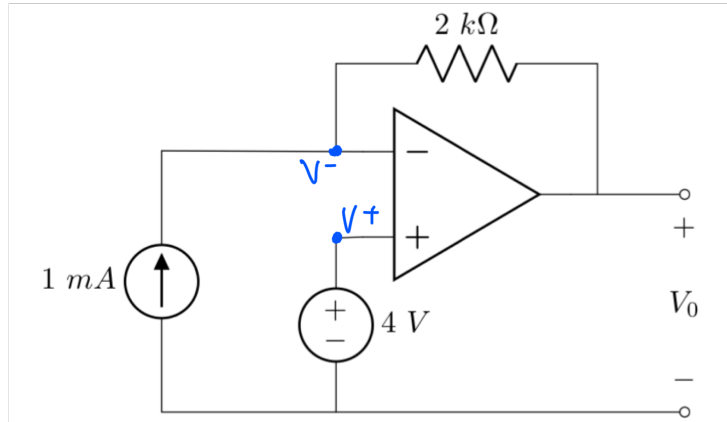

Ideal op-amp :

$$V^+ = V^- = 4V$$

Node V^- :


$$-1 \times 10^{-3} + \frac{V^- - V_o}{2000} = 0$$

$$1 - V_o = 2$$

$$-V_o = 2 - 4$$

$$V_o = 2V$$

(b)

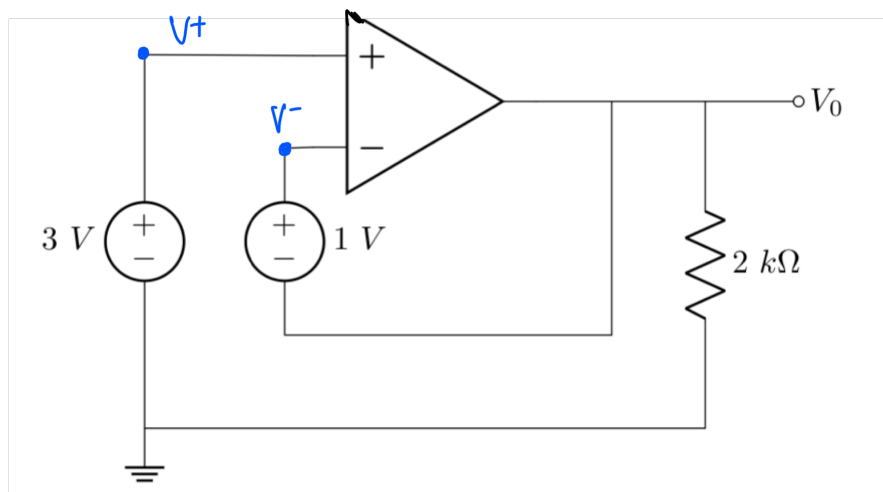


$$V^+ = V^- = 3V$$

$$V_o = V^- - 1$$

$$= 3 - 1$$

$$= 2V$$

5.13 Determine I_0

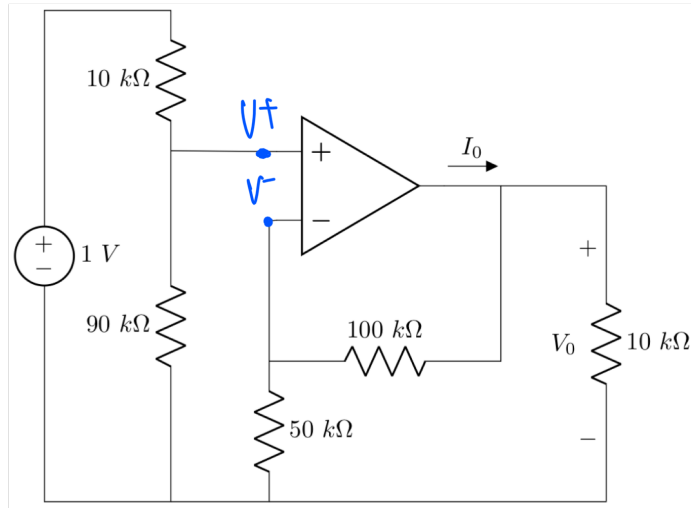

Ideal op-amp:

⇒ Voltage division

$$V^+ = 1 \times \frac{90\,000}{90\,000 + 10\,000}$$

$$= 0.9 \text{ V}$$

$$V^+ = V^-$$

⇒ Node @ V^-

$$\frac{V^- - V_0}{100\,000} + \frac{V^-}{50\,000} = 0$$

$$\frac{0.9 - V_0}{100\,000} + \frac{0.9}{50\,000} = 0$$


$$V_0 = 2.7 \text{ V}$$

⇒ Nodal @ V_o

$$-I_o + \frac{V_o - V^-}{100\ 000} + \frac{V_o}{10\ 000} = 0$$

$$I_o = \frac{2.7 - 0.9}{100\ 000} + \frac{2.7}{10000}$$
$$= 288\ \mu A$$

5.20 Determine V_o

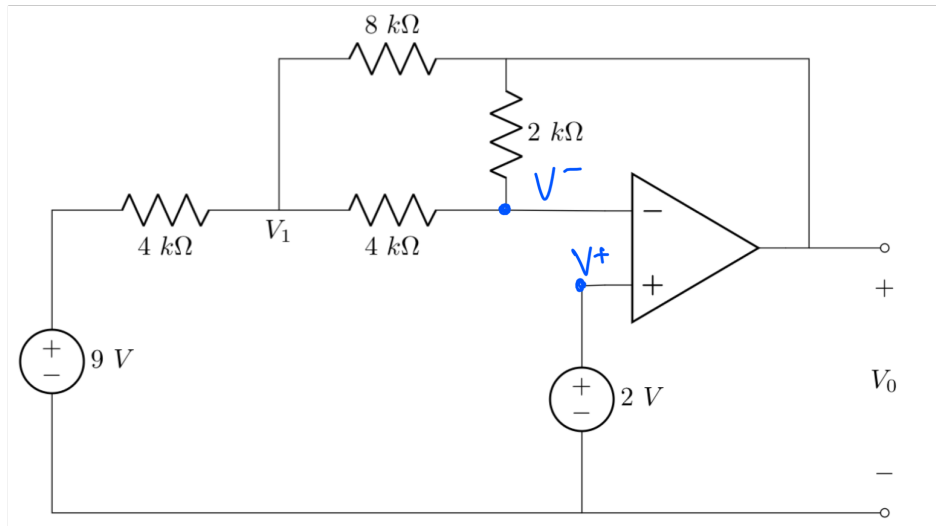

⇒ Ideal op-amp
 $V^+ = V^- = 2\text{ V}$

⇒ Nodal analysis node V_1

$$\frac{V_1 - 9}{4000} + \frac{V_1 - V^-}{4000} + \frac{V_1 - V_o}{8000} = 0$$
$$5V_1 - V_o = 22$$


⇒ Nodal analysis node V^-

$$\frac{V^- - V_1}{4000} + \frac{V^- - V_o}{2000} = 0$$
$$V_1 + 2V_o = 6$$

⇒ Solve

$$V_o = 0.727\text{ V}$$

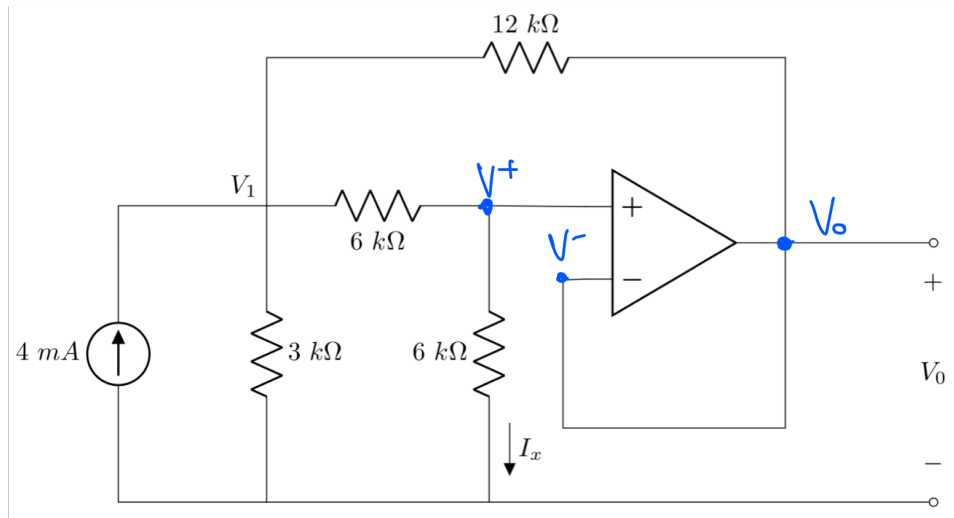- 5.31 (a) Determine V_o
 (b) Determine I_x



$$V^- = V_o$$

$$V^+ = V^- = V_o$$

$\Rightarrow$ Nodal at V_1 :

$$\frac{V_1}{3000} + \frac{V_1 - V^+}{6000} + \frac{V_1 - V_o}{12000} - 4 \times 10^{-3} = 0$$

$$\frac{V_1}{3000} + \frac{V_1 - V_o}{6000} + \frac{V_1 - V_o}{12000} = 4 \times 10^{-3}$$

$$7V_1 - 3V_o = 48 \quad (1)$$

$\Rightarrow$ Nodal at V^+ :

$$\frac{V^+ - V_1}{6000} + \frac{V^+}{6000} = 0$$

$$V_0 - V_1 + V_0 = 0$$

$$2V_0 = V_1$$

②

$\Rightarrow$ ② in ①

$$7(2V_0) - 3V_0 = 48$$


$$14V_0 - 3V_0 = 48$$

$$V_0 = 4.8636 \text{ V}$$

$$\begin{aligned} \Rightarrow I_x &= \frac{V^+}{6000} \\ &= \frac{4.8636}{6000} \end{aligned}$$

$$= 727.2727 \mu\text{A}$$

5.32 Determine I_x and V_o

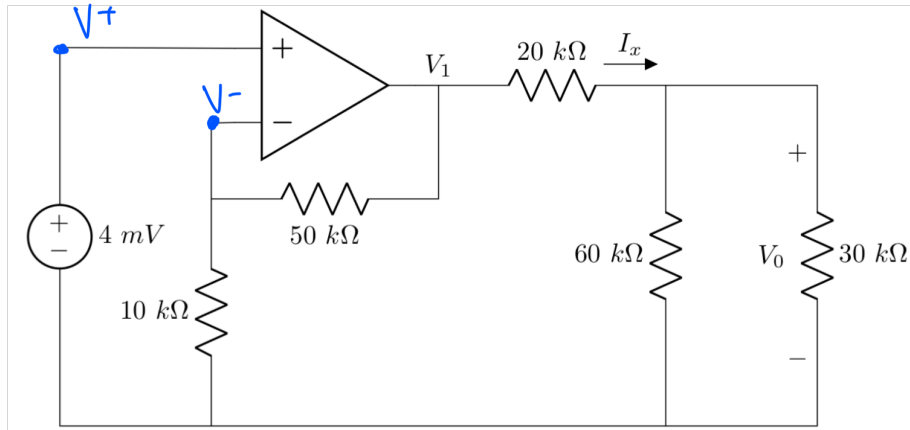

Ideal op-amp
 $V^+ = V^- = 4 \text{ mV}$

⇒ Nodal at V^-

$$\frac{4 \times 10^{-3} - V_1}{50000} + \frac{4 \times 10^{-3}}{10000} = 0$$

$$V_1 = 24 \text{ mV}$$

⇒ Nodal at V_o


$$\frac{V_o}{30000} + \frac{V_o}{60000} + \frac{V_o - V_1}{20000} = 0$$

$$V_o = 12 \text{ mV}$$

$$\Rightarrow I_x = \frac{V_1 - V_o}{20000}$$

$$= \frac{24 \times 10^{-3} - 12 \times 10^{-3}}{20 \times 10^3} = 0.6 \mu\text{A}$$

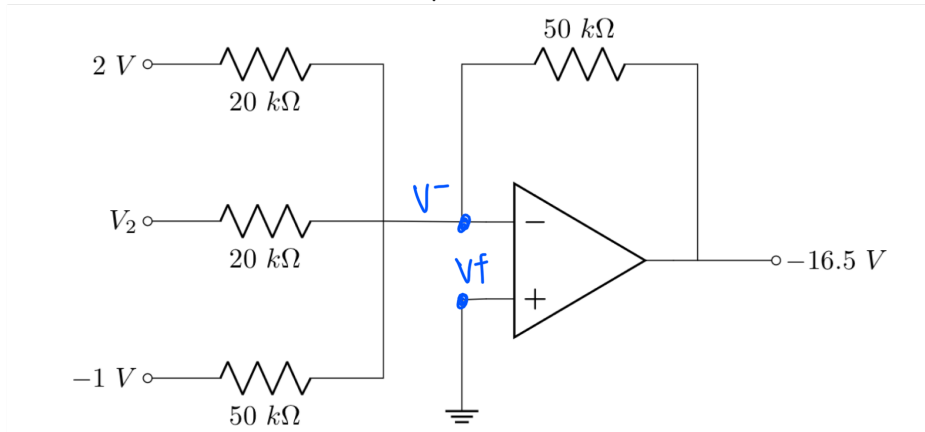5.39 Determine V_{TH} and R_{TH} across a-b



Ideal op-amp :
 $V^+ = V^- = 0V$

⇒ Node at V^-


$$\frac{V^- - (-16.5)}{50\ 000} + \frac{V^- - (-1)}{50\ 000} + \frac{V^- - 2}{20\ 000} + \frac{V^- - V_2}{20\ 000} = 0$$

$$\frac{16.5}{50\ 000} + \frac{1}{50\ 000} - \frac{2}{20\ 000} - \frac{V_2}{20\ 000} = 0$$

$$V_2 = 5V$$

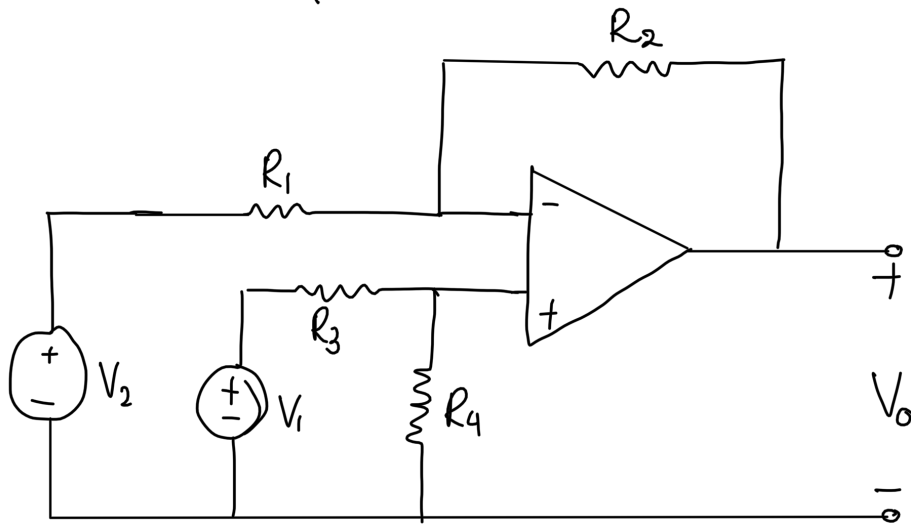5.45 Design an op-amp circuit with the following I-o relationship: $V_o = 3V_1 - 2V_2$

⇒ Only known op-amp circuit that does this is the differential amplifier.



Use Eq. 5.18 with V_1 and V_2 swapped:

$$V_o = \frac{R_2 \left(1 + \frac{R_1}{R_2} \right)}{R_1 \left(1 + \frac{R_3}{R_4} \right)} V_1 - \frac{R_2}{R_1} V_2 \quad (2)$$

$$V_o = 3V_1 - 2V_2 \quad (1)$$

$$\frac{R_2}{R_1} = 2 \quad (3) \quad \frac{R_2 \left(1 + \frac{R_1}{R_2} \right)}{R_1 \left(1 + \frac{R_3}{R_4} \right)} = 3 \quad (4)$$


Select any values for R_1 and R_4
 $\rightarrow$ Let $R_1 = 1\text{ k}\Omega$ $R_4 = 1\text{ k}\Omega$

$$\textcircled{3} \quad \therefore R_2 = 2 R_1 \\ = 2\text{ k}\Omega$$

$$\textcircled{4} \quad \frac{2 \times 10^3 \left(1 + \frac{1 \times 10^3}{2 \times 10^3} \right)}{1 \times 10^3 \left(1 + \frac{R_3}{1 \times 10^3} \right)} = 3$$

$$R_3 = 0$$

5.57 Determine V_o

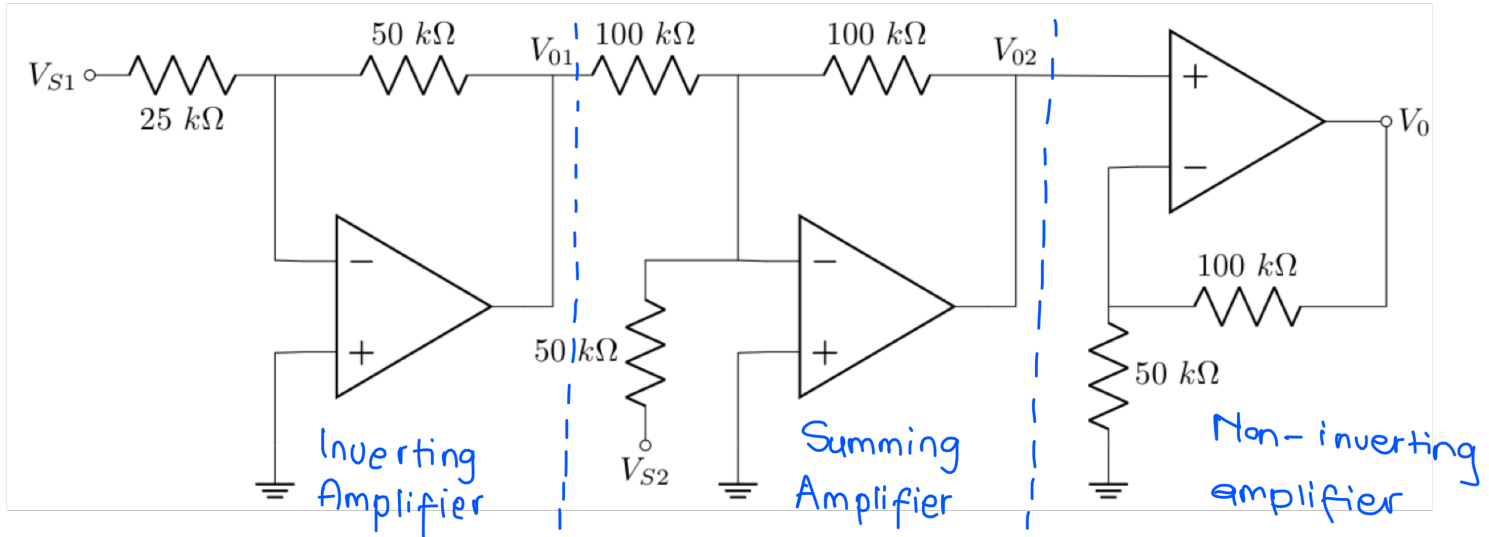

⇒ Inverting Amplifier

$$V_{01} = -\frac{50\text{ k}\Omega}{25\text{ k}\Omega} \cdot V_{S1}$$

$$= -2 V_{S1}$$

⇒ Summing Amplifier

$$V_{02} = -\left(\frac{100}{100}(-2V_{S1}) + \frac{100}{50}(V_{S2})\right)$$

$$= -(-2V_{S1} + 2V_{S2})$$


$$= 2V_{S1} - 2V_{S2}$$

⇒ Non-inverting amplifier

$$V_o = \left(1 + \frac{100}{50}\right)(2V_{S1} - 2V_{S2})$$

$$= 6(V_{S1} - V_{S2})$$

5.70 Determine V_0

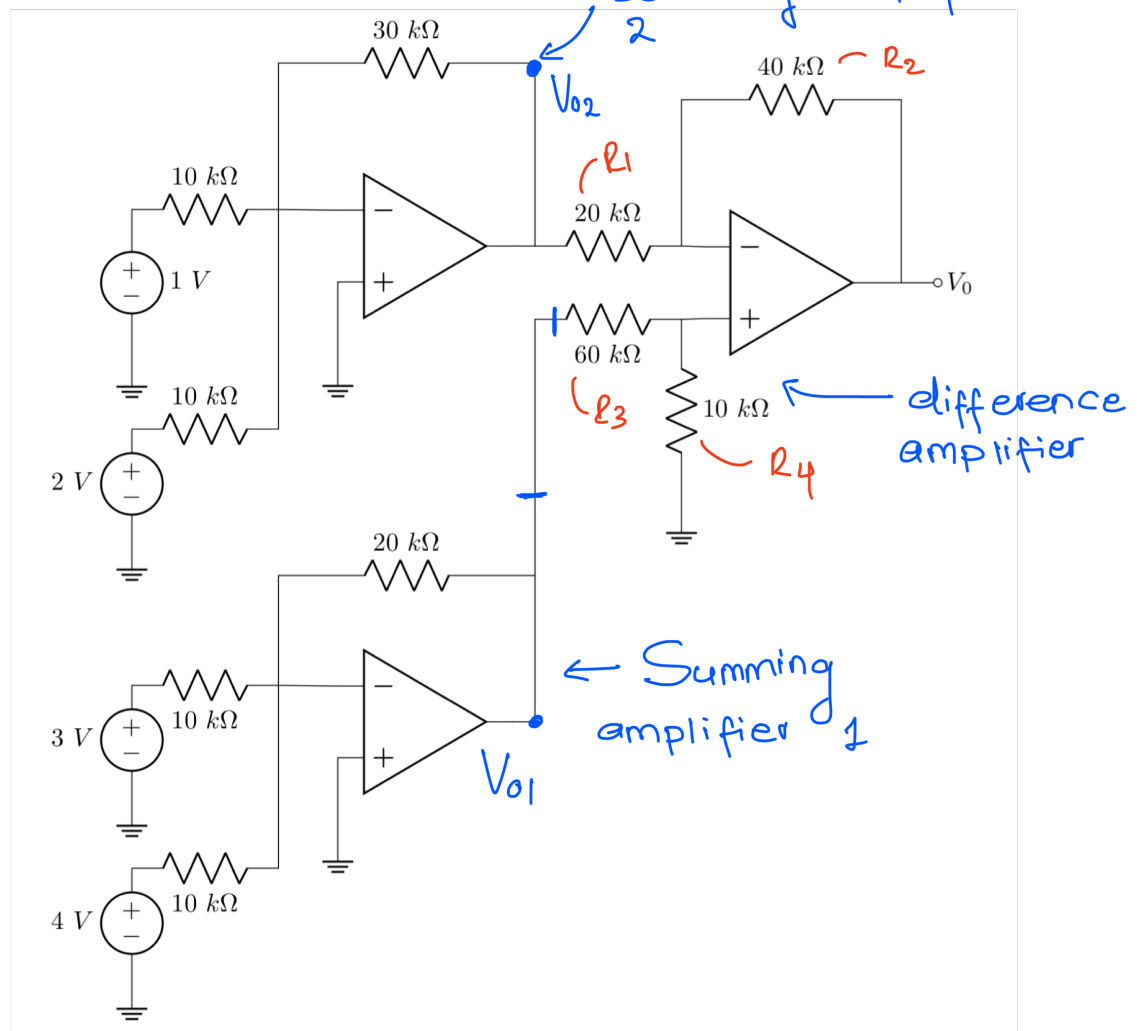

⇒ Summing amplifier 1

$$\begin{aligned}
 V_{01} &= - \left(\frac{R_f}{R_1} V_1 + \frac{R_f}{R_2} V_2 \right) \\
 &= - \left(\frac{20 \times 10^3}{10 \times 10^3} (3) + \frac{20 \times 10^3}{10 \times 10^3} (4) \right) \\
 &= -14 \text{ V}
 \end{aligned}$$

⇒ Summing amplifier 2

$$V_{o2} = - \left(\frac{30 \times 10^3}{10 \times 10^3} (1) + \frac{30 \times 10^3}{10 \times 10^3} (2) \right) \\ = -9 \text{ V}$$

⇒ Difference amplifier

$$V_o = \frac{R_2 \left(1 + \frac{R_1}{R_2} \right)}{R_1 \left(1 + \frac{R_3}{R_4} \right)} \cdot V_{o1} - \frac{R_2}{R_1} \cdot V_{o2} \\ = \frac{40 \times 10^3 \left(1 + \frac{20 \times 10^3}{40 \times 10^3} \right)}{20 \times 10^3 \left(1 + \frac{60 \times 10^3}{10 \times 10^3} \right)} \cdot (-14) - \frac{40 \times 10^3}{20 \times 10^3} \cdot (-9) \\ = 12 \text{ V}$$