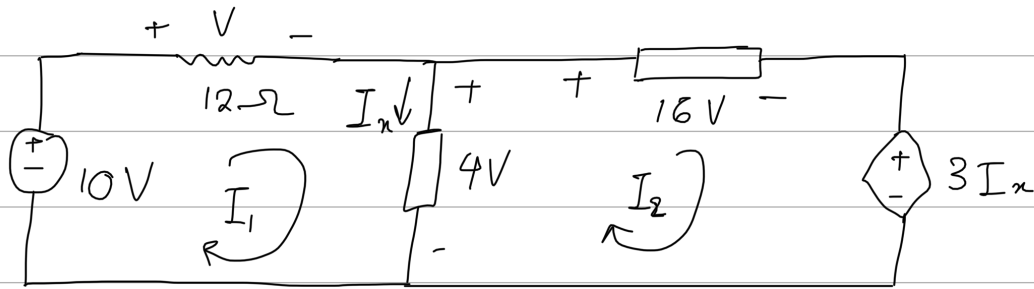


2 March

Tutorial 2

2.15 Find V and I_x



KVL Eq 2.19 $\sum_{m=1}^M V_m = 0$

$\Rightarrow$ Loop I_1

$$-10 + V + 4 = 0$$

$$V = 10 - 4$$

$$= 6 \text{ V}$$

$\Rightarrow$ Loop I_2


$$-4 + 16 + 3I_x = 0$$

$$3I_x = -16 + 4$$

$$I_x = \frac{-12}{3}$$

$$I_x = -4 \text{ A}$$

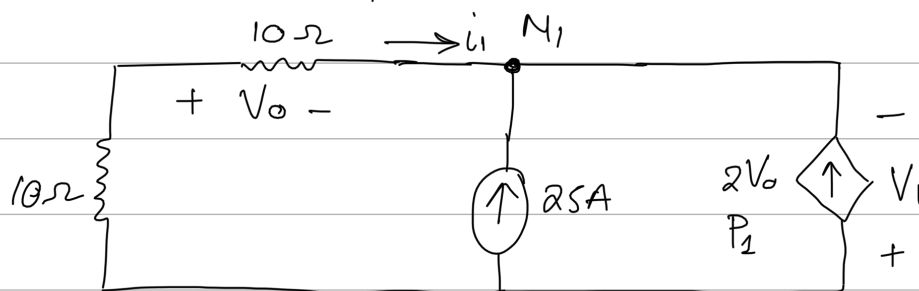2.22 Find V_o and power over the $2V_o$ source



Apply KCL Eq 2.13 $\sum_{n=1}^N i_n = 0$

$$\Rightarrow V_o = i_1 R_{10\Omega} \quad (1)$$

$$i_1 + 25 + 2V_o = 0 \quad (2)$$

Substitute (2) into (1)

$$\therefore V_o = (-25 - 2V_o) \cdot 10$$

$$V_o = -250 - 20 V_o$$

$$21 V_o = -250$$

$$V_o = -11.904 \text{ V}$$

$$\Rightarrow P = V i \quad \text{Eq 1.7}$$

$$i = 2V_o$$


$$= 2(-11.904)$$

$$= -23.808 \text{ A}$$

$$\begin{aligned} V &= i_1 R_{eq} \quad \text{where} \quad R_{eq} = 10 + 10 \\ &= [-25 - 2(-11.904)](20) \quad = 20 \Omega \\ &= -23.84 \text{ V} \end{aligned}$$

$$\begin{aligned} \therefore P_1 &= V i \\ &= (-23.84)(-23.808) \\ &= 567.583 \text{ W} \end{aligned}$$

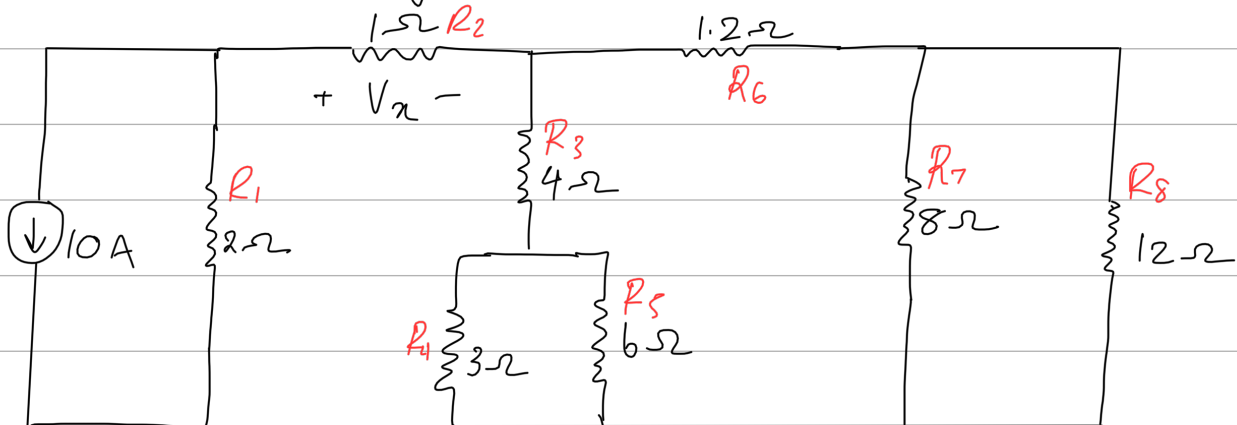2.23 In the circuit below, determine V_x and the power absorbed by the $12\text{-}\Omega$ resistor




$$R_7 \parallel R_8 \quad \& \quad R_4 \parallel R_5$$

From Eq 2.37
$$R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$$

$$\therefore R_7 \parallel R_8 = \frac{8(12)}{8+12} = 4.8\text{-}\Omega$$

$$R_4 \parallel R_5 = \frac{3(6)}{3+6} = 2\text{-}\Omega$$

Redraw :

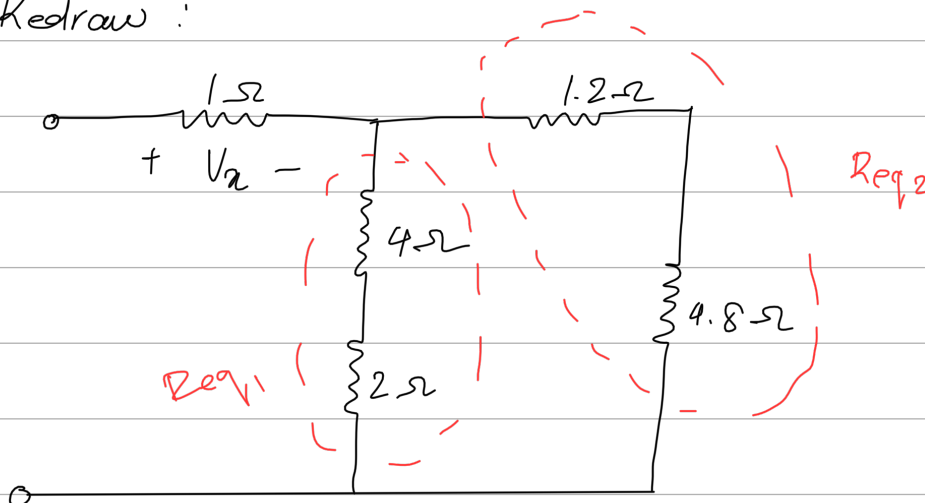

$$R_{eq1} = 4 + 2$$


$$= 6 \Omega$$

$$R_{eq2} = 1.2 + 4.8$$

$$= 6 \Omega$$

$$R_{eq1} \parallel R_{eq2} = \frac{6(6)}{6+6}$$

$$= 3 \Omega$$

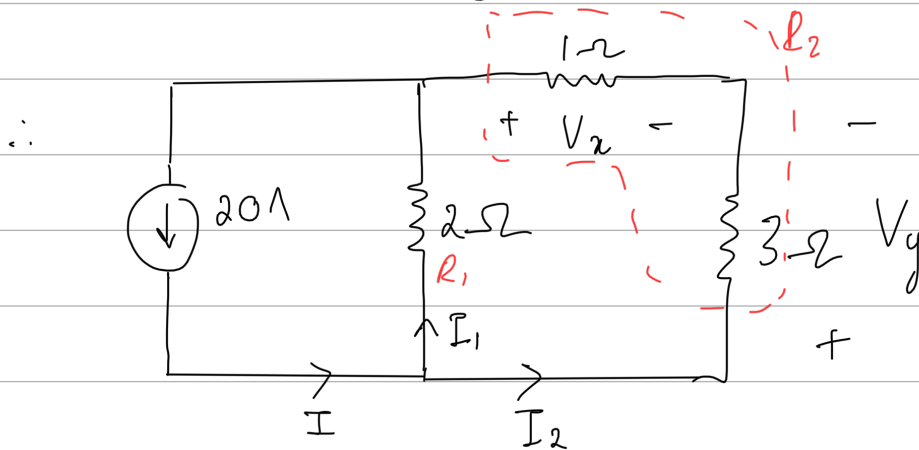

Apply current division Eq 2.43


$$I_2 = I \cdot \frac{R_1}{R_1 + R_2}$$

$$= 20 \cdot \frac{2}{2 + (1+3)}$$

$$= 6.667 \text{ A}$$

$$\begin{aligned}
 V_x &= -I_2 R \\
 &= -6.667 (1) \\
 &= -6.667 \text{ V}
 \end{aligned}$$

$$\Rightarrow P = V_i = \frac{V^2}{R}$$

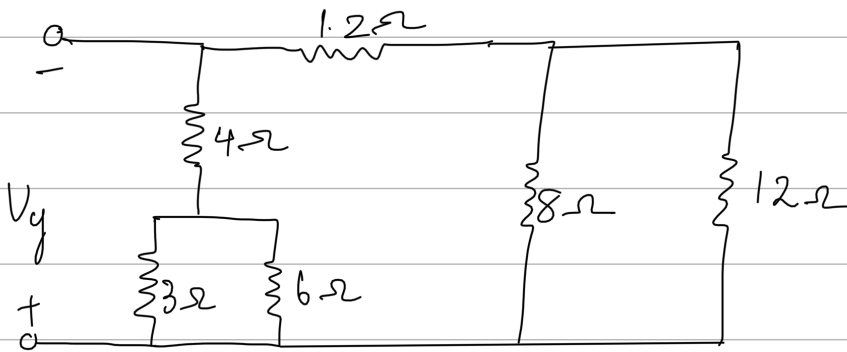


$$\begin{aligned}
 V_y &= I_2 \cdot R \\
 &= 6.667 (3) \\
 &= 20 \text{ V}
 \end{aligned}$$

Voltage division

$$\begin{aligned}
 V_{12} &= \frac{8 // 12}{8 // 12 + 1.2} \cdot 20 \\
 &= 16 \text{ V}
 \end{aligned}$$

$$\begin{aligned}
 P_{12} &= \frac{16^2}{12} \\
 &= 21.33 \text{ W}
 \end{aligned}$$

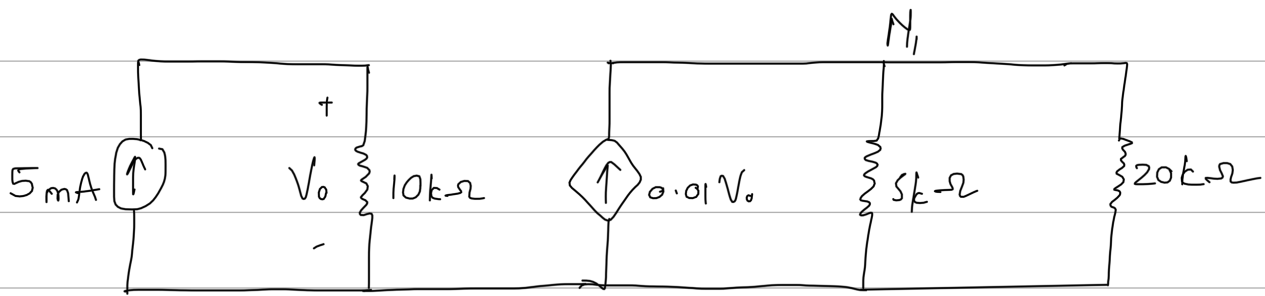2.25 Find $V_{20k\Omega}$; $i_{20k\Omega}$ and $P_{20k\Omega}$



Apply current division

$$i_{20k\Omega} = i \frac{R_{5k\Omega}}{R_{5k\Omega} + R_{20k\Omega}}$$

$$i_{20k\Omega} = 0.01V_o \left(\frac{5000}{5000 + 20000} \right)$$

$$i_{20k\Omega} = 0.002V_o \quad \dots \quad (1)$$

$$\begin{aligned} V_o &= iR \\ &= (5 \times 10^{-3})(10000) \\ &= 50V \quad \dots \quad (2) \end{aligned}$$


Substitute (2) into (1)

$$\begin{aligned} \therefore i_{20k\Omega} &= 0.002(50) \\ &= 0.1A \\ &= 100mA \end{aligned}$$

$$\begin{aligned}V_{20k\Omega} &= i_{20k\Omega} R_{20k\Omega} \\&= 0.1 (20\,000) \\&= 2000\,V \\&= 2\,kV\end{aligned}$$

$$\begin{aligned}P_{20kV} &= V_{20k\Omega} i_{20k\Omega} \\&= (2000)(0.1) \\&= 200\,W\end{aligned}$$

2.32 Find i_1, i_2, i_3 and i_4

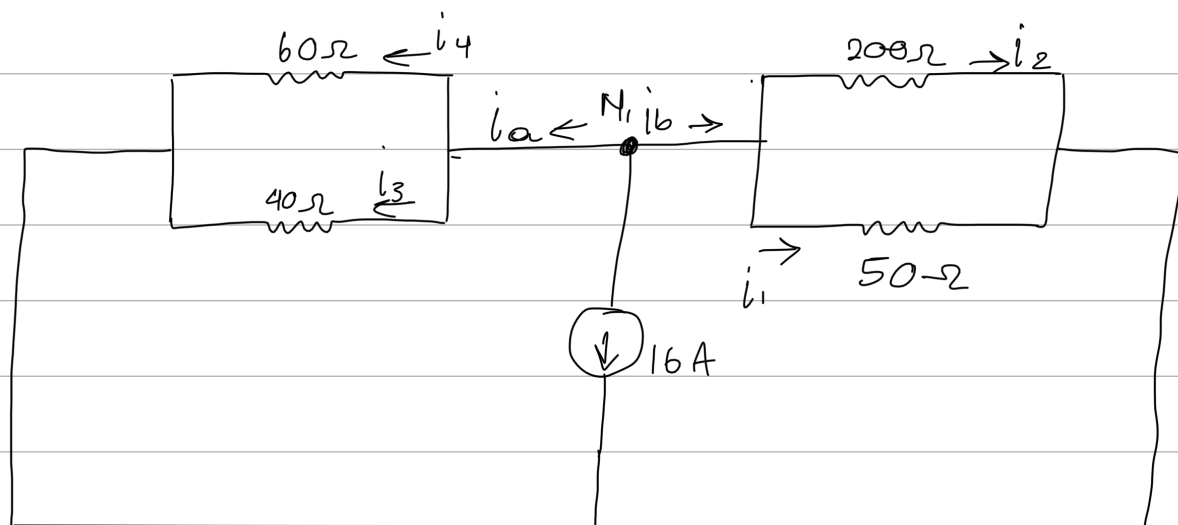


$$i_a = i_3 + i_4 \quad \text{and} \quad i_b = i_1 + i_2$$

Redraw:

$$\begin{aligned} R_a &= 60 // 40 \\ &= \frac{60(40)}{60+40} \\ &= 24 \Omega \end{aligned}$$
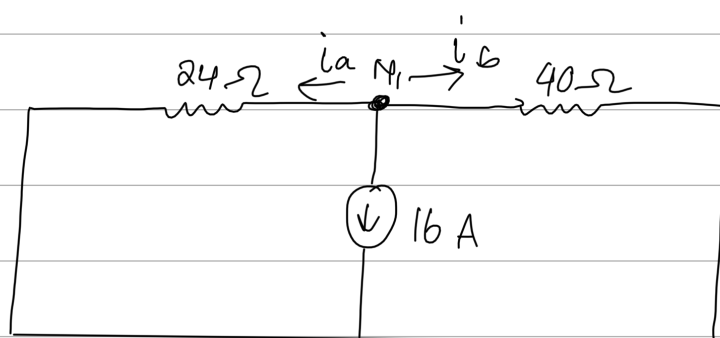
$$\begin{aligned} R_b &= 200 // 50 \\ &= \frac{200(50)}{200+50} \\ &= 40 \Omega \end{aligned}$$



$$\text{KCL} \Rightarrow i_a + i_b + 16 = 0$$

$$16 = -i_a - i_b$$


$\therefore i_a$ & i_b are -ve

Current division

$$\begin{aligned} i_a &= -i \frac{R_b}{R_a + R_b} \\ &= -16 \cdot \frac{40}{24 + 40} \\ &= -10 \text{ A} \end{aligned}$$

$$\begin{aligned} i_b &= -i \frac{R_a}{R_a + R_b} \\ &= -16 \cdot \frac{24}{24 + 40} \\ &= -6 \text{ A} \end{aligned}$$


For i_a ; using current division

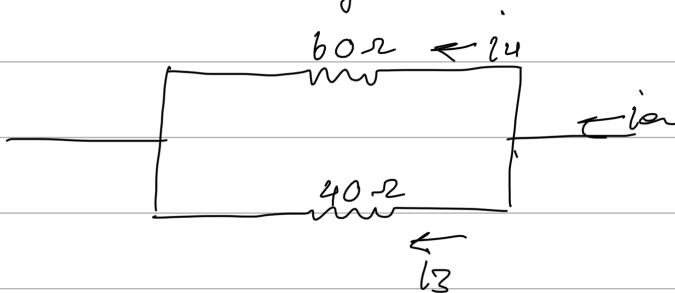

$$\begin{aligned} i_3 &= i_a \frac{60}{40 + 60} \\ &= -10 \cdot \frac{60}{100} \\ &= -6 \text{ A} \end{aligned}$$

$$\begin{aligned} i_a &= i_3 + i_4 \\ i_4 &= i_a - i_3 \\ &= -10 - (-6) \\ &= -4 \text{ A} \end{aligned}$$

For i_b

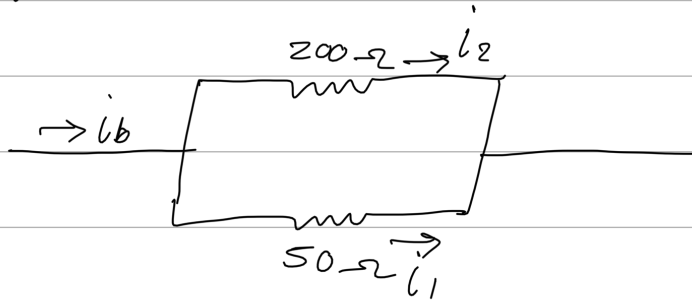

$$i_1 = i_b \frac{200}{200 + 50}$$

$$= -6 \cdot \frac{200}{250}$$

$$= -4.8\text{ A}$$


$$i_b = i_1 + i_2$$

$$i_2 = i_b - i_1$$

$$= -6 - (-4.8)$$


$$= -1.2\text{ A}$$

2.45b Find R_{eq} between terminals a-b

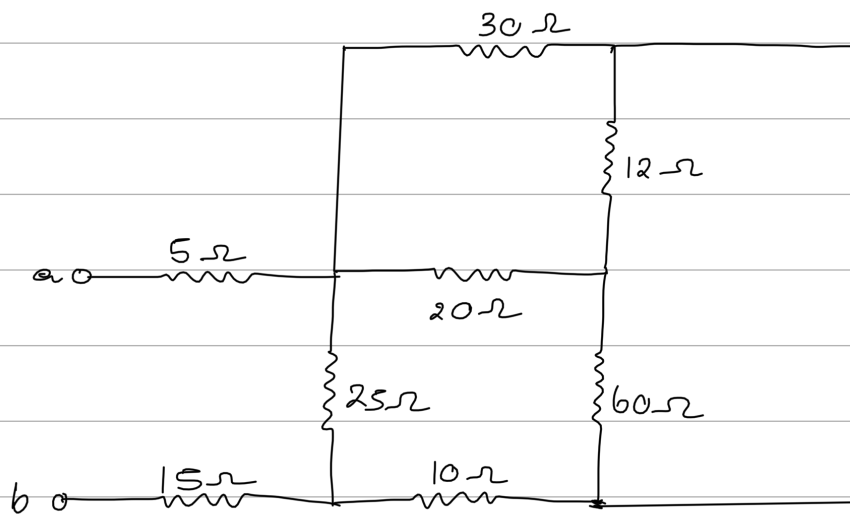


$$12 \parallel 60 = \frac{12(60)}{12 + 60}$$
$$= 10\Omega$$

Redraw

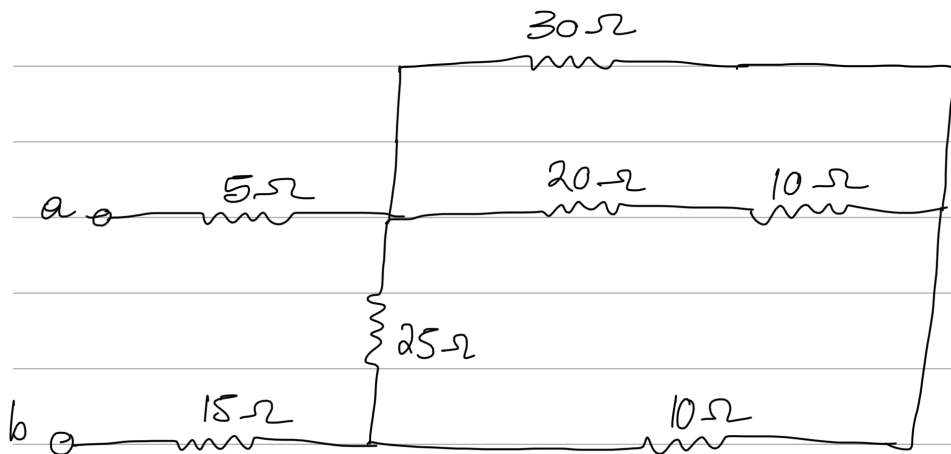


$$30 \parallel (20 + 10) = \frac{30(20 + 10)}{30 + (20 + 10)}$$
$$= 15\Omega$$

Redraw

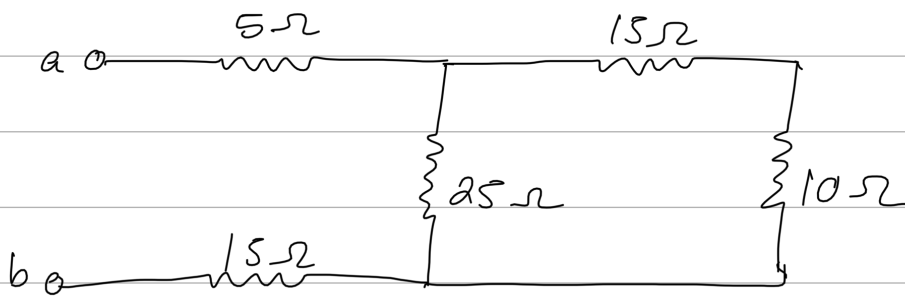



$$\begin{aligned} 25 \parallel (15 + 10) &= \frac{25(15 + 10)}{25(15 + 10)} \\ &= 12.5 \Omega \end{aligned}$$

Redraw

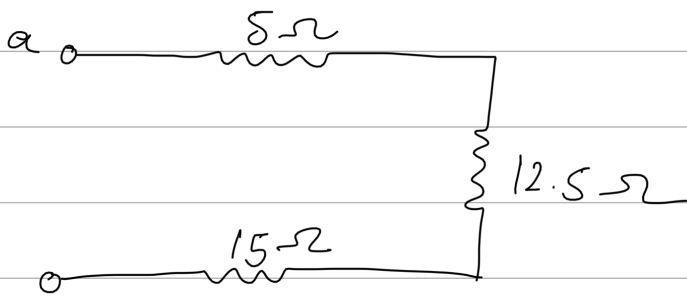

$$\begin{aligned} R_{eq} &= 5 + 12.5 + 15 \\ &= 32.5 \Omega \end{aligned}$$

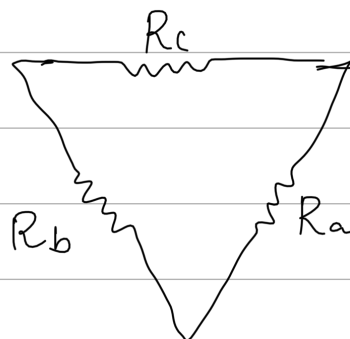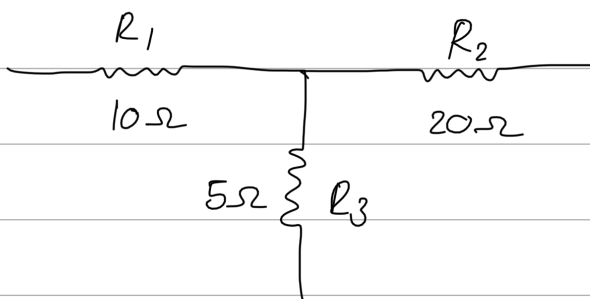2.51b Determine the equivalent resistance across a-b



$$R_a = \frac{R_1 R_2 + R_2 R_3 + R_1 R_3}{R_1}$$

$$= 35 \Omega$$


$$R_b = \frac{R_1 R_2 + R_2 R_3 + R_1 R_3}{R_2}$$

$$= 17.5 \Omega$$

$$R_c = \frac{R_1 R_2 + R_2 R_3 + R_1 R_3}{R_3}$$

$$= 70 \Omega$$

Redraw

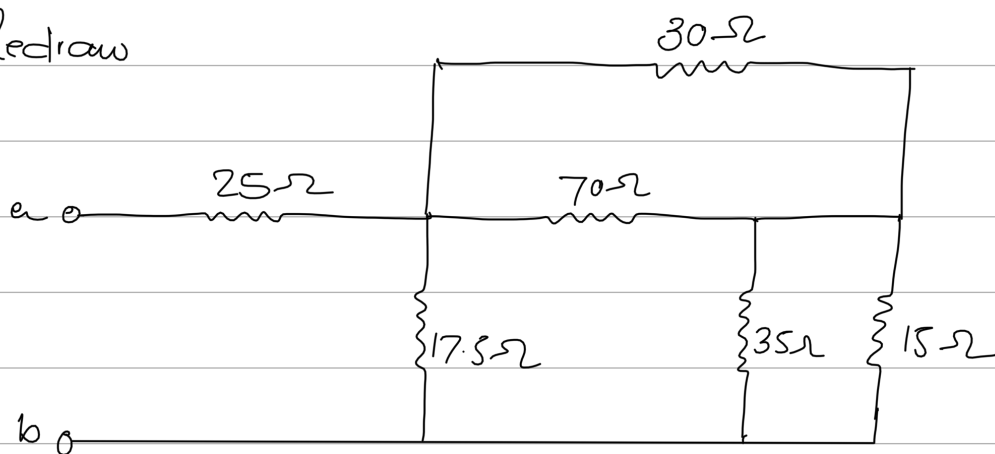



$$35 \parallel 15 = \frac{35(15)}{35+15}$$

$$= 10.5 \Omega$$

$$30 \parallel 70 = \frac{30(70)}{30+70}$$

$$= 21 \Omega$$

Redraw

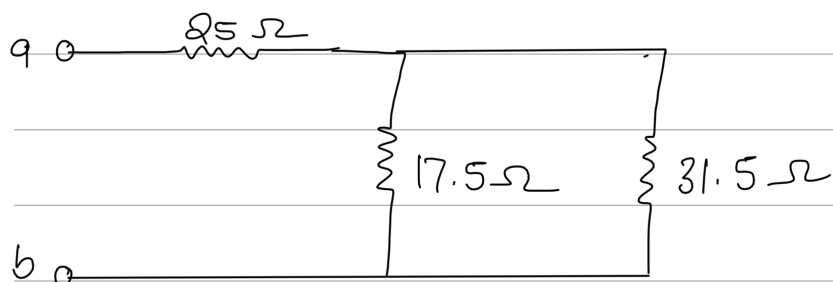
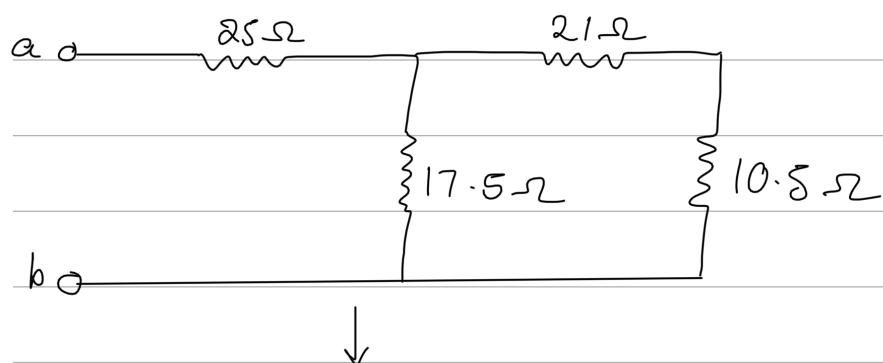


$$\therefore R_{eq} = 25 + 17.5 \parallel 31.5$$

$$= 25 + \frac{17.5(31.5)}{17.5 + 31.5}$$


$$= 36.25 \Omega$$

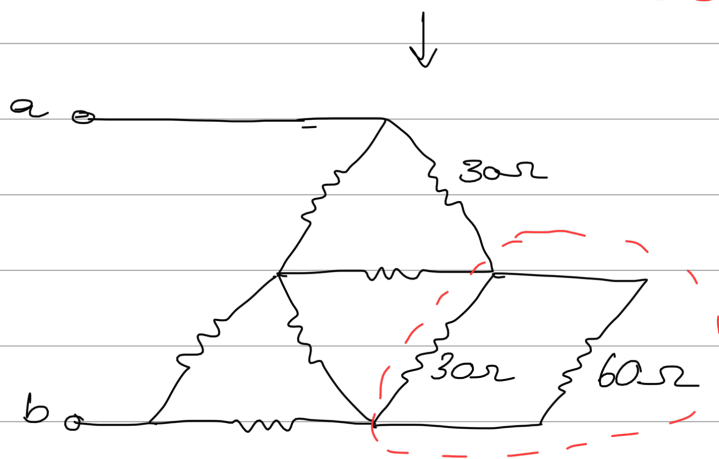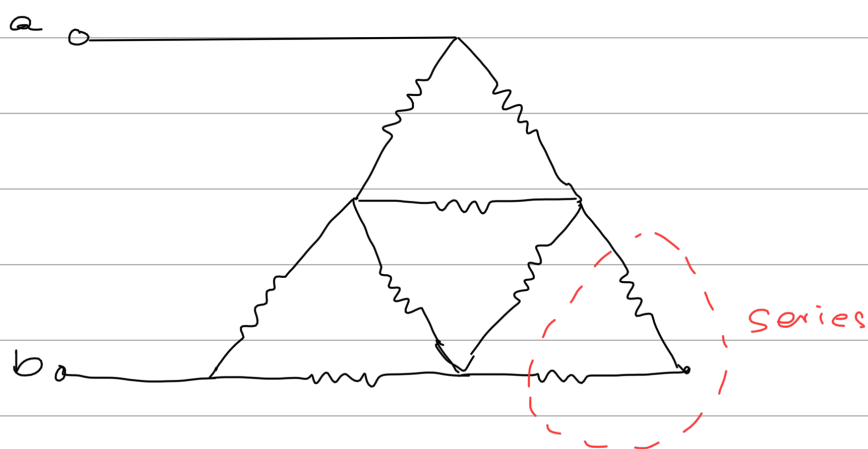2.53b Determine the equivalent resistance across a-b if all the elements are 30Ω



$$60 // 30 = \frac{60(30)}{60+30}$$


$$= 20\Omega$$

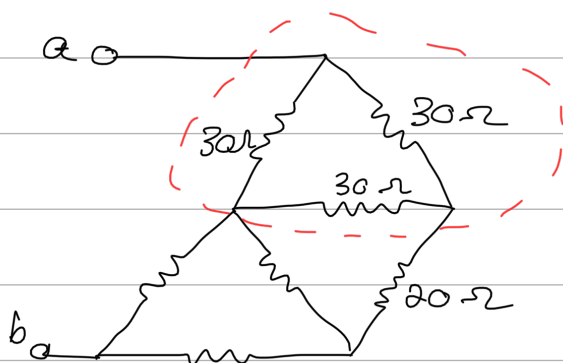




$$R_T = \frac{R_{\Delta}}{3}$$

$$= \frac{30}{3}$$

$$= 10\Omega$$

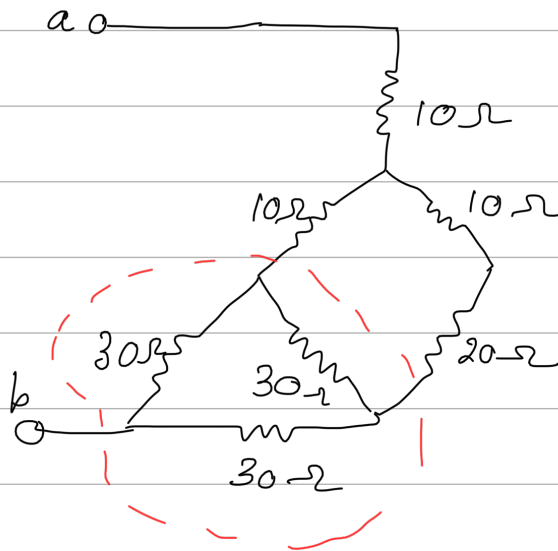
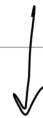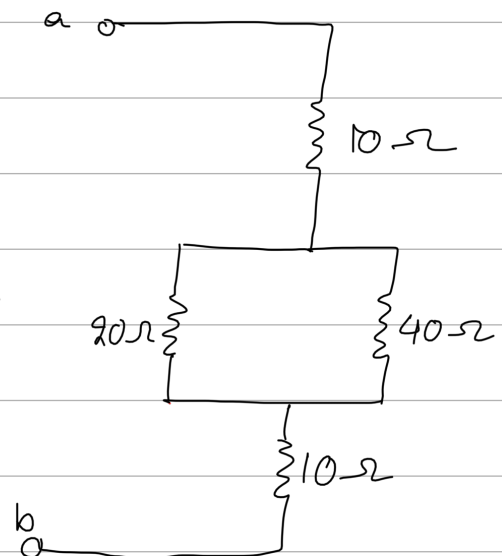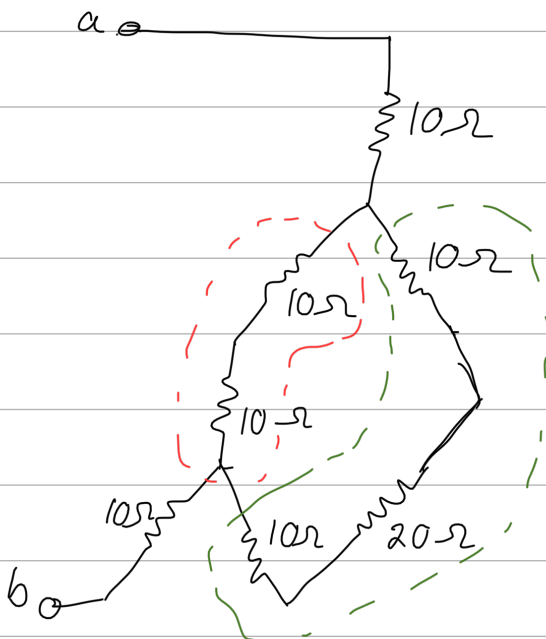
$$R_y = \frac{R_{\Delta}}{3} = 10\Omega$$



$$\therefore R_{eq} = 10 + 13.33 + 10 = 33.33\Omega$$

