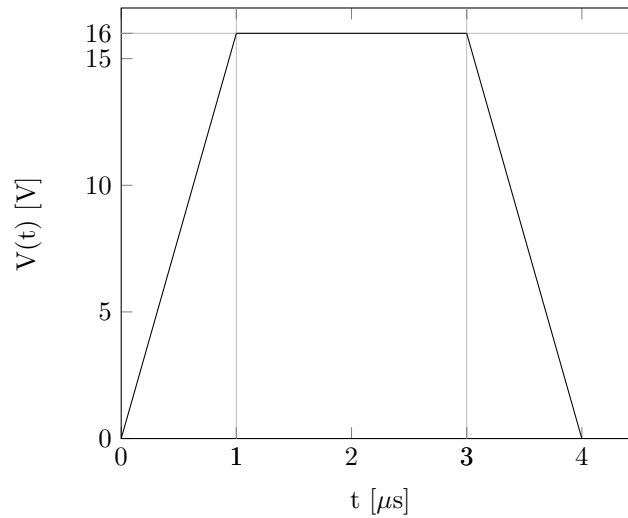



Tutorial 7

Question 6.10.




01 The voltage through a 5 mF capacitor is shown. Determine I_C between $t = 0$ and $4\mu\text{s}$. [2]

Question 6.12.

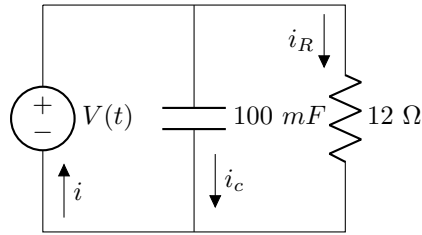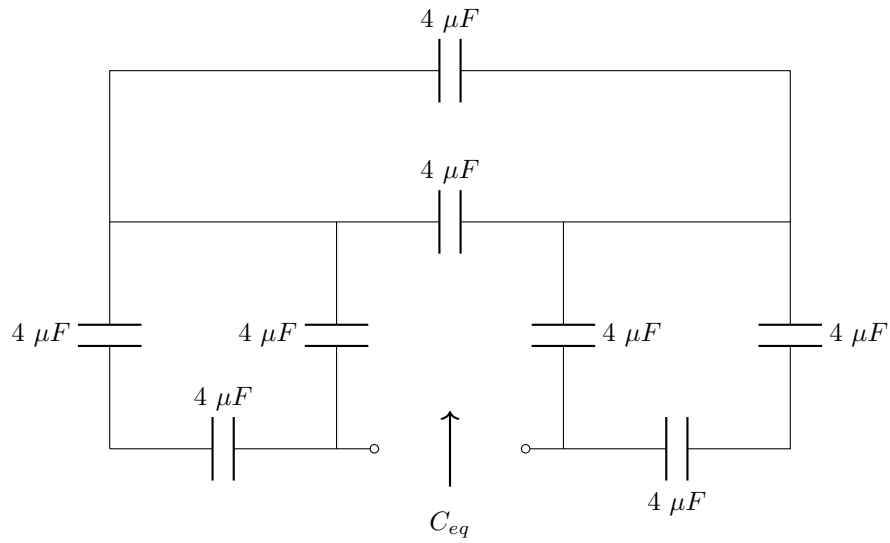


02 If $V(t) = 45e^{-2000t}$ V, find the power of the voltage source. [2]

Question 6.18.


**03** Find C_{eq} [2]

Question 6.40.

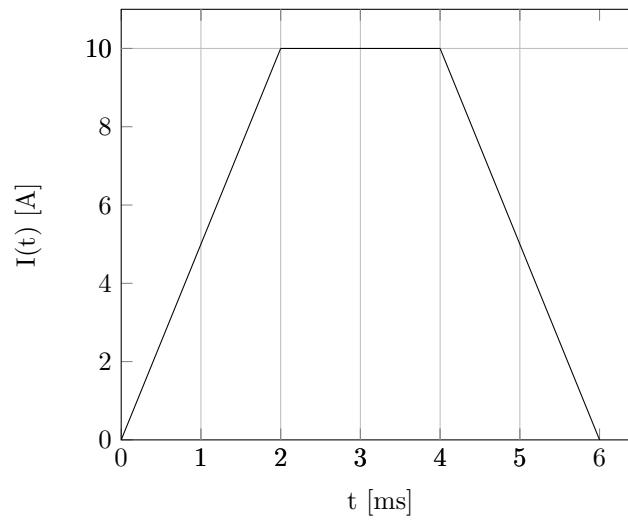


04 The current through a 5 mH inductor is shown. Determine V_L at $t = 1, 3$ and 5 ms . [2]

Question 6.46.

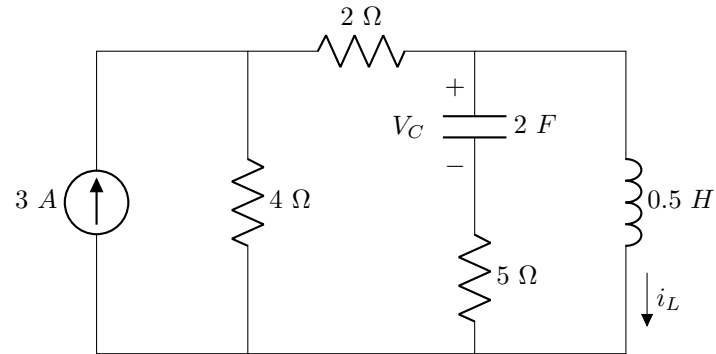

05 Determine V_C , i_L , W_C and W_L using DC conditions [4]

Question 6.54.

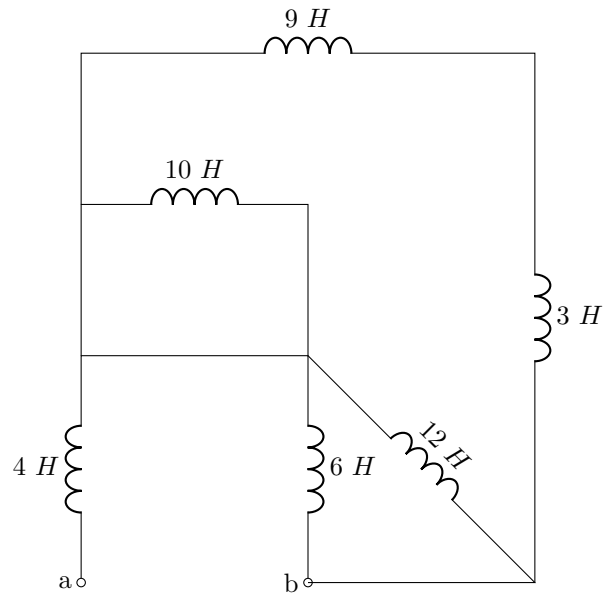

06 Find L_{eq} across a - b [2]