



Review Test Submission: Assignment Week 3

User Mr W (Wouter) W Nel

Course EBN 122 S2 2017

Test Assignment Week 3

Started 8/5/17 5:01 PM

Submitted 8/5/17 7:21 PM

Due Date 8/7/17 11:59 PM

Status Completed

Attempt Score 14.9 out of 20 points

Time 2 hours, 20 minutes

Elapsed

Instructions

Read over the document *ClickUP Assignments Instructions*.

Please direct any enquiries regarding ClickUP assignments to
EBN2017.ClickUptest@gmail.com

Save the answer to each question as you complete it.

At the end of the assignment click Save and Submit.

Give your final correct answer 3 significant digits.

Make sure you use the FULL STOP for your decimal place marker.

You must indicate the units, unless otherwise specified:

- There must be NO space between the answer and the units
- There must be between 1 and 3 digits to the left of the decimal point. *This means that you need enter 1kV rather than 1000V and 100mV rather than 0.1V*
- Write out 'ohm' to indicate Ω (use singular)
- Use 'u' to indicate micro.
- Only use pico(p), nano(n), micro(u), milli(m), kilo(k), mega(M), giga(G) and tera(T); do not use centi, deci and deca

Results Displayed


All Answers, Submitted Answers, Correct Answers, Feedback, Incorrectly Answered Questions

Question 1

2 out of 2 points



Calculate R_{eq2} when $R_I = 21\Omega$.

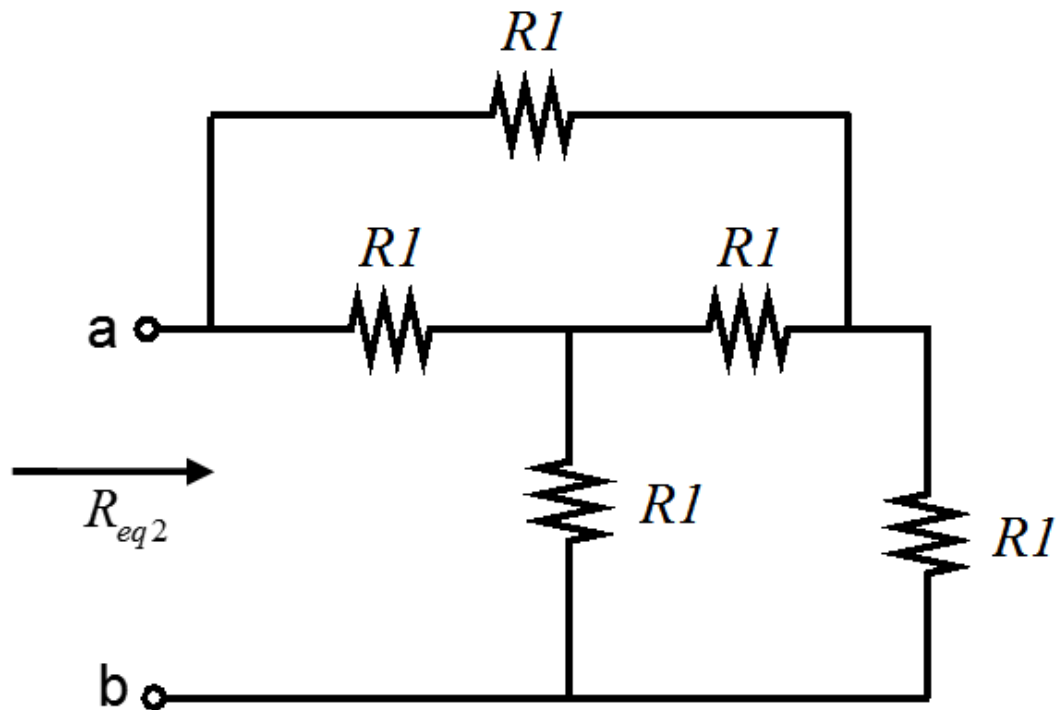

Selected Answer: ☒ 21ohm


Correct Answer: ☒ 21.00 $\pm$ 2% (ohm)

Question 2

2 out of 2 points



With $k = 43\Omega$ find R_{cd}

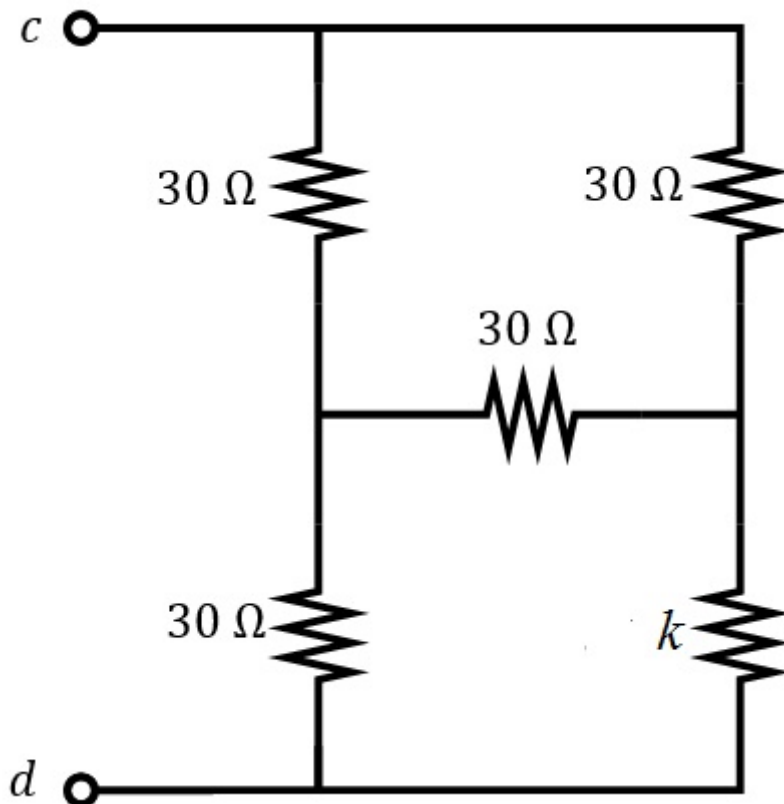

Selected Answer: ☒ 32.8ohm

Correct Answer:  $32.80 \pm 5\%$ (ohm)

Question 3

2 out of 2 points



Determine α if $I_1 = 2.5$ A

$$\begin{bmatrix} 4 & \alpha \\ -8 & 2 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 6 \\ -4 \end{bmatrix}$$

Selected Answer:  -0.5

Correct Answer:  $-0.500 \pm 5\%$

Question 4

2 out of 2 points



If $I = 16$ A, find m .

$$\begin{bmatrix} 5 & 8 \\ -1 & m \end{bmatrix} \begin{bmatrix} I \\ V \end{bmatrix} = \begin{bmatrix} 3 \\ -4 \end{bmatrix}$$

Selected Answer:  -1.25

Correct Answer:  $-1.25 \pm 5\%$

Question 5

2 out of 2 points



Determine V_1 , given $k = 3$:

$$\begin{bmatrix} 2 & -1 \\ -3 & 2 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} k \\ -5 \end{bmatrix}$$

Selected Answer:  1V

Correct Answer:  $1.00 \pm 2\%$

Question 6


2 out of 2 points



Use nodal analysis to set up two equations of the following form:

Provide h , if $I_1 = 4$ A.
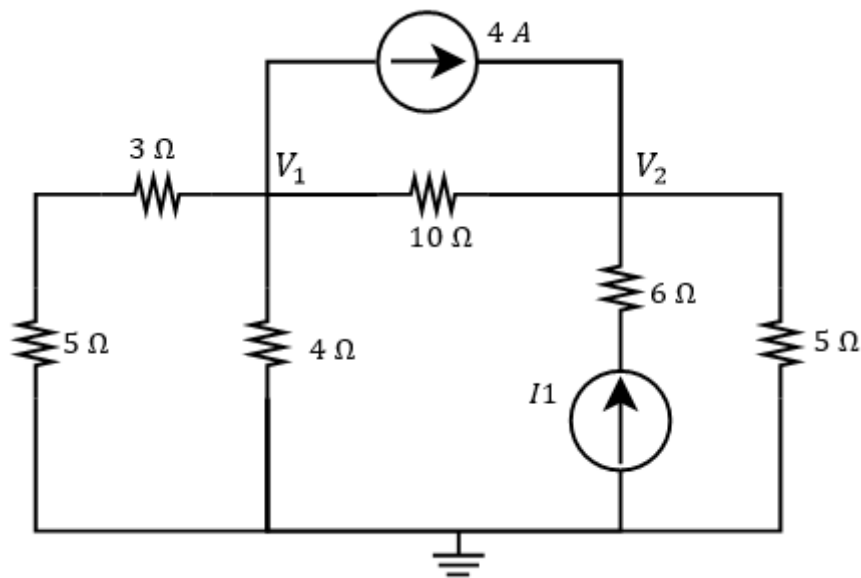
$$\begin{aligned} eV_1 + fV_2 &= -160 \\ -V_1 + gV_2 &= h \end{aligned}$$



Selected Answer: ☒ 80


Correct Answer: ☒ 80.00 ± 5%

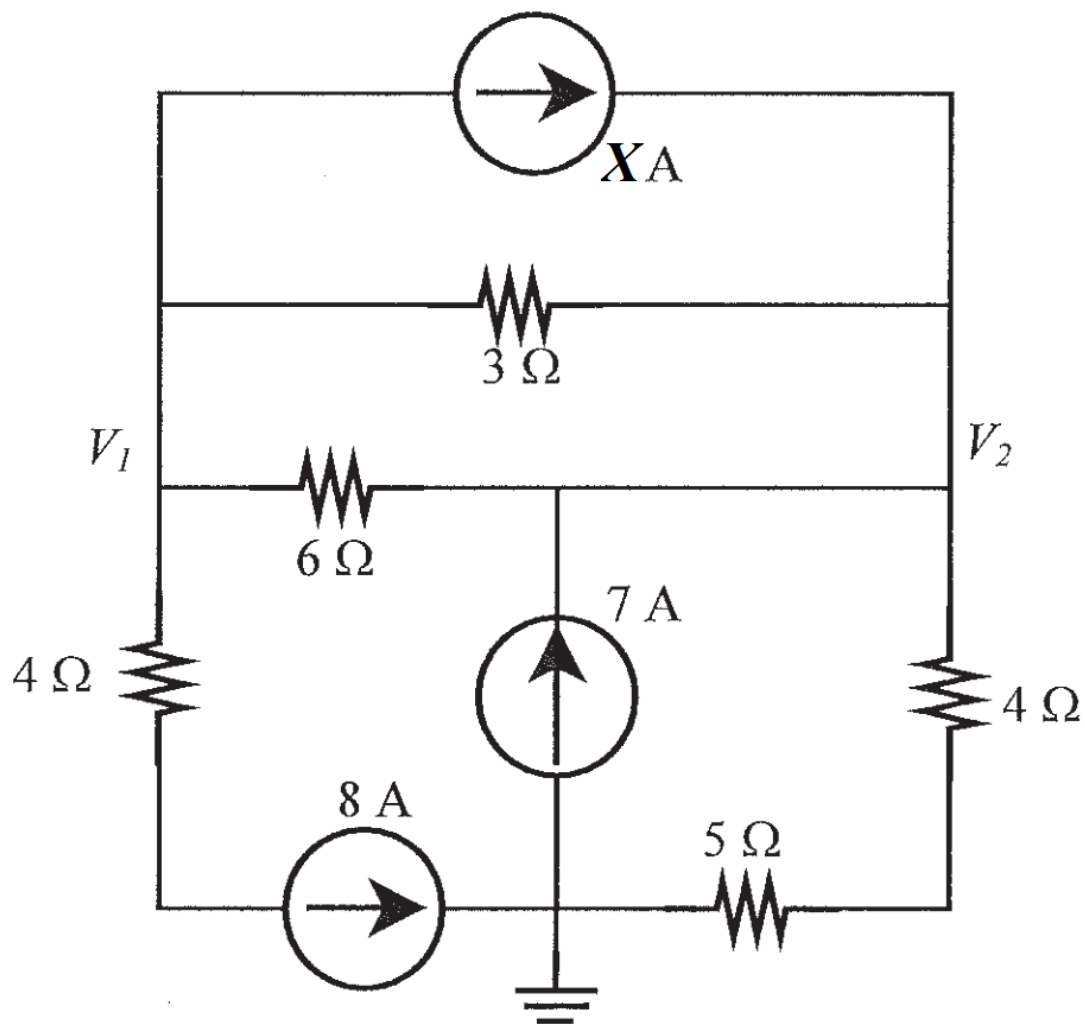Question 7

0 out of 2 points



Given $X = 7$ A, use nodal analysis to set up an equation of the following form for the circuit. Give the value of b :
 $-9V_1 + 11V_2 = b$



Selected Answer: ✖ -252


Correct Answer: ✔ 252.00 ± 5%

Question 8

2 out of 2 points



If $V_x = 9\text{ V}$ find V_o .

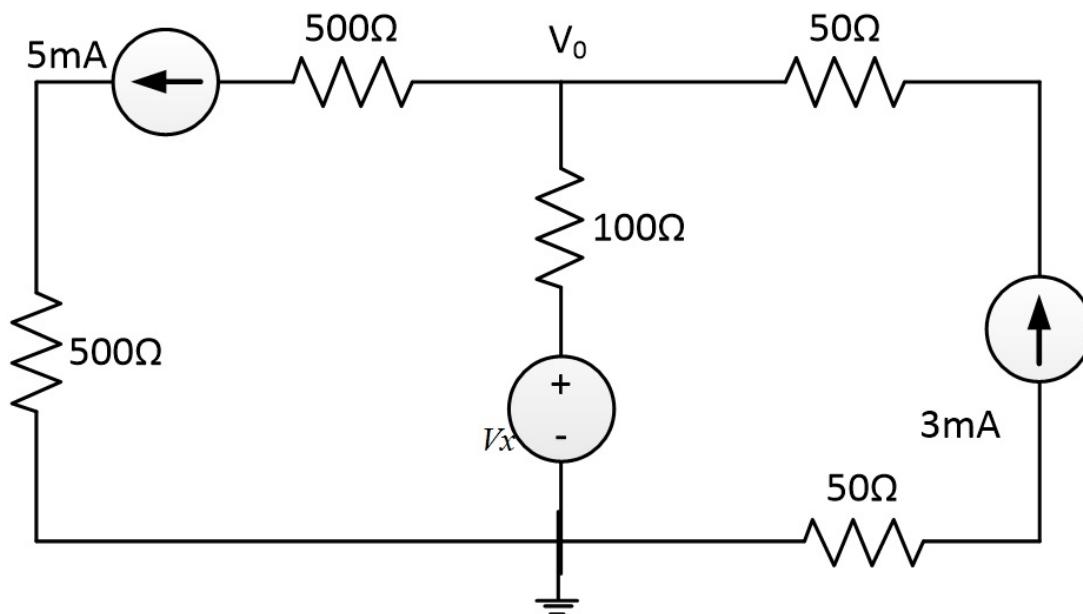

Selected Answer: ☒ 8.8V


Correct Answer: ☒ $8.80 \pm 2\%$ (V)

Question 9

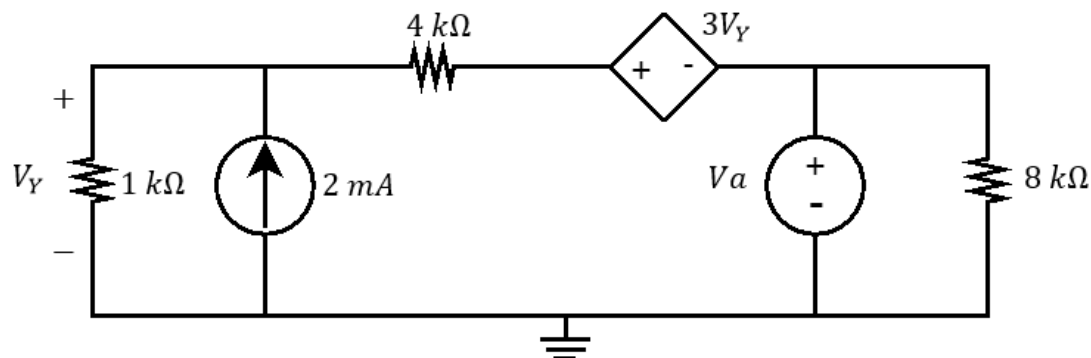0.4 out of 2 points



Use nodal analysis to determine V_y , when $V_a = 5$ V.



Selected Answer: ☒ 1.63V

Correct Answer: ☒ $6.50 \pm 5\%$ (V)


Question 10

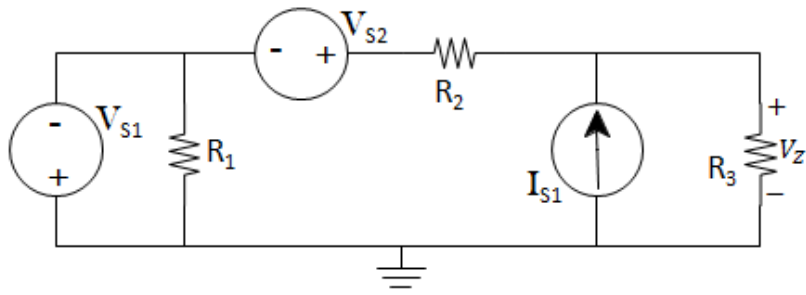0.5 out of 2 points



Determine the value of V_z .

$V_{S1}=7$ V, $V_{S2}=19$ V, $I_{S1}=33$ mA, $R_1=82\Omega$, $R_2=30\Omega$, $R_3=66\Omega$



Selected Answer: ✖ 5.49V

Correct Answer: ✔ $8.931 \pm 2\%$ (V)

Saturday, August 5, 2017 7:22:02 PM SAST

← OK