



Review Test Submission: Assignment Week 4

User Mr W (Wouter) W Nel

Course EBN 122 S2 2017

Test Assignment Week 4

Started 8/11/17 6:30 PM

Submitted 8/14/17 5:27 PM

Due Date 8/14/17 11:59 PM

Status Completed

Attempt Score 10.3 out of 20 points

Time Elapsed 70 hours, 56 minutes

Instructions

Read over the document *ClickUP Assignments Instructions*.

Please direct any enquiries regarding ClickUP assignments to EBN2017.ClickUptest@gmail.com

Save the answer to each question as you complete it.

At the end of the assignment click Save and Submit.

Give your final correct answer 3 significant digits.

Make sure you use the FULL STOP for your decimal place marker.

You must indicate the units, unless otherwise specified:

- There must be NO space between the answer and the units
- There must be between 1 and 3 digits to the left of the decimal point. *This means that you need enter 1kV rather than 1000V and 100mV rather than 0.1V*
- Write out 'ohm' to indicate Ω (use sigular)
- Use 'u' to indicate micro.
- Only use pico(**p**), nano(**n**), micro(**u**), milli(**m**), kilo(**k**), mega(**M**), giga(**G**) and tera(**T**); do not use centi, deci and deca


Results All Answers, Submitted Answers, Correct Answers, Feedback, Incorrectly Answered Questions Displayed

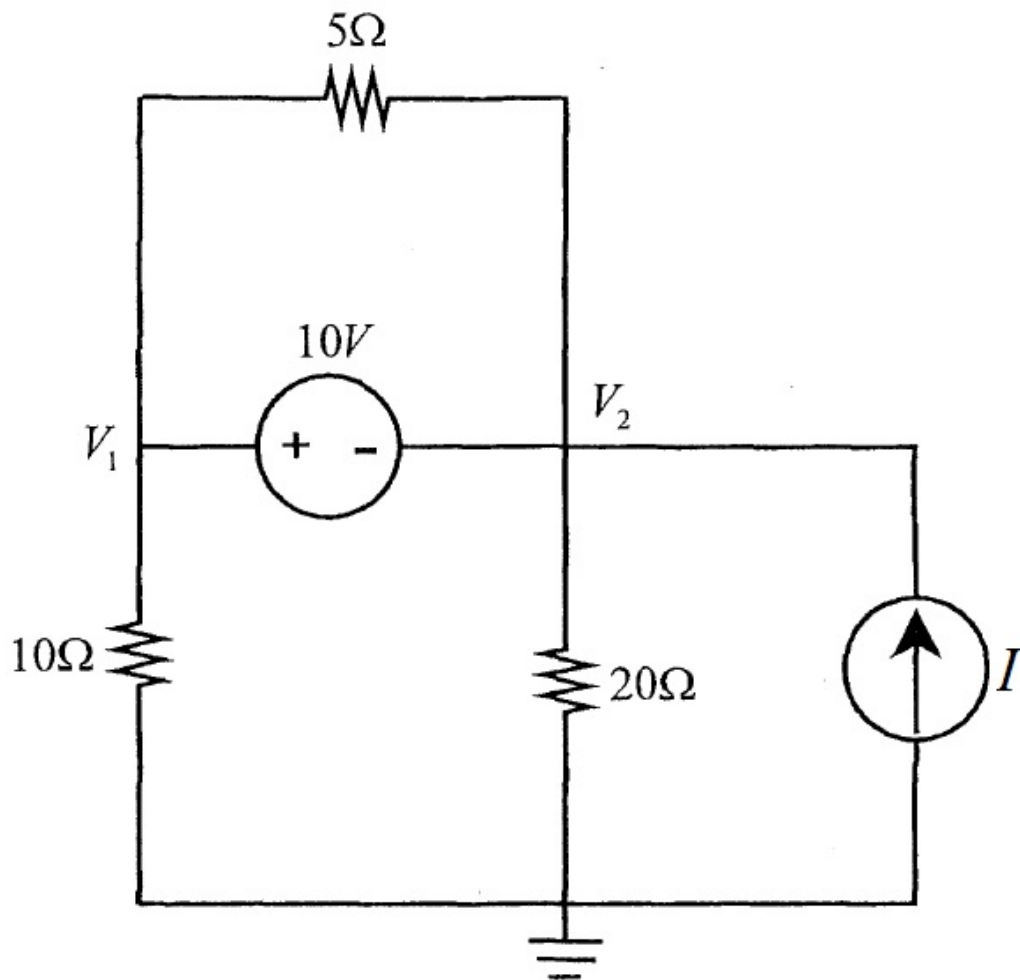Question 1

2 out of 2 points



Using nodal analysis, find V_1 if $I = 5\text{ A}$.



Selected Answer: ☒ 36.7V

Correct Answer: ☒ 36.67 ± 5% (V)


Question 2

2 out of 2 points



Use nodal analysis to solve for V_0 .

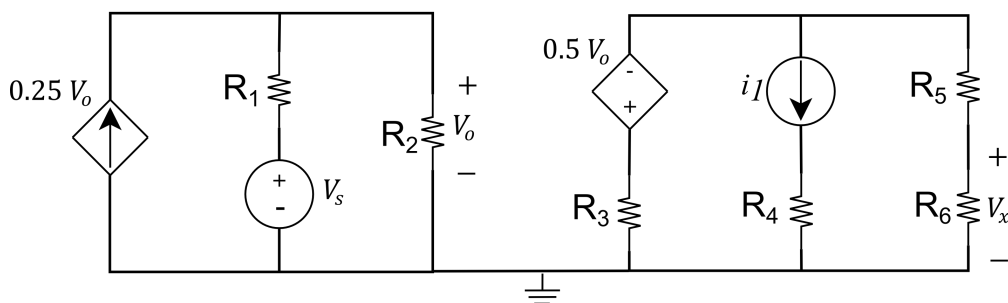☒ $R_1=13\Omega$, $R_2=98\Omega$, $R_3=85\Omega$, $R_4=64\Omega$, $R_5=63\Omega$, $R_6=42\Omega$ and $V_s=13V$




Selected Answer: ☒ -6.14V


Correct Answer: ☒ -6.140 ± 5 (V)

Question 3

0.5 out of 2 points

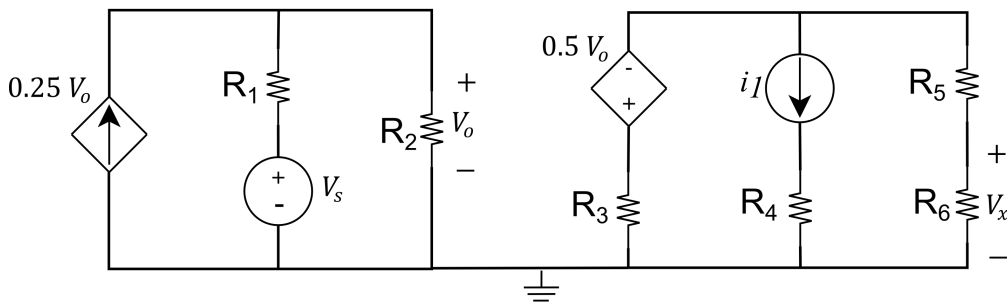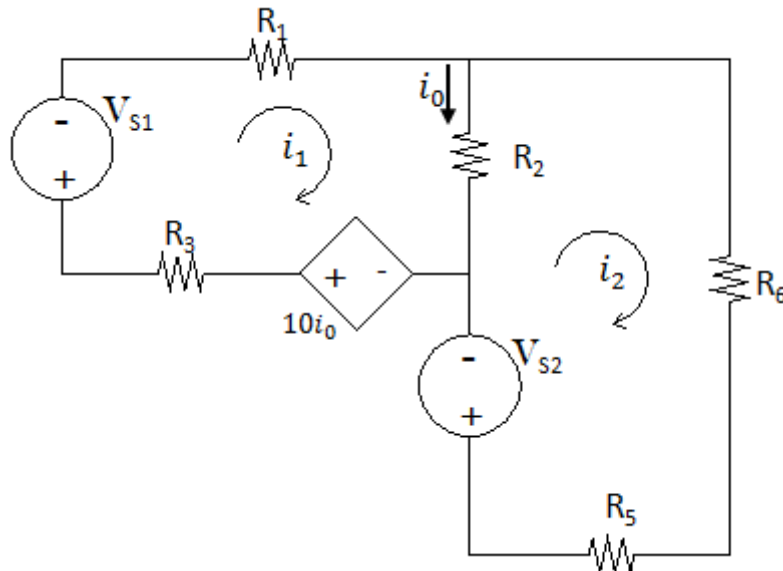Use nodal analysis to solve for V_x . $R_3=20\Omega$, $R_4=66\Omega$, $R_5=92\Omega$, $R_6=53\Omega$, $V_0=13V$, $i_1=2A$ Selected Answer: ✗ 12.9VCorrect Answer: ✓ -14.936 ± 2 (V)**Question 4**


0.5 out of 2 points

Determine i_0 . $R_1=84\Omega$, $R_2=34\Omega$, $R_3=71\Omega$, $R_5=97\Omega$, $R_6=91\Omega$, $V_{S1}=13V$ and $V_{S2}=8V$ Selected Answer: ✗ 237mACorrect Answer: ✓ $-30.934 \pm 5\%$ (mA)**Question 5**

0 out of 2 points

Use mesh analysis to solve I_2

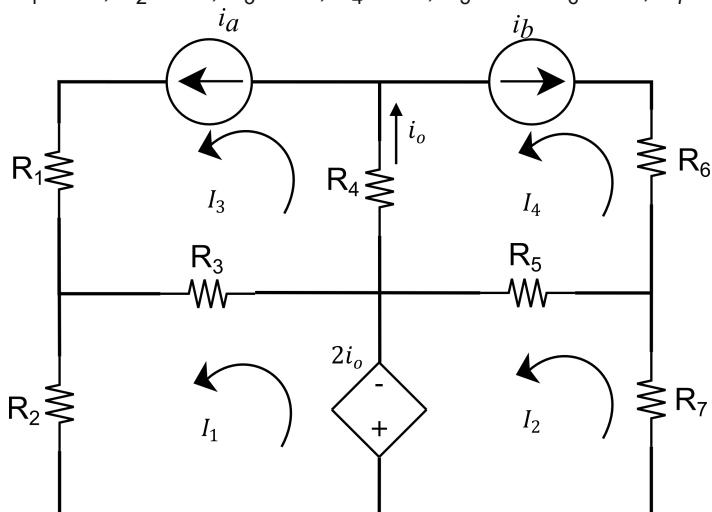$R_1=76\Omega$, $R_2=42\Omega$, $R_3=53\Omega$, $R_4=16\Omega$, $R_5=50\Omega$, $R_6=62\Omega$, $R_7=45\Omega$, $i_a=1A$ and $i_b=2A$



Selected Answer: ✖ -989mA


Correct Answer: ✔ $-0.989 \pm 5\%$ (A)

Question 6

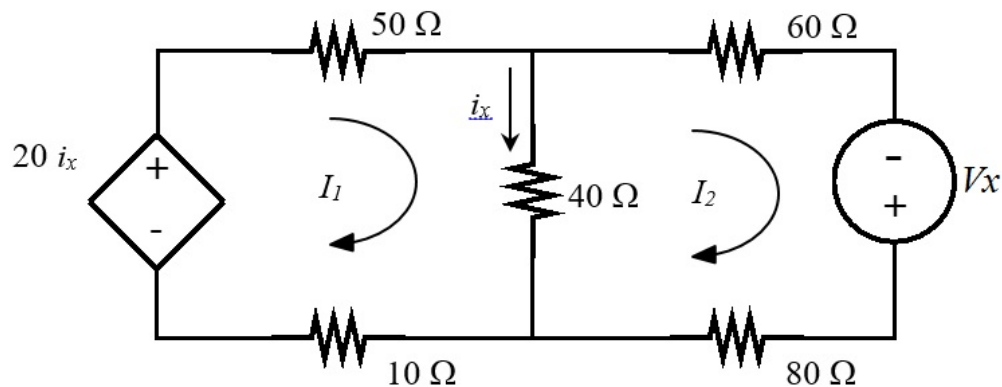0.4 out of 2 points



With $V_x = 221$ V find the value of I_2 using mesh analysis.



Selected Answer: ✖ -1.38A

Correct Answer: ✔ $1.30 \pm 5\%$ (A)


Question 7

2 out of 2 points



Use mesh analysis to solve I_1

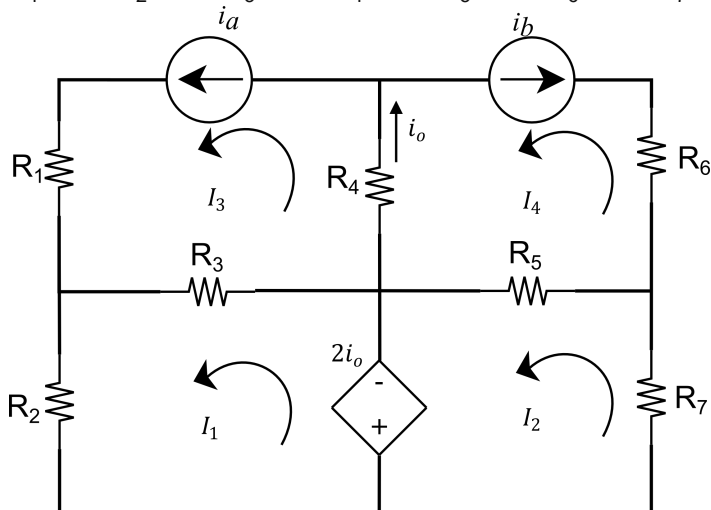$R_1=31\Omega$, $R_2=32\Omega$, $R_3=58\Omega$, $R_4=50\Omega$, $R_5=71\Omega$, $R_6=98\Omega$, $R_7=70\Omega$, $i_a=4A$ and $i_b=3A$



Selected Answer: ☒ 2.42A

Correct Answer: ☒ 2.422 ± 5% (A)


Question 8

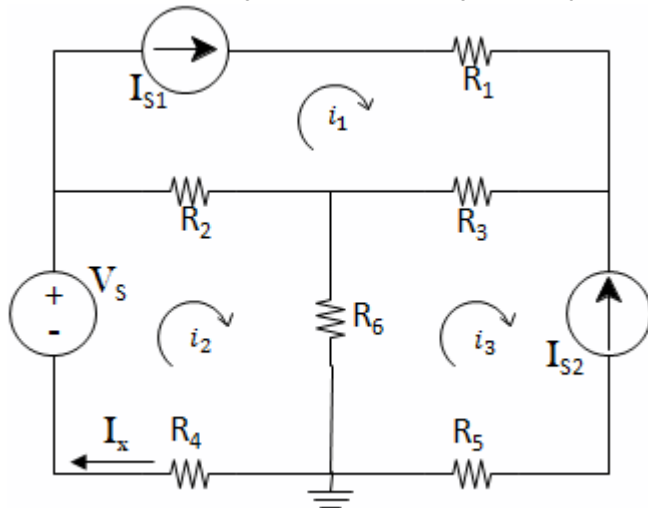0.4 out of 2 points



Determine I_x , with

$R_1=77\Omega$, $R_2=81\Omega$, $R_3=20\Omega$, $R_4=98\Omega$, $R_5=63\Omega$, $R_6=79\Omega$, $I_{S1}=45mA$, $I_{S2}=13mA$ and $V_S=11V$



Selected Answer: ☒ -32.4mA


Correct Answer: ☒ 52.783 ± 5% (mA)

Question 9

0.5 out of 2 points



If $k = 29 A$, determine i_2

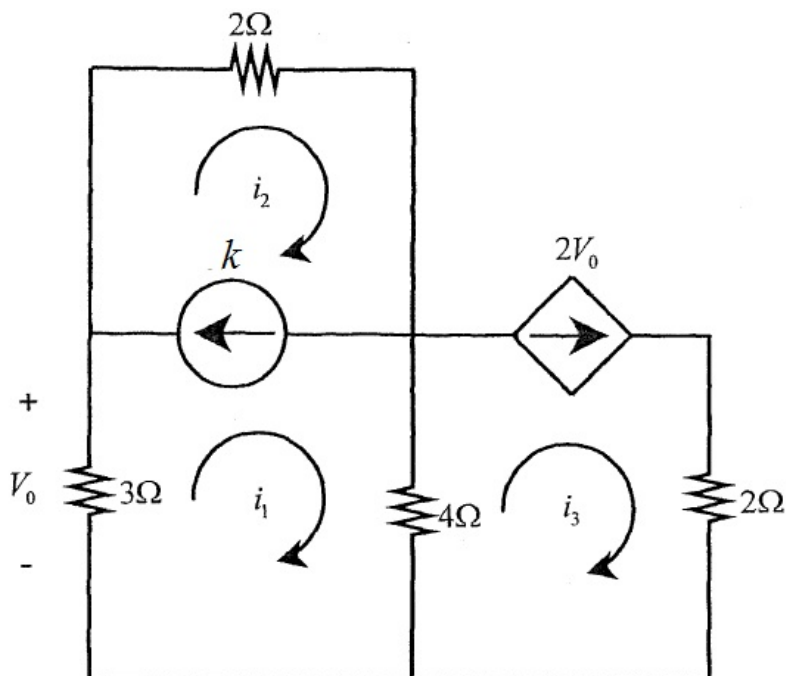

Selected Answer: ✗ 4.14A


Correct Answer: ✓ $27.24 \pm 2\%$ (A)

Question 10

2 out of 2 points



Given $I_x = 12$, find I_1 .

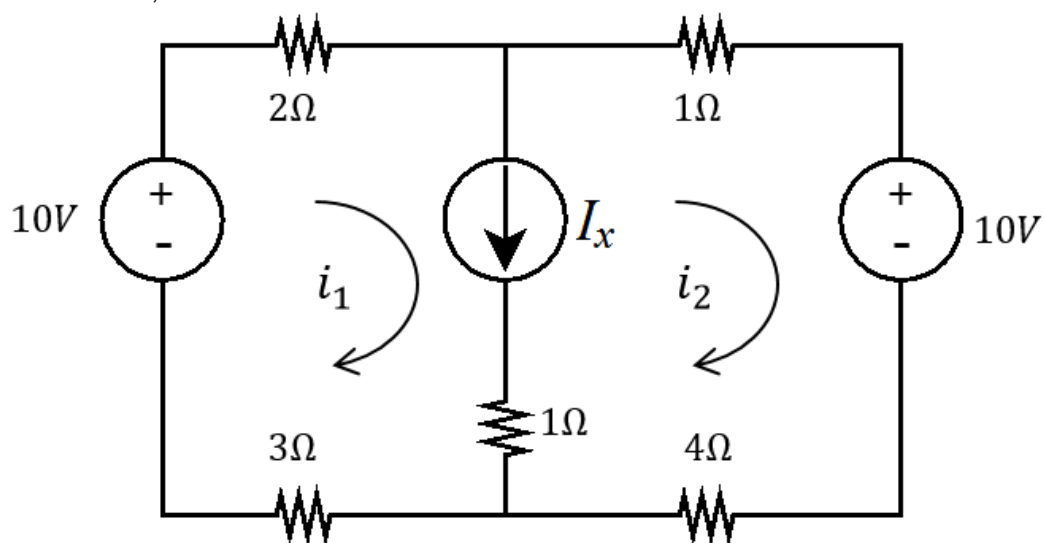

Selected Answer: ✓ 6A

Correct Answer: ✓ $6.00 \pm 5\%$ (A)

Monday, August 14, 2017 5:27:36 PM SAST

← OK