



## Review Test Submission: Assignment Week 9

User Mr W (Wouter) W Nel

Course EBN 122 S2 2017

Test Assignment Week 9

Started 9/18/17 8:18 AM

Submitted 9/25/17 1:52 PM

Due Date 9/25/17 11:59 PM

Status Completed

Attempt Score 24.2 out of 30 points

Time Elapsed 173 hours, 33 minutes

Instructions

Read over the document *ClickUP Assignments Instructions*.

The deadline is the time by which the assignment must be SUBMITTED (not just started)

Before sending an enquiring regarding ClickUP question to any-one please verify that your problem is valid ... i.e. if you suspect incorrect marking first check with a fellow student or two.

Please direct any enquiries regarding ClickUP assignments to EBN2017.ClickUptest@gmail.com

Save the answer to each question as you complete it.

At the end of the assignment click Save and Submit.

Give your final correct answer 3 significant digits.

Make sure you use the FULL STOP for your decimal place marker.

You must indicate the units, unless otherwise specified:

- Use SI units unless otherwise specified.
- There must be NO space between the answer and the units
- There must be between 1 and 3 digits to the left of the decimal point. *This means that you need enter 1kV rather than 1000V and 100mV rather than 0.1V*
- Write out 'ohm' to indicate  $\Omega$  (use singular)
- Use 'u' to indicate micro.
- Only use pico(p), nano(n), micro(u), milli(m), kilo(k), mega(M), giga(G) and tera(T); do not use centi, deci and deca

It does not have meaning to use milli(m) or kilo(k) when not as part of a unit. So when no units are required just write 0.1 or 1000.


Results All Answers, Submitted Answers, Correct Answers, Feedback, Incorrectly Answered  
Displayed Questions

### Question 1

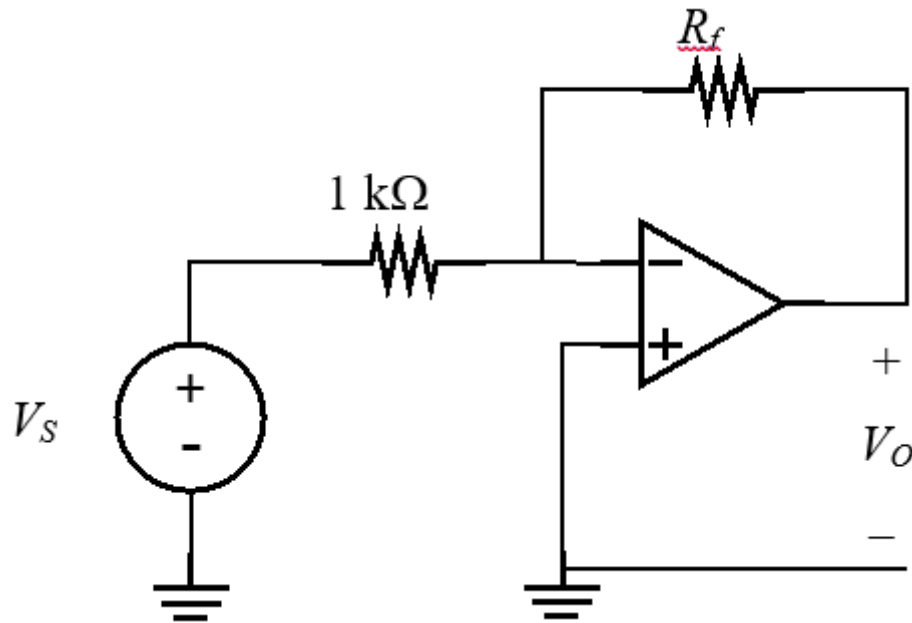0.2 out of 2 points



The range of the output voltage  $V_O$  is:  $-10 \leq V_O \leq -1$ . The range of the input voltage  $V_S$  is:  $1 \leq V_S \leq 9.9$ . Determine the maximum value of  $R_f$  (kOhm) which will satisfy the above constraints.



Selected Answer: ✗ 9.9kohm

Correct Answer: ✓  $1.01 \pm 5\%$  (kohm)


### Question 2

2 out of 2 points



What is the maximum value  $V_S$  can assume to ensure that the operational amplifier operates in its linear range?

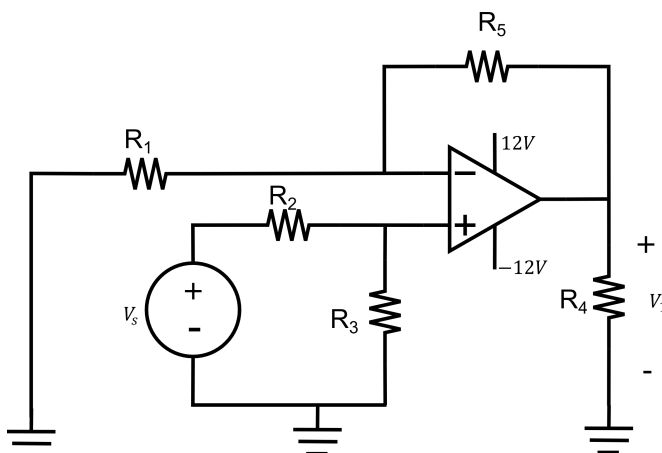
$R_1=5\Omega$ ,  $R_2=34\Omega$ ,  $R_3=11\Omega$ ,  $R_4=5\Omega$  and  $R_5=26\Omega$




Selected Answer: ✓ 7.92V

Correct Answer:   $7.918 \pm 2\%$  (V)**Question 3**

2 out of 2 points

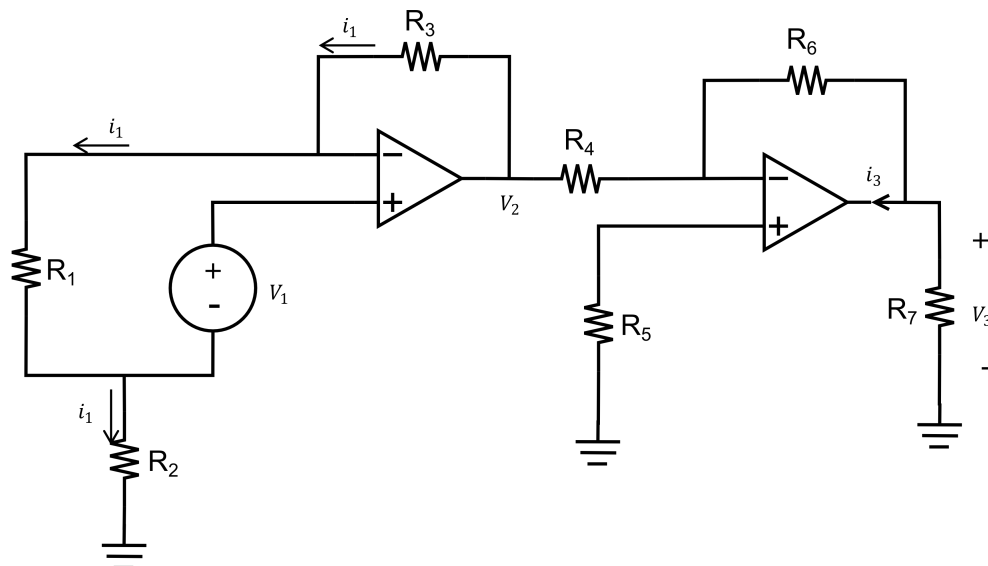
Determine the amplification factor  $V_3/V_2$  $R_1=8\text{k}\Omega$ ,  $R_2=5\text{k}\Omega$ ,  $R_3=17\text{k}\Omega$ ,  $R_4=4\text{k}\Omega$ ,  $R_5=5\text{k}\Omega$ ,  $R_6=16\text{k}\Omega$  and  $R_7=6\text{k}\Omega$ Selected Answer:  -4Correct Answer:   $-4.000 \pm 2\%$ **Question 4**

2 out of 2 points

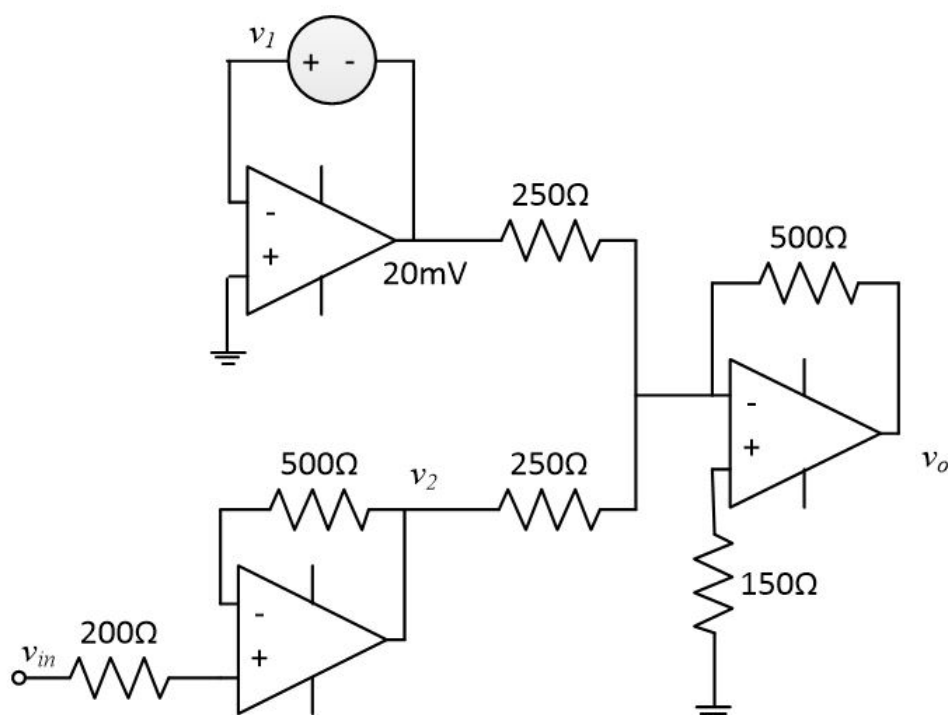
Find  $v_o$  if  $V_{in} = 7\text{ V}$ 

Selected Answer: ☒ -14.04VCorrect Answer: ☒ -14.04 ± 5% (V)**Question 5**

0 out of 2 points

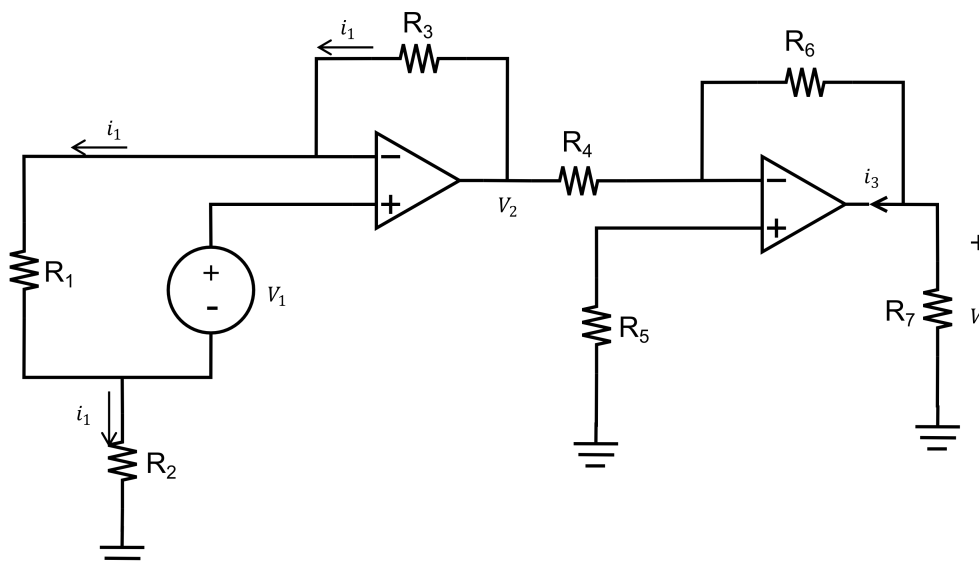Determine the amplification factor  $V_2/V_1$  $R_1=6k\Omega$ ,  $R_2=7k\Omega$ ,  $R_3=14k\Omega$ ,  $R_4=5k\Omega$ ,  $R_5=5k\Omega$ ,  $R_6=10k\Omega$  and  $R_7=2k\Omega$ Selected Answer: ☒ 0.19Correct Answer: ☒ 4.500 ± 2%**Question 6**

2 out of 2 points

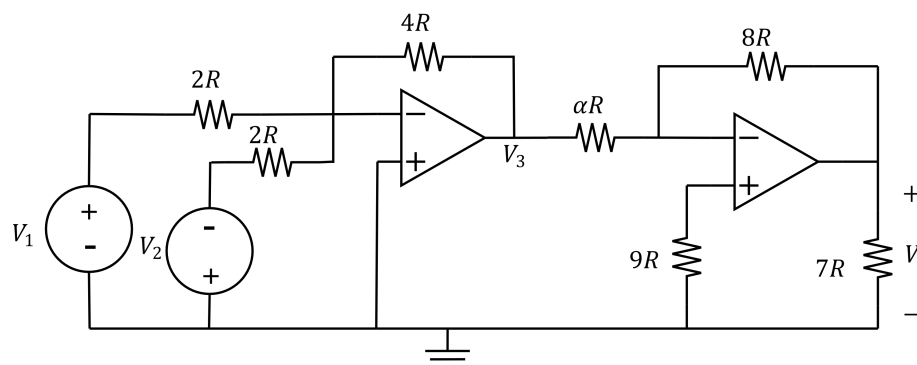If  $V_3=9V$  and  $V_2=9V$  determine the value for  $\alpha$  which will result in  $V_0=-14V$ Selected Answer: ☒ 5.14Correct Answer: ☒ 5.143 ± 2%**Question 7**

0.2 out of 2 points


The voltage across a  $9\mu F$  capacitor is given as  $2+8e^{-21t}$ . Determine the current

at  $t=40\text{ms}$ Selected Answer: ☒ 49.1  $\mu\text{A}$ Correct Answer: ☒  $-652.746 \pm 2\%$  ( $\mu\text{A}$ )**Question 8**

2 out of 2 points




The graph below shows the voltage across a  $3\text{H}$  inductor. Assuming the initial current through the inductor is  $9\text{ A}$ , what is the current at  $t=5.7\text{ s}$ ?

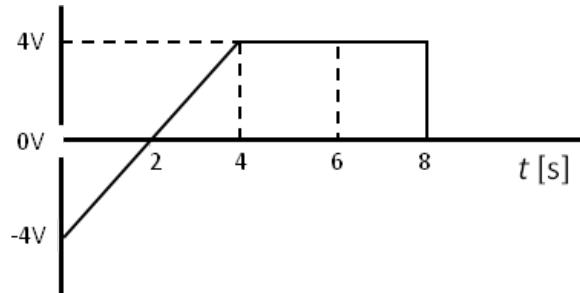Selected Answer: ☒  $11.3\text{A}$ Correct Answer: ☒  $11.267 \pm 2\%$  ( $\text{A}$ )**Question 9**

1.8 out of 2 points




Determine the equivalent capacitance  $C_{ab}$  of the circuit. Every capacitor has a value of  $13\text{ mF}$ . Give your answer in  $\text{mF}$  as well.

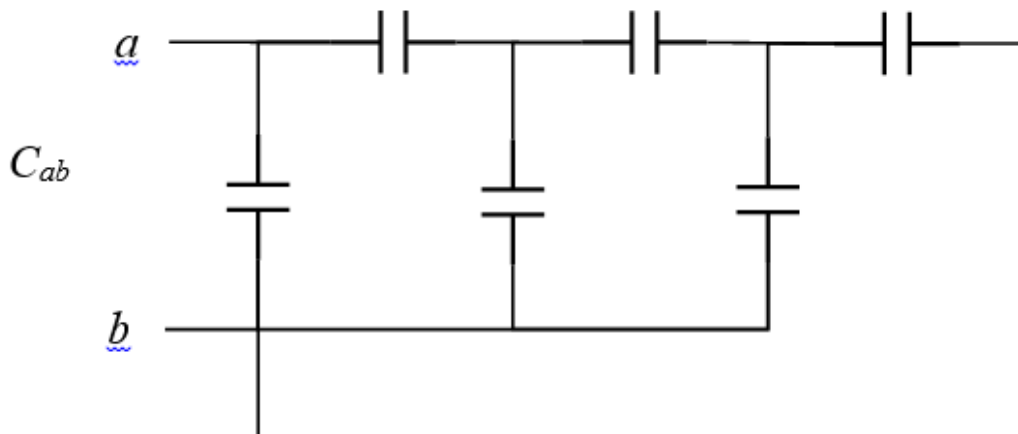Selected Answer: ☒  $21.1\mu\text{F}$ Correct Answer: ☒  $21.13 \pm 5\%$  ( $\text{mF}$ )**Question 10**

2 out of 2 points

Determine  $C_{eq}$ 

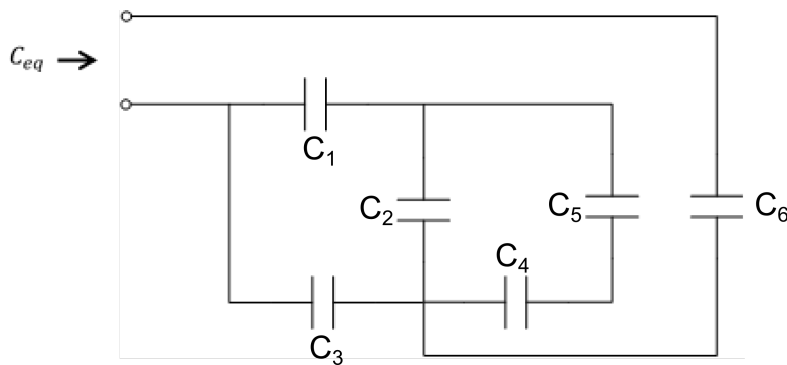$C_1=537\text{nF}$ ,  $C_2=539\text{nF}$ ,  $C_3=443\text{nF}$ ,  $C_4=539\text{nF}$ ,  $C_5=539\text{nF}$  and  $C_6=378\text{nF}$



Selected Answer: ☒ 253nF


Correct Answer: ☒ 253.066 ± 2% (nF)
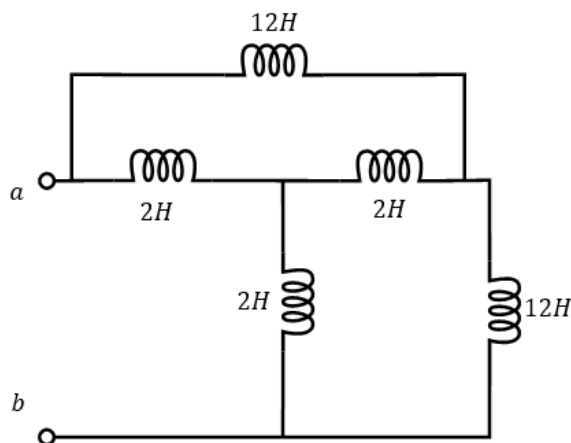
### Question 11

2 out of 2 points



Find the equivalent inductance  $L_{ab}$ .



Selected Answer: ☒ 3.43H

Correct Answer: ☒ 3.429 ± 2% (H)


### Question 12

2 out of 2 points



Find the equivalent inductance to the combination below.

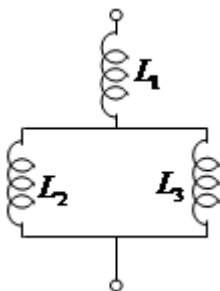$L_1=5\text{mH}$ ,  $L_2=12\text{mH}$  and  $L_3=11\text{mH}$ ,



Selected Answer: ☒ 10.7mH

Correct Answer: ☒ 10.739 ± 2% (mH)


## Question 13

2 out of 2 points



Calculate the energy stored by the inductor ( $w_L$ ). Assume steady state (direct current) conditions.

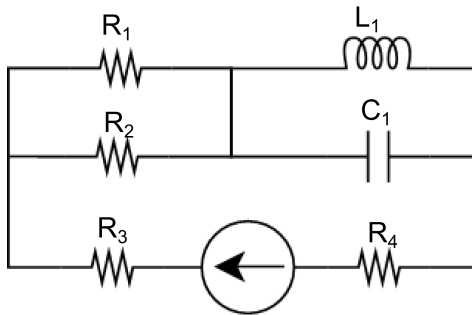$R_1=98\text{k}\Omega$ ,  $R_2=56\text{k}\Omega$ ,  $R_3=63\text{k}\Omega$ ,  $R_4=96\text{k}\Omega$ ,  $C_1=64\text{nF}$ ,  $L_1=19\text{mH}$  and the current source,  $I_S=88\text{mA}$ .



Selected Answer: ☒ 73.6  $\mu\text{J}$


Correct Answer: ☒ 73.568  $\pm$  2% ( $\mu\text{J}$ )
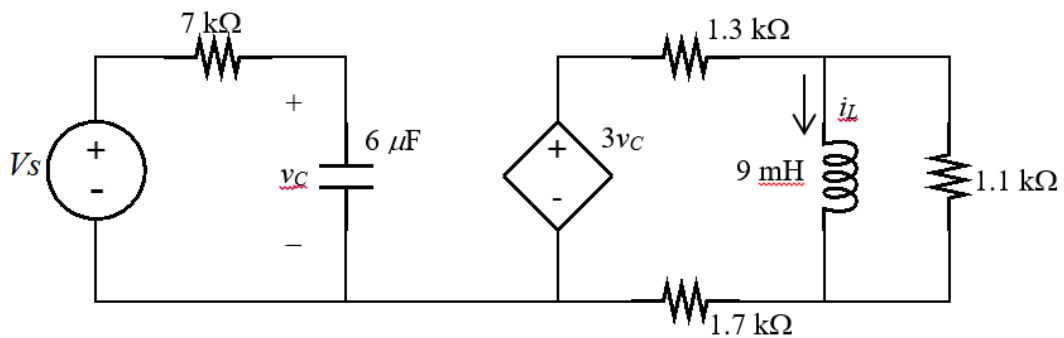
## Question 14

2 out of 2 points



Determine the energy stored in the inductor, given  $V_S = 26$ .



Selected Answer: ☒ 3.04  $\mu\text{J}$

Correct Answer: ☒ 3.04  $\pm$  1% ( $\mu\text{J}$ )


## Question 15

2 out of 2 points



Calculate the energy stored by the capacitor ( $w_C$ ). Assume direct current/steady state conditions.

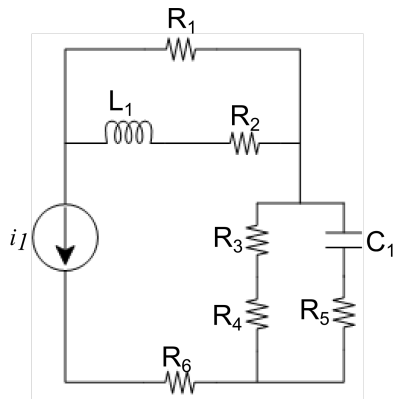$R_1=7\text{k}\Omega$ ,  $R_2=7\text{k}\Omega$ ,  $R_3=46\text{k}\Omega$ ,  $R_4=43\text{k}\Omega$ ,  $R_5=7\text{k}\Omega$ ,  $R_6=2\text{k}\Omega$ ,  $C_1=6\text{nF}$ ,  $L_1=1\text{mH}$  and  $i_1=49\text{mA}$



Selected Answer: ☒ 57.1mJ

Correct Answer: ☒ 57.055 ± 2 (mJ)

Monday, September 25, 2017 1:52:47 PM SAST

← OK