



Review Test Submission: Assignment 2

User	Miss SM (Sando) S Mkhwanazi
Course	EBN 122 S2 2019
Test	Assignment 2
Started	7/30/19 12:40 PM
Submitted	7/30/19 3:31 PM
Due Date	7/31/19 12:00 PM
Status	Completed
Attempt Score	7.4 out of 20 points
Time Elapsed	2 hours, 51 minutes

Instructions Read over the document *ClickUP Assignments Instructions*.

Save the answer to each question as you complete it.

At the end of the assignment click Save and Submit.

Give your final correct answer 3 significant digits.

Make sure you use the FULL STOP for your decimal place marker.

You must indicate the units, unless otherwise specified:

- There must be NO space between the answer and the units
- There must be between 1 and 3 digits to the left of the decimal point. *This means that you need enter 1kV rather than 1000V and 100mV rather than 0.1V*
- Write out 'ohm' to indicate Ω (use singular)
- Use 'u' to indicate micro (μ).
- Only use pico(p), nano(n), micro(u), milli(m), kilo(k), mega(M), giga(G) and tera(T); do not use centi, deci and deca


Results Displayed	Incorrectly Answered Questions
-------------------	--------------------------------

Question 1

0.5 out of 2 points



If $V_a = 12\text{ V}$, calculate I_x

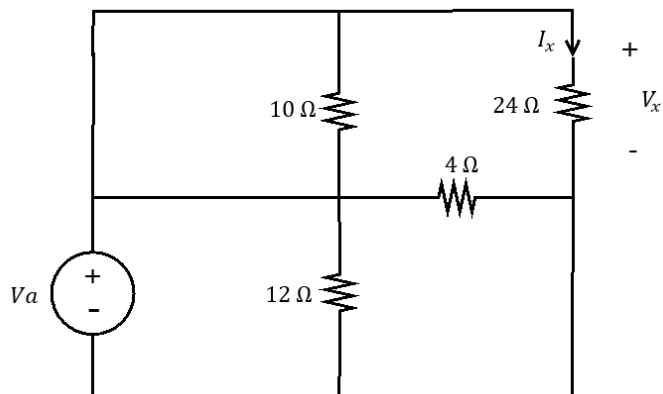


Question 2

0.5 out of 2 points



Calculate V_1 in the circuit if $V_x = 34$.

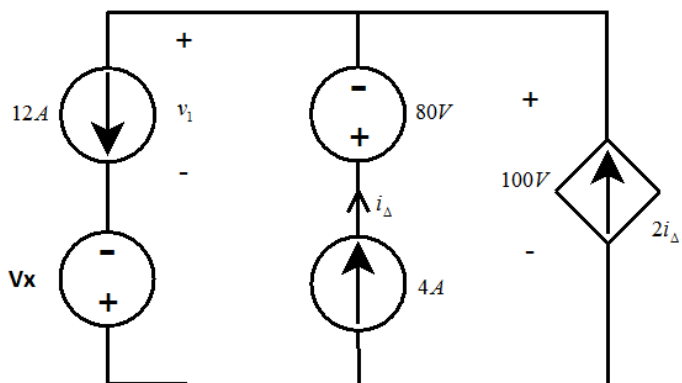


Question 3

0 out of 2 points



Given: $V_S = 7\text{ V}$, $R_1 = 79\Omega$, $R_2 = 61\Omega$, $R_3 = 41\Omega$, $R_4 = 59\Omega$, $R_5 = 47\Omega$, Determine the power, P_1 , dissipated in R_5 .

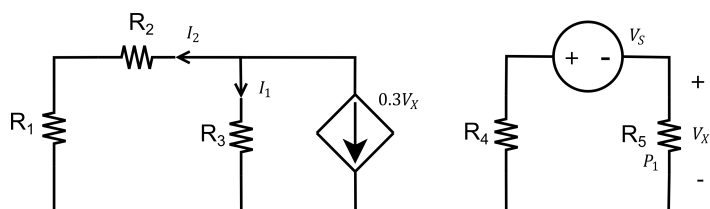


Question 4

2 out of 2 points




With $i_1 = 3\text{ A}$. Determine i_2 .

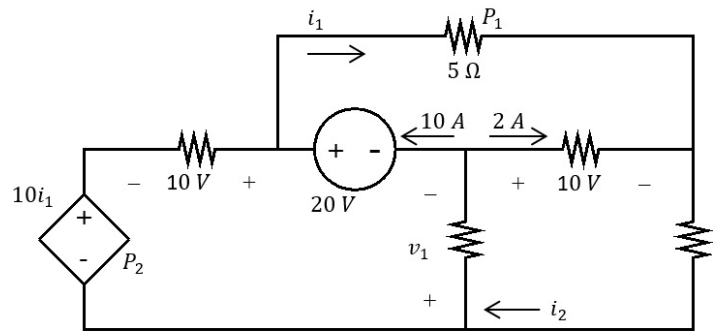


Question 5

0.4 out of 2 points

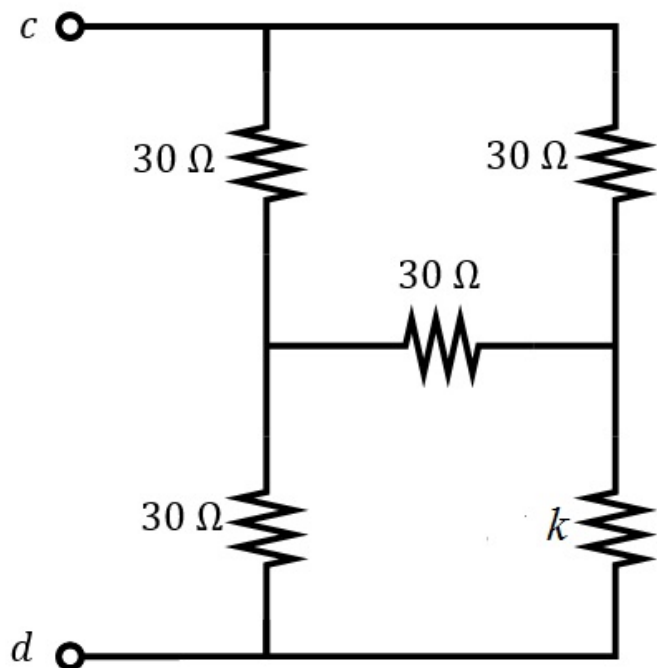With $k = 32\Omega$ find R_{cd} 

Question 6

2 out of 2 points

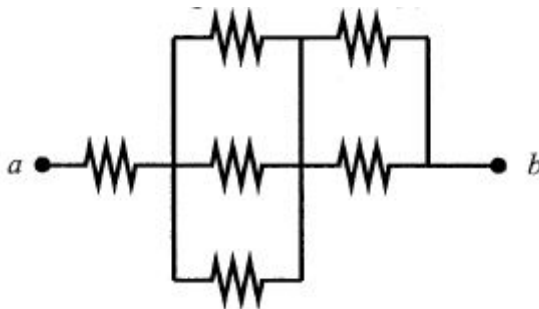
Determine the equivalent resistance between a-b if all the resistors are 2Ω .

Question 7

0 out of 2 points



How many nodes (n) [n], independent loops (l) [l], and branches (b) [b] are there in the following circuit?

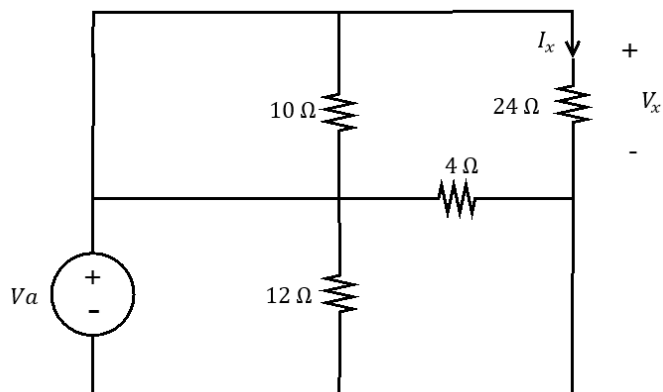


Question 8

0 out of 2 points



Given:

$I_1=8\text{A}$, $R_1=84\Omega$, $I_2=26\text{A}$, $R_2=68\Omega$, $I_3=9\text{A}$ and $R_3=70\Omega$, determine I_{x2}

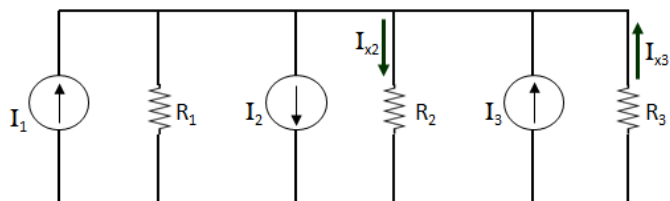


Question 9

2 out of 2 points



Assume $i_T = 11\text{ mA}$, and calculate i_y .

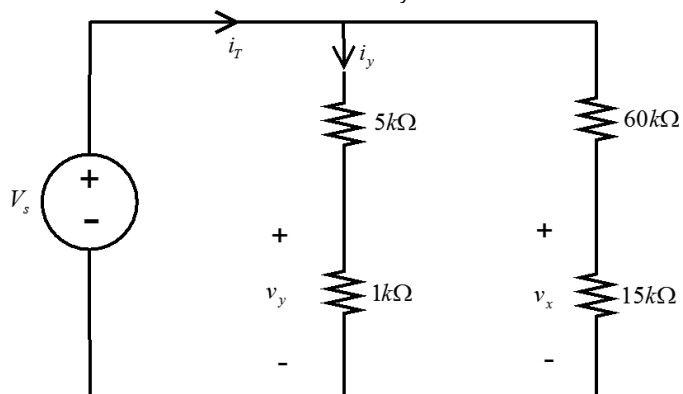


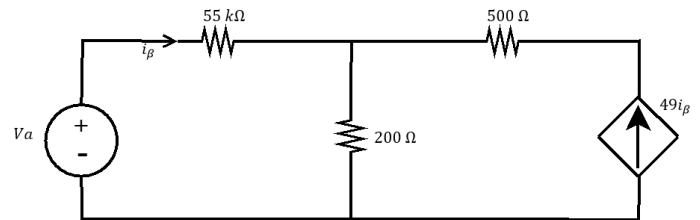Question 10

0 out of 2 points



Determine i_β using Kirchoff's laws and $V_a = 8.1\text{ V}$.



Tuesday, July 30, 2019 3:31:34 PM SAST

← OK