



Review Test Submission: Assignment Week 2

User Mr W (Wouter) W Nel

Course EBN 122 S2 2017

Test Assignment Week 2

Started 7/24/17 3:03 PM

Submitted 7/29/17 5:48 PM

Due Date 7/31/17 11:59 PM

Status Completed

Attempt Score 13.7 out of 22 points

Time 122 hours, 44 minutes

Elapsed

Instructions Read over the document *ClickUP Assignments Instructions*.

Save the answer to each question as you complete it.

At the end of the assignment click Save and Submit.

Give your final correct answer 3 significant digits.

Make sure you use the FULL STOP for your decimal place marker.

You must indicate the units, unless otherwise specified:

- There must be NO space between the answer and the units
- There must be between 1 and 3 digits to the left of the decimal point. *This means that you need enter 1kV rather than 1000V and 100mV rather than 0.1V*
- Write out 'ohm' to indicate Ω (use singular)
- Use 'u' to indicate micro.
- Only use pico(**p**), nano(**n**), micro(**u**), milli(**m**), kilo(**k**), mega(**M**), giga(**G**) and tera(**T**); do not use centi, deci and deca


Results All Answers, Submitted Answers, Correct Answers, Feedback, Incorrectly Answered Questions
Displayed

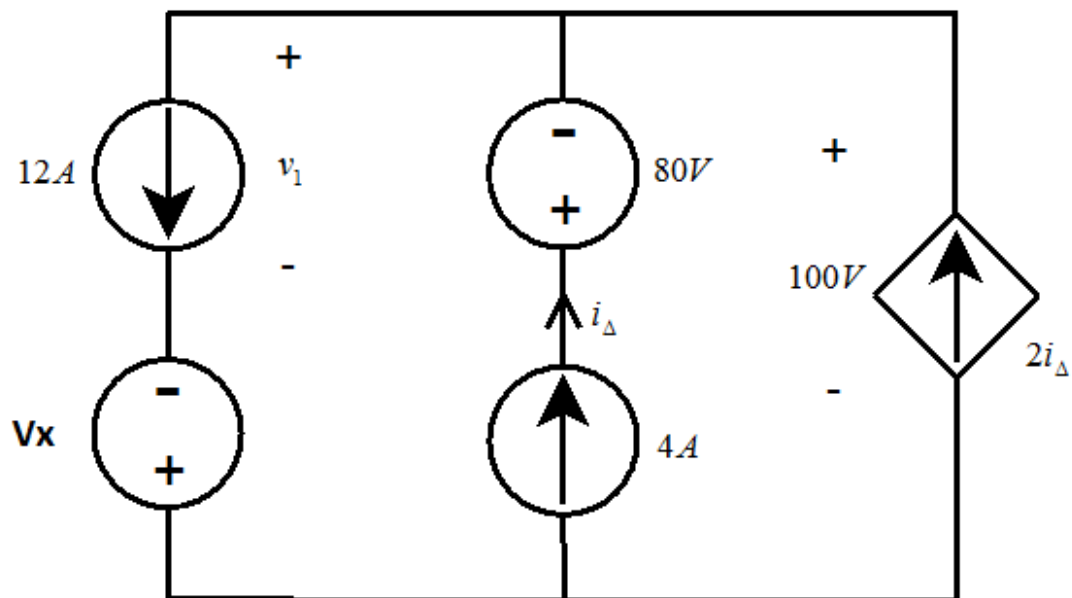Question 1

2 out of 2 points



Calculate V_1 in the circuit if $V_X=27$.



Selected Answer: ☒ 127V


Correct Answer: ☒ 127.000 ± 5% (V)

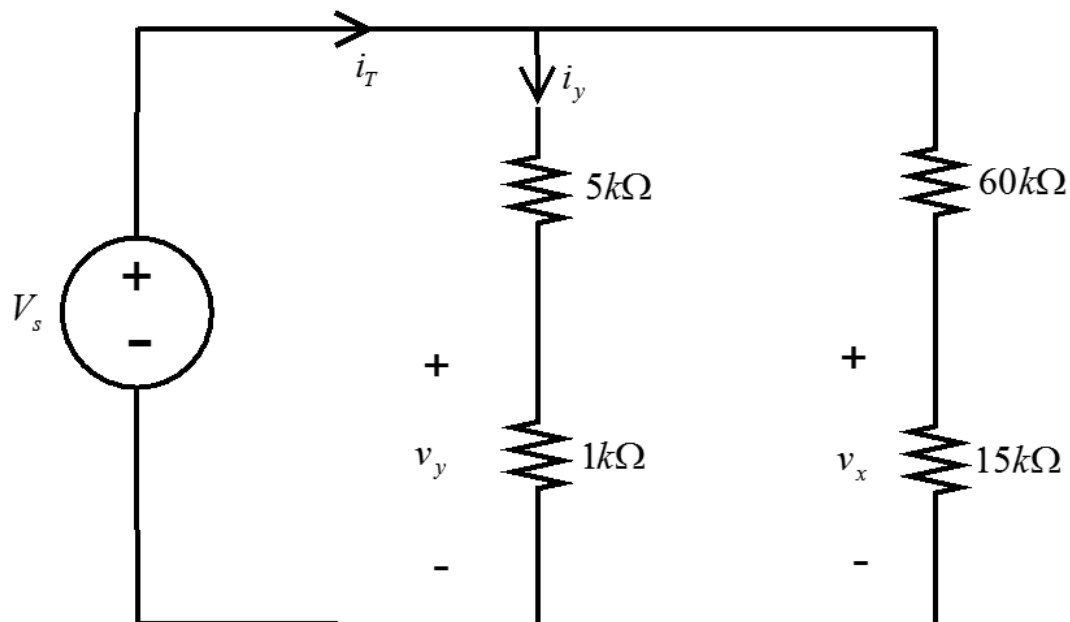Question 2

2 out of 2 points



Assume $V_s = 16$ V, and calculate and i_y .



Selected Answer: ☒ 2.67mA


Correct Answer: ☒ 2.67 ± 5% (mA)

Question 3

2 out of 2 points



If $V_a = 18$ V, calculate I_x

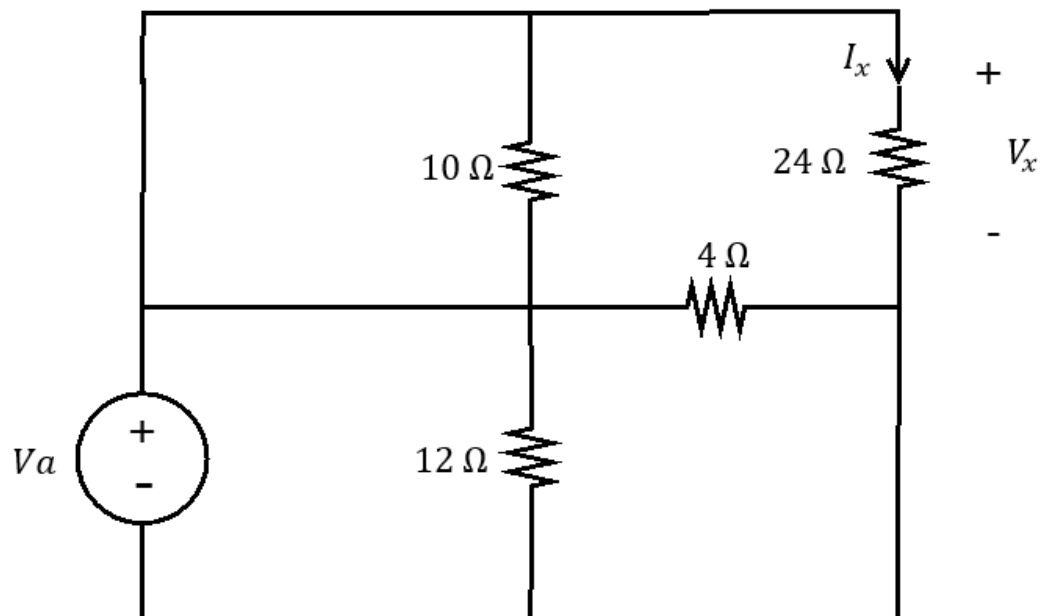

Selected Answer: ☒ 750mA


Correct Answer: ☒ 750.000 $\pm$ 5% (mA)

Question 4

0 out of 2 points



If $V_a = 47\text{ V}$, calculate V_x

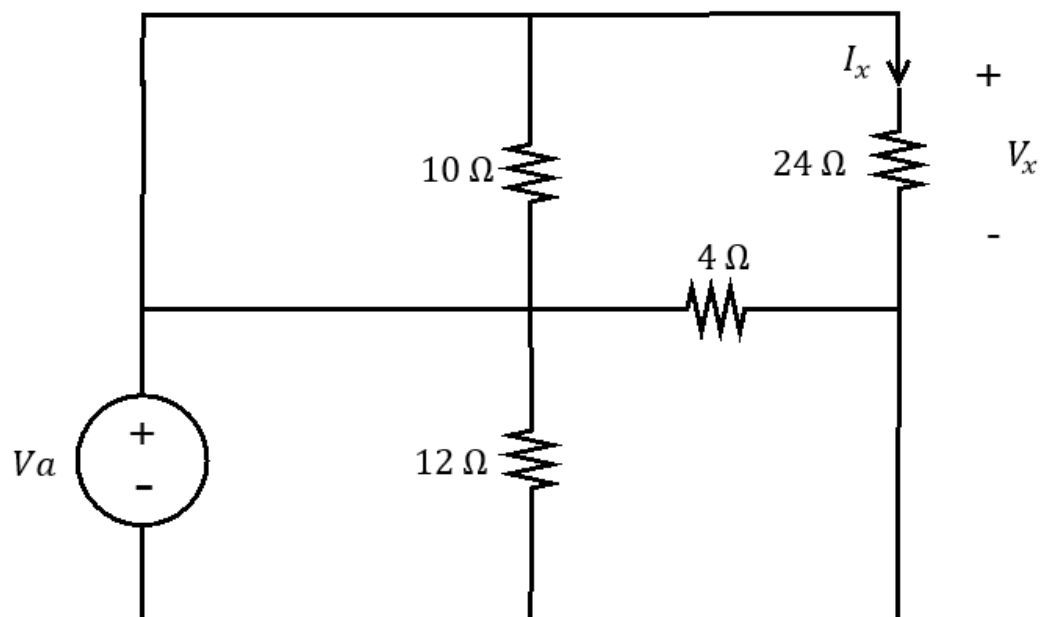

Selected Answer: ☒ 1.96A


Correct Answer: ☒ 47.000 $\pm$ 5% (V)

Question 5

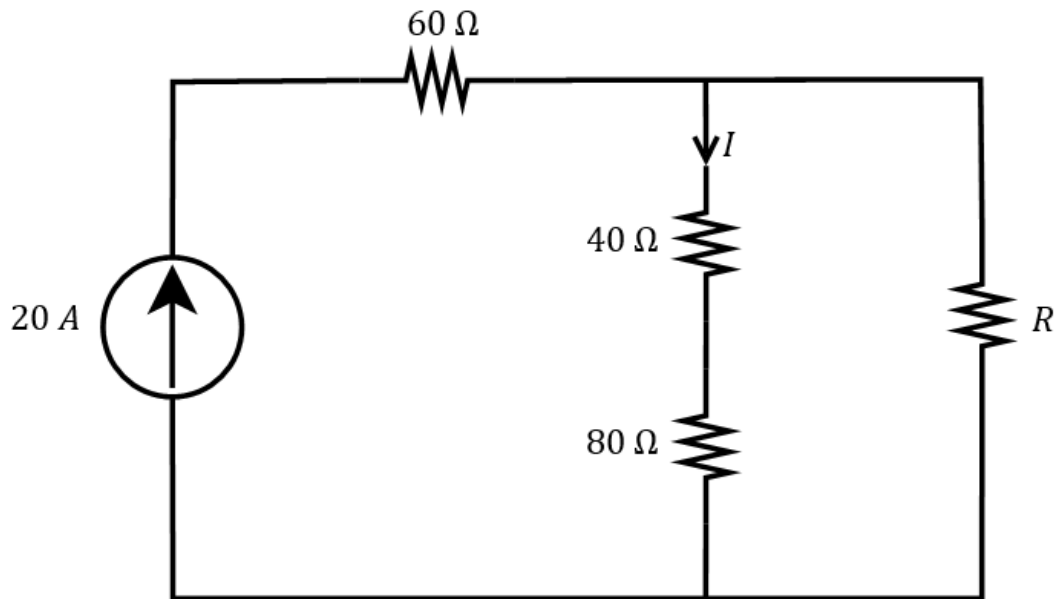0.5 out of 2 points



Determine the power (kW) associated with the $80\ \Omega$ resistor if $R = 37\ \Omega$.



Selected Answer: ✗ 3.55kW


Correct Answer: ✓ $1.78 \pm 5\%$ (kW)

Question 6

2 out of 2 points



With $i_1 = 3\text{ A}$. Determine i_2 .

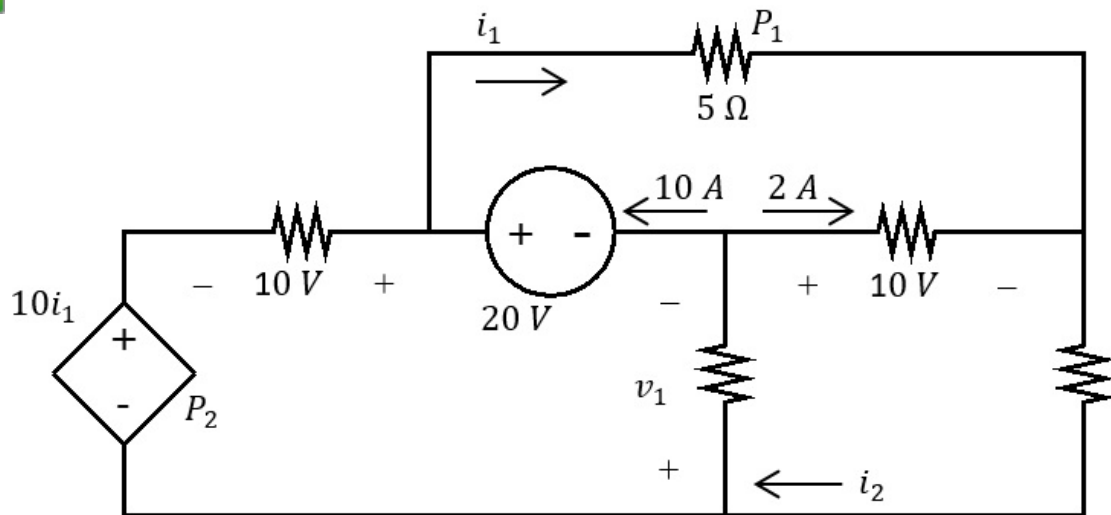

Selected Answer: ✓ 5A


Correct Answer: ✓ $5.000 \pm 5\%$ (A)

Question 7

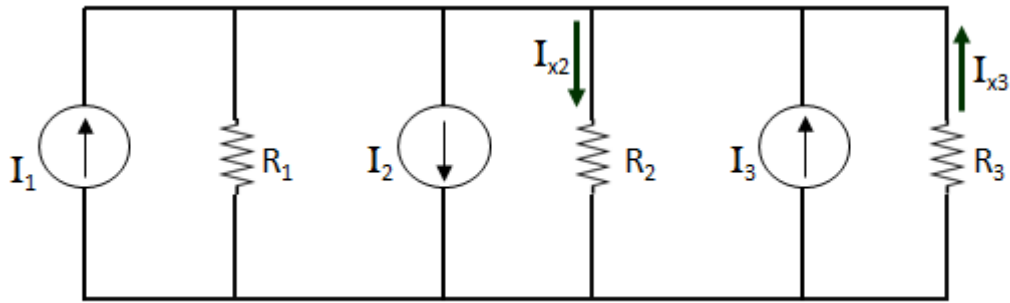0.2 out of 2 points



Given:
 $I_1 = 5\text{ mA}$, $R_1 = 78\ \Omega$, $I_2 = 3\text{ mA}$, $R_2 = 90\ \Omega$, $I_3 = 5\text{ mA}$ and $R_3 = 69\ \Omega$, determine voltage across R_2 .



Selected Answer: ✗ 742mV


Correct Answer: ✓ 182.176 ± 5% (mV)

Question 8

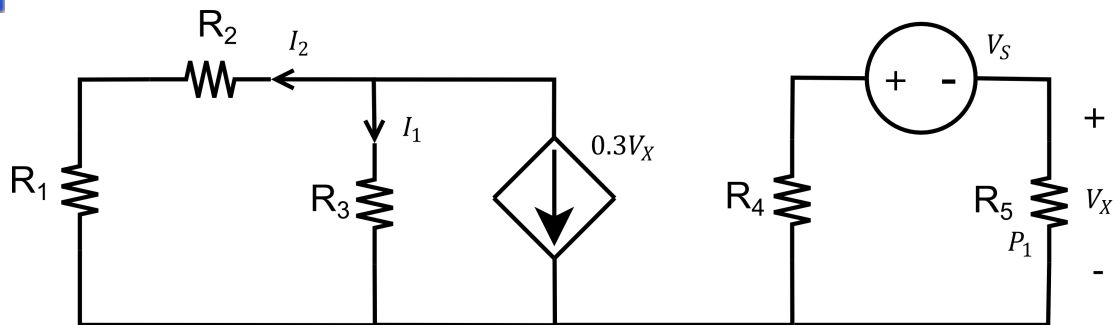0.5 out of 2 points



Given: $V_S = 11\text{V}$, $R_1 = 31\Omega$, $R_2 = 39\Omega$, $R_3 = 36\Omega$, $R_4 = 26\Omega$, $R_5 = 45\Omega$, Determine the current, I_1 .



Selected Answer: ✗ -1.38A


Correct Answer: ✓ 1.381 ± 5% (A)

Question 9

0.5 out of 2 points



If $i_R = 4.3\text{A}$, calculate V_S .

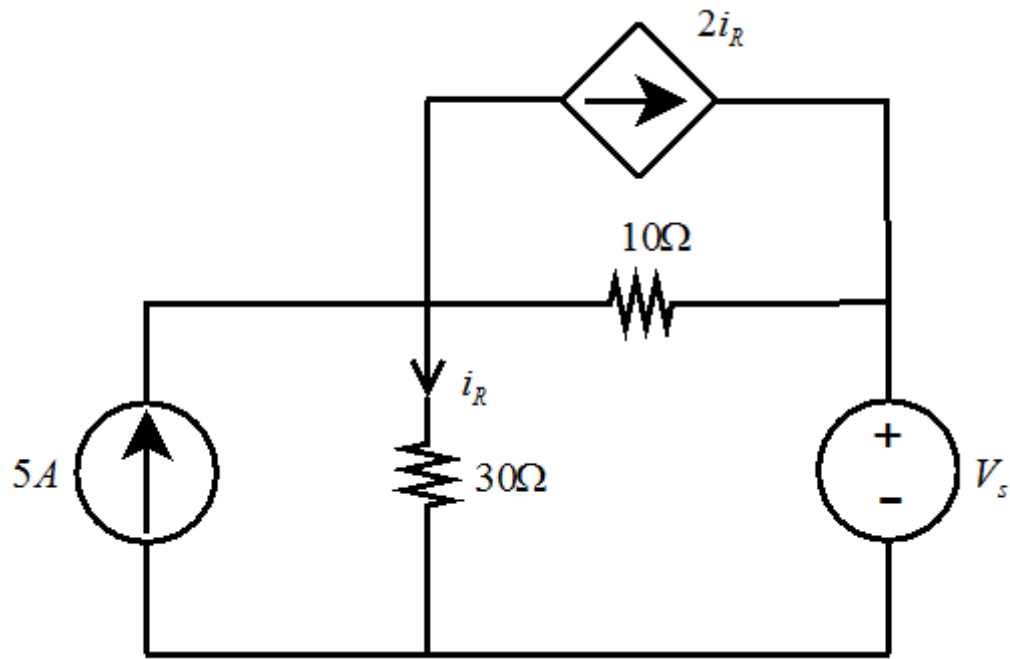

Selected Answer: ✗ -208V


Correct Answer: ✓ 208.00 ± 5% (V)

Question 10

2 out of 2 points



Calculate R_{eq} when $R_I = 288\Omega$.

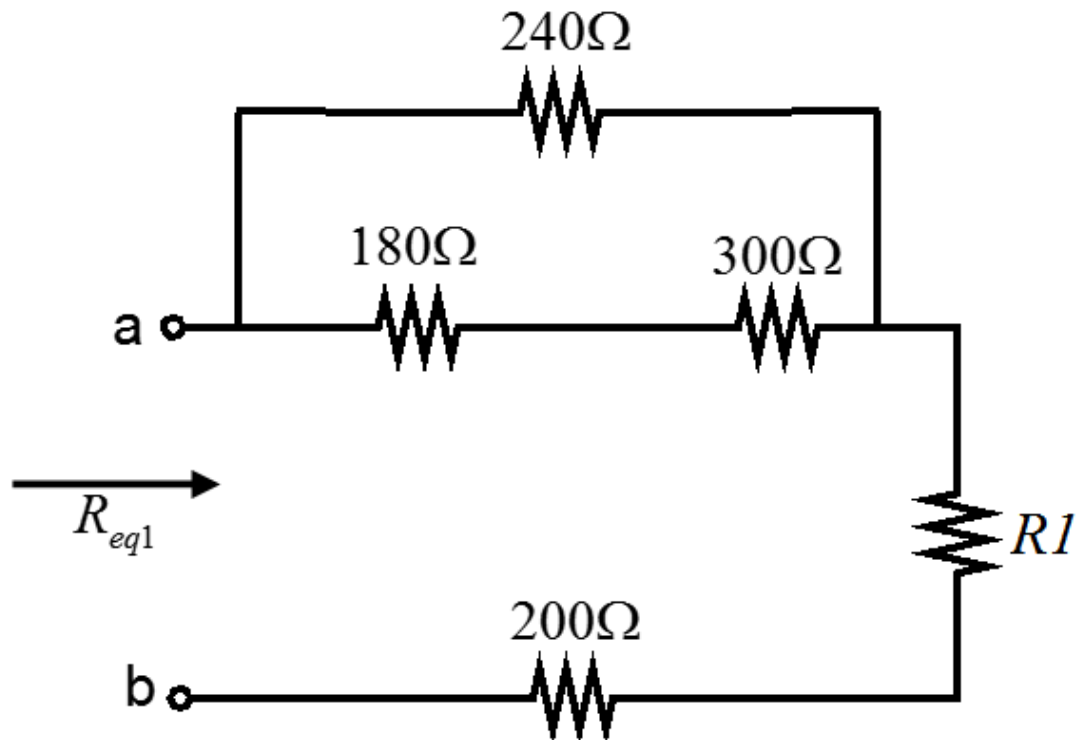

Selected Answer: ✓ 648ohm


Correct Answer: ✓ 648 ± 5% (ohm)

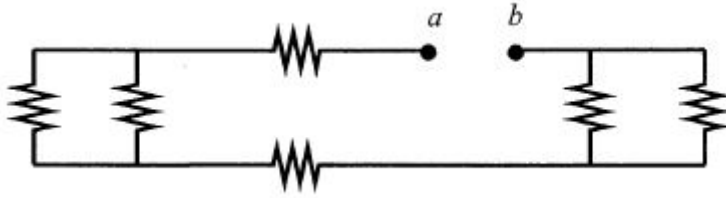Question 11

2 out of 2 points



Determine the equivalent resistance at terminals a-b for circuit when the resistors = 2 Ohms.



Selected Answer: ☒ 6ohm

Correct Answer: ☒ 6.00 ± 5% (ohm)

Saturday, July 29, 2017 5:48:56 PM SAST

← OK