



Review Test Submission: Assignment Week 2

User	Mr W (Wouter) W Nel
Course	EBN 122 S2 2017
Test	Assignment Week 2
Started	7/29/17 6:10 PM
Submitted	7/30/17 6:56 PM
Due Date	7/31/17 11:59 PM
Status	Completed
Attempt Score	17.5 out of 22 points
Time Elapsed	24 hours, 46 minutes
Instructions	Read over the document <i>ClickUP Assignments Instructions</i> .

Save the answer to each question as you complete it.

At the end of the assignment click Save and Submit.

Give your final correct answer 3 significant digits.

Make sure you use the FULL STOP for your decimal place marker.

You must indicate the units, unless otherwise specified:

- There must be NO space between the answer and the units
- There must be between 1 and 3 digits to the left of the decimal point. *This means that you need enter 1kV rather than 1000V and 100mV rather than 0.1V*
- Write out 'ohm' to indicate Ω (use singular)
- Use 'u' to indicate micro.
- Only use pico(**p**), nano(**n**), micro(**u**), milli(**m**), kilo(**k**), mega(**M**), giga(**G**) and tera(**T**); do not use centi, deci and deca


Results Displayed	All Answers, Submitted Answers, Correct Answers, Feedback, Incorrectly Answered Questions
-------------------	---

Question 1

2 out of 2 points



Determine V_{xy} if $V_x = 11$ V.

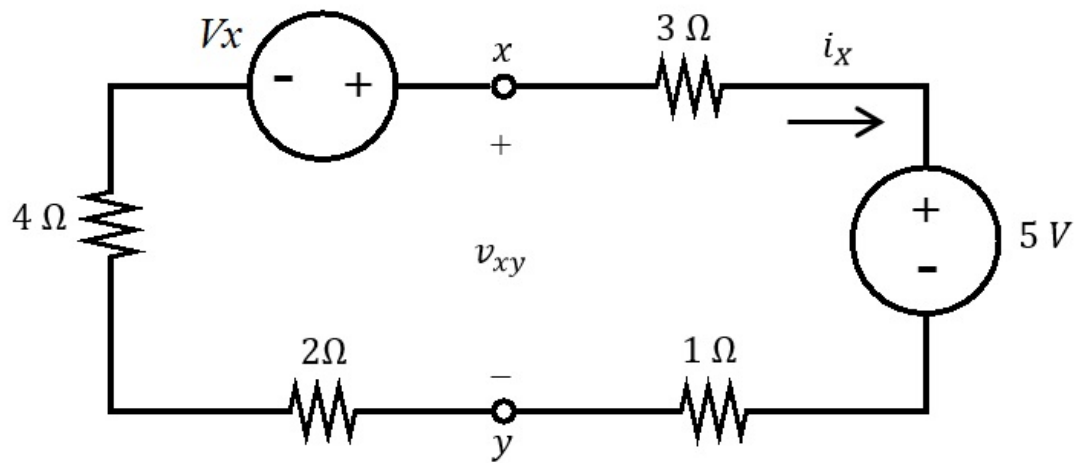

Selected Answer: ☒ 7.4V


Correct Answer: ☒ 7.400 ± 5% (V)

Question 2

2 out of 2 points



Assume $i_T = 9$ mA, and calculate i_y .

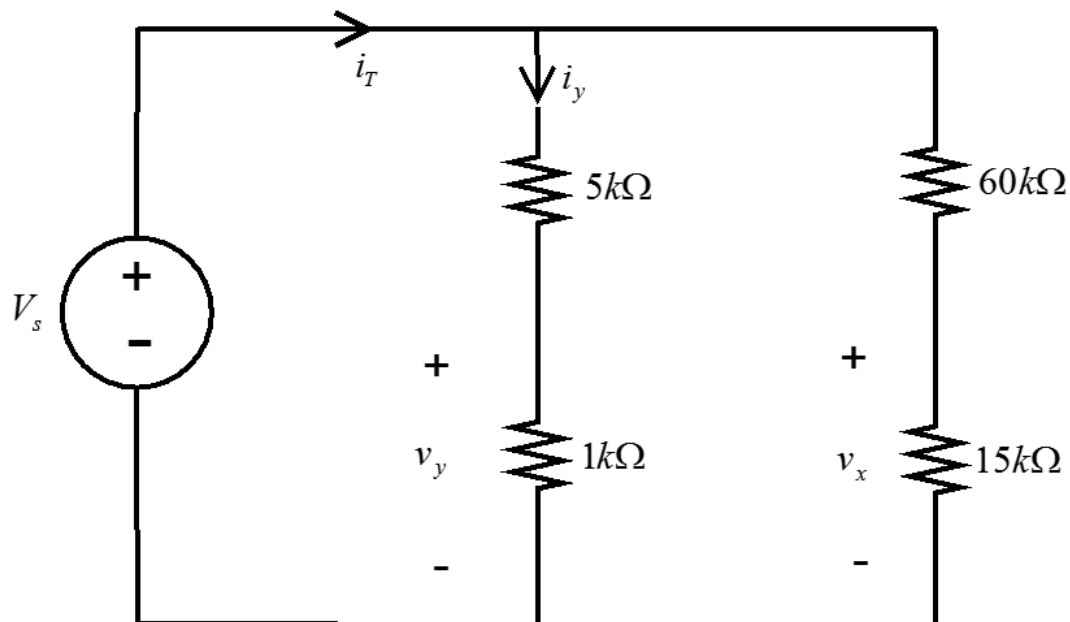

Selected Answer: ☒ 8.33mA


Correct Answer: ☒ 8.33 ± 5% (mA)

Question 3

2 out of 2 points



If $V_a = 11$ V, calculate V_x

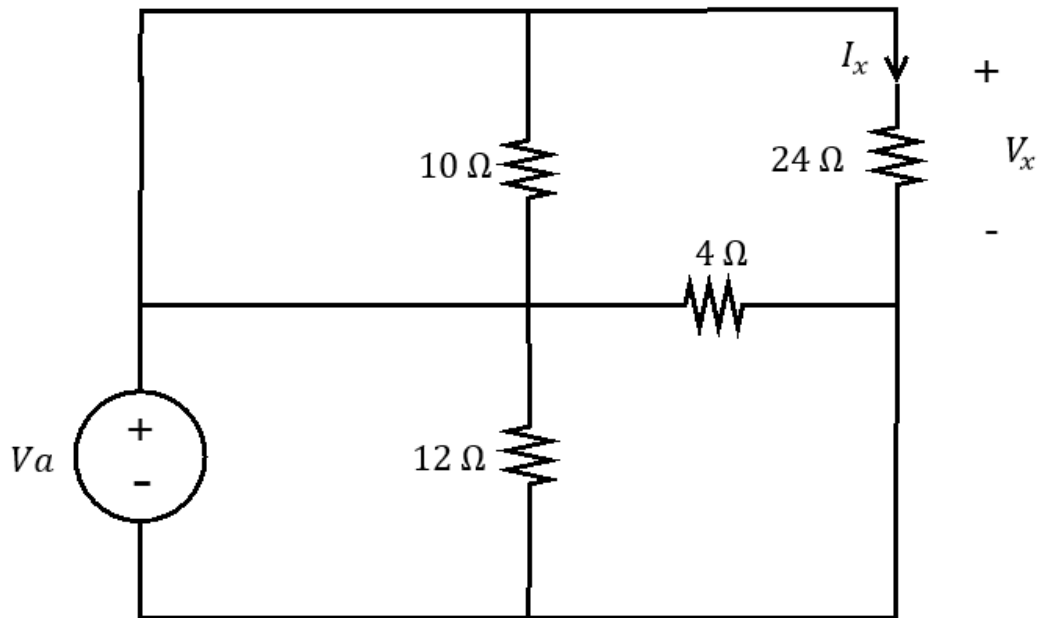

Selected Answer: ☒ 11V


Correct Answer: ☒ 11.000 $\pm$ 5% (V)

Question 4

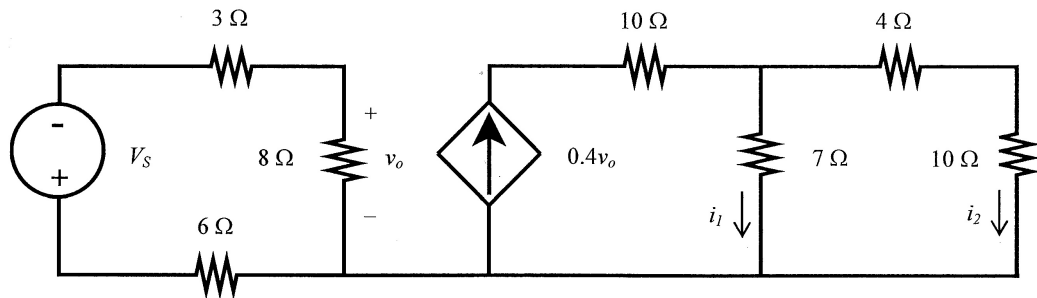0.5 out of 2 points



Determine V_o if $V_S = 8$ in the graph below



Selected Answer: ☒ 3.76V


Correct Answer: ☒ -3.76 $\pm$ 5% (V)

Question 5

2 out of 2 points



Determine i_o if $v_o = 8$ V.

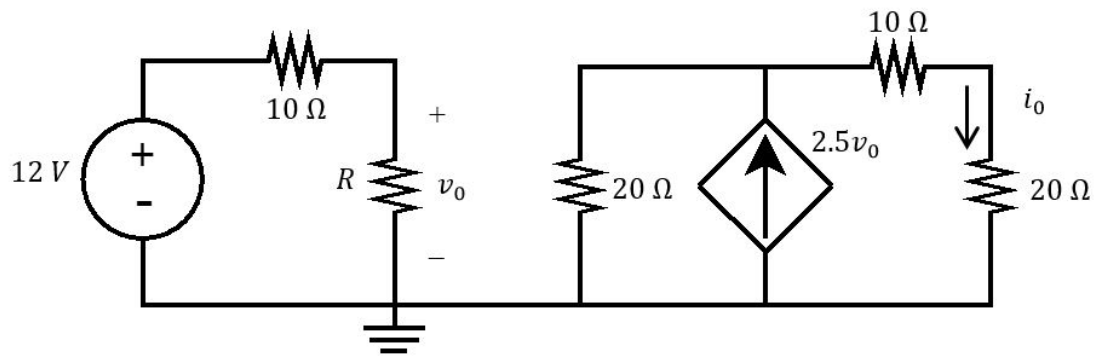

Selected Answer: ☒ 8A


Correct Answer: ☒ 8.00 ± 2% (A)

Question 6

2 out of 2 points



Determine P_1 if $I_0 = 9$ A.

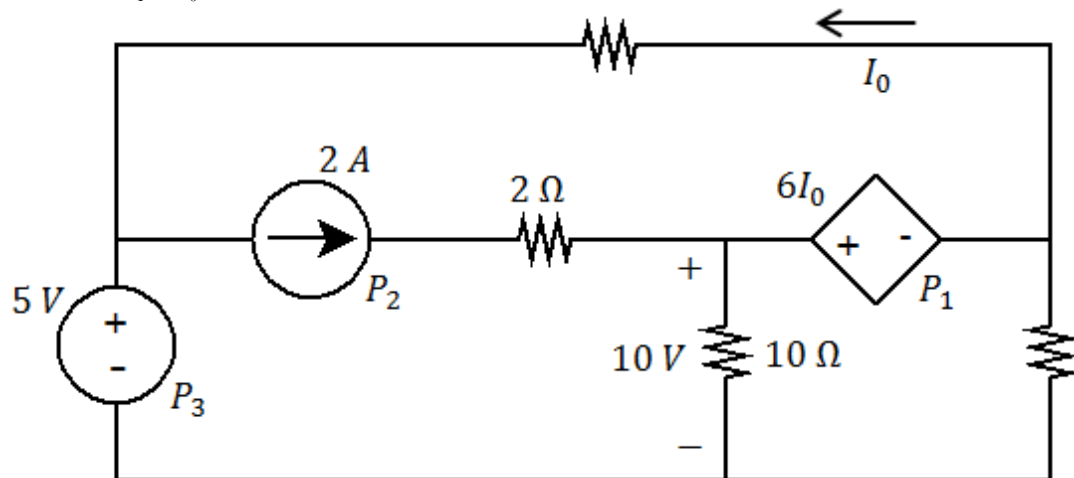

Selected Answer: ☒ 54W

Correct Answer: ☒ 54.00 ± 5% (W)


Question 7

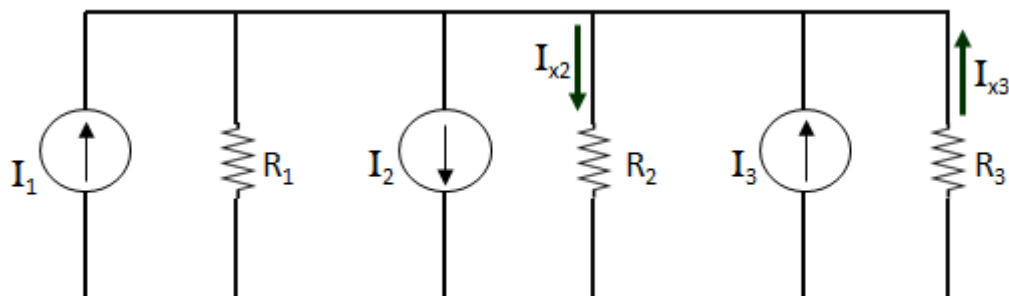0.5 out of 2 points



Given:

$I_1=9\text{A}$, $R_1=70\Omega$, $I_2=29\text{A}$, $R_2=97\Omega$, $I_3=9\text{A}$ and $R_3=63\Omega$, determine I_{x2}



Selected Answer: ☒ 5.71A


Correct Answer:  $-2.802 \pm 5\%$ (A)

Question 8

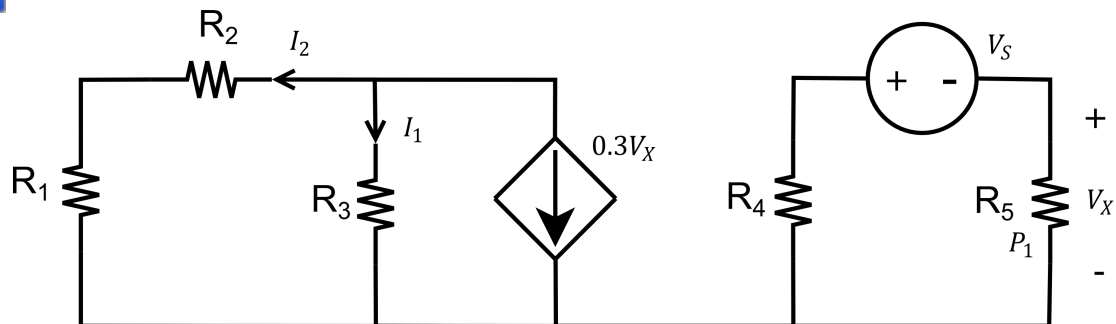0.5 out of 2 points



Given: $V_S = 23\text{V}$, $R_1=29\Omega$, $R_2=49\Omega$, $R_3=72\Omega$, $R_4=24\Omega$, $R_5=44\Omega$, Determine the current, I_2 .



Selected Answer:  7.29A


Correct Answer:  $2.143 \pm 5\%$ (A)

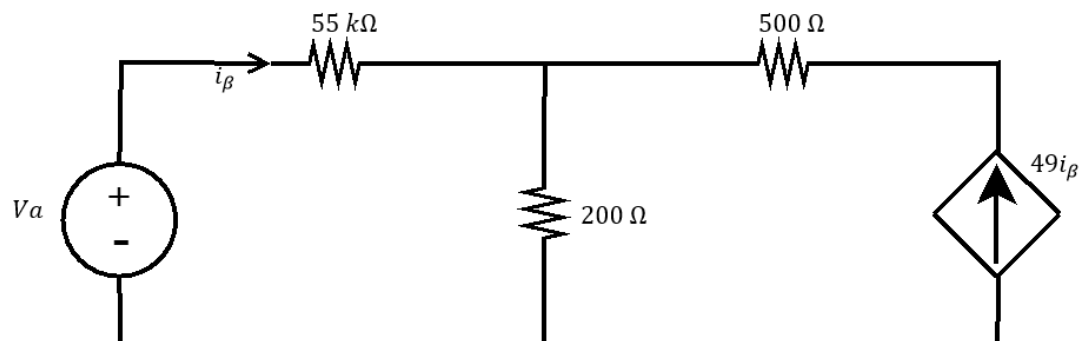Question 9

2 out of 2 points



Determine i_β using Kirchoff's laws and $V_a = 1\text{ V}$.



Selected Answer:  15.4uA


Correct Answer:  $15.38 \pm 5\%$ (uA)

Question 10

2 out of 2 points



Calculate R_{eq} when $R_I = 377\Omega$.

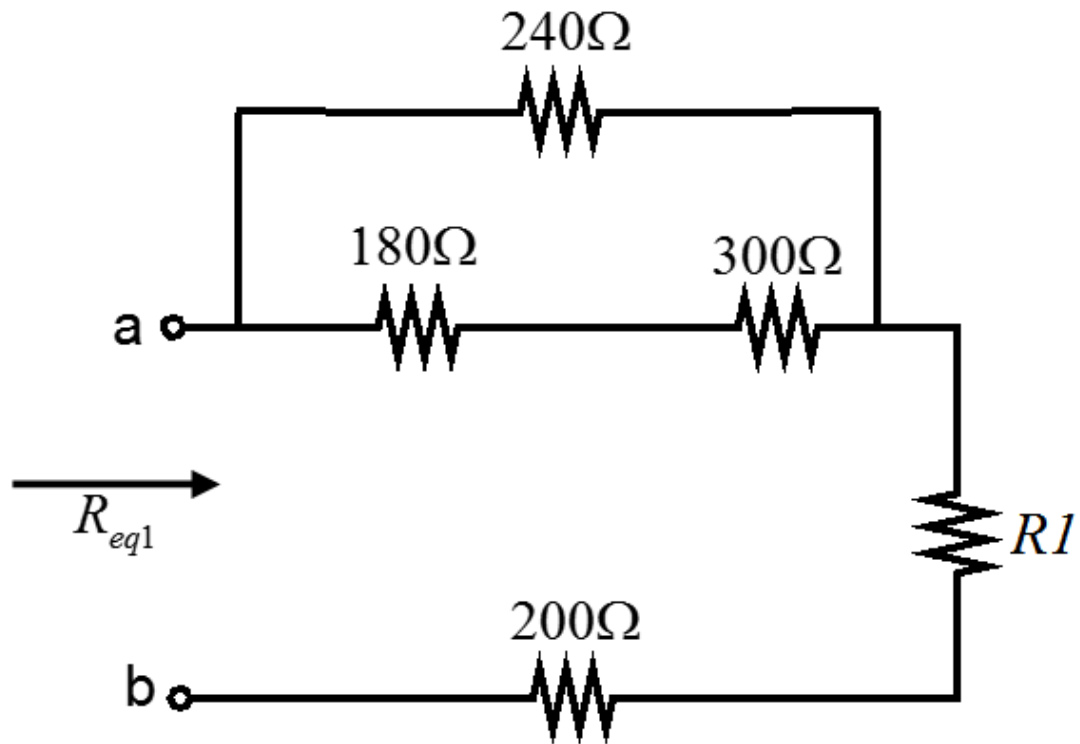

Selected Answer: ☒ 737ohm


Correct Answer: ☒ $737 \pm 5\%$ (ohm)

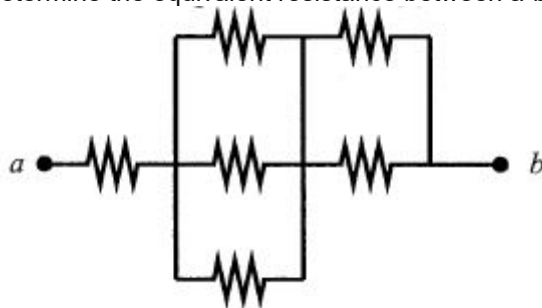Question 11

2 out of 2 points



Determine the equivalent resistance between a-b if all the resistors are 3Ω .



Selected Answer: ☒ 5.5ohm

Correct Answer: ☒ $5.50 \pm 5\%$ (ohm)

Sunday, July 30, 2017 6:56:43 PM SAST

← OK

