



Review Test Submission: Assignment Week 2

User Mr W (Wouter) W Nel

Course EBN 122 S2 2017

Test Assignment Week 2

Started 7/31/17 12:08 PM

Submitted 7/31/17 4:12 PM

Due Date 7/31/17 11:59 PM

Status Completed

Attempt Score 17.5 out of 22 points

Time 4 hours, 3 minutes

Elapsed

Instructions Read over the document *ClickUP Assignments Instructions*.

Save the answer to each question as you complete it.

At the end of the assignment click Save and Submit.

Give your final correct answer 3 significant digits.

Make sure you use the FULL STOP for your decimal place marker.

You must indicate the units, unless otherwise specified:

- There must be NO space between the answer and the units
- There must be between 1 and 3 digits to the left of the decimal point. *This means that you need enter 1kV rather than 1000V and 100mV rather than 0.1V*
- Write out 'ohm' to indicate Ω (use singular)
- Use 'u' to indicate micro.
- Only use pico(**p**), nano(**n**), micro(**u**), milli(**m**), kilo(**k**), mega(**M**), giga(**G**) and tera(**T**); do not use centi, deci and deca


Results All Answers, Submitted Answers, Correct Answers, Feedback, Incorrectly Answered Questions
Displayed

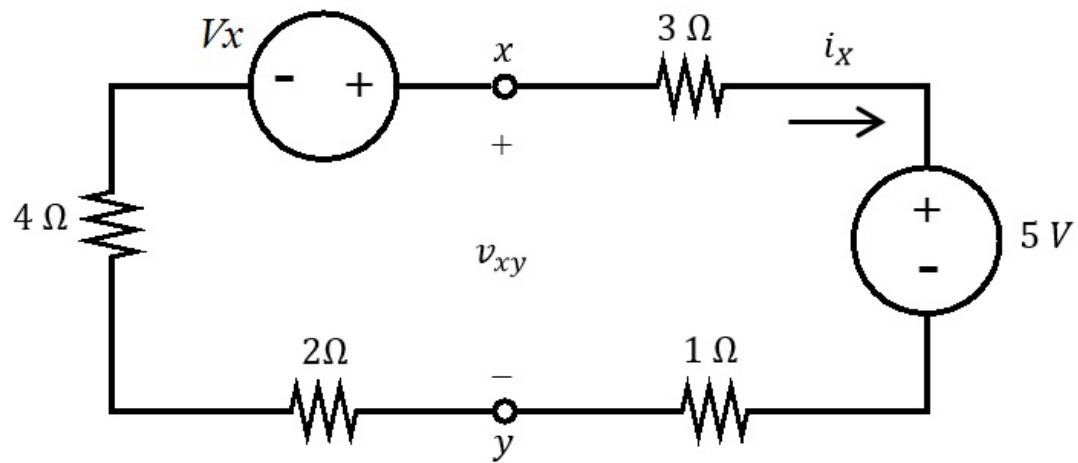Question 1

2 out of 2 points



Determine V_{xy} if $V_x = 14 \text{ V}$.



Selected Answer: ☒ 8.6V


Correct Answer: ☒ 8.600 ± 5% (V)

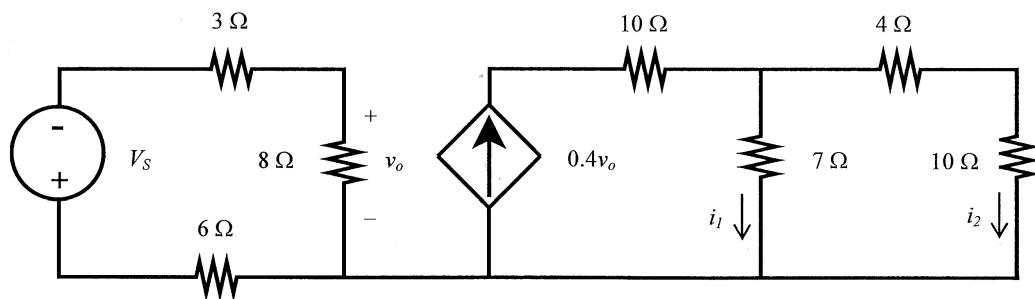Question 2

2 out of 2 points



Determine i_2 if $V_o = 13V$ in the figure below:



Selected Answer: ☒ 1.73A


Correct Answer: ☒ 1.73 ± 5% (A)

Question 3

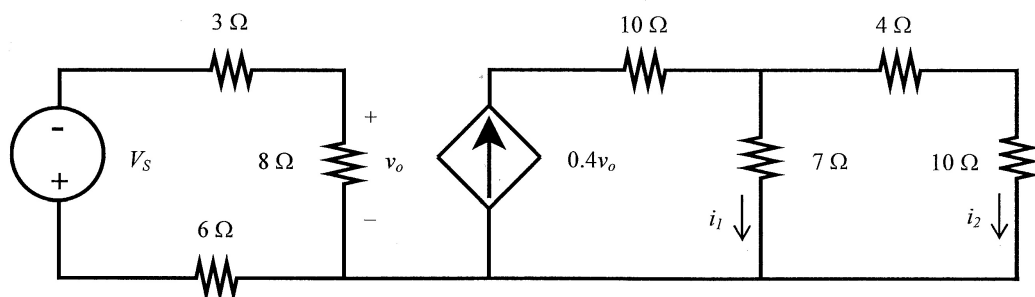0.5 out of 2 points



Determine V_o if $V_S = 12$ in the graph below




Selected Answer: ☒ 5.65V

Correct Answer: ☒ -5.65 ± 5% (V)


Question 4

2 out of 2 points

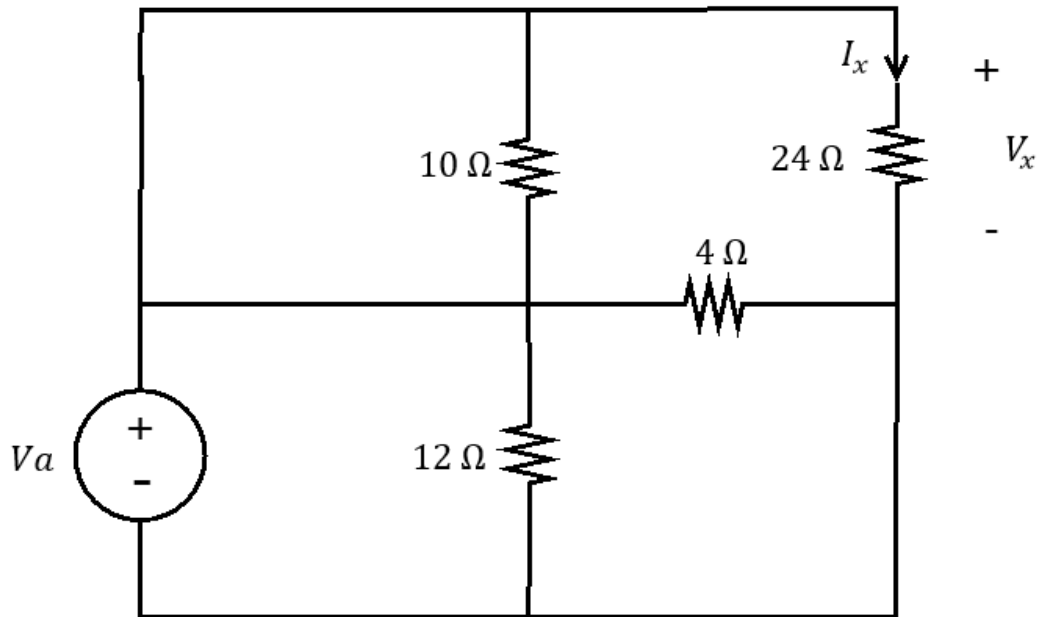If $V_a = 10\text{ V}$, calculate I_x Selected Answer: ☒ 417mACorrect Answer: ☒ 416.667 ± 5% (mA)

Question 5


0.5 out of 2 points

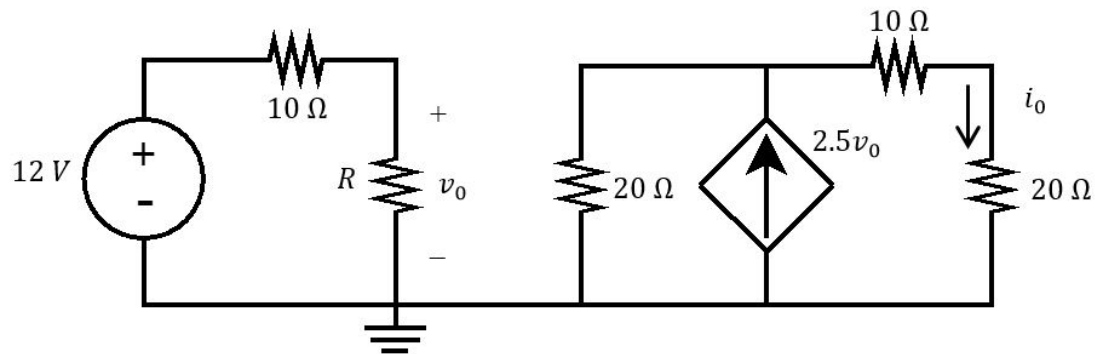Determine i_o if $v_o = 2\text{ V}$.Selected Answer: ☒ -10ACorrect Answer: ☒ 2.00 ± 2% (A)

Question 6

2 out of 2 points

Determine P_I if $I_o = 18\text{ A}$.

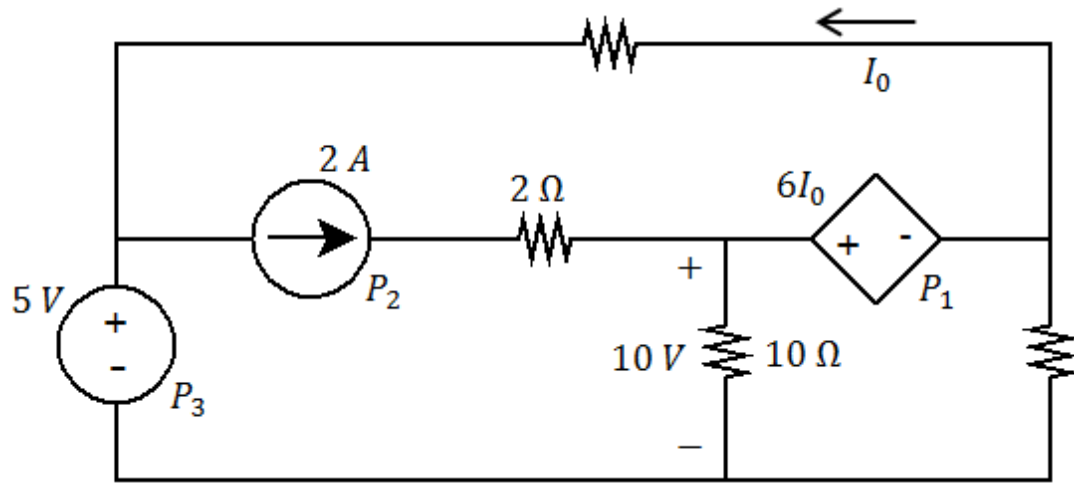

Selected Answer: ☒ 108W

Correct Answer: ☒ 108.00 ± 5% (W)


Question 7

2 out of 2 points



Given:

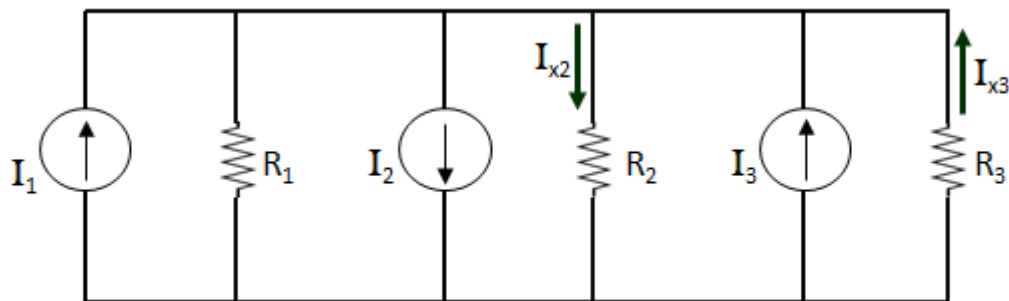☒ $I_1=8\text{mA}$, $R_1=81\Omega$, $I_2=3\text{mA}$, $R_2=82\Omega$, $I_3=5\text{mA}$ and $R_3=62\Omega$, determine voltage across R_2 .



Selected Answer: ☒ 246mV


Correct Answer: ☒ 245.882 ± 5% (mV)

Question 8

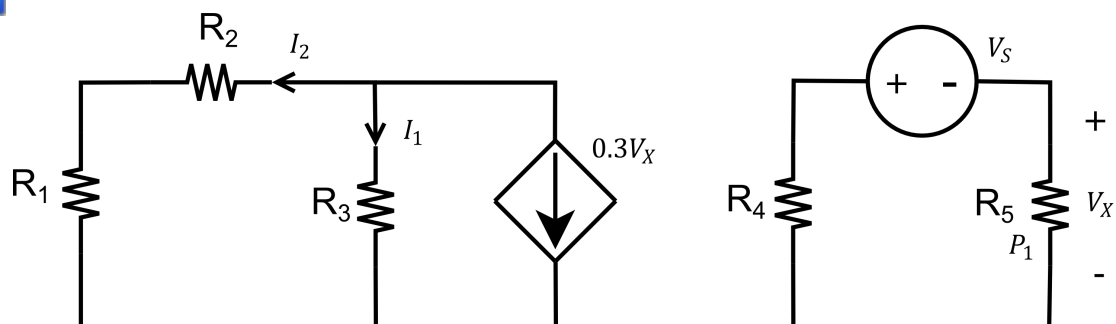0.5 out of 2 points




Given: $V_S = 23\text{V}$, $R_1=29\Omega$, $R_2=49\Omega$, $R_3=72\Omega$, $R_4=24\Omega$, $R_5=44\Omega$, Determine the current, I_2 .




Selected Answer: ☒ :: :: -2.14:::A

Correct Answer: ☒ $2.143 \pm 5\%$ (A)**Question 9**

2 out of 2 points

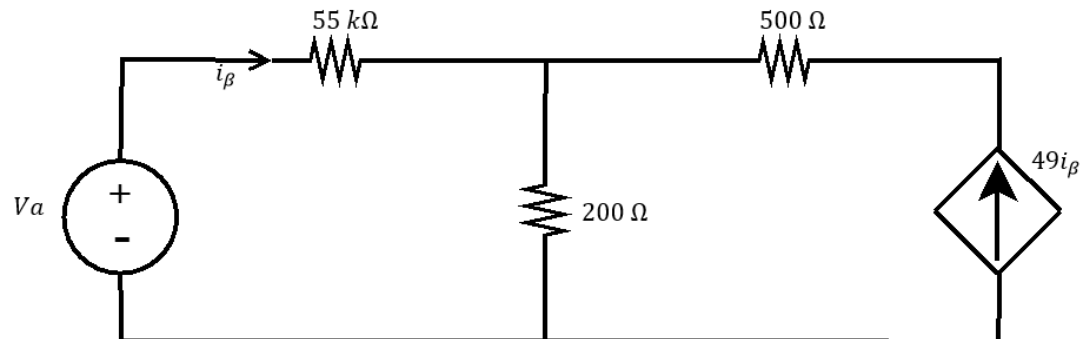Determine i_β using Kirchoff's laws and $V_a = 8.5$ V.Selected Answer: ☒ 131uACorrect Answer: ☒ $130.77 \pm 5\%$ (uA)**Question 10**


2 out of 2 points

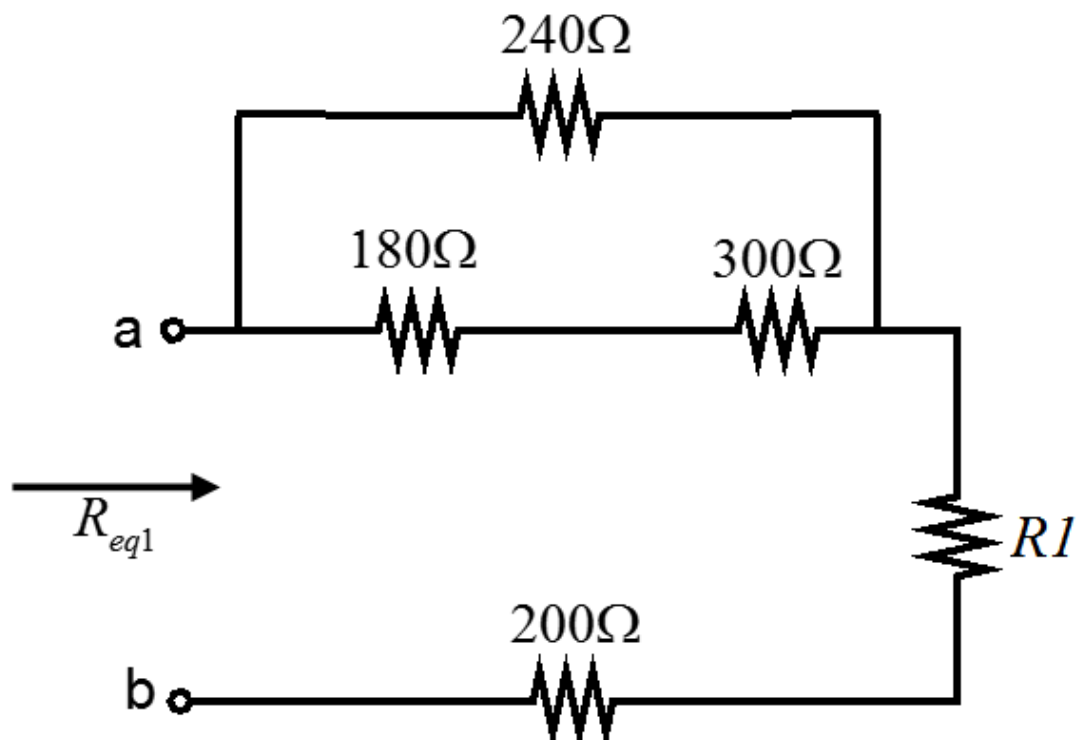Calculate R_{eq} when $R_I = 57\Omega$.Selected Answer: ☒ 417ohmCorrect Answer: ☒ $417 \pm 5\%$ (ohm)**Question 11**

2 out of 2 points



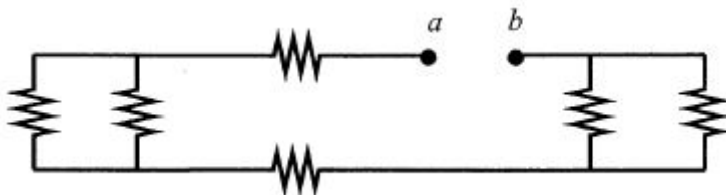Determine the equivalent resistance at terminals a-b for circuit when the resistors = 2 Ohms.



Selected Answer: ☒ 6ohm

Correct Answer: ☒ $6.00 \pm 5\%$ (ohm)

Monday, July 31, 2017 4:12:27 PM SAST

← OK