

2018EBN122C2**CLASS TEST**

Kopiereg voorbehou

21 September 2018

2018EBN122C2**KLASTOETS**

Copyright reserved

21 September 2018

MEMORANDUM

Maksimum punte: Maximum marks:	16	Volpunte: Full marks:	15
Duur van vraestel: Duration of paper:	30 min + 10 min to complete OCR form 30 min + 10 min om OKH vorm te voltooi	Oopboek / toeboek: Open / closed book:	Toe Closed
Totale aantal bladsye (hierdie blad ingesluit): Total number of pages (including this page):		8 + OCR	

Important

- Die eksamenregulasies van die Universiteit van Pretoria geld
The examination regulations of the University of Pretoria apply.
- **All questions must be answered on the Optical Character Recognition (OCR) form.**
Alle vrae moet op die Optiese Karakter Herkenning ('OCR')- vorm ingevul word.
- Read the instructions on the OCR form carefully.
Neem noukeurig kennis van die instruksies op die 'OCR'-vorm
- Answers must include units!
Antwoorde moet eenhede insluit!
- **Final answers must be written as real numbers and not as fractions, and must be rounded to 5 significant numbers**
Finale antwoorde moet as reële getalle geskryf word en nie as breuke nie, en moet afgerond word na 5 beduidende syfers.

Doseant(e) / Lecturer(s): D le Roux, JP de Villiers, JP Jacobs

INSTRUCTIONS**Do step 0 in the first 5 minutes of the session. (0-5 min)****Do step 1 in the first 30 minutes of the test. (5-35 min)****Do step 2 within the following 10 minutes. (35-45 min)****STEP 0 (-5 min to 0 min):** Complete the front page of the OCR form

STEP 1 (0 min to 30 min): Do your own calculations on the QUESTION PAPER. The question paper **will not** be taken in at the end of the test. Write down the answers for each question on the PRACTICE ANSWER SHEET. Be sure to include the units. The PRACTICE ANSWER SHEET **will not** be taken in at the end of the test.

STEP 2 (30 min to 40 min): Carefully copy the answers from the PRACTICE ANSWER SHEET to the OCR form.

- The Assessment ID is:

2018EBN122C2

- Use a mechanical pencil with 0.5mm HB lead to complete the form.
- Each cell should only have one character, and characters may not touch or cross the cell.
- **Do not use commas!** Please make use of full stops.

Examples

01	-	1	.	4	5						μ	A						
02	3	4	0								V							
03	1	5	.	2							k							
04	2	0									Ω							

INSTRUKSIES

Doen stap 0 in die eerste 5 minute van die *sessie*. (0-5 min)

Doen stap 1 in die eerste 30 minute van die *toets*. (5-35 min)

Doen stap 2 binne die daaropvolgende 10 minute. (35-45 min)

STAP 0 (-5 min to 0 min): Voltooi die voorblad van die *OCR*-vorm

STAP 1 (0 min to 30 min): Doen jou eie berekeninge op die *VRAESTEL*. Die *VRAESTEL* word **nie** aan die einde van die toets ingeneem nie. Skryf die antwoorde vir elke vraag op die *OEFEN-ANTWOORDBLAD*. Maak seker om eenhede in te sluit. Die *OEFEN-ANTWOORDBLAD* word **nie** ingeneem nie.

STAP 2 (35 min to 40 min): Dra die antwoorde vanaf die *OEFEN-ANTWOORDBLAD* oor na die *OCR*-vorm.

- Die *Assessment ID* is:


2018EBN122C2

- Gebruik 'n meganiese potlood met 0.5mm HB lood om antwoorde in te vul.
- Elke blokkie mag slegs een karakter bevat.
- Karakters mag nie aan die grense van die blokkies raak of oor dit steek nie.
- **Moenie kommas gebruik nie!** Maak asb. gebruik van punte.

Voorbeelde

01	-	1	.	4	5					m	A							
02	3	4	0							V								
03	1	5	.	2														
04	-	1								Ω								

Question 1-2 [4]		Vraag 1-2 [4]	
Determine the Thevenin equivalent voltage V_{Th} and resistance R_{Th} with reference to terminals $a-b$.		Bepaal die Thevenin ekwivalente spanning V_{Th} en weerstand R_{Th} met verwysing tot terminale a en b .	
01	V_{Th}	01	V_{Th}
02	R_{Th}	02	R_{Th}

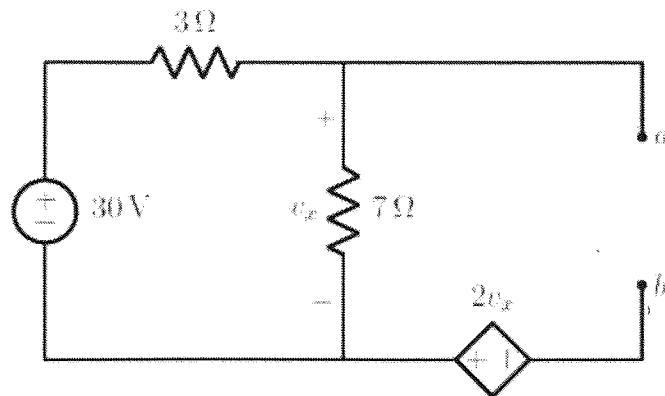

V_{Th} :

KVL: $v_x + V_{Th} + 2v_x = 0$


$$v_x = 30 \cdot \frac{7}{10} = 21 \text{ V}$$

$$\therefore 21 + V_{Th} + 42 = 0$$

$$V_{Th} = -63 \text{ V}$$

$\begin{matrix} \text{---} & a & \text{---} \\ & | & \\ & | & \\ & | & \\ \text{---} & b & \text{---} \end{matrix}$ V_{Th}

R_{Th} :

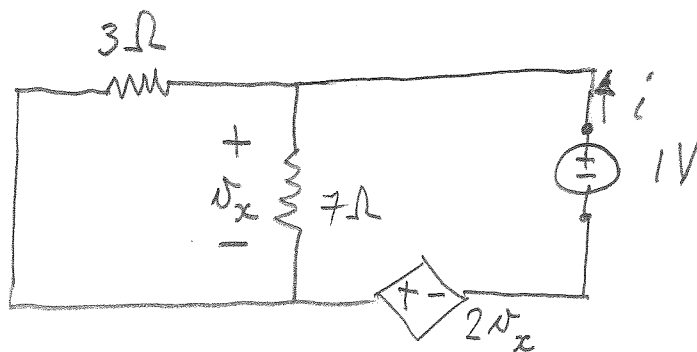

$$v_x - 1 + 2v_x = 0$$

$$v_x = i (3 \parallel 7)$$


$$= 2.1 i$$

$$2.1 i - 1 + 4.2 i = 0$$

$$\Rightarrow i = 0.15873 \text{ A}$$

$$R_{Th} = \frac{1}{i} = 6.3 \Omega$$

Question 3 [2]		Vraag 3 [2]	
03	It is known that maximum power is delivered to the $4\ \Omega$ load resistor. Determine R_1 .	03	Dit is bekend dat maksimum drywing oorgedra word aan die $4\ \Omega$ lasweerstand. Bepaal R_1 .

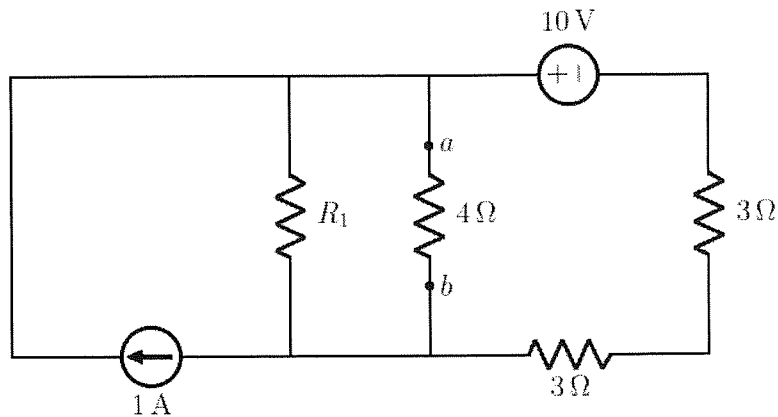


Max power transfer ^{to $4\ \Omega$} implies
 $R_{TH} = 4\ \Omega$

$$R_{TH} = R_1 \parallel (3 + 3)$$


$$4 = \frac{6R_1}{6 + R_1}$$

$$24 + 4R = 6R \Rightarrow R_1 = 12\ \Omega$$

Question 4 - 6 [4]		Vraag 4 - 6 [4]	
Simplify the circuit on the left by means of source transformation so that it looks like the one on the right. Determine:		Vereenvoudig die stroombaan aan die linkerkant met behulp van brontransformasie sodat dit lyk soos die kringbaan aan die regterkant. Bepaal:	
04	R_o [1]	04	R_o [1]
05	A [1]	05	A [1]
06	B [2]	06	B [2]

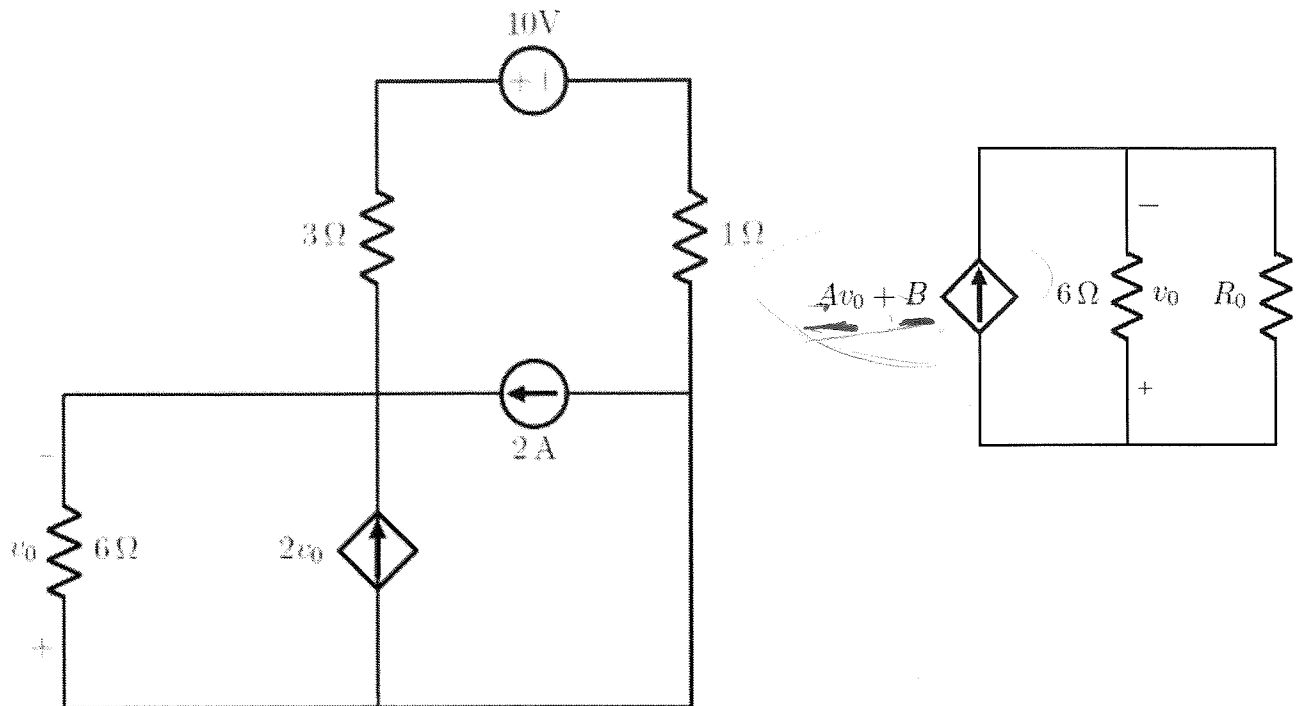


Q 4-6

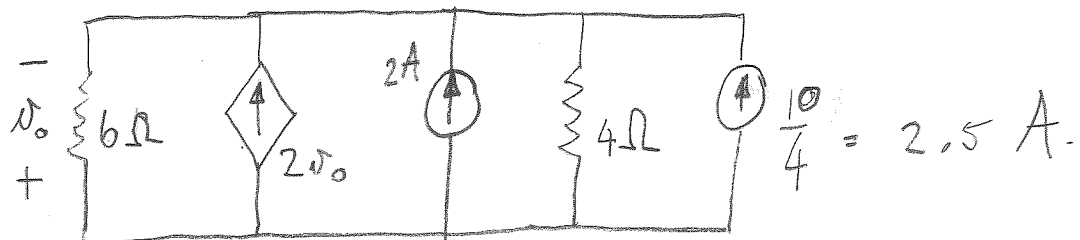


$\Rightarrow$
 $A = 2$
 $B = 4.5$ (sum of independent voltage sources)
 $R_o = 4 \Omega$

Question 7 [2]		Vraag 7 [2]	
07	Determine v_o . Assume that the op-amp is ideal.	07	Bepaal v_o . Aanvaar dat die OV ideaal is.

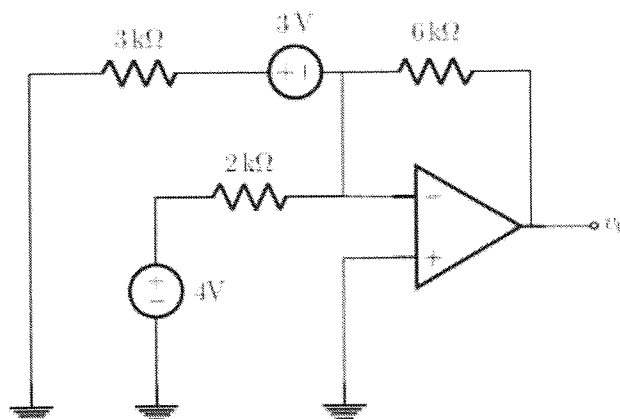


Summing amplifier:
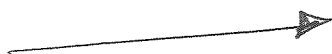
$$\begin{aligned}
 v_o &= - \left(\frac{6000}{3000} (-3) + \frac{6000}{2000} (4) \right) \\
 &= - (-6 + 12) \\
 &= -6 \text{ V}
 \end{aligned}$$



Questions 8-9 [4]		Vraag 8-9 [4]	
Two ideal op-amps are interconnected as indicated. It is known that $v_1 = -40$ V.		Twee ideale OV's word verbind soos aangetoon. Dit is bekend dat $v_1 = -40$ V.	
08	Determine v_2 . [2]	08	Bepaal v_2 . [2]
09	Determine i_1 . [2]	09	Bepaal i_1 . [2]

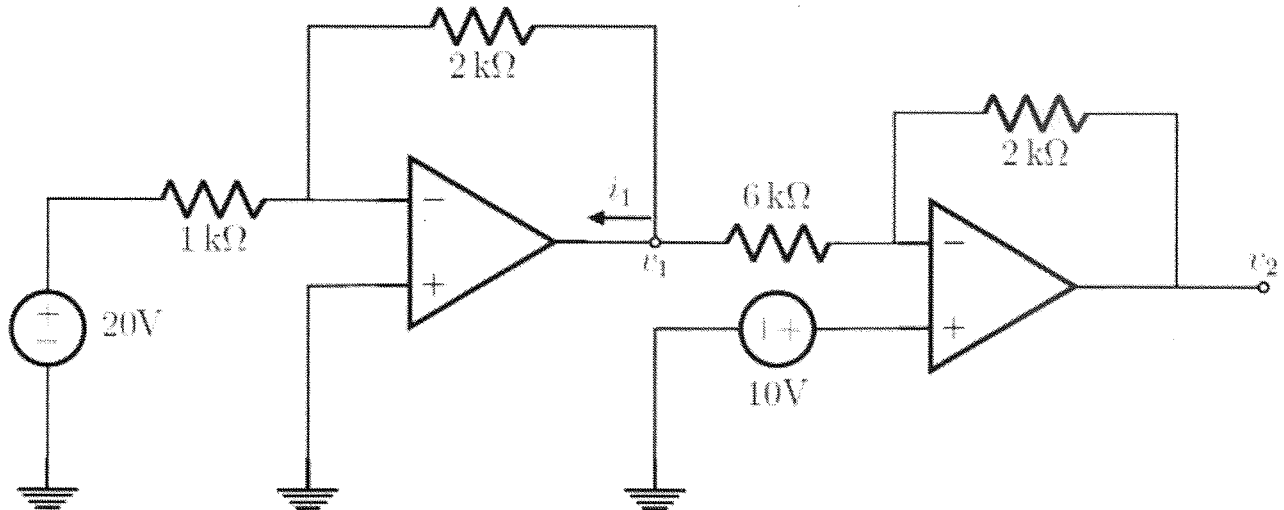

Q8-9 $\left(v_1 = -\frac{2000}{1000} 20 = -40 \text{ V} \right)$

v_2 : $\frac{10 - v_1}{6000} = \frac{v_2 - 10}{2000}$
 $10 - (-40) = 3v_2 - 30 \therefore v_2 = \frac{80}{3} = 26.667 \text{ V}$

i_1 : $i_1 = \frac{0 - v_1}{2000} + \frac{10 - v_1}{6000}$
 $= \frac{0 - (-40)}{2000} + \frac{10 - (-40)}{6000} = 28.333 \text{ mA}$

**PRACTICE ANSWER SHEET /
OEFEN-ANTWOORDBLAD**

This page may NOT be removed from the test. It will not be taken in.

Assessment ID	2	0	1	8	E	B	N	1	2	2	C	2		
---------------	---	---	---	---	---	---	---	---	---	---	---	---	--	--

Answer / Antwoord

Unit / Eenheid

Answers must be rounded to 5 significant numbers
Antwoorde moet afgerond word na 5 beduidende syfers.

01	$V_{Th} = -63$	V
02	$R_{Th} = 6.3$	Ω
03	$R_I = 12$	Ω
04	$R_0 = 4$	Ω
05	$A = 2$	
06	$B = 4.5$	
07	$v_0 = -6$	V
08	$v_2 = 26.667$	V
09	$i_I = 28.333$	mA.