

Class Test 2

Copyright reserved

Electricity and Electronics EBN 122

7 October 2022

Test Information

Maximum marks:	16	Full marks:	15
Duration of test:	35 min	Open/Closed book:	Closed
Total number of pages (this page included)		7	


Lecturers: Prof JP de Villiers, Prof JP Jacobs**INSTRUCTIONS****Do Step 0 in the first 5 minutes of the session. (-5 to 0 min)****Do Step 1 in the first 30 minutes of the test. (0-30 min)****Do Step 2 within the following 5 minutes. (30-35 min)****STEP 0 (-5 min to 0 min):** Complete the front page of the OCR answer sheet.**STEP 1 (0 min to 30 min):** Answer all questions in the question paper. Do your calculations in the spaces provided on the question paper.**STEP 2 (30 min to 35 min):** Transfer your answers to the OCR answer sheet, including units where applicable.

- The Assessment ID is: **2022EBN122C02**
- Read the detailed instructions on the front page of the OCR answer sheet as to how characters should be entered on the sheet.
- Use a mechanical pencil with 0.5 mm HB lead to complete the form.
- Each cell should only have one character, and characters may not touch or cross the cell.
- **Do not use commas!** Please make use of full stops as decimal points.


Section 1**Question 1 [2]**

Use source transformation to obtain Circuit B so that it is equivalent to Circuit A with respect to terminals $a - b$.


Circuit A:

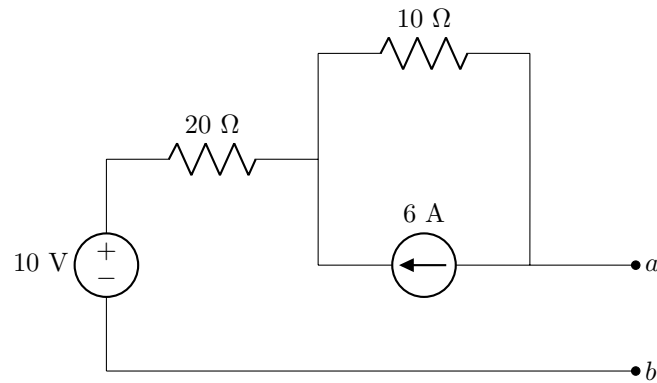

Circuit B:

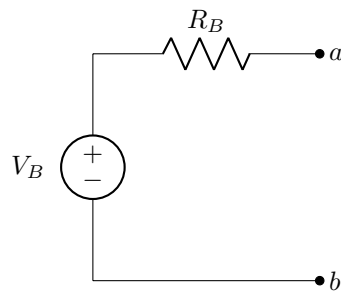



01 Calculate the value of the voltage source V_B . [2]

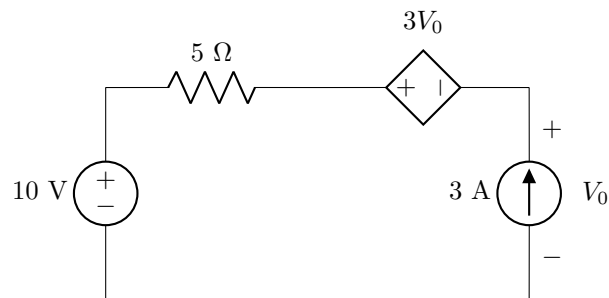Questions 2 to 3 [2]Calculate the independent contributions of the 10 V and 3 A sources to the voltage V_0 .**02** Contribution to V_0 of 10 V source. [1]**03** Contribution to V_0 of 3 A source. [1]


Questions 4 to 5 [4]


For the circuit shown, find the Thevenin equivalent voltage V_{Th} and Thevenin equivalent resistance R_{Th} with reference to terminals $a - b$.

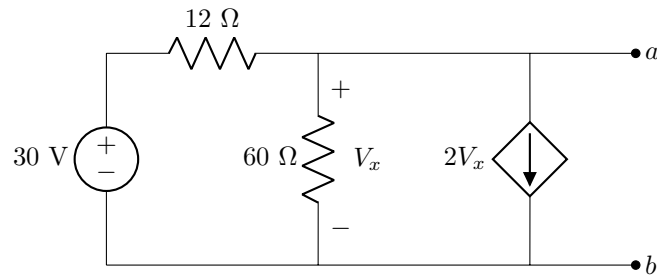**04** V_{Th} [2]**05** R_{Th} [2]**Total Section 1: [8]**

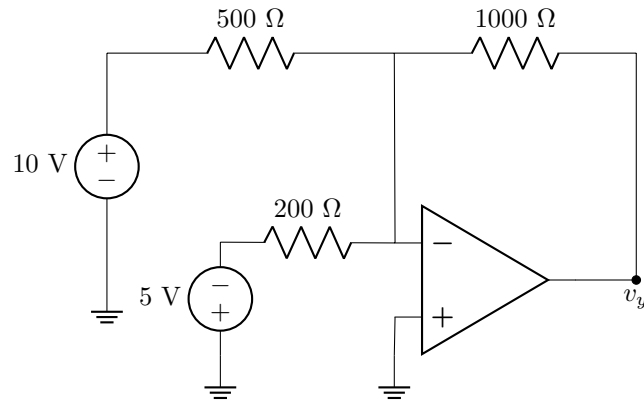Section 2**Question 6 [2]****06** Determine v_y . [2]

Questions 7 to 9 [3]

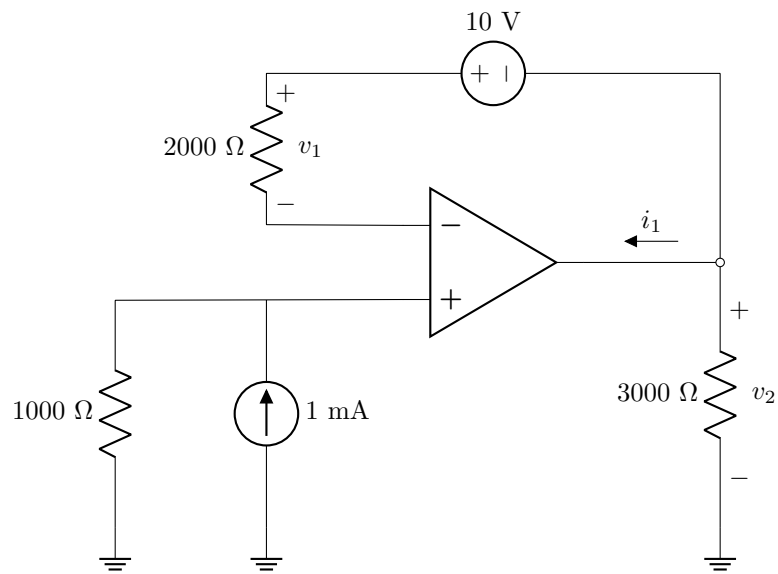**07** Determine v_1 . [1]**08** Determine v_2 . [1]**09** Determine i_1 . [1]

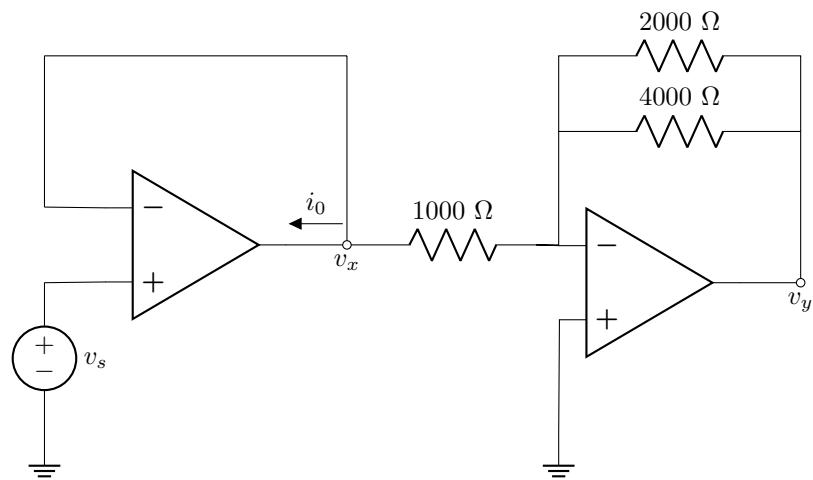Questions 10 to 12 [3]Given: $i_0 = 2 \text{ mA}$.

10	Determine v_x . [1]
11	Determine v_y . [1]
12	Determine v_s . [1]

Total Section 2: [8]**Grand Total : [16]**