

EBN111 KLASTOETS / CLASS TEST 2 (13 APRIL 2012)
ANTWOORDBLAD / ANSWER SHEET

Student se besonderhede/Student's details	
Van en voorletters: <i>Surname and initials:</i>	Studentenommer: <i>Student number:</i>
Graadkursus: <i>Degree Course:</i>	
Tel. nr.: <i>Tel no.:</i>	<i>Memo</i>

Tot:	16 /15
-------------	--------

VRAAG 1 – QUESTION 1 (16)	
1.1	$V_0 = -3V$ ✓✓
1.2	$V_{ab} = 60V$ ✓✓✓
1.3	$V_{TH} = 8,5V$ ✓✓ $R_{TH} = 50\Omega$ ✓✓
1.4	$I_N = -9,1A$ ✓✓
1.5	$V_{TH} = 14V$ ✓✓
1.6	$R_{TH} = 71,43\Omega$ ✓✓✓