

EBN111 KLASTOETS/CLASS TEST 2 (17 APRIL 2014)**ANTWOORDBLAD / ANSWER SHEET**

Van / Surname:	Memo	Studentenommer: Student number:							
Voorletters / Initials:		Taal / Language:	Afr		Eng				

Tot:	15 /15
-------------	--------

1	$I_{X(8A)} = -4A.$ ✓✓		
2	$V_0 = 8V$ ✓✓		
3	$V_{TH} = 2V$ ✓✓		
4	$R_N = 16\Omega$ ✓✓		
5	a) $V_0 = -2V$ ✓	b) $V_0 = 3V$ ✓	c) $V_0 = 1V$ ✓
6	$V_1 = 18V$ ✓	$V_0 = 9V$ ✓	
7	$I_2 = 1mA$ ✓	$V_3 = -1V$ ✓	