

Departement Elektriese, Elektroniese en
Rekenaar-Ingenieurswese

Department of Electrical, Electronic and
Computer Engineering

Eksamen

Kopiereg voorbehou

Examination

Copyright reserved

Module EBN122
Elektrisiteit en Elektronika
November 2016

Module EBN122
Electricity and Electronics
November 2016



UNIVERSITEIT VAN PRETORIA
UNIVERSITY OF PRETORIA
YUNIBESITHI YA PRETORIA

Eksamensinligting: Exam information:

Maksimum punte: <i>Maximum marks:</i>	90	Volpunte: <i>Full marks:</i>	94
Duur van vraestel: <i>Duration of paper:</i>	180 minute <i>180 minutes</i>	Oopboek / toeboek: <i>Open / closed book:</i>	Toe <i>Closed</i>
Totale aantal bladsye (hierdie blad ingesluit): <i>Total number of pages (including this page):</i>		27 (Antwoordblad uigesluit / <i>Answer sheet excluded</i>)	

BELANGRIK- IMPORTANT

- The examination regulations of the University of Pretoria apply.*
Die eksamenregulasies van die Universiteit van Pretoria geld.
- All questions must be answered on the ANSWER SHEET.*
Alle vrae moet op die ANTWOORDBLAD beantwoord word.
- The English text of this question paper will be given precedence in the interpretation of the content.*
Die Engelse teks van hierdie vraestel sal voorkeur geniet met betrekking tot die interpretasie van die inhoud.
- Students may do their own rough calculations on the question paper – the question paper will not be taken in.*
Studente mag hul eie rowwe berekeninge op die vraestel doen – die vraestel word nie ingeneem nie.
- Answers must include units!*
Antwoorde moet eenhede insluit!
- Only non-programmable calculators may be used.*
Slegs nie-programmeerbare sakrekenaars mag gebruik word.
- Polar form:** $A\angle\theta$; **Rectangular form:** $a + jb$
Polêre vorm: $A\angle\theta$; **Reghoekige vorm:** $a + jb$
- Final answers must be written as real numbers, and not as fractions.**
Finale antwoorde moet as reële getalle geskryf word, en nie as breuke nie.

Interne Eksaminator(e): <i>Internal examiner(s):</i>	D. le Roux, J. Joubert, R. Dos Santos, D. Ramotsoela
Eksterne eksaminator: <i>External examiner:</i>	W. Odendaal

QUESTION/VRAAG 1 [18]

Question 1.1 [6]

The voltage and current at the terminals of the circuit below are zero for $t < 0$ and $t > 40$ s. In the interval between 0 and 40s the expressions are

$$v(t) = t(1 - 0.025t) \text{ V}$$

$$i(t) = 4 - 0.2t \text{ A}$$

- (a) Calculate the power associated with the element at $t = 35$ s.
- (b) Calculate the amount of charge entering the element during the interval between 0 and 20s.
- (c) Calculate the total energy delivered to the circuit during the interval between 0 and 40s.


Vraag 1.1 [6]


Die spanning en stroom by die terminale van die stroombaan hieronder is nul vir $t < 0$ en $t > 40$ s. In die interval tussen 0 en 40s is die uitdrukkings

$$v(t) = t(1 - 0.025t) \text{ V}$$

$$i(t) = 4 - 0.2t \text{ A}$$

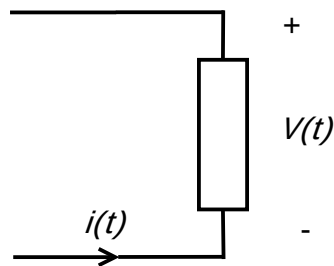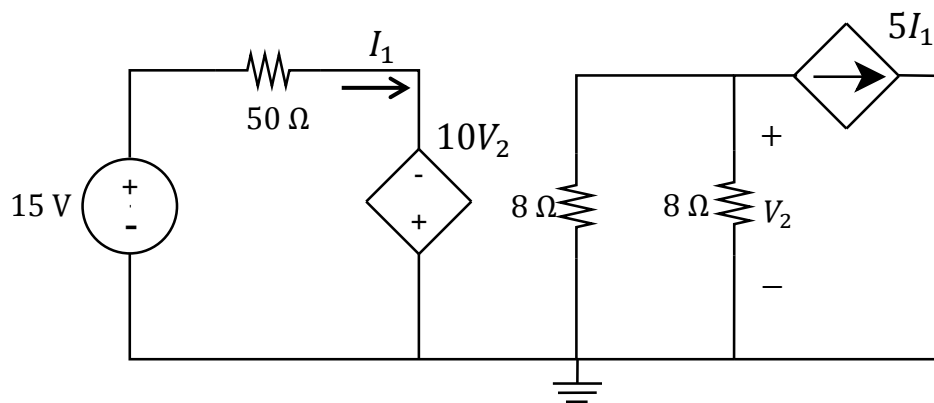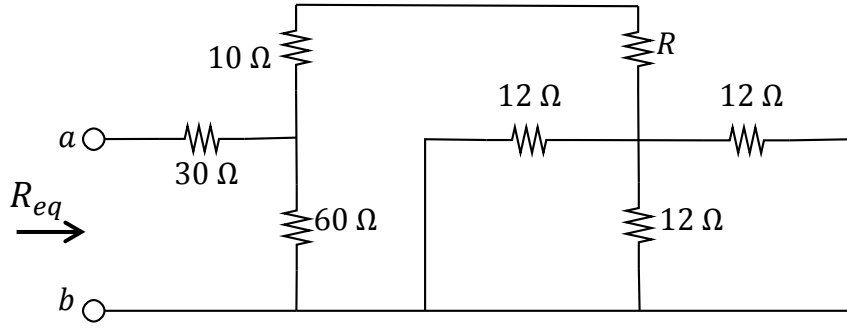
- (a) Bereken die drywing ge-assosieer met die element by $t = 35$ s.
- (b) Bereken die aantal lading wat die element binnevloei in die tydperk tussen 0 en 20s.
- (c) Bereken die totale energie gelewer aan die stroombaan in die tydperk tussen 0 en 40s.

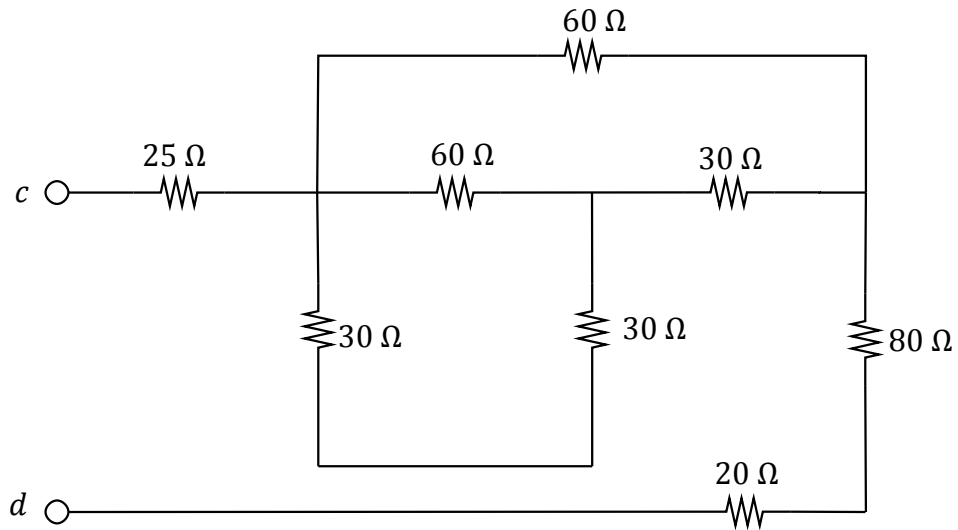


Question 1.2 [4]Determine I_1 and V_2 .**Vraag 1.2 [4]**Bepaal I_1 en V_2 .

Determine R if $R_{eq} = 50 \, \Omega$.

Bereken R indien $R_{eq} = 50 \, \Omega$.



Question 1.4 [2]Calculate the equivalent resistance w.r.t terminals c - d .**Vraag 1.4 [2]**Bereken die ekwivalente weerstand m.b.t. terminale c - d .

Question 1.5 [4]


For the circuit below, calculate

- a) I_S if $I_2 = 137.5$ mA
- b) V_1 if $I_1 = 225$ mA

Vraag 1.5 [4]

Vir onderstaande kringbaan, bereken

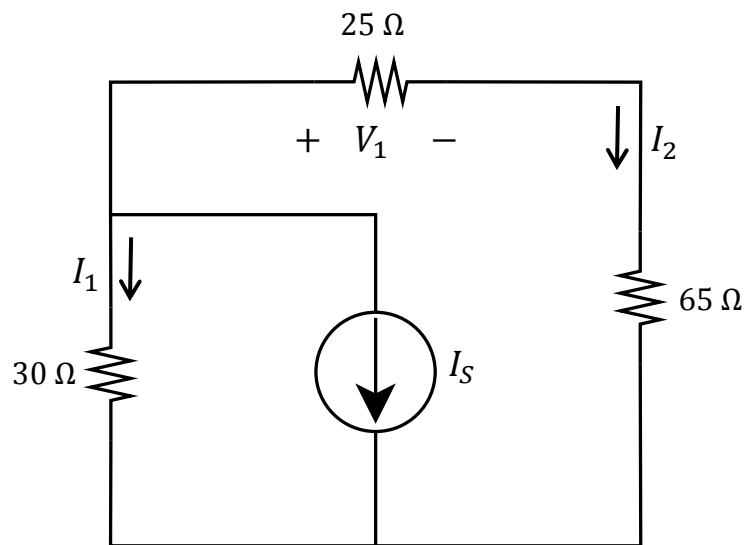- a) I_S indien $I_2 = 137.5$ mA
- b) V_1 indien $I_1 = 225$ mA



QUESTION/VRAAG 2 [32]

Question 2.1 [4]

Use mesh analysis to find the missing coefficients for the following equations:

$$ai_1 + bi_2 + ci_3 = -18$$

$$di_1 - i_2 = 0$$

$$-10i_1 + 14i_3 = 18$$


Vraag 2.1 [4]

Gebruik lus-analise om die onbekende koëffisiente te bepaal in die volgende vergelykings:

$$ai_1 + bi_2 + ci_3 = -18$$

$$di_1 - i_2 = 0$$

$$-10i_1 + 14i_3 = 18$$

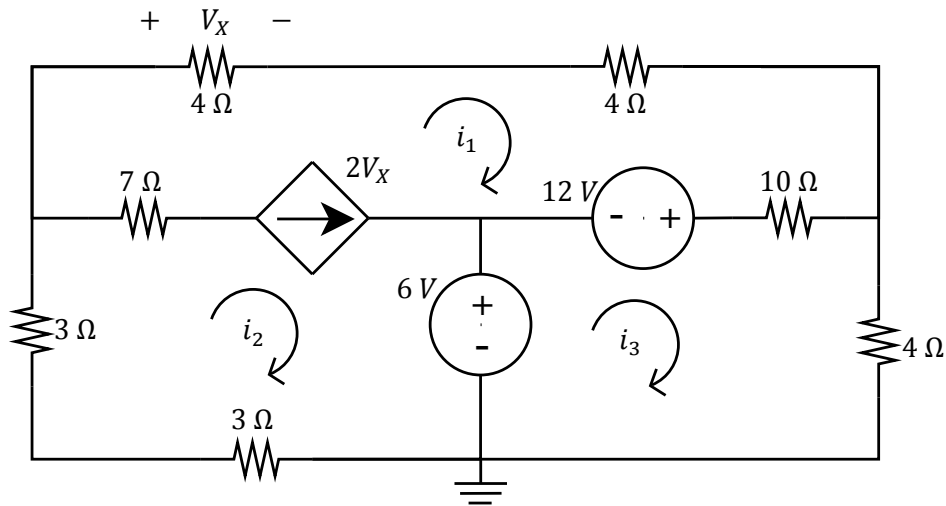

Question 2.2 [4]


Use nodal analysis to set up two equations of the following form:


$$\begin{aligned} eV_1 + fV_2 &= 6 \\ gV_1 + hV_2 &= 80 \end{aligned}$$

Vraag 2.2 [4]

Gebruik node-analise om twee vergelykings van die volgende vorm op te stel:

$$\begin{aligned} eV_1 + fV_2 &= 6 \\ gV_1 + hV_2 &= 80 \end{aligned}$$

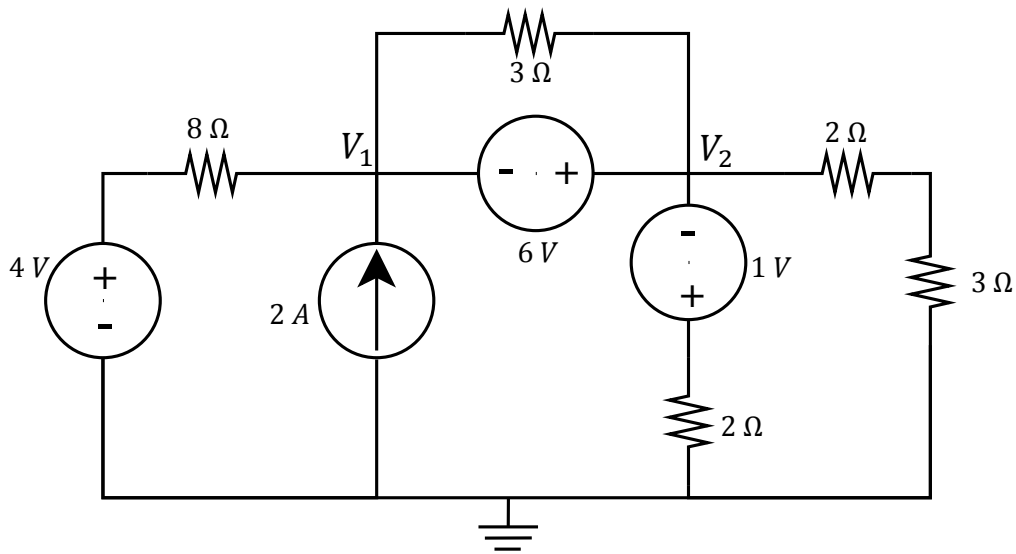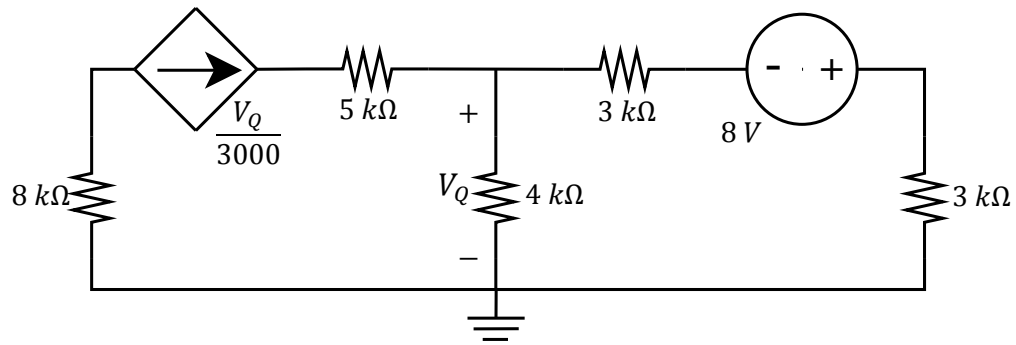

Question 2.3 [2]Determine V_Q . Use nodal or mesh analysis.**Vraag 2.3 [2]**Bepaal V_Q . Gebruik node- of lusanalyse.

Question 2.4 [4]

Given: $\beta = 99$ and $V_{BE} = 0.7$ V.

a) If $V_S = 3.4$ V, determine I_B .


b) If $I_B = 20$ μ A, determine V_{CE} .

Vraag 2.4 [4]

Gegee: $\beta = 99$ en $V_{BE} = 0.7$ V.

a) Indien $V_S = 3.4$ V, bepaal I_B .

b) Indien $I_B = 20$ μ A, bepaal V_{CE} .

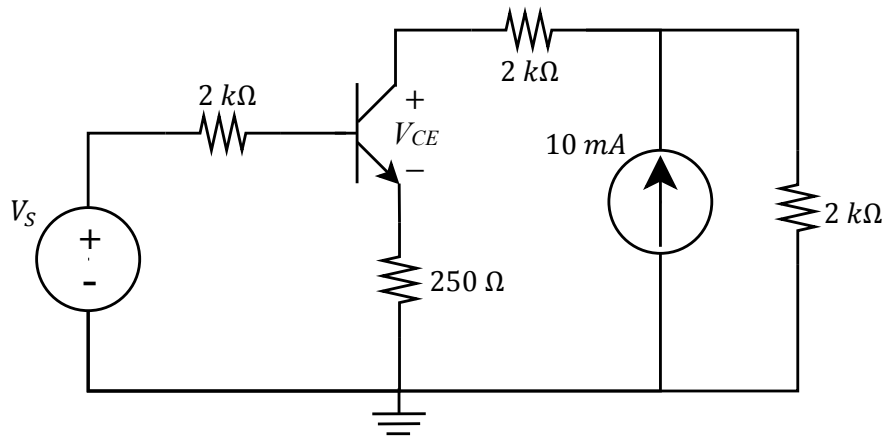


Question 2.5 [4]

Use superposition to determine the unique contribution of
a) the 1 A current source to V_0 , and
b) the 30 V voltage source to V_0 .

Vraag 2.5 [4]

Gebruik superposisie om die unieke bydra van
a) die 1 A stroombron tot V_0 ,
b) die 30 V spanningsbrong tot V_0 ,
te bereken.

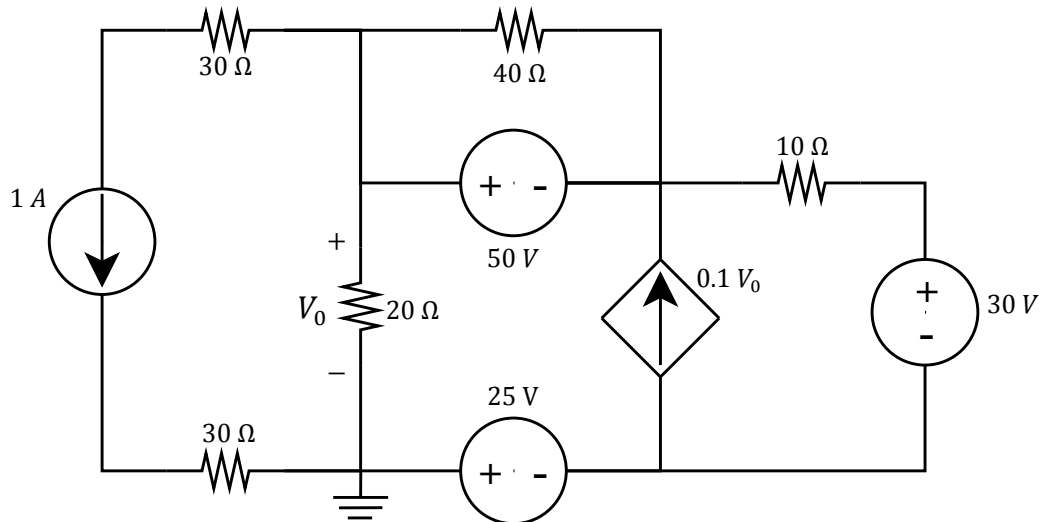

Question 2.6 [4]


The circuit on the left was obtained through source transformation of the circuit on the right.

- Calculate the value of R_T .
- Calculate the value of V_X .

Vraag 2.6 [4]

Die linkerkantse kringbaan is verkry deur brontransformasie van die regterkantse kringbaan.

- Bereken die waarde van R_T .
- Bereken die waarde van V_X .

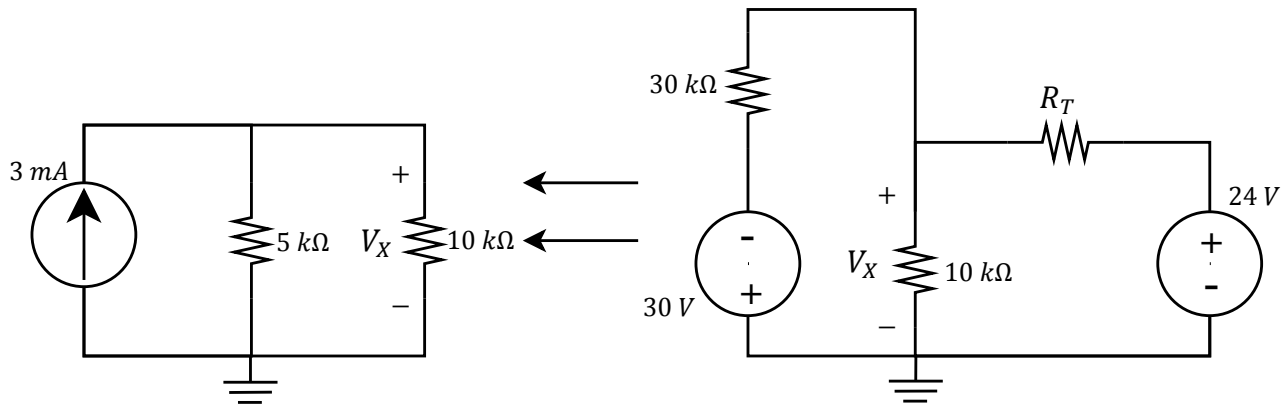


Question 2.7 [4]

Calculate the Thevenin equivalent with respect to terminals a - b .

Vraag 2.7 [4]

Bereken die Thevenin ekwivalent met verwysing tot terminale a en b .

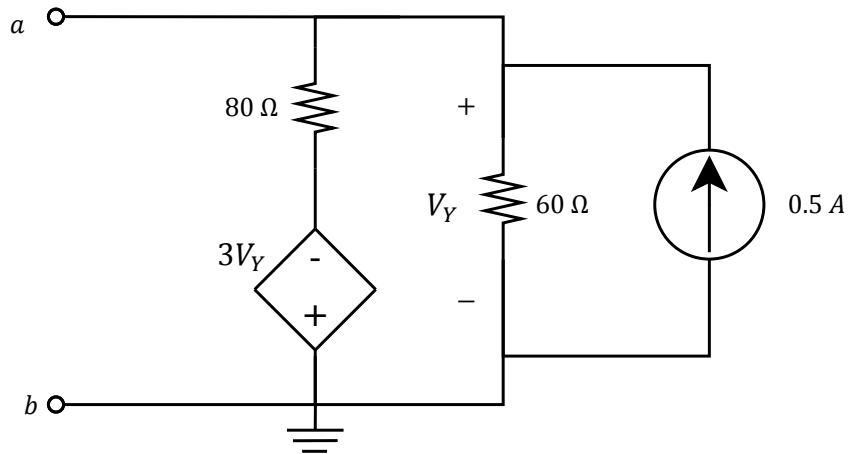


Question 2.8 [4]

Determine the Norton equivalent with respect to terminals a and b .

Vraag 2.8 [4]

Bepaal die Norton ekwivalent met betrekking tot terminale a en b .

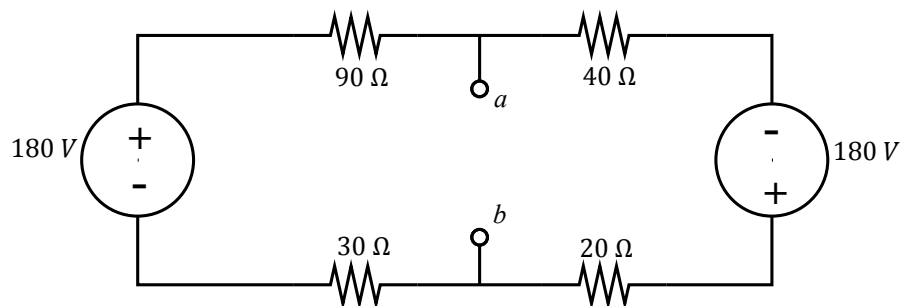

Question 2.9 [2]

A circuit delivers maximum power if the load connected to the circuit is $4\ \Omega$. If the load is changed to $2\ \Omega$, the power delivered to the load is 8 W.

Calculate the Thevenin equivalent voltage of the circuit.

Vraag 2.9 [2]

'n Kringbaan lewer maksimum drywing indien daar 'n las van $4\ \Omega$ aan die kringbaan gekoppel is. Indien die las na $2\ \Omega$ verander word, verbruik die las 8 W.

Bereken die Thevenin ekwivalente spanning van die kringbaan.


VRAAG/QUESTION 3 [20]


Question 3.1 [2]

Calculate i_o .

Vraag 3.1 [2]

Bereken i_o .

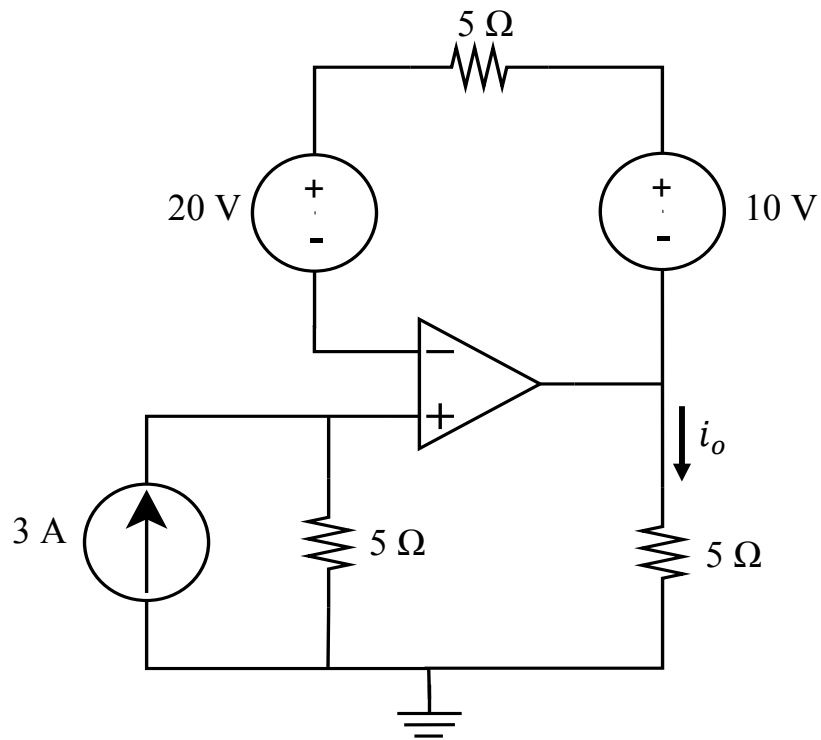

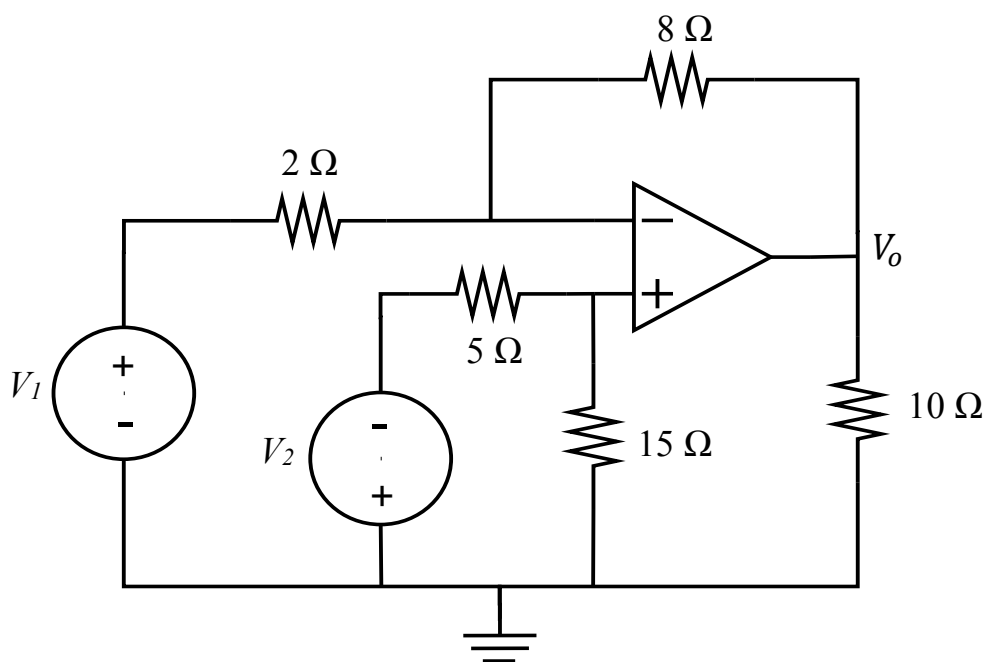Question 3.2 [4]Calculate V_o ,a) if $V_1 = 4\text{V}$ and $V_2 = 0\text{V}$ b) if $V_1 = 6\text{V}$ and $V_2 = 4\text{V}$ **Vraag 3.2 [4]**Bereken V_o ,a) as $V_1 = 4\text{V}$ en $V_2 = 0\text{V}$ b) as $V_1 = 6\text{V}$ en $V_2 = 4\text{V}$ 

Question 3.3 [6]


If $V_x = 6\text{ V}$ and $V_y = -10\text{ V}$, then determine:

- a) V_m
- b) V_n
- c) V_o

Vraag 3.3 [6]

As $V_x = 6\text{ V}$ en $V_y = -10\text{ V}$, dan bepaal:

- a) V_m
- b) V_n
- c) V_o

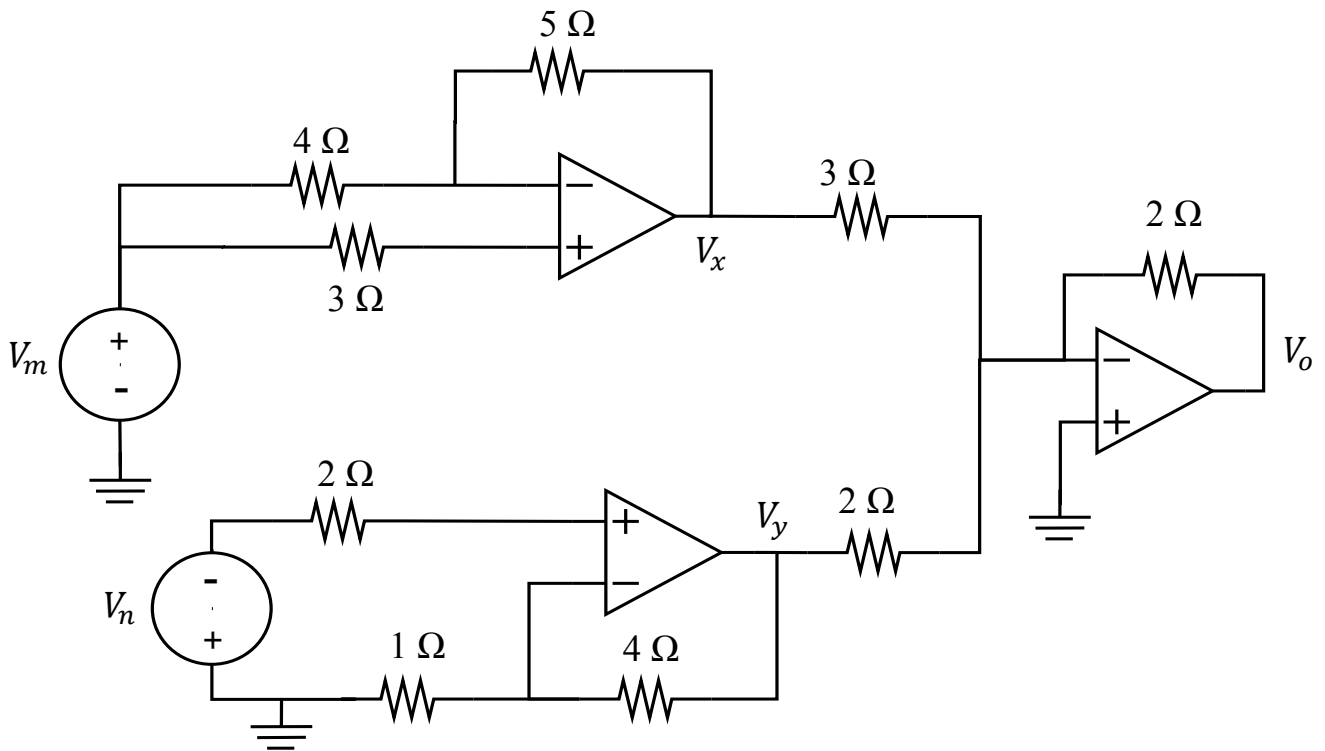

Question 3.4 [2]

Calculate $v_C(t)$ at $t = 2$, if $v_C(0) = 0\text{V}$ and,

$$i_1(t) = 2e^{-4t} \text{ A}$$


$$i_2(t) = 8t \text{ A}$$

Vraag 3.4 [2]

Bepaal $v_C(t)$ vir $t = 2$, as $v_C(0) = 0\text{V}$ en,

$$i_1(t) = 2e^{-4t} \text{ A}$$

$$i_2(t) = 8t \text{ A}$$

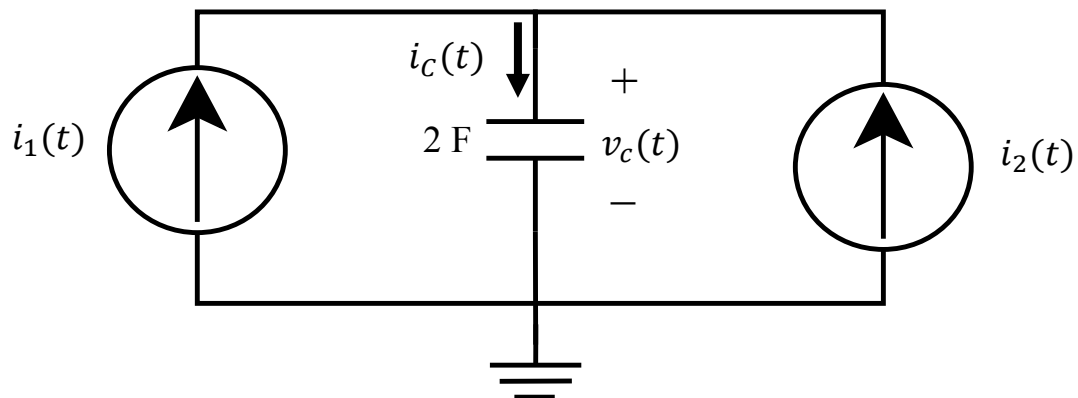


Question 3.5 [2]

Calculate C_{eq} .

Vraag 3.5 [2]

Bepaal C_{eq} .

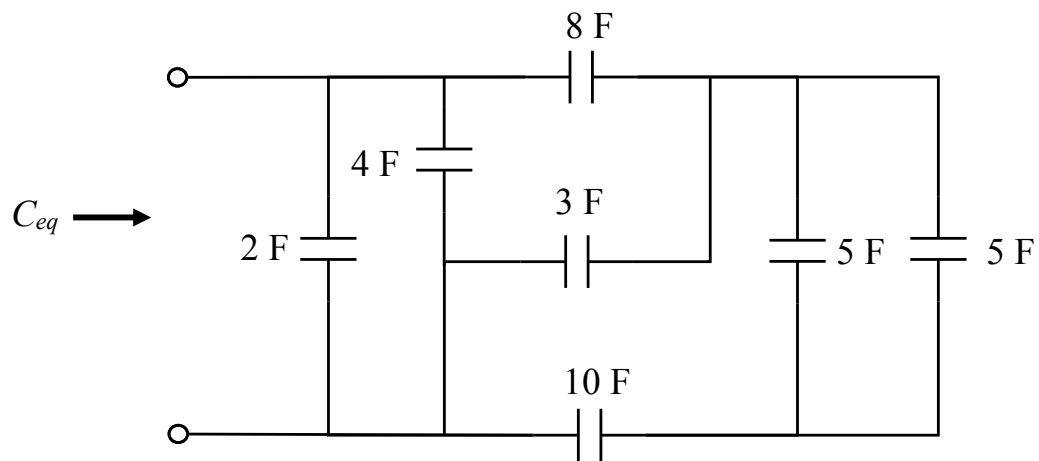


Question 3.6 [4]

Calculate the energy stored by the capacitor (w_C) and inductor (w_L). Assume direct current conditions.

Vraag 3.6 [4]

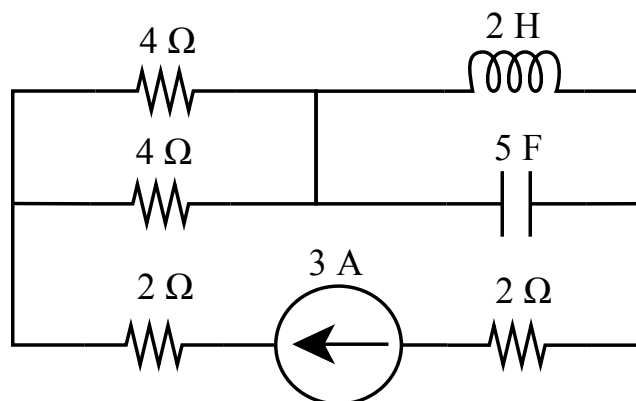Bepaal die energie gestor in die kapasitor (w_C) en die inductor (w_L). Aanvaar gelykstroom toestande.



VRAAG/QUESTION 4 [24]

Question 4.1 [6]

- a) Write $v(t)$ as a single phasor in **rectangular form**:
 $v(t) = 15\cos(\omega t + 45^\circ) - 10\sin(\omega t + 45^\circ)$ V
- b) What is the voltage across a $2\ \mu\text{F}$ capacitor when the current through it is $i_C(t) = 4\sin(10^6 t + 25^\circ)$ A. Assume the current is flowing into the + of the reference voltage defined across the capacitor. Assume $v_C(0) = 0$ V.
- c) A current source of $i(t) = 10\sin(377t + 30^\circ)$ A is applied to a single component. The resulting voltage across the element is
 $v(t) = -65\cos(377t + 120^\circ)$ V.
Determine the value of the component (you have to decide if it is a resistor, inductor or capacitor).

Vraag 4.1 [6]

- a) Skryf $v(t)$ as 'n enkele fasor in **reghoekige vorm**:
 $v(t) = 15\cos(\omega t + 45^\circ) - 10\sin(\omega t + 45^\circ)$ V
- b) Bepaal die spanning oor 'n $2\ \mu\text{F}$ kapasitor as die stroom deur die kapasitor $i_C(t) = 4\sin(10^6 t + 25^\circ)$ A is. Aanvaar dat die stroom invloei by die + van die verwysings-spanning wat gedefinieer is oor die kapasitor. Aanvaar $v_C(0) = 0$ V.
- c) 'n Stroombron $i(t) = 10\sin(377t + 30^\circ)$ A word aangewend oor 'n enkele komponent. Die resultante spanning oor die element is
 $v(t) = -65\cos(377t + 120^\circ)$ V.
Bereken die waarde van die komponent (besluit eers of dit 'n weerstand, induktor of kapasitor is).

Question 4.2 [4]

a) Simplify and write the answer in **polar form**:

$$\bar{I}_1 = \frac{(3 + j4)^* + (8\angle -90^\circ)^*}{2e^{j45^\circ}}$$

b) Determine $\bar{V}_1$ in **polar form**:

$$\begin{bmatrix} 2 + j4 & -j2 \\ -j2 & 2 \end{bmatrix} \begin{bmatrix} \bar{V}_1 \\ \bar{V}_2 \end{bmatrix} = \begin{bmatrix} 2\angle 180^\circ \\ 2\angle 0^\circ \end{bmatrix}$$

Vraag 4.2 [4]

a) Vereenvoudig en skryf die antwoord in **polêre vorm**:

$$\bar{I}_1 = \frac{(3 + j4)^* + (8\angle -90^\circ)^*}{2e^{j45^\circ}}$$

b) Bepaal $\bar{V}_1$ in **polêre vorm**:


$$\begin{bmatrix} 2 + j4 & -j2 \\ -j2 & 2 \end{bmatrix} \begin{bmatrix} \bar{V}_1 \\ \bar{V}_2 \end{bmatrix} = \begin{bmatrix} 2\angle 180^\circ \\ 2\angle 0^\circ \end{bmatrix}$$

Question 4.3 [2]

Determine the total impedance $\bar{Z}_{ab}$ between terminals a and b . Write the answer in **rectangular form**.

Vraag 4.3 [2]

Bepaal die totale impedansie $\bar{Z}_{ab}$ tussen terminale a en b . Skryf die antwoord in **reghoekige vorm**.

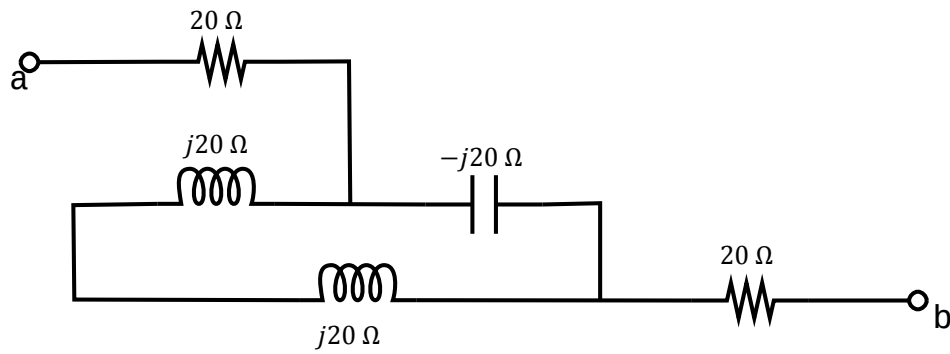

Question 4.4 [4]

Use nodal analysis to set up two equations of the following form:

$$(a_1 + jb_1)\bar{V}_1 + (a_2 + jb_2)\bar{V}_2 = 20\angle 0^\circ$$


$$(a_3 + jb_3)\bar{V}_1 + (a_4 + jb_4)\bar{V}_2 = 50\angle -90^\circ$$

Vraag 4.4 [4]

Gebruik node-analise om twee vergelykings van die volgende vorm op te stel:

$$(a_1 + jb_1)\bar{V}_1 + (a_2 + jb_2)\bar{V}_2 = 20\angle 0^\circ$$

$$(a_3 + jb_3)\bar{V}_1 + (a_4 + jb_4)\bar{V}_2 = 50\angle -90^\circ$$

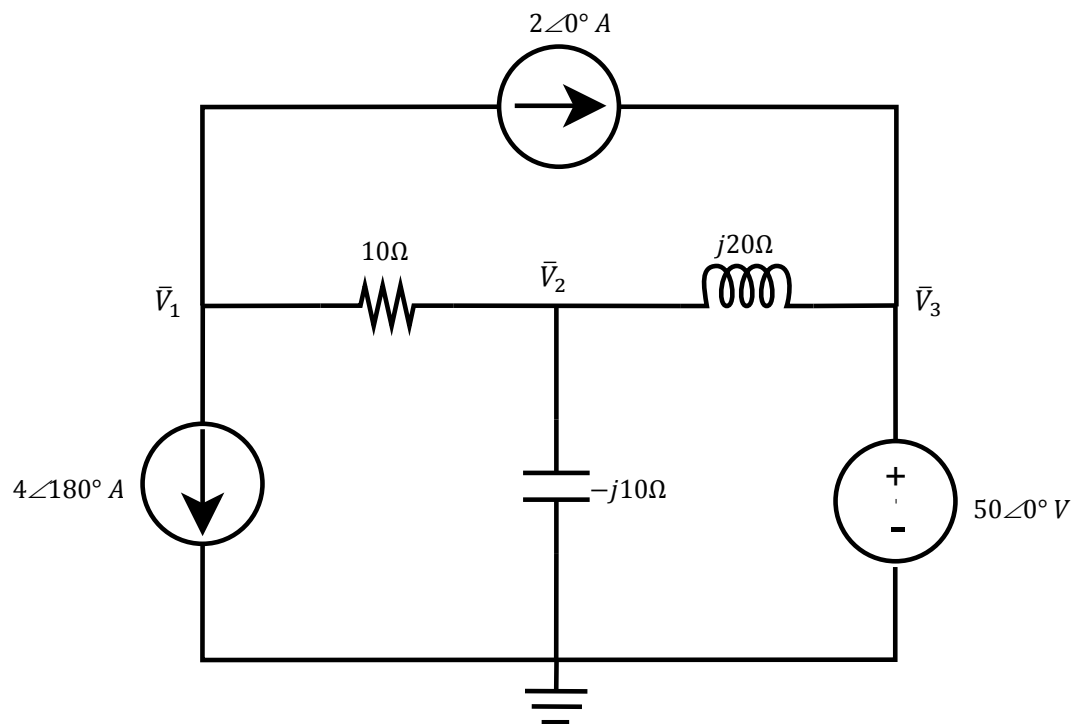


Question 4.5 [4]

Find the Thevenin equivalent wrt terminals a-b. Write the answer as phasors in **polar form**.

Vraag 4.5 [4]

Bepaal die Thevenin-ekwivalent tov terminale a-b. Skryf die antwoorde as fasors in **polêre vorm**.

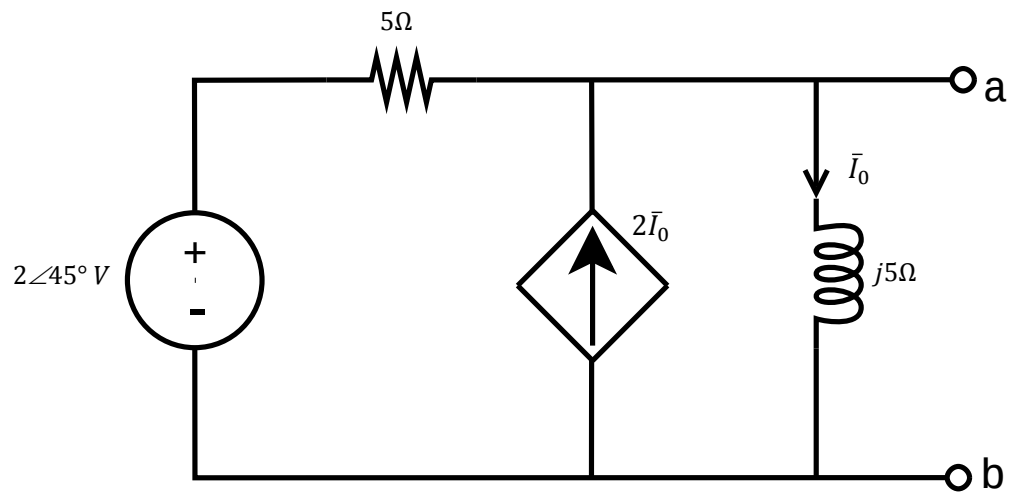

Question 4.6 [4]

Find the Norton equivalent wrt terminals a-b. Write the answers as phasors in **polar form**.

Vraag 4.6 [4]

Bepaal die Norton-ekwivalent tov terminale a-b. Skryf die antwoorde as fasors in **polêre vorm**.

