

**Exam**

Copyright reserved

**Electricity and Electronics EBN 111**

13 June 2022

**Test Information**

|                                            |         |                   |        |
|--------------------------------------------|---------|-------------------|--------|
| Maximum marks:                             | 93      | Full marks:       | 90     |
| Duration of test:                          | 200 min | Open/Closed book: | Closed |
| Total number of pages (this page included) |         | 32                |        |

**Lecturers:** Prof X. Ye, Prof J.D. le Roux, Mr V. Dube**Assistant Lecturers:** N. Matic, K. Mphaga, J. Thiselton, D. Wepener, L. Zheve**ECSA GA assessment**

The following ECSA graduate attributes are assessed at entry level in this question paper: GA1 and GA2.

**Important**

1. The examination regulations of the University of Pretoria apply.
2. The departmental rules relevant to electronically graded assessments apply.
3. Write your answers on the OCR forms provided. The question number **01** in this question paper corresponds to Row 01 of the OCR form, etc.
4. Read the instructions on the OCR form carefully.
5. Answers must include units where applicable.
6. Final answers must be written as real numbers and not as fractions. Use at least 4 significant figures to write numbers, including complex numbers.

**INSTRUCTIONS****Do STEP 0 in the first 5 minutes of the session. (-5 to 0 min)****Do STEP 1 in the next 90 minutes of the test. (0-180 min)****Do STEP 2 within the next 20 minutes. (180-200 min)**

**STEP 0 (-5 min to 0 min):** Complete the front page of the OCR form, and also fill in your name and student number on additional pages of the OCR forms.

**STEP 1 (0 min to 180 min):** Do your own calculations on the question paper. Write down the answers on the PRACTICE ANSWER SHEET. Be sure to include the units where applicable.

**STEP 2 (180 min to 200 min):** Carefully copy the answers from the PRACTICE ANSWER SHEET to the OCR form.

- The Assessment ID is: **2022EBN111E01**
- Use a mechanical pencil with 0.5 mm HB lead to complete the form.
- Each cell should only have one character, and characters may not touch or cross the cell.
- **Do not use commas!** Make use of full stops as decimal points.

|                  |
|------------------|
| <b>Section 1</b> |
|------------------|

|                       |
|-----------------------|
| <b>Question 1 [2]</b> |
|-----------------------|

An electric motor can deliver 50 kJ in 2 minutes. Find the annual cost (in Rand) of running the motor if it is used for 5 hours a day, 300 days a year. The cost of electricity is R1/kWh.

|           |                           |
|-----------|---------------------------|
| <b>01</b> | Annual cost (in Rand) [2] |
|-----------|---------------------------|


$$P = \frac{\Delta W}{\Delta T} = \frac{50 \text{ kJ}}{2 \text{ min} \times 60 \text{ s/min}} = 0.4167 \text{ kW}$$

$$\begin{aligned} \text{Cost} &= 0.4167 \text{ kW} \times 5 \text{ h} \times 300 \times \text{R1/kWh} \\ &= \underline{\text{R } 625} \end{aligned}$$

|                       |
|-----------------------|
| <b>Question 2 [2]</b> |
|-----------------------|

A 9 V battery is used to power a remote controlled car. The power delivery from the battery falls linearly from 5 W to 2 W in 100 minutes. Determine the total energy  $W_T$  used by the car.

|           |           |
|-----------|-----------|
| <b>02</b> | $W_T$ [2] |
|-----------|-----------|

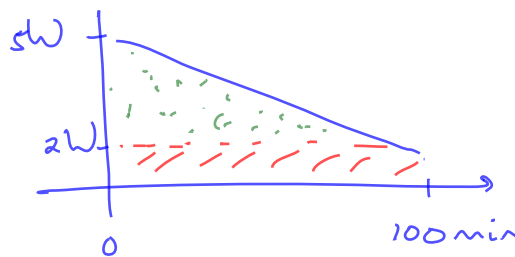


$$\begin{aligned} W_T &= \int p dt = 2 \times 100 \text{ min} \times 60 \text{ s/min} \\ &\quad + \frac{1}{2} (5 - 2) \times 100 \text{ min} \times 60 \text{ s/min} \\ &= \underline{21 \text{ kJ}} \end{aligned}$$
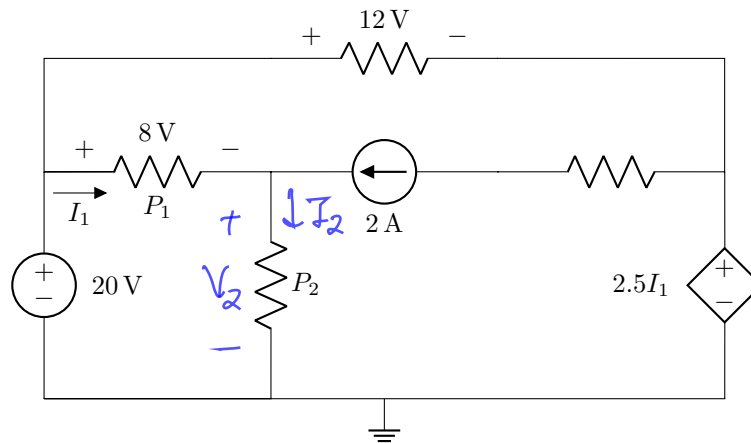
## Questions 3 to 4 [4]

For the circuit shown below, determine  $P_1$  and  $P_2$ .

(There is sufficient information in the circuit to solve the problem.)



03  $P_1$  [2]

04  $P_2$  [2]

③ \* KVL:  $-20 + 12 + 2.5 I_1 = 0$

$$I_1 = 3.2 \text{ A}$$

\*  $P_1 = 3.2 \times 8 = \underline{25.6 \text{ W}}$


④ \* KCL:  $I_2 = 3.2 + 2 = 5.2 \text{ A}$

\* KVL:  $-20 + 8 + V_2 = 0$   
 $V_2 = 12 \text{ V}$


\*  $P_2 = 5.2 \times 12$   
 $= \underline{62.4 \text{ W}}$

## Questions 5 to 6 [4]

For the circuit below:

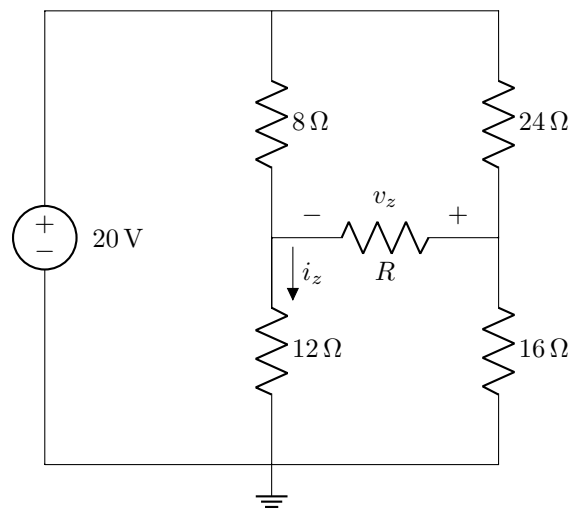**05** If  $R = 0\Omega$ , determine  $i_z$ . [2]**06** If  $R \rightarrow \infty$ , determine  $v_z$ . [2]

65

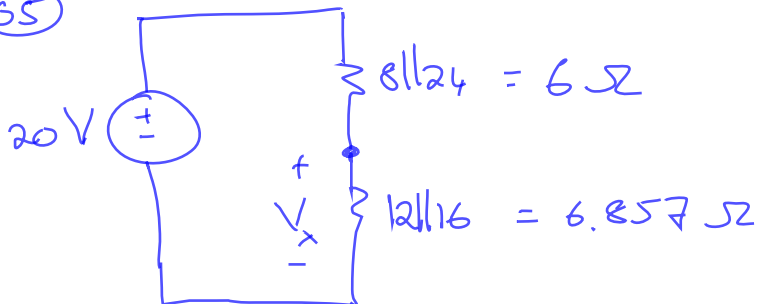


$$V_x = \frac{6.857 \times 20}{6 + 6.857} = 10.667 \text{ V}$$

$$i_z = \frac{10.667}{6.857} = 1.56 \text{ A}$$

0.8889A


06

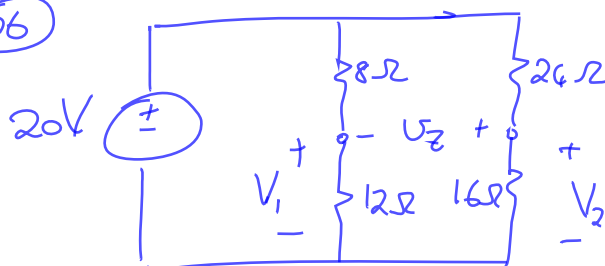

$$V_1 = \frac{20 \times 12}{12 + 8} = 12 \text{ V}$$


$$V_2 = \frac{20 \times 16}{16 + 24} = 8 \text{ V}$$

$$V_z = V_2 - V_1 = -4 \text{ V}$$


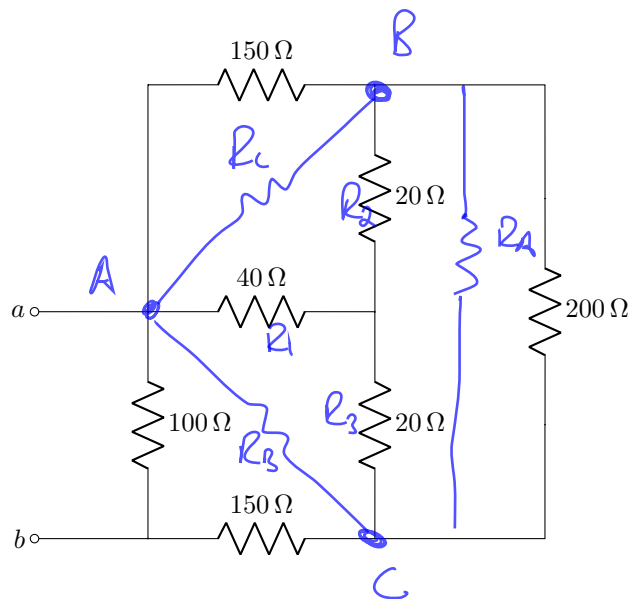
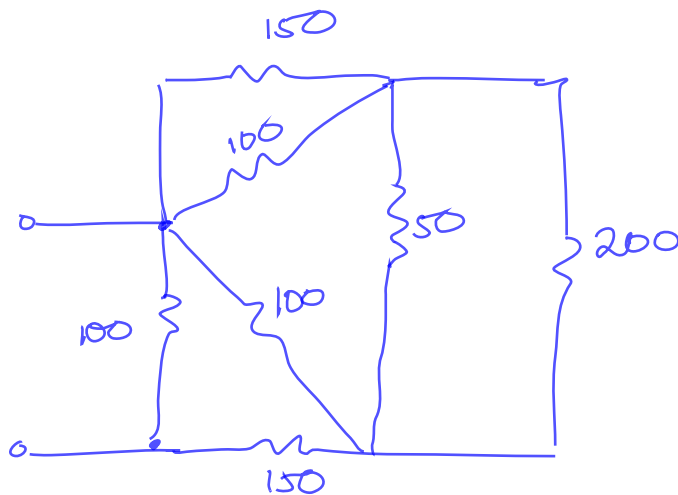
**Question 7 [2]**Determine the equivalent resistance  $R_{ab}$ .07  $R_{ab}$  [2]

$$\star R_A = \frac{20 \times 20 + 40 \times 20 + 40 \times 20}{40} = \frac{2000}{40} = 50 \Omega$$

$$\star R_B = R_C = \frac{2000}{20} = 100 \Omega$$



$$\begin{aligned} R_{ab} &= 100 \parallel (150 + 100 \parallel (100 \parallel 150 + 200 \parallel 50)) \\ &= 100 \parallel (150 + 100 \parallel (60 + 40)) \\ &= 100 \parallel (150 + 50) = 100 \parallel 200 = 66.667 \Omega \end{aligned}$$

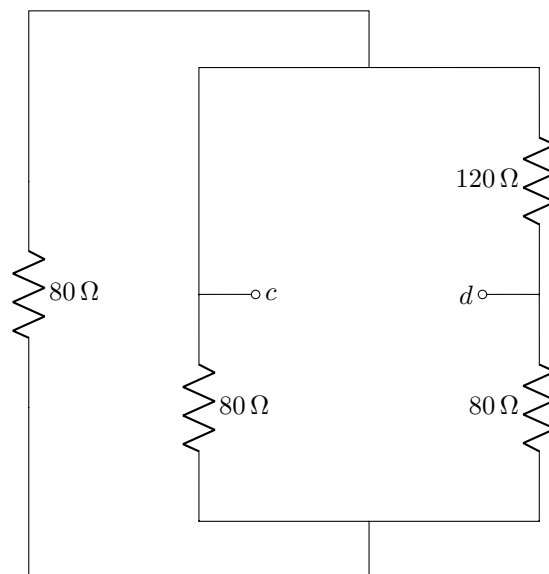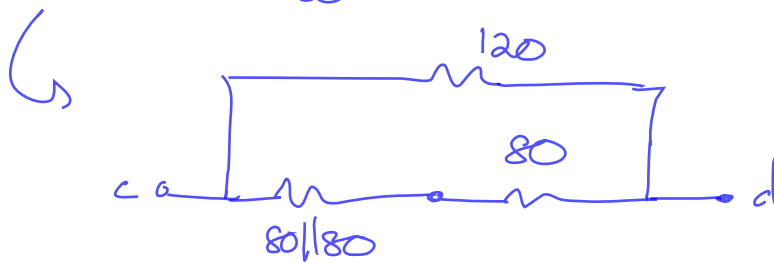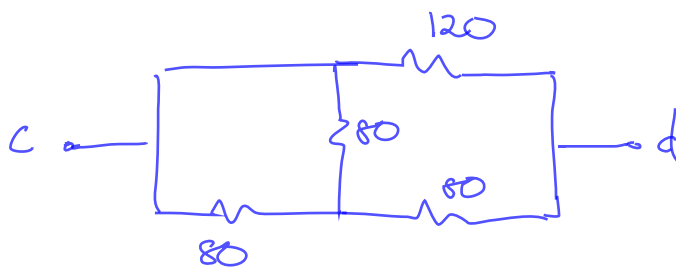**Question 8 [2]**Determine the equivalent resistance  $R_{cd}$ .**08**  $R_{cd}$  [2]

$$R_{cd} = 120 \parallel (40 + 80)$$

$$= \underline{60 \Omega}$$


**Questions 9 to 12 [4]**

Use nodal analysis to set up two equations in the form:

$$av_1 + bv_2 = 51,$$

$$cv_1 + dv_2 = -205.$$

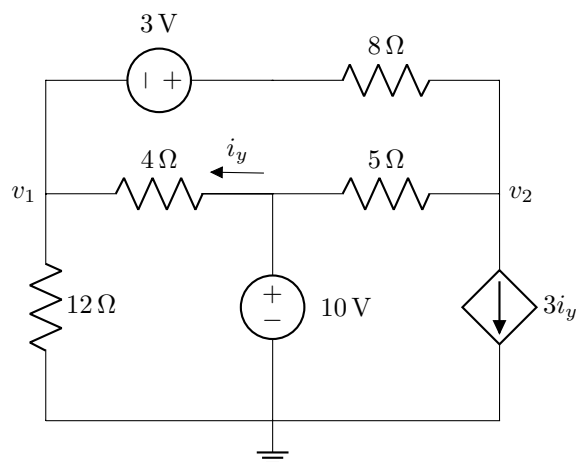Calculate the unknown coefficients  $a$ ,  $b$ ,  $c$ , and  $d$ .



|    |         |
|----|---------|
| 09 | $a$ [1] |
| 10 | $b$ [1] |
| 11 | $c$ [1] |
| 12 | $d$ [1] |

$$\star \quad \frac{v_1}{12} + \frac{v_1 - 10}{4} + \frac{v_1 + 3 - v_2}{8} = 0$$

$$(\times 24) \quad 2v_1 + 6v_1 - 60 + 3v_1 + 9 - 3v_2 = 0$$

$$\underline{11v_1 - 3v_2 = 51} \rightarrow$$

$$\star \quad 3i_y + \frac{v_2 - 10}{5} + \frac{v_2 - 3 - v_1}{8} = 0$$

$$(\times 40) \quad 120i_y + 8v_2 - 80 + 5v_2 - 15 - 5v_1 = 0$$

$$120i_y - 5v_1 + 13v_2 = 95$$

$$\text{but } i_y = \frac{10 - v_1}{4}$$

$$\therefore 120\left(\frac{10 - v_1}{4}\right) - 5v_1 + 13v_2 = 95$$

$$\hookrightarrow \quad \underline{-35v_1 + 13v_2 = -205}$$


**Questions 13 to 16 [4]**

Use mesh analysis to set up two equations in the form:

$$ei_2 + fi_3 = 90,$$

$$-i_2 + gi_3 = h.$$

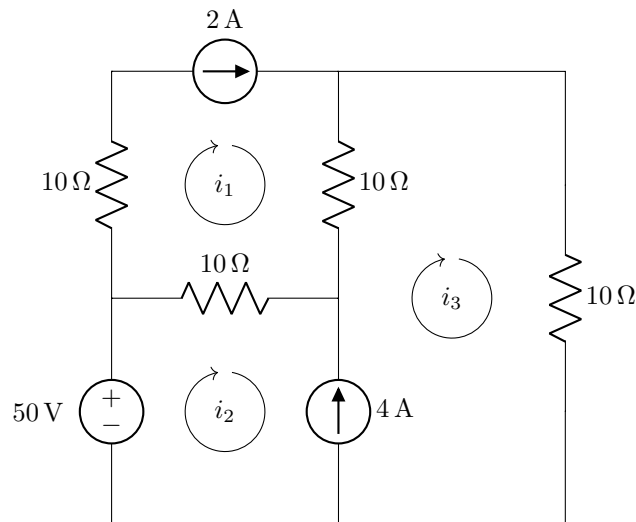Calculate the unknown coefficients  $e$ ,  $f$ ,  $g$ , and  $h$ .



|           |         |
|-----------|---------|
| <b>13</b> | $e$ [1] |
| <b>14</b> | $f$ [1] |
| <b>15</b> | $g$ [1] |
| <b>16</b> | $h$ [1] |

$$* i_1 = 2A$$

Supermesh


$$-50 + 10i_2 - 10i_1 + 10i_3 - 10i_1 + 10i_3 = 0$$

$$10i_2 + 20i_3 = 50 + 20(2) = 90$$

KCL:

$$-i_2 + i_3 = 4$$

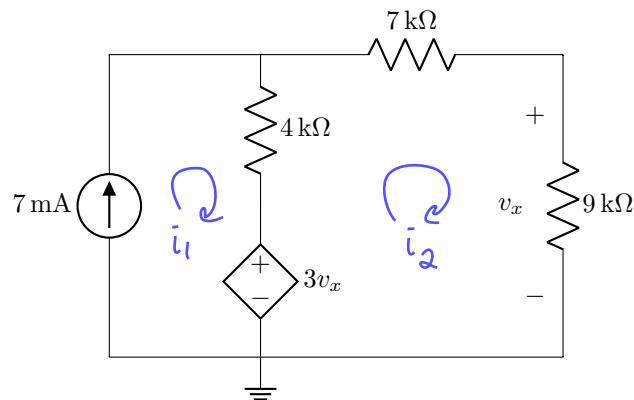

**Question 17 [2]**Determine  $v_x$  using either nodal or mesh analysis.17  $v_x$  [2]\* Mesh:

$$i_1 = 7 \text{ mA}$$

$$-3v_x + i_2(4\text{k} + 7\text{k} + 9\text{k}) - i_1(4\text{k}) = 0$$

$$(20\text{k})i_2 - 3v_x = 4\text{k} \times 7\text{mA}$$

$$\text{but } i_2 = \frac{v_x}{9\text{k}}$$

$$\therefore \frac{20\text{k}}{9\text{k}} v_x - 3v_x = 28$$

$$v_x = \frac{28}{\frac{20}{9} - 3} = -36 \text{ V} \rightarrow$$

\* Nodal

$$7\text{mA} = \frac{V_1 - 3v_x}{4\text{k}} + \frac{V_1}{16\text{k}}$$

$$(\times 16\text{k}) \quad 112 = 4V_1 - 12v_x + V_1 = 5V_1 - 12v_x$$

$$\text{but } v_x = \frac{9V_1}{16} \rightarrow V_1 = \frac{16v_x}{9}$$

$$\hookrightarrow 112 = \left(5\left(\frac{16}{9}\right) - 12\right)v_x$$


$$v_x = -36 \text{ V} \rightarrow$$

## Questions 18 to 20 [3]

The matrix below was constructed by means of inspection in terms of the node voltages for the circuit below:

$$\begin{bmatrix} 0.35 & -0.1 & -0.05 \\ -0.1 & 0.4 & -0.2 \\ -0.05 & -0.2 & 0.25 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \end{bmatrix} = \begin{bmatrix} 100 \\ 50 \\ -10 \end{bmatrix}$$

Determine  $R_1$ ,  $R_2$ , and  $I_S$ .

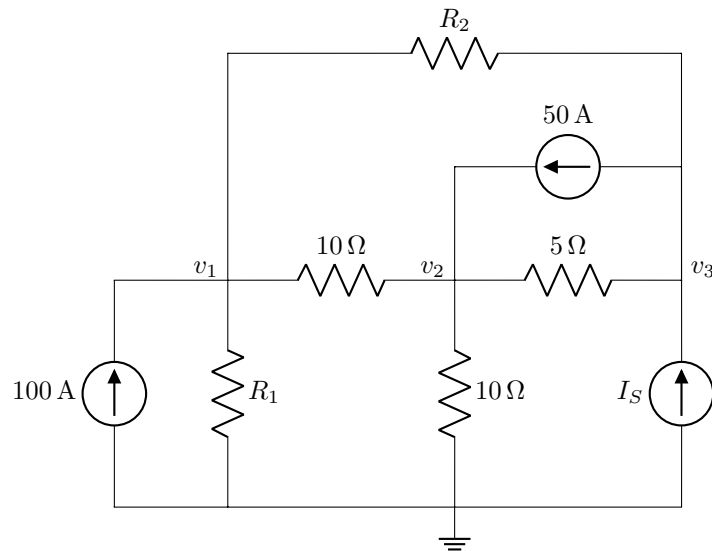

18  $R_1$  [1]

19  $R_2$  [1]

20  $I_S$  [1]

$$* R_2 = \frac{1}{0.05} = \underline{20\Omega}$$


$$* R_1 = (0.35 - 0.05 - 0.1)^{-1} = \frac{1}{0.2} = \underline{5\Omega}$$

$$* I_S - 50 = -10$$

$$I_S = \underline{40 A}$$

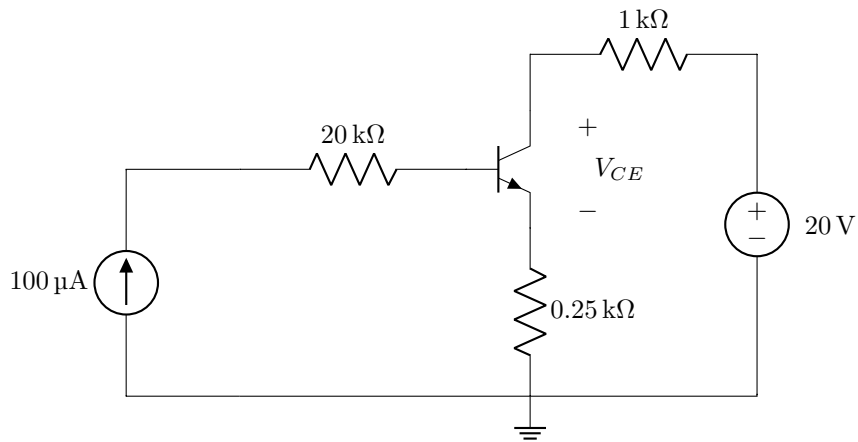**Question 21 [2]**

Assume  $I_B = 100 \mu\text{A}$  and  $\beta = 99$ , determine  $V_{CE}$ .



**21** |  $V_{CE}$  [2]


$$\begin{aligned} V_{CE} &= 20 - 1k(99 \times 100\mu) - 0.25k(99+1)(100\mu) \\ &= 20 - 9.9 - 2.5 \\ &= \underline{7.6 V} \end{aligned}$$

**Total Section 1: [31]**

## Section 2
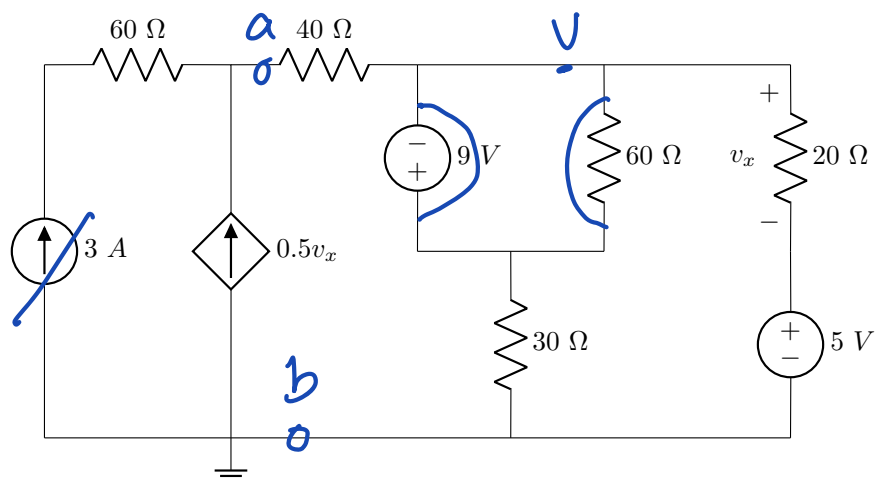
## Questions 22 to 23 [4]

Use superposition to determine: 1)  $v_x^1$ , the exclusive contribution from the 5 V independent voltage source to  $v_x$ ; and 2)  $v_x^2$ , the exclusive contribution from the 3 A independent current source to  $v_x$ .



22  $v_x^1$  [2]

23  $v_x^2$  [2]

22. When only 5V is functioning, use nodal analysis

$$-0.5V_x + \frac{V}{30} + \frac{V-5}{20} = 0, \quad V_x = V-5$$

$$-0.5(V-5) + \frac{V}{30} + \frac{V-5}{20} = 0, \quad \times 60$$

$$-30(V-5) + 2V + 3V - 15 = 0$$

$$\Rightarrow -25V = -135 \Rightarrow V = 5.4 \text{ V}$$


$$V_x^1 = V - 5 = 0.4 \text{ V}$$

23. When only the 3A is functioning, use nodal analysis:

$$V_x = 12(3 + 0.5V_x)$$

$$\Rightarrow 5V_x = -36$$

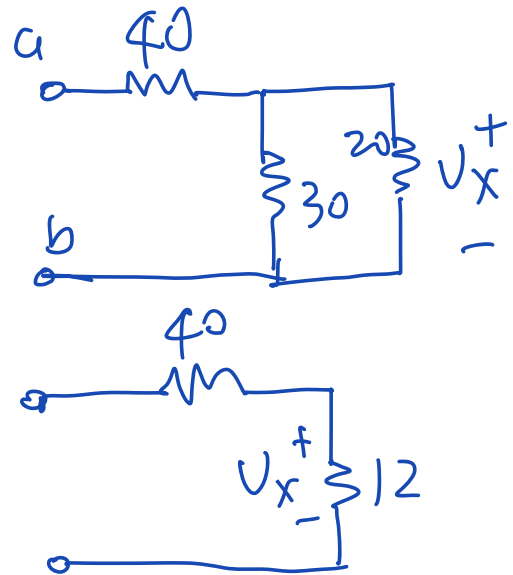
$$\Rightarrow \underline{V_x = -7.2 \text{ V.}}$$





## Questions 24 to 25 [3]

Use source transformation to transform Circuit A to Circuit B.

Circuit A:

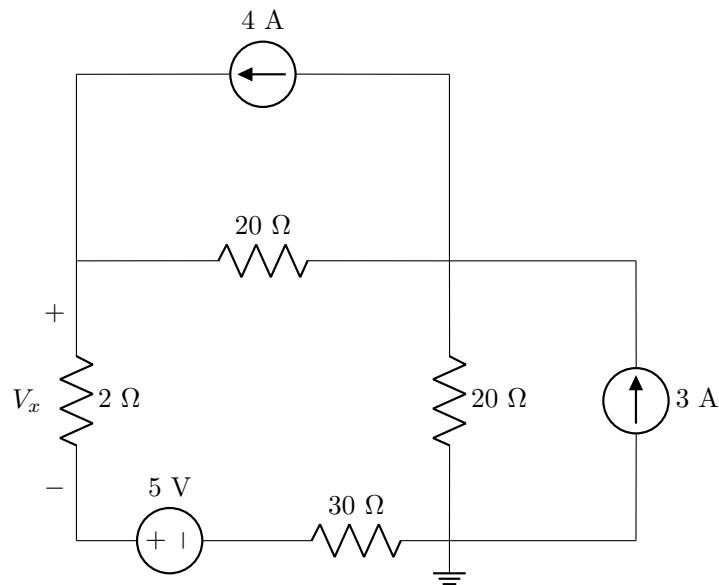


Circuit B:

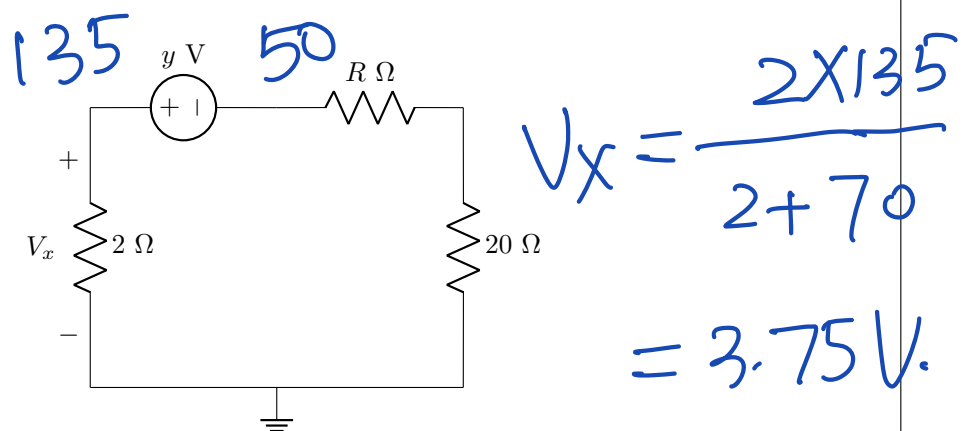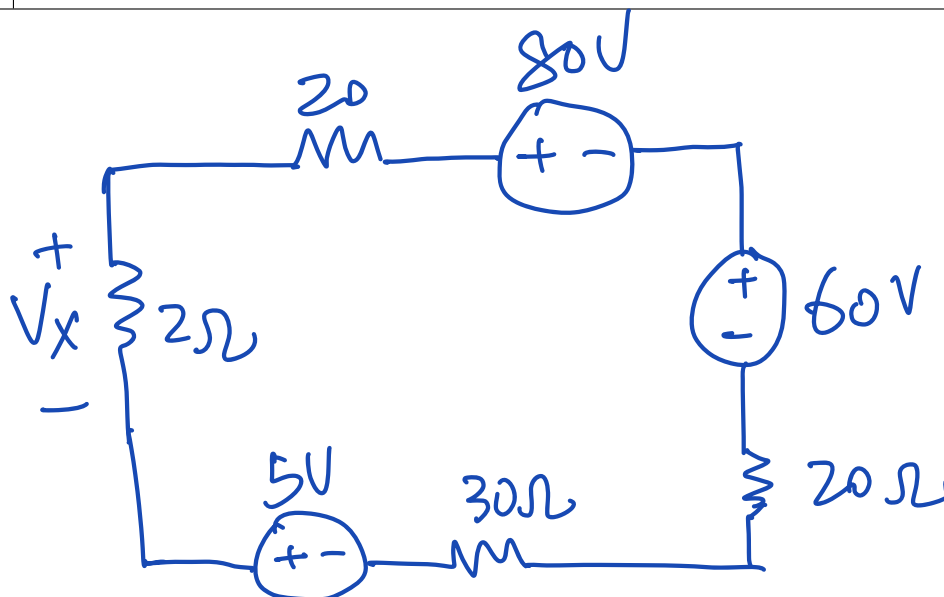
24  $y$  [2]25  $V_x$  [1]

## Questions 26 to 27 [4]

Determine the Thévenin equivalent voltage  $V_{Th}$ , and the Thévenin equivalent resistance  $R_{Th}$  between terminals  $a - b$ .

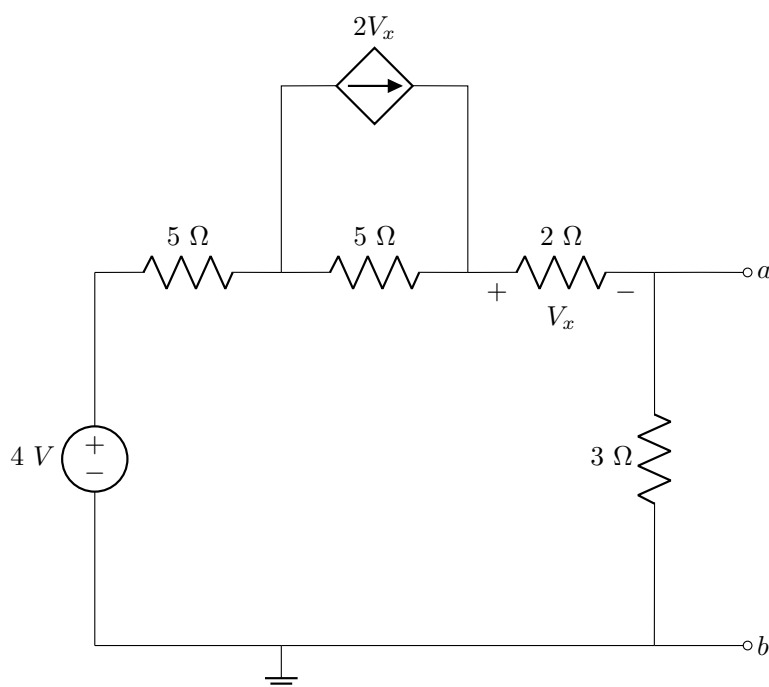26  $V_{Th}$  [2]27  $R_{Th}$  [2]

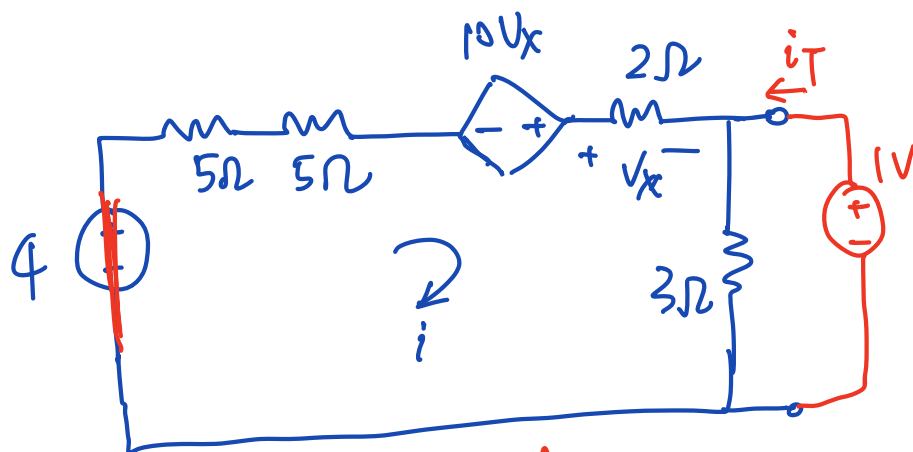
$$\begin{aligned}
 V_{Th} &= 3i, \quad V_x = 2i \\
 -4 + 15i - 10V_x &= 0 \\
 -4 + 25i - 20i &= 0 \\
 \Rightarrow 5i &= 4 \Rightarrow i = 0.8 \\
 V_{Th} &= 2.4V.
 \end{aligned}$$



$$\begin{aligned}
 i_T &= \frac{1}{3} + \frac{1 - 10V_x}{12} \\
 V_x &= -2 \cdot \frac{1 - 10V_x}{12} \\
 \Rightarrow 12V_x &= -2 + 20V_x \\
 \Rightarrow V_x &= \frac{1}{4}, \Rightarrow i_T = \frac{1}{3} + \frac{1 - 2.5}{12} \\
 &= \frac{1}{3} - \frac{1}{8} \\
 R_{Th} &= \frac{1}{i_T} = 4.8\Omega
 \end{aligned}$$
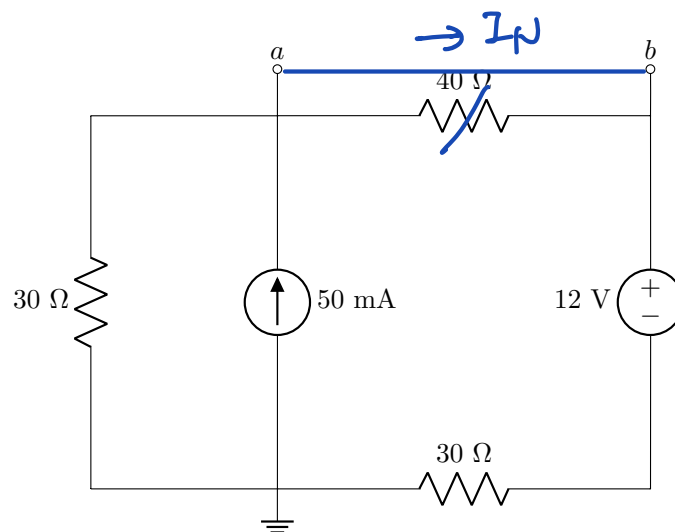
## Questions 28 to 29 [4]

Determine the Norton equivalent current  $I_N$  and resistance  $R_N$  between terminals  $a - b$ .




28  $I_N$  [2]

29  $R_N$  [2] : use source transformation.

$$R_N = 40 \parallel 60 = 24 \Omega.$$


$$I_N = \frac{1.5 - 12}{60} = -0.175.$$

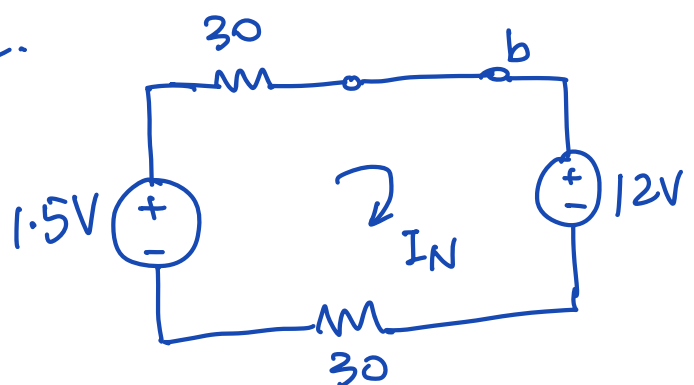



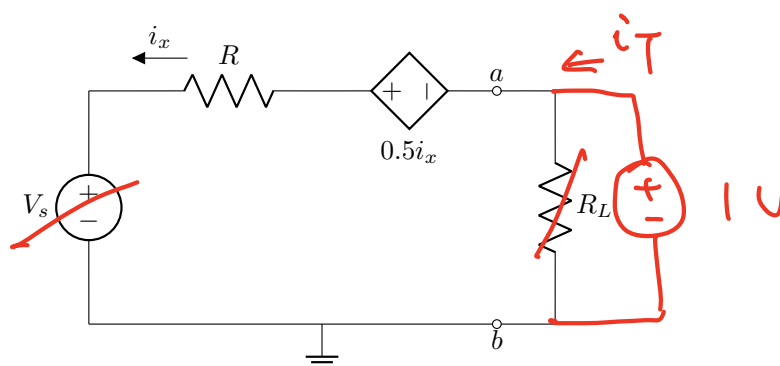**Question 30 [2]**

In the circuit below,  $i_x = 2$  mA, and the maximum power  $P_{max} = 500$  mW is delivered to the load  $R_L$ . Determine the Thévenin equivalent voltage  $V_{TH}$  of the circuit between terminals  $a - b$ .



30  $V_{TH}$  [2]

$$P_{max} = \frac{V_{Th}^2}{4R_L} = 0.5$$

when open circuit:  $V_{Th} = V_s - 0.5i_x$ ,  $i_x = 0$

$$\Rightarrow V_{Th} = V_s,$$

$$i_T = i_x = \frac{1 + 0.5i_x}{R} \Rightarrow R = \frac{1 + 0.5i_x}{i_x} = \frac{1}{i_x} + 0.5$$


$$i_x = 1 \text{ A} \Rightarrow R_{Th} = \frac{1}{i_T} = \frac{R}{1 + 0.5i_x} = 0.5 \Omega.$$

$$R_{Th} = R_L.$$

$$\Rightarrow V_{Th} = \sqrt{4 \times 0.5 \times 0.5} = 1 \text{ V.}$$

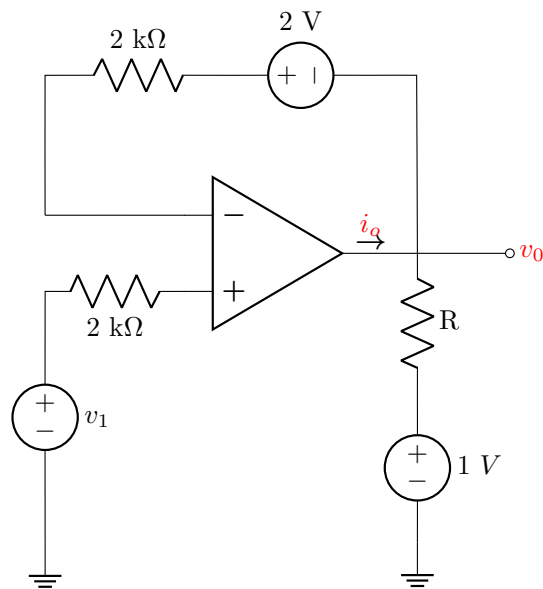**Questions 31 to 32 [4]**

Assume that the operational amplifier is ideal, determine  $v_1$  and  $i_o$  if  $v_o = 5\text{ V}$  and  $R = 4\text{ k}\Omega$ .



**31**  $v_1$  [2]


**32**  $i_o$  [2]

$$V_o = V_i - 2 = 5\text{ V} \Rightarrow V_i = 7\text{ V}.$$

$$i_o = \frac{V_o - 1}{R} = \frac{4}{4\text{ k}} = 1\text{ mA}.$$

## Questions 33 to 34 [4]

The operational amplifier is ideal.

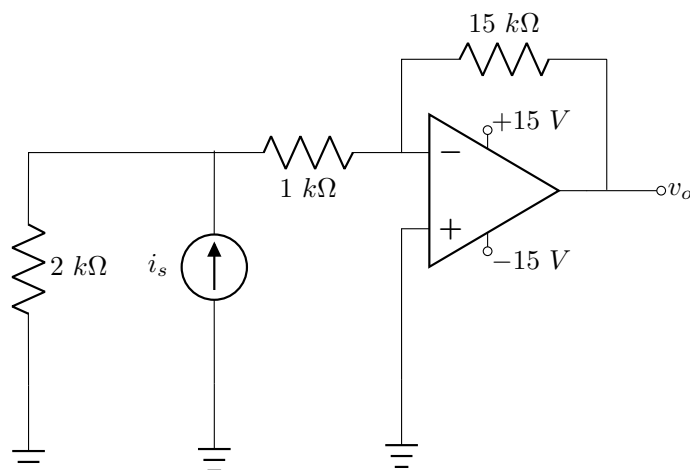**33** Determine  $v_o$  when  $i_s = 6$  mA. [2]**34** What is the maximum value of  $i_s$  that drives the operational amplifier to negative saturation? [2]

*minimum such that is just about to enter*

$$33. \quad i = i_s \cdot \frac{2}{2+1} = 6 \cdot \frac{2}{3} = 4 \text{ mA.}$$

$$= \frac{0 - V_o}{15k} \Rightarrow V_o = -60 \text{ V.}$$

Due to saturation,  $V_o = -15 \text{ V.}$


$$34. \quad i = i_s \cdot \frac{2}{3} = \frac{0 - V_o}{15k}$$

$$\Rightarrow V_o = -i_s \cdot 15k \cdot \frac{2}{3} \leq -15$$

$$\Rightarrow i_s \geq 15 \cdot \frac{3}{2} \cdot \frac{1}{15k}$$

$$i_s \geq 1.5 \text{ mA.}$$

$$i_s^{\min} = 1.5 \text{ mA}$$

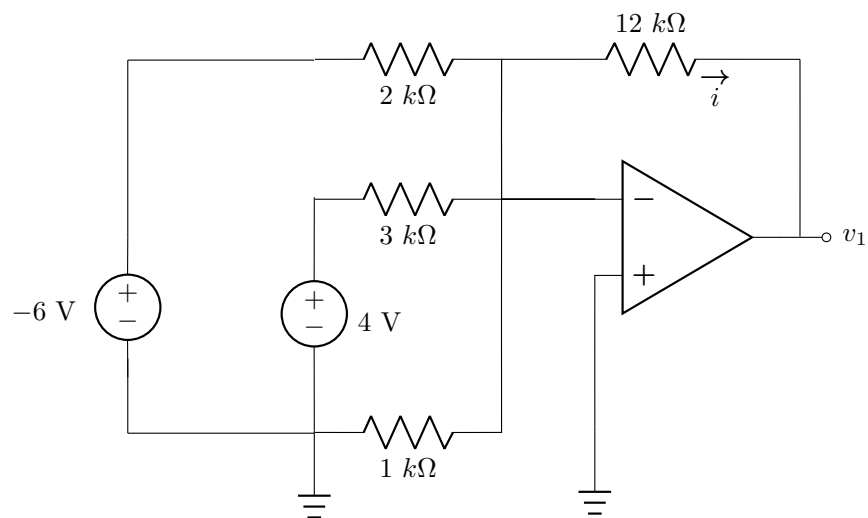**Question 35 [2]**Assume that the operational amplifier is ideal, determine  $v_1$ .**35** |  $v_1$  [2]

35.


$$\frac{-6}{2\text{k}} + \frac{4}{3\text{k}} = \frac{0 - v_1}{12\text{k}}$$

$$\Rightarrow -36 + 16 = -v_1$$

$$\Rightarrow v_1 = 20\text{ V.}$$

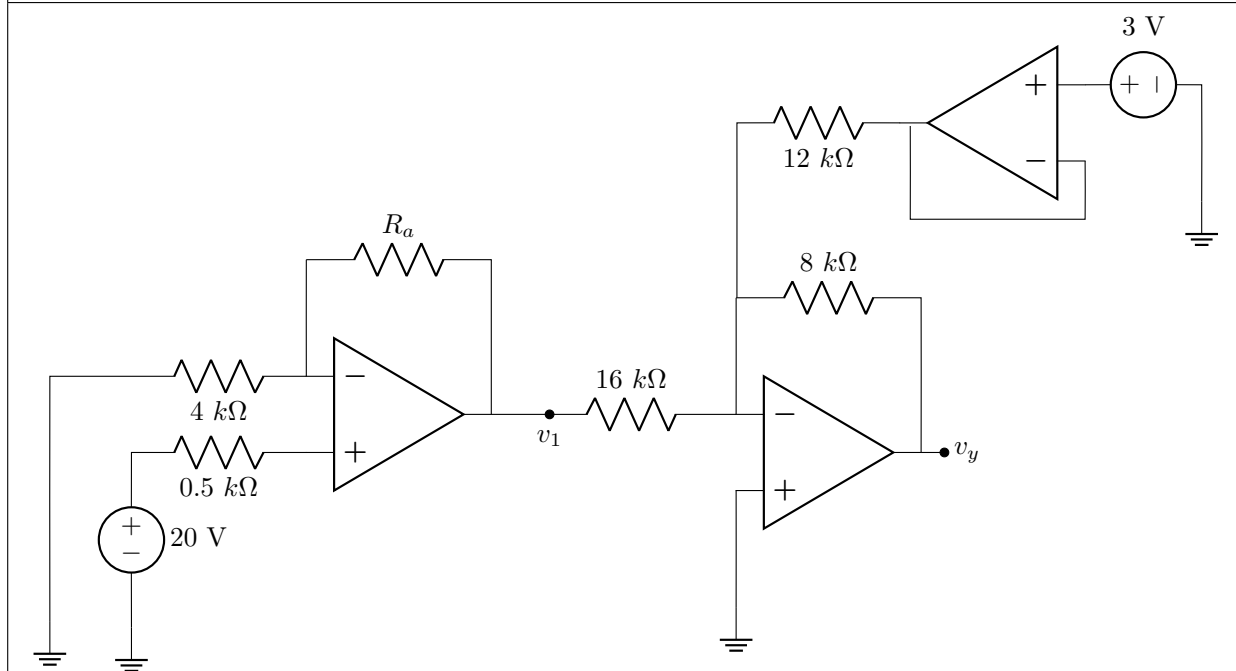**Questions 36 to 37 [4]**

Assume that the operational amplifiers are ideal, calculate  $R_a$  and  $v_y$  when  $v_1 = 30$  V.



**36**  $R_a$  [2]

**37**  $v_y$  [2]

36.  $30 = 20 \left( 1 + \frac{R_a}{4k} \right) \Rightarrow 1 + \frac{R_a}{4k} = 1.5$   
 $\Rightarrow R_a = 2k \Omega.$


37.  $v_y = -30 \cdot \frac{8}{16} - 3 \cdot \frac{8}{12}$   
 $= -15 - 2 = -17V.$

**Total Section 2: [31]**

|                  |
|------------------|
| <b>Section 3</b> |
|------------------|


|                        |
|------------------------|
| <b>Question 38 [1]</b> |
|------------------------|

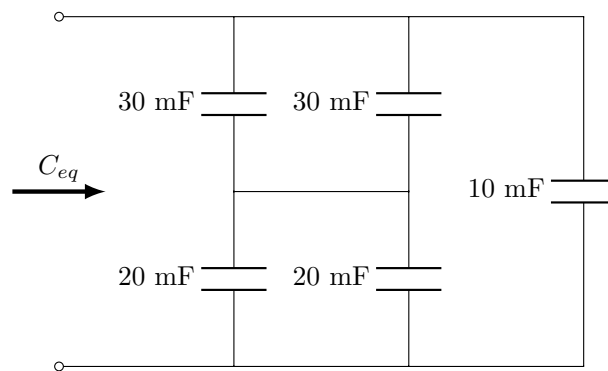Find the equivalent capacitance  $C_{eq}$  in the circuit below.



|           |              |
|-----------|--------------|
| <b>38</b> | $C_{eq}$ [1] |
|-----------|--------------|


(38)

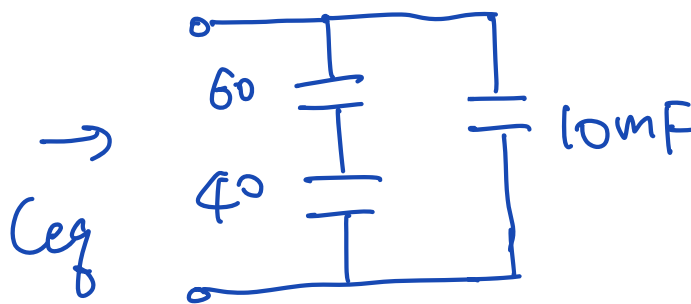

$$\frac{60 \times 40}{60 + 40} = 24 \text{ mF} \Rightarrow C_{eq} = 34 \text{ mF}.$$

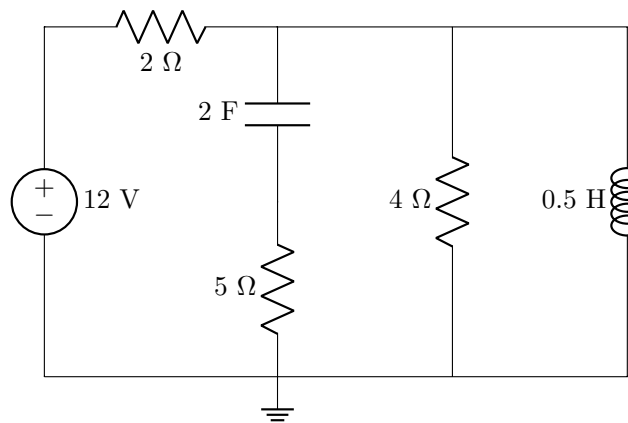**Question 39 [2]**

Under dc conditions, the energy stored in the inductor is denoted as  $w_L$  and the energy stored in the capacitor is  $w_C$ . Calculate the total energy  $w_T = w_C + w_L$ .



39  $w_T$  [2]

39


$$V_C = 0 \Rightarrow w_C = 0$$

$$i_L = \frac{12}{2} = 6 \text{ A}$$

$$\Rightarrow w_L = \frac{1}{2} L i_L^2 = \frac{1}{2} \times 0.5 \times 6^2 = 9 \text{ J.}$$

$$w_T = w_L + w_C = 9 \text{ J}$$

## Questions 40 to 41 [4]

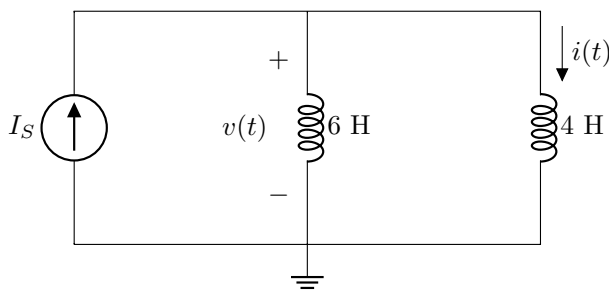

- |    |                                                                               |
|----|-------------------------------------------------------------------------------|
| 40 | When $I_S = 4e^{-2t}$ A, determine $v(t)$ at $t = 2$ ms. [2]                  |
| 41 | When $I_S = 2t + 1$ A, determine $i(t)$ at $t = 4$ s, given $i(0) = 2$ A. [2] |

$$\begin{aligned}
 40: v(t) &= L \frac{di}{dt} = (6 \parallel 4) \times (4e^{-2t})' \\
 &= 2.4 \times 4 \times (-2) e^{-2t} \\
 &= -19.2 e^{-2t} \\
 v(2\text{ms}) &= -19.2 e^{-2 \times 2 \times 10^{-3}} = -19.12 \text{ V.}
 \end{aligned}$$

$$41: v(t) = L \frac{di}{dt} = 2.4 \cdot 2 = 4.8 \text{ V.}$$

$$\begin{aligned}
 i(t) &= \frac{1}{L} \int_0^t 4.8 dt + 2 \\
 &= \frac{1}{4} \cdot [4.8t]_0^t + 2 \\
 &= \frac{1}{4} \times 4.8 \times 4 + 2 = 6.8 \text{ A.}
 \end{aligned}$$



## Questions 42 to 43 [4]

Consider two sinusoid waveforms  $v_1(t)$  and  $v_2(t)$ , where

$$v_1(t) = -60 \cos(30t + 10^\circ), \text{ and}$$

$$v_2(t) = 50 \cos(30t + 50^\circ) - 120 \sin(30t).$$

The waveforms  $v_1(t)$  and  $v_2(t)$  can be represented by phasors  $\mathbf{V}_1$  and  $\mathbf{V}_2$ , respectively.

42 Choose the correct statement.

1.  $v_1$  leads  $v_2$  by  $60^\circ$ .
2.  $v_2$  leads  $v_1$  by  $60^\circ$ .
3.  $v_1$  leads  $v_2$  by  $101.47^\circ$ .
4.  $v_2$  leads  $v_1$  by  $101.47^\circ$ .

5. **None** of the above statements are correct.

Write the correct statement number as your answer, choose one from 1, 2, 3, 4, or 5. [2]

43 Find  $\mathbf{V}_T = \mathbf{V}_1 + \mathbf{V}_2$ . [2]


$$42: V_2' = 50 \angle 50^\circ$$

$$V_2'' = 120 \angle 90^\circ$$

$$V_2 = 161.53 \angle 78.52^\circ$$


Rotate  $V_1, V_2$  counter clockwise by  $120^\circ$ , then

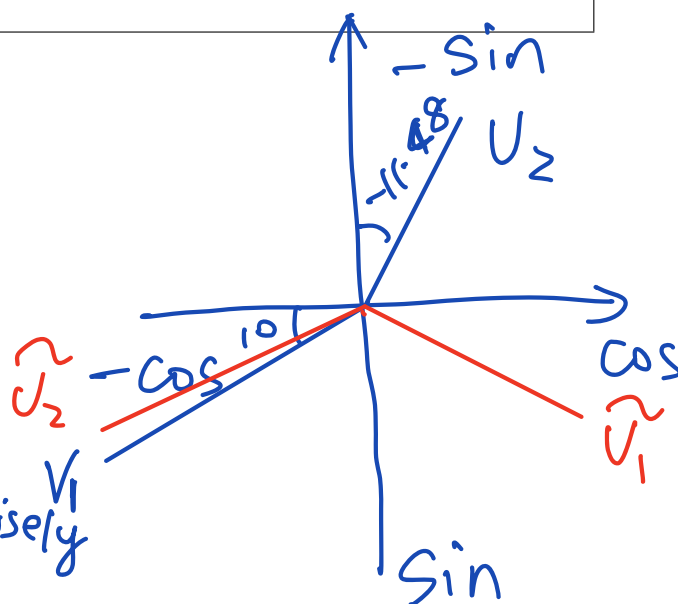$V_1$  leads  $V_2$  by  $111.48^\circ$ .



$$43: V_T = 150.32 \angle 100.33^\circ$$

## Questions 44 to 45 [4]

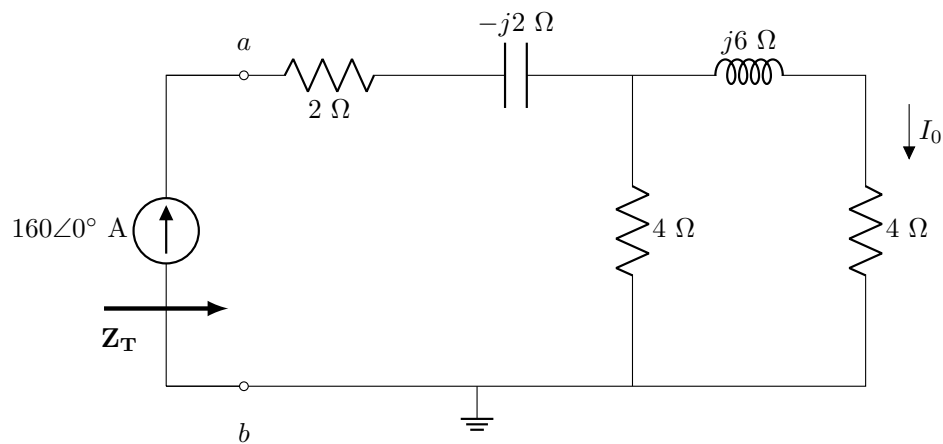

44 Find  $Z_T$  with respect to terminals  $a - b$ . [2]


45 Find  $I_0$ . [2]

(44)

$$Z_T = 2 - j2 + \frac{4(4 + j6)}{8 + j6} = 4.72 - j1.04 \Omega.$$

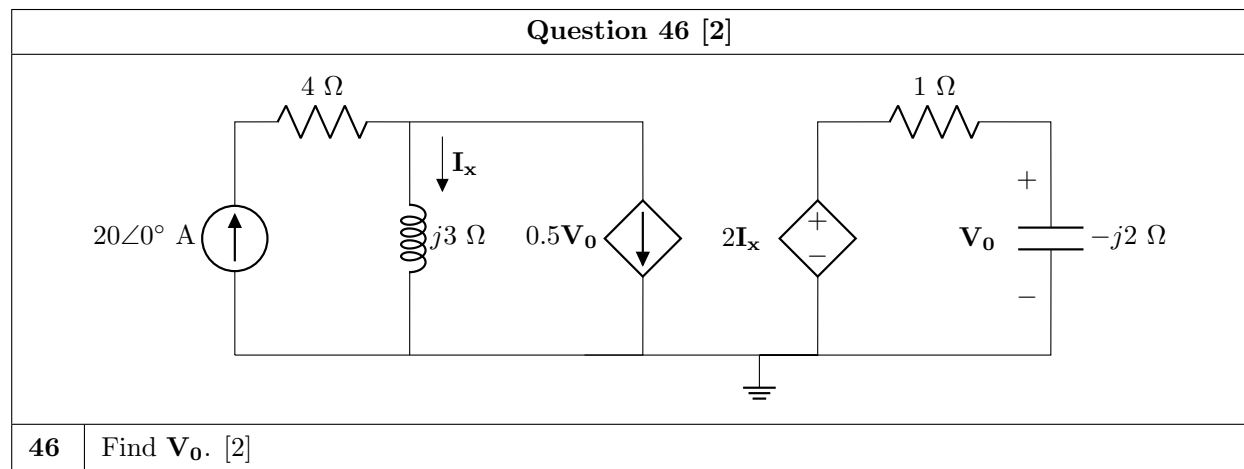(45)

$$I_0 = 160 \cdot \frac{4}{8 + j6} = 51.2 - j38.4 \text{ (A)}$$



46

$$I_x = 20 - 0.5V_0$$

$$V_0 = 2I_x \cdot \frac{-j2}{1-j2} \Rightarrow$$

$$(1-j2)V_0 = 2(20 - 0.5V_0)(-j2)$$


$$= (40 - V_0)(-j2)$$

$$= -j80 + j2V_0$$

$$(1-j4)V_0 = -j80$$

$$\Rightarrow V_0 = \frac{-j80}{1-j4} = 18.82 - j4.706 \text{ V}$$

## Questions 47 to 48 [4]

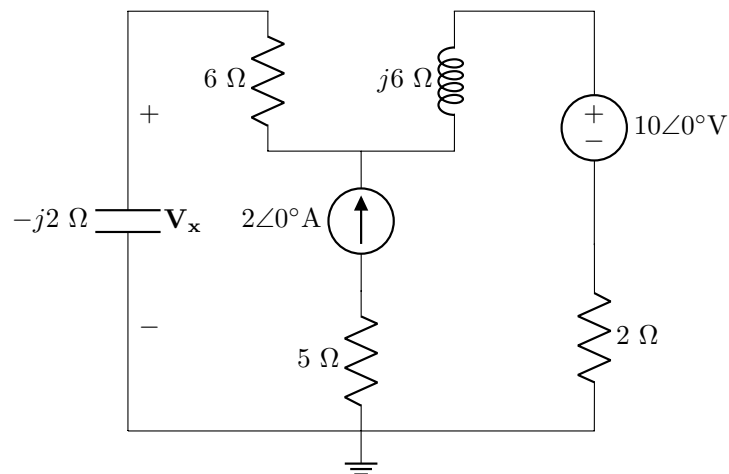

47 Find  $\mathbf{V}_x^1$ , the exclusive contribution from the voltage source to  $\mathbf{V}_x$ . [2]

48 Find  $\mathbf{V}_x^2$ , the exclusive contribution from the current source to  $\mathbf{V}_x$ . [2]

47: When  $2\angle 0^\circ \text{ A}$  is off, then

$$V_x^1 = 10 \cdot \frac{-j2}{8+j4} = -1-j2$$


48: when  $10\angle 0^\circ$  is off, then

$$V_x^2 = 2 \cdot \frac{2+j6}{8+j4} \cdot (-j2) = 2-j2$$



## Questions 49 to 50 [4]

Use source transformation to transfer Circuit A to Circuit B.

Circuit A:

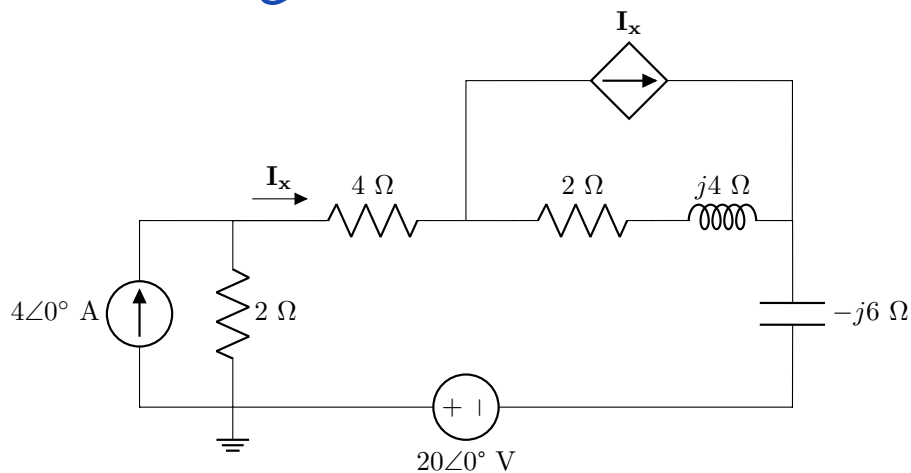

Circuit B:

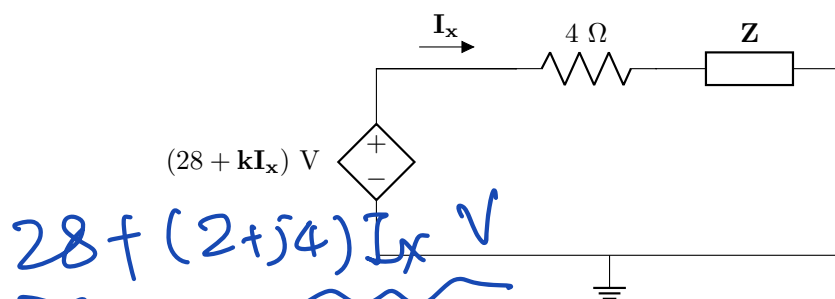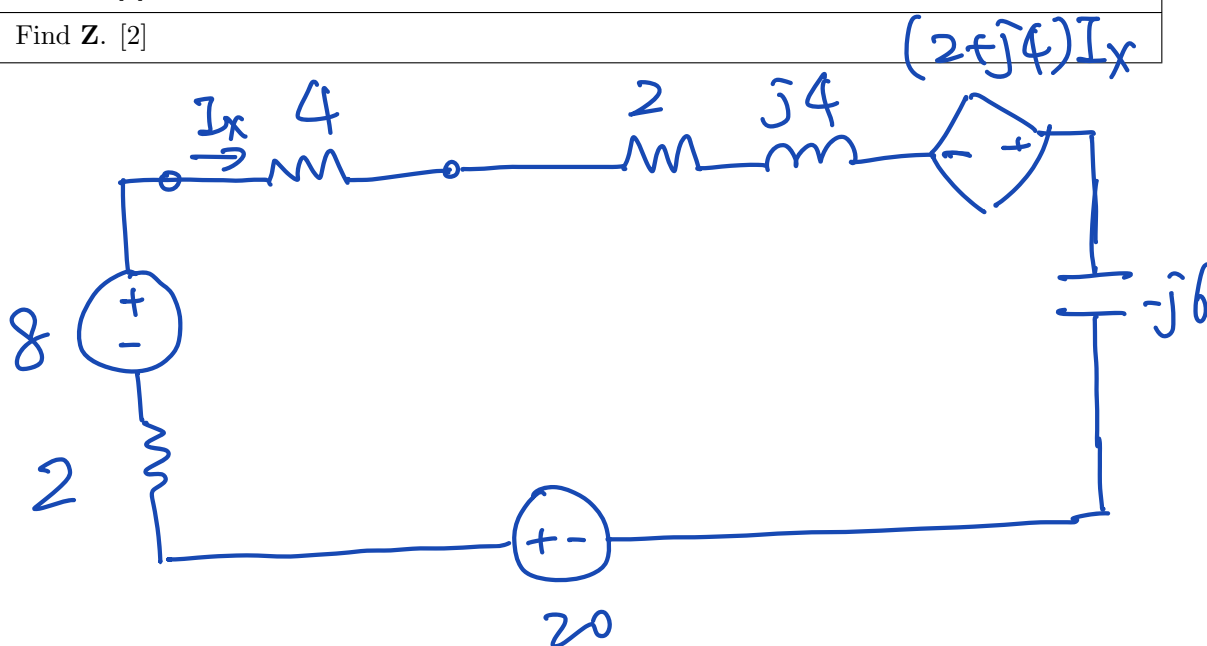
49 Find  $k$ . [2]50 Find  $Z$ . [2]

49  $Z = 2 + j4 - j6 + 2 = 4 - j2\ \Omega$ .

50  $k = 2 + j4$ .

## Questions 51 to 52 [4]

Find the Thévenin equivalent voltage  $V_{Th}$ , and Thévenin equivalent impedance  $Z_{Th}$  with respect to terminals  $a - b$ .

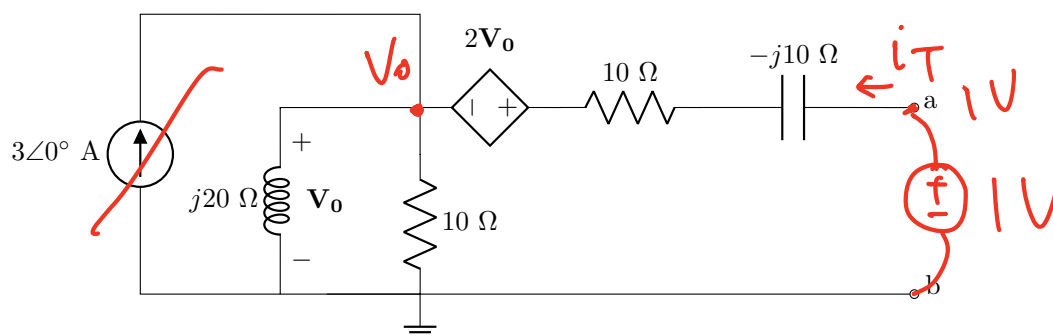51  $V_{Th}$  [2]52  $Z_{Th}$  [2]

$$V_{Th} = 2V_0 + V_0 = 3V_0$$

$$V_0 = 3 \cdot \frac{j20 \times 10}{10 + j20} = 24 + j12$$

$$\Rightarrow V_{Th} = 72 + j36 \text{ V.}$$

$$\frac{V_0}{j20} + \frac{V_0}{10} + \frac{3V_0 - 1}{10 - j10} = 0, \quad \text{for } Z_{Th}, \text{ add } 1\angle 0^\circ \text{ V test voltage.}$$

switch off  $3\angle 0^\circ \text{ A}$ .

$$-j0.05 V_0 + 0.1 V_0 + (0.15 + j0.15) V_0 = 0.05 + j0.05$$


$$\Rightarrow (0.25 + j0.1) V_0 = 0.05 + j0.05$$

$$V_0 = \frac{0.05 + j0.05}{0.25 + j0.1} = \frac{5 + j5}{25 + j10} = \frac{1 + j}{5 + j2}$$

$$i_T = \frac{1-3U_0}{10-j10} = \frac{2-j}{(10-j10)(5+j2)}$$

$$Z_T = \frac{1}{i_T} = \frac{(10-j10)(5+j2)}{2-j}$$

$$= 34+j2 \Omega.$$

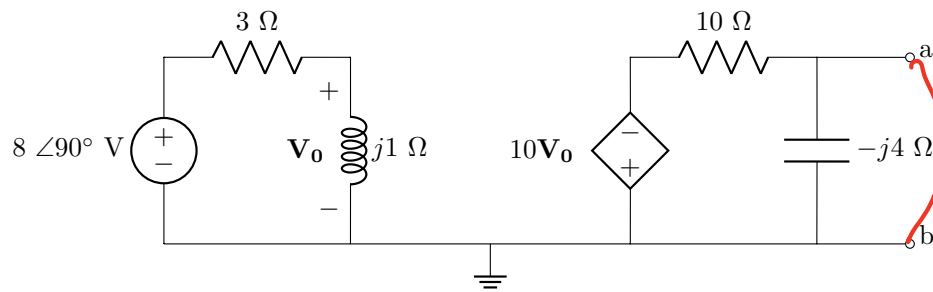**Question 53 [2]**Determine the Norton equivalent current  $I_N$  with respect to terminals  $a - b$ .53  $I_N$  [2]

$$I_N = \frac{-10V_0}{10} = -V_0.$$

$$V_0 = j8 \cdot \frac{j}{3+j} = \frac{-8}{3+j}$$

$$\Rightarrow I_N = \frac{8}{3+j} = 2.4 - j0.8 \text{ A}$$

**Total Section 3: [31]****Grand Total : [93]**



**PRACTICE ANSWER SHEET**

|                |   |   |   |   |   |   |   |   |   |   |   |   |   |
|----------------|---|---|---|---|---|---|---|---|---|---|---|---|---|
| Assessment ID: | 2 | 0 | 2 | 2 | E | B | N | 1 | 1 | 1 | E | 0 | 1 |
|----------------|---|---|---|---|---|---|---|---|---|---|---|---|---|

| Enter complex numbers on OCR forms: |   |   |   |   |   |   |   |   |   |   |
|-------------------------------------|---|---|---|---|---|---|---|---|---|---|
| 5                                   | ∠ | - | 9 | 0 | ° |   |   |   | V |   |
| 6                                   | . | 9 | ∠ | 1 | 5 | . | 9 | ° | μ | A |
| 1                                   | 2 | - | j | 8 |   |   |   |   |   |   |
| j                                   | 1 | 5 |   |   |   |   |   |   | Ω |   |
| -                                   | 1 | . | 5 | + | j | 8 | . | 2 | m | V |

Complex numbers can be entered in either **rectangular** or **polar** form.

**Rectangular:** The  $j$  is at the start of the imaginary number.

The  $j$  is in the CENTRE of the cell.

The  $j$  does NOT cross or touch cell boundaries!

**Polar:** The degree sign ° is directly after the angle value.

**Round irrational numbers to a minimum of 4 significant figures.**

| Answer    |                        | Unit             |
|-----------|------------------------|------------------|
| SECTION 1 |                        |                  |
| 01        | Annual cost (in Rand)= | No unit required |
| 02        | $W_T =$                |                  |
| 03        | $P_1 =$                |                  |
| 04        | $P_2 =$                |                  |
| 05        | $i_z =$                |                  |
| 06        | $v_z =$                |                  |
| 07        | $R_{ab} =$             |                  |
| 08        | $R_{cd} =$             |                  |
| 09        | $a =$                  | No unit required |
| 10        | $b =$                  | No unit required |
| 11        | $c =$                  | No unit required |
| 12        | $d =$                  | No unit required |
| 13        | $e =$                  | No unit required |
| 14        | $f =$                  | No unit required |
| 15        | $g =$                  | No unit required |
| 16        | $h =$                  | No unit required |
| 17        | $v_x =$                |                  |
| 18        | $R_1 =$                |                  |
| 19        | $R_2 =$                |                  |
| 20        | $I_S =$                |                  |
| 21        | $V_{CE} =$             |                  |

Round irrational numbers to a minimum of 4 significant figures.

| Answer    |                           | Unit             |
|-----------|---------------------------|------------------|
| SECTION 2 |                           |                  |
| 22        | $v_x^1 =$                 |                  |
| 23        | $v_x^2 =$                 |                  |
| 24        | $y =$                     |                  |
| 25        | $V_x =$                   |                  |
| 26        | $V_{Th} =$                |                  |
| 27        | $R_{Th} =$                |                  |
| 28        | $I_N =$                   |                  |
| 29        | $R_N =$                   |                  |
| 30        | $V_{TH} =$                |                  |
| 31        | $v_1 =$                   |                  |
| 32        | $i_o =$                   |                  |
| 33        | $v_o =$                   |                  |
| 34        | $i_s =$                   |                  |
| 35        | $v_1 =$                   |                  |
| 36        | $R_a =$                   |                  |
| 37        | $v_y =$                   |                  |
| SECTION 3 |                           |                  |
| 38        | $C_{eq} =$                |                  |
| 39        | $w_T =$                   |                  |
| 40        | $v(2 \text{ ms}) =$       |                  |
| 41        | $i(4 \text{ s}) =$        |                  |
| 42        | The correct statement is: | No unit required |
| 43        | $\mathbf{V_T} =$          |                  |
| 44        | $\mathbf{Z_T} =$          |                  |
| 45        | $\mathbf{I_0} =$          |                  |
| 46        | $\mathbf{V_0} =$          |                  |
| 47        | $\mathbf{V_x^1} =$        |                  |
| 48        | $\mathbf{V_x^2} =$        |                  |
| 49        | $\mathbf{k} =$            | No unit required |
| 50        | $\mathbf{Z} =$            |                  |
| 51        | $\mathbf{V_{Th}} =$       |                  |
| 52        | $\mathbf{Z_{Th}} =$       |                  |
| 53        | $\mathbf{I_N} =$          |                  |