

Circuit Theorems - Chapter 4

- L#1 4.2 Linearity Property
- 4.3 Superposition
- L#2 4.4 Source Transformation
- L#3 4.5 Thevenin's Theorem
- L#4 4.6 Norton's Theorem
- L#5 4.8 Maximum Power Transfer




UNIVERSITEIT VAN PRETORIA
UNIVERSITY OF PRETORIA
YUNIBESITHI YA PRETORIA

Department of Electrical, Electronic and Computer Engineering

1

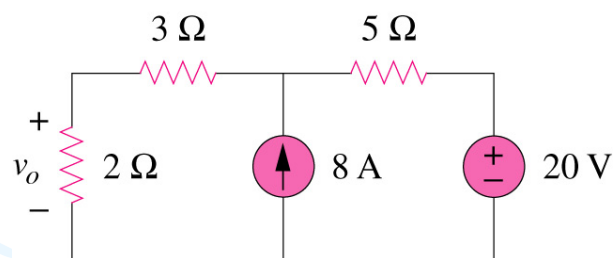4.1 Motivation

If you are given the following circuit, are there any other alternative(s) to determine the voltage across 2Ω resistor?



What are they? And how?

Can you work it out by inspection?



UNIVERSITEIT VAN PRETORIA
UNIVERSITY OF PRETORIA
YUNIBESITHI YA PRETORIA

Department of Electrical, Electronic and Computer Engineering

2

4.2 Linearity Property

It is the property of an element describing a linear relationship between cause and effect.

A linear circuit is one whose **output** is linearly related (or directly proportional) to its **input**.

Two property of linearity

1. Homogeneity (scaling):


$$v = Ri$$

$$\rightarrow kv = kRi$$

2. Additive (Superposition):

$$v_1 = Ri_1 \text{ and } v_2 = Ri_2$$

$$v = v_1 + v_2 = (i_1 + i_2)R$$

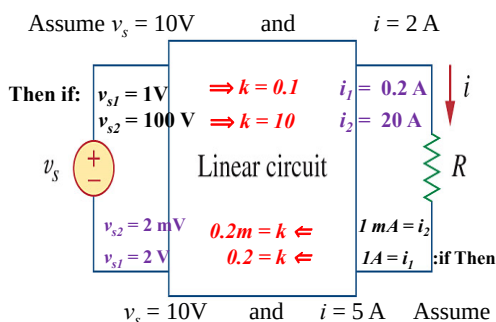


Department of Electrical, Electronic and Computer Engineering

3

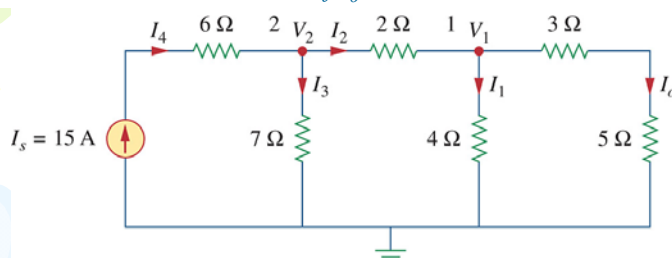Example 4.2

Assume $I_o = 1A$. Use linearity to find the relationship between I_o and I_s .
If $I_s = 15A$, what is the actual value of I_o in the circuit?



1. If $I_o = 1A$: $V_1 = 1 \times (3+5) = 8V$.
2. With $V_1 = 8V$: $I_1 = 8/4 = 2A$.
3. With $I_1 = 2A$: $I_2 = I_o + I_1 = 1+2 = 3A$ (KCL)
4. With $I_2 = 3A$: $V_2 = V_1 + I_2 \times 2 = 8+6 = 14V$ $I_2 = \frac{V_2 - V_1}{2}$
5. With $V_2 = 14V$: $I_3 = 14/7 = 2A$
6. With $I_3 = 2A$: $I_4 = I_2 + I_3 = 3 + 2 = 5A$ (KCL)
7. Thus: $I_o/I_4 = I_o/I_s = 1/5 = k$
8. Due to linearity: $I_{o_actual} = k * I_{s_actual} = 3A$




Department of Electrical, Electronic and Computer Engineering

4

PP 4.2

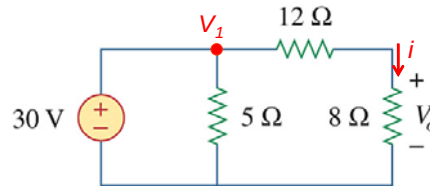Use linearity to calculate the relationship between V_1 and V_o . If $V_1=30\text{ V}$, what is the actual value of V_o ?



Using voltage division

$$V_o = V_1 \frac{8}{12+8} = 0.4 V_1 \Rightarrow k = 0.4$$

If V_1 equals 30 V, then according to linearity principle:

$$V_o = 0.4 V_1 \Rightarrow = 0.4 \times 30 = 12\text{ V}$$



UNIVERSITEIT VAN PRETORIA
UNIVERSITY OF PRETORIA
YUNIBESITHI YA PRETORIA

Department of Electrical, Electronic and Computer Engineering

5

4.3 Superposition Theorem

The voltage across (or current through) an element in a linear circuit is the algebraic sum of the voltage across (or currents through) that element due to EACH independent source acting alone.

$$\triangleright v = v_1 + v_2 + \dots + v_n$$

$$\triangleright i = i_1 + i_2 + \dots + i_n$$

The principle of superposition helps us to analyze a linear circuit with more than one independent source by calculating the contribution of each independent source separately.




UNIVERSITEIT VAN PRETORIA
UNIVERSITY OF PRETORIA
YUNIBESITHI YA PRETORIA

Department of Electrical, Electronic and Computer Engineering

6

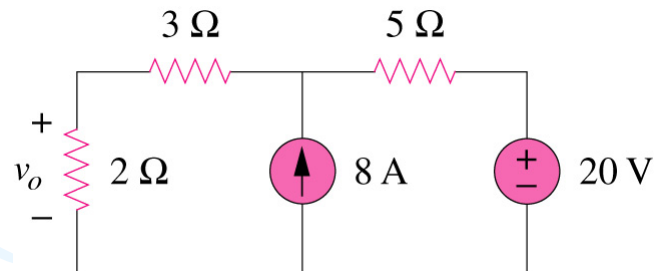4.3 Superposition Theorem

We consider the effects of 8A and 20V one by one, then add the two effects together for final v_o .



$$v_o = v_{8A} + v_{20V}$$

4.3 Superposition Theorem

STEPS

Steps to apply superposition principle

1. Turn off all independent sources except one source. Find the output (voltage or current) due to that active source using nodal or mesh analysis.
2. Repeat step 1 for each of the other independent sources.
3. Find the total contribution by adding algebraically all the contributions due to the independent sources.


4.3 Superposition Theorem

Zeroing of Sources


How do you **turn off** a source, i.e. make it zero?

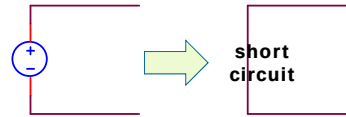1. Independent sources:

- Independent voltage sources are replaced by 0 V (**short circuit** ($R=0\ \Omega$)).



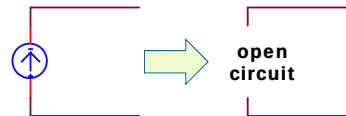- Independent current sources are replaced by 0 A (**open circuit** ($R \rightarrow \infty\ \Omega$)).



2. Dependent sources **are left intact** because they are controlled by circuit variables.




UNIVERSITEIT VAN PRETORIA
UNIVERSITY OF PRETORIA
YUNIBESITHI YA PRETORIA

Department of Electrical, Electronic and Computer Engineering

9


PP 4.5: Use superposition to find I .

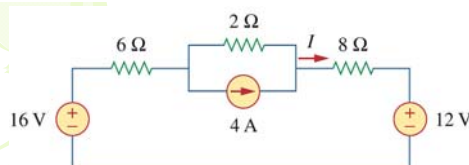


$$I = I_{16V} + I_{12V} + I_{4A}$$

I_{16V} – current due to 16 V source
 I_{12V} – current due to 12 V source
 I_{4A} – current due to 4 A source

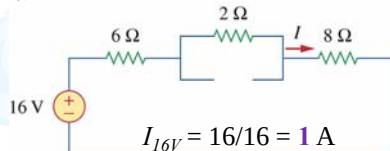
I_{16V} : Switch off the 4 A and 12 V sources



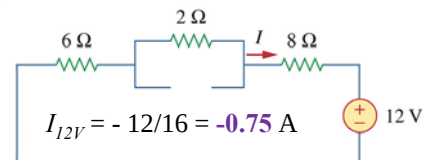I_{12V} : Switch off the 4 A and 16 V sources



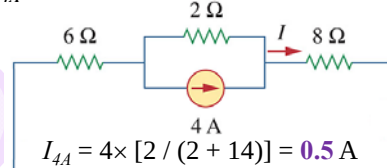I_{4A} : Switch off the 12 V and 16 V sources



$$\begin{aligned}
 I &= I_{16V} + I_{12V} + I_{4A} \\
 &= 1 + (-0.75) + 0.5 \\
 &= 0.75\text{ A}
 \end{aligned}$$






UNIVERSITEIT VAN PRETORIA
UNIVERSITY OF PRETORIA
YUNIBESITHI YA PRETORIA

Department of Electrical, Electronic and Computer Engineering

10

PP 4.4: Use superposition to find v_x .

$$v_x = v_{x20V} + v_{x4A}$$

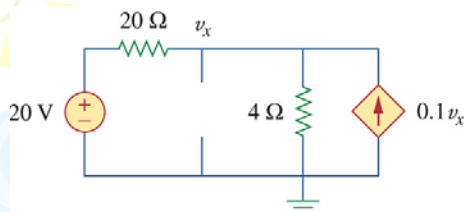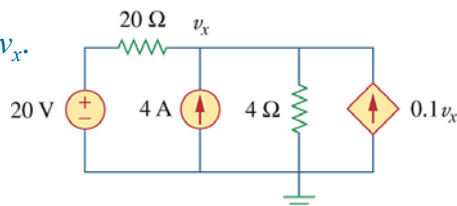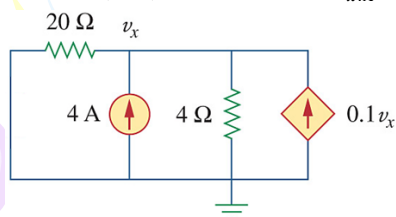Switch off (zero) the 4 A source: v_{x20V} Switch off (zero) the 20 V source: v_{x4A} **Nodal-analysis:**

$$\frac{v_{x20V} - 20}{20} + \frac{v_{x20V}}{4} - 0.1v_{x20V} = 0$$

$$v_{x20V} - 20 + 5v_{x20V} - 2v_{x20V} = 0$$

$$v_{x20V} = 5 \text{ V}$$

Nodal-analysis:

$$\frac{v_{x4A}}{20} - 4 + \frac{v_{x4A}}{4} - 0.1v_{x4A} = 0$$

$$v_{x4A} - 80 + 5v_{x4A} - 2v_{x4A} = 0$$

$$v_{x4A} = 20 \text{ V}$$

$$\text{Total: } v_x = v_{x20V} + v_{x4A} = 5 + 20 = 25 \text{ V}$$

UNIVERSITEIT VAN PRETORIA
UNIVERSITY OF PRETORIA
YUNIBESITHI YA PRETORIA

Department of Electrical, Electronic and Computer Engineering

11

Ch. 4 L# 2:

4.4 Source Transformations


- An equivalent circuit is one whose v - i characteristics are identical with the original circuit.
- It is the process of replacing a voltage source V_S in series with a resistor R by a current source I_S in parallel with a resistor R , or vice versa.

UNIVERSITEIT VAN PRETORIA
UNIVERSITY OF PRETORIA
YUNIBESITHI YA PRETORIA


Department of Electrical, Electronic and Computer Engineering

12

4.4 Source Transformation

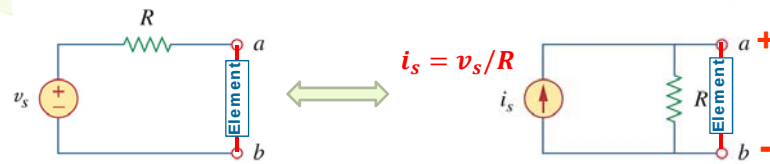

(a) Independent source transform

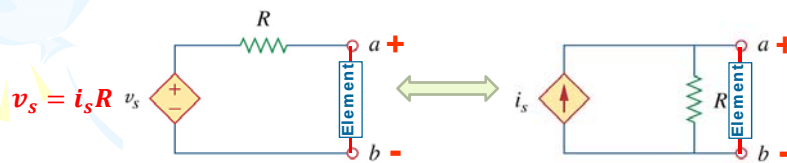


(b) Dependent source transform



Department of Electrical, Electronic and Computer Engineering

13

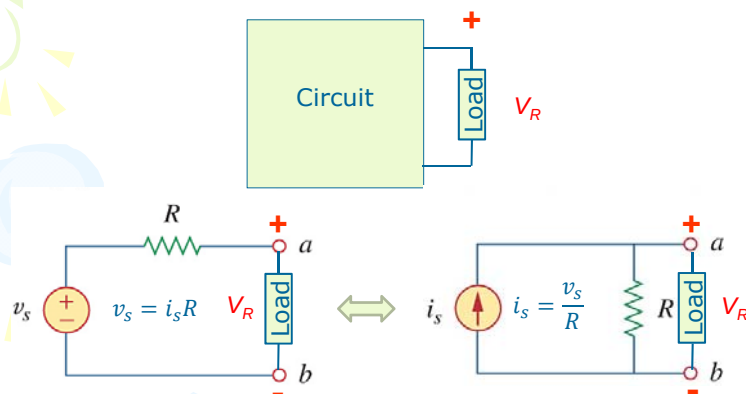4.4 Source Transformation From a Load's perspective





A load connected between terminals a - b will not know the difference. The load will see the same voltage and conduct the same current. (I.e. V_R is the same for both circuits.)



Department of Electrical, Electronic and Computer Engineering

14

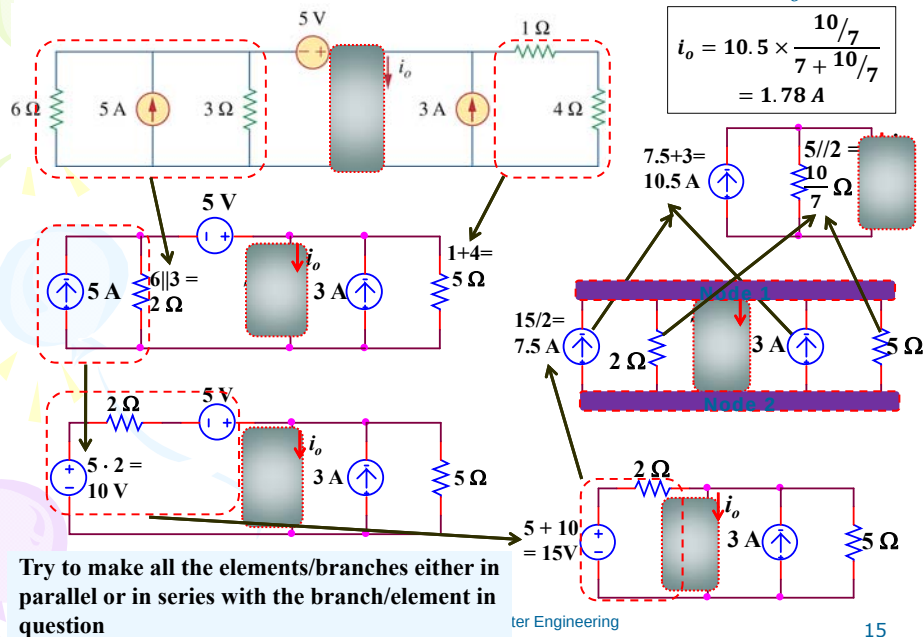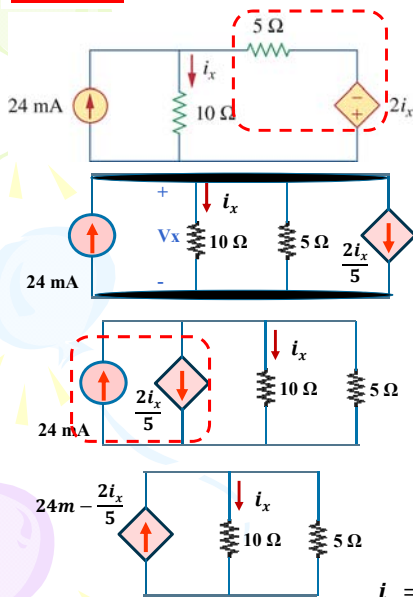PP 4.5: Use source transformation and determine i_o .**PP 4.7:** Use source transformation and determine i_x .

Very IMPORTANT:
Do NOT transform the part of the circuit with the unknown variable!

Method 2: Nodal Analysis
KCL: $-24 \text{ mA} + i_x + \frac{v_x}{5} + \frac{2i_x}{5} = 0$
but $v_x = 10i_x$
 $\therefore (\times 5): 5i_x + 10i_x + 2i_x = 120 \text{ m}$
 $\therefore i_x = 7.06 \text{ mA}$




UNIVERSITEIT VAN PRETORIA
UNIVERSITY OF PRETORIA
YUNIBESITHI YA PRETORIA

Department of Electrical, Electronic and Computer Engineering

16

Problem 4.24: Determine v_x .


Is it possible to make all the elements in single series loop?

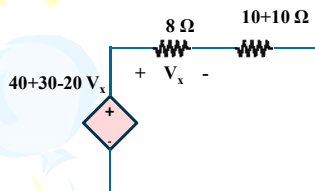

Method 2: Voltage Divider

$$v_x = \frac{8}{8 + 20} (70 - 20v_x)$$

$$\therefore v_x = 2.98 \text{ V}$$

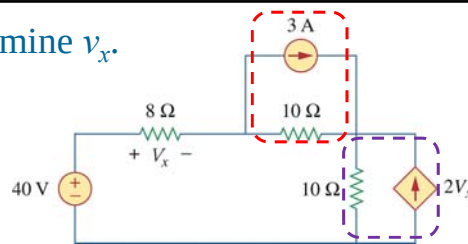

Method 1: KVL

$$-40 + v_x + 10i - 30 + 10i + 20v_x = 0$$

$$i = \frac{v_x}{8}$$

$$21v_x + 20 \frac{v_x}{8} = 70$$

$$\therefore v_x = 2.98 \text{ V}$$



UNIVERSITEIT VAN PRETORIA
UNIVERSITY OF PRETORIA
YUNIBESITHI YA PRETORIA

Department of Electrical, Electronic and Computer Engineering

17

Summary

Superposition

$$v = v_1 + v_2 + \dots + v_n$$

$$i = i_1 + i_2 + \dots + i_n$$


How do you turn off a source,
i.e. make it zero?

1. Independent sources:

Independent voltage sources are replaced by 0 V (short circuit ($R=0 \Omega$)).

Independent current sources are replaced by 0 A (open circuit ($R \rightarrow \infty \Omega$)).

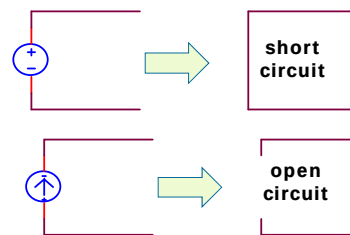
2. Dependent sources are left intact because they are controlled by circuit variables.



Source Transformation

Dependent source

$$v_s = i_s R$$

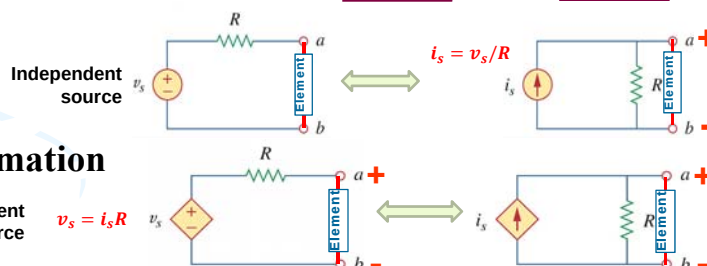

UNIVERSITEIT VAN PRETORIA
UNIVERSITY OF PRETORIA
YUNIBESITHI YA PRETORIA

Department of Electrical, Electronic and Computer Engineering

18


Ch. 4 L# 3:

4.5 Thevenin's Theorem

A linear two terminal circuit can be replaced by an equivalent circuit consisting of voltage source (V_{TH}) in series with a resistor (R_{TH}), where

- V_{TH} is the open-circuit voltage at the terminals
- R_{TH} is the equivalent resistance at the terminal when all independent sources are off

Terminals a-b are terminals between which you want to determine the Thevenins equivalent can be anywhere in the circuit.

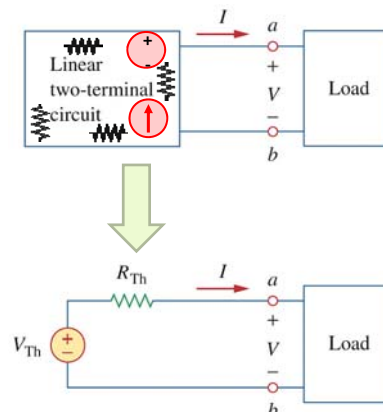

Case1: Circuit with **NO** dependant source

Case2: Circuit with dependant source



Department of Electrical, Electronic and Computer Engineering


19

Case1: Circuit with NO dependant source

How to determine V_{th} and R_{th}

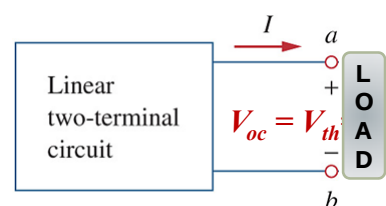
1. Calculating V_{TH} :

- Open-circuit, remove the element (load)
- Calculate the voltage drop (potential difference) across the terminal (node) of the element (load).



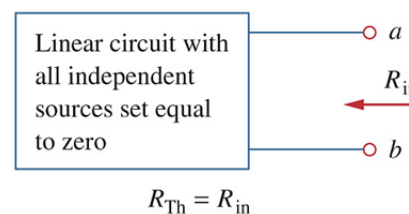2. Calculating R_{TH} :


- Switch off all independent sources
- Short-circuit the voltage source
- Open-circuit the current source
- Circuit should only have resistor
- Calculate the $R_{eq} = R_{TH} = R_{in}$



Department of Electrical, Electronic and Computer Engineering

20

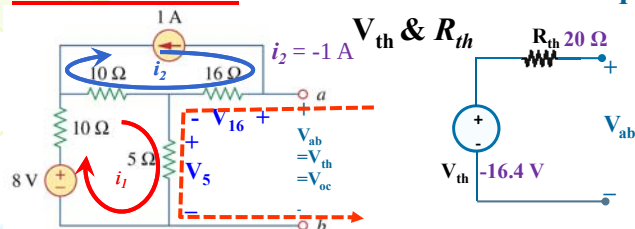Problem 4-39: Determine the Thevenin equivalent circuit.



Note: Circuit is already short circuited.
Or load is already removed

1. Calculating V_{TH} :

- Open-circuit, remove the element (load)
- Calculate the voltage drop (potential difference) across the terminal (node "ab") of the element (load).

$$V_{th} = V_{ab} = V_{16} + V_5$$

It is easier to use Mesh over Node

$$= 16 i_2 + 5 i_1$$

$$= 16 (-1) + 5 i_1$$

$$\text{Loop 1: } -8 + 10i_1 + 10(i_1 - i_2) + 5i_1 = 0$$


$$25i_1 = -2 \quad i_1 = -0.08 \text{ A}$$

$$V_{th} = 16 (-1) + 5 (-0.08)$$

$$V_{th} = -16.4 \text{ V}$$

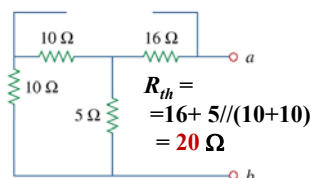2. Calculating R_{TH} :

- Switch off all independent sources
- Short-circuit the voltage source
- Open-circuit the current source
- Circuit should only have resistor
- Calculate the $R_{eq} = R_{TH} = R_{in}$




UNIVERSITEIT VAN PRETORIA
UNIVERSITY OF PRETORIA
YUNIBESITHI YA PRETORIA

Department of Electrical, Electronic and Computer Engineering

21

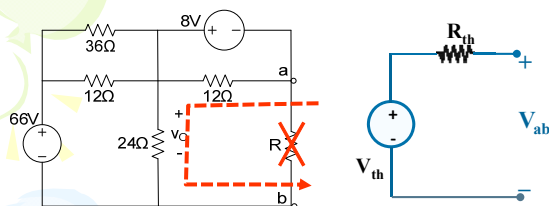Calculate the Thévenin equivalent resistance R_{TH} across load R (terminal a-b).



1. Calculating V_{TH} :

- Open-circuit, remove the element (load)
- Calculate the voltage drop (potential difference) across the terminal (node "ab") of the element (load).

$$V_{th} = V_{ab} = V_{12} + V_o$$

$$V_{12} = -8 \text{ V}$$


Vo using voltage divider

$$V_o = 66 \left(\frac{24}{24 + (36 || 12)} \right) = 48 \text{ V}$$

$$V_{th} = -8 + 48 = 40 \text{ V}$$

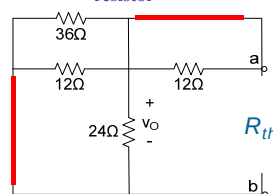2. Calculating R_{TH} :

- Short-circuit the voltage source
- Open-circuit the current source
- Circuit should only have resistor



$$R_{th} = (12 || 36 || 24) = 6.55 \Omega$$



UNIVERSITEIT VAN PRETORIA
UNIVERSITY OF PRETORIA
YUNIBESITHI YA PRETORIA

Department of Electrical, Electronic and Computer Engineering


22

Case2: Circuit with dependent source


- Calculating V_{TH} :
 - Same as that with Case1
- Calculating $R_{TH}=R_{eq}$:
 - Switch off all independent sources
 - Short-circuit the voltage source;
 - Open-circuit the current source
 - Circuit should only have resistors and dependant source.
 - With dependant source present, it is trivial to calculate R_{eq}
 - We excite the open-terminal with a voltage source (v_o) or current source (i_o)
 - Since the circuit is linear

$$R_{TH} = \frac{v_o}{i_o}$$

Exciting with voltage source

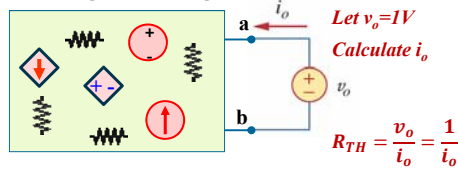


Exciting with current source

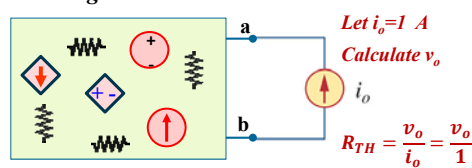

UNIVERSITEIT VAN PRETORIA
UNIVERSITY OF PRETORIA
YUNIBESITHI YA PRETORIA

Department of Electrical, Electronic and Computer Engineering

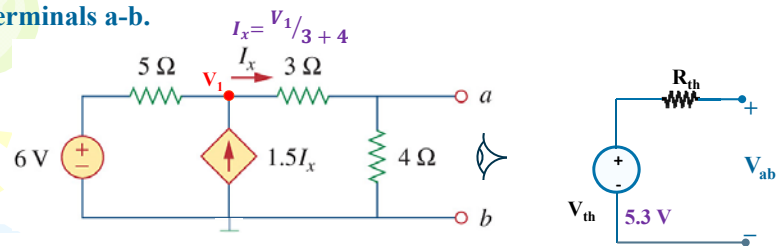PP 4-9: Determine the Thevenin equivalent circuit to the left of terminals a-b.



KCL@V1

$$i_{5\Omega} - 1.5 I_x + I_x = 0$$

$$i_{5\Omega} - 0.5 I_x = 0$$

$$\frac{V_1 - 6}{5} - 0.5 \frac{V_1}{3 + 4} = 0$$

Solve for V1

$$V_1 = 9.3 V$$

Using voltage divider

$$V_{th} = \frac{4}{7} V_1$$

$$= 9.3 \times \frac{4}{7} = 5.3V$$



UNIVERSITEIT VAN PRETORIA
UNIVERSITY OF PRETORIA
YUNIBESITHI YA PRETORIA

Department of Electrical, Electronic and Computer Engineering

PP 4-9: continued R_{th} : using CURRENT Test Source

Zero Ind. Sources

Excite using 1A current source

$$\therefore R_{th} = \frac{V_o}{I_{test}} = \frac{V_o}{1} = V_o$$

Calculate $V_{ab} = V_o$

KCL @ V_x

$$i_5 - 1.5I_x + I_3 = 0$$

$$\frac{V_x}{5} - 0.5I_x = 0$$

$$\frac{V_x}{5} - 0.5 \frac{V_x - V_o}{3} = 0$$

Simplify

$$0.5V_x + 2.5V_o = 0 \quad (2)$$

KCL @ V_o

$$i_{3\Omega} + i_{4\Omega} - 1 = 0$$

$$\frac{V_o - V_x}{3} + \frac{V_o}{4} - 1 = 0$$

Simplify

$$-4V_x + 7V_o = 12 \quad (1)$$

(1) + 8 x (2) :

$$27V_o = 12$$

$$V_o = 0.4 V$$

$R_{th} = 0.4 \Omega$

PP 4-9: continued R_{th} : using - VOLTAGE Test Source $R_{th} = 0.4 \Omega$

Zero Ind. Sources

Excite using 1V voltage source

$$R_{th} = \frac{V_{test}}{i_o} = \frac{1}{i_o}$$

Calculate i_o

KCL @ V_x

$$\frac{V_x}{5} - 1.5I_x + \frac{V_x - 1}{3} = 0$$

But: $I_x = \frac{V_x - 1}{3}$

$$\frac{V_x}{5} - 1.5 \frac{V_x - 1}{3} + \frac{V_x - 1}{3} = 0$$

Solve for V_x

$$\therefore V_x = -5 V$$

KCL @ V_o

$$\frac{1 - V_x}{3} - i_o + \frac{1}{4} = 0$$

$$4V_x + 12i_o = 7$$


$$4(-5) + 12i_o = 7$$

$$i_o = 2.25 A$$

$R_{th} = \frac{1}{2.25} = 0.4 \Omega$

P4.54: Find the Thevenin equivalent between terminal a-b

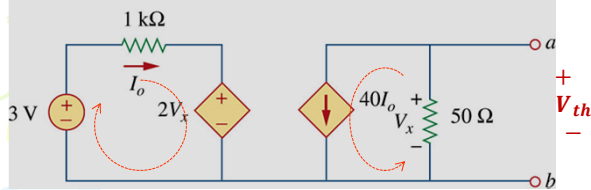Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



$$1000I_o + 2V_x - 3 = 0$$

$$V_x = V_{th} = -40I_o \times 50 \\ = -2000I_o$$

Solve for V_x

$$V_x = 2V$$




UNIVERSITEIT VAN PRETORIA
UNIVERSITY OF PRETORIA
YUNIBESITHI YA PRETORIA

Department of Electrical, Electronic and Computer Engineering

P4.54: R_{th}

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

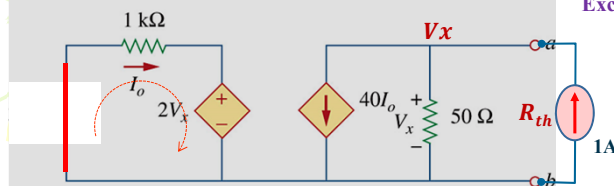Turn OFF all independent sources
Excite using 1A current source



$$1000I_o + 2V_x = 0 \quad (2)$$

Solve for V_x

$$V_x = -50/3V$$

$$R_{th} = -50/3 \Omega$$

$$R_{th} = \left(\frac{V_x}{1} \right) = V_x$$

KCL @ a

$$40I_o + \left(\frac{V_x}{50} \right) = 1$$


$$2000I_o + V_x = 50 \quad (1)$$



UNIVERSITEIT VAN PRETORIA
UNIVERSITY OF PRETORIA
YUNIBESITHI YA PRETORIA

Department of Electrical, Electronic and Computer Engineering

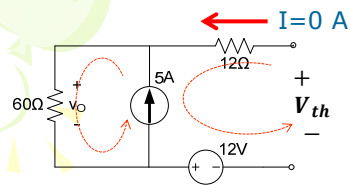Question: Determine the Thévenin equivalent.




$$V_{th} = V_{12\Omega} + V_{5A} + 12$$

$$\Rightarrow V_{12\Omega} = 0$$

$$V_{5A} = 60 \times 5 = 300 \text{ V}$$

$$V_{th} = 300 + 12 = 312 \text{ V}$$

Turn OFF all independent sources

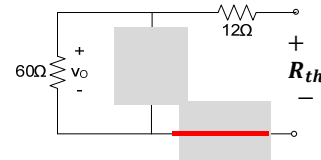

$$R_{th} = 12 + 60 = 72 \Omega$$




UNIVERSITEIT VAN PRETORIA
UNIVERSITY OF PRETORIA
YUNIBESITHI YA PRETORIA

Department of Electrical, Electronic and Computer Engineering

29


Ch. 4 L# 4: 4.6 Norton's Theorem

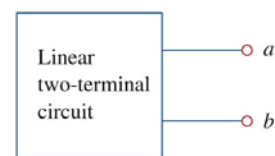It states that a linear two-terminal circuit can be replaced by an equivalent circuit of a current source I_N in parallel with a resistor R_N .



Where:

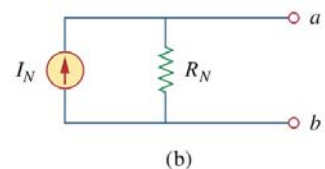- Terminals a-b are terminals between which you want to determine the Norton equivalent.
- Can be anywhere in the circuit.
- I_N is the short circuit current (i_{sc}) through the terminals.
- R_N is the input or equivalent resistance at the terminals when the independent sources are turned off. ($R_N = R_{th}$)




UNIVERSITEIT VAN PRETORIA
UNIVERSITY OF PRETORIA
YUNIBESITHI YA PRETORIA

Department of Electrical, Electronic and Computer Engineering


30

PP 4-11:

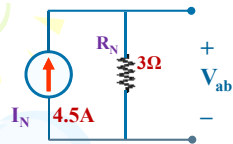
Determine the Norton equivalent circuit to the left of terminals a-b.




R_N: Zero ind. sources

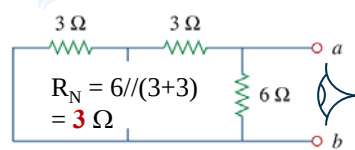

Case1: Circuit with NO dependant source

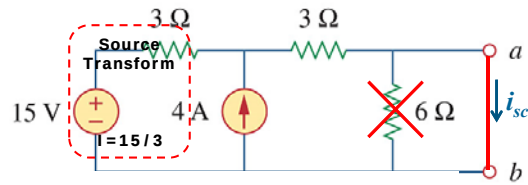

I_N: Calculate i_{sc} = I_N:

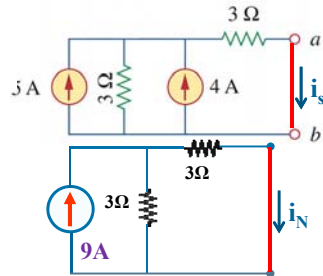

$$I_N = 9/2 = 4.5 \text{ A}$$




UNIVERSITEIT VAN PRETORIA
UNIVERSITY OF PRETORIA
YUNIBESITHI YA PRETORIA

Department of Electrical, Electronic and Computer Engineering

31


PP 4-12: Determine the Norton equivalent circuit.

Case2: Circuit with dependant source

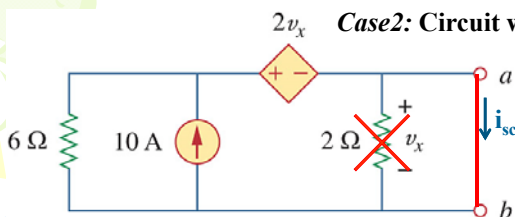

I_N: Calculate i_{sc} = I_N

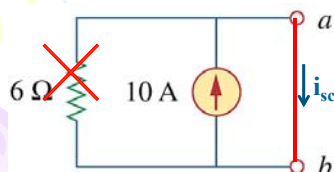Observe: SC makes $v_x = 0$ V and hence also $2v_x = 0$.



6 Ω shorted, hence no current through the 6 Ω:


$$i_{sc} = 10 \text{ A}$$



UNIVERSITEIT VAN PRETORIA
UNIVERSITY OF PRETORIA
YUNIBESITHI YA PRETORIA

Department of Electrical, Electronic and Computer Engineering

32

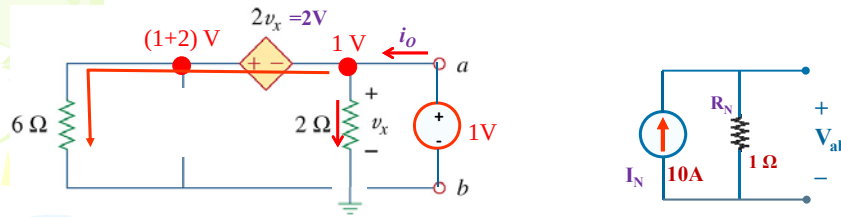PP 4-12: Determine the Norton equivalent circuit. R_N  **R_N : Using Nodal analysis**Zero Ind. Sources + **1V** Test Source

$$R_N = \frac{V_{test}}{i_o} = \frac{1}{i_o}$$

Calculate i_o

KCL @ 1V node:

$$i_o = i_{2\Omega} + i_{6\Omega}$$

$$i_o = \frac{1}{2} + \frac{1+2}{6} = 1 \text{ A}$$

$$= \frac{1}{1} = 1 \Omega$$


 R_N : Repeat using 1 A sourceUNIVERSITEIT VAN PRETORIA
UNIVERSITY OF PRETORIA
YUNIBESITHI YA PRETORIA

Department of Electrical, Electronic and Computer Engineering

33

Problem 4-51:

Determine the Norton equivalent circuit between terminals a-b.

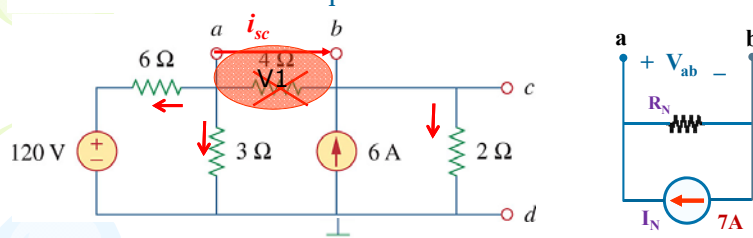Calculate $i_{sc} = I_N$ **Method #1: Nodal Analysis**

KCL @ V1:

$$i_6 + i_3 - 6 + i_2 = 0$$

$$\frac{V_1 - 120}{6} + \frac{V_1}{3} - 6 + \frac{V_1}{2} = 0$$

$$V_1 - 120 + 2V_1 - 36 + 3V_1 = 0$$

$$V_1 = 26 \text{ V}$$

KCL at node b:

$$-i_{sc} - 6 + i_2 = 0$$

$$-i_{sc} - 6 + \frac{V_1}{2} = 0$$

$$i_{sc} = I_N = -6 + \frac{26}{2} = 7 \text{ A}$$

or KCL at node a:


$$i_{sc} + i_6 + i_3 = 0$$

$$i_{sc} = -\frac{26 - 120}{6} - \frac{26}{3} = 7 \text{ A}$$


UNIVERSITEIT VAN PRETORIA
UNIVERSITY OF PRETORIA
YUNIBESITHI YA PRETORIA

Department of Electrical, Electronic and Computer Engineering

34


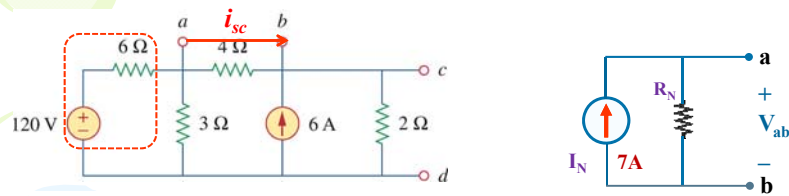
Problem 4-51: Method 2: I_N Calculate $i_{sc} = I_N$

Method #2: using Source Transformations

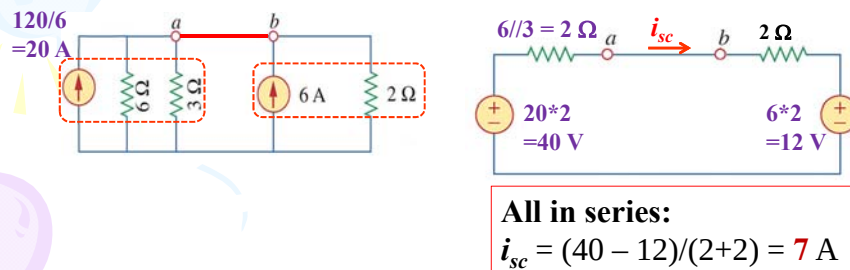UNIVERSITEIT VAN PRETORIA
UNIVERSITY OF PRETORIA
YUNIBESITHI YA PRETORIA

Department of Electrical, Electronic and Computer Engineering

35

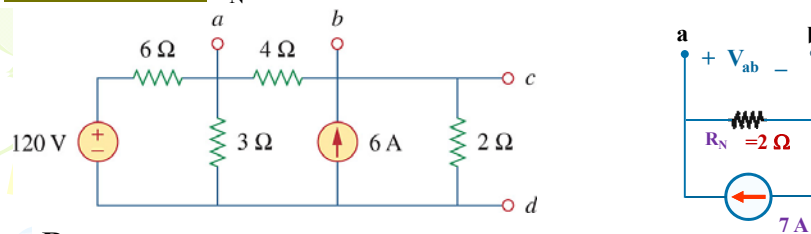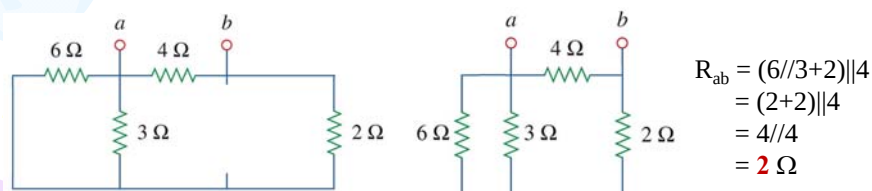
Problem 4-51: R_N  R_N : Zero Ind. SourcesUNIVERSITEIT VAN PRETORIA
UNIVERSITY OF PRETORIA
YUNIBESITHI YA PRETORIA

Department of Electrical, Electronic and Computer Engineering

36

4.6 Norton's Theorem

Norton vs Thevenin

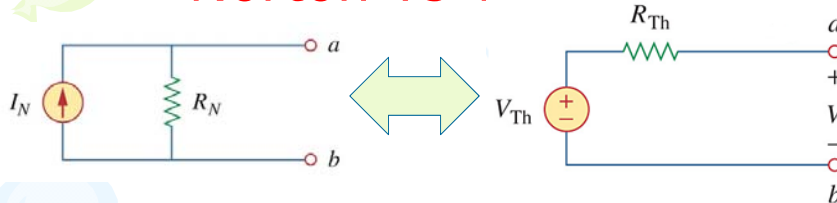

Norton equivalent = Source transformation of the Thevenin equivalent and vice versa.

Where:

$$R_N = R_{th}$$

$$I_N = V_{th}/R_{th} = V_{th}/R_N$$

$$V_{th} = I_N R_{th} = I_N R_N$$



UNIVERSITEIT VAN PRETORIA
UNIVERSITY OF PRETORIA
YUNIBESITHI YA PRETORIA

Department of Electrical, Electronic and Computer Engineering

37

Ch. 4 L# 5:



4.8 Maximum Power Transfer

If the entire circuit is replaced by its Thevenin equivalent except for the load, the power delivered to the load is:

$$P = i^2 R_L = \left(\frac{V_{Th}}{R_{Th} + R_L} \right)^2 R_L$$

For maximum power dissipated in R_L , P_{max} , for a given R_{Th} and V_{Th} :
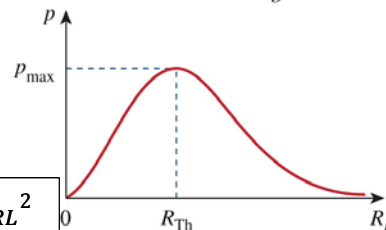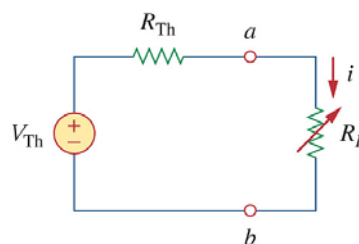
$$R_L = R_{th} \rightarrow P_{max} = \frac{V_{th}^2}{4R_{th}} = \frac{V_{RL}^2}{4R_L}$$



The power transfer profile with different R_L

38





UNIVERSITEIT VAN PRETORIA
UNIVERSITY OF PRETORIA
YUNIBESITHI YA PRETORIA


Department of Electrical, Electronic and Computer Engineering

Ex 4-13: Determine R_L for maximum power transfer as well as what P_{max} will be.

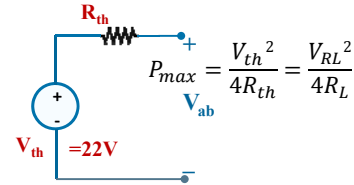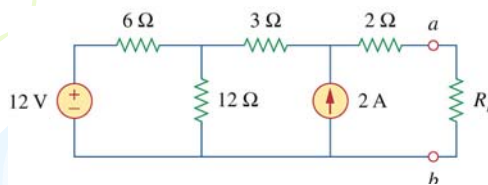Method: Determine the Thevenin equivalents: V_{th} and R_{th} between nodes "a-b"




V_{th} : using Super position:

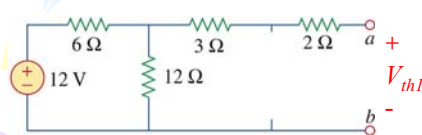

$$V_{th1} = V_{12\Omega} = 12 \text{ V} \times 12 / (6 + 12) = 8 \text{ V}$$

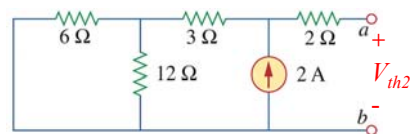NO voltage drop across 3Ω and 2Ω resistor.



$$V_{th2} = I \times R_{eq} = 2 \text{ A} \times ((6 // 12) + 3) = 2 \times (4 + 3) = 14 \text{ V}$$

$$\therefore V_{th} = V_{th1} + V_{th2} = 8 + 14 = 22 \text{ V}$$






UNIVERSITEIT VAN PRETORIA
UNIVERSITY OF PRETORIA
YUNIBESITHI YA PRETORIA


Department of Electrical, Electronic and Computer Engineering

39

Ex 4-13: R_{th} : Zeroing of sources:

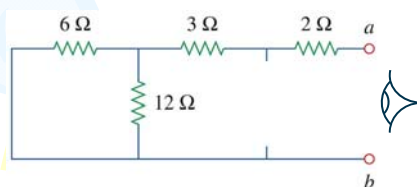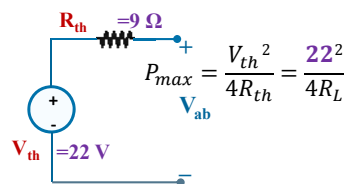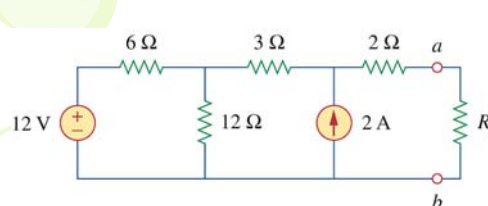
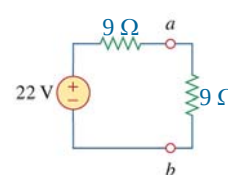
$$R_{th} = 6 // 12 + 3 + 2 = 9 \Omega = R_L$$




$$P_{max} = \frac{22^2}{4 \times 9} = 13.44 \text{ W}$$



UNIVERSITEIT VAN PRETORIA
UNIVERSITY OF PRETORIA
YUNIBESITHI YA PRETORIA

Department of Electrical, Electronic and Computer Engineering

40

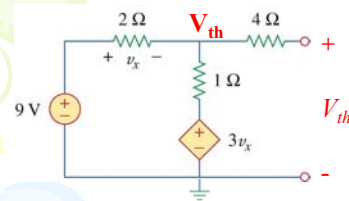PP4-13: Determine R_L for maximum power transfer as well as P_{max} 

$$v_x = 9 - V_{th}$$


$$\text{KCL@}V_{th} \quad \frac{V_{th} - 9}{2} + \frac{V_{th} - 3v_x}{1} = 0$$

$$\frac{V_{th} - 9}{2} + \frac{V_{th} - 3(9 - V_{th})}{1} = 0$$

$$V_{th} - 9 + 2(V_{th} - 27 + 3V_{th}) = 0$$



$$V_{th} + 2V_{th} + 6V_{th} = 9 + 54$$

$$V_{th} = 63/9 = 7 \text{ V}$$

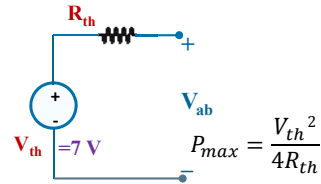UNIVERSITEIT VAN PRETORIA
UNIVERSITY OF PRETORIA
YUNIBESITHI YA PRETORIA

Department of Electrical, Electronic and Computer Engineering

41

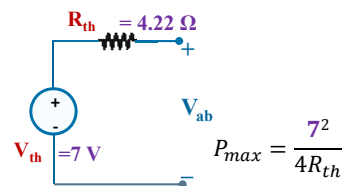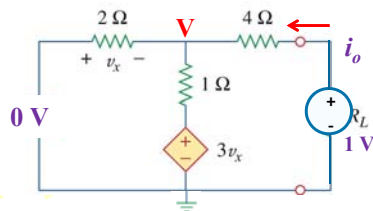PP4-13: R_{th} & P_{max}  **R_{th} :** Zero 9V & Excite using 1V test source

Nodal: KCL@ V

$$i_2 + i_1 + i_4 = 0$$

$$v_x = -V$$

$$\times 4 \left\{ \frac{V}{2} + \frac{V - 3v_x}{1} + \frac{V - 1}{4} = 0 \right.$$

$$2V + 4(V - 3(-V)) + (V - 1) = 0$$

$$2V + 16V + V = 1$$

$$V = 1/19$$

$$i_o = \frac{1 - V}{4} = 0.237 \text{ A}$$

$$R_{th} = R_L = \frac{v_{test}}{i_o} = \frac{1}{0.237} = 4.22 \Omega$$

$$P_{max} = \frac{7^2}{4 \times 4.22} = 2.90 \text{ W}$$

UNIVERSITEIT VAN PRETORIA
UNIVERSITY OF PRETORIA
YUNIBESITHI YA PRETORIA

Department of Electrical, Electronic and Computer Engineering



42

Problem 4.66:

Determine the maximum power that can be delivered to resistor R .


Max power is delivered to R when $R=R_{th}$

R_{th} : Zero all source

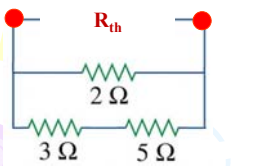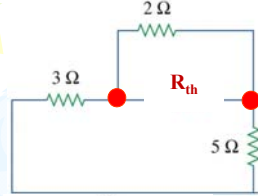

$$R_{th} = 2 \parallel (3+5) = 1.6 \Omega$$

$$P_{max} = \frac{V_{th}^2}{4R_{th}}$$

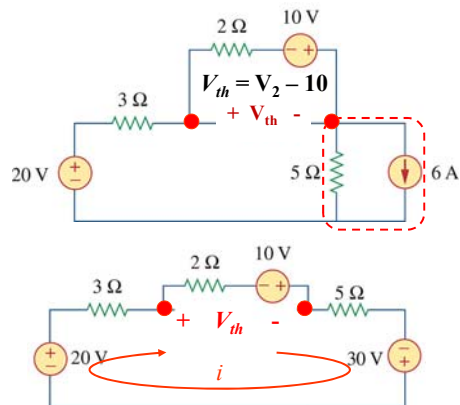

voltage divider

$$V_2 = \frac{2}{2+5+3}(20+10+30) = 12 \text{ V}$$

$$V_{th} = 12 - 10 = 2 \text{ V}$$

or

$$i = (20+10+30)/(3+2+5) = 6 \text{ A}$$

$$V_{th} = 2 \times 6 - 10 = 2 \text{ V}$$

$$P_{max} = \frac{2^2}{4 \times 1.6} = 0.625 \text{ W}$$



UNIVERSITEIT VAN PRETORIA
UNIVERSITY OF PRETORIA
YUNIBESITHI YA PRETORIA

Department of Electrical, Electronic and Computer Engineering

43

Additional problems




UNIVERSITEIT VAN PRETORIA
UNIVERSITY OF PRETORIA
YUNIBESITHI YA PRETORIA

Department of Electrical, Electronic and Computer Engineering

44

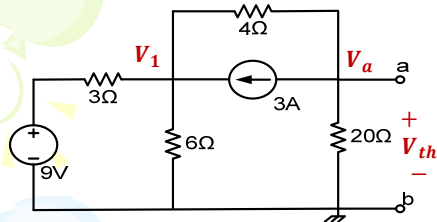Question: Determine V_{th} and R_{th} across terminal a-b?



KCL @ V_1

$$i_3 + i_3 + i_4 = 3$$

$$\frac{V_1 - 9}{3} + \frac{V_1}{6} + \frac{V_1 - V_a}{4} = 0$$

$$9V_1 - 3V_a = 72 \quad (2)$$

Solve (1) & (2)

$$V_{th} = -4.62 \text{ V}$$

$$V_{th} = V_{20}$$

KCL @ V_a

$$i_{20} + 3 + i_4 = 0$$

$$\frac{V_a}{20} + 3 + \frac{V_a - V_1}{4} = 0$$


$$6V_a - 5V_1 = -60 \quad (1)$$



Department of Electrical, Electronic and Computer Engineering

45

Question: R_{th}

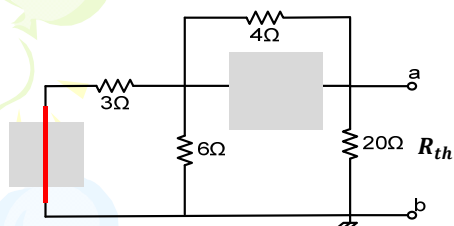

Turn OFF all independent sources

$$R_{th} = (3 || 6 + 4) || 20$$

$$= (2 + 4) || 20$$

$$= 6 || 20$$


$$= 4.62 \Omega$$



Department of Electrical, Electronic and Computer Engineering

46

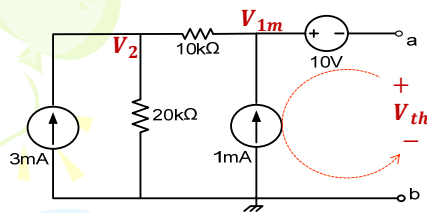Question: Calculate V_{th} and R_{th} across terminal a-b?



$$V_{th} = -10 + V_{1m}$$

KCL @ V_1

$$-1m + \frac{V_{1m} - V_2}{10k} = 0$$

$$V_{1m} - V_2 = 10 \quad (1)$$

KCL @ V_2


$$\frac{V_2 - V_{1m}}{10k} + \frac{V_2}{20k} - 3m = 0$$

$$-2V_{1m} + 3V_2 = 6 \quad (2)$$

Solve for V_{1m}

$$V_{1m} = 36 \text{ V}; \quad V_2 = 26 \text{ V}$$

$$V_{th} = -10 + 36 = 26 \text{ V}$$

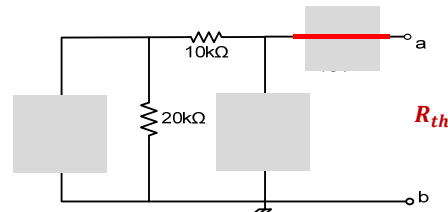

Turn OFF all independent sources

$$R_{th} = 10k + 20k = 30 \text{ k}\Omega$$




UNIVERSITEIT VAN PRETORIA
UNIVERSITY OF PRETORIA
YUNIBESITHI YA PRETORIA

Department of Electrical, Electronic and Computer Engineering

47

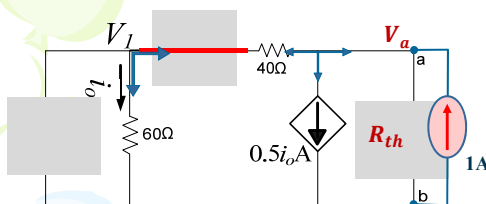Question: Find the Thévenin equivalent R_{TH} with respect to terminals a-b.



Remove the load between "ab"
Turn OFF all independent sources
Excite using 1A current source

$$R_{th} = \left(\frac{V_a}{1}\right) = V_a \quad R_{th} = 66.67 \Omega$$

KCL @ a

$$0.5i_o + \left(\frac{V_a - V_1}{40}\right) = 1 \quad (1)$$

$$i_o = \frac{V_1}{60} \quad (2)$$

KCL @ V_1

$$\frac{V_1}{60} + \left(\frac{V_1 - V_a}{40}\right) = 0 \quad (3)$$

Solve for V_a

$$V_a = 66.67 \text{ V}$$




UNIVERSITEIT VAN PRETORIA
UNIVERSITY OF PRETORIA
YUNIBESITHI YA PRETORIA

Department of Electrical, Electronic and Computer Engineering

48

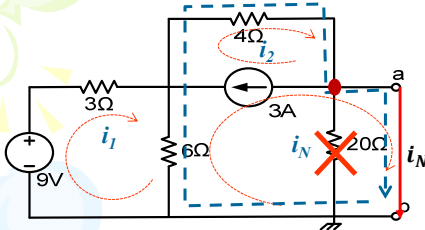Question: Determine the Norton current i_N for the circuit across terminal a-b?



KLC@ i1

$$-9 + 3i_1 + 6i_1 - 6i_N = 0$$

$$9i_1 - 6i_N = 9 \quad (1)$$

KLC@ SM

$$4i_2 + 6i_N - 6i_1 = 0 \quad (2)$$

KLC@ CS

$$-i_2 + 3 + i_N = 0$$

$$-i_2 + i_N = -3 \quad (3)$$

Solve for i_N

$$i_N = -1 \text{ A}$$