
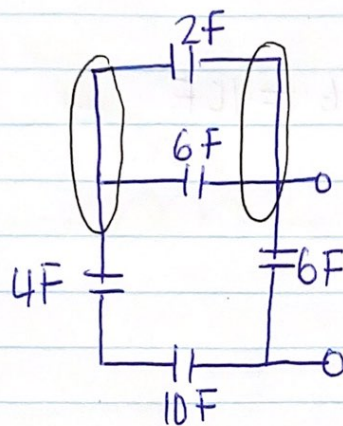


Chapter 6: Capacitance and Inductance

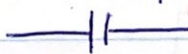


$C = \text{Capacitor (F)}$
 $\rightarrow \text{SI unit}$

$L = \text{Inductor (H)}$
 $\rightarrow \text{SI unit}$

Note: When capacitors are in series, use the parallel method to add them


When capacitors are in parallel, use the series method to add them.

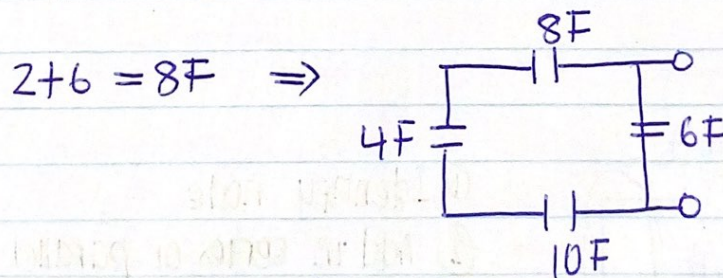Using the circuit above, Calculate equivalent Capacitance (C_{eq})




$$\Rightarrow \left(\frac{1}{8} + \frac{1}{4} + \frac{1}{10} \right)^{-1} = \frac{40}{19} F$$

$\Rightarrow$

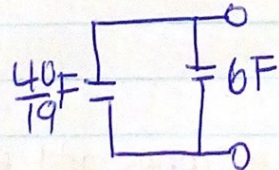

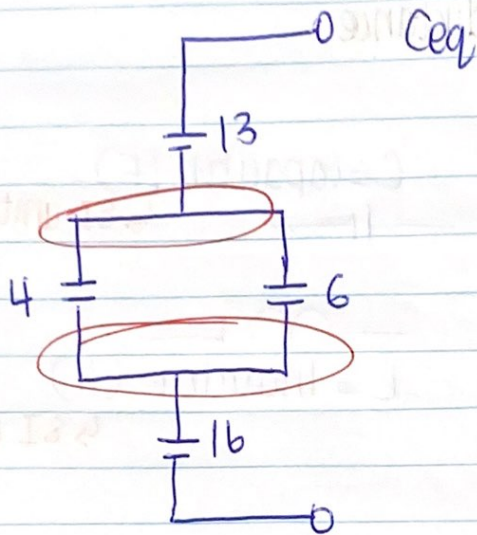
$$\Rightarrow \frac{40}{19} + 6 = \frac{154}{9} F$$



$$4+6 = 10F$$

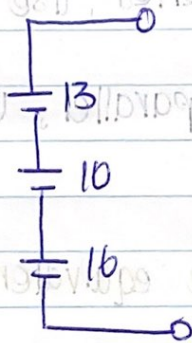⇒ Note: When capacitors are in series, use the formula




$$\left(\frac{1}{13} + \frac{1}{10} + \frac{1}{16} \right)^{-1} = \text{New Capacitor}$$

Method to add them.

Find the circuit above, calculate equivalent capacitance.

Inductors

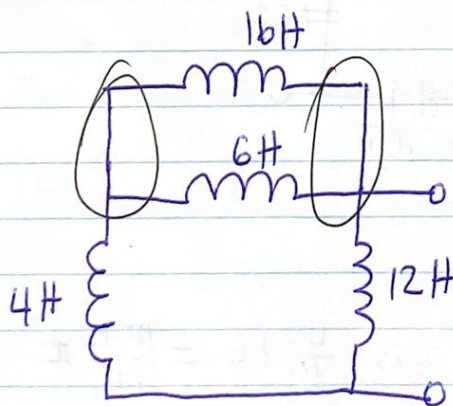

① Identify node


② Add in series or parallel

Note: When inductors are in series, add them in series


When inductors are in parallel, add them in parallel

Calculate I_{eq}
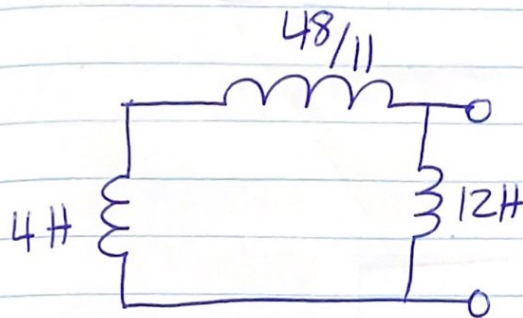
$$\left(\frac{1}{16} + \frac{1}{6}\right)^{-1} = \frac{48}{11}$$





$$\frac{48}{11} + 12 = \frac{92}{11}$$

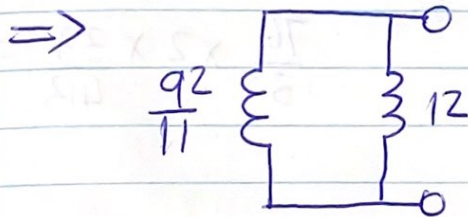

$$\frac{92}{11} + 12 = \frac{224}{11}$$

Example 2

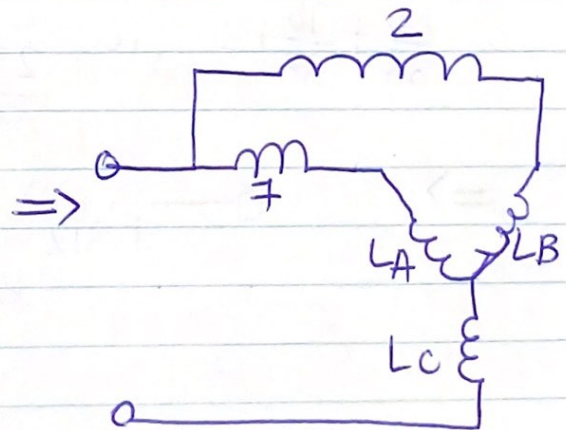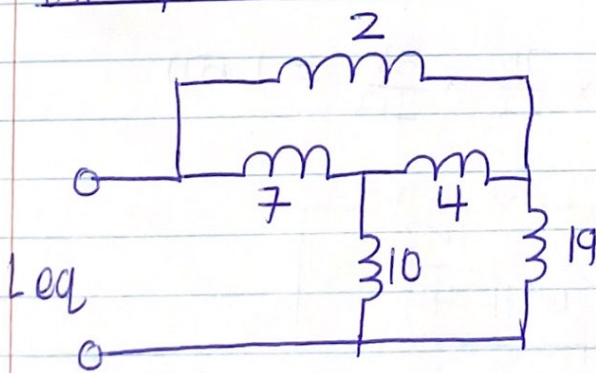


$$L_A = \frac{4 \times 10}{4 + 10 + 19} = \frac{40}{33}$$

$$L_B = \frac{4 \times 19}{4 + 10 + 19} = \frac{76}{33}$$


$$L_C = \frac{10 \times 19}{4 + 10 + 19} = \frac{190}{33}$$

⇒

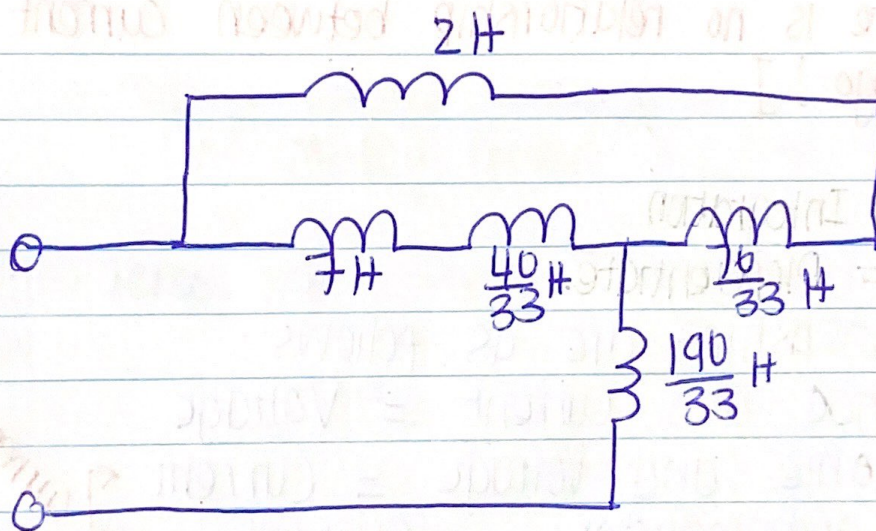


$$7 + \frac{40}{33} = 8.212 \quad \Bigg| \quad \frac{76}{33} + 2 = 4.303$$


⇒

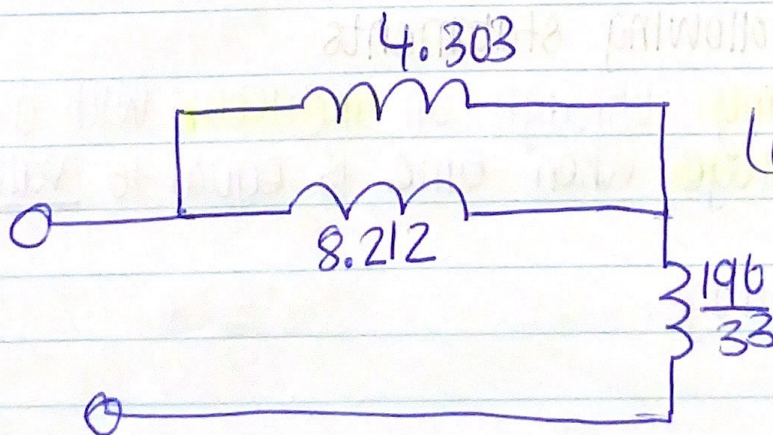
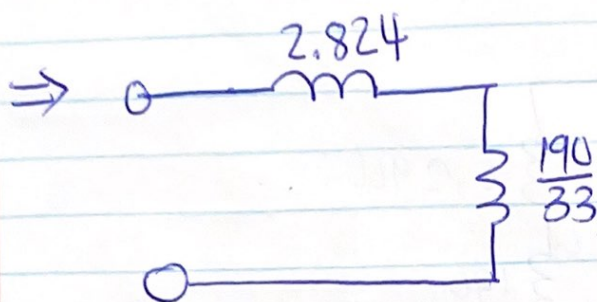
$$\left(\frac{1}{4.303} + \frac{1}{8.212} \right)^{-1} = 2.824 H$$


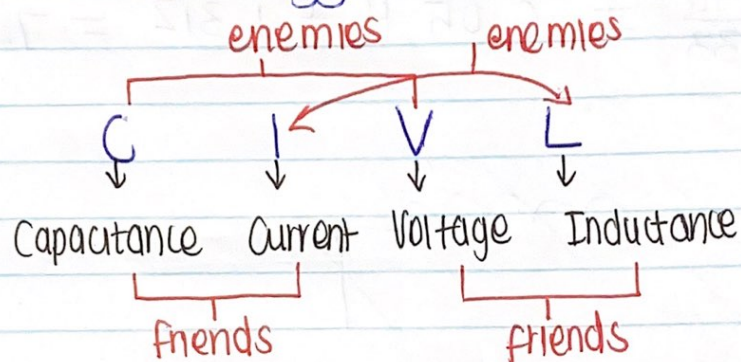
$$2.824 + \frac{190}{33} = 8.58 \text{ H.}$$



[NB: There is no relationship between current and voltage!]

Friends = Integration

Enemies = Differentiate.

The relationships are as follows:

1. Capacitance and Current = Voltage
2. Capacitance and Voltage = Current
3. Voltage and Inductor = Current
4. Current and Inductor = Voltage.

Given the following statements

- ① Current passing through an inductor with a given value.
Calculate voltage when time is equal to value.

Given.

I } Find Voltage.
 L

→ Voltage with respect to or as a function of time
 $\therefore V(t) = L \frac{di(t)}{dt} \rightarrow \text{diff current} \rightarrow \text{time}$

② voltage across a capacitor

Given
 V

across means $\frac{1}{C} \int V(t) dt$

$\frac{C}{I} = ? \quad \therefore I(t) = C \frac{dV(t)}{dt} \rightarrow \text{diff Voltage} \rightarrow \text{time}$

③ Current passing through a capacitor between t_1 and t_2

Given:

$\frac{I}{C} = ? \quad \therefore V(t) = \left[\frac{1}{C} \int_{t_1}^{t_2} i(t) dt \right] + V(0)$

$V(0)$ = voltage when time is zero, value is usually given.

④ Voltage across an inductor between t_1 and t_2

Given

V
 L


$\therefore I(t) = \left[\frac{1}{L} \int_{t_1}^{t_2} V(t) dt \right] + I(0)$

$I = ?$

$I(0)$ = current when time is zero, value usually given.

Examples

1.

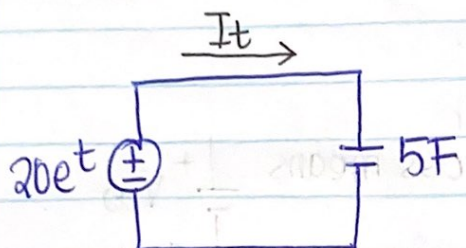

Calculate I_t .

Given
V and C


$$\Rightarrow I(t) = C \frac{dV}{dt}$$

time =

Use calculator.

$$I(t) = 164,87 \text{ A}$$

2.

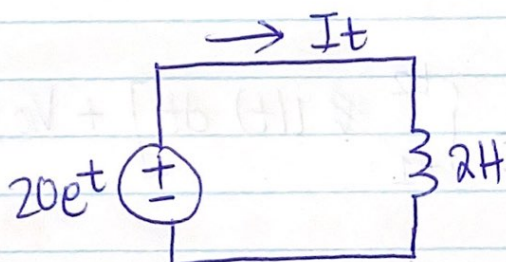

Calculate I_t


Given
V and L

$$I(t) = \left[\frac{1}{L} \int_{t_0}^{t_1} V(t) dt \right] + I(t)$$

$$= \left(\frac{1}{2} \int_0^{0.5} 20e^x dx \right) + 0 \quad \left. \vphantom{\int_0^{0.5}} \right\} \text{use calculator}$$

$$I(t) = 6,487 \text{ A}$$

3.

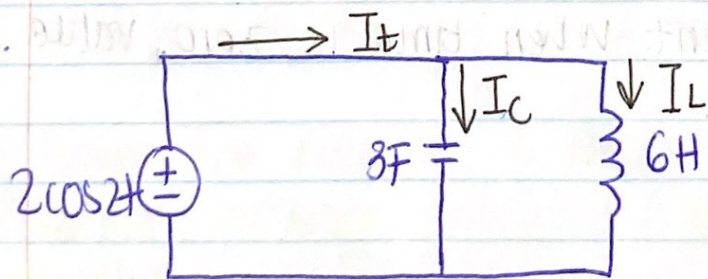

NB: set calculator to radians.

Shift $\rightarrow$ Mode $\rightarrow$ 4

$$I_t = I_C + I_L$$

$$I_o = 5 \text{ A}$$

$$I_n = I_{out}$$

Given

V and $C \Rightarrow$ find I_C

$$I_C = C \frac{dV_t}{dt}$$

$$\text{calculator} = 3 \left(\frac{d}{dx} 2 \cos(2x) \right) \Big|_{x=2}$$

$$I_C = \underline{9.08 \text{ A}}$$

Given

V and $L \Rightarrow$ find I_L .

$$I_L = \left(\frac{1}{L} \int_{t_0}^{t_1} V(t) dt \right) + I_{(0)}$$

$$\begin{aligned} \text{calculator} \Rightarrow &= \left(\frac{1}{6} \int_0^2 (2 \cos(2x)) \right) + 5 \\ &= \underline{4.87} \end{aligned}$$


$$\begin{aligned} \therefore I(t) &= I_C + I_L \\ &= 9.08 + 4.87 \\ &= \underline{13.96 \text{ A}} \end{aligned}$$

Example 4

Find $V_C(t)$ at $t = 2 \text{ sec}$, $V(0) = 0$

$$i_1 = 2e^{-4t}$$

$$i_2 = 8t$$

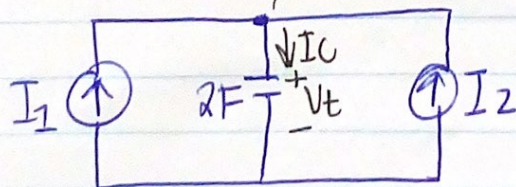

Given

$$\begin{aligned} I \text{ and } C \\ V_t = ? \end{aligned}$$

$$\begin{aligned} I_1 & \quad I_2 \\ & \downarrow I_C \\ \text{In} &= \text{Out} \end{aligned}$$

$$I_c = I_1 + I_2$$

$$I_c = 2e^{-4t} + 8t.$$

$$V_c(t) = \left[\frac{1}{C} \int_{t_0}^{t_1} I(t) dt \right] + V_0$$

$$= \left(\frac{1}{2} \int_0^2 (2e^{-4t} + 8t) \right) + 0$$

$$V_c(t) = \underline{8.25 \text{ V}} \rightarrow$$