

EBN

122

Chapter 1:

Basic Concepts:

1.2. Electric Charge: (C) $\rightarrow$ electric prop. of particles.

$$q(e^-) = +1.602 \times 10^{-19} C$$

$$1 C = \frac{1}{e} = 6.24 \times 10^{18} e^-$$

1. Units:

Mega	10^6	M
Kilo	10^3	k
Milli	10^{-3}	m
Micro	10^{-6}	μ
Nano	10^{-9}	n
Pico	10^{-12}	p


1.3. Current: (A)

$$i \triangleq \frac{dq}{dt} = \frac{\Delta q}{\Delta t}$$




* Can be the slope of a graph.

(charge) $Q = \int_{t_0}^t i dt.$

DC current:

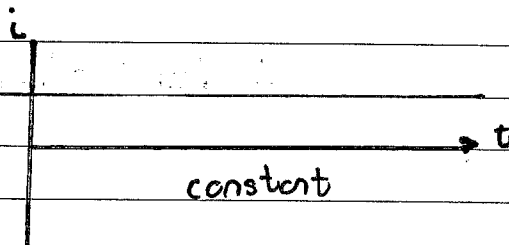

AC current:

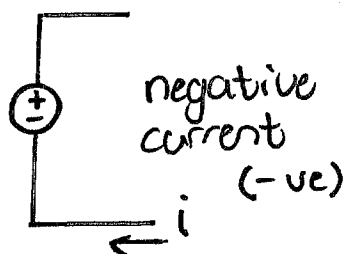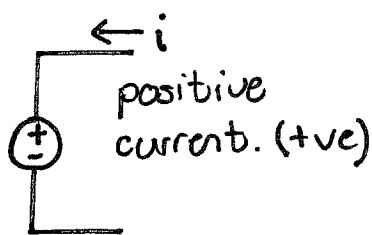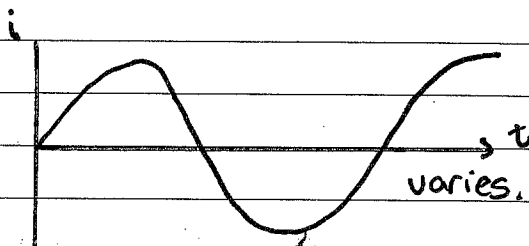

$\therefore$ With DC : $Q = i \times \Delta t.$

With AC : $Q = \int_{t_0}^t i dt.$

* Across a circuit
or over an
component.

1.4 Voltage: $\rightarrow$ energy required to move 1
unit of charge. (V)

- work is done by emf.

$w = \text{energy (J)}$

$q = \text{charge (C)}$

- $$V_{ab} = \frac{dw}{dq} = \frac{\Delta w}{\Delta q}$$

- $$V_{ab} = V_a - V_b$$

* $V_{ab} > 0$ potential of a $\uparrow$ potential
of b.

* $V_{ab} < 0$ potential of a $\downarrow$ potential
of b.

$$\therefore V_{ab} = -V_{ba}$$

Note: protons +
 $\therefore$ current
 charge +

Examples:

- ① Calc. amount of charge in 6 mil protons.

$$Q = (6 \times 10^6)(1.602 \times 10^{-19})$$

$$= 9.612 \times 10^{-13} \text{ C}$$

- ② A rechargeable battery delivers 60 mA for 18 h. How much charge can be delivered?

$$Q = \int_{t_0}^{t_i} I \, dt = I \Delta t.$$

$$t = 18 \times 60 \times 60 = 64800 \text{ s}$$

$$Q = (60 \times 10^{-3} \text{ A})(64800 \text{ s})$$

$$= 3888 \text{ C}$$

- ③ Given the total charge of a terminal
 $q = 10 - 10e^{-2t} \text{ mC}$
 find the current @ 1.0 s.

$$I = \frac{dq}{dt} \quad I = \frac{d}{dt} (10 - 10e^{-2t})$$

$$= 20e^{-2t} \text{ mA}$$

$$I(1) = 20e^{-2(1)} \text{ mA}$$

$$= 2.707 \text{ mA}$$

$$q = i \times t$$

④ The current through an element is represented by

$$i = \begin{cases} 4 \text{ A} & 0 < t < 1 \text{ from } 0 \rightarrow 2 \\ 4t^2 \text{ A} & t > 1 \end{cases}$$


$$Q = \int_{t_0}^{t_2} I dt.$$

$$Q = \int_0^1 4 A dt + \int_1^2 4t^2 A dt$$

$$= 4 + \left(\frac{4}{3} (2)^3 - \frac{4}{3} (1)^3 \right)$$

$$= 13.333 \text{ C}$$

⑤ The change in i through an element

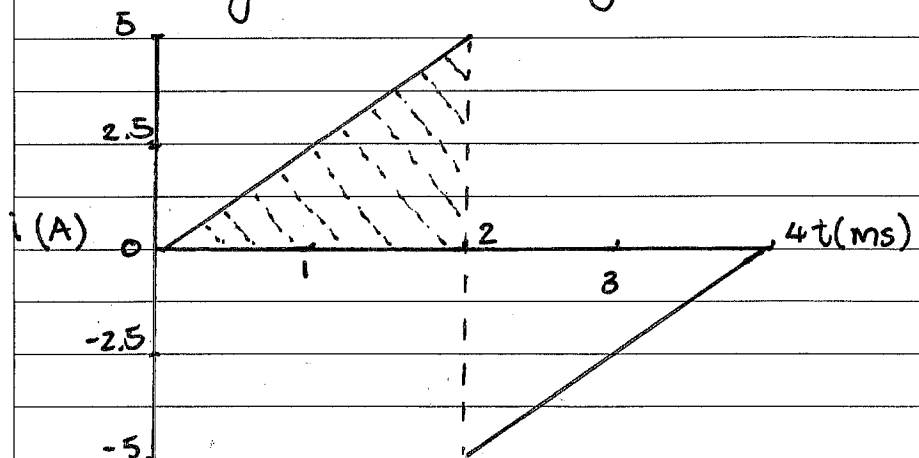

$$Q = \int_0^2 i dt$$

$$= \frac{1}{2} (2)(5)$$

$$= \underline{5 \text{ mC}} \rightarrow$$

Unit 1.5

* See where current is entering.

Power & Energy

↘ Rate at which (w) energy is consumed/delivered.

$$p = \frac{dw}{dt} = \frac{dw}{dq} \times \frac{dq}{dt} = v \cdot i$$

(a) DC system: $p(t) = P = VI$ - constant.

(b) AC system: $p(t) = v(t)i(t)$ - time function.

$$\left. \begin{array}{l} \sum p = 0 \\ \Rightarrow p_{\text{delivered}} = p_{\text{absorbed}} \end{array} \right\} \text{Conservation of energy.}$$

Energy: → Capacity to do work.

$$1 \text{ Wh} = 3600 \text{ J}$$

$$1 \text{ kWh} = 3.6 \text{ MJ}$$


•

$$w = \int_{t_0}^t p \, dt$$

Note: $p = v \cdot i$

• $w = \int_{t_0}^t v \cdot i \, dt$

Unit 1.6.

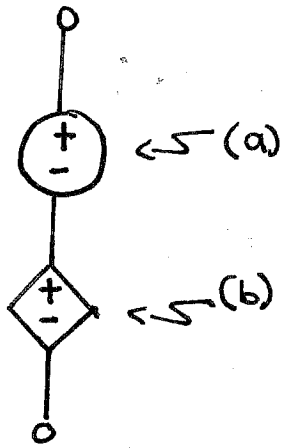

①

Circuit Elements:

Active elements (Energy sources)

2 Types:

Independent Source:

- Round


Dependant Source:

CCVS, VCCS, CCCS, VCVS

- Square.

②

Passive elements:

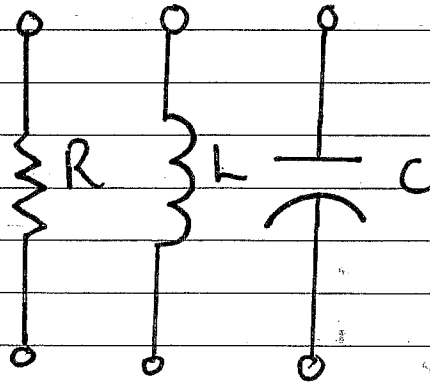



Resistors (R)

Inductors (L)

Capacitors (C)

Note:

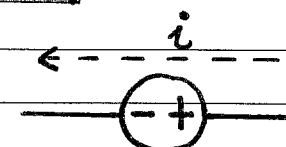①  Current from + to - then $p = +V \cdot i$

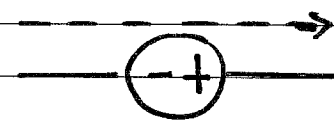②  Current from - to + then $p = -V \cdot i$

if $p < 0$ then supplied.
 $p > 0$ then absorbed.

1.5 & 1.6 Examples:

- ① To move a charge $q = 6\text{C}$ from $a \rightarrow b$ requires -30J : Find the Voltage drop. V_{ab} . $q = 6\text{C}$ $w = -30\text{J}$

$$V_{ab} = \frac{dw}{dq} = \frac{\Delta w}{\Delta q}$$

$$= \frac{-30}{6} = -5\text{V}$$

- ② Find the power delivered to an element at $t = 5\text{ms}$ if current entering is $i = 5 \cos 60\pi t \text{ A}$ & $v = 10 + 5 \int_0^t i \text{ dt}$ V

$$\Rightarrow v = 10 + 5 \int_{t_0}^t 5 \cos 60\pi t \text{ dt}$$

$$= 10 + \frac{5}{12\pi} (\sin 60\pi t)$$

*

$$p = +v \cdot i$$

$$p = \left\{ 5 \cos 60\pi (5 \times 10^{-3}) \right\} \left\{ 10 + \frac{5}{12\pi} (\sin 60\pi (5 \times 10^{-3})) \right\}$$

$$p = 29.7\text{W}$$

- ③ An element draws 15A when connected to a 240V line. How long will it take to consume 180kJ .

$$w = \int_{t_0}^t p \text{ dt} = p \Delta t$$


$$\Delta t = \frac{w}{p} = \frac{180\,000}{240 \times 15}$$

$$\Delta t = 50\text{s}$$

$$V = 240\text{V}$$

$$i = 15\text{A}$$

$$w = 180\,000\text{J}$$

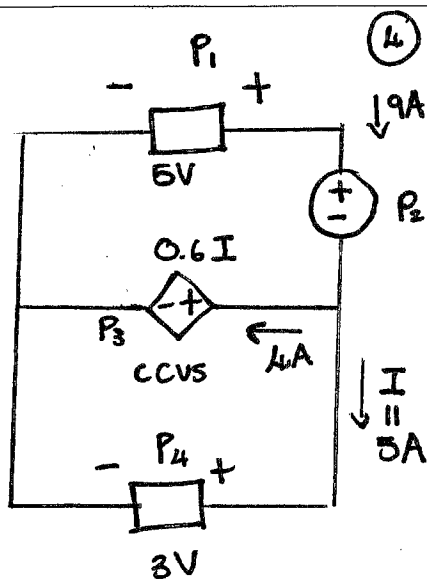

④ Calculate the power absorbed in each component.

$$p_1: P = -V \cdot i$$

$$= -45W \quad (\text{power supply})$$

$$p_2: P = V \cdot i$$

$$= 18W$$

$$p_3: V = 0.6(5) = 3V$$

$$P = 12W$$

$$p_4: P = V \cdot i$$

$$= 15W$$

$$t = 86400s$$

$$V = 5V$$

$$i = 1mA$$

⑤ A battery supplies a constant 1mA (DC) of 5V for 1 day. Determine the energy used.

$$p = V \cdot i$$

$$= 5 \times (1 \times 10^{-3})$$

$$= 5 \times 10^{-3} W$$

★

$$W = p \Delta t$$

$$W = (5 \times 10^{-3})(86400)$$

$$= 432J$$

Elec. cost: R5/kWh
 $p = 3kW$

⑥ A 3kW kettle needs 20s to boil 100ml of water. What is the cost of 1.5L of water to boil?

$$\text{Cost of 100 ml} : 3 \times 5 \times (20 \div 60 \div 60)$$

$$= R0,0833$$

$$\text{Cost of 1.5L} = \frac{0,0833}{100} \times 1500$$

$$= \underline{\underline{R 1.25}}$$

Chapter 2: Basic Laws:

Ohm's Law: (gradient of graph = IR) $\{V = I \times R\}$

$$\text{gradient} = \frac{\Delta V}{\Delta i}$$

$$\Rightarrow R = \frac{V}{I}$$


$$\frac{1}{R} = \frac{I}{V} = G \text{ (conductance)}$$

* The voltage across a resistor is directly prop. to the current I .


$$R = \rho \frac{\text{Length.}}{\text{Area}} = \Omega$$

ρ = resistivity.

Passive Sign Convention:

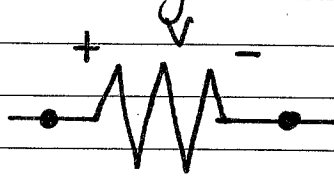



$$V = +iR$$

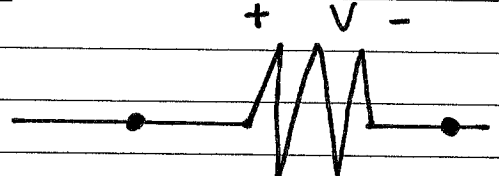

$$V = -iR$$


Resistance Extremes:

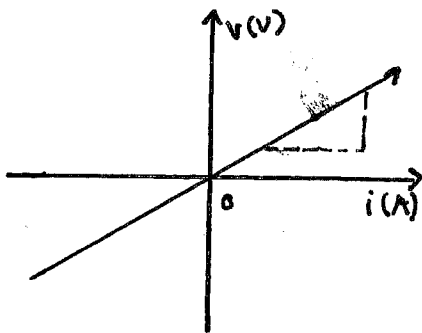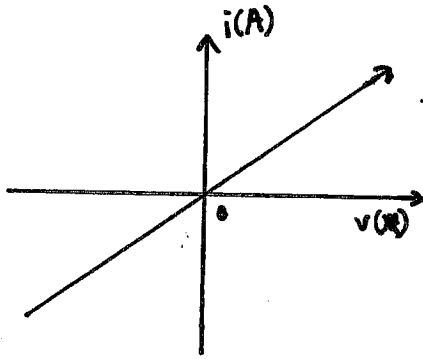$R = 0 \rightarrow$ short circuit $R = \infty \rightarrow$ Open circuit.



R depends on:

- Length
- Size
- Type.

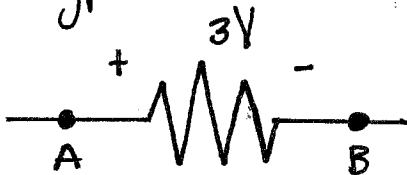

$$V_{ab} = 3V$$

$$V_{ba} = -3V.$$

Conductance:

$$G = \frac{1}{R} \quad [S] \quad R [\Omega]$$

$$i = G \cdot V$$

(2.2.)

Power dissipated in a Resistor:

$$\textcircled{1} P = V \cdot I \quad \textcircled{2} V = IR$$

Power: *

$$P = \frac{V^2}{R}$$


$$P = I^2 \times R.$$

$$\therefore \underline{\underline{R \geq 0}}$$

(2.3.)

Nodes, Branches & Loops

- ① Branch: A single element. (2 terminals). (5 Branches)
- ② Node: Point of connection between 2 or more branches. (3 Nodes)
- ③ Loops: Any closed path in a circuit. (3 Loops).
* Can't Cross on element twice.

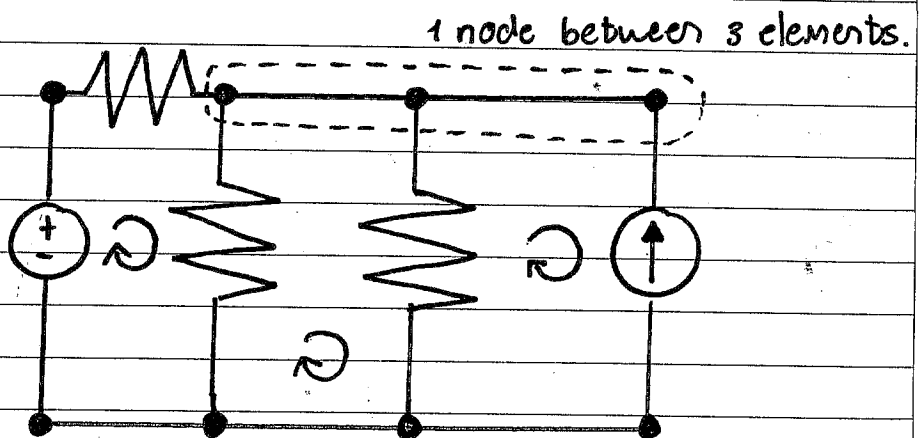Independent Loops:

A loop that contains at least 1 branch that is not part of any other independent loops.

$$b = l + n - 1$$

↓ Branches
 ↓ nodes.
 ↓ loops


Series el Parallel:

Kirchoff's Law:Current Law:KCL:

→ Algebraic sum of currents entering & exiting a node is equal to 0.
(or closed boundary).

Current in Parallel:

$$\sum_{n=1}^n i_n = 0.$$

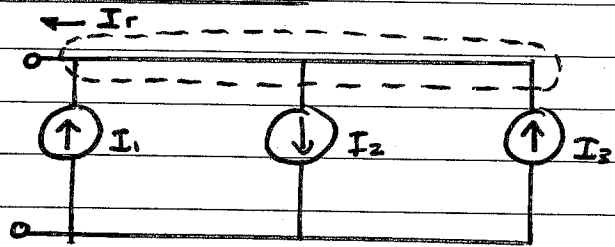

$$-I_r + I_1 - I_2 + I_3 = 0.$$

∴ Current sources can NOT be connected in series.

Voltage law:KVL:


→ Algebraic sum of voltages (analysed clockwise) will be = 0 (around a closed path).

∴ Voltage sources can NOT be connected in parallel.

$$KVL = \sum V_n = 0.$$

Note: create a point on the node & analyse current from that point.

• (enter a node +
exit a node -)

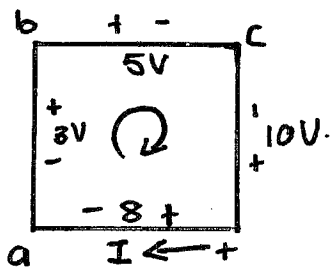


$$-3 + 5 - 10 + 8 = 0$$

• Enter - then
-V, Enter +
then +V.

Series Resistors & Voltage DivisionSeries:

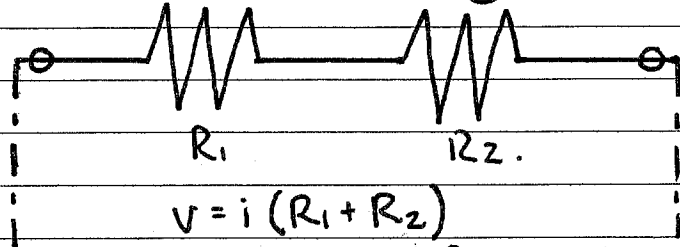- Two or more elements are in series if they are cascaded & carry the same current I .



$$R_{\text{equivalent}} = R_1 + R_2.$$

(2.5) Voltage Division: (resistors in series).

$$R = \frac{V}{I}$$

$$V = i R_{\text{eq.}} \Rightarrow i = \frac{V}{R_1 + R_2}.$$

$$\Rightarrow V_1 = \frac{V}{R_1 + R_2} \times R_1$$


$$V_2 = \frac{V}{R_1 + R_2} \times R_2$$

* Req for more than 2 R's:


$$R_{\text{eq}} = \sum_{n=1}^n R_n$$

$$\Rightarrow V_n = \frac{R_n}{\sum_{n=1}^n R_n} \times V.$$

voltage divided proportionally.

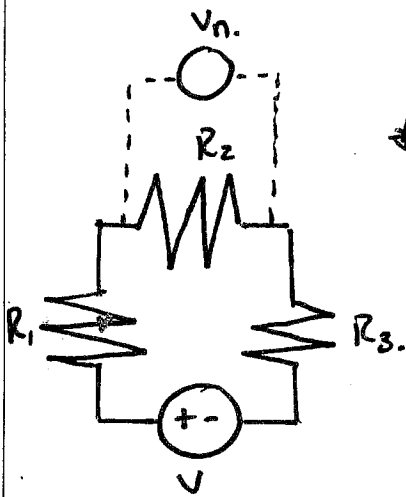

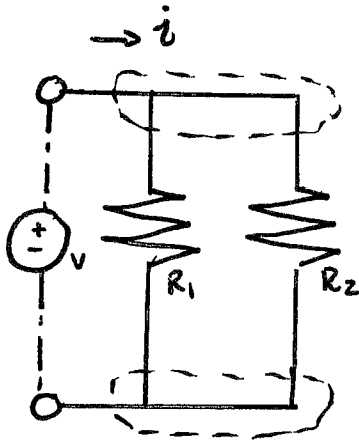(2.6) Parallel Resistors & Current Division.



Parallel:

- Two or more elements are in || if they connect to the same 2 nodes (Same Voltage across them).

$$i = \frac{V}{R_{eq.}}$$

$$i = i_1 + i_2.$$

$$i = V \times C_{eq.}$$

OIR

$$i = \frac{V}{R_1} + \frac{V}{R_2}$$

$$C_{eq.} = C_1 + C_2$$

$$C_{eq.} = \frac{1}{R_1} + \frac{1}{R_2}.$$

$$i = V \left(\frac{1}{R_1} + \frac{1}{R_2} \right)$$

*


$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} = \frac{R_2 + R_1}{R_2 \times R_1}.$$

(2.6) Current Division: (resistors in parallel).

$$i_n = \frac{C_n}{C_1 + C_2 + \dots + C_n} i$$


$$C_{eq.} = \sum_{n=1}^N C_n.$$

Voltage Division summary:

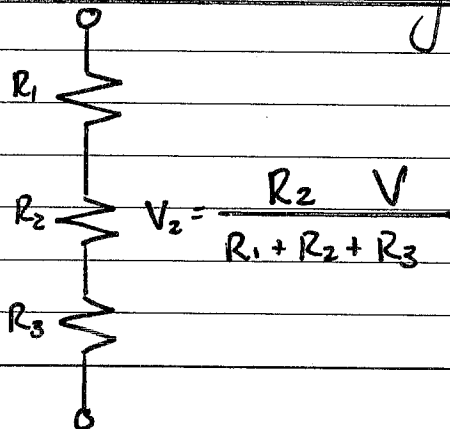


$$V_2 = \frac{R_2}{R_1 + R_2 + R_3} V$$

Current Division:

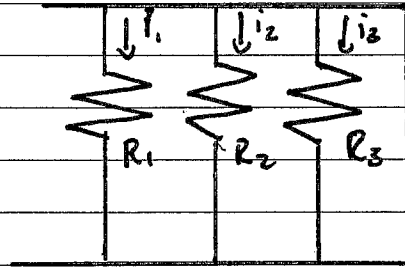


$$i_2 = \frac{G_2 i}{G_1 + G_2 + G_3}$$


Adding Resistors:

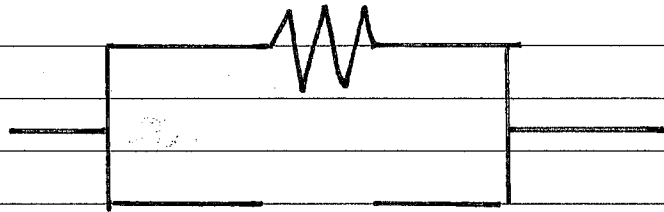

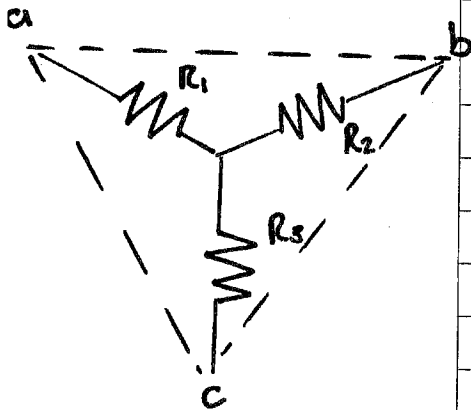
$$R_1 \parallel R_{\infty} = \left(\frac{1}{R_1} + \frac{1}{R_{\infty}} \right)^{-1}$$




Wye - * - T Network:

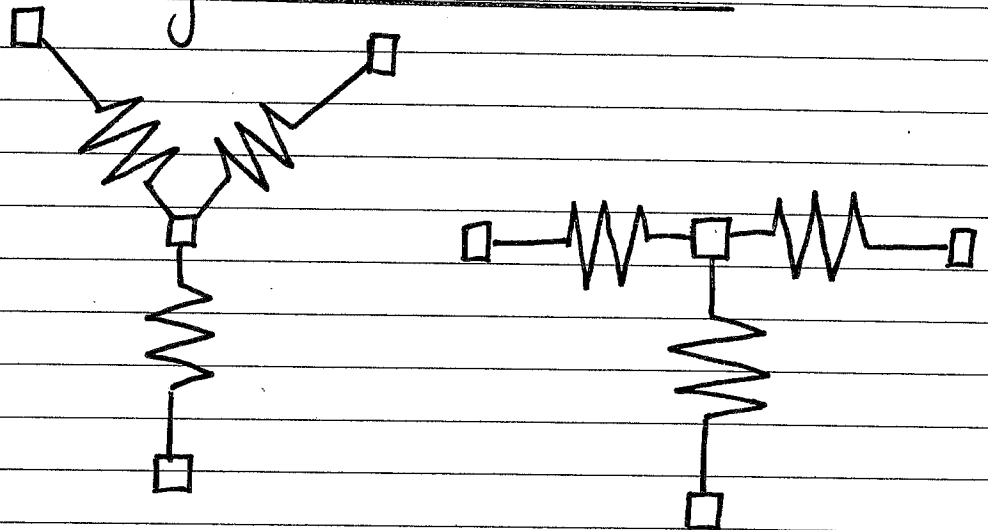

Delta or Pi network:

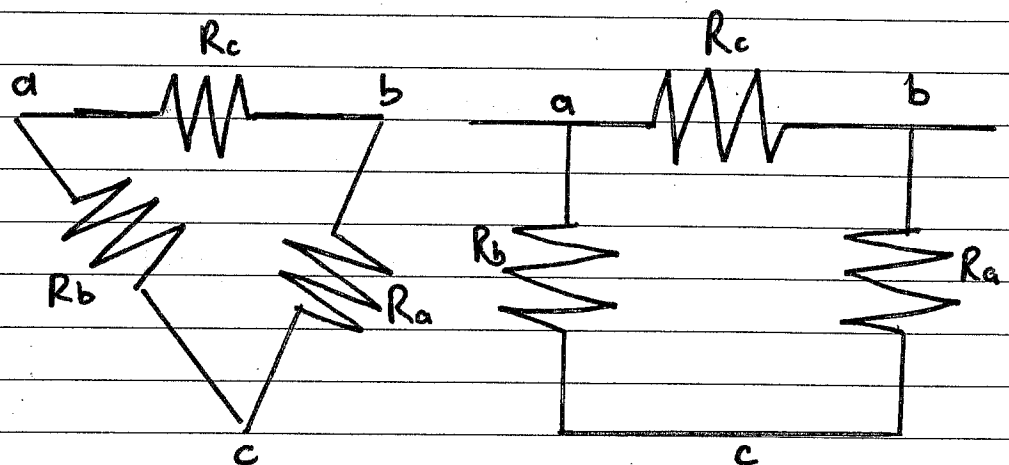

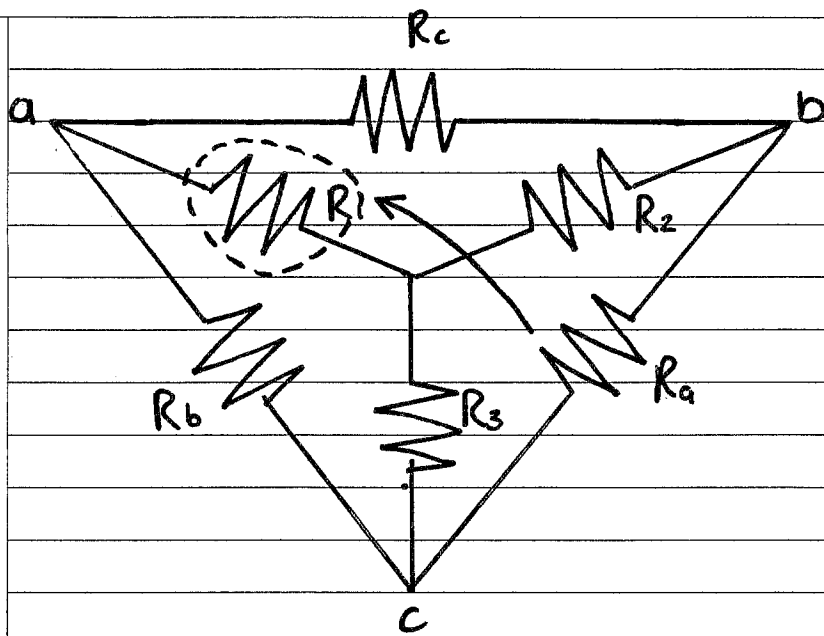Why? Sometimes resistors are not in $\parallel$ or series.



$$R_1 = \frac{R_b \times R_c}{R_a + R_b + R_c}$$

adjacent Δ -resistors.
 $\leftarrow \Sigma$ of Δ resistors.

$$R_2 = \frac{R_c \times R_a}{R_a + R_b + R_c}$$

$$R_a = \frac{R_1 R_2 + R_2 R_3 + R_1 R_3}{R_1}$$

* All multiples possible
 $\uparrow$
 opposite Y-resistor.

Chapter 3:3 Laws:

- KCL : Nodal Anal.
- KVL : Mesh.
- Ohm's Law.

Nodal Analysis:

KCL: Nodal Analysis.
(Voltage Node analysis)

KVL: Mesh Analysis.
(Current analysis)

Steps: (For analysing)
(Node Voltages).


1. Select: A ref. (ground) node.

2. Assign: Voltages to remaining "critical" nodes i.e. $V_1, V_2, V_3, V_4 \dots$

3. Apply KCL: To non-reference nodes.
(Ohm's Law)

4. Solve:

eg. 1.

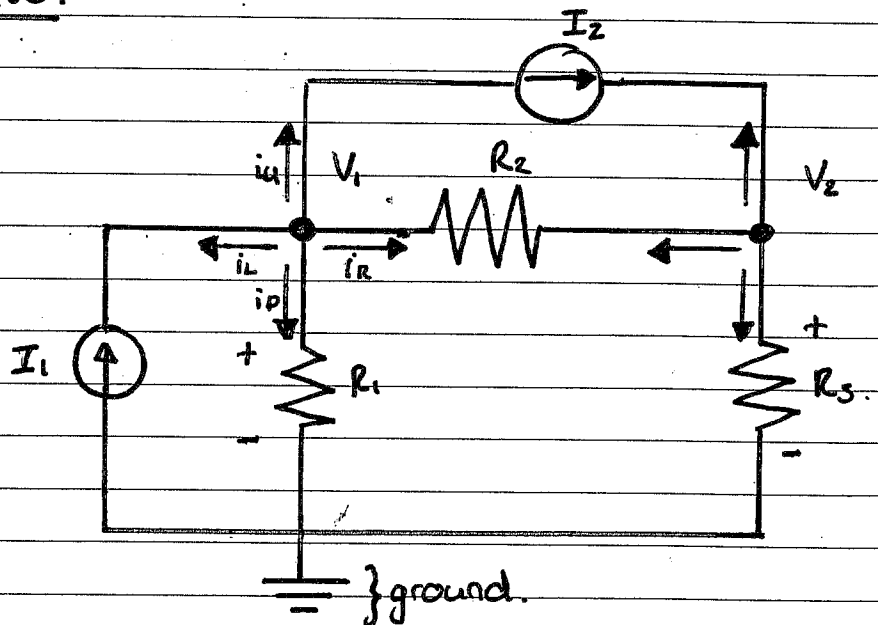

• Critical Node:

- * Node with more than 2 branches.

- Current OUT of node (unless CCS)

- Current flows from High to Low volt.


$$\therefore i = \frac{V_{\text{High}} - V_{\text{Low}}}{R_{\text{Branch}}}$$

$$\sum i_{(\text{node})} = 0.$$

Ref. Node: @ - terminal of Voltage source.

Analyse Node.

eg. 2.

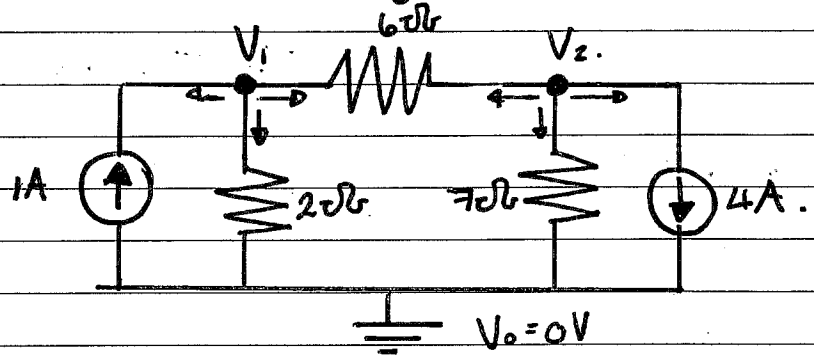

Method 1:

• Elimination:

$$\text{For } V_1: \quad +1A - \frac{V_1 - V_2}{6} - \frac{V_1 - 0}{2} = 0. \quad \left. \vphantom{\frac{V_1 - V_2}{6}} \right\} \times -6$$

$$-6 + V_1 - V_2 + 3V_1 = 0$$

$$\textcircled{1} \quad 4V_1 - V_2 = 6.$$

$$\text{For } V_2: \quad -4A - \frac{V_2 - V_0}{7} - \frac{V_2 - V_1}{6} = 0 \quad \left. \vphantom{\frac{V_2 - V_1}{6}} \right\} \times -42.$$

$$168 + 6V_2 + 7V_2 - 7V_1 = 0$$

$$\textcircled{2} \quad 13V_2 - 7V_1 = -168$$

$$\text{Solve: } V_2 = -14V$$

$$V_1 = -2V.$$

Method 2:

• Cramer's Rule:


(Find the Determinant) {WTW}

$$\textcircled{1} \quad 4V_1 - 1V_2 = 6$$

$$\textcircled{2} \quad 13V_2 - 7V_1 = -168.$$

$$V_1 = \frac{\Delta_1}{\Delta} = \frac{\begin{vmatrix} 6 & -1 \\ -168 & 13 \end{vmatrix}}{\begin{vmatrix} 4 & -1 \\ -7 & 13 \end{vmatrix}} = \frac{-90}{45} = -2V.$$

e.g. 3.

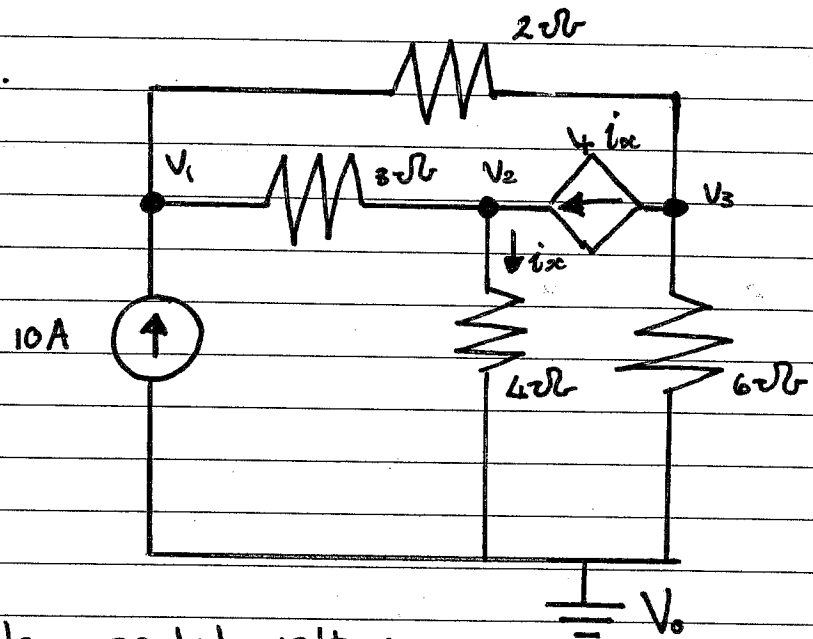

1. Calc. nodal voltages:

$$\textcircled{1} \text{ } V_1: \left. \begin{aligned} 10A - \frac{V_1 - V_2}{3} - \frac{V_1 - V_3}{2} &= 0 \end{aligned} \right\} \times 6$$

$$-60A + 2V_1 - 2V_2 + 3V_1 - 3V_3 = 0$$

$$\textcircled{1} \quad 5V_1 - 2V_2 - 3V_3 = 60$$

$$\textcircled{2} \text{ } V_2: \left. \begin{aligned} \frac{V_2 - V_0}{4} + \frac{V_2 - V_1}{3} - 4i_x &= 0 \end{aligned} \right\} \times 12.$$

$$3V_2 + 4V_2 - 4V_1 - 12V_2 = 0.$$

$$\textcircled{2} \quad -4V_1 - 5V_2 + 0V_3 = 0.$$

$$\textcircled{3} \text{ } V_3: \left. \begin{aligned} \frac{V_3 - V_1}{2} + \frac{V_3 - V_0}{6} + 4i_x &= 0 \end{aligned} \right\} \times 6$$

$$\textcircled{3} \quad -3V_1 + 6V_2 + 4V_3 = 0.$$

Matrix:

5	-2	-3	V_1	=	60
-4	-5	0	V_2	=	0
-3	6	4	V_3	=	0

$$V_1 = \begin{vmatrix} 60 & -2 & -3 \\ 0 & -5 & 0 \\ 0 & 6 & 4 \end{vmatrix} \quad V_2 = \begin{vmatrix} 5 & 60 & -3 \\ -4 & 0 & 0 \\ -3 & 0 & 4 \end{vmatrix} +$$

$$\begin{vmatrix} 5 & -2 & -3 \\ -4 & -5 & 0 \\ -3 & 6 & 4 \end{vmatrix} \quad \begin{vmatrix} 5 & -2 & -3 \\ -4 & -5 & 0 \\ -3 & 6 & 4 \end{vmatrix}$$


* $i_{oc} = \frac{V_2 - V_0}{4}$

* $i_x = \frac{V_2}{4}$


3.3.

Super Node:

Voltage source enclosed by non-ref. node. as well as elements connected in || with the voltage source.

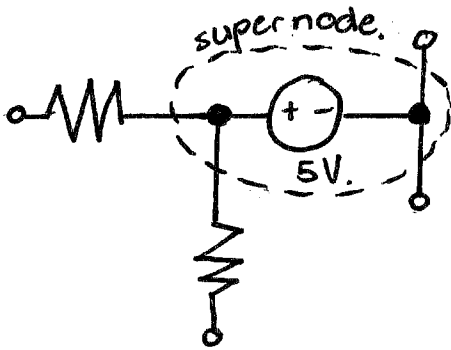

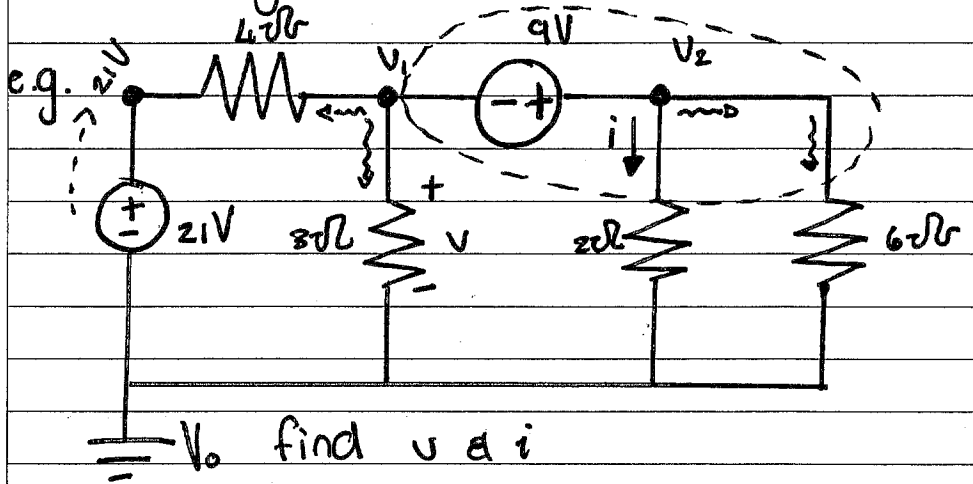* 1st find ΔV over super node.
(1st equation).



① $V_2 - V_1 = 9$ KCL @ supernode:

$$\frac{V_1 - 21}{4} + \frac{V_1}{3} + \frac{V_2}{2} + \frac{V_2}{6} = 0 \quad \times 12$$

② $7V_1 + 8V_2 = 63$

Cramer's Rule:


$$\begin{bmatrix} -1 & 1 \\ 7 & 8 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 9 \\ 63 \end{bmatrix}$$

$$V_1 = \frac{\begin{vmatrix} 9 & 1 \\ 63 & 8 \end{vmatrix}}{\begin{vmatrix} -1 & 1 \\ 7 & 8 \end{vmatrix}} = \frac{9}{-15}$$

$$V_2 = \frac{\begin{vmatrix} -1 & 9 \\ 7 & 63 \end{vmatrix}}{\begin{vmatrix} -1 & 1 \\ 7 & 8 \end{vmatrix}} = \frac{-126}{-15}$$

$V_1 = -0.6V$


$V_2 = 8.4V$

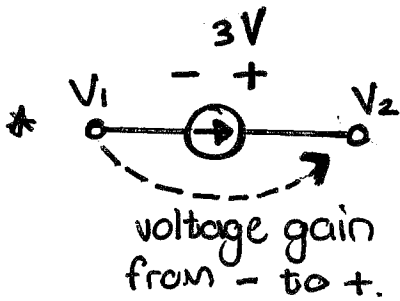

$\Rightarrow V_1 + 3V = V_2$

Mesh Analysis:

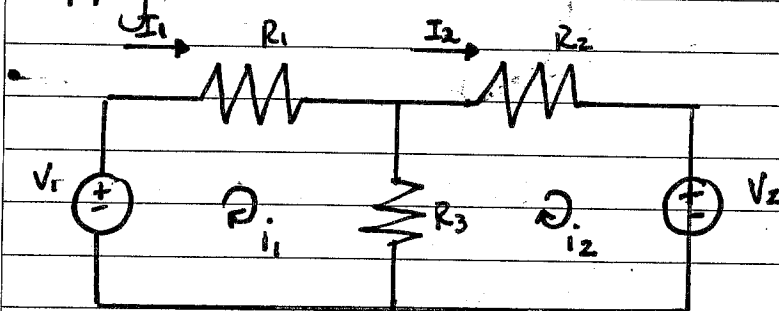- A mesh is a loop that does not include any other loop.
- Apply KVL to find unknown current.




- * 2 Meshes.
- * 3 Loops.

Step 1: Assign Mesh current.
 → Label.
 → Direction.

Step 2: KVL → equations.


Step 3: Solve for the unknown.

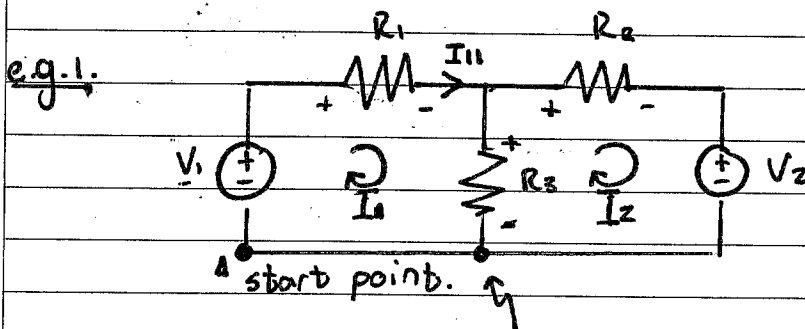

* $\sum V \text{ in loop} = 0$

eq.1) $-V_1 + R_1 \times I_1 + R_3(I_1 - I_2) = 0$

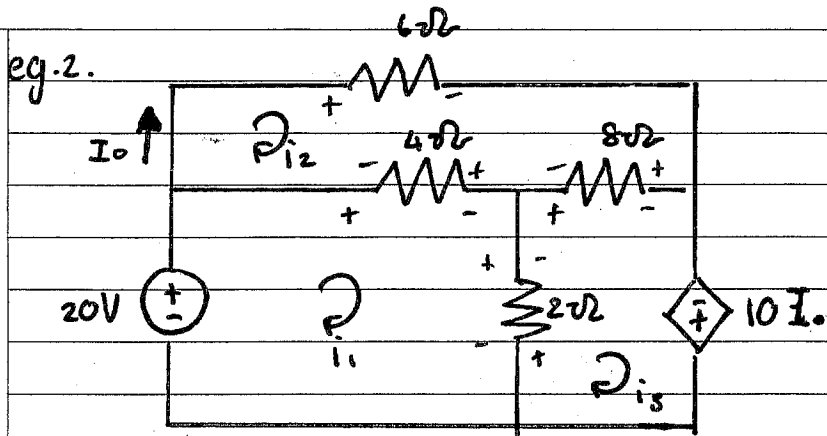eq.2) $R_3(I_2 - I_1) + R_2 I_2 + V_2 = 0$



Find I_o :

$$\text{Mesh(1)}: -20 + 4i_1 + 2(i_1 - i_3) - 4i_2 = 0$$

$$\text{Mesh(2)}: 2(i_3 - i_1) + 8(i_3 - i_2) - 10I_o = 0$$

$$\text{Mesh(3)}: 6i_2 + 8(i_2 - i_3) + 4(i_2 - i_1) = 0$$

$$\textcircled{1} \quad 6i_1 - 4i_2 - 2i_3 = 20$$

$$\textcircled{2} \quad -2i_1 - 18i_2 + 10i_3 = 0$$

$$\textcircled{3} \quad -4i_1 + 18i_2 - 8i_3 = 0$$

$$\begin{bmatrix} 6 & -4 & -2 \\ -2 & -18 & 10 \\ -4 & 18 & -8 \end{bmatrix}$$


$$i_2 = \begin{vmatrix} 6 & 20 & -2 \\ -2 & 0 & 10 \\ -4 & 0 & -8 \end{vmatrix} \quad \underline{\underline{1120}}$$

$$\begin{vmatrix} 6 & -4 & -2 \\ -2 & -18 & 10 \\ -4 & 18 & -8 \end{vmatrix} \quad \underline{\underline{-224}}$$

$$i_2 = -5A$$

$$I_o = -5A$$

eg. 2.

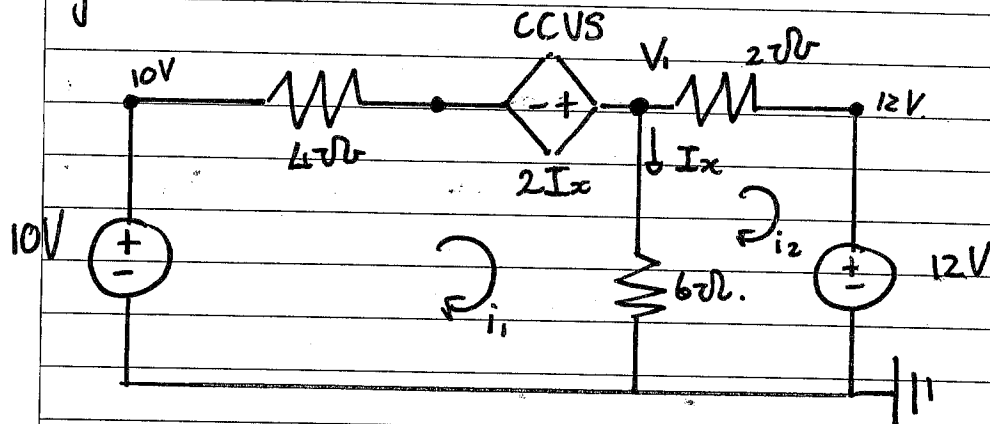

~~$I_x = 6(i_2)$~~
 $I_x = i_1 - i_2$

Mesh Analysis:
KVL

Mesh 1: $-10 + 4i_1 - 2I_x + 6(i_1 - i_2) = 0$.

Mesh 2: $6(i_2 - i_1) + 2i_2 + 12 = 0$

$i_1 = 0.8A \quad i_2 = -0.9A$

$\Rightarrow I_x = \cancel{0.1A} \quad 1.7A$

Nodal Analysis:
KCL
(1 crit. node)

$\frac{V_1 - 2I_x - 10}{4} + \frac{V_1 - 12}{2} + \frac{V_1}{6} = 0$


$I_x = \frac{V_1}{6}$

(a) sub $I_x = \frac{V_1}{6} \Rightarrow V_1 = 10.2V$

(b) sub $V_1 = 6I_x \Rightarrow I_x = 1.7A$


Supermesh:

Both in opp. direct:

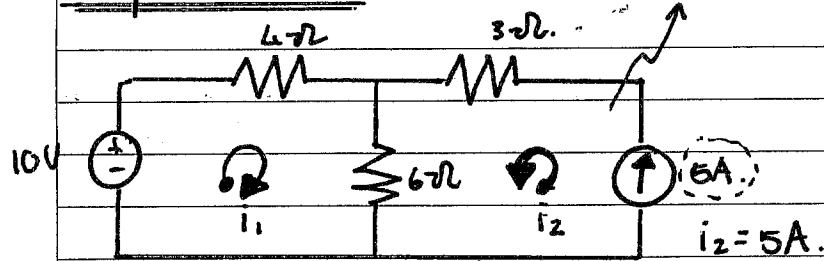

$$\text{Mesh 1: } -10 + 4i_1 + 6(i_1 + 5) = 0$$

$$\Rightarrow i_1 = -2A.$$

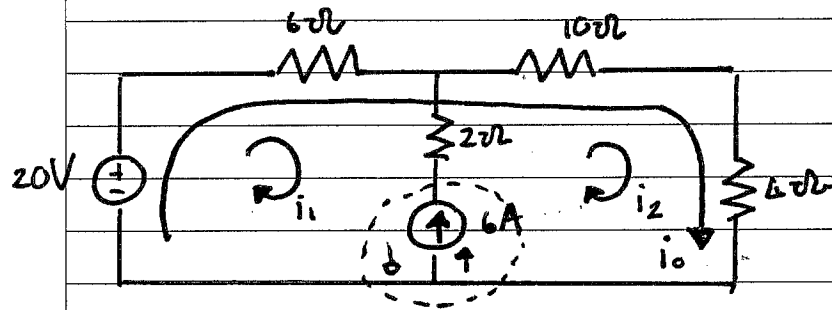

$$\textcircled{1} * \quad 6 = i_2 - i_1$$


$$\text{Mesh 1: } -20V + 6i_1 + 2(i_1 - i_2) + \dots = 0.$$

* Failed using KVL
 $\Rightarrow$ Supermesh.

Supermesh: (ignore common branch)

$$\textcircled{2} * \quad -20 + 6i_1 + 10i_2 + 4i_2 = 0$$

eg. 3.

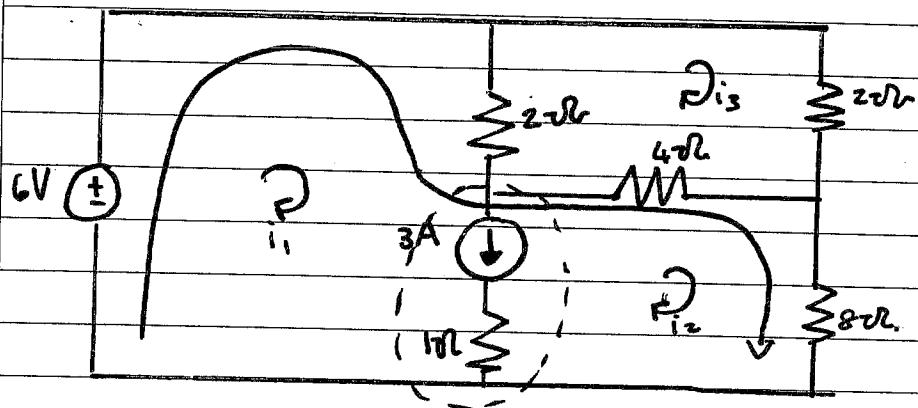

Branch Current: $3 = i_1 - i_2$ (1)

Super mesh:

$$-6 + 2(i_1 - i_3) + 4(i_2 - i_3) + 8i_2 = 0 \quad (2)$$

Mesh 3:

$$2(i_3 - i_1) + 2i_3 + 4(i_3 - i_2) = 0 \quad (3)$$


$$(1) \quad i_1 - i_2 - 0i_3 = 3$$

$$(2) \quad 2i_1 + 12i_2 - 6i_3 = 6$$

$$(3) \quad -2i_1 - 4i_2 + 8i_3 = 0$$

$$\begin{bmatrix} 1 & -1 & 0 \\ 2 & 12 & -6 \\ -2 & -4 & 8 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} 3 \\ 6 \\ 0 \end{bmatrix}$$

* Mesh current
= all mesh
currents.

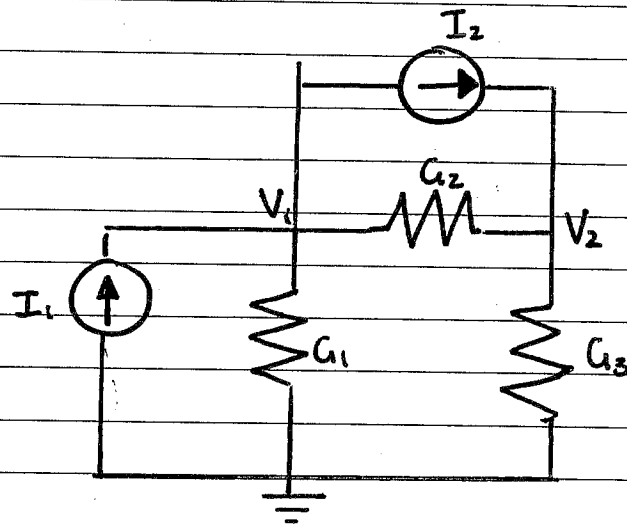Mesh & Nodal analysis by inspection.

$$C_{ji} = C_{ij} \quad i \neq j$$

C_{11} = Total conductance (with node 1)

C_{22} = Total conductance (with node 2)

C_{12} = - (Common Conductance)

C_{21} = - (Common Conductance)

Vector:


"current account"
current entering
or leaving via
current source.

$$\begin{pmatrix} G_1 + G_2 & -G_2 \\ -G_2 & G_2 + G_3 \end{pmatrix} \begin{pmatrix} V_1 \\ V_2 \end{pmatrix} = \begin{pmatrix} I_1 - I_2 \\ I_2 \end{pmatrix}$$

conductance matrix nodal voltages.

• sum of independent current source entering a node.

Nodal Analysis By Inspection:

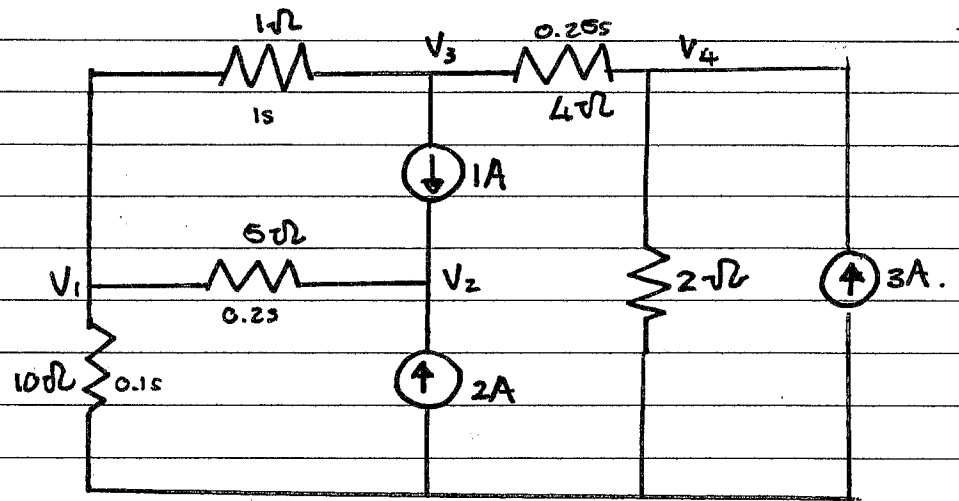

* Note: it is a symmetric matrix.


$$\begin{pmatrix} 1.3 & -0.2 & -1 & 0 \\ -0.2 & 0.2 & 0 & 0 \\ -1 & 0 & 1.25 & -0.25 \\ 0 & 0 & -0.25 & 0.75 \end{pmatrix} \begin{pmatrix} V_1 \\ V_2 \\ V_3 \\ V_4 \end{pmatrix} = \begin{pmatrix} 0 \\ 3 \\ -1 \\ 3 \end{pmatrix}$$

$$C_{11} = 1 + 0.1 + 0.2 = 1.3$$

$$C_{22} = 0.2$$

$$C_{33} = 1 + 0.25 = 1.25$$

$$C_{44} = 0.75$$

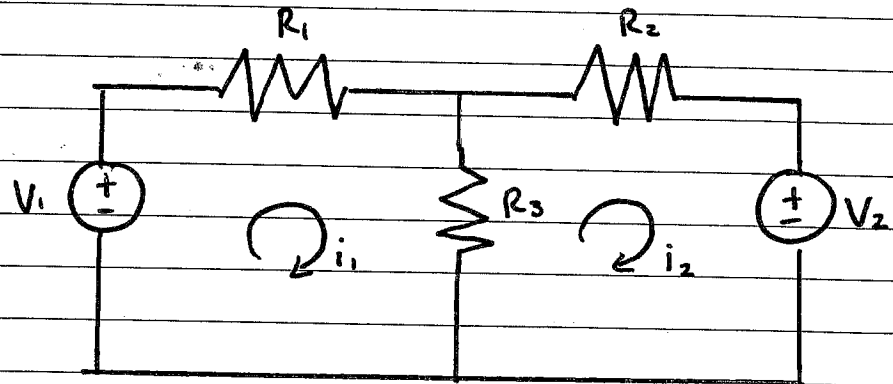Mesh Analysis by Inspection.

⇒ Symmetric.

$$R_{ij} = R_{ji}$$

R_{12} = Resistance between loops $\times (-1)$

R_{21} = Resistance between loops $\times (-1)$

R_{11} = Resistance in loop

R_{22} = Resistance in loop.

$$\begin{pmatrix} R_1 + R_3 & -R_3 \\ -R_3 & R_2 + R_3 \end{pmatrix} \begin{pmatrix} i_1 \\ i_2 \end{pmatrix} = \begin{pmatrix} V_1 \\ -V_2 \end{pmatrix}$$


Resistance Matrix Vector for mesh current.

sum. of independent voltage increase of a mesh.

note:

$$\rightarrow \begin{pmatrix} - & + \end{pmatrix} = +V_1$$
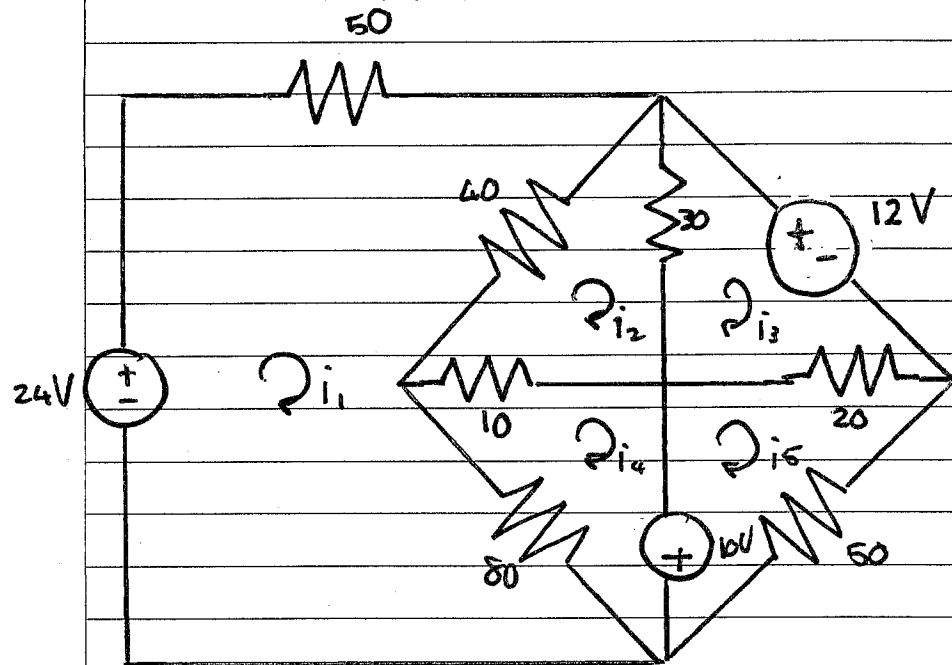
$$\leftarrow \begin{pmatrix} - & + \end{pmatrix} = -V_1$$




$$\begin{pmatrix} 170 & -40 & 0 & -80 & 0 \\ -40 & 80 & -30 & -10 & 0 \\ 0 & -30 & 50 & 0 & -20 \\ -80 & -10 & 0 & 90 & 0 \\ 0 & 0 & -20 & 0 & 80 \end{pmatrix} \begin{pmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \\ i_5 \end{pmatrix} = \begin{pmatrix} 24 \\ 0 \\ -12 \\ 10 \\ -10 \end{pmatrix}$$

Transistors:

* BJT

Bipolar Junction Transistor.

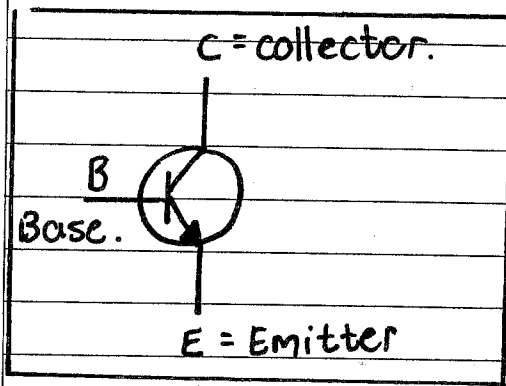


2 Types:

- BJT.
- FET.

Note: V from + to - terminal.
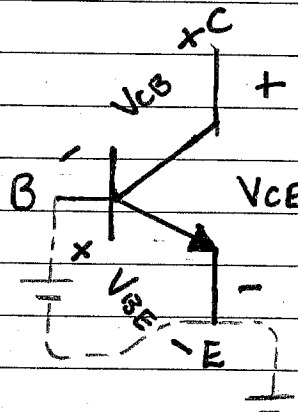
$$\Rightarrow \overset{-}{B} \text{ --- } V_{CB} \text{ --- } \overset{+}{C}$$




Voltage:

$$V_{CE} = V_{BE} + V_{CB}$$

$$= 0.7 + V_{CB}$$

$$V_{BE} = 0.7V$$

Current:

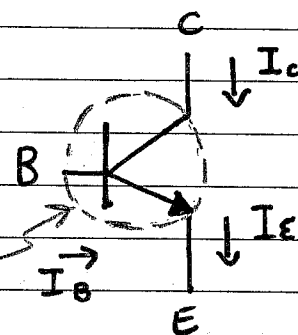


$$I_B + I_C = I_E \quad (1)$$

Analyse as a supernode.

β = common-emitter current gain.

β : constant
no unit.
50-100

α : approaching 1
0.98-0.99.

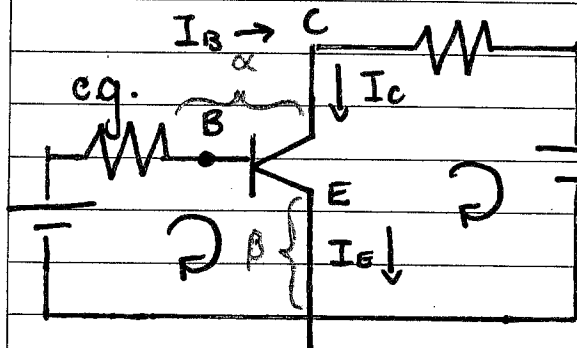

$$I_C = \beta I_B \quad (2)$$

α = common-base current gain.

$$I_C = \alpha I_E \quad (3)$$


Derived Formulas:

① $I_E = (1 + \beta) I_B$

② $\alpha = \frac{\beta}{1 + \beta} \Rightarrow \alpha \rightarrow 1, \underline{\underline{\alpha < 1}}$

③ $\beta = \frac{\alpha}{1 - \alpha}$


Equivalent Network model:

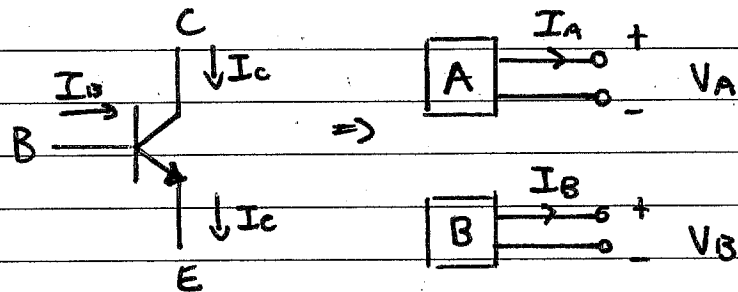

* Other factors were not taken into consideration.


$$I_A = I_B \quad \& \quad V_A = V_B.$$

$\Rightarrow$ A is equivalent to B

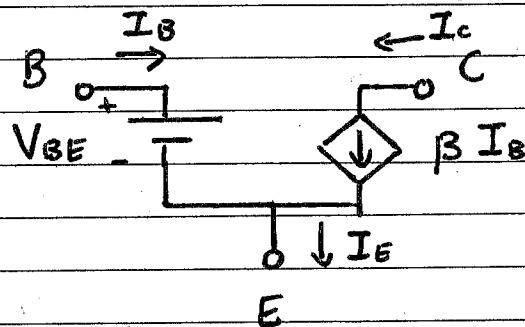

- $V_{BE} = 0.7V$
- $I_C = \beta I_B$
- $I_C = I_B + I_E$

Transistor circuit analysis:

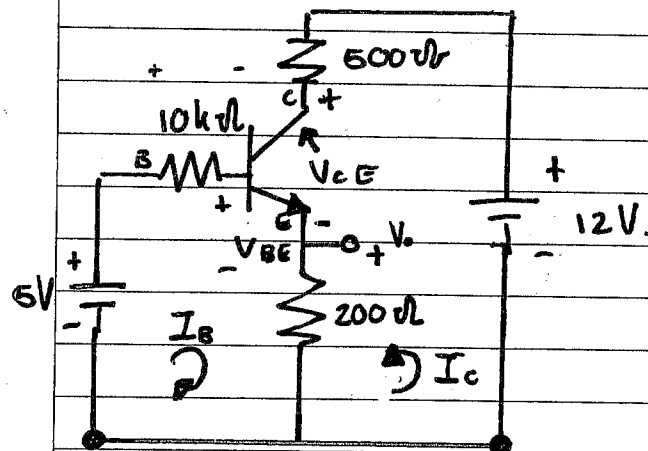

Mesh I_B : $-5 + 10000(I_B) + V_{BE} + V_o = 0$

V_{out} : $V_o = 200(I_B + I_C)$

Mesh I_C : $-12 + 500(I_C) + V_{CE} + V_o = 0$

Relationship: $I_C = \beta I_B$

$$-5 + 10^4 I_B + 0.7 + 200(I_B + \beta I_B) = 0.$$



$$\Rightarrow 10^4 I_B + 200 \times 101 I_B = 4.3$$

$$\Rightarrow 30200 I_B = 4.3.$$

$$\Rightarrow I_B = 0.1424 \text{ mA}$$

$$-12 + 500(100 \times 0.1424 \times 10^{-3}) + V_{CE} + 200(0.14 \times 10^{-3} + 100 I_B) = 0.$$

$$\Rightarrow V_{CE} = 2V$$

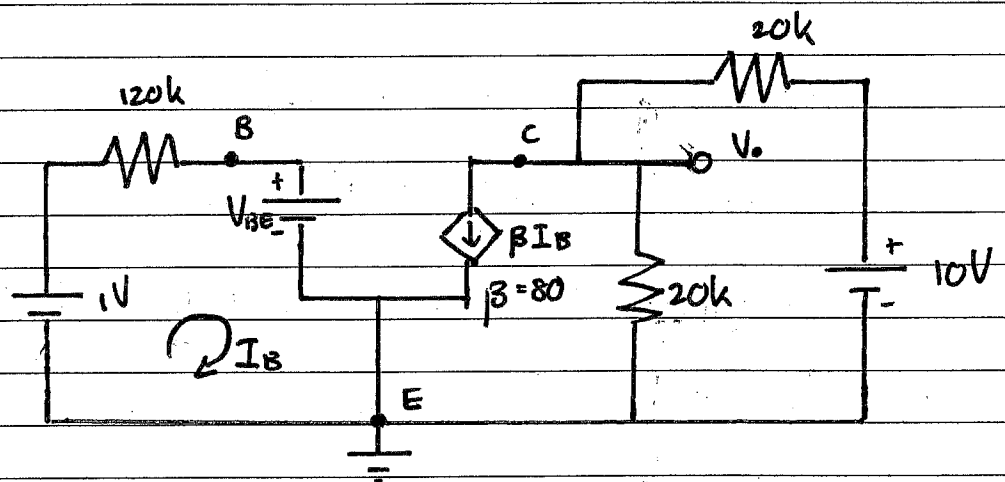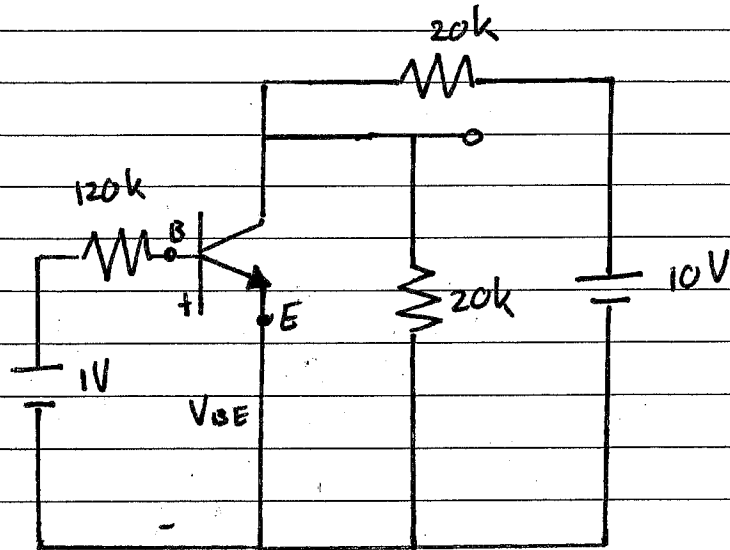

$$-1 + 120 \times 10^3 \times I_B + 0.7 = 0$$

$$\Rightarrow I_B = 2.5 \mu A$$

$$\beta I_B + \frac{V_o}{20k} + \frac{V_o - 10}{20k} = 0$$


$$80 \times (2.5 \times 10^{-6}) \times 20 \times 10^3 + 2V_o = 10$$

$$\Rightarrow 4 + 2V_o = 10$$

$$\Rightarrow V_o = 3V$$

$$I_o = \frac{3V}{20k\Omega} = 150 \mu A$$

Determine: V_{CE} & I_B . $V_{BE} = 0.7$
 $\beta = 100$.

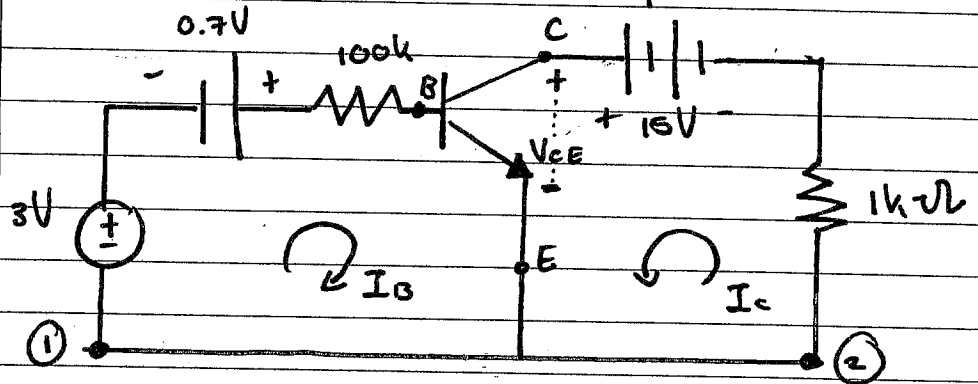

Mesh 1:

$$-3 - 0.7 + (100 \times 10^3) \times I_B + V_{BE} = 0.$$

$$\Rightarrow \underline{I_B = 30 \mu A}$$

Mesh 2:

$$10^3 \times I_C - 15 + V_{CE} = 0$$


$$\Rightarrow 10^3 \times \underbrace{100}_{\beta} \times \underbrace{30 \times 10^{-6}}_{I_B} - 15 = -V_{CE}$$

$$\Rightarrow \underline{V_{CE} = 12V.}$$

$$I_C = \beta I_B$$

Chapter 4: Circuit Theorems.

Linearity & Superposition:

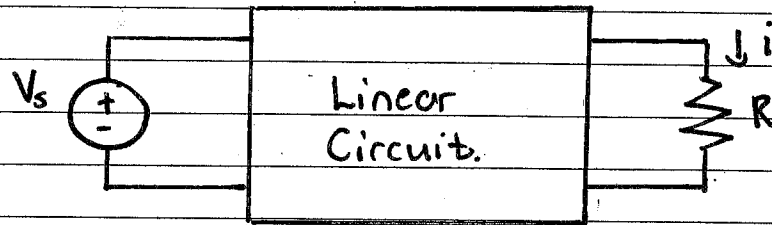

- If $V_s = 10V \Rightarrow i = 2A$ (Observed results)

then. $V_s = 1V \Rightarrow i = 0.2 A$

$V_s = 100V \Rightarrow i = 20 A$

Two Properties: (Of linearity).

(a)* Homogeneity (scaling)

* $V = I \times R$


$kV = kI \times R$

(b)* Additivity

* $V_1 = I_1 R$
 $V_2 = I_2 R \quad \Rightarrow V_1 + V_2 = (I_1 + I_2) R$

Linearity:

Output linearly related to Input.

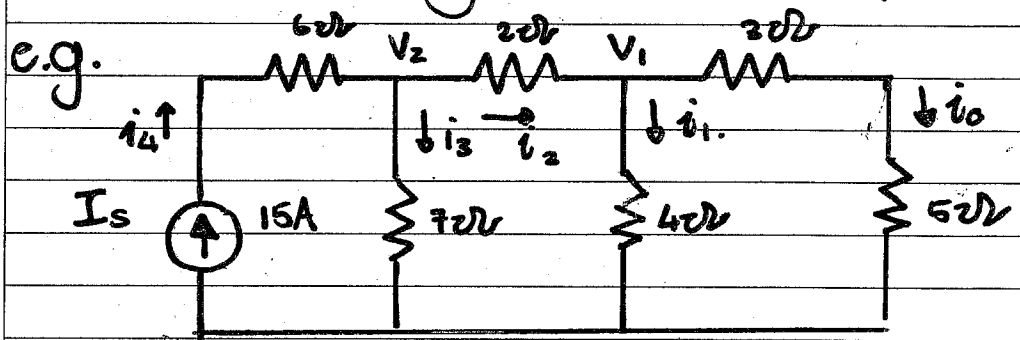

$V_1 = 1 \times (3 + 5) = 8V$

$V_2 = V_1 + I_2 \times 2 = 14V$

$I_1 = 8/4 = 2A$

$I_3 = 14/7 = 2A$

$I_2 = I_1 + I_3 = 3A$


Note:

Let $i_o = 1A$.



Find $\frac{i_o}{i_s} = k$.

$I_{o_actual} = k \cdot I_{s_actual}$

Superposition Theorem:

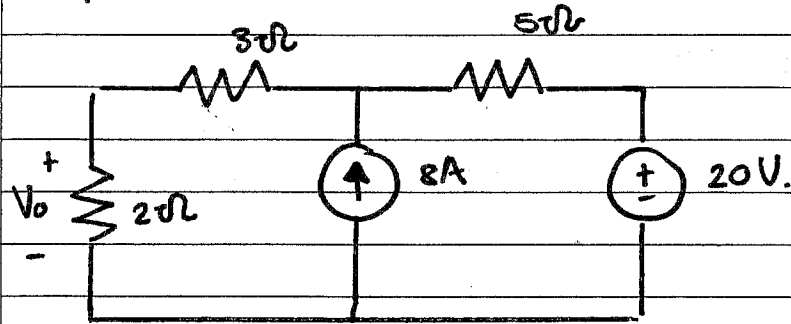

1. Turn off INDEPENDENT sources.

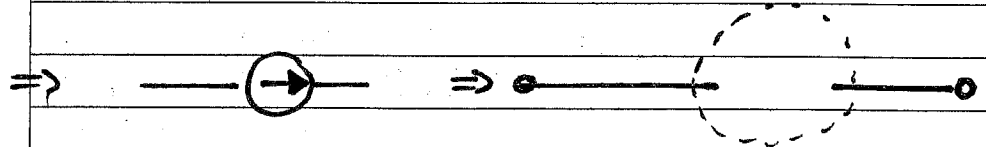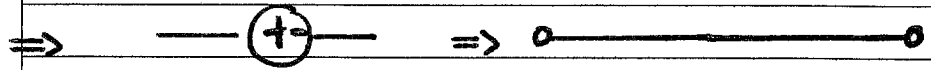

* Leave Dependent Sources.

2. Repeat step 1 with analysis.

3. Summation (Additivity).

Theory: Voltage across element is the sum of voltage across element due to EACH independent source alone.


Short Circuit: $R = 0\Omega$

Open Circuit: $R = \infty\Omega$

Source Transformation:

Equivalent circuit: A new circuit whose V & I characteristics are identical with the original circuit.

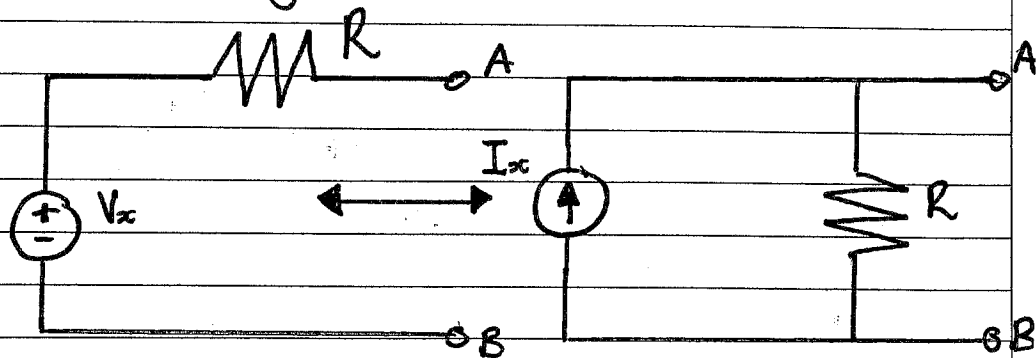* Measurements at A & B yields same result.




Value:



- ① Change Configuration: (series $\rightarrow$ parallel) (V $\rightarrow$ A)
- ② Define Values: $\rightarrow R$ (does NOT change)
- ③ Value of Source: $I_s = \frac{V_s}{R}$ OR $V_s = I_s R$

Direction:

- ① Arrow of (A) pointing to + end.

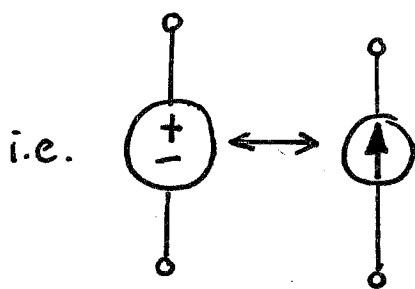

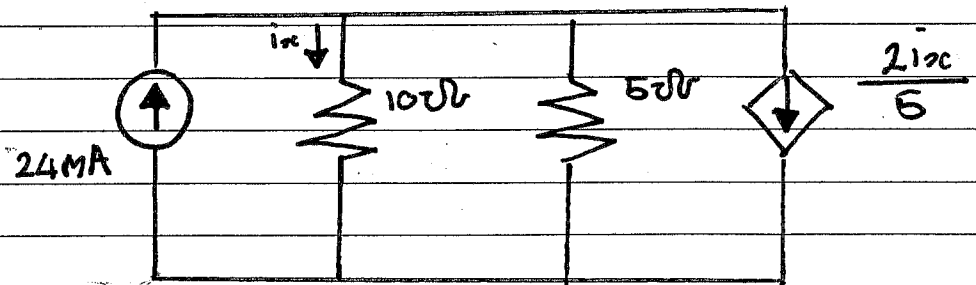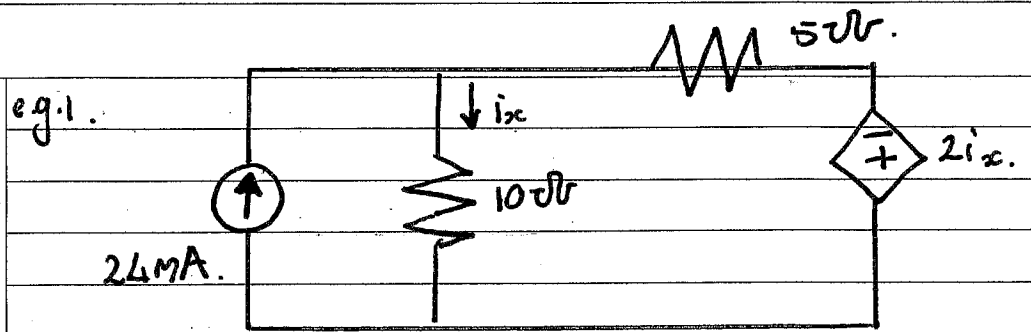* Same applies to independent & dependent sources.



$$i_x = \frac{5}{10 + 5} \left(\frac{24\text{mA} - 2i_x}{5} \right)$$


Notes:

Do NOT transform part of circuit with unknown variable.

- * Transistor NOT linear.
- * Linear : R, Voltage s.
Current s.


Thévenin's Theorem:

Linear two-terminal circuit.

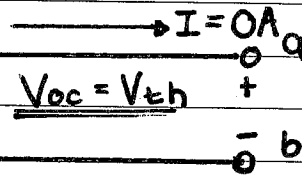


V_{oc} = Open Circuit Voltage

e.g.

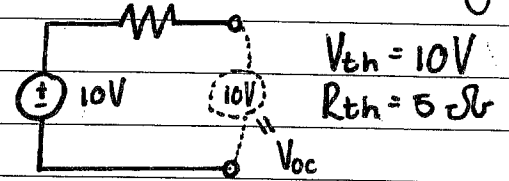

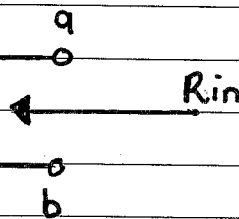Linear circuit with all independent sources set equal to zero



$$R_{th} = R_{in}$$


Method 1: Zeroing of sources:

- * If the circuit has no dependent sources.

Method 2: Application of test sources:


- * If the circuit DOES contain dependent sources

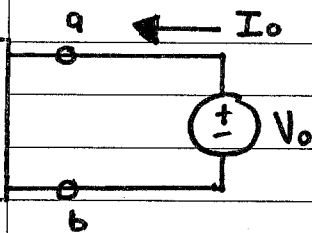Circuit with all independent sources set = 0



$$R_{Th} = \frac{V_o}{I_o}$$

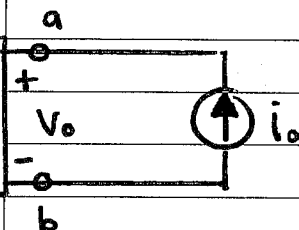Circuit with all independent sources set = 0





$$R_{Th} = \frac{V_o}{i_o}$$

* Note: We ignore the 1Ω resistor.

$$V_{Th} = V_{ab}$$

(Use diff. methods)
(V over 4Ω)

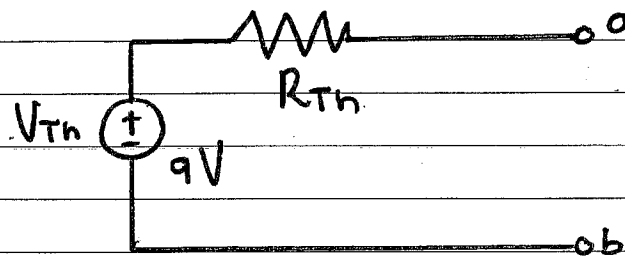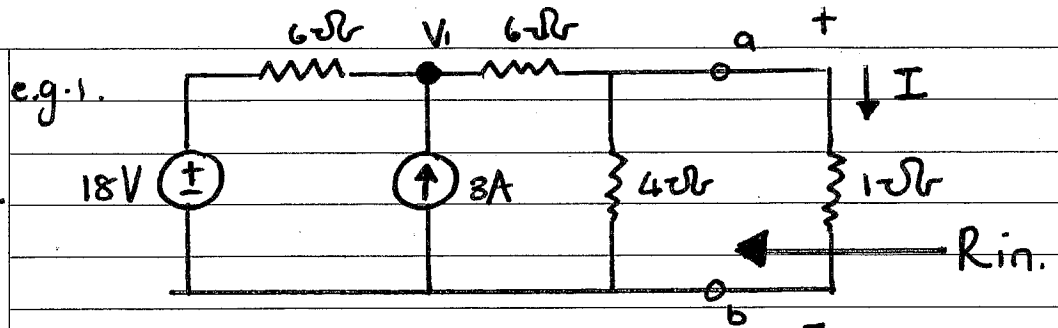- Nodal
- Mesh
- Superposition.
- Transformation.



$$\frac{V_1 - 18}{6} + \frac{V_1}{10} = 3$$

For V_{Th} :

$$90 = 5V_1 - 90 + 3V_1$$

$$V_1 = 22.5 \text{ V}$$

$$V_{Th} = V_1 \cdot \frac{4}{10}$$

$$\underline{\underline{V_{Th} = 9 \text{ V}}}$$

For R_{Th} :

$$R_{Th} = 4 \parallel (6 + 6) = \frac{48}{16} = \underline{\underline{3 \Omega}}$$

Notes:

Calculating V_{Th} .

* Remove load.

* Calc. voltage drop across terminal.


Calculating R_{Th} :

* Short all voltage sources.

* Open all current sources.

* Circuit with ONLY resistors.

* Calc. $R_{eq} = R_{Th} = R_{in}$.

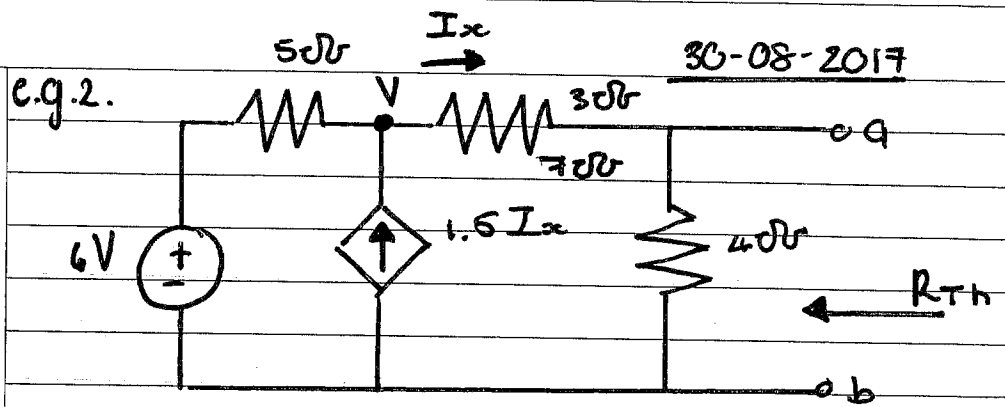

$$V_{Th} = V_{ab}, \quad \frac{V-6}{5} + \frac{V}{7} = 1.5I_x = 1.5 \frac{V}{7}$$


$$\Rightarrow \frac{V-6}{5} = \frac{V}{14}$$

$$\Rightarrow V = 28/3 \text{ V}$$

For V_{Th} :

$$V_{Th} = \frac{28}{3} \times \frac{4}{7} = \frac{16}{3} \text{ V}$$

For R_{Th} :

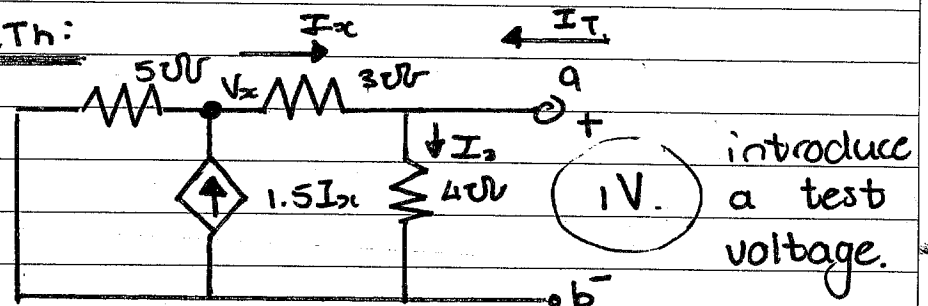


$$(1) \quad 1.5I_x = \frac{V_x}{5} + \frac{V_x - 1}{3}$$

$$(2) \quad \frac{V_x - 1}{3} = \frac{V_x}{5} \quad \begin{matrix} V_x = -5 \text{ V} \\ I_x = -2 \text{ A} \end{matrix}$$

$$(3) \quad I_2 = \frac{1}{4} = 0.25 \text{ A}$$

$$I_T = 2 + 0.25 = 2.25 \text{ A}$$

$$R_{Th} = \frac{V_{Th}}{I_T} =$$

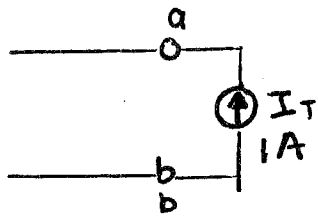

same circuit diff. approach:

$$0.5 I_x = \frac{V}{6} = 0.5 \cdot \frac{V - V_T}{3}$$

$$\frac{V}{6} = \frac{V - V_T}{6} \quad (1)$$

$$\frac{V - V_T}{3} + 1 = \frac{V}{4} \quad (2)$$

$$\underline{V_T = \frac{4}{9} V.}$$


$$R_{Th} = \frac{V_{Th}}{I_{Th}} = \frac{1}{9/4} = \frac{4}{9} \Omega$$

Notes:

✓ Cancel out the R_1 resistor if over a-b terminal.

★ If Dependent sources present use a test voltage.


$$R_{TH} = \frac{V_o}{i_o.}$$

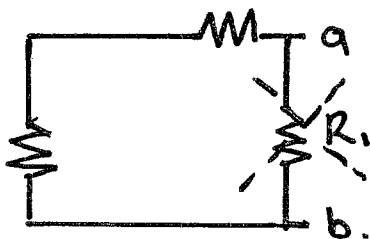

(chap 4)


- Norton's eq. circuit = Thevenin eq. circuit.
- $R_{Th} = R_N$
- $I = \frac{V_{Th}}{R_{Th}}$
- $I = I_N$.

Norton's Theorem: (4.6).

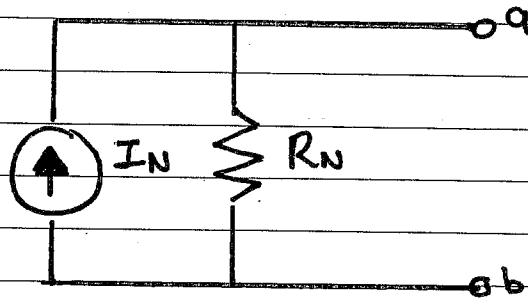

Determine I_N :

Linear two-terminal circuit:

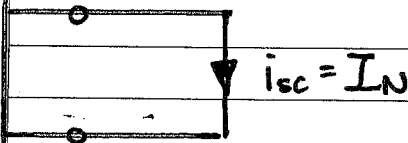

- Norton equivalent current is the short circuit current.

Determine R_N :

Method 1: Zero independent sources.



Method 2: by testing $\rightarrow$ (A) $\rightarrow$ (V)

Method 3:

$$R_{Th} = \frac{V_{oc}}{I_{sc}}$$

$$R_{Th} = R_N =$$

I_N :

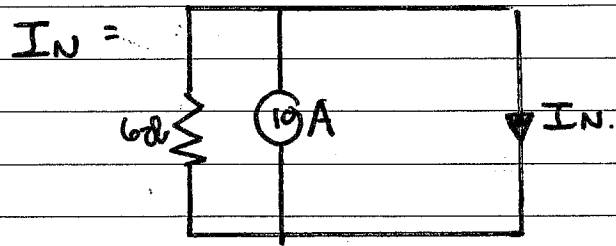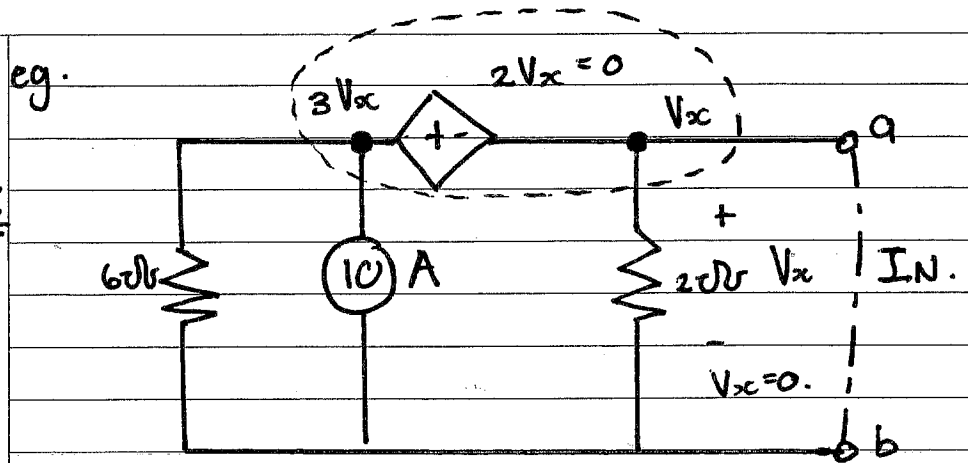

$I_N = 10A$

R_N :



$$R_N = \frac{V_{oc}}{I_N}, \quad I_N = 10A$$

$$10 = \frac{3V_x}{6} + \frac{V_x}{2} \Rightarrow V_x = 10V$$

$$R_N = 1\Omega$$

Maximum Power Transfer.

Power transfer profile with diff. R_L :

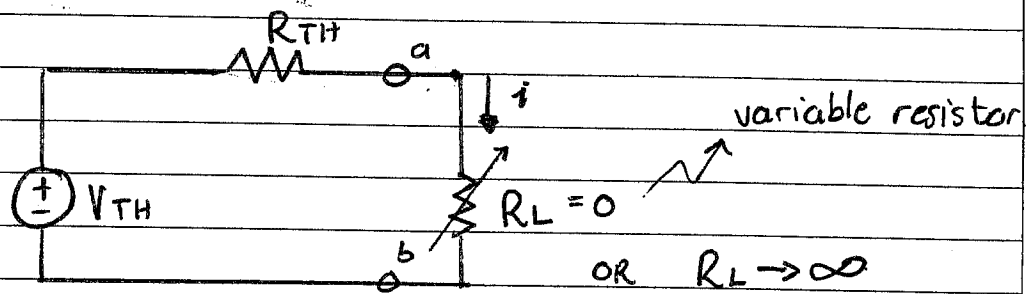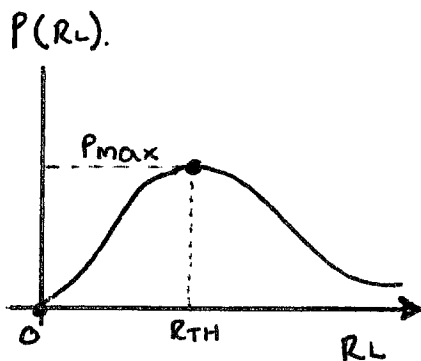

$$P(R_L) = i^2 \cdot R_L = \left(\frac{V_{TH}}{R_{TH} + R_L} \right)^2 \cdot R_L$$

if $R_L \rightarrow \infty$, $i = 0$ (open circuit)

$$P_{max} = \left(\frac{V_{TH}}{2R_{TH}} \right)^2 \cdot R_{TH} \quad \left\{ \text{Where } R_L = R_{TH} \right\}$$

$$* \quad P_{max} = \frac{V_{TH}^2}{4R_{TH}} = \frac{V_{RL}^2}{R_{TH}} \quad \text{Proof:}$$

Note: $f(x) = \begin{cases} \text{max} \\ \text{min} \end{cases}$

$$f'(x) = 0.$$

$$\begin{aligned} P'(R_L) &= \left(V_{TH}^2 (R_{TH} + R_L)^{-2} R_L \right)' \\ &= V_{TH}^2 \left[-2(R_{TH} + R_L)^{-3} R_L + (R_{TH} + R_L)^{-2} \right] \end{aligned}$$

$$P_{max} \rightarrow P'(R_L) = 0$$

$$\Rightarrow \frac{-2R_L}{(R_{TH} + R_L)^3} + \frac{1}{(R_{TH} + R_L)^2} = 0.$$

$$\Rightarrow -2R_L + R_{TH} + R_L = 0.$$

$$\Rightarrow R_L = R_{TH} \rightarrow P'(R_L) = 0.$$

$\rightarrow$ Maximum power.

$$R_{TH} + R_L \neq 0$$


[illegible]

Chapter 5:Op Amp:




* Behaves as a VCVS.
 * Operational Amplifier.

- integrated circuit. (IC).


- active ~~current~~ element.
circuit.

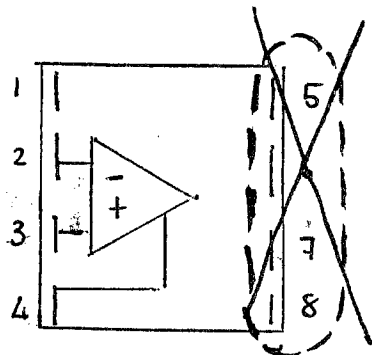

• Note how incorrect nrs. causes error.

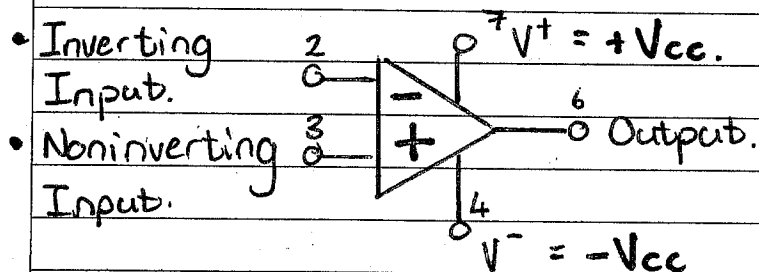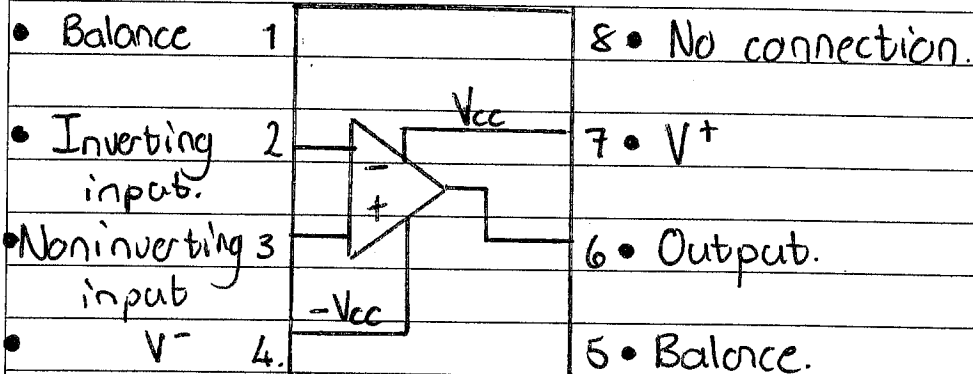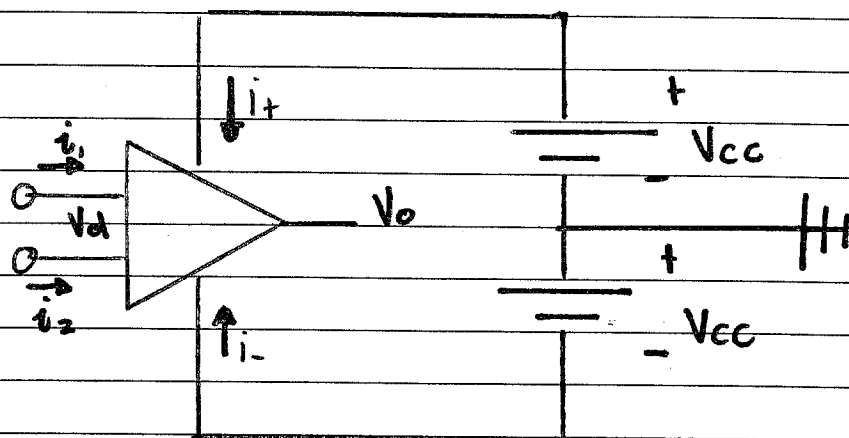Connection:

Equivalent Circuit: ①

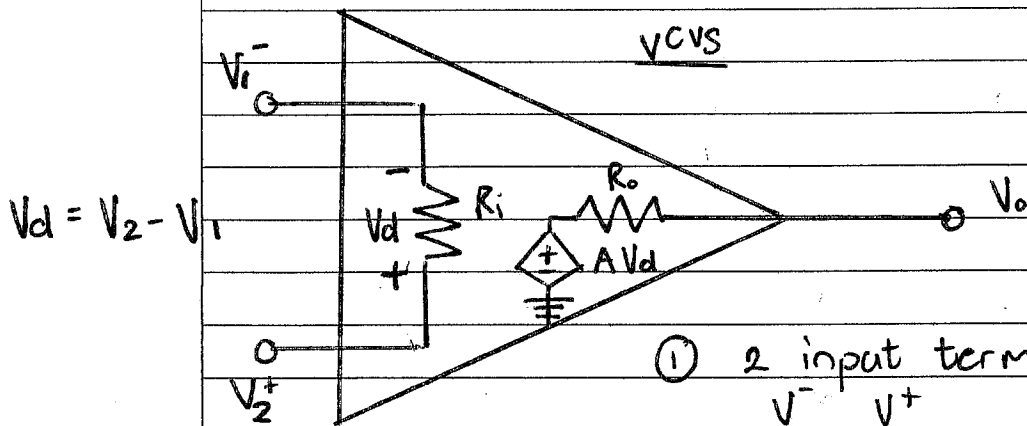

- ① 2 input terminals.
 V^- V^+
- ② R_i : input resistance.
- ③ R_o : output resistance.

OR.

$$V_o = A(V_2 - V_1)$$

* $V_d = V^+ - V^-$ (voltage diff. of input)

* $V_o = AV_d$ (function of V_d)


* A : Open loop voltage gain.

* Open loop: feedback loop.

- Op Amps amplifies the voltage difference of V^+ & V^-

$$\text{Closed Loop Gain} = \frac{V_o}{V_s}$$

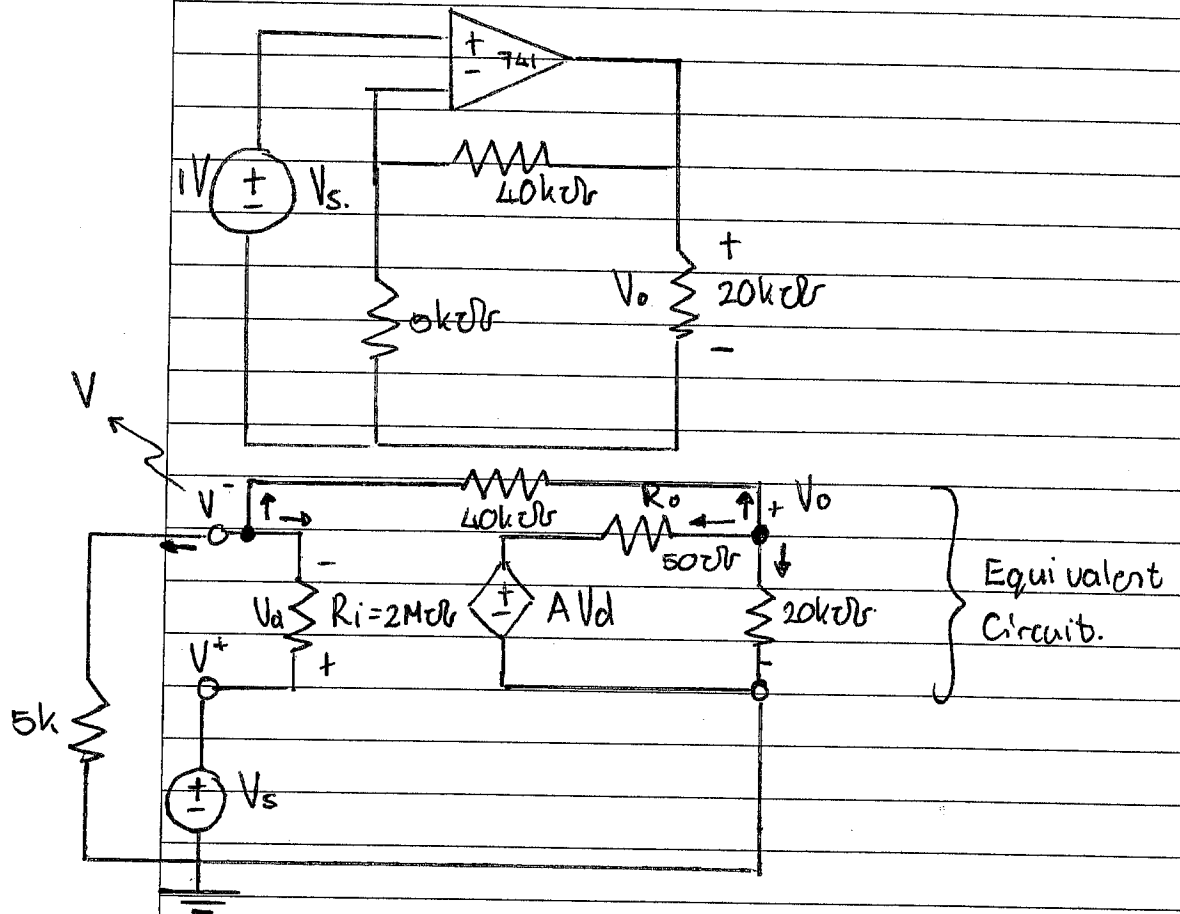Example: $A = 2 \times 10^5$ 741 Op Amp.
 $R_i = 2 \text{ M}\Omega$
 $R_o = 50 \Omega$



$$\textcircled{1} \quad \frac{V}{5\text{k}} + \frac{V - V_o}{40\text{k}} + \frac{V - V_s}{2000\text{k}} = 0$$

$$\textcircled{2} \quad \frac{V - V_o}{40\text{k}} = \frac{V_o - A V_d}{R_o} + \frac{V_o}{20\text{k}} = 0$$

$$1) \quad 400V + 50V - 50V_o + V - V_s = 0. \quad V = \frac{50V_o + V_s}{451}$$

$$451V - 50V_o = V_s \quad \Rightarrow \quad 451$$


$$2) \quad V - V_o = (40 \times 10^3) \cdot \frac{V_o - 2 \times 10^5 (V_s - V)}{50} + 2V_o$$

$$V - V_o = 800V_o - 16 \times 10^7 (V_s - V) + 2V_o$$

$$\Rightarrow V = \frac{50V_o + V_s}{451}, \quad V_s = 1V.$$

[illegible]


Equivalent Circuit ②.

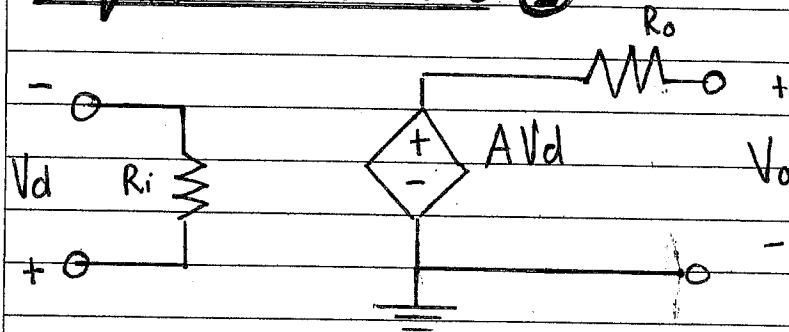

V_{cc} = Supply Voltage.

Parameter	Range	Ideal
A	$10^5 - 10^8$	∞
R_i	$10^6 - 10^{13} \Omega$	∞
R_o	$10 - 100 \Omega$	0
V_{cc}	5 - 24 V	

Practical limitations:

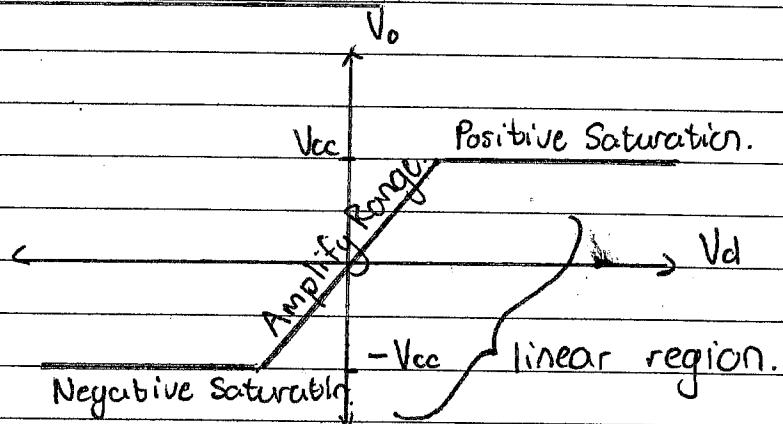


Linear region: $V_d = V^+ - V^-$
 $V_o = A V_d$

Positive saturation: $V_o = V_{cc}$ (max output)

Negative saturation: $V_o = -V_{cc}$

Ideal Op Amp:

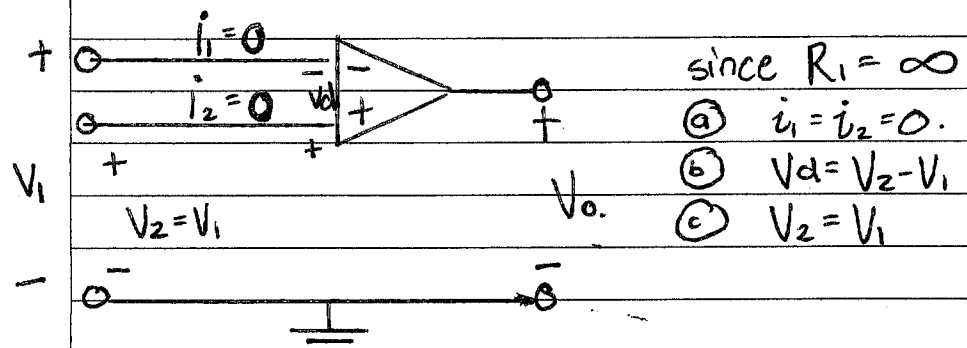

Characteristics:

1. Infinite open-loop gain, $A \approx \infty$
2. Infinite input resistance, $R_i \approx \infty$
3. Zero output resistance, $R_o \approx 0$.

Inverting & Noninverting Amps.


Inverting Amp.

1. Config. of inverting Amp

- a) Signal input from inverting terminal.
- b) Only 1 source connected to V^-
- c) Non-inverting input is grounded.

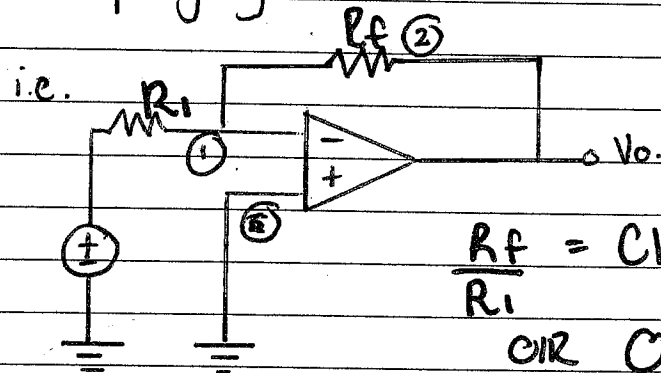2. Function:

- Reversing polarity of input signal while amplifying it.



$$\frac{R_f}{R_i} = \text{Closed-loop gain.}$$

OR Op-amp gain.

Non-inverting Amplifier:

- * Produce +ve voltage gain.
- * Source connected to V^+

Summing amplifier:

- * More than 1 source.



Difference amplifier:

- * Source at each input.

[illegible]

[illegible]

[illegible]

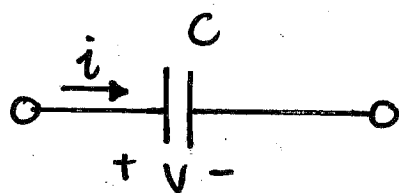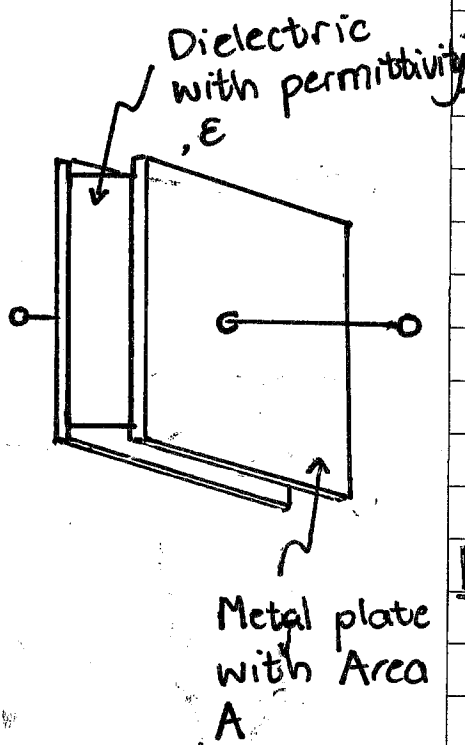Chapter 6:Capacitors:

C = Capacitance
↳ Farad, [F]

- Passive Element.
- Store energy in electric field.


$$C = \frac{\epsilon A}{d}$$

A = Surface Area, plate [m²]
 ϵ = Permittivity, dielectric [F/m]
 d = Distance between plates [m]

$$\epsilon = \epsilon_r \cdot \epsilon_0$$

ϵ_r = Relative permittivity of material.

ϵ_0 = Permittivity of air (8.854×10^{-12} F/m)

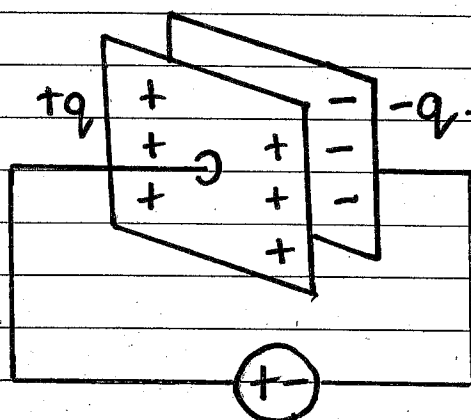Electrical Characteristics:

$$C = \frac{q}{V}$$

$$q(t) = C \times V(t)$$


$$i(t) = C \frac{d(V(t))}{dt}$$

$i > 0$ charging.
 $i < 0$ discharging.

$$V(t) = \frac{1}{C} \int_{-\infty}^t i(t) dt = \frac{1}{C} \int_{t_0}^t i(t) dt + V(t_0)$$

Rhyme: qualification = CV.

$$i = C \times \frac{dv}{dt}$$

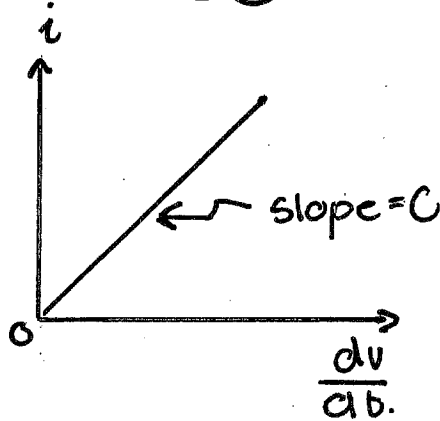

$$\left(\frac{dv}{dt} = 0 \right) [DC]$$

if $\frac{dv}{dt} = \infty$ $i = \infty$
 $\Rightarrow \infty$ heat
 i.e. can't change abruptly.

Energy: (w), [J]

$$(1) \quad w = \frac{1}{2} C v^2 = \frac{q^2}{2C}$$

* energy stored in capacitor.

Power:

$$(2) \quad p = vi = v \times C \times \frac{dv}{dt}$$


Characteristics:

* Open Circuit for DC

* Voltage cannot change abruptly.

* Does NOT dissipate energy, only stores energy (charging) or provide energy (discharging)

Series & Parallel Capacitors:

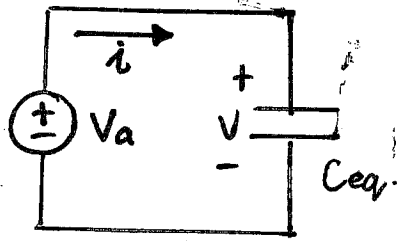


$$V = \frac{1}{C} \int_{t_0}^t i \, dt + V(t_0)$$

$$i = C \frac{dv}{dt}$$

* Series Capacitors
add like ||
Resistors.


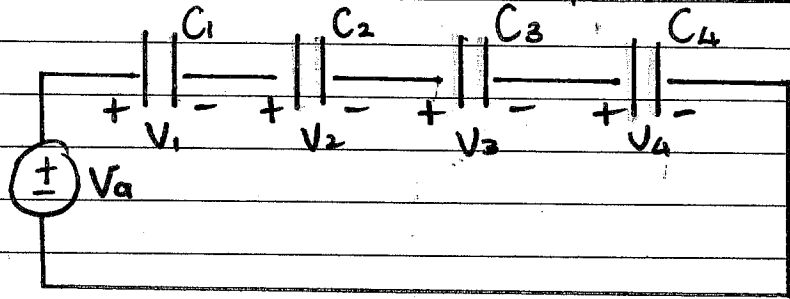
* Parallel Capacitors
add like series
Resistors



- All capacitors in series with V-source.
- $V_1 + V_2 + V_3 + V_4 = V_a$


$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} + \frac{1}{C_4}$$
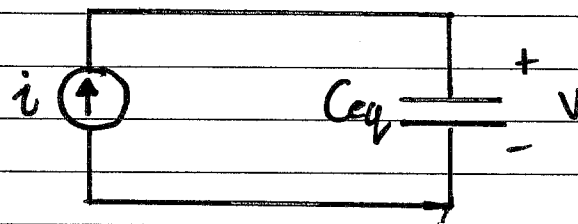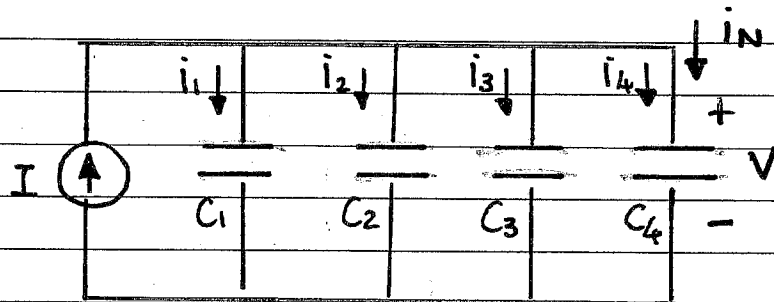
$$V = \left(\frac{1}{C_{eq}} \right) \int_{t_0}^t i \, dt + V(t_0)$$




$$C_{eq} = C_1 + C_2 + C_3 + C_4$$

$$i = C_{eq} \frac{dv}{dt}$$

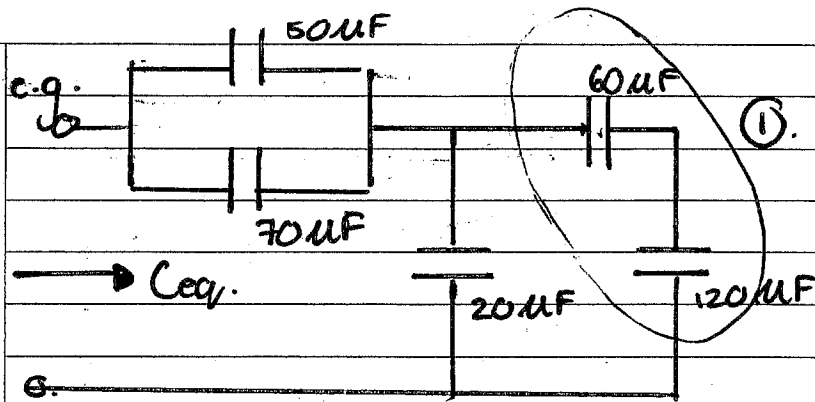

$$\textcircled{1} \quad \frac{60 \times 120}{60 + 120} = 40 \mu F$$

$$\textcircled{2} \quad 120 \mu F$$

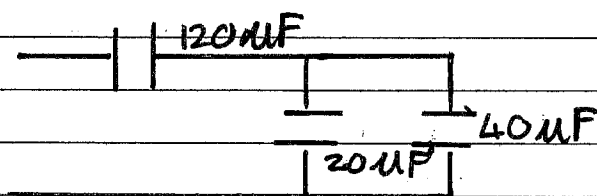

$$C_{eq} = \frac{60 \times 120}{60 + 120} \mu F = 40 \mu F$$

Examples:

- 1) $C = 3 \mu F$, calc. Voltage.
 $q = 0.12 \text{ mC}$ How much w stored?

$$W = \frac{1}{2} C V^2 \quad W = \frac{1}{2} C \left(\frac{q}{C} \right)^2$$

$$q = CV$$

$$W = \frac{1}{2} \frac{(0.12 \times 10^{-3})^2}{3 \times 10^{-6}}$$

$$W = 2.4 \text{ mJ}$$

$$V = \frac{q}{C} = \frac{0.12 \times 10^{-3}}{3 \times 10^{-6}}$$

- 2) $C = 10 \mu F$

$$V(t) = 50 \sin(2000t) \text{ V}$$

calc. $i(t)$.

$$i(t) = C \times \frac{dV(t)}{dt}$$

$$= (10 \times 10^{-6}) \times 50 \times 2000 \times \cos(2000t)$$

- 3) $i(t) = 50 \sin(120\pi t) \text{ mA}$


$$C = 100 \mu F$$

calc. $V(1 \text{ ms})$ & $V(5 \text{ ms})$ Assume $V(0) = 0$

$$V(t) = \frac{1}{C} \int_0^t 50 \sin(120\pi t) \times 10^{-3} dt$$

$$V(t) = \frac{50}{12\pi} (-\cos(120\pi t) + 1)$$

$$V(1 \text{ ms}) = 93.137 \text{ mV}$$

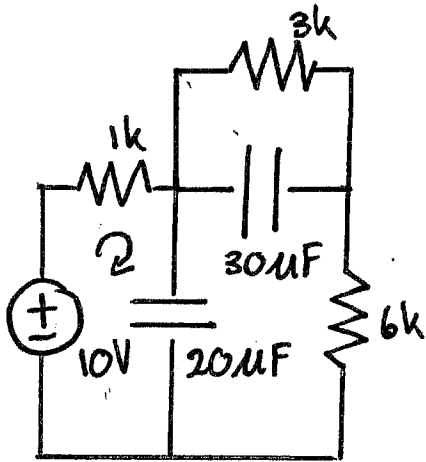

DC conditions.

Calc. W in 2 capacitors.

* fully charged.

$$4) W = \frac{1}{2} C V^2$$

$$V_{30\mu F} = 3V$$

$$V_{20\mu F} = 9V.$$

$$W_{30\mu F} = \frac{1}{2} (30 \times 10^{-6}) \times 3^2$$

$$= 135 \mu J$$


$$V_{30\mu F} = \frac{3k}{1k + 3k + 6k} \times 10.$$

$$KVL: -10V + \frac{1k}{10k} \times 10 + V_{20\mu F}$$

$$V_{20\mu F} = 9V.$$



(Chapter 6).

- Coil of conducting wire.

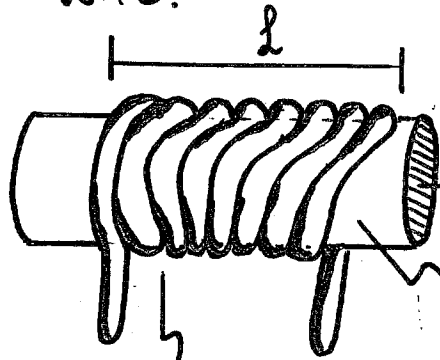

Number of turns (N)

Inductance, L [H].
(Henry)

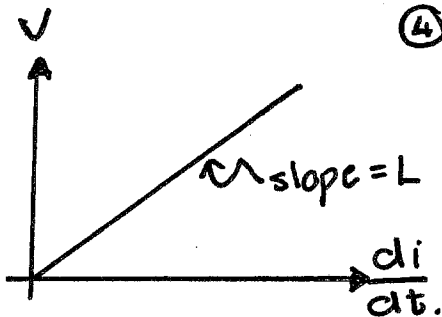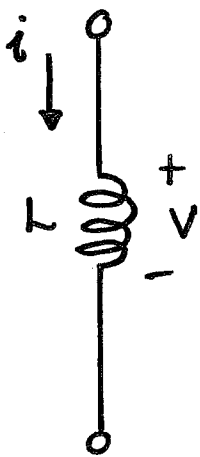Inductors:

- * Passive element
- * Store energy in magnetic field.

→ Cross-sectional Area.

Core Material. $L = \frac{N^2 \mu A}{l}$ [H]

N : Number of turns.

μ : Permeability of core [H/m]

A : Cross-sectional area [m²]

l : Length of coil [m]

μ_r : Relative permeability (scalar).

μ_0 : Permeability of vacuum [H/m]

$$\textcircled{1} \quad i = \frac{1}{L} \int_{t_0}^t v(t) dt + i(t_0)$$

$$\textcircled{2} \quad v = L \frac{di}{dt} \quad \textcircled{3} \quad p = vi = L \frac{di}{dt} i$$


(Power).

$$\textcircled{4} \quad w = \frac{1}{2} L i^2$$

(Energy)


* Inductor opposes change in current.

Metal core

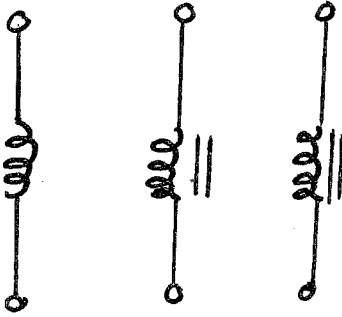


Hollow (air)
core.


Variable

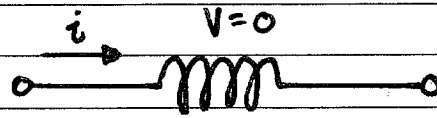

$i = \text{constant}$

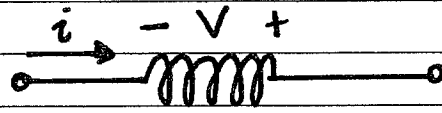

$i = \text{increasing.}$

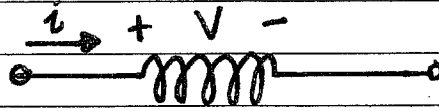

$i = \text{decreasing.}$

Electrical Characteristics. (Inductors)

* Short circuit to DC ($\frac{di}{dt} \neq 0$)

$$(\frac{di}{dt} \neq \infty)$$

* Current can't change abruptly.

* Does NOT dissipate energy.

Short Circuit in DC

eg. Calc. $\frac{1}{2}$ through 1mH inductor
if $i(t) = 20\cos(100t)\text{mA}$.

$$E = \frac{1}{2} L i(t)^2 = \frac{1}{2} \times 10^{-3} \times [20\cos(100t) \times 10^{-3}]^2$$

$$= 200 \cos^2(100t) \times 10^{-9}$$

$$= 0.2 \cos^2(100t) \mu\text{J}.$$

$$V = L \frac{di}{dt} = 10^{-3} (20\cos(100t) \times 10^{-3})$$

$$= -2\sin(100t)\text{mV}.$$


eg. V across 2H inductor is $v(t) = 10(1-t)\text{V}$
Determ. i through inductor.
at $t=4$ if $i(0) = 2\text{A}$.

$$i(t) = \frac{1}{L} \int_0^t 10(1-t) dt + i(0).$$

$$= 5 \int_0^t (1-t) dt + i(0).$$

$$= 5 \left[t - \frac{1}{2}t^2 \right]_0^t + 2.$$
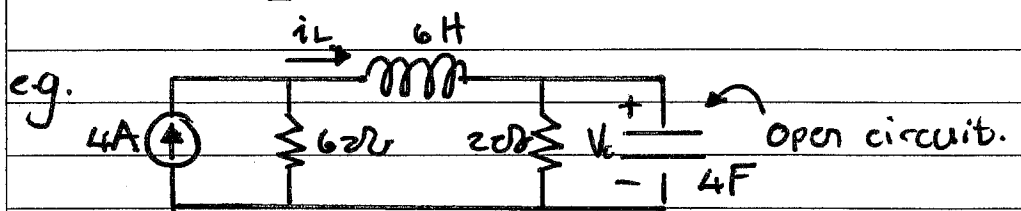
$$i(4) = 5 \left[4 - \frac{1}{2}(16) \right] + 2 = -18\text{A}.$$



$$i_L = 4 \times \frac{6}{6+2} = 3\text{A}$$


$$V_c = 3 \times 2 = 6\text{V}$$

$$E_c = \frac{1}{2} C V_c^2 = \frac{1}{2} \times 4 \times 6^2 = 72\text{J}.$$

$$E_L = \frac{1}{2} L i$$

Series & Parallel inductors:

Series.

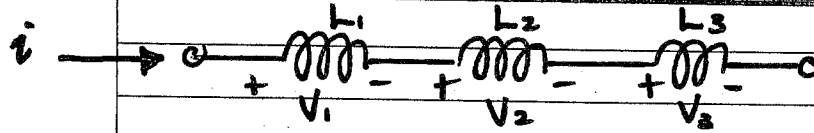


$$V = V_1 + V_2 + \dots + V_N$$

* Add same as resistance.

$$L_{eq} = L_1 + L_2 + \dots + L_N$$

Parallel.

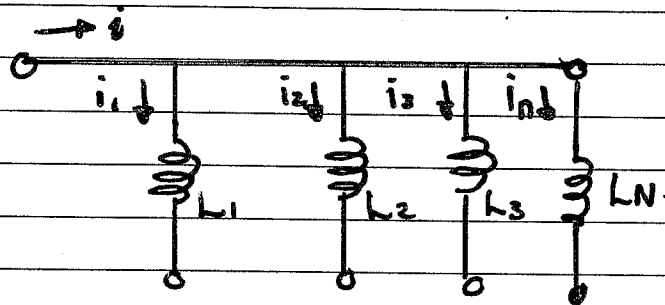

$$\frac{1}{L_{eq}} = \frac{1}{L_1} + \frac{1}{L_2} + \dots + \frac{1}{L_N}$$

$$i = \frac{1}{L} \int_{-\infty}^t v(t) dt + i(t_0)$$

Resistance.

(Ω) Ohms.

Inductance

(H) Henries.

Capacitance

(F) Farads.


Current, Voltage Relationship:


Element	Inductance	Capacitance.
V	$V = L \frac{di}{dt}$	$v(t) = \frac{1}{C} \int_0^t i(t) dt + v(t_0)$
i	$i = \frac{1}{L} \int_0^t v(t) dt + i(t_0)$	$i(t) = C \frac{dv}{dt}$
P	$P = L i \left(\frac{di}{dt} \right)$	$P = C v \left(\frac{dv}{dt} \right)$
W	$W = \frac{1}{2} L i^2$	$W = \frac{1}{2} C v^2 = \frac{q^2}{2C}$

Series

Parallel.

Chapter 6:

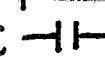
Variable	Resistor (R — )	Capacitor (C — )	Inductor. (L — )
V_{across}	$V = i \times R$	$V = \frac{1}{C} \int i \, dt$	$V = L \times \frac{di}{dt}$
i	$i = \frac{V}{R}$	$i = C \frac{dV}{dt}$	$i = \frac{1}{L} \int V \, dt$
P (power)	$P = i^2 R$ $= i \cdot V$	0	0
W (energy)	0	$E = \frac{1}{2} C V^2$	$E = \frac{1}{2} L i^2$
Series eq.	$R_T = R_1 + R_2 + \dots$	$\frac{1}{C_T} = \frac{1}{C_1} + \frac{1}{C_2} + \dots$	$L_T = L_1 + L_2 + \dots$
Parallel eq.	$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \dots$	$C_T = C_1 + C_2 + \dots$	$\frac{1}{L_T} = \frac{1}{L_1} + \frac{1}{L_2} + \dots$

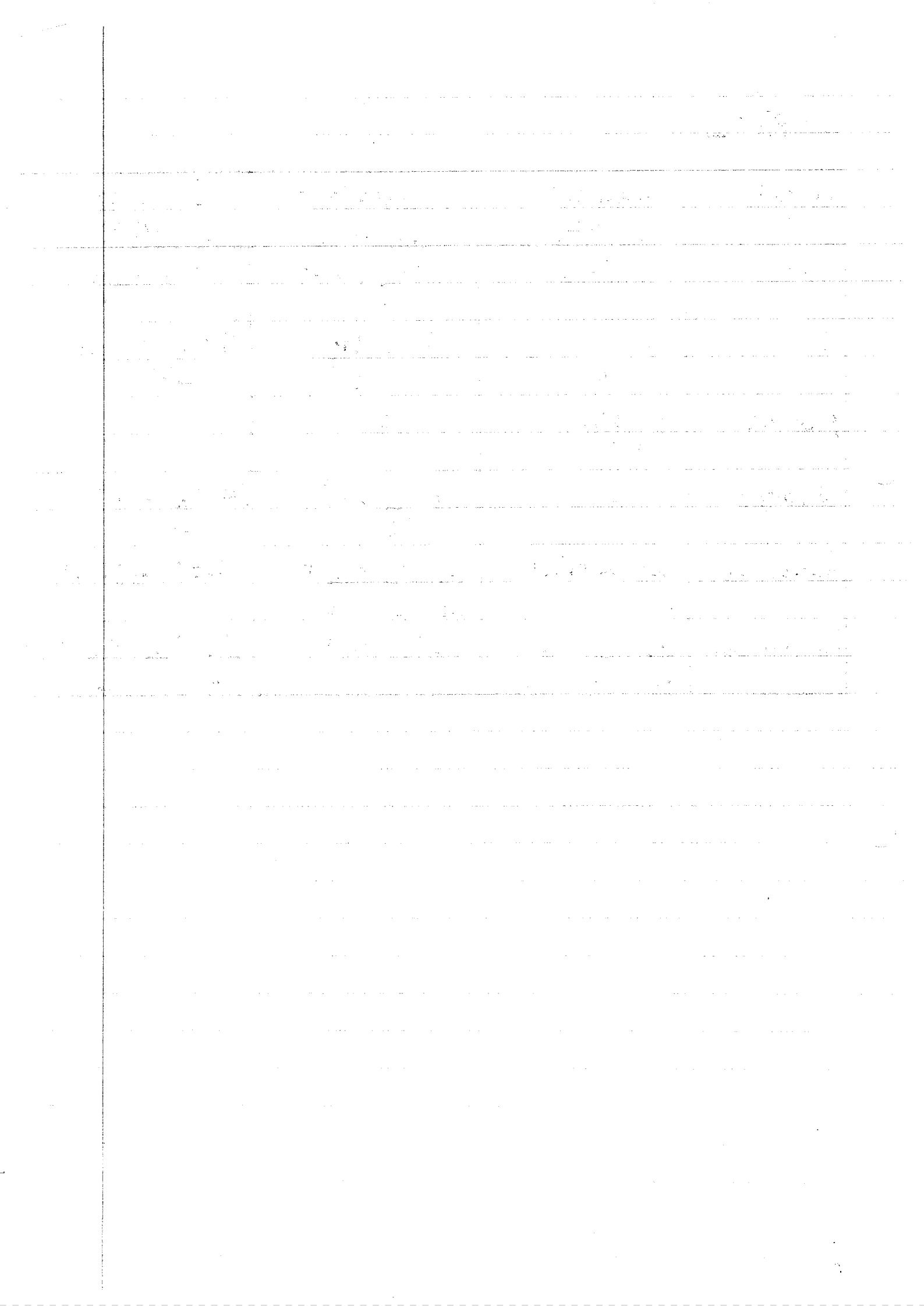

EBN 122. Sinusoidal Steady-State Analy. 27-09-2017.

Chapter 9: Sinusoids:

AC - alternating current.

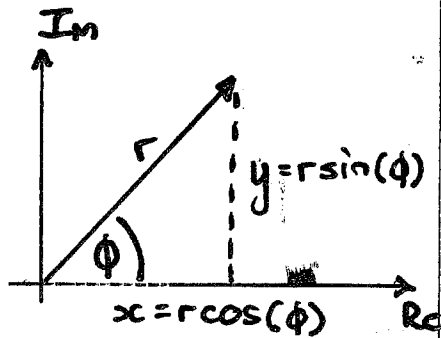


$$\phi = \text{phase} \\ = \tan^{-1}\left(\frac{y}{x}\right)$$

eg. $z = 2 + j6$
 $r = 6.32$
 $\phi = 71.57$

$$z_1 = 6.32 \angle 71.56^\circ \\ = 6.32 e^{j71.56^\circ}$$

eg. $V = 3.32 \angle 32^\circ$
 $x = 3.32 \cos(32)$
 $y = 3.32 \sin(32)$ *
 $V = 2.82 + j1.76$ *

* Signal with sin or cos function.

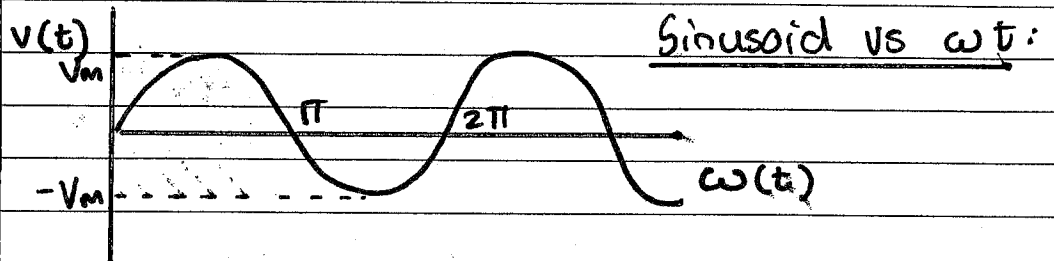

$$v(t) = V_m \sin(\omega t + \phi)$$


ω = angular frequency (rad/s)

V_m = amplitude of sinusoid

t = time in seconds (s)

ωt = argument of a sinusoid (rad)

ϕ = phase of sinusoid, rad or degrees

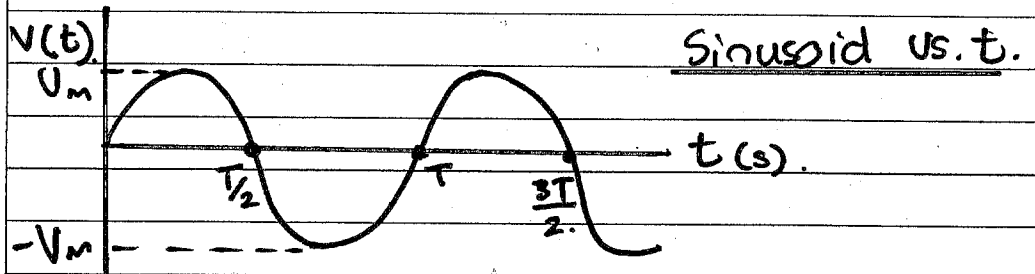

T = Period


$$\text{At } t = T : \omega t = 2\pi \quad \omega T = 2\pi \\ \Rightarrow T = \frac{2\pi}{\omega} \text{ [s]}$$

$$f = \frac{1}{T} = \frac{\omega}{2\pi} \text{ [Hz]}$$

$$\omega = 2\pi f \text{ [rad/s]}$$

How sinusoids came about:
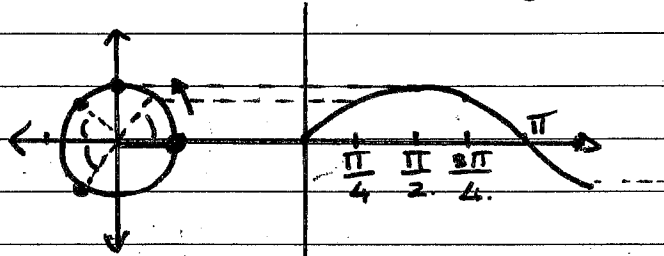
$$e^{j\omega t} \begin{matrix} \nearrow \text{rad} \\ \searrow \text{deg.} \end{matrix} = \cos \omega t + j \sin \omega t.$$



rotation about a
point in a circle.

$$\text{deg} \rightarrow \text{rad} \quad \varphi = \frac{\theta^\circ}{180} \times \pi$$

$$\text{rad} \rightarrow \text{deg}$$

Note: Let z_1 & z_2 = complex nrs.

① $a + jb$
↳ rectangular form.

$\left. \begin{matrix} z_1 + z_2 \\ z_1 - z_2 \end{matrix} \right\}$ use rectangular format.

② $r \angle \phi$
↳ phasor form
↳ polar form.



$\left. \begin{matrix} z_1 \times z_2 \\ \frac{z_1}{z_2} \end{matrix} \right\}$ use polar format.

z^* = conjugate.

$$\begin{aligned} & * (r \angle \phi)^n \\ & = r^n \angle (\phi \times n) \end{aligned}$$

③ $e^{j\phi}$
↳ exponential
form.
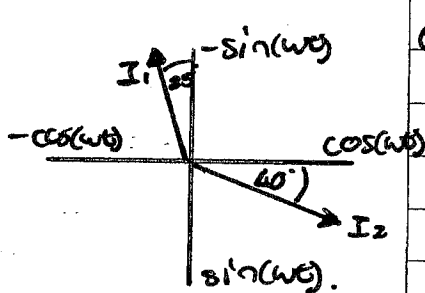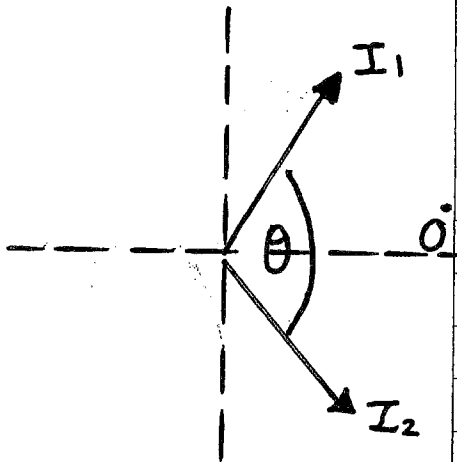
$$\text{Note: } a \angle \phi = a e^{j\phi}$$



① Transform to $\cos(\omega t + \theta)$.

② Rotate i_1, i_2 to bottom Quads.

$$(115 + 40) = 155$$

③ Rotate counter clockwise, the one passes 0° first leads.

Sinusoid: Lead & Lag

- Convert to $\cos$ & $< 180^\circ$
- Positive if $\curvearrowright$
- Which passes 0° first?
- Both vectors start @ bottom 2 quads.

e.g. $i_1 = -4 \sin(377t + 25^\circ)$
 $i_2 = 5 \cos(377t - 40^\circ)$

$$i_1 = -4 \cos(377t + 115^\circ)$$

$$i_2 = 5 \cos(377t - 40^\circ)$$

(Rotate clockwise 120°)

$$i_1 = -4 \cos(377t - 5^\circ)$$

$$i_2 = 5 \cos(377t - 160^\circ)$$

i_1 leads i_2 by 155°

$$\Delta\phi = \phi_1 - \phi_2$$

$$\Delta\phi > 0 \quad i_1 \text{ leads } i_2.$$

$$\Delta\phi < 0 \quad i_2 \text{ leads } i_1.$$

Note: All sinusoids MUST be represented as $f(t) = A_m \cos(\omega t \pm \phi)$


Phasor:

Analyse Sinusoid as Cosine.

$$\text{deg} \rightarrow \text{rad}: \frac{\theta \pi}{180}$$

$$\text{rad} \rightarrow \text{deg}: \frac{\phi 180}{\pi}$$

Phasor & circuit Elements:

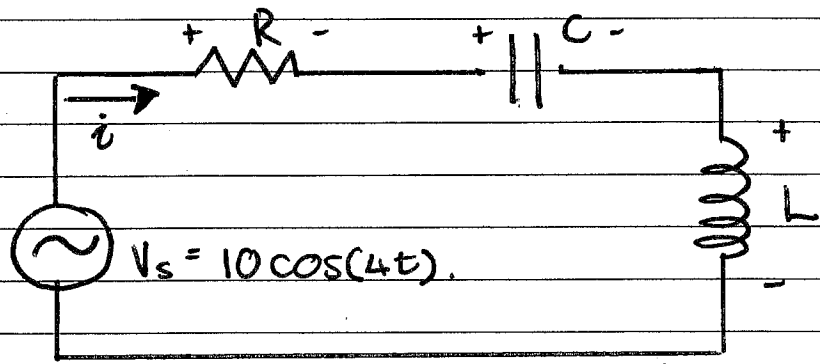

Phasor: $\rightarrow$ complex number.
 $\rightarrow$ represents amplitude & phase of a sinusoid (Cosine).

AC signal & phasor:

$$\text{Euler's identity } e^{j\phi} = \cos\phi + j\sin\phi$$

Understand Cosine function:

$$V(t) = V_m \cos(\omega t + \phi)$$

$$e^{j\omega t} = \cos\omega t + j\sin\omega t$$

$$e^{j(\omega t + \phi)} = \cos(\omega t + \phi) + j\sin(\omega t + \phi)$$

$$\Rightarrow V(t) = V_m \cos(\omega t + \phi) = \text{Re}(V_m e^{j(\omega t + \phi)})$$

$$= \text{Re}(V_m e^{j\phi}) \cdot e^{j\omega t}$$

$$= \text{Re}(\bar{V} \cdot e^{j\omega t})$$

$\bar{V}$ is the phasor.
 $e^{j\omega t}$ is the rotating vector.

$$\bar{V} = V_m \cdot e^{j\phi} = V_m \angle \phi = x + jy$$

Trig identities: (Sinusoid Transform)

$$\sin(a+b) = \sin a \cos b + \cos a \sin b.$$

$$\cos(a+b) = \cos a \cos b - \sin a \sin b.$$

$$\text{e.g. } \sin(\omega t + 180^\circ) = \sin(\omega t) \cos(180^\circ) + \cos(\omega t) \sin(180^\circ) \\ = -\sin(\omega t)$$

$$\cos(\omega t + 180^\circ) = \cos(\omega t) \cos(180^\circ) - \sin(\omega t) \sin(180^\circ) \\ = -\cos(\omega t)$$


$$* \sin(\omega t) = \cos(\omega t - 90^\circ)$$

$$\sin(\omega t + 90^\circ) = \sin(\omega t) \cos(90^\circ) + \cos(\omega t) \sin(90^\circ) \\ = \cos(\omega t)$$

$$\cos(\omega t + 90^\circ) = -\sin(\omega t).$$


Sinusoid Transform (graphical)
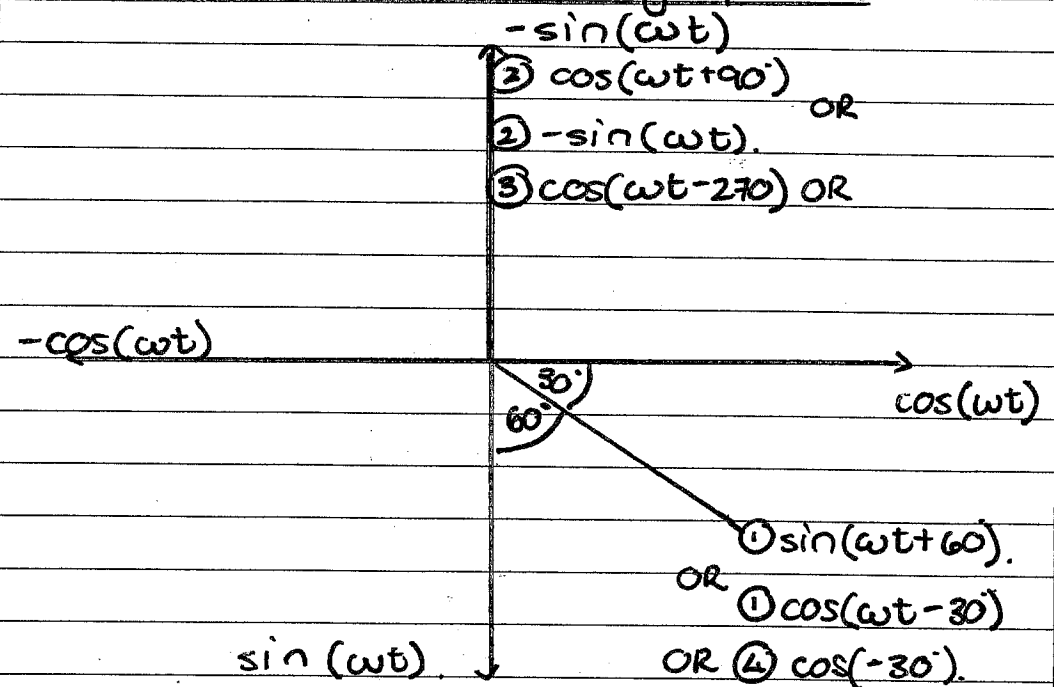
$$-\cos(\omega t + 150^\circ) \\ = -\cos(\omega t + 180^\circ - 30^\circ)$$




$$\begin{array}{ll} \text{(1) } \sin(\omega t + 60^\circ) & \text{(3) } \cos(\omega t - 270^\circ) \\ \text{(2) } \cos(\omega t + 90^\circ) & \text{(4) } -\cos(\omega t + 150^\circ) \end{array}$$

Phase angle:

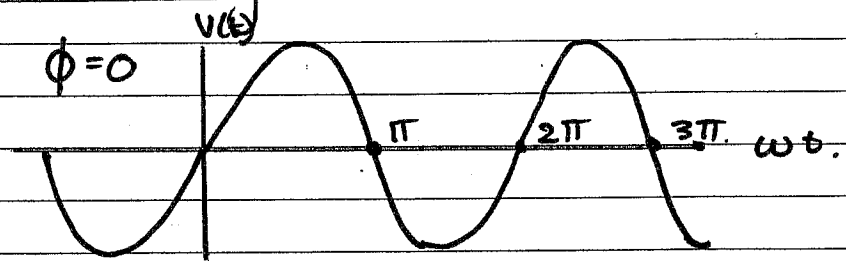


$$V(t) = V_m \sin(\omega t + \phi)$$

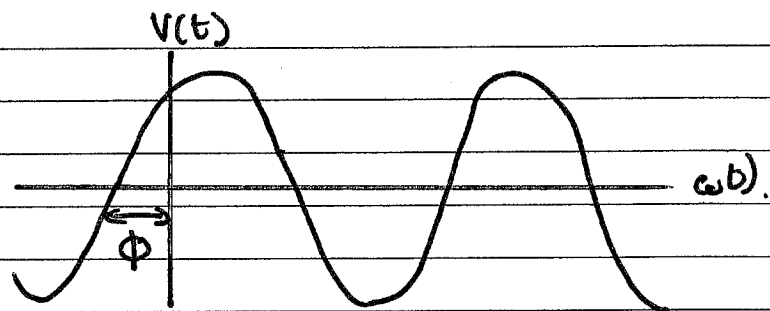When $V(t)=0$ $\omega t + \phi = 0$
 $\omega t = 0 \Rightarrow t = 0.$



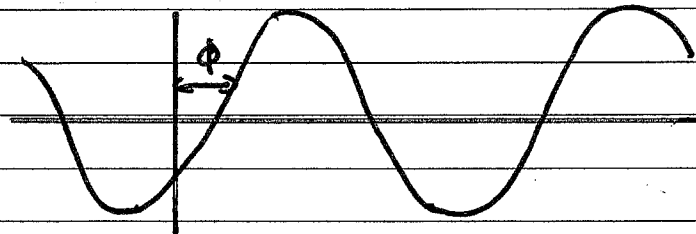$\omega t + \phi = 0$ $\omega t = -\phi < 0$
 $t < 0.$



$\omega t + \phi = 0.$ $\omega t =$

e.g. $\sin(\omega t + \pi/3) \leftarrow$
 $\sin(\omega t - \pi/3) \rightarrow$

Note:

$$j = \sqrt{-1}$$

$$= \cos(\omega t + 90^\circ)$$

$$= 1 \angle 90^\circ$$

Phasor Transformation:

$$v(t) = V_m \cos(\omega t + \phi) \leftrightarrow \bar{V} = V_m \angle \phi$$

(time domain) (phasor domain)


- ① V_m : positive.
- ② V_m : must be cosine function.
- ③ $-180^\circ \leq \phi \leq 180^\circ$

Time Domain Represent: Phasor Domain rep.

$$\begin{aligned} V &= V_m \cos(\omega t + \phi) & \leftrightarrow & V_m \angle \phi \\ V &= V_m \sin(\omega t + \phi) & \leftrightarrow & V_m \angle \phi - 90^\circ \\ i &= I_m \cos(\omega t + \phi) & \leftrightarrow & I_m \angle \phi \\ i &= I_m \sin(\omega t + \phi) & \leftrightarrow & I_m \angle \phi - 90^\circ \end{aligned}$$

e.g. express as a phasor & get sum.
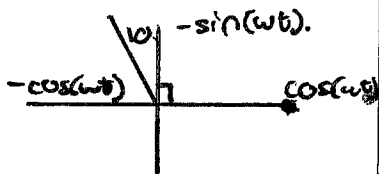
$$i_2 = -4 \cos(10t + 10^\circ) \text{ A.}$$



$$i_2 = 4 \cos(10t + 100^\circ) \text{ A.}$$

$$\begin{aligned} i_1 &= 7 \cos(10t + 40^\circ) \text{ A.} \\ i_2 &= -4 \cos(10t + 10^\circ) \text{ A} \end{aligned}$$

$$\begin{aligned} \bar{I}_1 &= 7 \angle 40^\circ \text{ A.} \\ \bar{I}_2 &= 4 \angle 100^\circ \text{ A} \end{aligned}$$

$$\begin{aligned} \bar{I}_1 + \bar{I}_2 &= 7 \angle 40^\circ + 4 \angle 100^\circ \\ &= \sqrt{93} \angle 61^\circ \text{ A} \\ &= 4.67 + j 8.44 \end{aligned}$$

Time Domain

$$\begin{aligned} * \int v dt & \leftrightarrow \frac{\bar{V}}{j\omega} \\ * \frac{dv}{dt} & \leftrightarrow j\omega \bar{V} \end{aligned}$$

Phasor Domain.

[illegible]

Euler's identity:

$$* A e^{j\phi} = A [\cos \phi + j \sin \phi]$$

AC signal as a Phasor:

$$\begin{aligned} * v(t) &= V_m \cos(\omega t + \phi) \\ &= \operatorname{Re} \{ V_m e^{j(\omega t + \phi)} \} \\ &= \operatorname{Re} \{ V_m e^{j\omega t} \cdot e^{j\phi} \} \end{aligned}$$

$$\text{Let } V_m e^{j\phi} = V$$

$$\Rightarrow v(t) = \operatorname{Re} \{ V e^{j\omega t} \}$$

$$\Rightarrow V = \bar{V} = V_m e^{j\phi} = V_m \angle \phi$$

Transformation:

$$\begin{array}{ccc} v(t) = V_m \cos(\omega t + \phi) & \leftrightarrow & \bar{V} = V_m \angle \phi \\ \text{(time domain)} & & \text{(phasor domain)} \end{array}$$

Revision:

$$e^{j\phi} = \bar{V}$$

$$e^{j(\omega t + \phi)} = e^{j\phi} \cdot e^{j\omega t}$$

$$\omega = 2\pi f$$

$$V(t) = V_m \cos(\omega t + \phi)$$

$$= \text{Re} [V_m \cdot e^{j(\omega t + \phi)}]$$

$$= \text{Re} [V_m \cdot \underbrace{e^{j\phi}}_{\text{rotating vector } (\bar{V})} \cdot e^{j\omega t}]$$

$$* \frac{d(V(t))}{dt} = \text{Re} [j\omega \bar{V} e^{j\omega t}]$$

$$\hookrightarrow \frac{d(\bar{V})}{dt} \longrightarrow j\omega \bar{V}$$

$$* \int V(t) dt = \text{Re} \left[\int \bar{V} e^{j\omega t} dt \right]$$

$$= \text{Re} \left[\frac{\bar{V}}{j\omega} e^{j\omega t} \right]$$

$$\hookrightarrow \int \bar{V} dt \longrightarrow \frac{\bar{V}}{j\omega}$$

Impedance: (Z) [Ω]

* ratio between $\nearrow$ phasor voltage.
 $\searrow$ phasor current.

$\bar{V}$ = phasor voltage.

$\bar{I}$ = phasor current.


$$Z = \frac{\bar{V}}{\bar{I}} = R + jX$$

$\downarrow$ Resistance. $\nwarrow$ Reactance.

Admittance (Y):


$$Y = \frac{1}{Z} = G + jB$$

Circuit Elements: (Impedance) [Z]

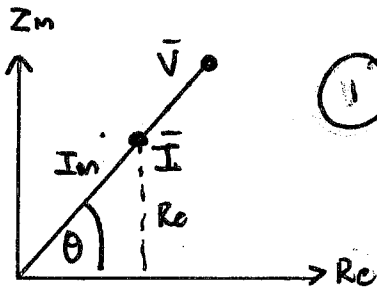

"In phase"
= same ϕ angle.

①

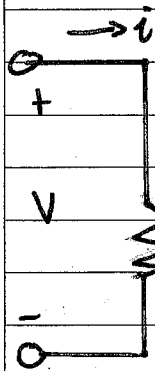

$$i(t) = I_m \cos(\omega t + \phi)$$


$$* \bar{I} = I_m \angle \phi$$

$$v(t) = R \cdot I_m \cos(\omega t + \phi)$$

$$* \bar{V} = I_m R \angle \phi$$

$$* Z_R = \frac{\bar{V}}{\bar{I}} = R \angle 0^\circ \text{ } \} \text{ in phase.}$$

②

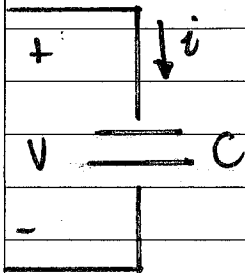

$$v(t) = V_m \cos(\omega t + \phi)$$

$$\bar{V} = V_m \angle \phi$$

$$i(t) = C \left(\frac{dv}{dt} \right)$$

$$= C \times V_m [-\sin(\omega t + \phi)] \cdot \omega$$


$$= -\omega (V_m \sin(\omega t + \phi)) \times C$$

$$i(t) = \omega C V_m \cos(\omega t + \phi + 90^\circ)$$

$$\bar{I} = \omega (V_m \angle (\phi + 90^\circ))$$

$$= j\omega (V_m \angle \phi)$$
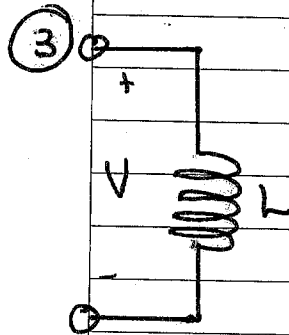
$$* Z_C = \frac{\bar{V}}{\bar{I}} = \frac{1}{j\omega C}$$



$$i(t) = I_m \cos(\omega t + \phi)$$

$$\bar{I} = I_m \angle \phi$$


$$\bar{V}(t) = L \frac{di(t)}{dt}$$

$$= \omega L I_m \angle \phi + 90^\circ$$

$$\bar{V} = j\omega L I_m \angle \phi$$

$$* Z_L = \frac{\bar{V}}{\bar{I}} = j\omega L$$

Inductor:

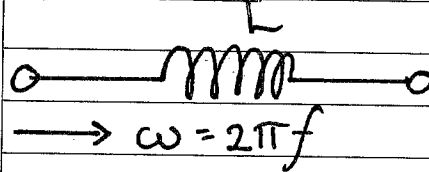


$$Z_L = j\omega L \quad (\Omega)$$

(Becomes short circuit in DC)

(Becomes open circuit in AC).

Capacitor:

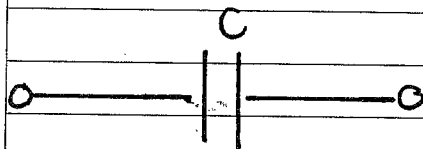


$$Z_C = \frac{1}{j\omega C} = -j \frac{1}{\omega C} \quad (\Omega)$$

(Becomes open circuit in DC)

(Becomes short circuit in AC)


eg. $V = 10 \cos(100t + 30^\circ)$

$$\bar{V} = 10 \angle 30^\circ$$

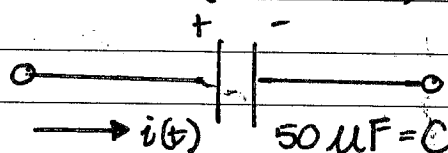

$$Z_C = \frac{1}{j(100)(50 \times 10^{-6})}$$

$$\bar{I}_C = \frac{\bar{V}}{Z_C}$$

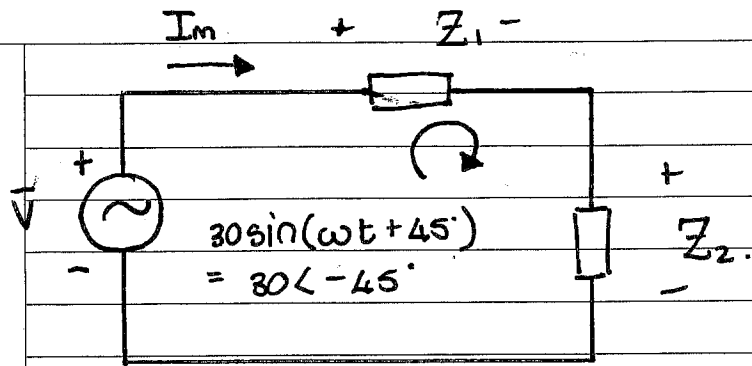


$$Z_T = Z_1 + Z_2$$


Apply KVL: $-\vec{V} + \vec{V}_{Z_1} + \vec{V}_{Z_2} = 0$

Ohm's Law: $\vec{V}_{Z_1} = \vec{I} \times Z_1$

Voltage Division: $\vec{V}_{Z_1} = \vec{V} \times \frac{Z_1}{Z_1 + Z_2}$

Summary of Voltage-Current relat.:

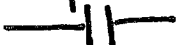Element	Time Domain	Freq. Domain	Impedance	Admittance
Resistor (R) 	$v(t) = R i(t)$	$V = R \cdot I$	$Z = R$	$Y = \frac{1}{R}$
Inductor (L) 	$v(t) = L \frac{di}{dt}$	$V = j\omega L \cdot I$	$Z_L = j\omega L$	$Y_L = \frac{1}{j\omega L}$
Capacitor (C) 	$i(t) = C \frac{dv}{dt}$	$V = \frac{I}{j\omega C}$	$Z_C = \frac{1}{j\omega C}$	$Y_C = j\omega C$

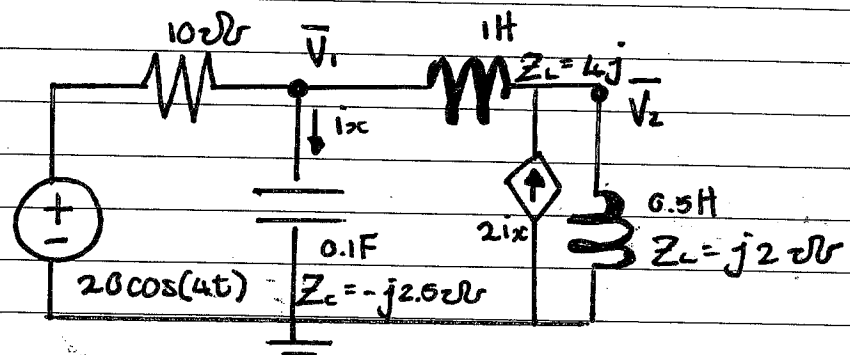

Step 1: $V(t) = 20 \cos 4t$

① $V = 20 \angle 0^\circ$

② $Z_r = 10 \Omega$

③ (11) $Z_c = \frac{1}{j\omega C} = -j \frac{1}{(4)(0.1)} = -j2.5 \Omega$

④ (11) $Z_{L1} = j\omega L = j4 \Omega$

⑤ (11) $Z_{L0.5} = j\omega L = j2 \Omega$

Step 2:

Note: source transform would yield 1 equation for nodal.

Use Nodal Analysis: (KCL)

$$\bar{V}_1: \frac{\bar{V}_1 - 20 \angle 0^\circ}{10 \Omega} + \frac{\bar{V}_1}{-j2.5} + \frac{\bar{V}_1 - \bar{V}_2}{j4} = 0 \quad (1)$$

$$\bar{V}_2: \frac{\bar{V}_2 - \bar{V}_1}{j4} + \frac{\bar{V}_2}{j2} - \frac{2 \cdot \bar{V}_1}{-j2.5} = 0 \quad (2)$$

① $(-3 + j2)\bar{V}_1 + 5\bar{V}_2 = j40$

② $11\bar{V}_1 + 15\bar{V}_2 = 0$

$$\begin{bmatrix} -3 + j2 & -5 \\ 11 & 15 \end{bmatrix} \begin{bmatrix} \bar{V}_1 \\ \bar{V}_2 \end{bmatrix} = \begin{bmatrix} j40 \\ 0 \end{bmatrix} \text{ - cramer's rule.}$$


$$\bar{V}_1 = 18 + j6.$$

$$\bar{i}_x = -2.4 + 7.2j = 7.6 \angle 108.4^\circ$$

$$i_x(t) = 7.59 \cos(4t + 108.4^\circ)$$

ω - get from source.

$$* i_x = \frac{\bar{V}_1}{-j2.5}.$$

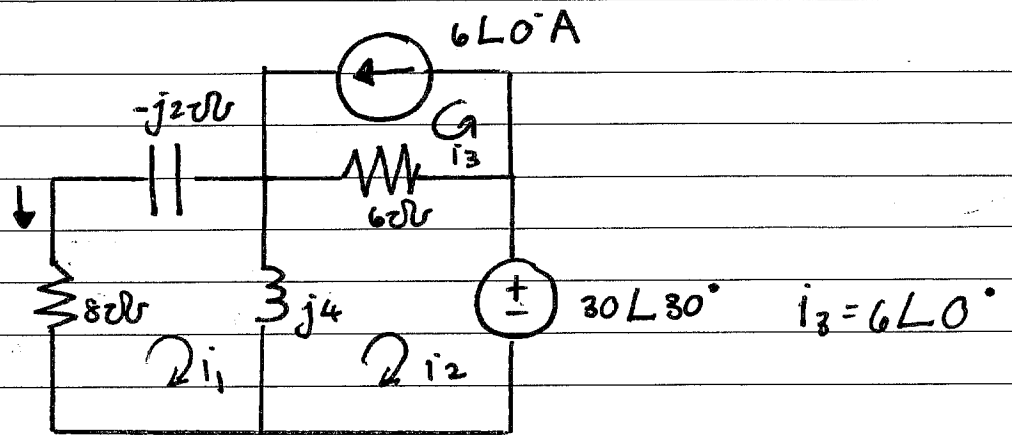

$$\bar{I}_1: 8I_1 + (-j2)I_1 + j4(I_1 - I_2) = 0$$

$$\bar{I}_2: j(4)(I_2 - I_1) + 6(I_2 + 6) + 30\angle 30^\circ = 0.$$

Chapter 10:Sinusoidal Circuit Theorems:Steps of AC circuit:



- 1) Transform to phasor domain.
- 2) Solve
- 3) Transform to time domain.

Nodal Analysis: (solve same as chap 4)

* Note: $\frac{1}{j} = -j$ and $\frac{1}{-j} = j$

Mesh Analysis:

* Take note of the signs...

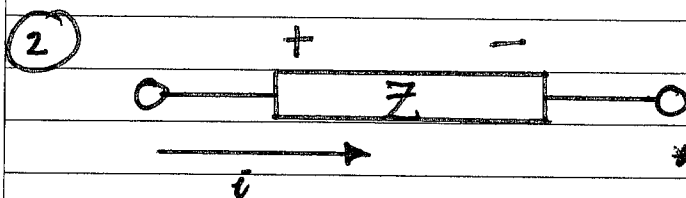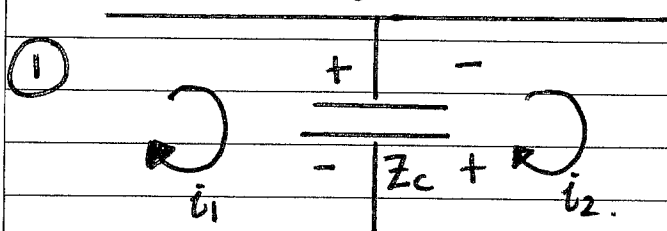

* Always +ve to incoming current ✓


Superposition: (same same)

* $\text{⊖} \rightarrow \text{⊕}$ = open circuit.

* $\text{⊖} \leftarrow \text{⊕}$ = short circuit.

Source Transformation:


Thevenin
Equivalent.

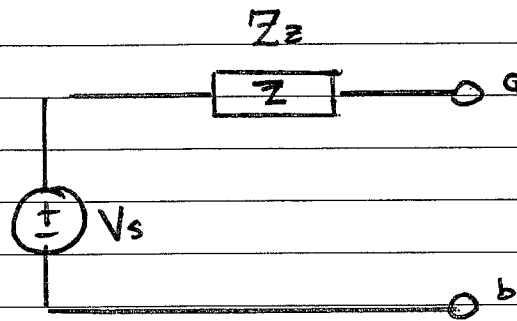

$$V_s = Z_s \times I$$



Norton
Equivalent.

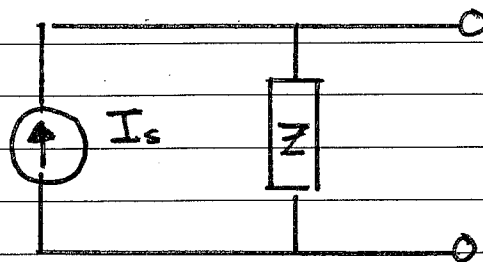

$$I_s = \frac{V_s}{Z_s}$$

Circuits:Steps:

- ① Change Time domain $\longrightarrow$ Phasor domain.
- ② Solve complex equation.
- ③ Change Phasor domain $\longrightarrow$ Time domain.
